
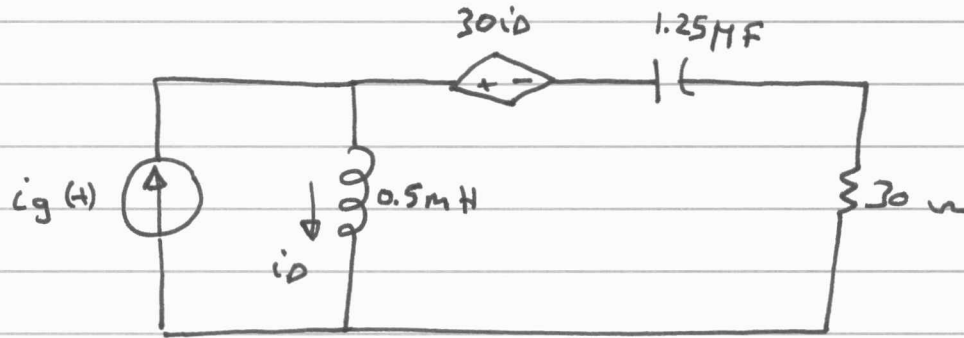


10.6

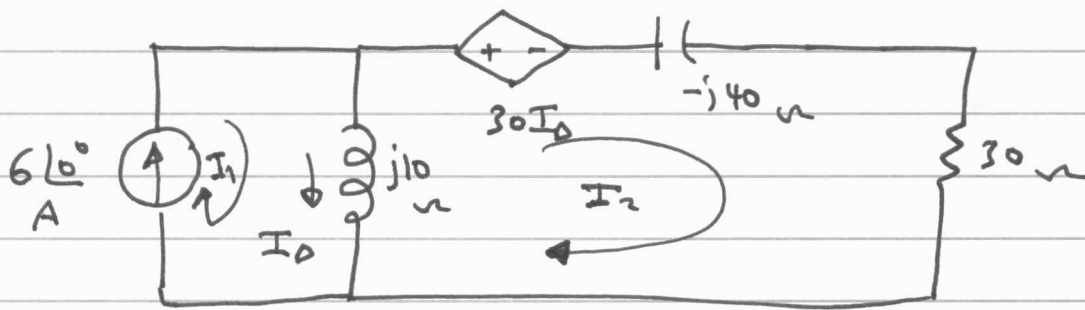

$$i_g(t) = 6 \cos 20,000t \text{ A}$$

$$j\omega L = j10 \Omega \quad ; \quad \frac{1}{j\omega C} = -j \frac{1}{\omega C} = -j40 \Omega$$



$$\vec{I}_1 = 6\angle 0^\circ$$


$$-30\vec{I}_D = -j10\vec{I}_1 + (30 - j30)\vec{I}_2$$

$$\vec{I}_D = \vec{I}_1 - \vec{I}_2$$

$$\therefore \vec{I}_2 = -2 - j6 = 6.32 \angle -108.43^\circ \text{ A}$$

$$P_{30\Omega} = \frac{|\vec{I}_2|^2 \cdot 30}{2} = 600 \text{ watt.}$$


10.25

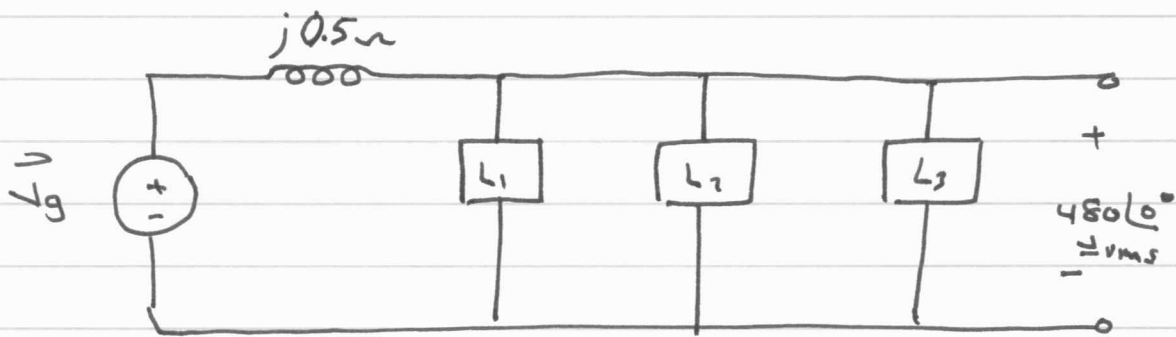

$L_1 : P_{av1} = 7.5 \text{ kW} , Q_1 = 9 \text{ kVAR}$

$L_2 : P_{av2} = 2.1 \text{ kW} , Q_2 = -1.8 \text{ kVAR}$

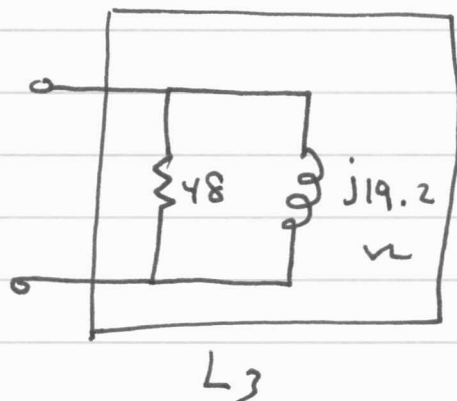L_3 : consist of a 48Ω resistor in parallel with an inductive reactance of 19.2Ω .



$$\vec{S}_1 = 7500 + j9000 = \vec{V}_{rms} \cdot \vec{I}_{rms1}^*$$

$$\therefore \vec{I}_{rms1} = 15.625 - j18.75 \text{ A rms}$$

$$\vec{S}_2 = 2100 - j1800 = \vec{V}_{rms} \cdot \vec{I}_{rms2}^*$$


$$\therefore \vec{I}_{rms2} = 4.375 + j3.75 \text{ A rms}$$

$$\vec{I}_{rms3} = \frac{480 \angle 0^\circ}{48} + \frac{480 \angle 0^\circ}{j19.2} = 10 - j25 \text{ A rms}$$

$$\vec{I}_g = \vec{I}_{rms1} + \vec{I}_{rms2} + \vec{I}_{rms3} = 30 - j40 \text{ A rms}$$

$$\vec{V}_g = 480 \angle 0^\circ + j0.5 \vec{I}_g = 500.22 \angle 1.72^\circ \text{ V rms}$$

10.27

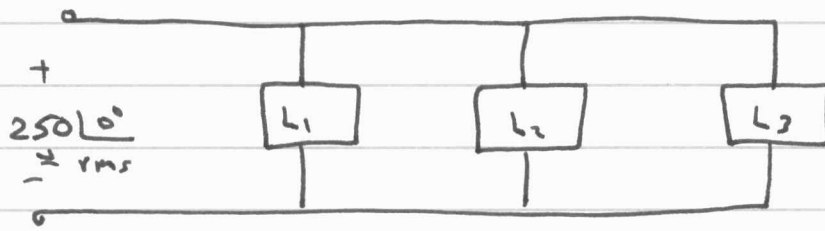

$$L_1: P_{av1} = 16 \text{ kW}; Q_1 = 28 \text{ kVAR}$$

$$L_2: P_{av2} = 10 \text{ kVA, at } 0.6 \text{ pf Lead}$$

$$L_3: P_{av3} = 8 \text{ kW, at unity power factor}$$

$$\vec{S}_1 = 16000 + j 28000 \quad \text{VA}$$

$$P_{av2} = (10)(0.6) = 6 \text{ kW}$$

$$Q_2 = -6 \tan(\cos^{-1} \text{pf}) = -8 \text{ kVAR}$$

$$\therefore \vec{S}_2 = 6 - j 8 \quad \text{kVA}$$

$$\vec{S}_3 = 8000 \quad \text{VA}$$

$$\vec{S}_3 = 8000$$


$$\vec{S}_T = \vec{S}_1 + \vec{S}_2 + \vec{S}_3 = 30000 + j 10000 \quad \text{VA}$$

$$\vec{S}_T = (250 \angle 0^\circ) \vec{I}_s^*$$

$$\therefore \vec{I}_s = 120 - j 40 \quad \text{A rms}$$

$$Z = \frac{V}{I} = \frac{250 \angle 0^\circ}{120 - j 40} = 1.98 \angle 18.43^\circ \quad \Omega$$

10.34

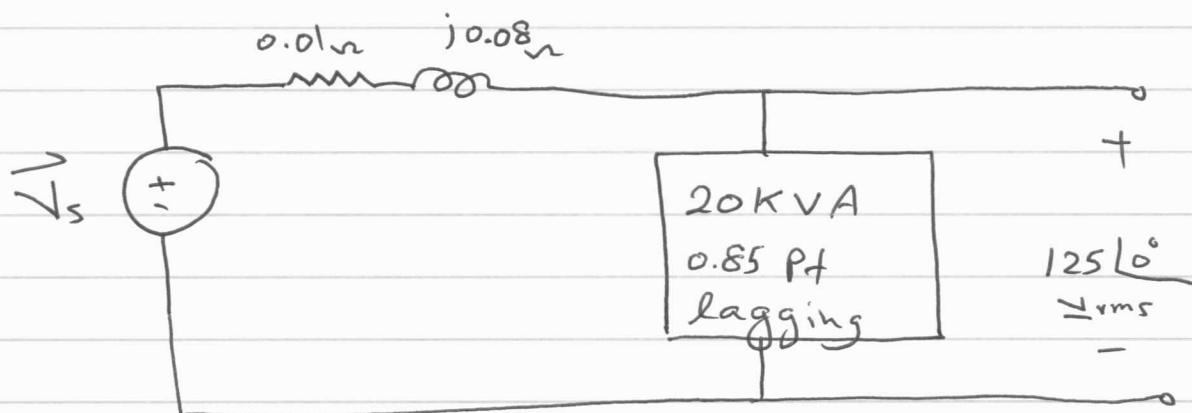

$$P_{av} = (20,000)(0.85) = 17000 \text{ W}$$

$$Q_L = P_{av} \tan(\cos^{-1} Pf) = 10535.65 \text{ VAR}$$

$$\therefore \vec{S}_L = 17000 + j10535.65$$

$$\vec{S}_L = \vec{V}_L \cdot \vec{I}_L^*$$

$$\therefore \vec{I}_L = 138 - j84.29 \text{ A rms}$$

$$\vec{V}_s = (0.01 + j0.08) \vec{I}_L + 125 \angle 0^\circ = 133.48 \angle 4.31^\circ \text{ V rms}$$

$$\therefore |\vec{V}_s| = 133.48 \text{ V rms}$$

b) $P_{\text{loss}} = 0.01 |\vec{I}_L|^2 = 256 \text{ W}$

c) $Q_{Lini} = 103535.65 \text{ VAR}$

$$Q_{LFin} = 0$$

$$\therefore Q_c = -103535.65 \text{ VAR}$$

$$C = -\frac{Q_c}{\omega V^2} = 1788.59 \text{ } \mu\text{F}$$

$$d) \vec{S}_{L_{\text{new}}} = 17000 \angle 0^\circ = \vec{V}_L \cdot \vec{I}_{L_{\text{new}}}^*$$

$$\therefore \vec{I}_{L_{\text{new}}} = 136 \angle 0^\circ \text{ A rms}$$


$$\vec{V}_s = (0.01 + j0.08) \vec{I}_{L_{\text{new}}} + 125 \angle 0^\circ$$

$$\vec{V}_s = 126.83 \angle 4.92^\circ \text{ V rms}$$


$$\therefore |\vec{V}_s| = 126.83 \text{ V rms}$$

$$e) P_{\text{loss}_{\text{new}}} = (0.01) |\vec{I}_{L_{\text{new}}}|^2 = 184.96 \text{ W}$$

10.46

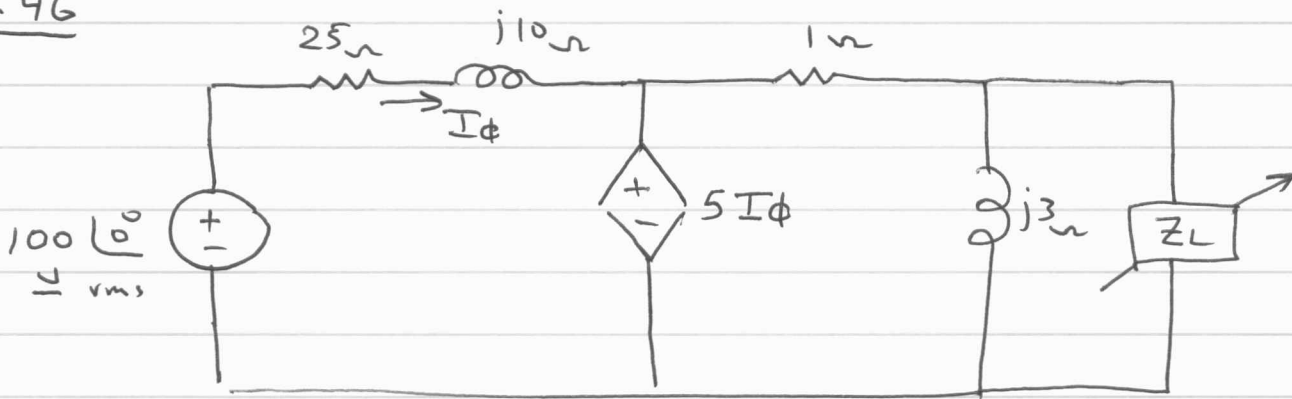

To find \vec{V}_{TH} , and Z_{TH}

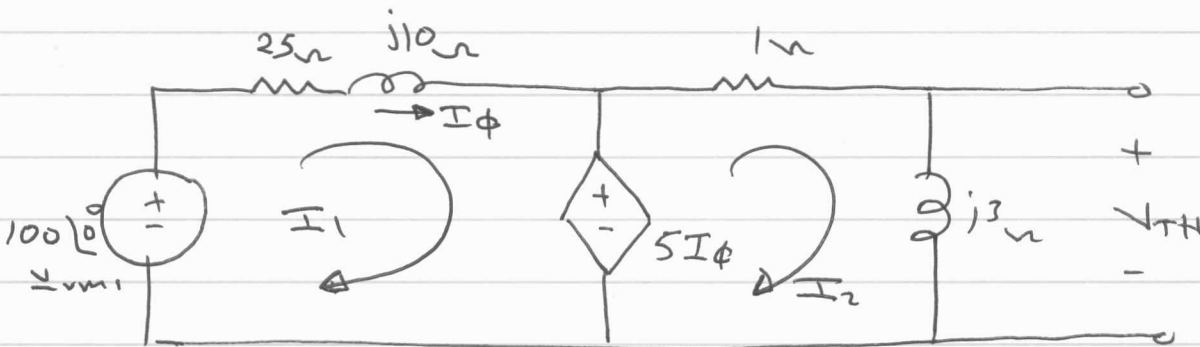

$$100\angle 0^\circ - 5\vec{I}_\phi = (25 + j10)\vec{I}_1$$

$$\vec{I}_\phi = \vec{I}_1$$



$$\therefore \vec{I}_1 = \vec{I}_\phi = 3 - j1 \text{ A rms}$$

$$5\vec{I}_\phi = (1 + j3)\vec{I}_2$$

$$\therefore \vec{I}_2 = \frac{15 - j15}{1 + j3}$$

$$\therefore \vec{V}_{TH} = j3 \vec{I}_2 = 15\angle 0^\circ \text{ V rms}$$
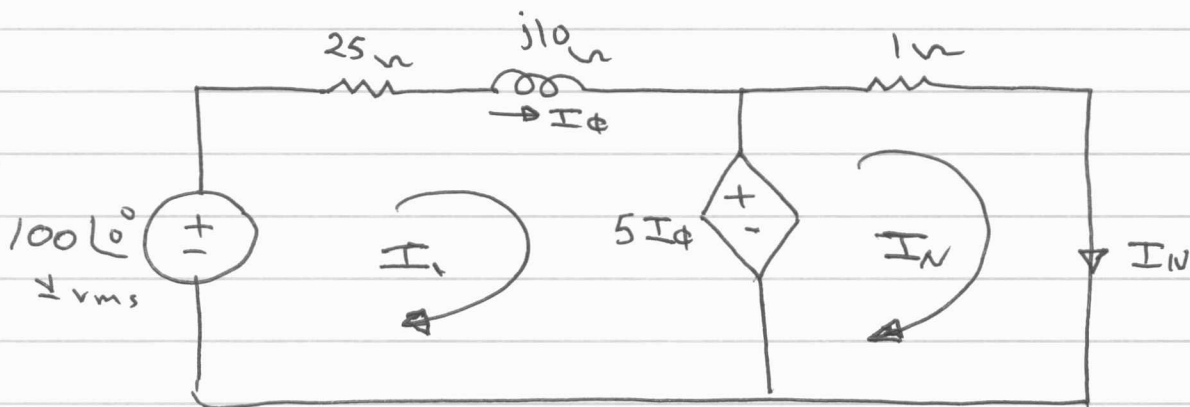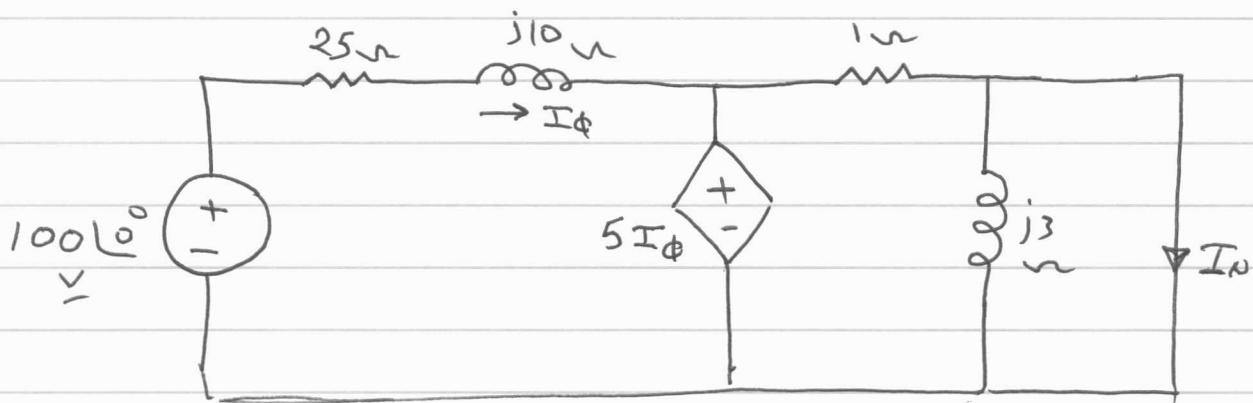
$$\text{To find } Z_{TH} = \frac{\vec{V}_{TH}}{\vec{I}_N}$$



$$100\angle 0^\circ - 5\vec{I}_\phi = (25 + j10)\vec{I}_1$$

$$\vec{I}_\phi = \vec{I}_1$$

$$\therefore \vec{I}_1 = \vec{I}_\phi = 3 - j1 \text{ A rms}$$


$$5\vec{I}_\phi = 1 \cdot \vec{I}_N$$

$$\therefore \vec{I}_N = 15 - j5 \text{ A}$$

$$\therefore Z_{TH} = \frac{V_{TH}}{I_N} = 0.9 + j0.03 \Omega$$

$$\therefore Z_L = Z_{TH}^* = 0.9 - j0.03$$

$$P_{L, \max} = \frac{|\vec{V}_{TH}|^2}{8R_{TH}} = 62.5 \text{ W}$$

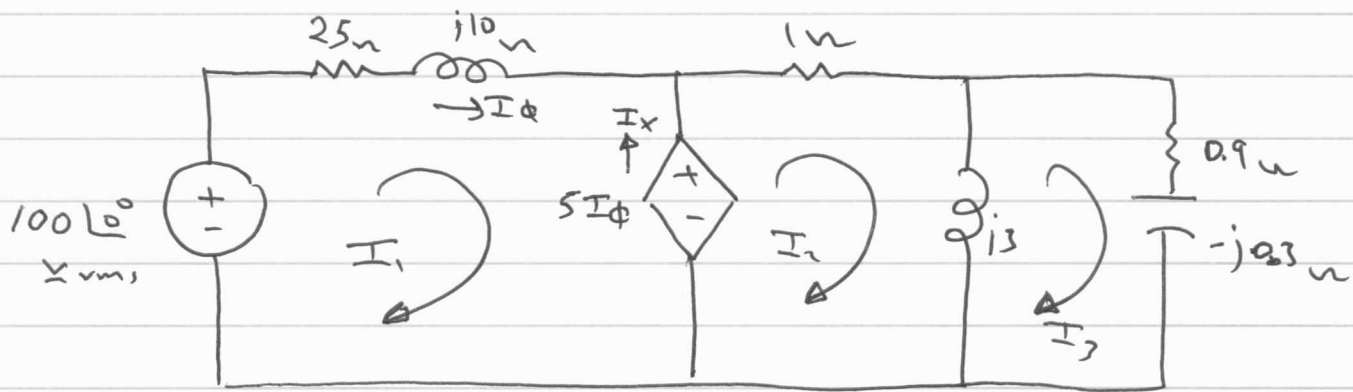

$$100\angle 0^\circ - 5I_\phi = (25 + j10)\vec{I}_1$$

$$\vec{I}_\phi = \vec{I}_1$$

$$\therefore \vec{I}_1 = \vec{I}_\phi = 3 - j1 \quad \text{A rms} = 3.162\angle -18.435^\circ \quad \text{A rms}$$

$$5\vec{I}_\phi = (1 + j3)\vec{I}_2 - j3\vec{I}_3$$

$$0 = -j3\vec{I}_2 + (0.9 + j2.7)\vec{I}_3$$

$$\therefore \vec{I}_2 = 7.5 - j2.5 \quad \text{A rms}$$

$$\vec{I}_x = \vec{I}_2 - \vec{I}_1 = 4.5 - j1.5 \quad \text{A rms}$$

$$\begin{aligned} P_{100\angle 0^\circ} &= (100)(3.162) \cos(0 + 18.435) \\ &= 300 \text{ W supply} \end{aligned}$$

$$\begin{aligned} P_{5I_\phi} &= 15|\vec{I}_\phi| \cdot |\vec{I}_x| \cos 0 \\ &= 75 \text{ W supply} \end{aligned}$$

$$\therefore \text{Total power developed} = 375 \text{ W}$$

$$\% \text{ delivered} = \frac{62.5}{375} \times 100\%$$

$$= 16.67\%$$