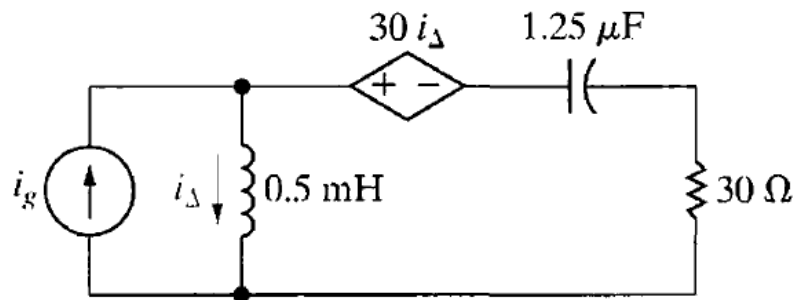


## ENEE2301 CH10 PROBLEMS

- 10.6** Find the average power dissipated in the  $30\ \Omega$  resistor in the circuit seen in Fig. P10.6 if  $i_g = 6 \cos 20,000t$  A.


PSPICE  
MULTISIM

Figure P10.6




**10.25** The three parallel loads in the circuit shown in Fig. P10.25 can be described as follows: Load 1 is absorbing an average power of 7.5 kW and 9 kVAR of magnetizing vars; load 2 is absorbing an average power of 2.1 kW and generating 1.8 kVAR of magnetizing reactive power; load 3 consists of a  $48 \Omega$  resistor in parallel with an inductive reactance of  $19.2 \Omega$ . Find the rms magnitude and the phase angle of  $\mathbf{V}_g$  if  $\mathbf{V}_o = 480 \angle 0^\circ$  V (rms).

**Figure P10.25**

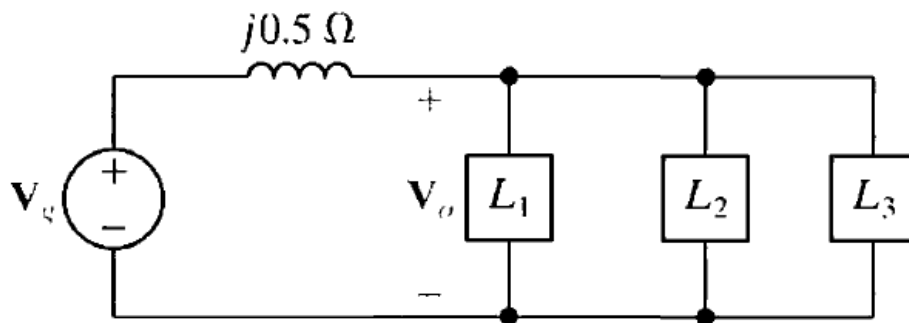

- 10.27** Three loads are connected in parallel across a 250 V (rms) line, as shown in Fig. P10.27. Load 1 absorbs 16 kW and 18 kVAR. Load 2 absorbs 10 kVA at 0.6 pf lead. Load 3 absorbs 8 kW at unity power factor.
- Find the impedance that is equivalent to the three parallel loads.
  - Find the power factor of the equivalent load as seen from the line's input terminals.

**Figure P10.27**

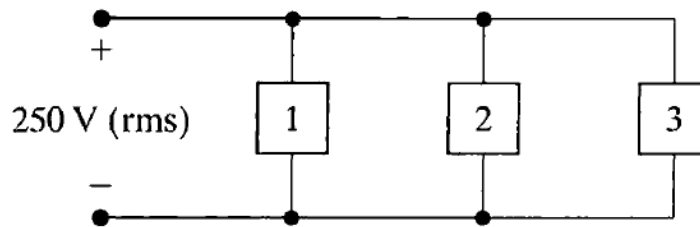

**10.34** A group of small appliances on a 60 Hz system requires 20 kVA at 0.85 pf lagging when operated at 125 V (rms). The impedance of the feeder supplying the appliances is  $0.01 + j0.08 \Omega$ . The voltage at the load end of the feeder is 125 V (rms).

- a) What is the rms magnitude of the voltage at the source end of the feeder?
  - b) What is the average power loss in the feeder?
  - c) What size capacitor (in microfarads) across the load end of the feeder is needed to improve the load power factor to unity?
  - d) After the capacitor is installed, what is the rms magnitude of the voltage at the source end of the feeder if the load voltage is maintained at 125 V (rms)?
- 
- e) What is the average power loss in the feeder for (d)?

**10.46** The load impedance  $Z_L$  for the circuit shown in Fig. P10.46 is adjusted until maximum average power is delivered to  $Z_L$ .

a) Find the maximum average power delivered to  $Z_L$ .

b) What percentage of the total power developed in the circuit is delivered to  $Z_L$ ?

**Figure P10.46**

