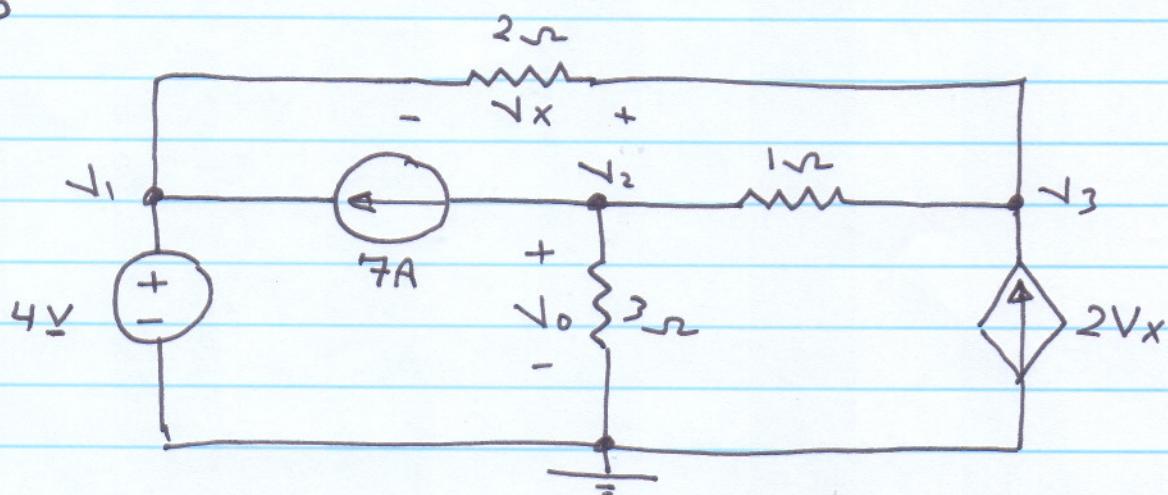


4.25



$$V_1 = 4$$

Constrain equation

$$-7 = \left(1 + \frac{1}{3}\right)V_2 - V_3$$


$$2Vx = -\frac{1}{2}V_1 - V_2 + \left(1 + \frac{1}{2}\right)V_3$$

$$Vx = V_3 - V_1$$

Solving

$$V_0 = V_2 = 1.5 V$$

4.28

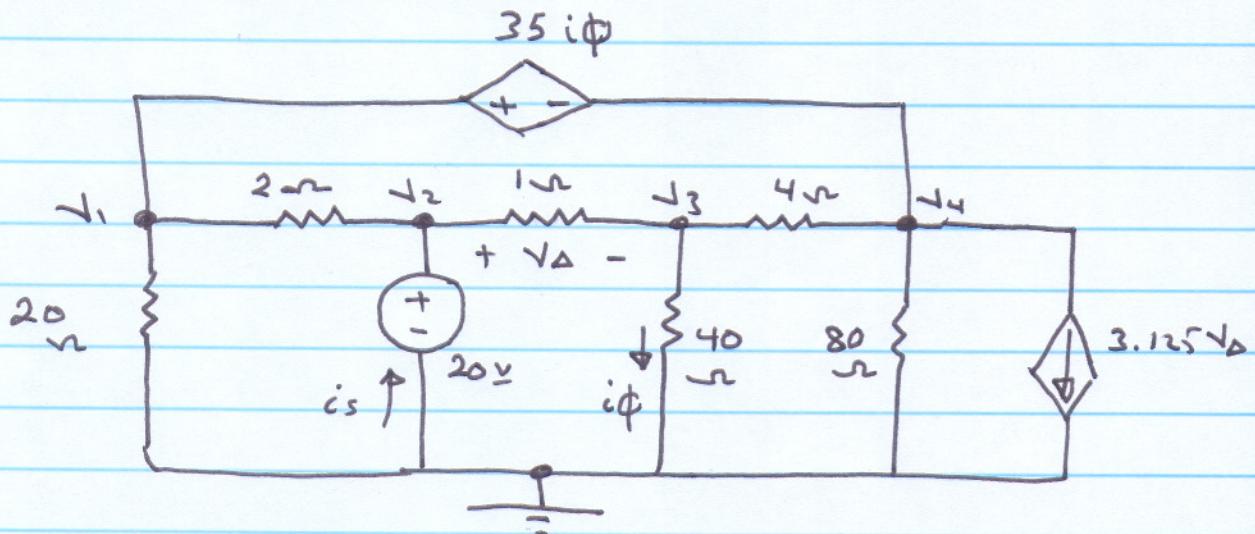

$$V_2 = 20 \text{ constrain equation}$$

$$V_1 - V_4 = 35i\phi \text{ constrain equation}$$

$$i\phi = \frac{V_3}{40}$$

$$0 = -V_2 + \left(1 + \frac{1}{4} + \frac{1}{40}\right)V_3 - \frac{1}{4}V_4$$

$$-3.125V_D = \left(\frac{1}{2} + \frac{1}{20}\right)V_1 - \frac{1}{2}V_2 - \frac{1}{4}V_3 + \left(\frac{1}{4} + \frac{1}{80}\right)V_4$$

$$V_D = V_2 - V_3$$


Solving :

$$V_1 = -20.25V ; V_3 = 10V , \text{ and } V_4 = -29V$$

$$i_s = \frac{V_2 - V_1}{2} + \frac{V_2 - V_3}{1} = 30.125A$$

$$P_{20V} = 20i_s = 602.5 \text{ Watt Supply}$$

4.42

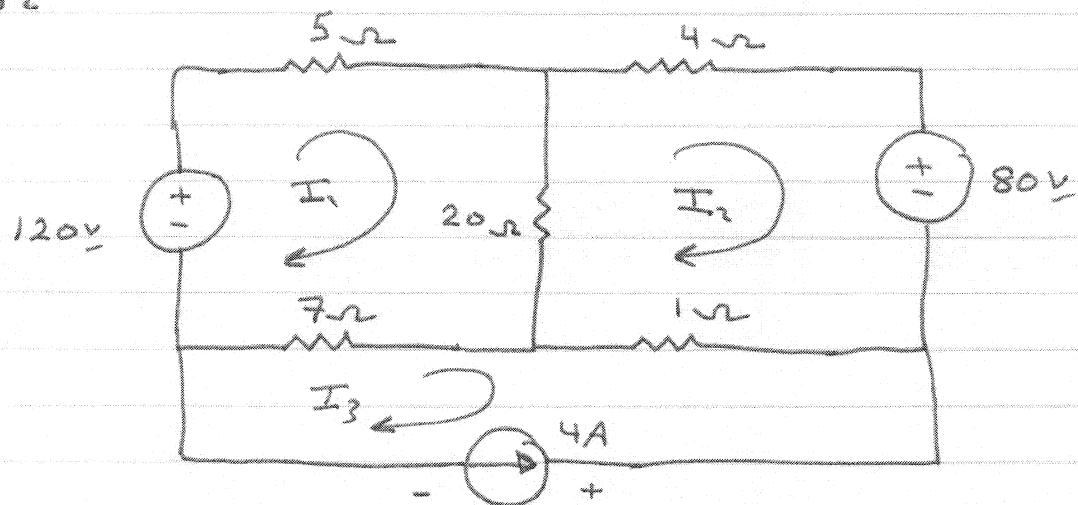

$$I_3 = -4A \quad \text{constraint equation}$$

$$120 = 32 I_1 - 20 I_2 - 7 I_3$$

$$-80 = -20 I_1 + 25 I_2 - I_3$$

Solving:

$$I_1 = 1.55 A, \text{ and } I_2 = -2.12 A$$

$$V_{4A} = 1(I_2 - I_3) + 7(I_1 - I_3) = 40.73 V$$

$$P_{\text{out}} = 162.92 \text{ W (Supply)}$$

$$P_{120V} = (120)(I_1) = 186 \text{ Watt Supply}$$

$$P_{80V} = (80)(I_2) = 169.6 \text{ Watt Supply}$$


$$\sum P_{\text{Supply}} = 518.52 \text{ Watt.}$$

$$\sum P_{\text{resistances}} = 5(1.55)^2 + 4(-2.12)^2 + 20(3.67)^2 + 7(5.55)^2 + 1(1.88)^2$$


$$= 518.52 \text{ Watt (dissipated)}$$

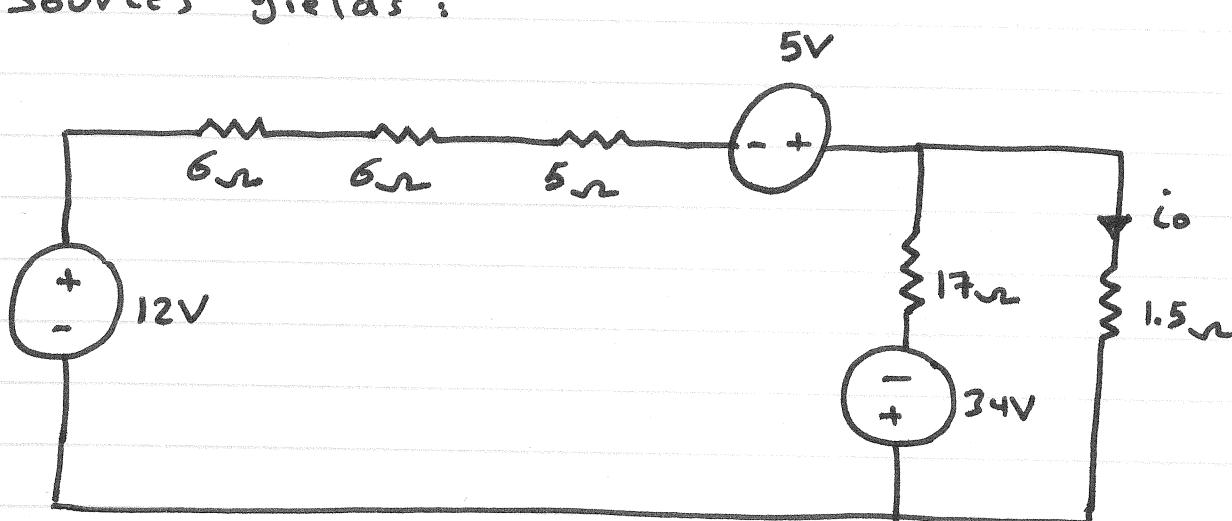4.60


Applying source transformation to both current sources yields :



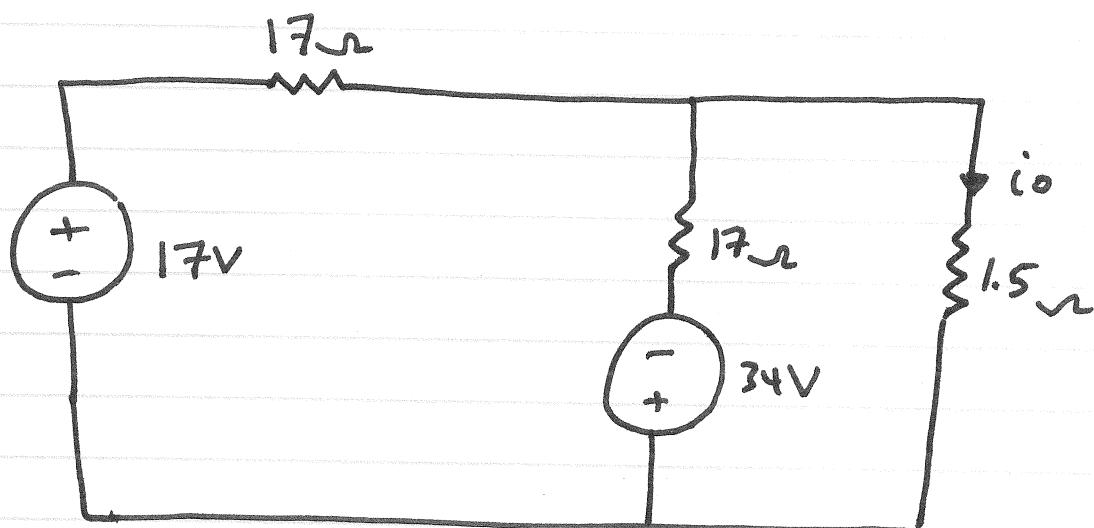
Combining the 12V and 5V into one source and adding the 3 resistors (6Ω , 6Ω , and 5Ω) in series



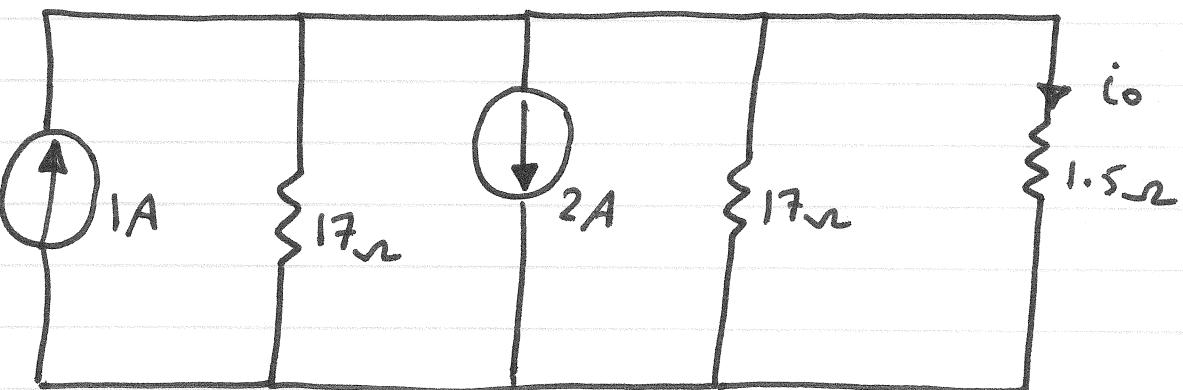Now Source transformation for both voltage sources



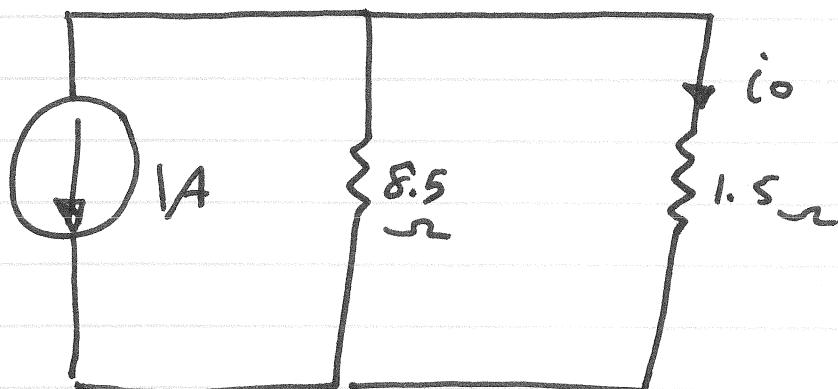
Combining 1A, 2A Sources and the
17 Ω , 17 Ω resistors



$$i_o = -\frac{8.5}{8.5 + 1.5} \cdot 1A$$

$$i_o = -0.85 A$$

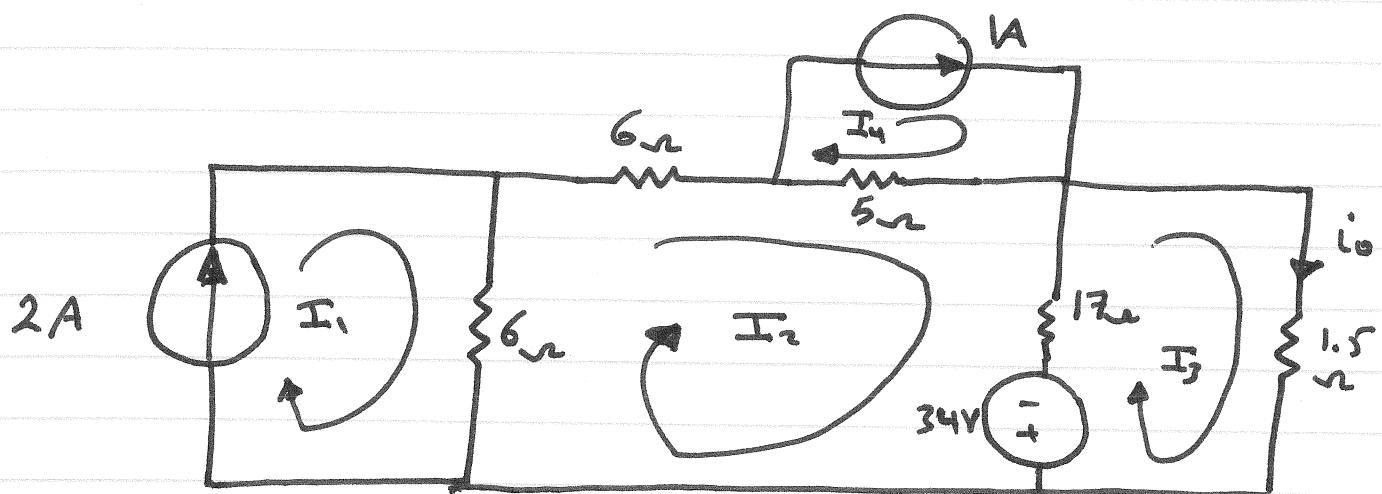b) Verification by mesh - Current method.



$$I_1 = 2A \quad \text{Constrain equation}$$

$$I_4 = 1A \quad \text{Constrain equation}$$

mesh 2 KVL :

$$34 = -6I_1 + 34I_2 - 17I_3 - 5I_4$$

mesh 3 KVL :

$$-34 = -17I_2 + 18.5I_3$$


Solving for I₂ and I₃ yields :

$$I_3 = -0.85A$$

$$I_2 = 1.075A$$

$$\therefore i_0 = I_3 = -0.85A$$

4.66

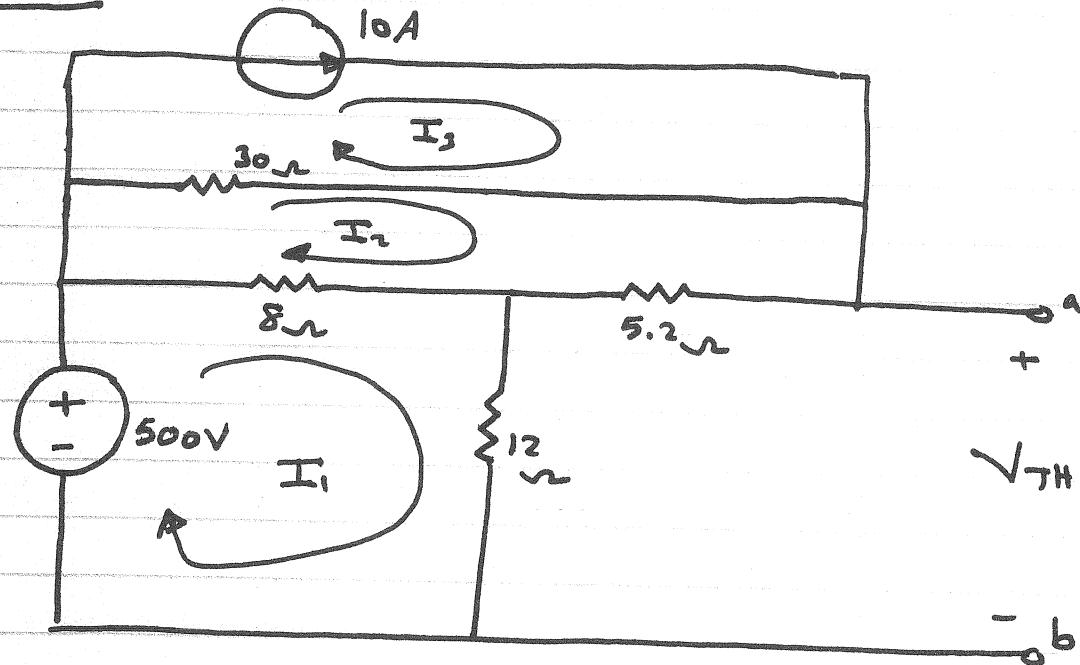

$$\sqrt{TH} = (5.2\Omega) I_2 + (12\Omega) I_1$$

$I_3 = 10A$ Constrain equation

KVL for mesh 1 :

$$500 = 20 I_1 - 8 I_2$$

KVL for mesh 2 :

$$0 = 43.2 I_2 - 30 I_3 - 8 I_1$$


Solving for I_1 and I_2 yields :

$$I_1 = 30A$$

$$I_2 = 12.5A$$


$$\therefore \sqrt{TH} = (5.2)(12.5) + (12)(30) = 425V$$

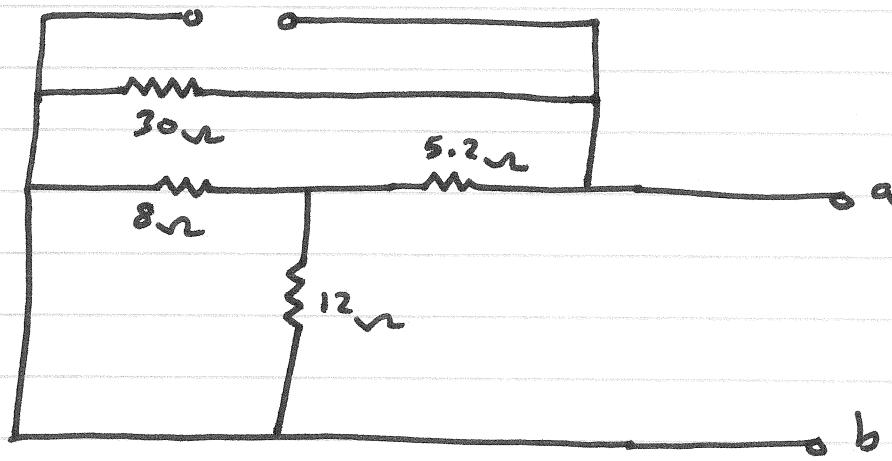To find R_{TH} , set all the independent sources to zero.




$$R_{TH} = 30\Omega \parallel (5.2\Omega + 8\Omega \parallel 12\Omega)$$

$$R_{TH} = 7.5\Omega$$

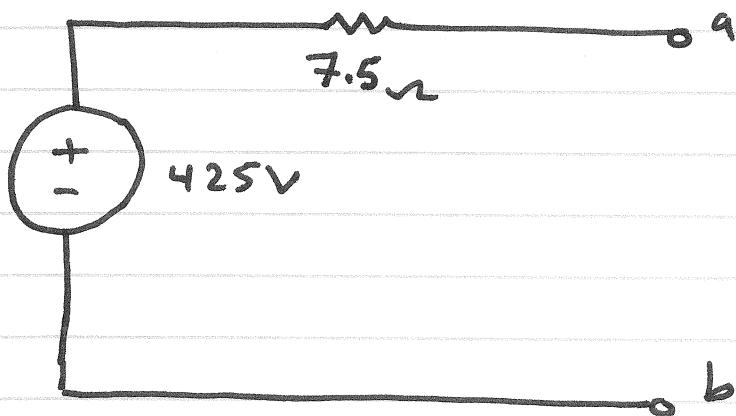

4.73

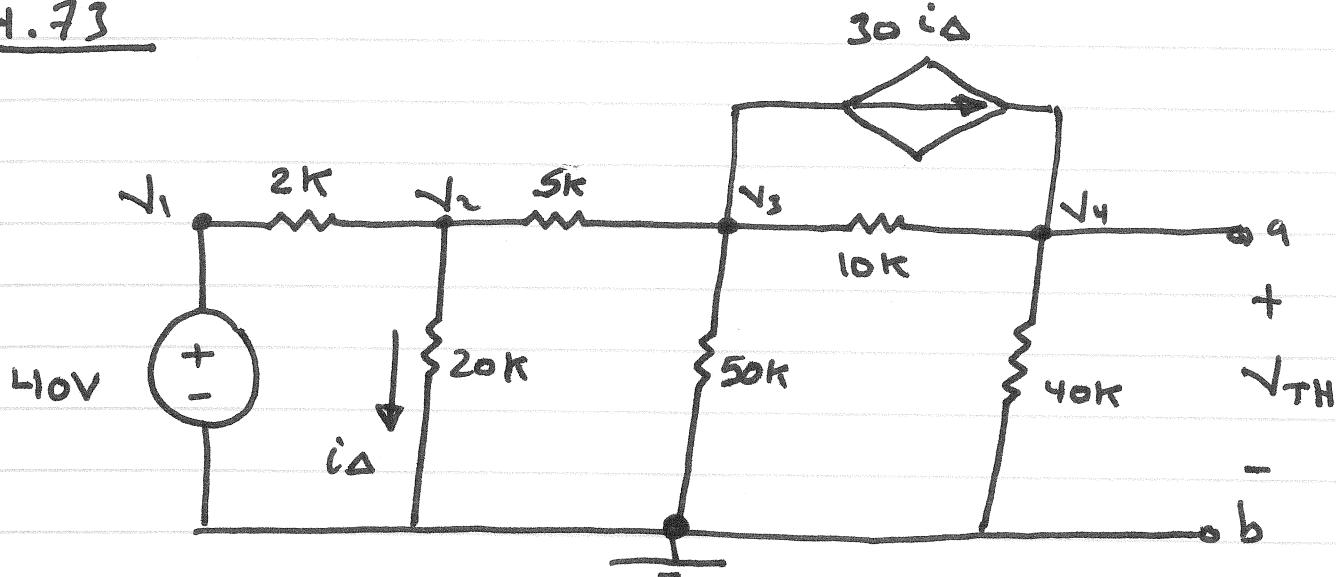

$$V_{TH} = V_4$$

KCL at node 2 :

$$\left(\frac{1}{2k} + \frac{1}{20k} + \frac{1}{5k} \right) V_2 - \frac{1}{2k} V_1 - \frac{1}{5k} V_3 = 0$$

KCL at node 3 ,

$$-30i\Delta = -\frac{1}{5k} V_2 + \left(\frac{1}{5k} + \frac{1}{50k} + \frac{1}{10k} \right) V_3 - \frac{1}{10k} V_4$$

$$i\Delta = \frac{V_2}{20k}$$

KCL at node 4 :


$$30i\Delta = -\frac{1}{10k} V_3 + \left(\frac{1}{10k} + \frac{1}{40k} \right) V_4$$

$$V_1 = 40V \text{ constrain equation}$$

Solving for V_4

$$V_4 = 280V \therefore V_{TH} = 280V$$
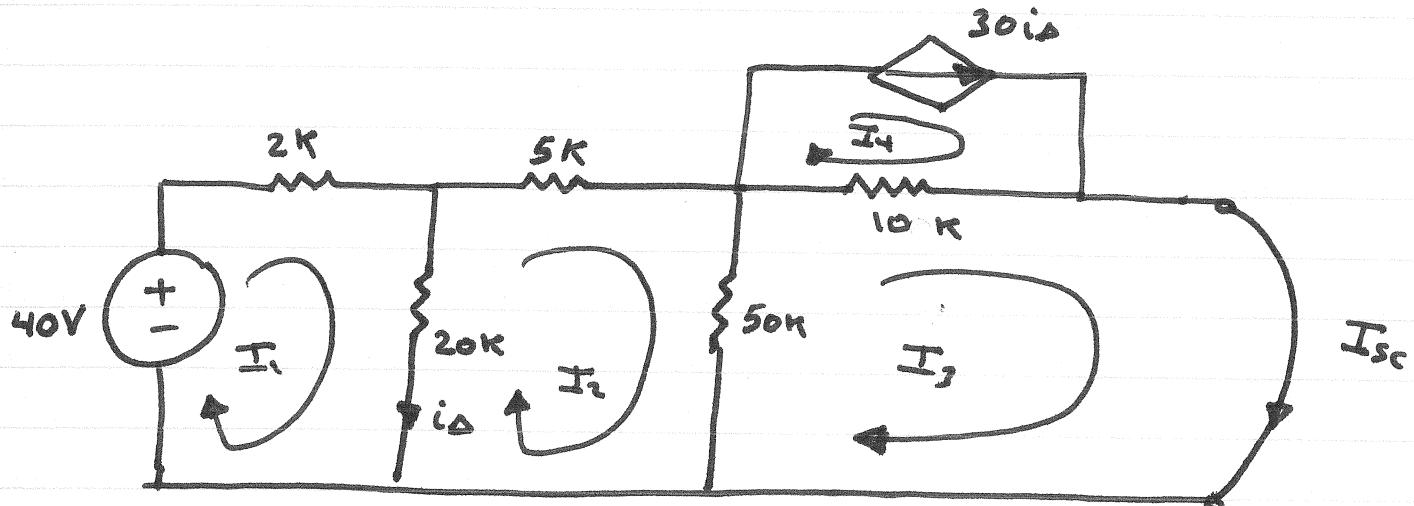
$$\text{To find } R_{TH} = \frac{V_{TH}}{I_N}$$



$$I_{sc} = I_N = I_3$$

KVL for mesh 1 :

$$40 = 22K I_1 - 20K I_2$$

KVL for mesh 2 ,

$$0 = -20K I_1 + 75K I_2 - 50K I_3$$

KVL for mesh 3 :

$$0 = -50K I_2 + 60K I_3 - 10K I_4$$


$$I_4 = 30 i\Delta \quad \text{constraint equation}$$

$$i\Delta = I_1 - I_2$$


$$\text{Solving for } I_3 = I_{sc} = I_N = 14mA$$

$$\therefore R_{TH} = \frac{V_{TH}}{I_N} = 20K\sqrt{2}$$

4.88

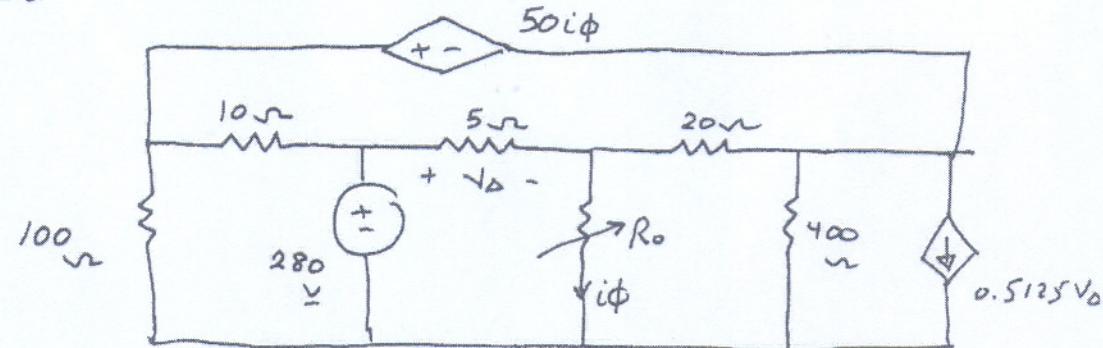

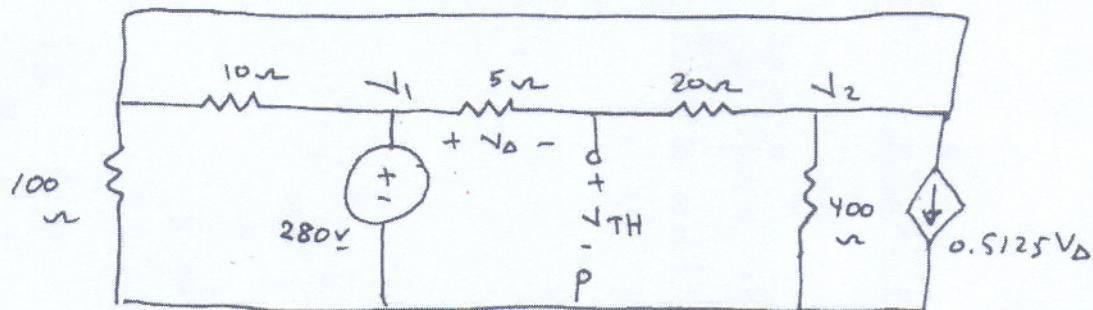i) To find V_{TH} ; $i\phi = 0 \rightarrow 50i\phi = 0 \rightarrow \text{Short Circuit}$



Supernode

$$\text{V}_2 \left(\frac{1}{100} + \frac{1}{10} + \frac{1}{400} + \frac{1}{25} \right) - \left(\frac{1}{10} + \frac{1}{25} \right) \text{V}_1 = -0.5125 \text{V}_\Delta$$


$$\text{V}_1 = 280 \quad \text{Constrain equation}$$

$$\text{V}_\Delta = \frac{5}{5+20} (\text{V}_1 - \text{V}_2)$$

$$\therefore \text{V}_2 = 210 \text{V} ; \quad \text{V}_\Delta = \frac{5}{25} (280 - 210) = 14 \text{V}$$

$$\text{V}_{TH} = -\text{V}_\Delta + 280 = 266 \text{V}$$

2) To find $R_{TH} = \frac{V_{TH}}{I_N}$

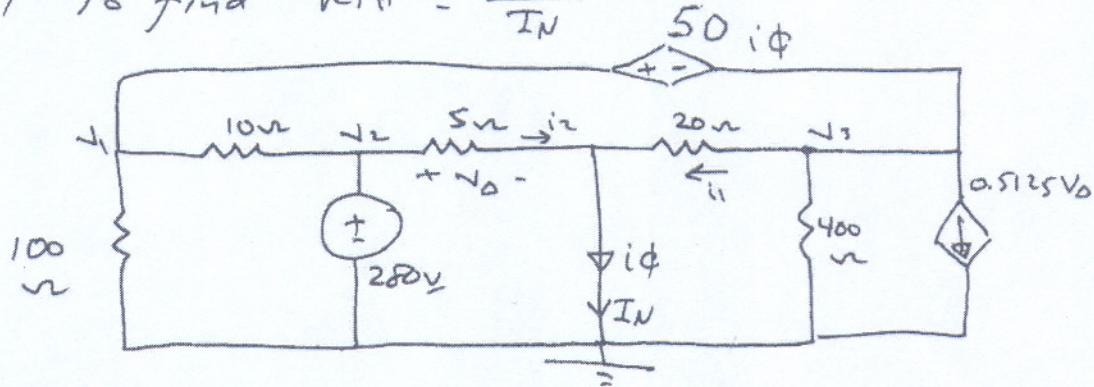

$$V_1 - V_2 = 50i\phi = 50I_N$$

$$V_2 = 280V$$


Supernode equation

$$V_3 \left(\frac{1}{400} + \frac{1}{20} \right) + V_1 \left(\frac{1}{10} + \frac{1}{10} \right) - \frac{1}{5} V_2 = -0.5125V_0$$

$$V_0 = 280V \quad ; \quad V_3 = -968V$$


$$I_N = i_1 + i_2 = \frac{-968}{20} + \frac{280}{5} = 7.6A$$
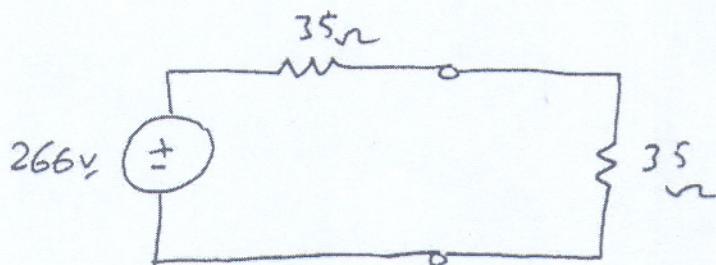
$$\therefore R_{TH} = \frac{266}{7.6} = 35\Omega$$



$$P_{max} = \frac{V_{TH}^2}{4R_{TH}} = 505.4W$$

c)

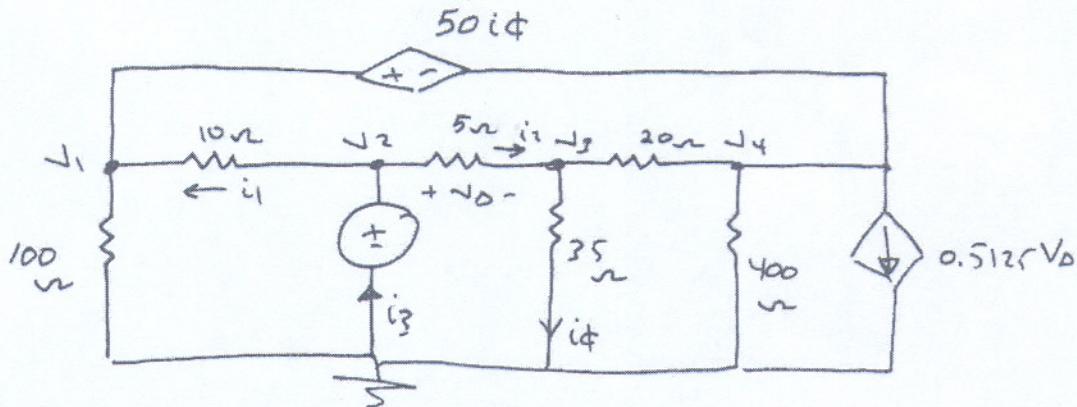

$$v_1 - v_4 = 50i\phi \quad ; \quad i\phi = \frac{v_2}{35}$$

$$v_2 = 280V$$

$$v_3 \left(\frac{1}{5} + \frac{1}{35} + \frac{1}{20} \right) - \frac{1}{5} v_2 - \frac{1}{20} v_4 = 0$$

Supernode

$$v_1 \left(\frac{1}{10} + \frac{1}{100} \right) + v_4 \left(\frac{1}{400} + \frac{1}{20} \right) - \frac{1}{10} v_2 - \frac{1}{20} v_3 = -0.5125 V_D$$

$$v_0 = v_2 - v_3 \quad ; \quad v_3 = 133V$$

$$\therefore v_1 = -189V$$

$$i_1 = \frac{280 + 189}{10} = 46.9A$$


$$i_2 = \frac{280 - 133}{5} = 29.4A$$

$$i_g = i_3 = i_1 + i_2 = 76.3A$$


$$P_{\text{Supply}} = (76.3)(280) = 21364W$$

Supply

4.92

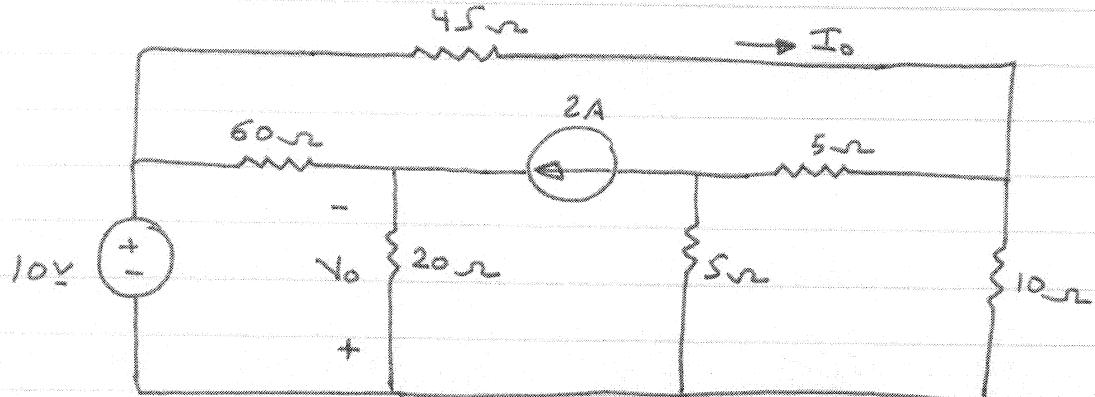


i) let V_s on, I_s off (open circuit)

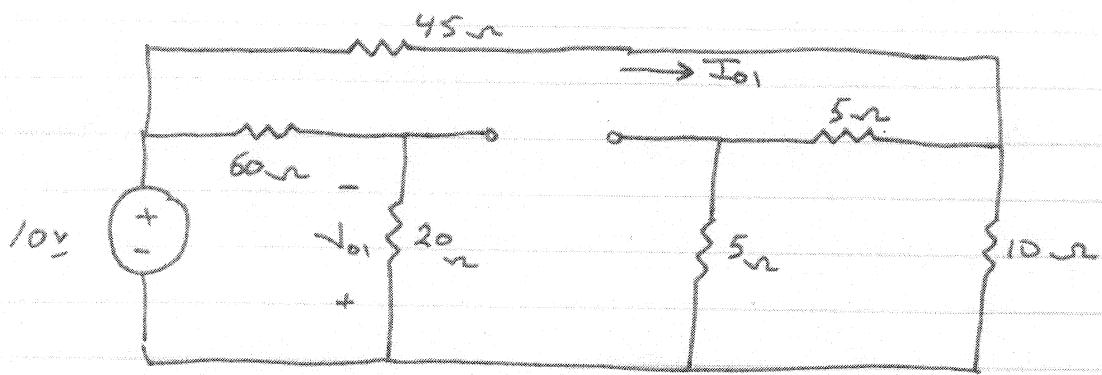

$$I_{o1} = \frac{10}{45 + 10 \parallel (5+5)} = 0.2 \text{ A}$$

$$V_{o1} = \frac{20}{20+60} (-10) = -2.5 \text{ V}$$

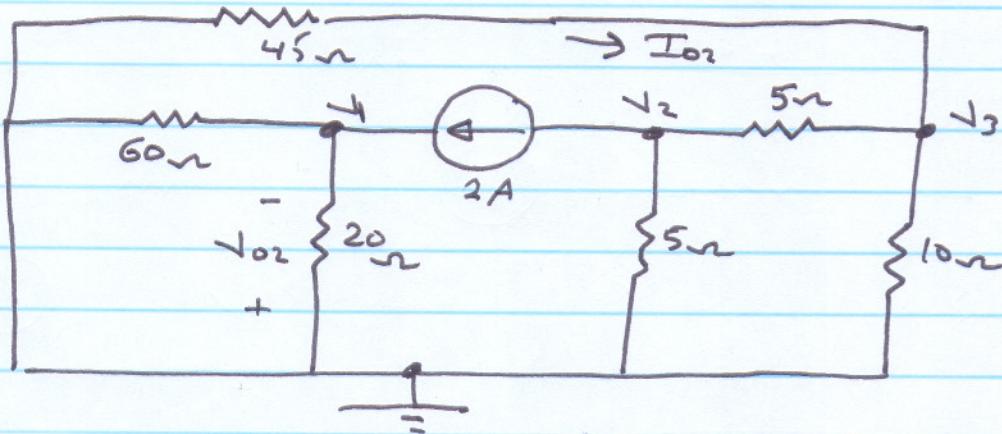2) let I_{01} , \downarrow s off (short circuit)



$$2 = \left(\frac{1}{20} + \frac{1}{60} \right) \downarrow_1 -$$

$$-2 = \left(\frac{1}{5} + \frac{1}{5} \right) \downarrow_2 - \frac{1}{5} \downarrow_3$$

$$0 = -\frac{1}{5} \downarrow_2 + \left(\frac{1}{5} + \frac{1}{10} + \frac{1}{45} \right) \downarrow_3$$

Solving :

$$\downarrow_2 = -7.25, \quad \downarrow_3 = -4.5 \text{ V}, \text{ and } \downarrow_1 = 30 \text{ V}$$

$$\downarrow_{02} = -\downarrow_1 = -30 \text{ V}$$

$$I_{02} = -\frac{\downarrow_3}{45} = 0.1 \text{ A}$$

$$\therefore I_0 = I_{01} + I_{02} = 0.3 \text{ A}$$

$$\downarrow_0 = \downarrow_{01} + \downarrow_{02} = -32.5$$