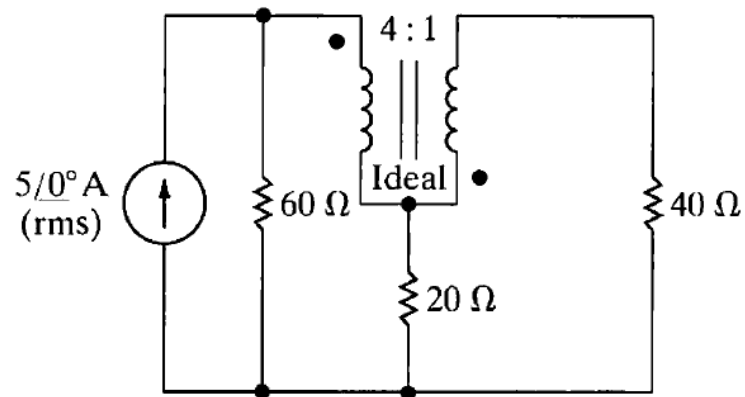


Transformer Problems


- 10.39** a) Find the average power delivered by the sinusoidal current source in the circuit of Fig. P10.39.
b) Find the average power delivered to the $20\ \Omega$ resistor.

Figure P10.39



- 10.44** For the frequency-domain circuit in Fig. P10.44, calculate:
- the rms magnitude of V_o .
 - the average power dissipated in the $70\ \Omega$ resistor.
 - the percentage of the average power generated by the ideal voltage source that is delivered to the $70\ \Omega$ load resistor.

Figure P10.44

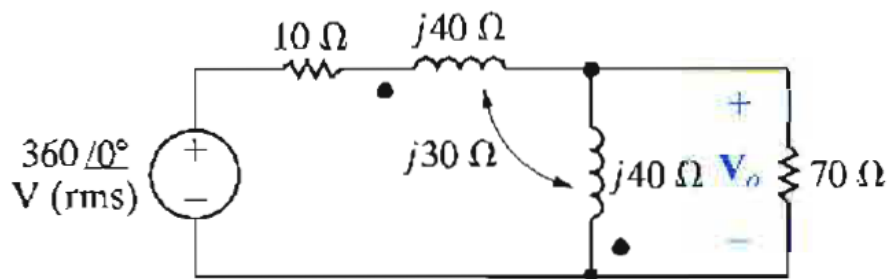


- 10.45** The $70\ \Omega$ resistor in the circuit in Fig. P10.44 is replaced with a variable impedance Z_o . Assume Z_o is adjusted for maximum average power transfer to Z_o .
- What is the maximum average power that can be delivered to Z_o ?
 - What is the average power developed by the ideal voltage source when maximum average power is delivered to Z_o ?

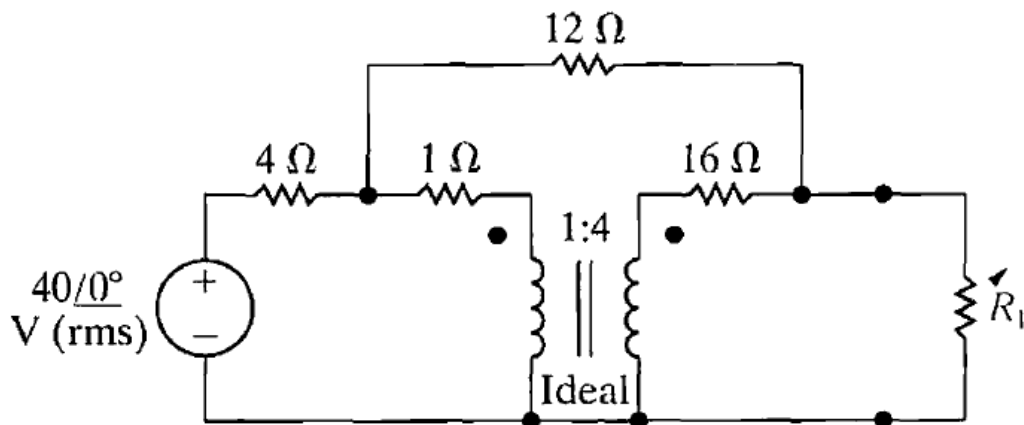10.62 The variable load resistor R_L in the circuit shown in Fig. P10.62 is adjusted for maximum average power transfer to R_L .

PSPICE
MULTISIM

- Find the maximum average power.
- What percentage of the average power developed by the ideal voltage source is delivered to R_L when R_L is absorbing maximum average power?
- Test your solution by showing that the power developed by the ideal voltage source equals the power dissipated in the circuit.



10.64 Find the average power delivered to the $10\ \Omega$ resistor in the circuit of Fig. P10.64.

Figure P10.64

