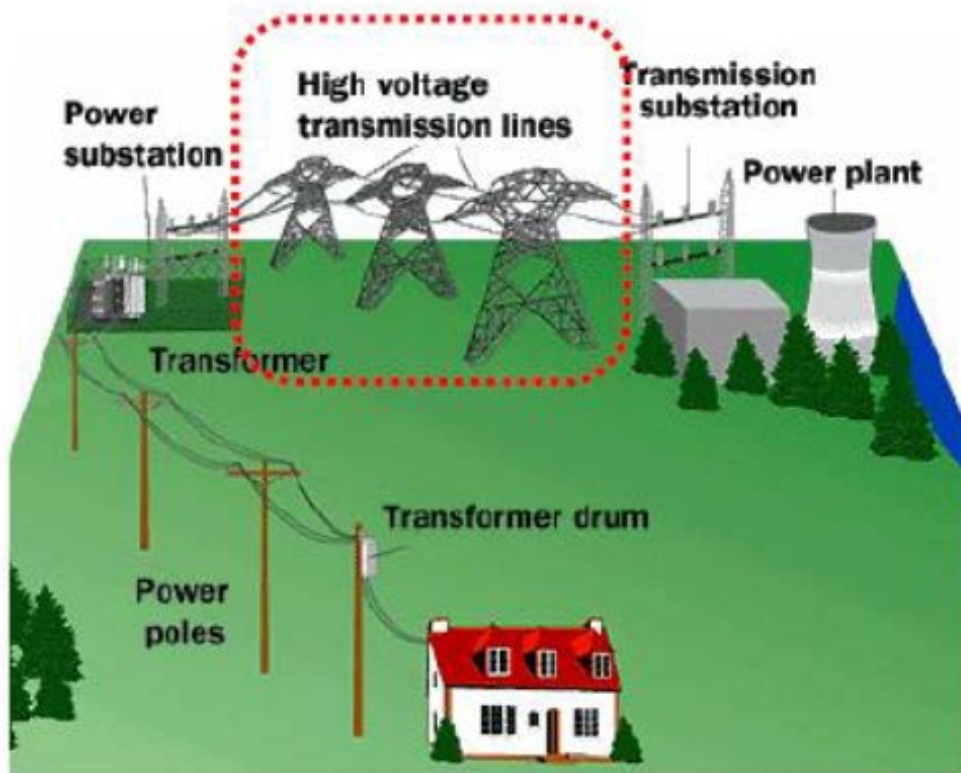


Chapter 11

Balanced Three Phase Circuits




ENEE2301 - Birzeit University

Balanced Three-Phase Circuits

What is a Three-Phase Circuit?

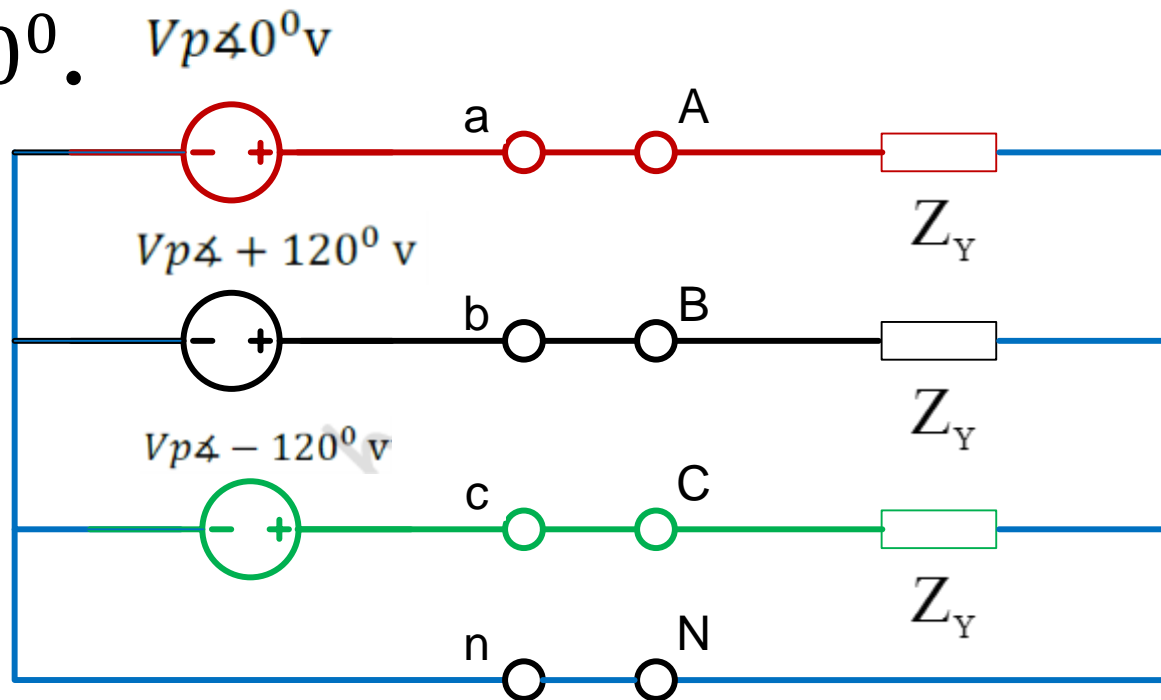It is a system produced by a generator consisting of three sources having the same amplitude and frequency but out of phase with each other by 120° .




Advantages


- 1- Almost all the electric power is generated and distributed in three-phase.
- 2- The instantaneous power in a three-phase system is constant
==> There is less vibration in the rotating machinery which in turn performs more efficiently.
- 3- The amount of power loss in the three-phase system is only half the power loss in the cables for the single phase system.
- 4- Thinner conductors can be used to transmit the same KVA at the same voltage.

Balanced Three Phase Generator

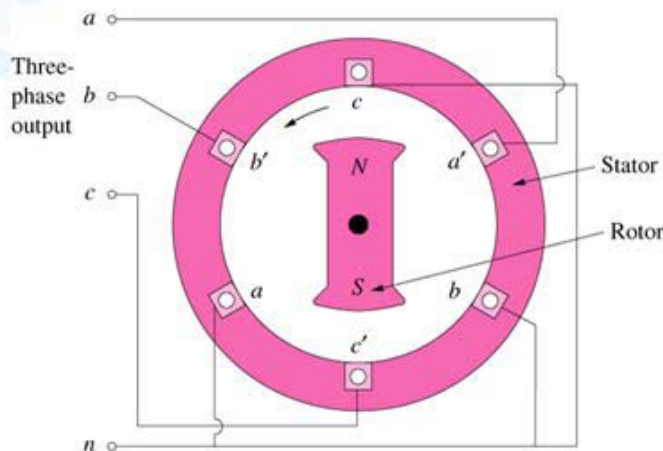A three-phase generator consists of a rotating magnet (rotor) surrounded by a stationary winding (stator).



A three-phase generator

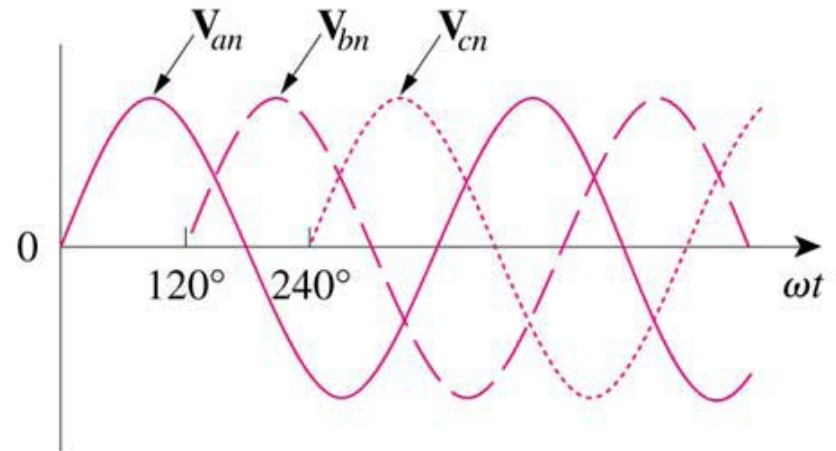

The generated voltages

The Three – Phase Generator:


- a) Has three induction coils.
- b) Placed 120° apart on the rotor.
- c) The three coils have an equal number of turns.
- d) The voltage induced across each coil will have the same peak value, shape and frequency.

Balanced Three-Phase Sources:


- Two possible configurations

1- The Y-connected source

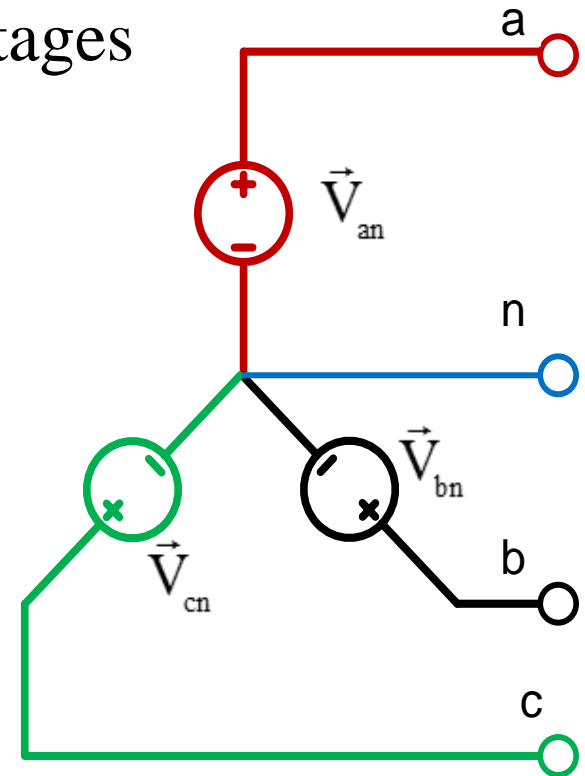\vec{V}_{an} , \vec{V}_{bn} and \vec{V}_{cn} are called phase voltages



2) The Δ - connected source

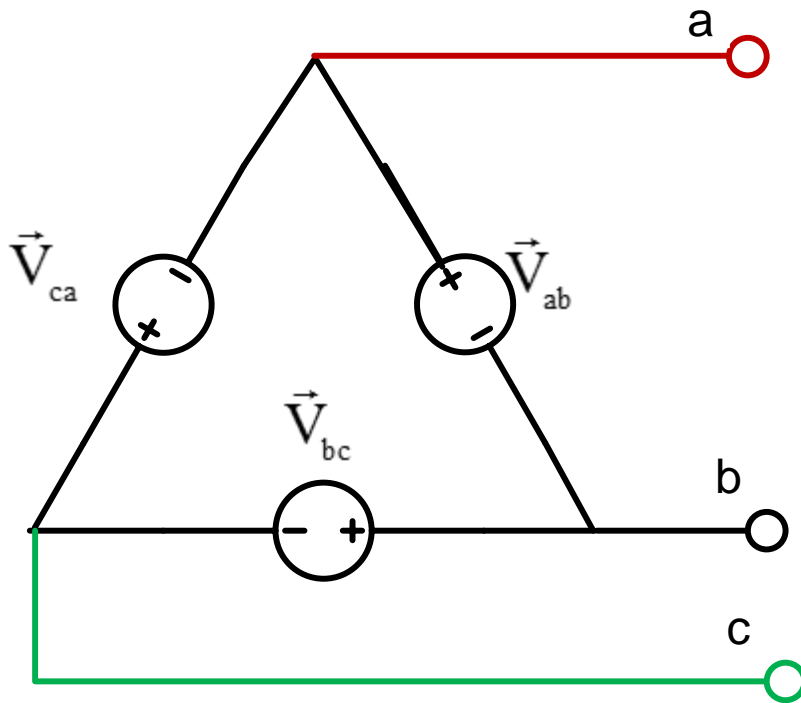

\vec{V}_{ab} , \vec{V}_{bc} and \vec{V}_{ca} are called line to line voltages

The Phase Sequence


- The phase sequence is the time order in which the voltages pass through their respective maximum values

1- abc sequence (positive sequence)

$$\vec{V}_{an} = \vec{V}_a = V_P \angle 0^\circ$$

$$\vec{V}_{bn} = \vec{V}_b = V_P \angle -120^\circ$$
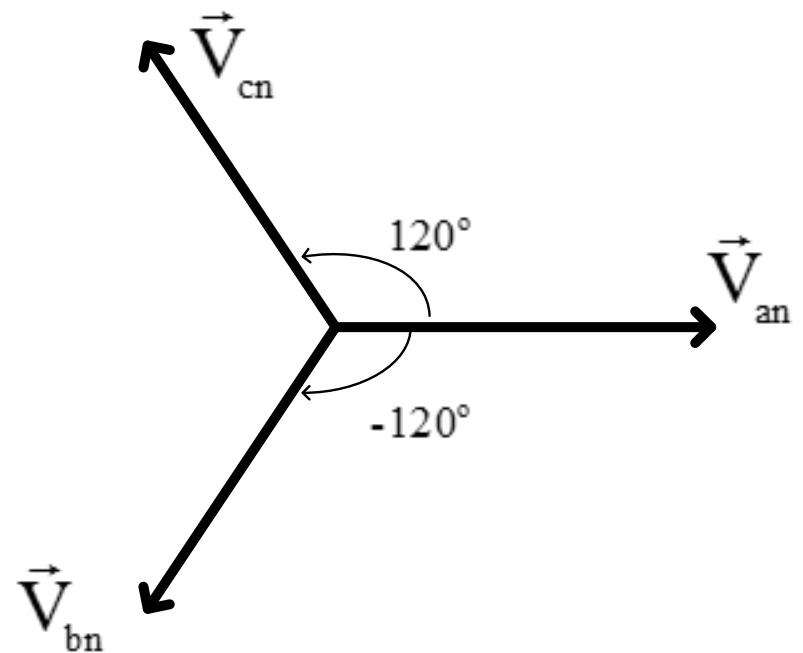
$$\vec{V}_{cn} = \vec{V}_c = V_P \angle +120^\circ$$





abc sequence

$$\vec{V}_{an} = \vec{V}_a = V_P \angle 0^\circ$$

$$\vec{V}_{bn} = \vec{V}_b = V_P \angle -120^\circ$$
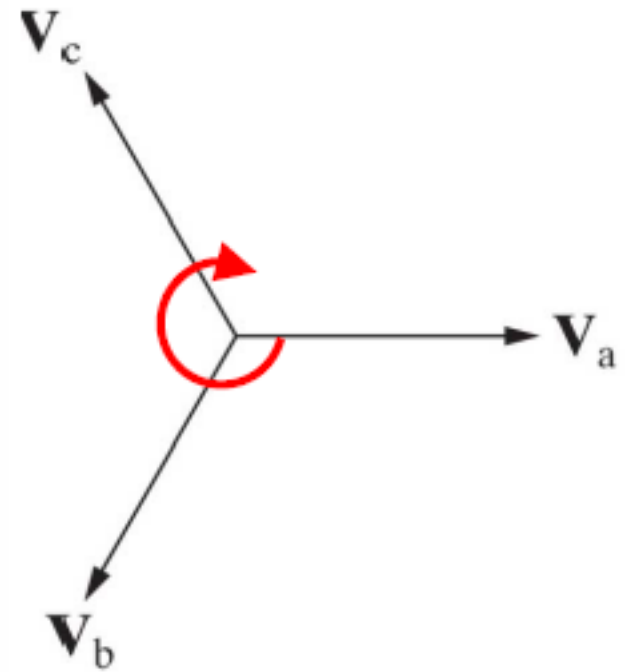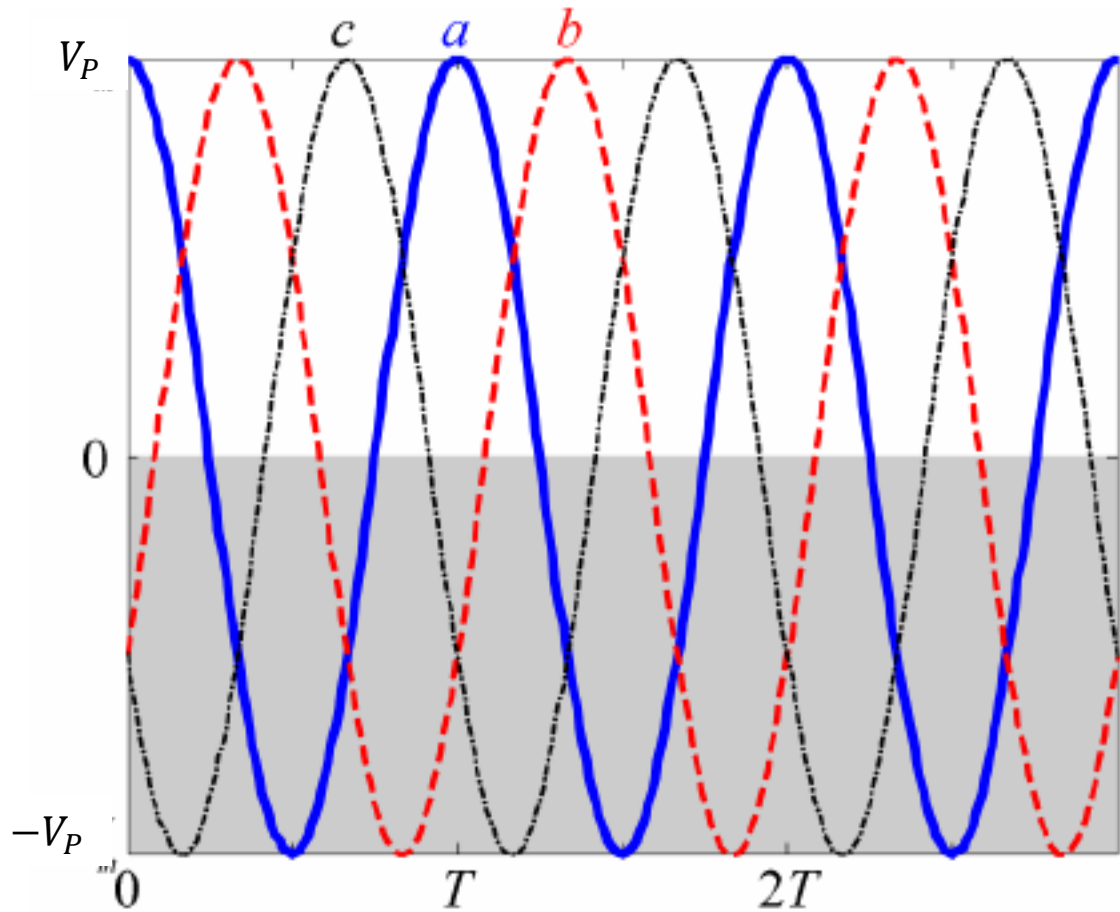
$$\vec{V}_{cn} = \vec{V}_c = V_P \angle +120^\circ$$




2- acb sequence (Negative sequence)

$$\vec{V}_{an} = \vec{V}_a = V_P \angle 0^\circ$$

$$\vec{V}_{bn} = \vec{V}_b = V_P \angle +120^\circ$$
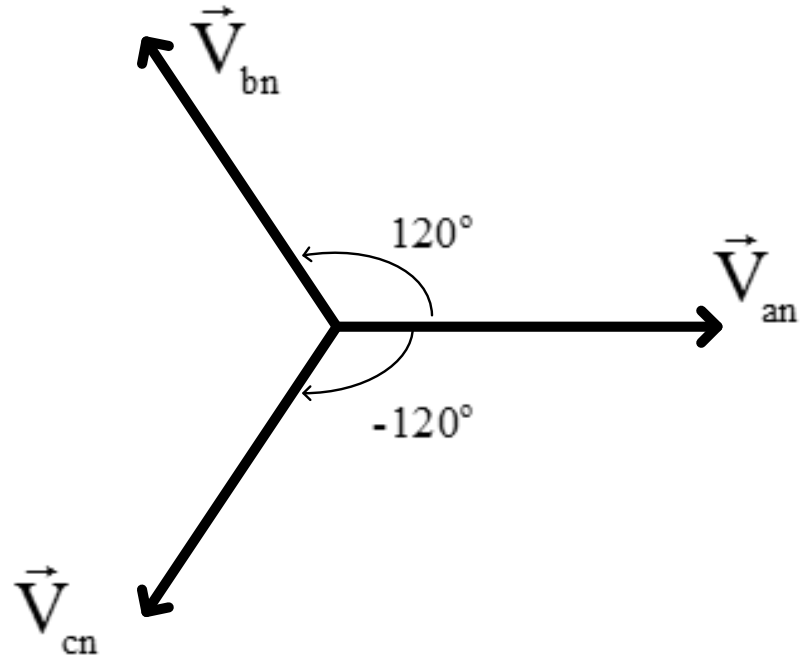
$$\vec{V}_{cn} = \vec{V}_c = V_P \angle -120^\circ$$



$$\vec{V}_{an} + \vec{V}_{bn} + \vec{V}_{cn} = 0$$

$$\vec{V}_{an} = \vec{V}_a = V_P \angle 0^\circ$$

$$\vec{V}_{bn} = \vec{V}_b = V_P \angle -120^\circ$$

$$\vec{V}_{cn} = \vec{V}_c = V_P \angle +120^\circ$$


$$\vec{V}_{an} = V_P$$

$$\vec{V}_{bn} = V_P \cos(-120^\circ) + jV_P \sin(-120^\circ)$$

$$\vec{V}_{bn} = V_P \left(-\frac{1}{2} - j\frac{\sqrt{3}}{2} \right)$$


$$\vec{V}_{cn} = V_P \cos(+120^\circ) + jV_P \sin(+120^\circ)$$
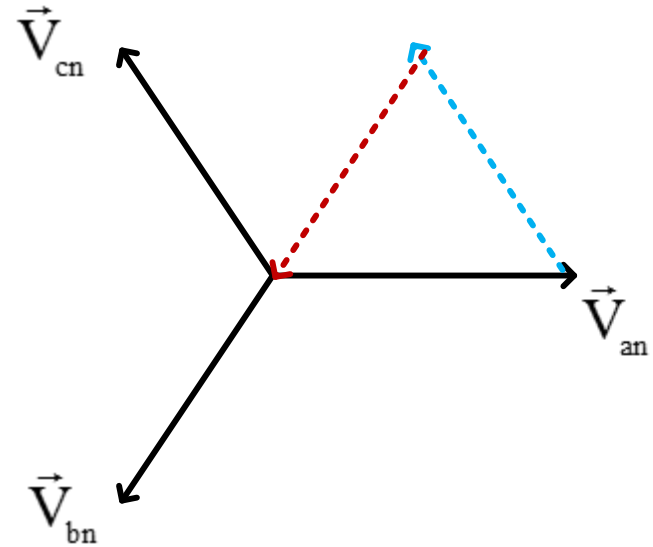
$$\vec{V}_{cn} = V_P \left(-\frac{1}{2} + j\frac{\sqrt{3}}{2} \right)$$



$$\begin{aligned} \ddots & \quad \vec{V}_{an} + \vec{V}_{bn} + \vec{V}_{cn} = 0 \\ \ddots & \quad \vec{V}_{an(t)} + \vec{V}_{bn(t)} + \vec{V}_{cn(t)} = 0 \end{aligned}$$

Balanced set

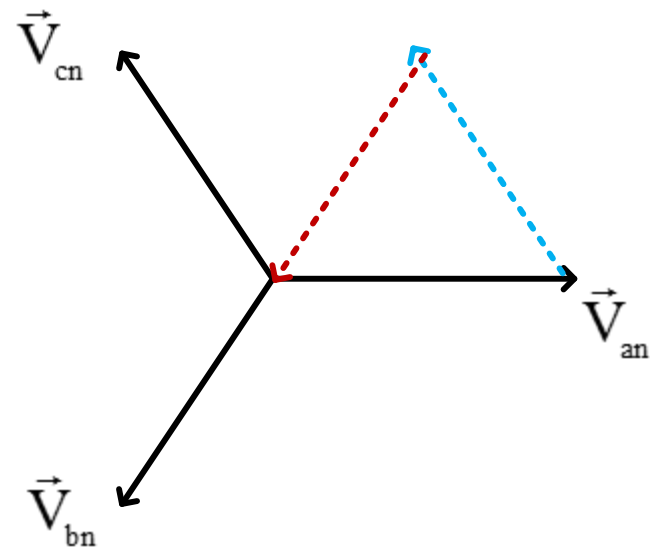

Line to Line Voltages

let

$$\vec{V}_{an} = V_P \angle 0^\circ$$

$$\vec{V}_{bn} = V_P \angle -120^\circ$$

$$\vec{V}_{cn} = V_P \angle +120^\circ$$




$$\vec{V}_{ab} = \vec{V}_{an} + \vec{V}_{nb}$$

$$\vec{V}_{ab} = \vec{V}_{an} - \vec{V}_{bn}$$

$$\vec{V}_{ab} = V_P \angle 0^\circ - V_P \angle -120^\circ$$

$$\vec{V}_{ab} = V_P - V_P \left(\cos(-120^\circ) + j\sin(-120^\circ) \right)$$

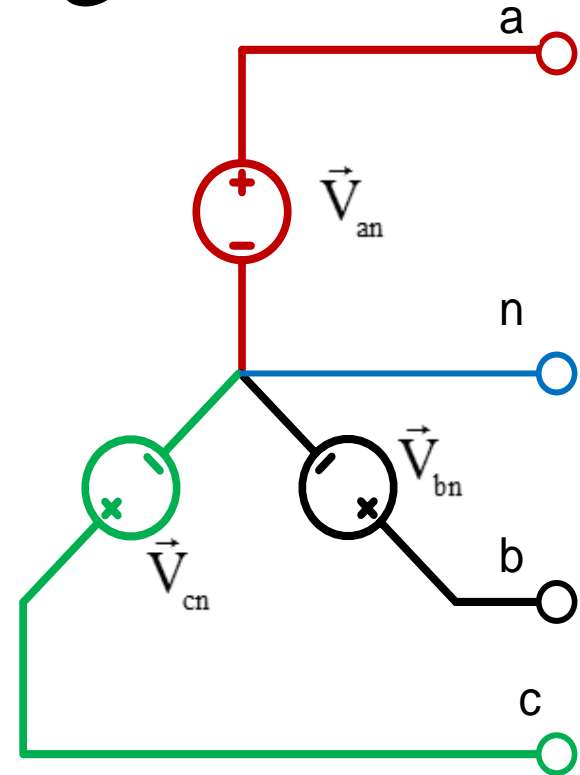\vec{V}_{ab} , \vec{V}_{bc} , \vec{V}_{ca} are line to line voltages



$$\overrightarrow{V_{ab}} = Vp - Vp\left(-\frac{1}{2} - j\frac{\sqrt{3}}{2}\right)$$

$$\overrightarrow{V_{ab}} = Vp\left(1 + \frac{1}{2} + j\frac{\sqrt{3}}{2}\right)$$

$$\overrightarrow{V_{ab}} = Vp\left(\frac{3}{2} + j\frac{\sqrt{3}}{2}\right)$$

$$\overrightarrow{V_{ab}} = vp\sqrt{\left(\frac{3}{2}\right)^2 + \left(\frac{\sqrt{3}}{2}\right)^2} \angle \tan^{-1}\left(\frac{\frac{\sqrt{3}}{2}}{\frac{3}{2}}\right)$$

$$\overrightarrow{V_{ab}} = Vp\sqrt{3} \angle + 30^\circ \text{ v}$$

$$\overrightarrow{V_{ab}} = \sqrt{3} \overrightarrow{V_{an}} \angle + 30^\circ \text{ v}$$

$$\overrightarrow{V_{bc}} = \sqrt{3} \overrightarrow{V_{bn}} \angle + 30^\circ \text{ v}$$

$$\overrightarrow{V_{ca}} = \overrightarrow{V_{cn}}\sqrt{3} \angle + 30^\circ \text{ v}$$

For negative sequence:

$$\overrightarrow{V_{an}} = V_p \angle 0^\circ \text{ V}$$

$$\overrightarrow{V_{bn}} = V_p \angle +120^\circ \text{ V}$$


$$\overrightarrow{V_{cn}} = V_p \angle -120^\circ \text{ V}$$

$$\overrightarrow{V_{ab}} = V_p \sqrt{3} \angle -30^\circ \text{ V}$$

$$\therefore \overrightarrow{V_{ab}} = \sqrt{3} \overrightarrow{V_{an}} \angle -30^\circ \text{ V}$$

$$\therefore \overrightarrow{V_{bc}} = \sqrt{3} \overrightarrow{V_{bn}} \angle -30^\circ \text{ V}$$
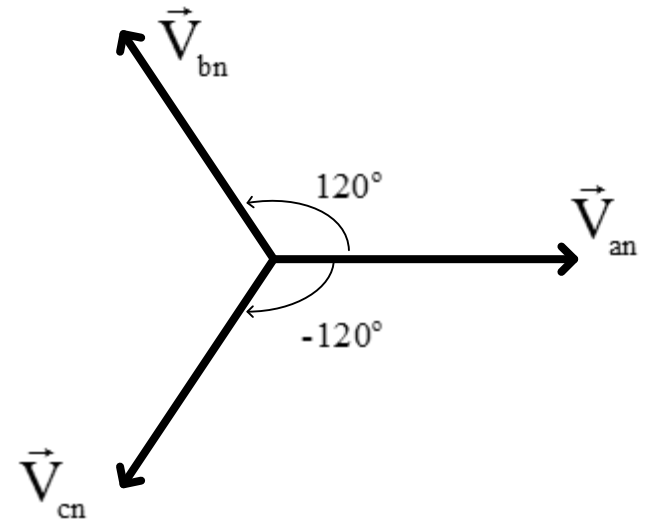
$$\therefore \overrightarrow{V_{bc}} = V_p \sqrt{3} \angle +90^\circ \text{ V}$$





$$\therefore \overrightarrow{V_{ca}} = V_p \sqrt{3} \angle -150^\circ \text{ V}$$

$$\therefore \overrightarrow{V_{ca}} = \sqrt{3} \overrightarrow{V_{cn}} \angle -30^\circ \text{ V}$$

Balanced Three Phase Loads

- A balanced load has equal impedances on all the phases. Two connection schemes are used:


1- Y-connected load

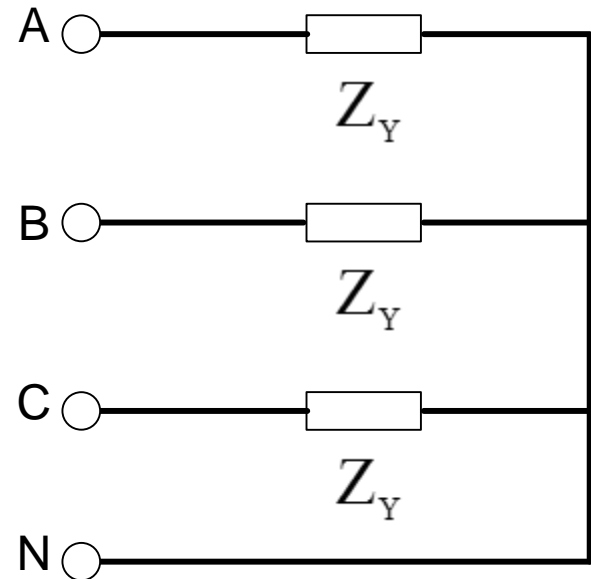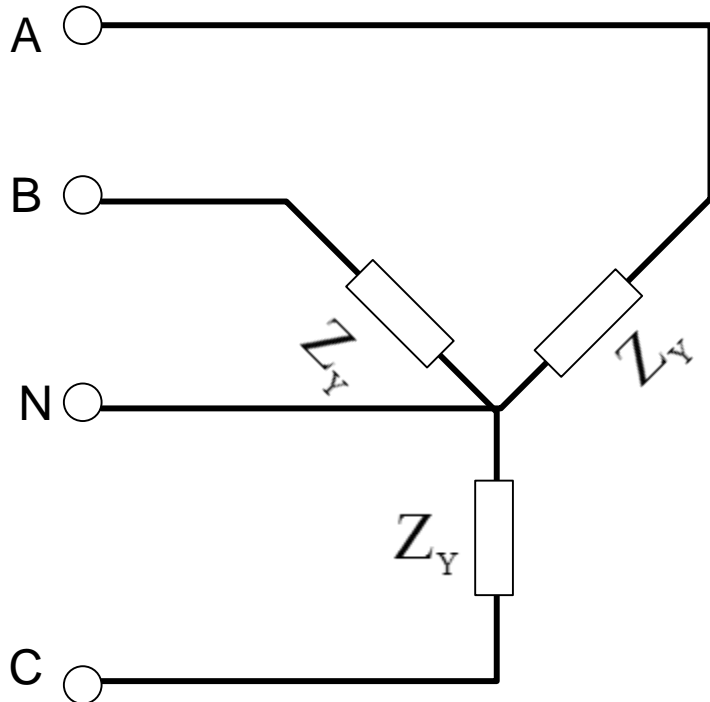

Unknowns to be solved

- Line (line-to-line) voltage: voltage across any pair of lines.

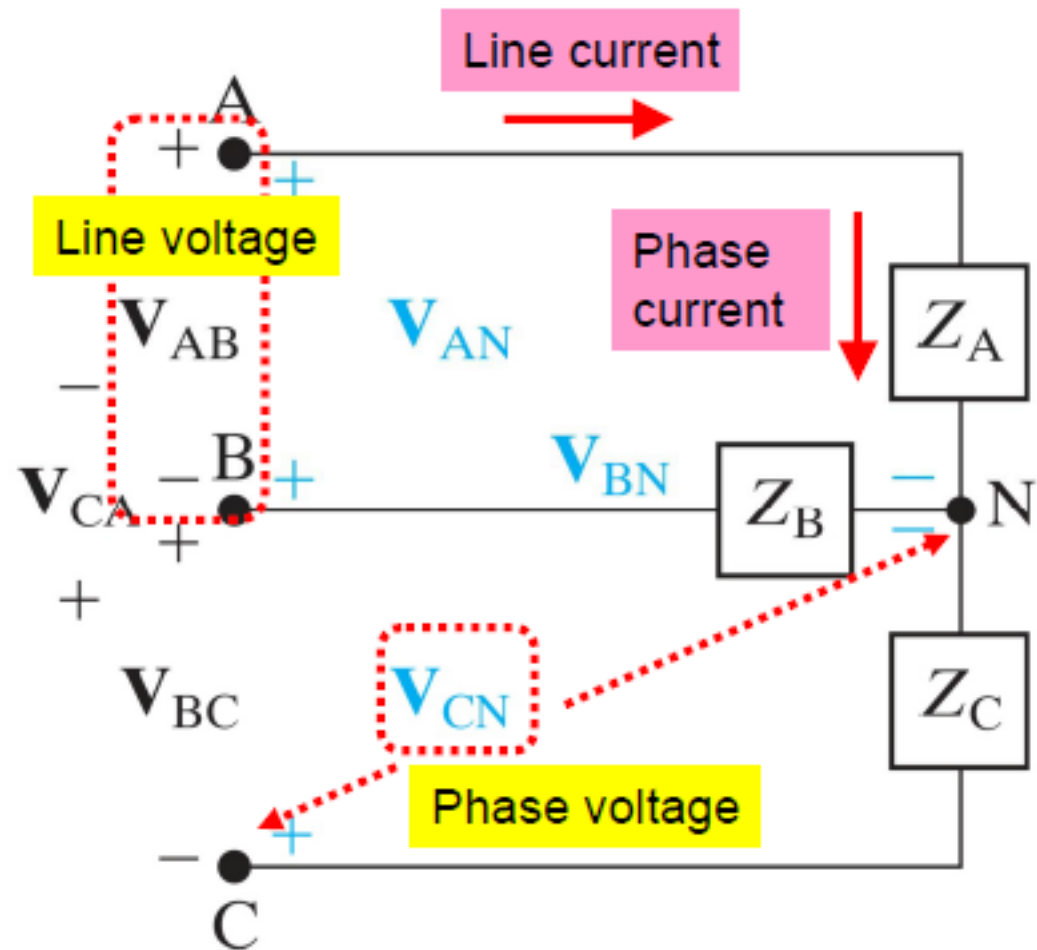
- Phase (line-to-neutral) voltage: voltage across a single phase.



- For Y-connected load, line current equals phase current.


Balanced Three Phase Loads

2- Δ -connected load

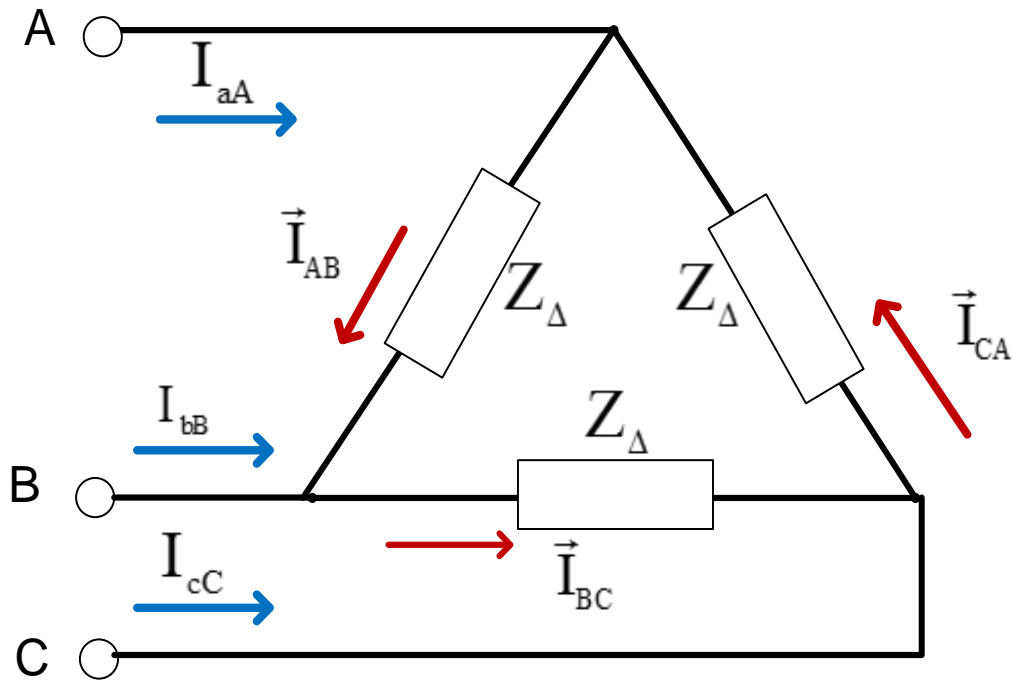

$$Z_Y = \frac{Z_{\Delta}}{3}$$

$$Z_{\Delta} = 3Z_Y$$

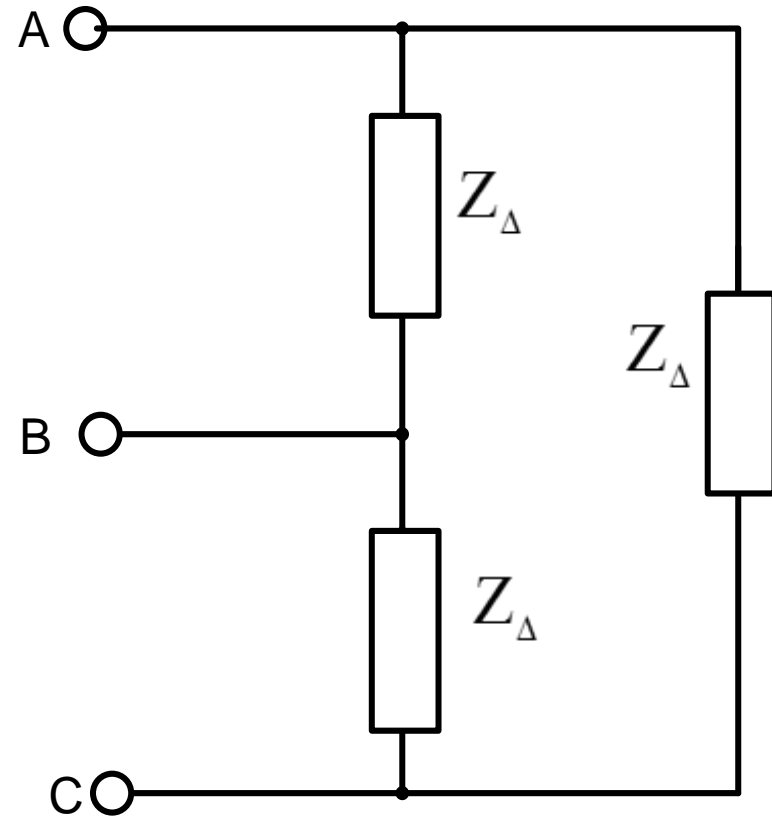


Three Phase Connections

- Both the three phase source and the three phase load can be connected either Wye or Delta

 We have 4 possible connection types.


- Y-Y Connection
- Y- Δ Connection
- Δ - Δ Connection
- Δ - Y Connection

Three-phase systems

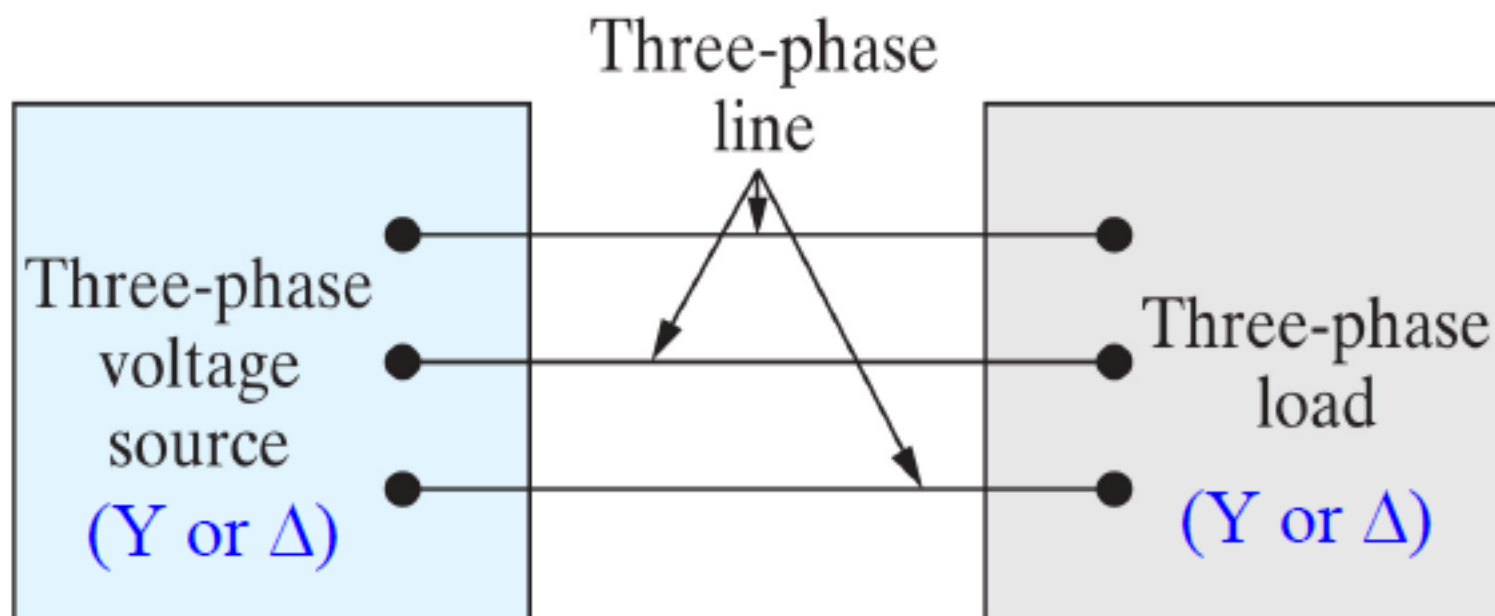

- Source-load can be connected in four configurations: Y-Y, Y- Δ , Δ -Y, Δ - Δ .
- It's sufficient to analyze Y-Y, while the others can be treated by Δ -Y and Y- Δ transformations.

Balanced Y-Y System

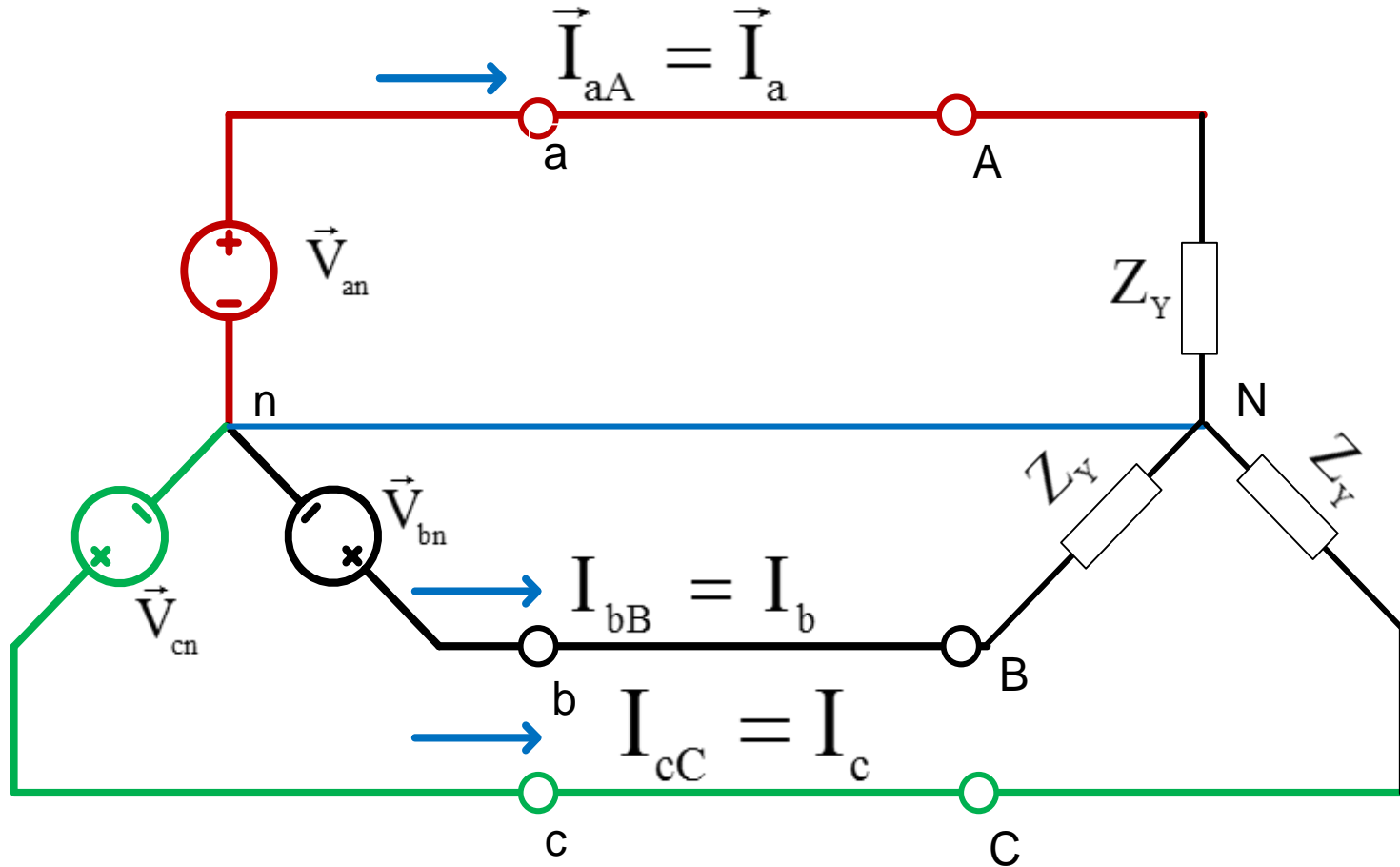


$$\vec{I}_{aA} = \vec{I}_a = \frac{\vec{V}_{an}}{Z_Y}$$

$$\vec{I}_{bB} = \vec{I}_b = \frac{\vec{V}_{bn}}{Z_Y}$$

$$\vec{I}_{cC} = \vec{I}_c = \frac{\vec{V}_{cn}}{Z_Y}$$

Balanced Y-Y System

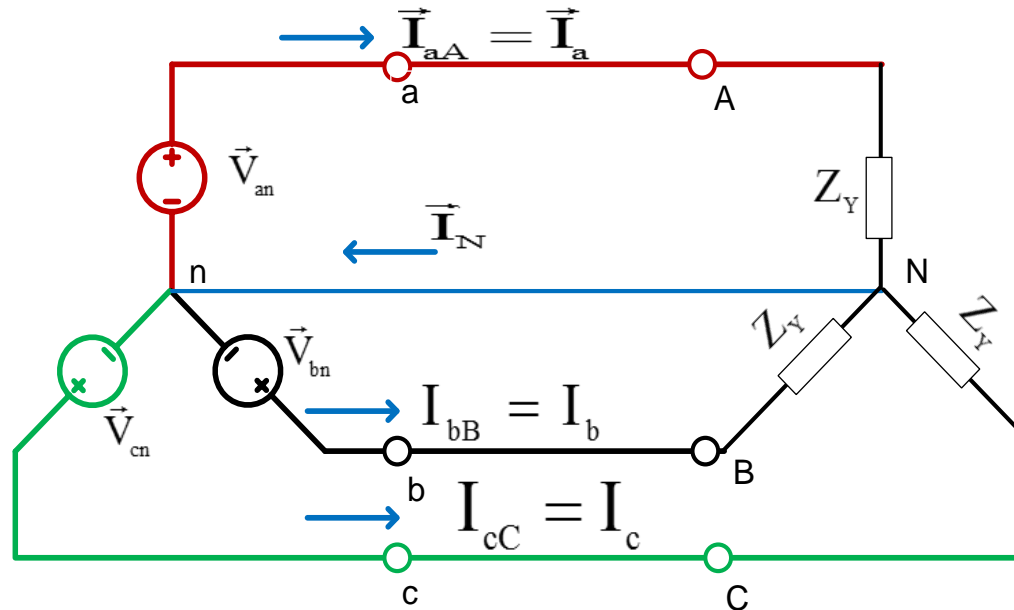

$$\text{KCL: } \vec{I}_N = \vec{I}_a + \vec{I}_b + \vec{I}_c$$

$$= \frac{\vec{V}_{an}}{Z_Y} + \frac{\vec{V}_{bn}}{Z_Y} + \frac{\vec{V}_{cn}}{Z_Y}$$

$$= \frac{1}{Z_Y} (\vec{V}_{an} + \vec{V}_{bn} + \vec{V}_{cn})$$

$$\vec{I}_N = \frac{1}{Z_Y} (\text{Zero}) = 0$$

\Rightarrow it could be replaced by open circuit

Example

- Calculate The line currents

If the following is given:


$$\vec{V}_{an} = 120 \angle 0^\circ \text{ V rms}$$

$$\vec{V}_{bn} = 120 \angle -120^\circ \text{ V rms}$$

$$\vec{V}_{cn} = 120 \angle +120^\circ \text{ V rms}$$


$$Z_Y = (1 + j1)\Omega$$

$$Z_T = (20 + j10)\Omega$$

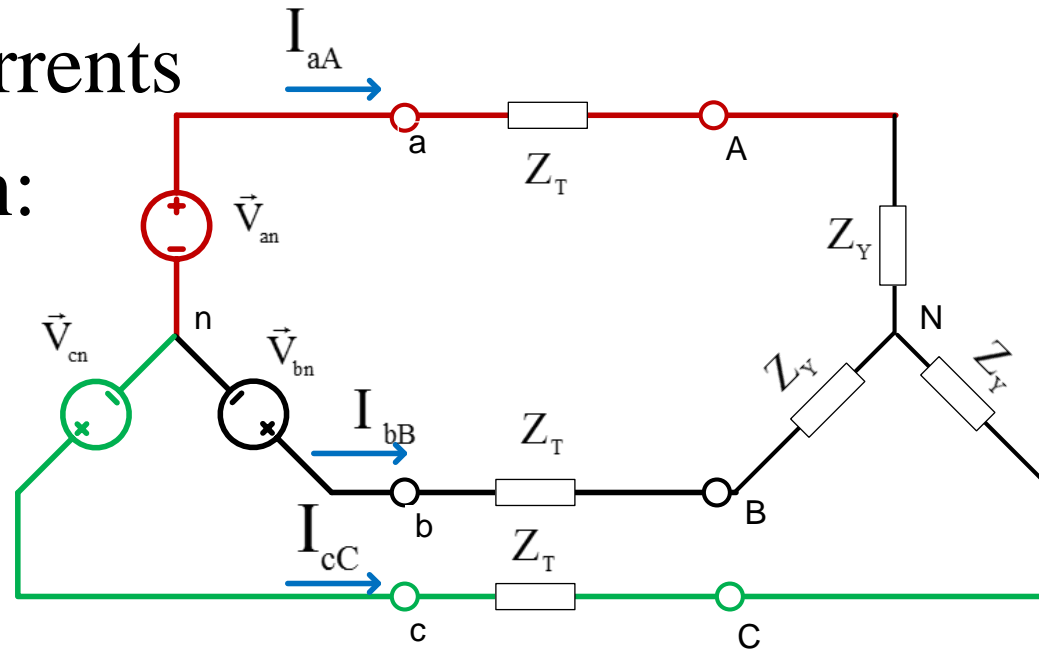


Solution

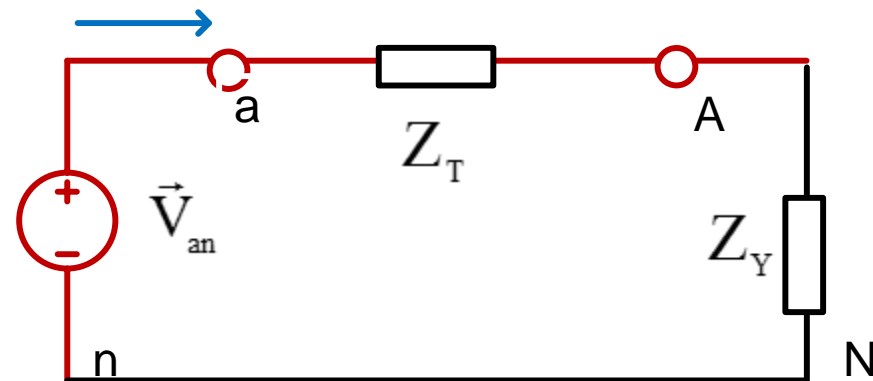We can use single phase Representation (since we have balanced three phase system)



Solution
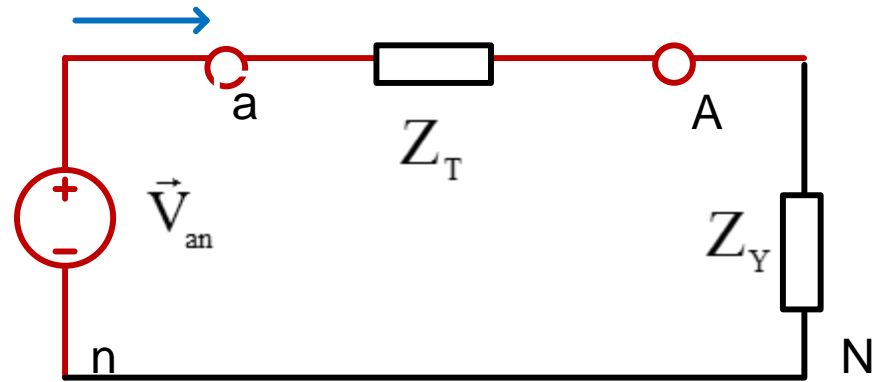
$$\vec{I}_{aA} = \frac{\vec{V}_{an}}{Z_T + Z_Y} = \frac{120 \angle 0^\circ}{(1 + j1) + (20 + j10)}$$



$$\therefore \vec{I}_{aA} = \frac{120 \angle 0^\circ}{(21 + j11)} = 5.06 \angle -27.65^\circ \text{ A rms}$$

$$\therefore \vec{I}_{bB} = 5.06 \angle -27.65^\circ - 120^\circ = 5.67 \angle -147.65^\circ \text{ A rms}$$

$$\therefore \vec{I}_{cC} = 5.06 \angle -27.65^\circ + 120^\circ = 5.67 \angle 92.35^\circ \text{ A rms}$$

Note: It is enough to find one of the line currents and the other two are shifted by an angle equal to the phase voltage shift

Balanced Y- Δ system

Example

Calculate The line currents

If the following is given:

$$\vec{V}_{an} = 120 \angle 30^\circ$$

$$Z_{\Delta} = (6 + j6)\Omega$$


$$Z_T = 0$$

Positive Sequence

\therefore


$$\vec{V}_{bn} = 120 \angle -90^\circ$$

$$\vec{V}_{cn} = 120 \angle 150^\circ$$

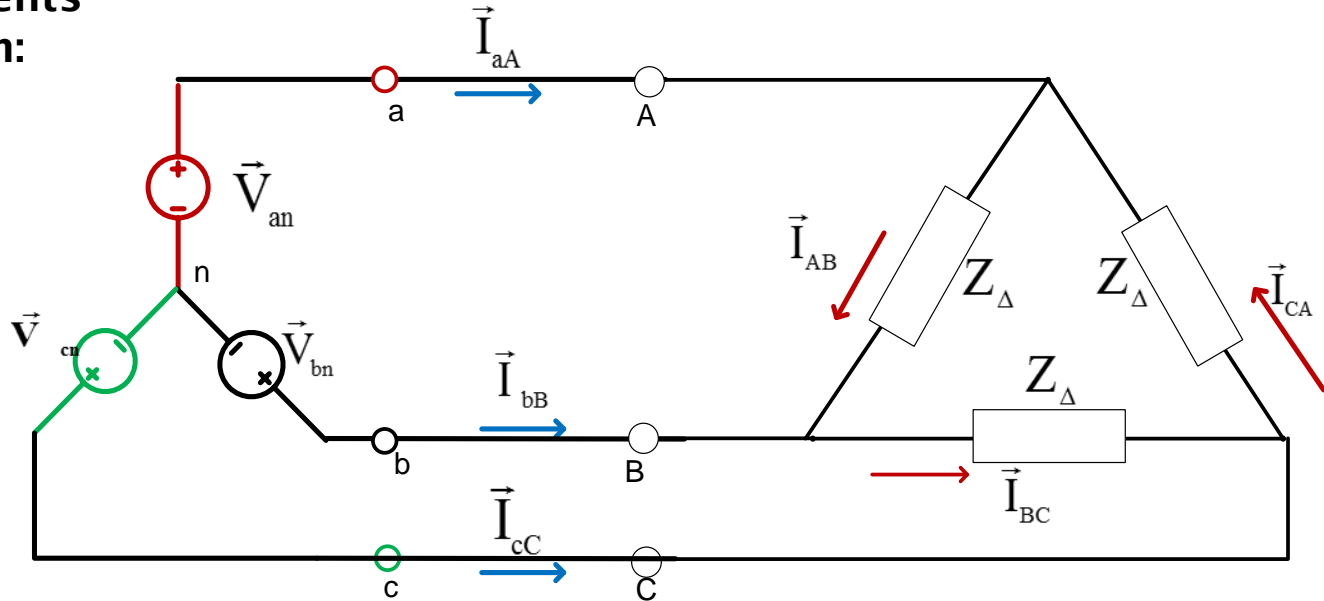

Balanced Y- Δ system

Calculate The line currents:

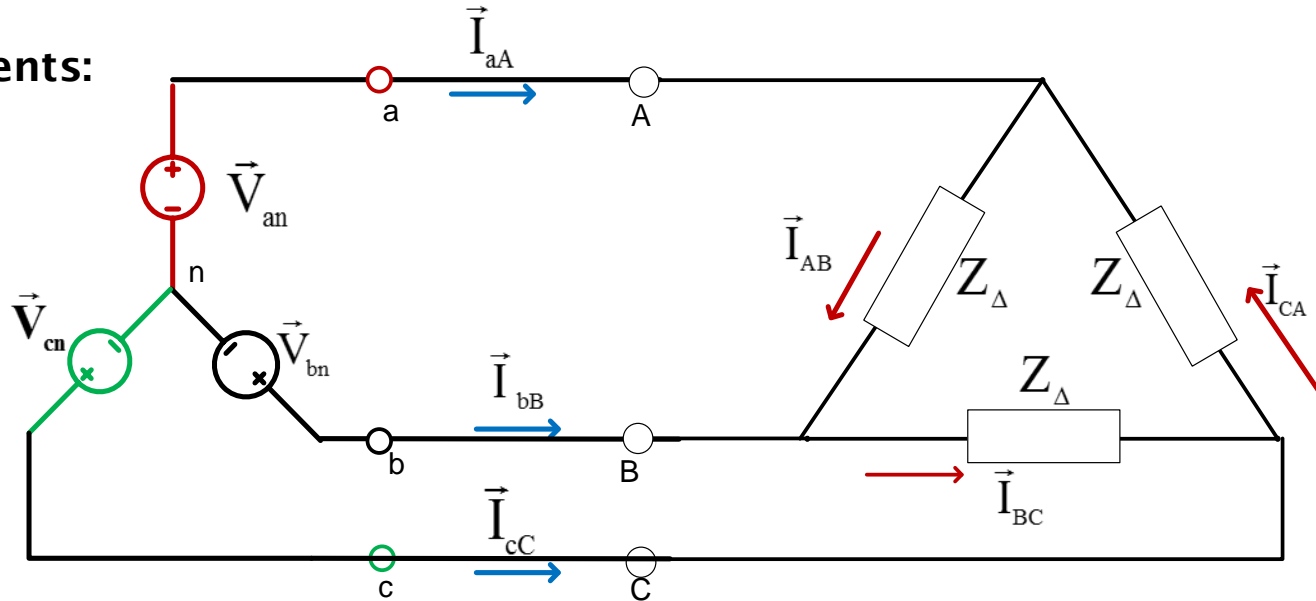

$$\vec{V}_{ab} = \vec{V}_{AB} = 120\sqrt{3} \angle 60^\circ \text{ V rms}$$

$$\vec{I}_{AB} = \frac{\vec{V}_{AB}}{Z_{\Delta}} = 24.5 \angle 15^\circ \text{ A rms}$$

$$\therefore \vec{I}_{BC} = 24.5 \angle -105^\circ \text{ A rms}$$

$$\therefore \vec{I}_{CA} = 24.5 \angle 135^\circ \text{ A rms}$$

$\vec{I}_{AB}, \vec{I}_{BC}, \vec{I}_{CA}$ are the phase currents of the load

Balanced Y- Δ system

Calculate The line currents:

KCL @ A

$$\vec{I}_{aA} = \vec{I}_{AB} - \vec{I}_{CA}$$

$$= 24.5 \angle 15^\circ - 24.5 \angle 135^\circ$$


$$= 42.44 \angle -15^\circ \text{ A rms}$$

$$\vec{I}_{aA} = \sqrt{3} \vec{I}_{AB} \angle -30^\circ \quad \Rightarrow$$

Line current lags the phase current
by only -30° for abc sequence

$$\therefore \vec{I}_{bB} = 42.44 \angle -135^\circ \text{ A rms}$$

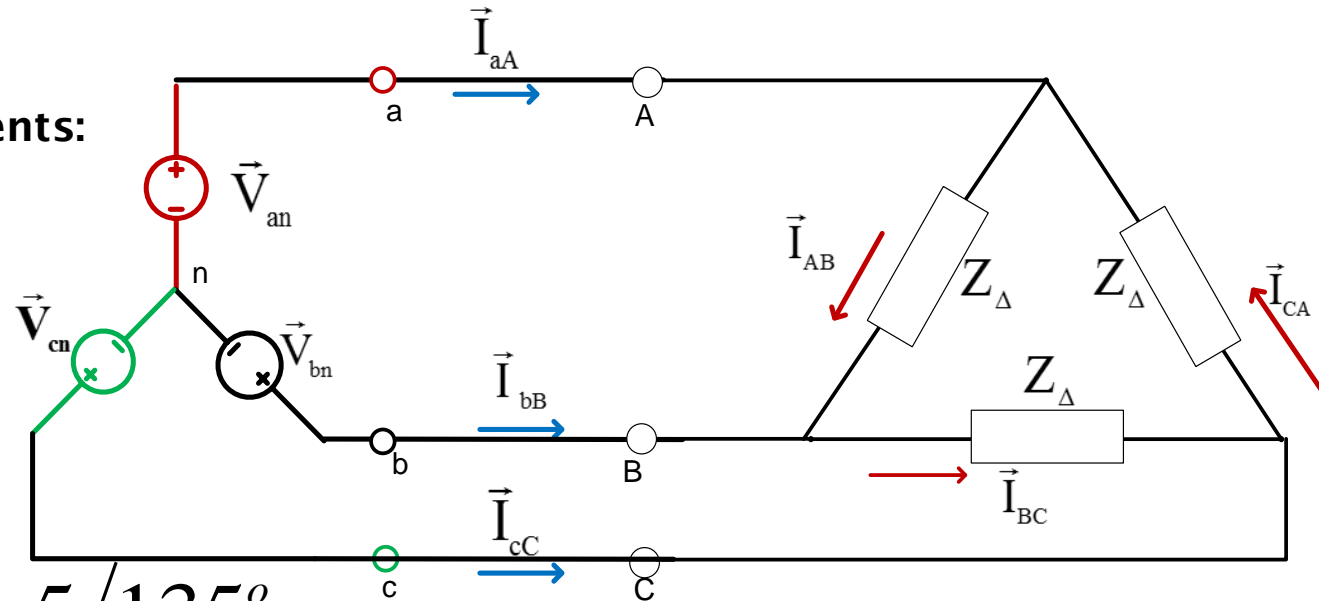
$$\therefore \vec{I}_{cC} = 42.44 \angle 105^\circ \text{ A rms}$$



Second Method

Using Δ -Y transformation for the load

$$Z_Y = \frac{Z_{\Delta}}{3}$$

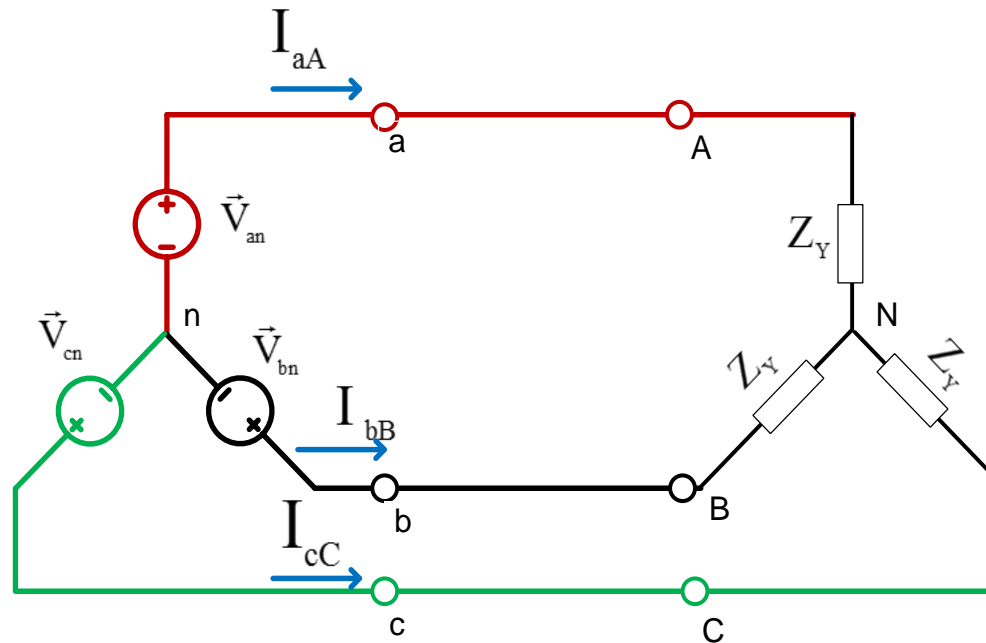

Second Method


$$Z_Y = \frac{6 + j6}{3} = 2 + j2$$

$$\vec{I}_{aA} = \frac{\vec{V}_{an}}{Z_Y} = \frac{120 \angle 30^\circ}{(2 + j2)}$$

$$\therefore \vec{I}_{aA} = 42.44 \angle -15^\circ \text{ A rms}$$

$$\therefore \vec{I}_{bB} = 42.44 \angle -15^\circ - 120^\circ = 42.44 \angle -135^\circ \text{ A rms}$$

$$\therefore \vec{I}_{cC} = 42.44 \angle -15^\circ + 120^\circ = 42.44 \angle 105^\circ \text{ A rms}$$

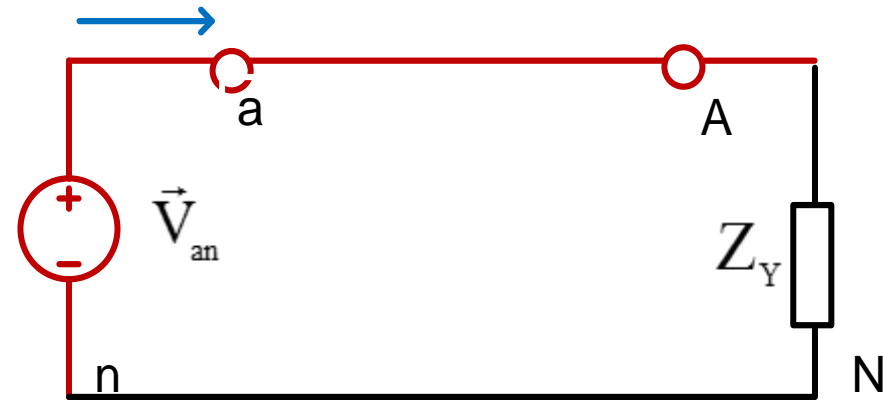

Example 2


$$\vec{V}_{an} = 120 \angle 0^\circ \text{ V rms}$$

$$Z_{\Delta} = (118.5 + j85.8)\Omega$$

$$Z_T = (0.3 + j0.9)\Omega$$

$$Z_S = (0.2 + j0.5)\Omega$$

abc sequence

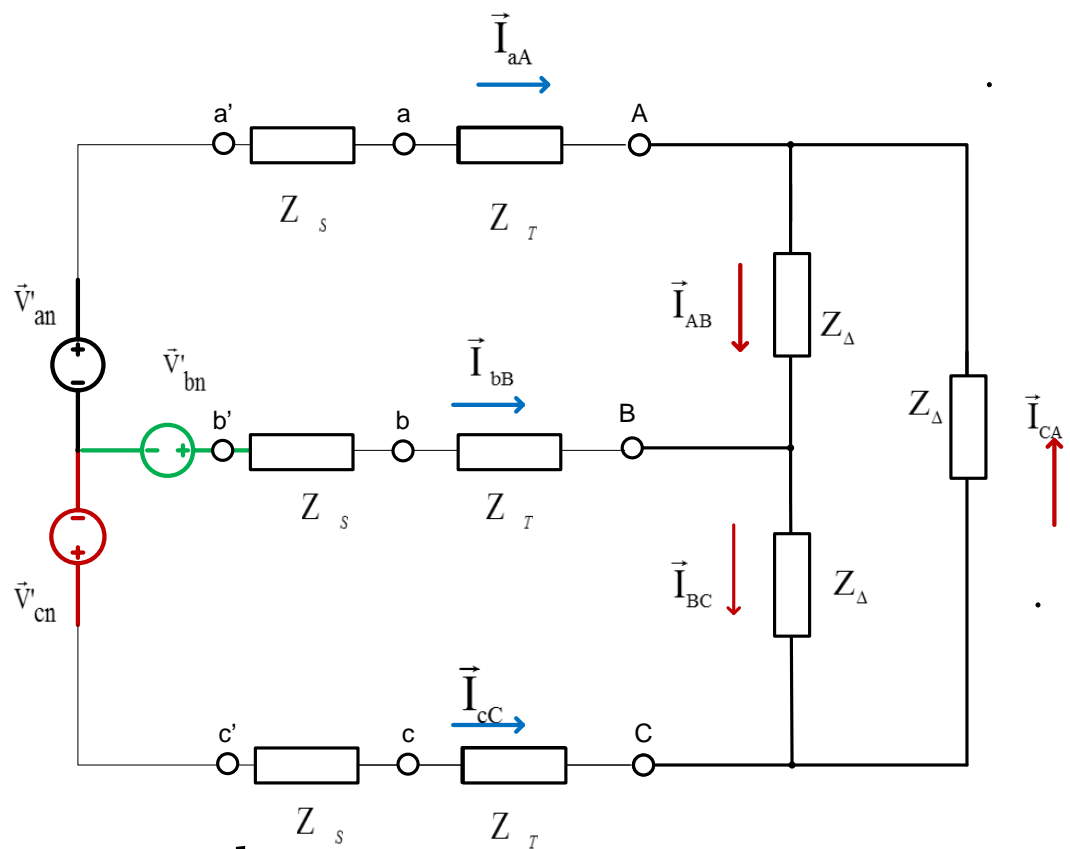


- 1) Calculate The line currents:
- 2) Calculate The phase currents of the load
- 3) Calculate The phase voltage at the load terminal V_{AB} , V_{BC} , V_{CA}

Single Phase Representation

$$Z_Y = \frac{Z_{\Delta}}{3} = \frac{118.5 + j85.8}{3}$$

$$= 39.5 + j28.6$$

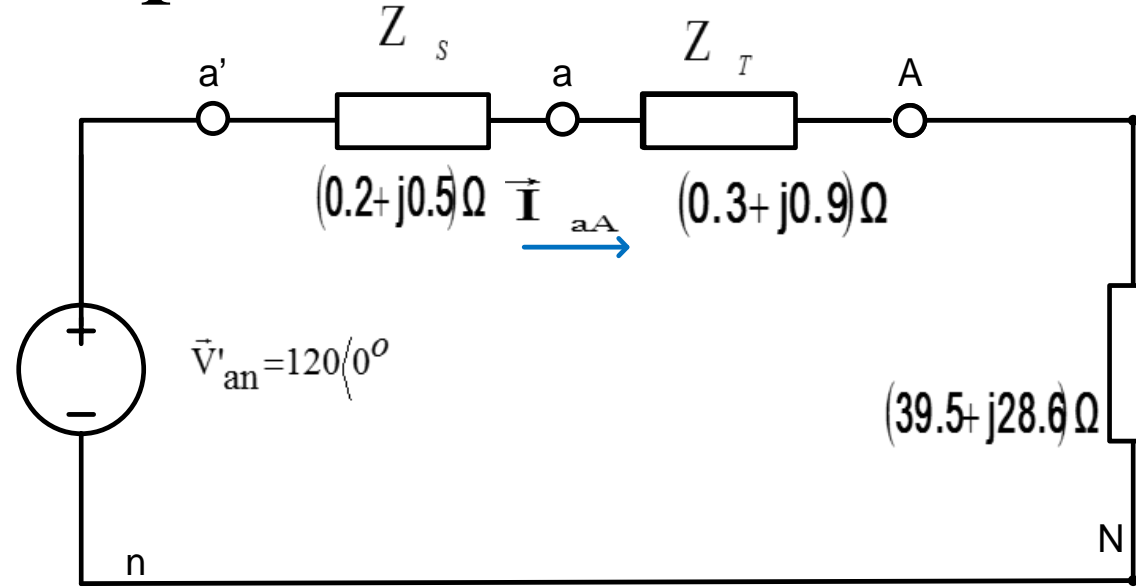

$$\bar{I}_{aA} = \frac{120}{Z_S + Z_T + Z_Y} = \frac{120}{0.2 + j0.5 + 0.3 + j0.9 + 39.5 + j28.6 +}$$

$$\bar{I}_{aA} = 2.4 \angle -36.87^\circ \text{ A rms}$$

$$\bar{I}_{bB} = 2.4 \angle -156.87^\circ \text{ A rms}$$

$$\bar{I}_{cC} = 2.4 \angle 83.13^\circ \text{ A rms}$$

2) Calculate The phase currents of the load

$$\vec{I}_{AB} = \frac{1}{\sqrt{3}} \vec{I}_{aA} \angle 30^\circ \text{ A rms}$$

$$\therefore \vec{I}_{AB} = \left(\frac{1}{\sqrt{3}} \angle 30^\circ \right) \left(2.4 \angle -36.87^\circ \right) \text{ A rms}$$

$$\therefore \vec{I}_{AB} = \left(1.39 \angle -6.87^\circ \right) \text{ A rms}$$

$$\therefore \vec{I}_{BC} = \left(1.39 \angle -126.87^\circ \right) \text{ A rms}$$

$$\therefore \vec{I}_{CA} = \left(1.39 \angle 113.13^\circ \right) \text{ A rms}$$

3) Calculate The phase voltage at the load terminal V_{AB} , V_{BC} , V_{CA}

First Method

$$\vec{V}_{AB} = Z_{\Delta} \vec{I}_{AB}$$

$$\therefore \vec{V}_{AB} = (118.5 + j85.8) \left(1.39 \angle -6.87^{\circ} \right) \text{ A rms}$$

$$\therefore \vec{V}_{AB} = 202.72 \angle 29.04^{\circ} \text{ V rms}$$

$$\therefore \vec{V}_{BC} = 202.72 \angle -90.96^{\circ} \text{ V rms}$$

$$\therefore \vec{V}_{CA} = 202.72 \angle 149.04^{\circ} \text{ V rms}$$

3) Calculate The phase voltage at the load terminal V_{AB}, V_{BC}, V_{CA}

Second Method: From single phase representation

$$\vec{V}_{AN} = Z_Y \vec{I}_{aA}$$

$$\therefore \vec{V}_{AN} = (39.5 + j28.6) \left(2.4 \angle -36.87^\circ \right) \text{ V rms}$$

$$\therefore \vec{V}_{AN} = 117.04 \angle -0.96^\circ \text{ V rms}$$


$$\therefore \vec{V}_{AB} = \sqrt{3} \angle +30^\circ \vec{V}_{AN}$$

$$\therefore \vec{V}_{AB} = \sqrt{3} \angle +30^\circ \left(117.04 \angle -0.96^\circ \right) = 202 \angle 29.04^\circ \text{ V rms}$$

$$\therefore \vec{V}_{BC} = 202.72 \angle -90.96^\circ \text{ V rms}$$

$$\therefore \vec{V}_{CA} = 202.72 \angle 149.04^\circ \text{ V rms}$$

Power in Balanced Three Phase System

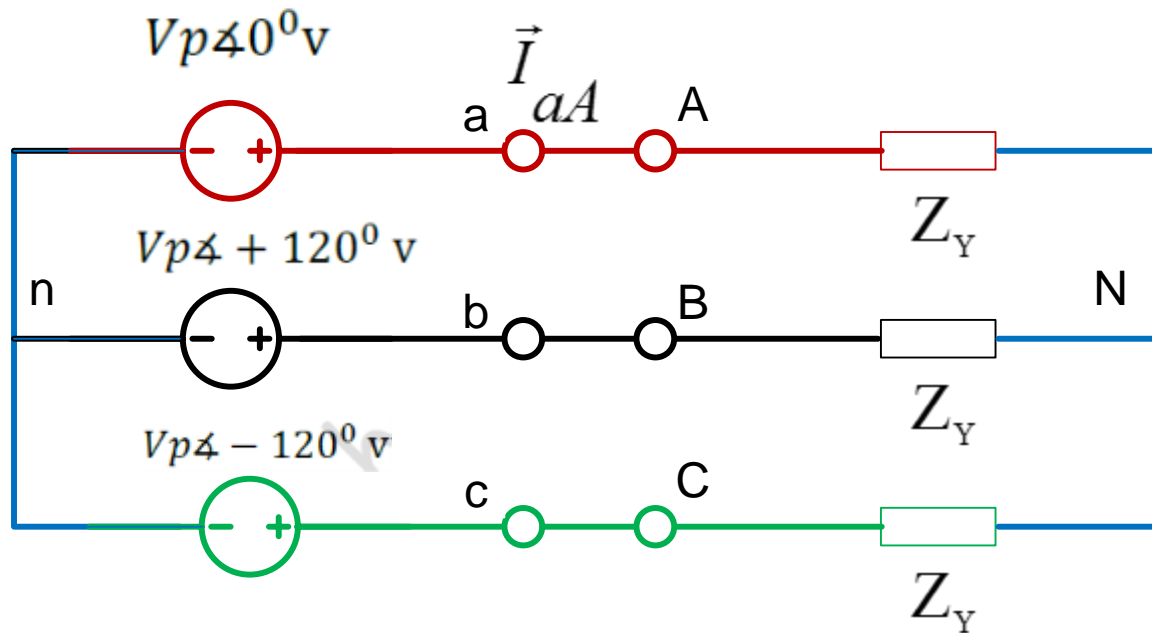

The total instantaneous power in a balanced three phase system is constant

$$\vec{V}_{AN}(t) = \sqrt{2}V_P \cos(\omega t)$$

$$\therefore \vec{V}_{BN}(t) = \sqrt{2}V_P \cos(\omega t - 120^\circ)$$

$$\therefore \vec{V}_{CN}(t) = \sqrt{2}V_P \cos(\omega t + 120^\circ)$$

$$\vec{i}_{aA}(t) = \sqrt{2} I_P \cos(\omega t - \theta)$$

$$\vec{i}_{bB}(t) = \sqrt{2} I_P \cos(\omega t - \theta - 120^\circ)$$

$$\vec{i}_{cC}(t) = \sqrt{2} I_P \cos(\omega t - \theta + 120^\circ)$$

$$P(t) = P_a(t) + P_b(t) + P_c(t)$$

$$P_a(t) = 2 V_P I_P \cos(\omega t) \cos(\omega t - \theta)$$

$$P_b(t) = 2 V_P I_P \cos(\omega t - 120^\circ) \cos(\omega t - \theta - 120^\circ)$$

$$P_c(t) = 2 V_P I_P \cos(\omega t + 120^\circ) \cos(\omega t - \theta + 120^\circ)$$

Using

$$\cos(\alpha) \cos(\beta) = \frac{1}{2} [\cos(\alpha + \beta) + \cos(\alpha - \beta)]$$

$$P(t) = V_P I_P [3 \cos(\theta)]$$

$$= 3 V_P I_P \cos(\theta)$$

Power Calculations in Balanced 3 Φ Systems

1) Average Power in Balanced Y load

$$P_A = V_{AN} I_{AN} \cos(\theta_{vA} - \Phi_{iA})$$


$$P_B = V_{BN} I_{BN} \cos(\theta_{vB} - \Phi_{iB})$$

$$P_C = V_{CN} I_{CN} \cos(\theta_{vC} - \Phi_{iC})$$

$$V_{AN} = V_{BN} = V_{CN} = V_{\Phi}$$

$$I_{AN} = I_{BN} = I_{CN} = I_{\Phi}$$
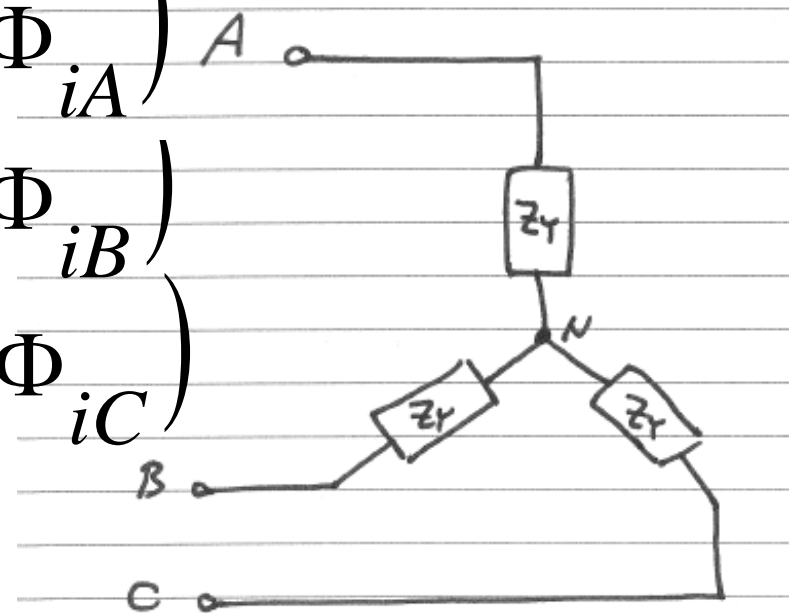
$$(\theta_{vA} - \Phi_{iA}) = (\theta_{vB} - \Phi_{iB}) = (\theta_{vC} - \Phi_{iC}) = \theta_{\Phi}$$



$$P_A = P_B = P_C = V_{\Phi} I_{\Phi} \cos(\theta_{\Phi})$$

$$P_T = 3V_{\Phi} I_{\Phi} \cos(\theta_{\Phi})$$

but

$$V_{\Phi} = \frac{V_L}{\sqrt{3}} \quad \& \quad I_{\Phi} = I_L$$

$$\begin{aligned} \therefore P_T &= 3 \frac{V_L}{\sqrt{3}} I_L \cos(\theta_{\Phi}) \\ &= \sqrt{3} V_L I_L \cos(\theta_{\Phi}) \end{aligned}$$

2) Reactive Power in balanced Y load

$$Q_A = Q_B = Q_C = V_{\Phi} I_{\Phi} \sin(\theta_{\Phi})$$

$$Q_T = 3V_{\Phi} I_{\Phi} \sin(\theta_{\Phi})$$

$$\therefore Q_T = \sqrt{3}V_L I_L \sin(\theta_{\Phi})$$

2) Complex Power in balanced Y load

$$\vec{S}_A = \vec{S}_B = \vec{S}_C = V_{\Phi} \vec{I}_{\Phi}^* = P_{\Phi} + jQ_{\Phi}$$

$$\therefore \vec{S}_T = 3\vec{S}_{\Phi} = 3\vec{V}_{\Phi} \vec{I}_{\Phi}^* = \sqrt{3}V_L I_L \angle \theta_{\Phi}$$

1) Average Power in Balanced Δ load

$$P_A = V_{AB} I_{AB} \cos\left(\theta_{v_{AB}} - \Phi_{i_{AB}}\right)$$


$$P_B = V_{BC} I_{BC} \cos\left(\theta_{v_{BC}} - \Phi_{i_{BC}}\right)$$

$$P_C = V_{CA} I_{CA} \cos\left(\theta_{v_{CA}} - \Phi_{i_{CA}}\right)$$

$$V_{AB} = V_{BC} = V_{CA} = V_{\Phi}$$

$$I_{AB} = I_{BC} = I_{CA} = I_{\Phi}$$
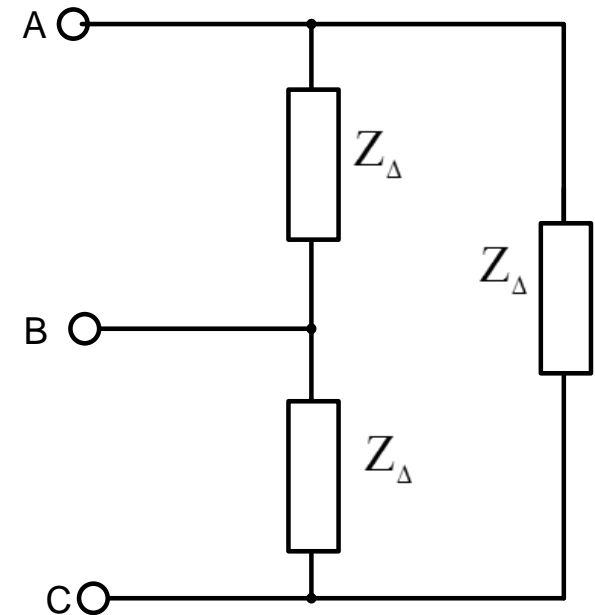
$$\left(\theta_{v_{AB}} - \Phi_{i_{AB}}\right) = \left(\theta_{v_{BC}} - \Phi_{i_{BC}}\right) = \left(\theta_{v_{CA}} - \Phi_{i_{CA}}\right) = \theta_{\phi}$$



$$P_A = P_B = P_C = V_{\Phi} I_{\Phi} \cos(\Phi)$$

$$P_T = 3V_{\Phi} I_{\Phi} \cos(\Phi)$$

but

$$V_{\Phi} = V_L \quad \& \quad I_{\Phi} = \frac{I_L}{\sqrt{3}}$$

$$\begin{aligned} \therefore P_T &= 3V_L \frac{I_L}{\sqrt{3}} \cos(\Phi) \\ &= \sqrt{3} V_L I_L \cos(\Phi) \end{aligned}$$

This is the same formula derived earlier for the Y connected circuit

Reactive Power in Balanced Δ load

$$Q_A = Q_B = Q_C = Q_\Phi = V_\Phi I_\Phi \sin(\theta_\Phi)$$

$$Q_T = 3V_\Phi I_\Phi \sin(\theta_\Phi)$$
$$= \sqrt{3}V_L I_L \sin(\theta_\Phi)$$


Complex Power in balanced Δ load

$$\vec{S}_A = \vec{S}_B = \vec{S}_C = V_\Phi I_\Phi^* = \vec{S}_\Phi = P_\Phi + jQ_\Phi$$

$$\therefore \vec{S}_T = 3\vec{S}_\Phi = 3\vec{V}_\Phi \vec{I}_\Phi^* = \sqrt{3}V_L I_L \angle \theta_\Phi$$

Comparing the Power Loss

a) A Single Phase System

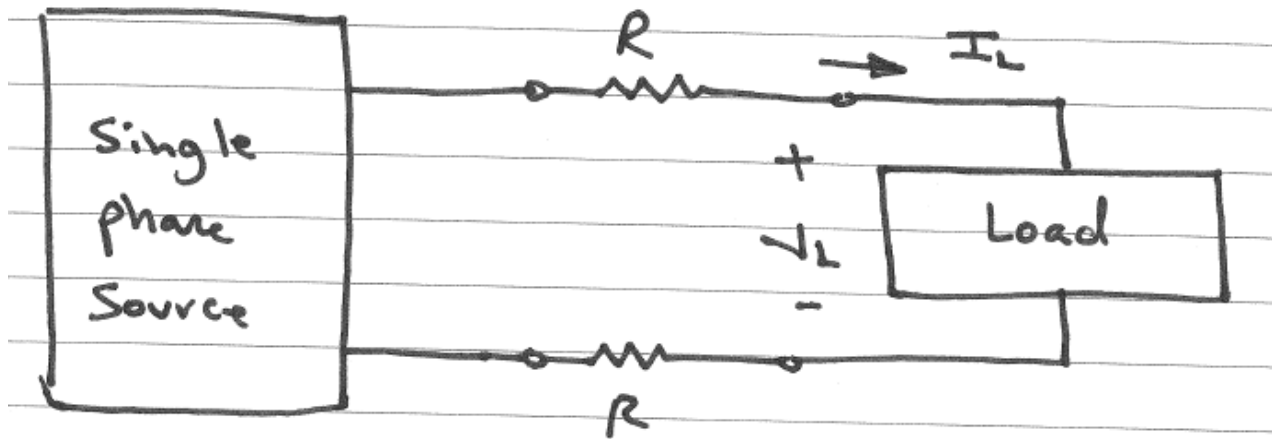

$$P_{\text{Loss}} = 2 I_L^2 \cdot R$$

$$I_L = \frac{P_L}{V_L \cdot \text{Pf}}$$

$$P_{\text{Loss}} = 2 \frac{P_L^2}{V_L^2 \cdot \text{Pf}^2} \cdot R$$



b) a three phase system

$$P_{\text{Loss}} = 3 I_L^2 \cdot R$$

$$I_L = \frac{P_L}{\sqrt{3} V_L \cdot \text{Pf}}$$

$$P_{\text{Loss}} = \frac{P_L^2}{V_L^2 \cdot \text{Pf}^2} \cdot R$$

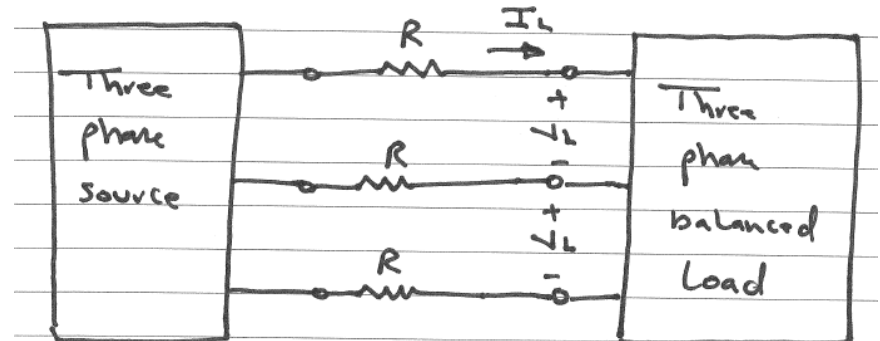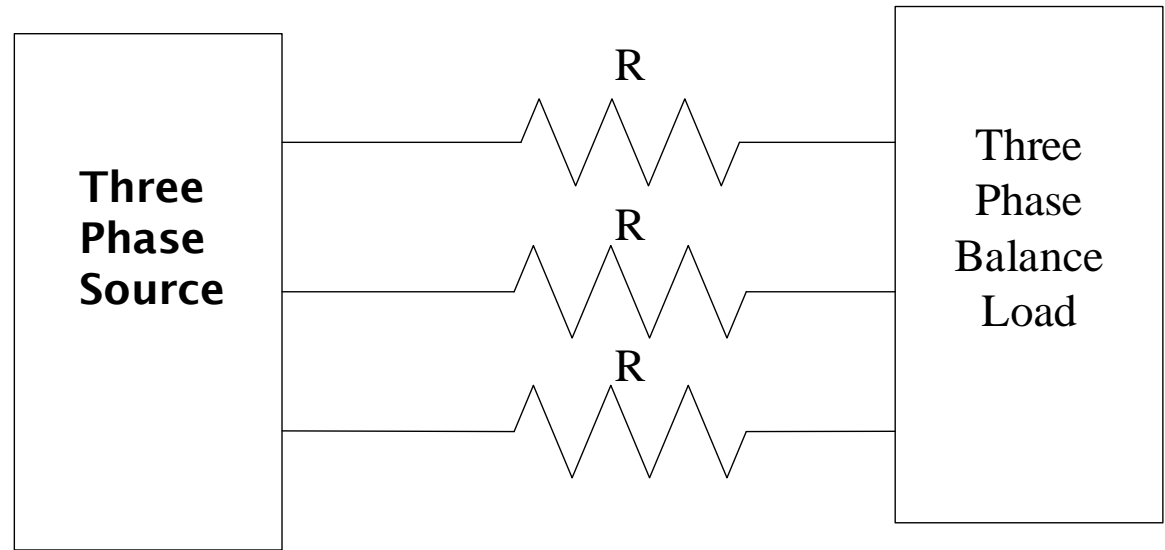
This proves that power loss is half power loss in single phase circuit



Example


- A balanced 3 Φ load requires 480 kW at a lagging power factor of 0.8. (Y-Y system)
- The load is fed from a line having an impedance of $(0.005 + j0.025) \Omega / \Phi$
- The line voltage at the terminal of the load is $600 V_{\text{rms}}$

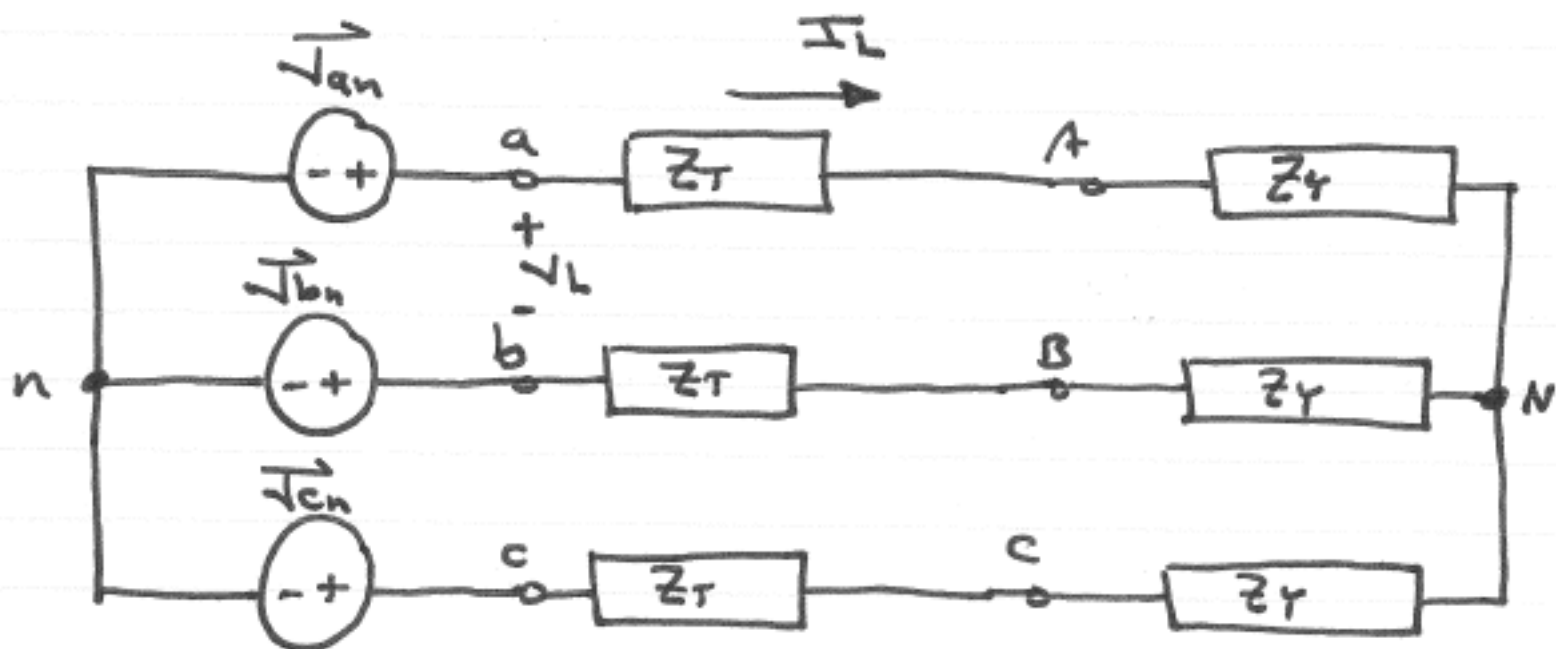- 1) Calculate The Magnitude of the line current
- 2) Calculate the magnitude of the line voltage at the sending end of the line
- 3) Calculate the power factor at the sending end of the line



Solution

- Single Phase Representation

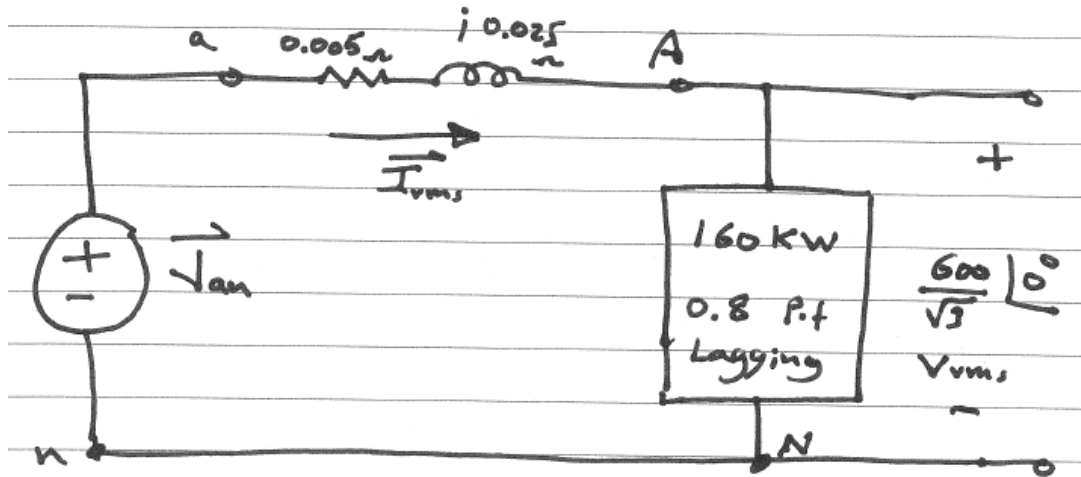

$$P_{av} = 160 \text{ kW}$$

$$Q = P_{av} \tan[\cos^{-1}(PF)]$$

$$= 120 \text{ kVAR}$$

$$\vec{S} = P_{av} + jQ$$

$$\vec{S} = 160 + j120 \text{ kVA}$$


$$\vec{S} = 160 + j120 \text{ kVA}$$

$$\vec{S} = \vec{V}_{rms} \cdot \vec{I}_{rms}^*$$

$$\therefore \vec{I}_{rms} = 577.35 \angle -36.87^\circ \text{ A}_{rms}$$

$$\therefore I_L = 577.35 \text{ Arms}$$
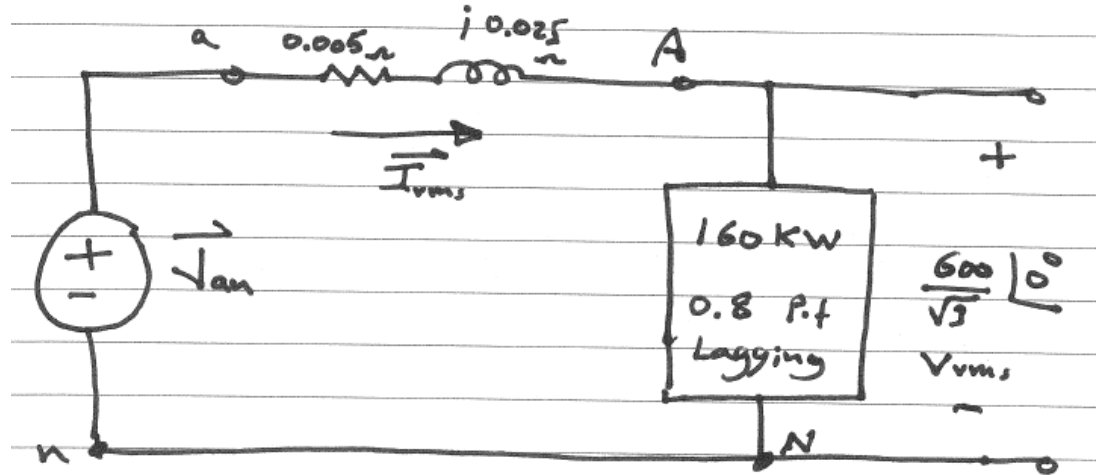
$$\vec{V}_{an} = (0.005 + j0.025) \vec{I}_{\text{rms}} + \frac{600}{\sqrt{3}} \angle 0^\circ$$



$$\vec{V}_{an} = 357.51 \angle 1.57^\circ \text{ V}_{\text{rms}}$$

$$\therefore V_{an} = 357.51 \text{ V}_{\text{rms}}$$

$$\therefore V_L = \sqrt{3} V_{an}$$

$$\therefore V_L = 619.23 \text{ V}_{\text{rms}}$$


$$Pf = \text{Cos} \left(\theta_v - \Phi_i \right)$$

$$Pf = \text{Cos} \left(1.57^\circ + 36.87^\circ \right)$$

$$Pf = 0.783 \text{ lagging}$$

Measuring Avg Power in 3- Φ System

The Two- Wattmeter Method

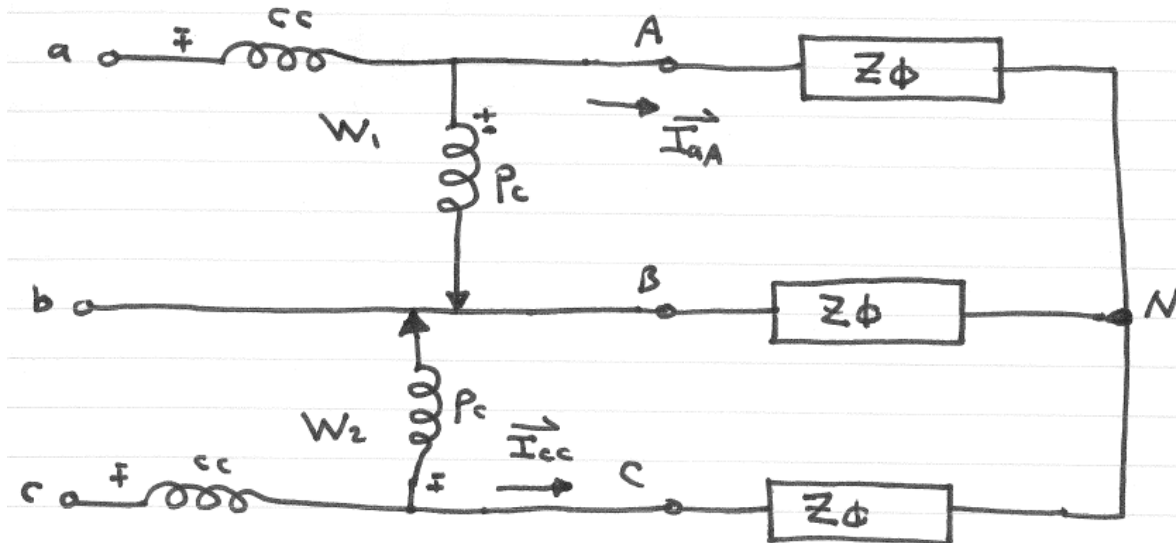

$$Z_{\phi} = |Z| \angle \theta_z; \theta_z \equiv \text{impedance angle}$$

$$W_1 = V_{AB} \cdot I_{aA} \cos \theta_1$$

$$\theta_1 \equiv \text{The angle between } \bar{V}_{AB} \text{ and } \bar{I}_{aA}$$


For a positive phase sequence:

$$\bar{V}_{AB} = \bar{V}_{AN}\sqrt{3}\angle 30^{\circ}$$

$$\bar{I}_{aA} = \bar{I}_{AN}$$

$$\therefore \theta_1 = \theta_Z + 30^{\circ}$$
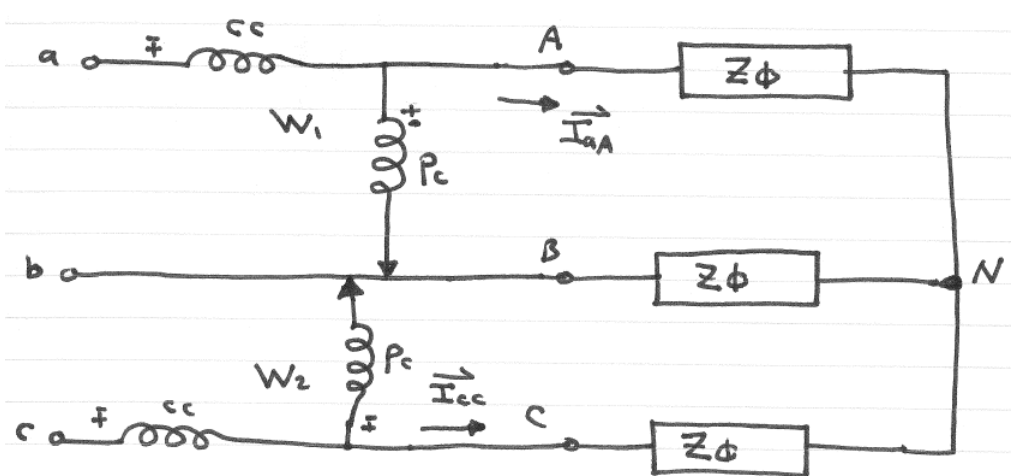
$$\therefore W_1 = V_L \cdot I_L \cos(\theta_Z + 30^{\circ})$$



$$W_2 = V_{CB} \cdot I_{cC} \cos \theta_2$$

$\theta_2 \equiv$ The angle between \bar{V}_{CB} and \bar{I}_{cC}

$$\therefore \theta_2 = \theta_Z - 30^\circ \quad \rightarrow \quad \text{Since we have } V_{CB} \text{ not } V_{BC}$$

$$\bar{V}_{CB} = -\bar{V}_{BC}$$

$$\bar{V}_{CB} = \bar{V}_{BC} \langle 180^\circ$$

$$\bar{V}_{CB} = \bar{V}_{CA} \langle -240^\circ \langle 180^\circ$$

$$\bar{V}_{CB} = \bar{V}_{CA} \langle -60^\circ$$

$$\bar{V}_{CB} = \bar{V}_{CA} \angle -60^\circ$$

$$\bar{V}_{CB} = \sqrt{3} \bar{V}_{CN} \angle +30^\circ \angle -60^\circ$$

$$\bar{V}_{CB} = \sqrt{3} \bar{V}_{CN} \angle -30^\circ$$

$$\bar{I}_{cC} = \bar{I}_{CN}$$

$$\therefore \theta_2 = \theta_Z - 30^\circ$$

$$\therefore W_2 = V_L \cdot I_L \cos(\theta_Z - 30^\circ)$$

$$W_1 = V_L \cdot I_L \cos(\theta_Z + 30^\circ)$$

$$W_2 = V_L \cdot I_L \cos(\theta_Z - 30^\circ)$$

$$P_T = W_1 + W_2$$

$$\cos(\theta_Z + 30^\circ) = \cos \theta_Z \cdot \cos 30^\circ - \sin \theta_Z \cdot \sin 30^\circ$$

$$\cos(\theta_Z - 30^\circ) = \cos \theta_Z \cdot \cos 30^\circ + \sin \theta_Z \cdot \sin 30^\circ$$

$$\therefore W_1 + W_2 = V_L \cdot I_L (2 \cos \theta_Z \cos 30^\circ)$$

$$W_1 + W_2 = \sqrt{3} V_L \cdot I_L (\cos \theta_Z)$$

This is the same expression as that for total power derived earlier

Example

Calculate the reading of each Wattmeter

if $\bar{V}_{AN} = 120 \angle 0^\circ$ $Z_\Phi = (8 + j6)\Omega$

- Solution

$$Z_\Phi = 10 \angle 36.87^\circ \Omega$$

$$\bar{I}_{aA} = \frac{120 \angle 0^\circ}{Z_\Phi} = 12 \angle -36.87^\circ \text{ A}_{\text{RMS}}$$

$$\text{a) } Z_{\Phi} = (8 + j6) \Omega \quad \theta_z = 36.87^{\circ}$$

$$I_L = 12 \text{ A}_{\text{rms}}$$

$$V_L = \sqrt{3}(120) \text{ V}_{\text{rms}}$$

$$W_1 = V_L \cdot I_L \cos(\theta_z + 30^{\circ})$$

$$\begin{aligned} W_1 &= \sqrt{3}(120) \cdot 12 \cdot \cos(36.87^{\circ} + 30^{\circ}) \\ &= 979.7 \text{ Watt} \end{aligned}$$

$$W_2 = V_L \cdot I_L \cos(\theta_z - 30^{\circ})$$

$$\begin{aligned} W_2 &= \sqrt{3}(120) \cdot 12 \cdot \cos(36.87^{\circ} - 30^{\circ}) \\ &= 2476.25 \text{ Watt} \end{aligned}$$

$$\text{b) } Z_{\Phi} = (8 - j6) \Omega \quad \theta_Z = -36.87^{\circ}$$

$$I_L = 12 \text{ A}_{\text{rms}}$$

$$V_L = \sqrt{3}(120) \text{ V}_{\text{rms}}$$

$$\begin{aligned} W_1 &= \sqrt{3}(120) \cdot 12 \cdot \text{Cos}(-36.87^{\circ} + 30^{\circ}) \\ &= 2476.25 \text{ Watt} \end{aligned}$$

$$\begin{aligned} W_2 &= \sqrt{3}(120) \cdot 12 \cdot \text{Cos}(-36.87^{\circ} - 30^{\circ}) \\ &= 979.75 \text{ Watt} \end{aligned}$$

$$c) \quad Z_{\Phi} = (5 + j5\sqrt{3})\Omega = 10 \angle 60^{\circ} \quad \theta_Z = 60^{\circ}$$

$$I_L = 12 \text{ A}_{\text{rms}}$$


$$V_L = \sqrt{3}(120) \text{ V}_{\text{rms}}$$

$$\begin{aligned} W_1 &= \sqrt{3}(120) \cdot 12 \cdot \text{Cos}(60^{\circ} + 30^{\circ}) \\ &= 0 \text{ Watt} \end{aligned}$$


$$\begin{aligned} W_2 &= \sqrt{3}(120) \cdot 12 \cdot \text{Cos}(60^{\circ} - 30^{\circ}) \\ &= 2160 \text{ Watt} \end{aligned}$$

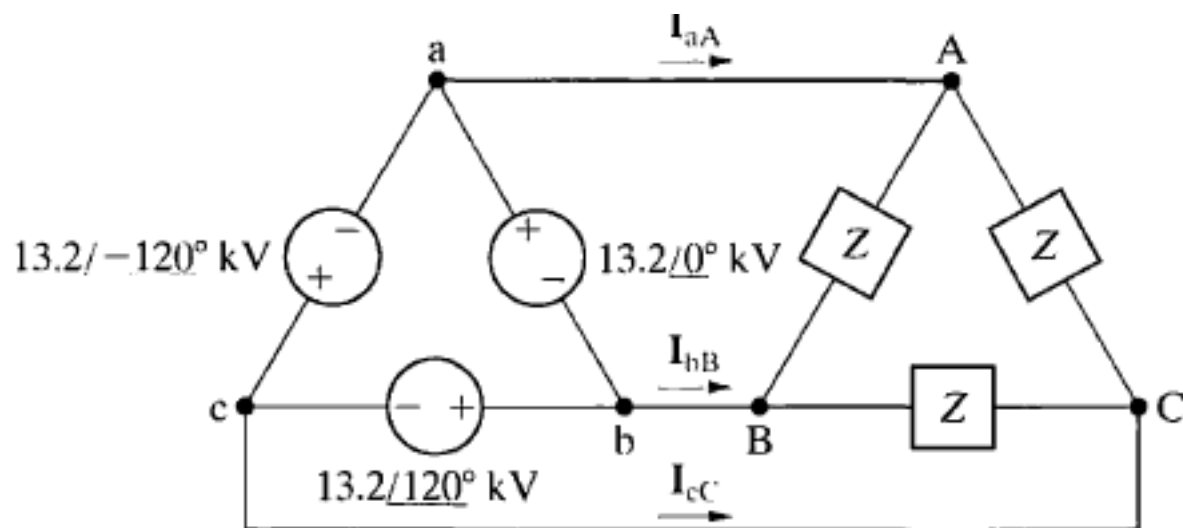11.17 The impedance Z in the balanced three-phase circuit in Fig. P11.17 is $100 - j75 \Omega$. Find

- \mathbf{I}_{AB} , \mathbf{I}_{BC} , and \mathbf{I}_{CA} ,
- \mathbf{I}_{aA} , \mathbf{I}_{bB} , and \mathbf{I}_{cC} ,
- \mathbf{I}_{ba} , \mathbf{I}_{cb} , and \mathbf{I}_{ac} .



$I_{AB}??$

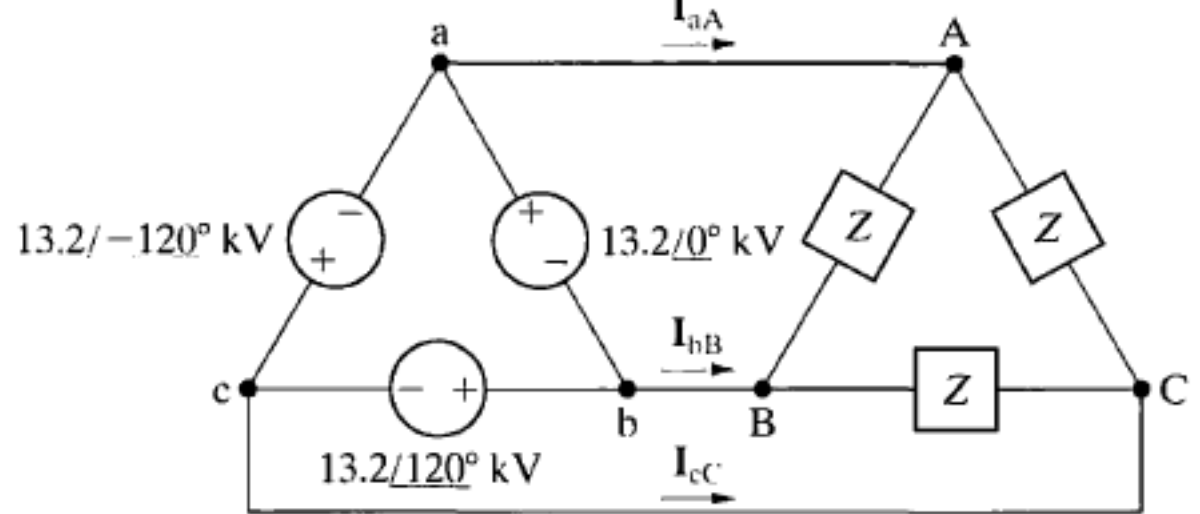

$$[a] \quad I_{AB} = \frac{13,200/0^\circ}{100 - j75} = 105.6/\underline{36.87^\circ} \text{ A (rms)}$$

$$I_{BC} = 105.6/\underline{156.87^\circ} \text{ A (rms)}$$

$$I_{CA} = 105.6/\underline{-83.13^\circ} \text{ A (rms)}$$

$$[b] \mathbf{I}_{aA} = \sqrt{3} \angle -30^\circ \mathbf{I}_{AB} = 182.9 \angle 66.87^\circ \text{ A (rms)}$$

$$\mathbf{I}_{bB} = 182.9 \angle -173.13^\circ \text{ A (rms)}$$

$$\mathbf{I}_{cC} = 182.9 \angle -53.13^\circ \text{ A (rms)}$$

$$[c] \mathbf{I}_{ba} = \mathbf{I}_{AB} = 105.6 \angle 36.87^\circ \text{ A (rms)}$$

$$\mathbf{I}_{cb} = \mathbf{I}_{BC} = 105.6 \angle 156.87^\circ \text{ A (rms)}$$

$$\mathbf{I}_{ac} = \mathbf{I}_{CA} = 105.6 \angle -83.13^\circ \text{ A (rms)}$$

