

ENEE2301

**Network Reduction Techniques
and Network Theorems 2**

Ch4

Reading Assignment: Sections 4.9 - 4.16, in *Electric Circuits, 10th Ed.* by Nilsson

Network Reduction Techniques and Network Theorems

Chapter 4, Sections 9-16, in the text by Nilsson covers several useful network reduction techniques and network theorems.

The purposes of these techniques and theorems are:

- To provide alternate analysis methods
- To provide methods for simplifying circuits
- To provide methods for representing circuits in the simplest possible form
- To gain insight into circuit behavior

Topics to be covered


- Source Transformations
- Superposition
- Thevenin's and Norton's Theorems
- Maximum Power Transfer Theorem

Thevenin's & Norton's Theorems

Any one-port network N may be represented by either of the following types of equivalent circuits:

Thevenin Equivalent Circuit (TEC) – consisting of a voltage source and a series impedance

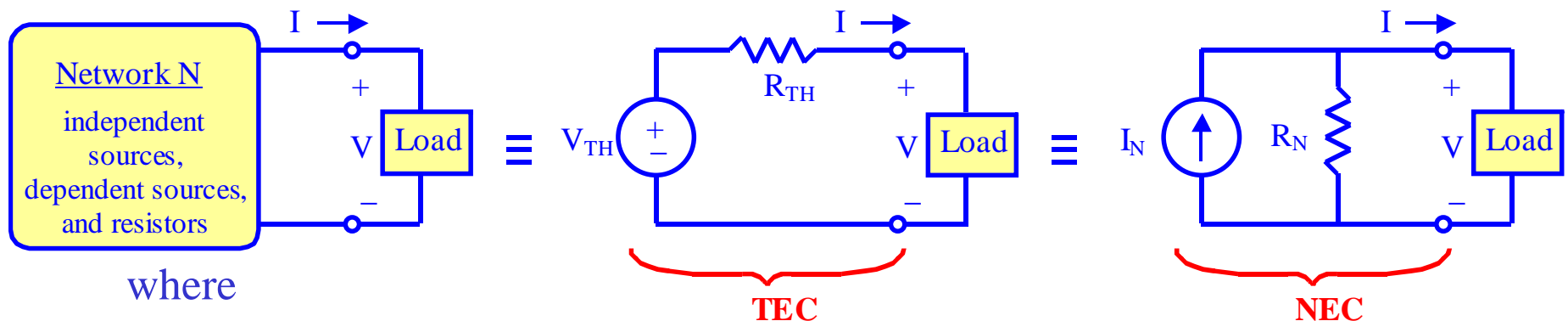
Norton Equivalent Circuit (NEC) – consisting of a current source and a parallel impedance



$V_{TH} = V_{OC} =$ Thevenin voltage or open-circuit voltage


$I_N = I_{SC} =$ Norton current or short-circuit current

$R_{TH} = R_N =$ Thevenin or Norton resistance $= \frac{V_{OC}}{I_{SC}} = R_{EQ} \Big|_{\text{Seen by the load with independent sources killed}}$

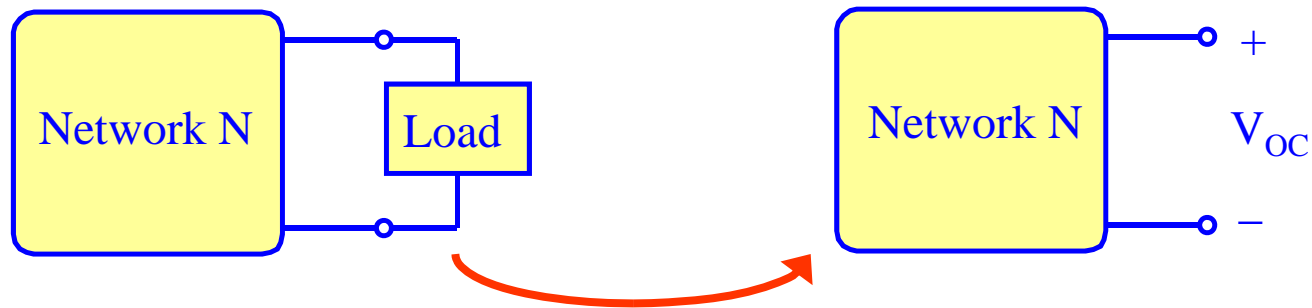Illustration of V_{OC} and I_{SC} :

Remove the load and the voltage across the open terminals is V_{OC}
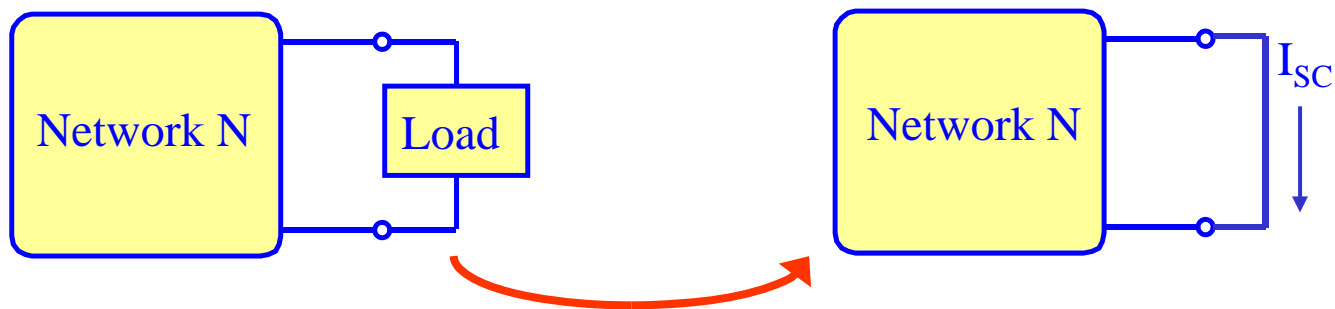
$$V_{TH} = V_{OC} = \text{Thevenin voltage or open-circuit voltage}$$



Replace the load by a short circuit (wire) and the current through the short is I_{SC}

$$I_N = I_{SC} = \text{Norton current or short-circuit current}$$

There are 3 ways to find the TEC or NEC for a given circuit:

Examples using each of the three methods will be provided on the following pages.

- 1) Reduce the circuit into the form of a TEC or NEC using source transformations
 - Not possible with dependent sources, though a partial reduction may be useful
 - Recall that not all sources are transformable

- 2) Find V_{oc} or I_{sc} . Also find $R_{Th} = R_{eq}$ Seen by the load with independent sources killed
 - For a simple circuit, this can often be done by combining series & parallel R's.
 - If the circuit has dependent sources, R_{Th} can be found by adding an external voltage or current source (any value) to the output terminals and by finding :

$$R_{Th} = \frac{V_T}{I_T} = \frac{\text{Terminal voltage}}{\text{Terminal current}}$$


- 3) Find V_{oc} and I_{sc} . Also calculate $R_{Th} = \frac{V_{oc}}{I_{sc}}$. This is the most general method and is probably the best choice for circuits with dependent sources.

Finding Thevenin resistance by adding external sources


As indicated in Method 2 for finding a TEC or NEC, R_{TH} can also be found as follows:

$$R_{th} = \frac{\text{terminal voltage}}{\text{terminal current}} \quad \text{With independent sources killed}$$

Discussion: If the dead circuit really acts like a resistor (R_{TH}), then we can add any voltage source across the circuit (resistor), solve for the current, and use Ohm's Law to find R_{TH} . Similarly, we can add any value current source and solve for the voltage. This technique is illustrated below.

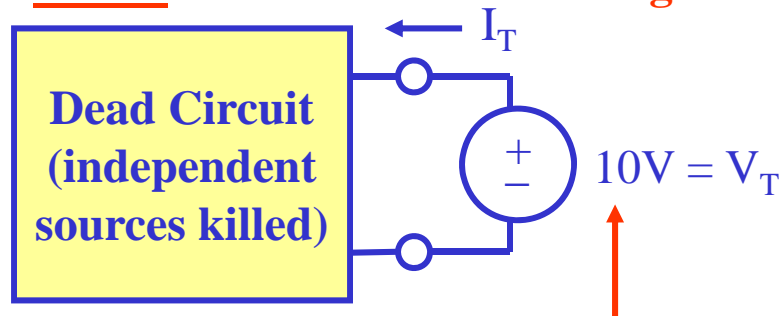Case 1: Add an external voltage source



Add any value of voltage source and solve for I_T

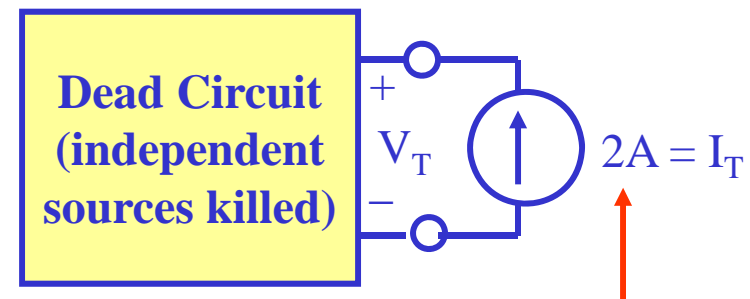Case 2: Add an external current source


Add any value of current source and solve for V_T

In either case above, calculate $R_{th} = \frac{V_T}{I_T} = \frac{\text{terminal voltage}}{\text{terminal current}}$

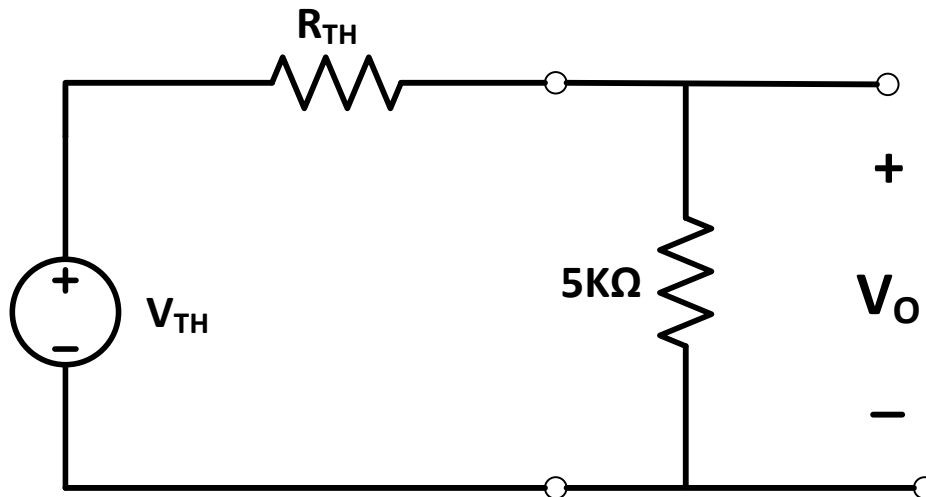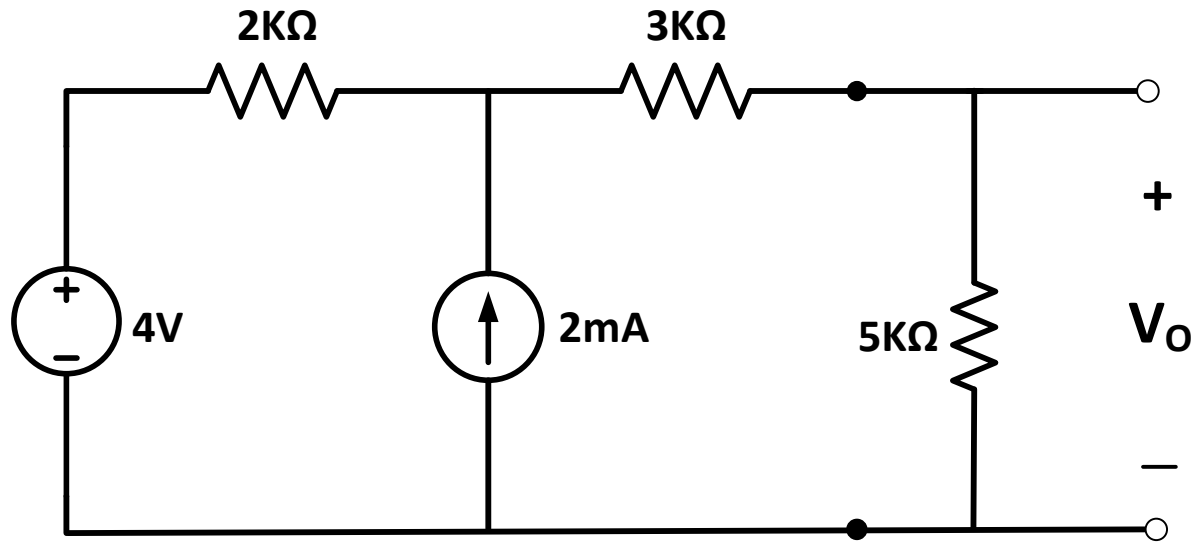Example: Find V_o using Thevenin's Theorem




1) To find V_{Th} :

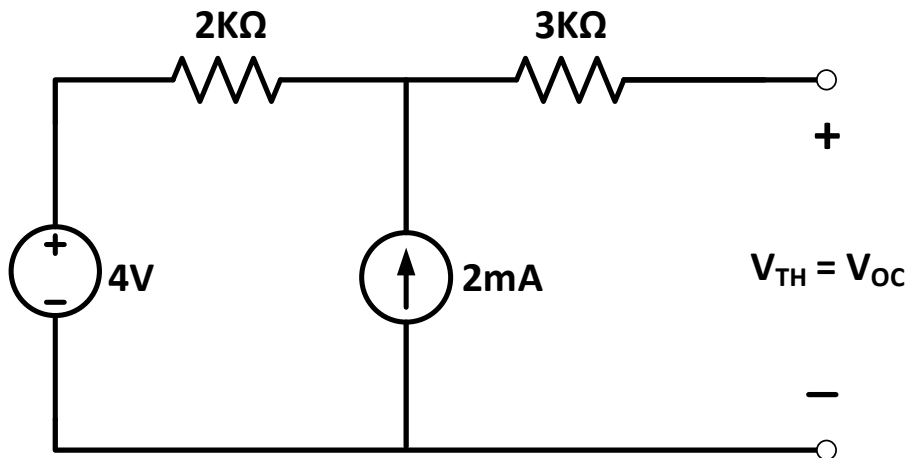


$$V_{Th} = [(2K)(2mA)] + 4 = 8V$$

2) To find R_{Th} :

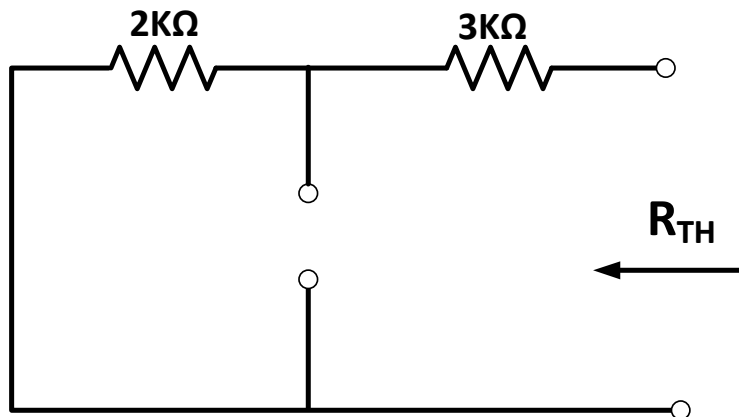



$$R_{Th} = 3K\Omega + 2K\Omega = 5K\Omega$$

3) To find V_o :

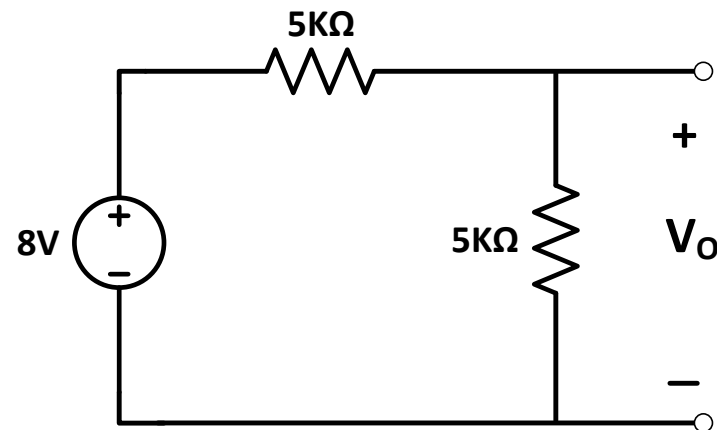

$$V_o = \frac{5}{5+5} * 8 = 4V$$


Example: Find V_o using Norton's Theorem

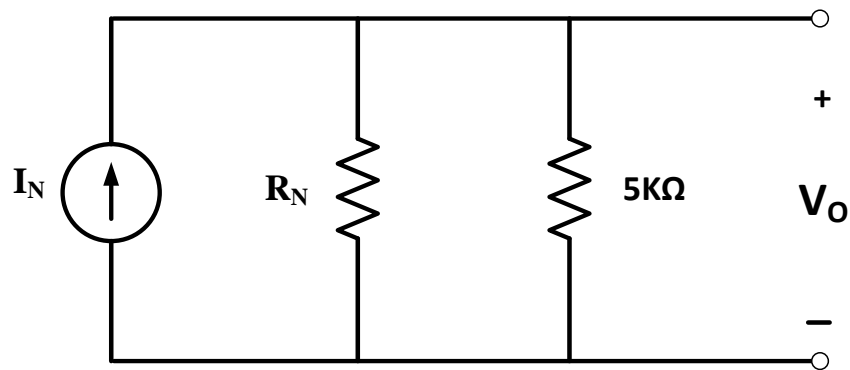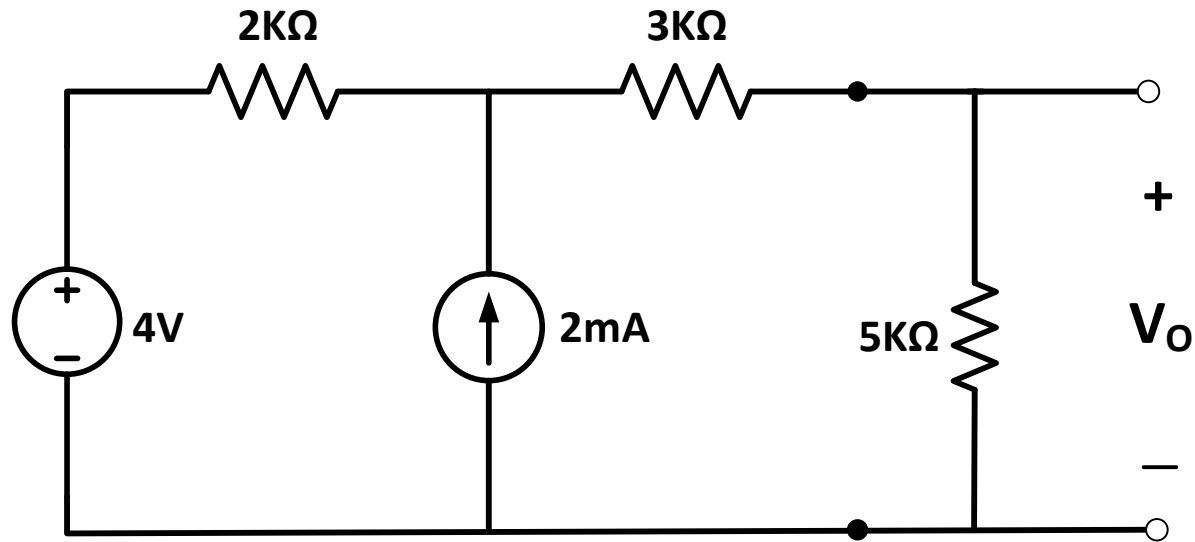


$$V_o = (R_N // 5K\Omega) I_N$$

1) To find I_N :

$$I_N = I_{sc}$$

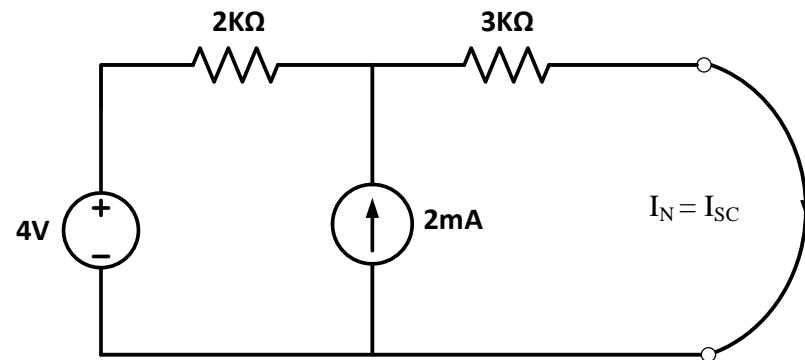

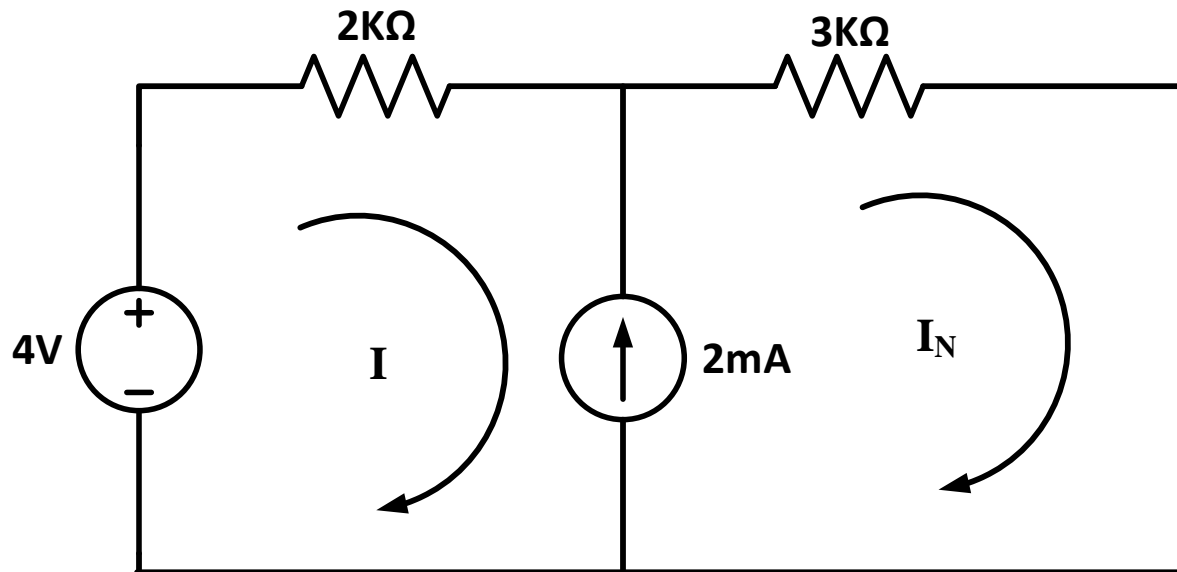


$$2mA = I_N - I \quad \dots\dots\dots \text{Constraint equation}$$

$$4 = (2K) I + (3K) I_N \quad \dots\dots\dots \text{Supermesh equation}$$

$$\therefore I_N = 1.6 mA$$


2) To find $R_N = R_{Th}$

Turn off all the independent sources

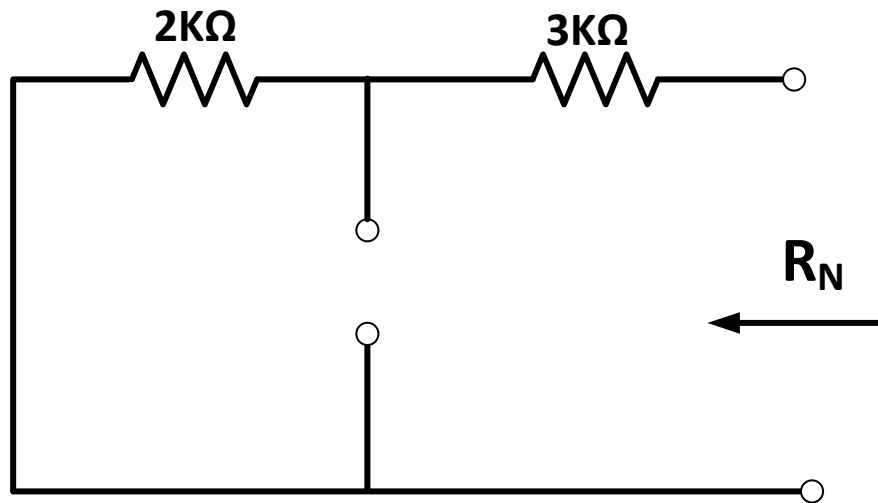

$$R_N = 3K\Omega + 2K\Omega = 5K\Omega$$


3) To find V_O

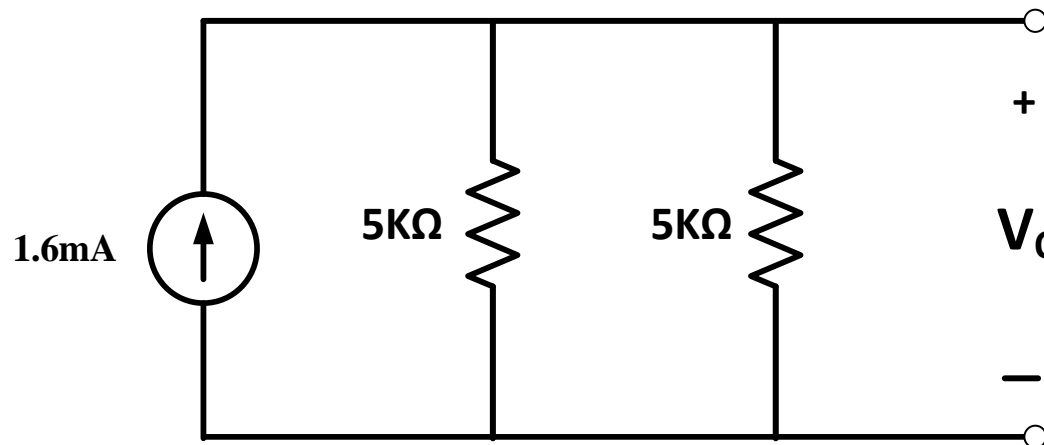


$$V_O = (5K\Omega // 5K\Omega) (1.6 mA)$$

$$V_O = 4 V$$


Find V_o using Thevenin's theorem

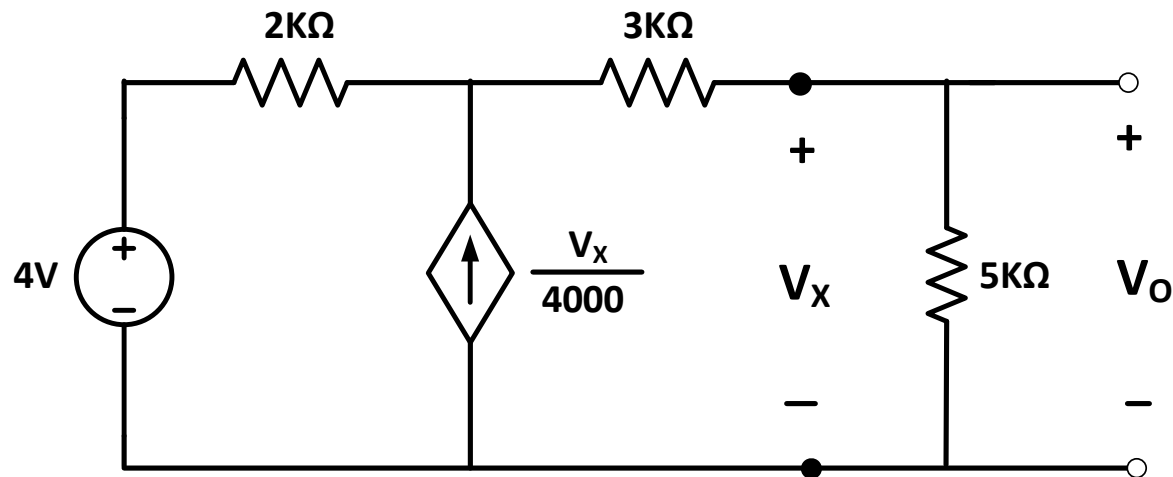

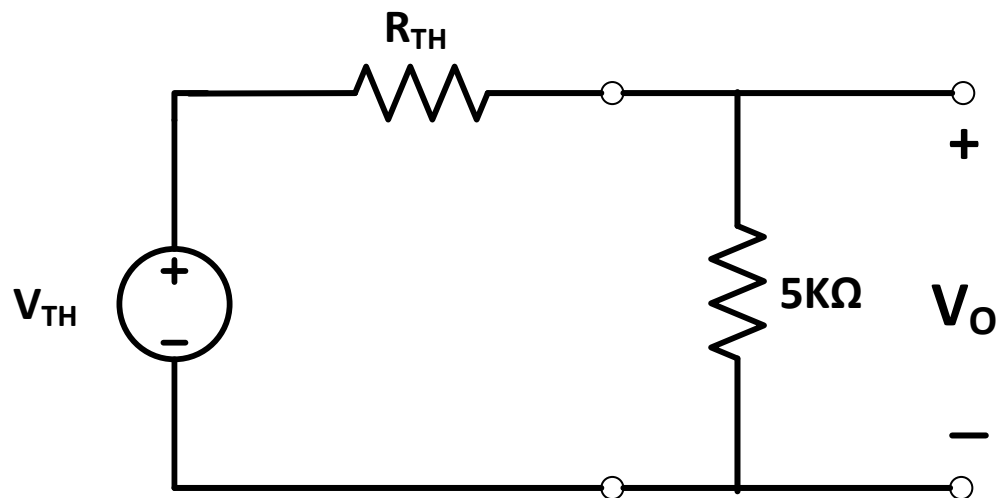After finding TEC and putting back the 5kohm load ,
the circuit will be:



1) To find V_{Th}

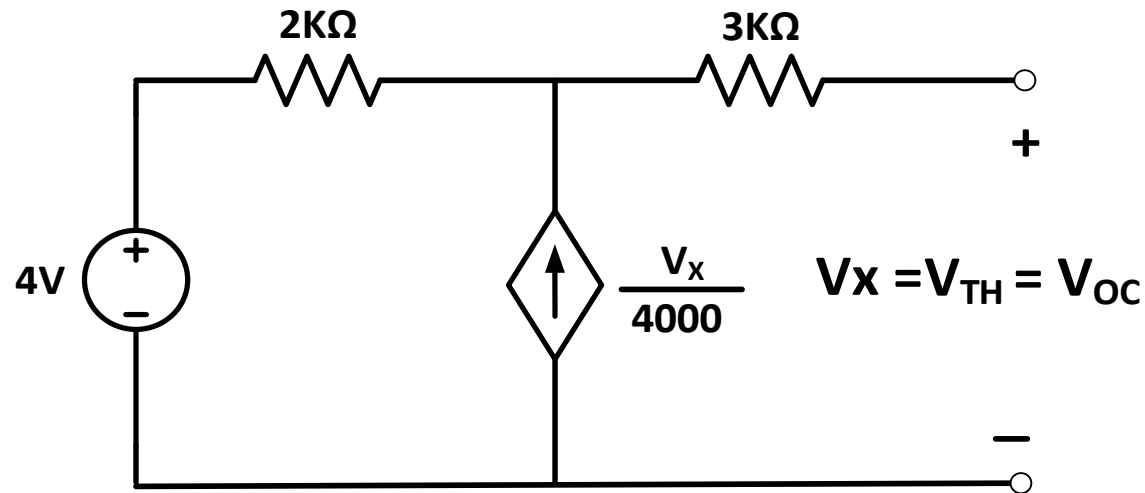


$$V_{Th} = (2K) \left(\frac{V_x}{4000} \right) + 4 \quad \leftarrow \text{Note that current through the 3 kohm Is equal to zero (open circuit)}$$

$$V_x = V_{Th}$$


$$\therefore V_{Th} = 8 V$$

1) To find R_{Th}

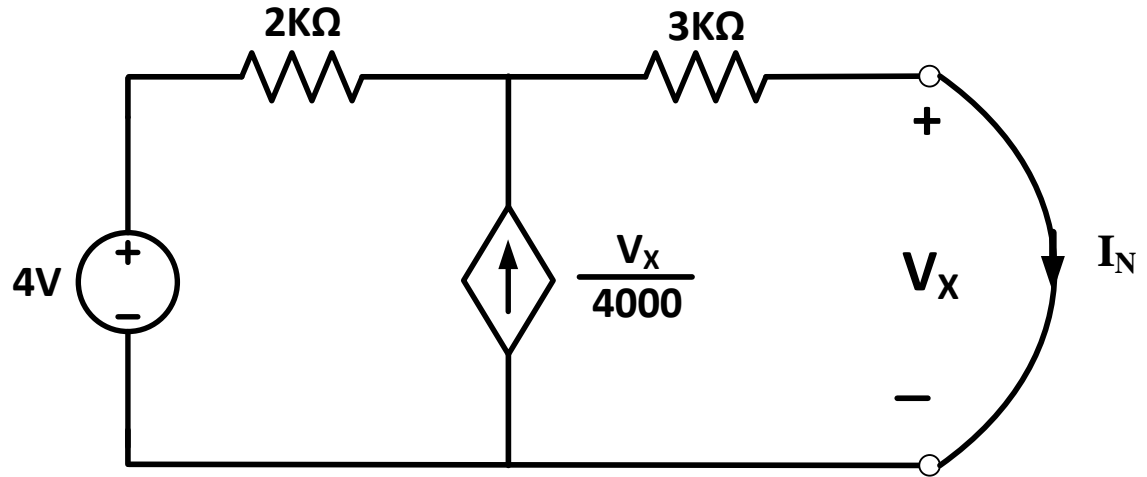a) Method 1: $R_{Th} = \frac{V_{Th}}{I_N}$


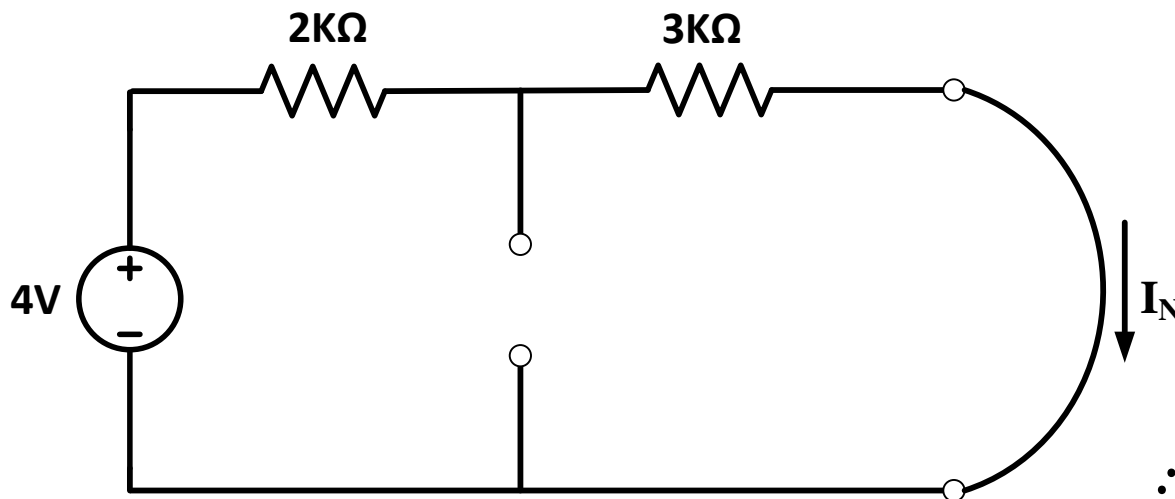
$$V_x = 0 \quad \longrightarrow \quad \frac{V_x}{4000} = 0 \quad \longrightarrow \quad \text{Open circuit.}$$





$$I_N = \frac{4V}{5K\Omega} = 0.8mA$$

$$\therefore R_{Th} = \frac{8V}{0.8mA} = 10K\Omega$$

Method 2: $R_{Th} = V_T / I_T$

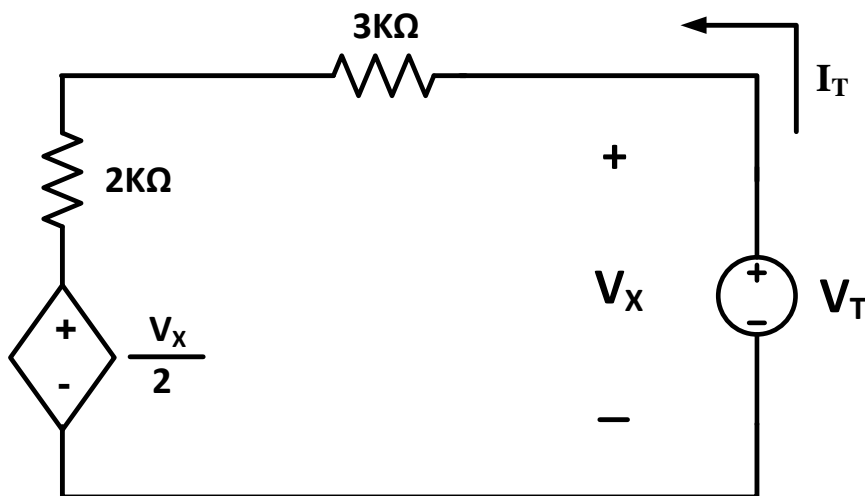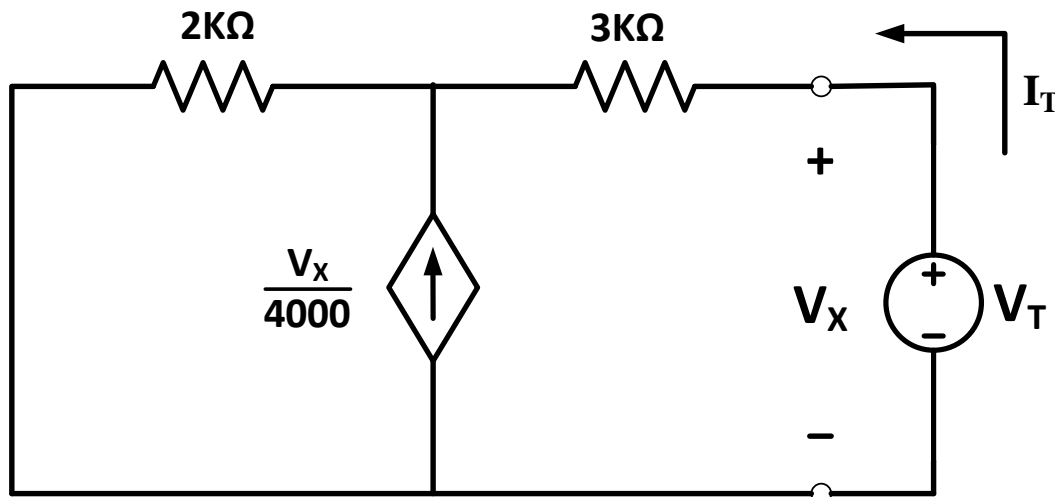while All independent sources set to zero




$$-V_T + 3K I_T + 2K I_T + \frac{V_x}{2} = 0$$

$$V_x = V_T$$

$$\therefore R_{Th} = \frac{V_T}{I_T} = 10 K\Omega$$


Equivalent Circuit

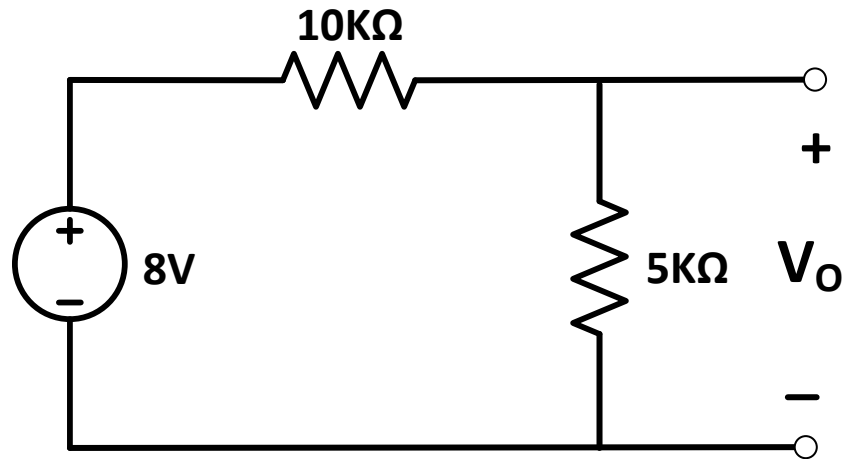


$$V_O = \frac{5K}{5K + 10K} (8V)$$

$$V_O = \frac{8}{3} V$$

Find I_x using Thevenin's theorem

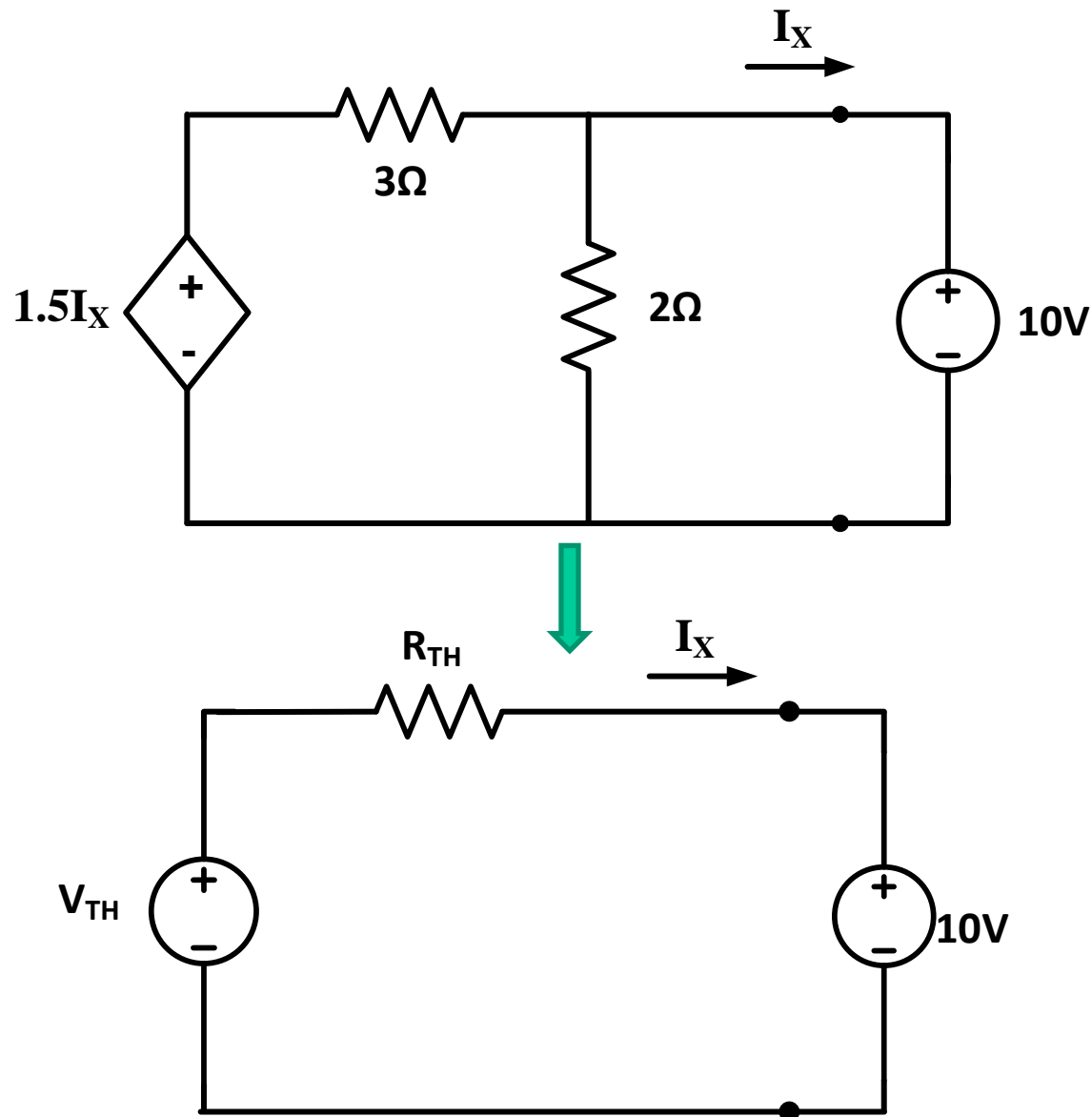



1) To find V_{Th}

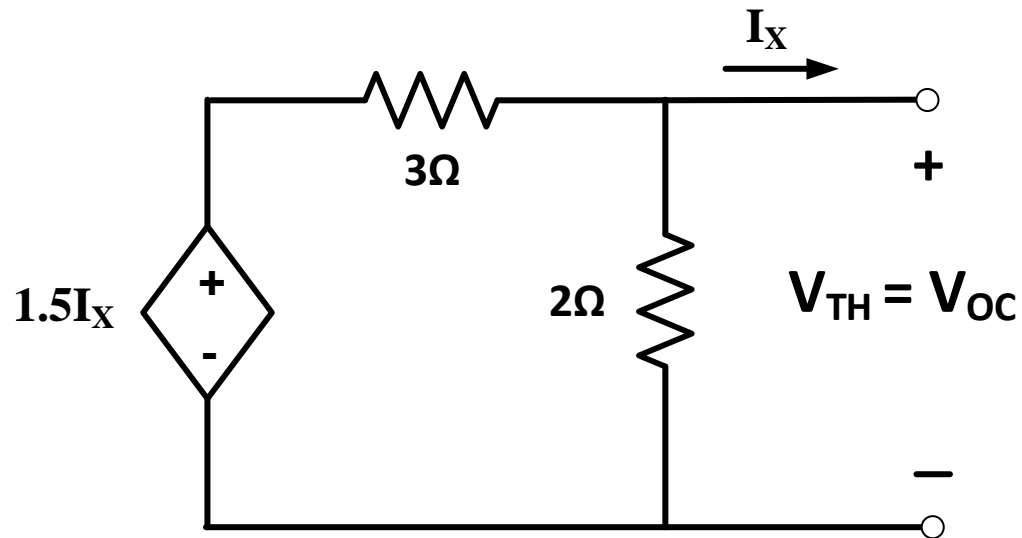

Since there is no independent sources

$$\therefore V_{Th} = 0$$

2) To find R_{Th} : $\frac{V_T}{I_T}$

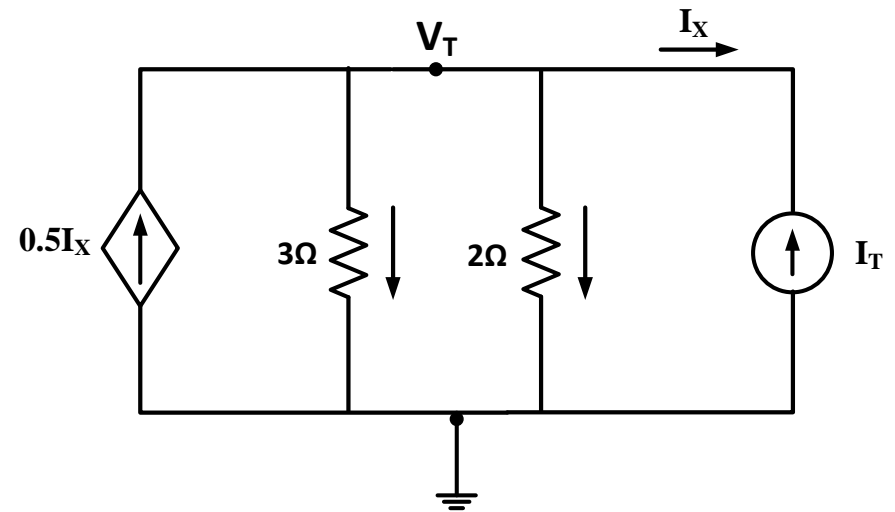
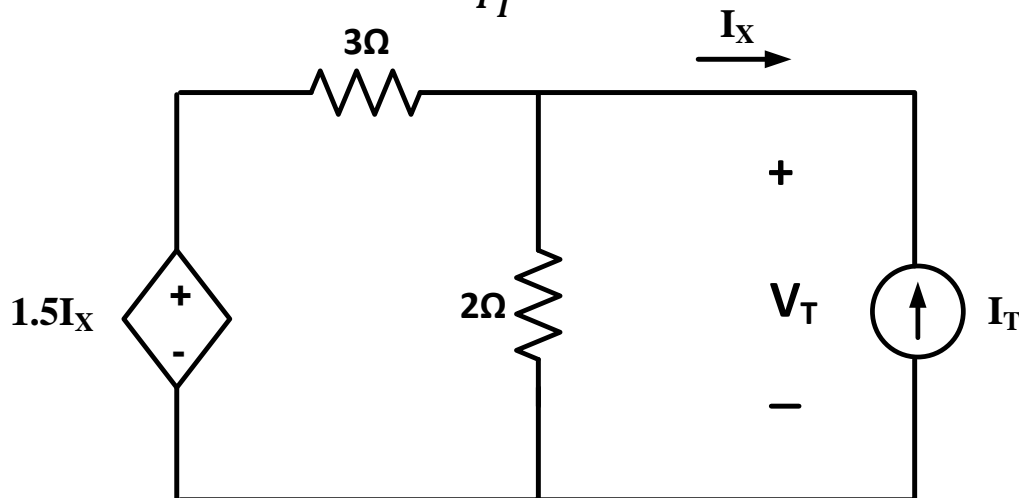


KCL

$$0.5 I_X + I_T = \frac{V_T}{3} + \frac{V_T}{2}$$

$$I_X = -I_T$$

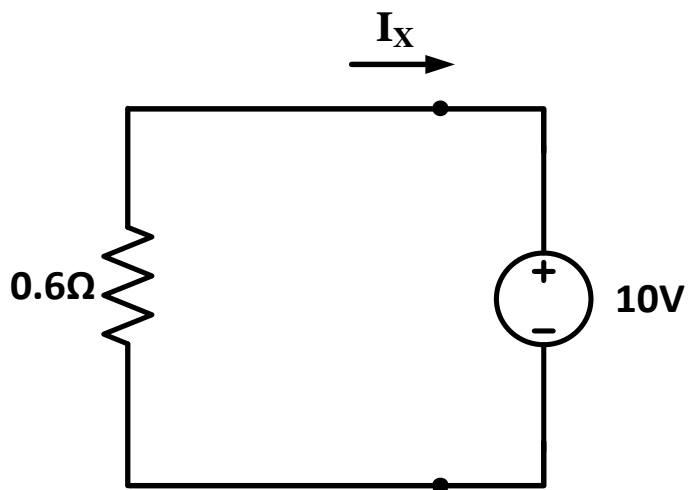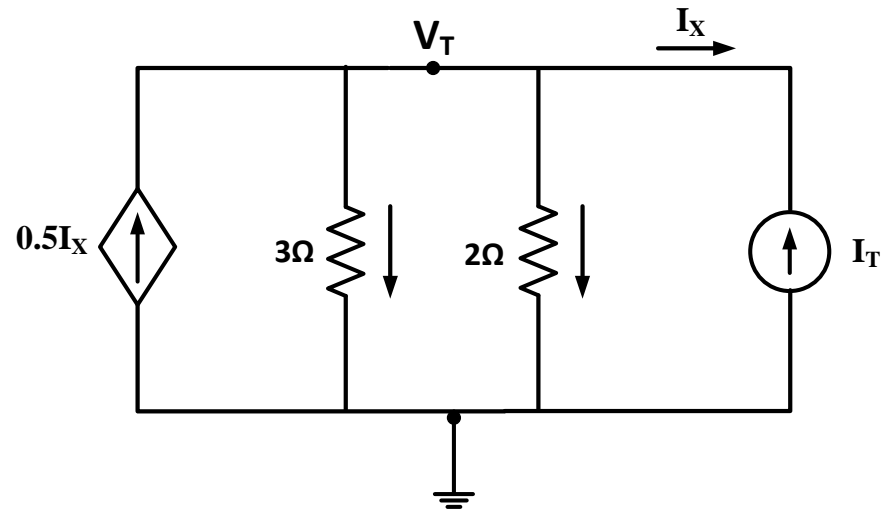
$$\therefore R_{Th} = \frac{V_T}{I_T} = 0.6 \Omega$$



$$I_X = -\frac{10}{0.6} = -16.67 \text{ A}$$

Assessment 4.18

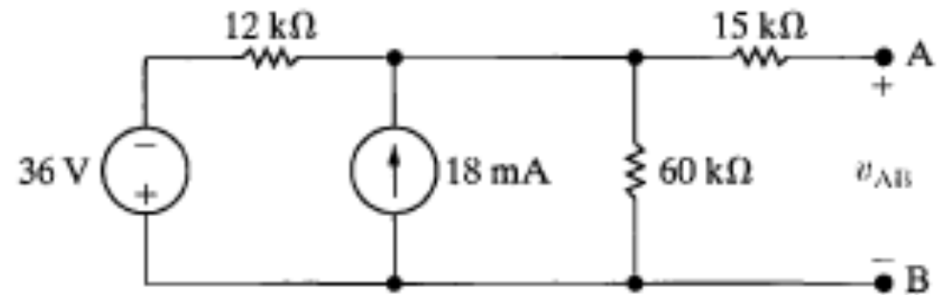
A voltmeter with an internal resistance of $100\text{ k}\Omega$ is used to measure the voltage v_{AB} in the circuit shown. What is the voltmeter reading?




Answer: 120 V.

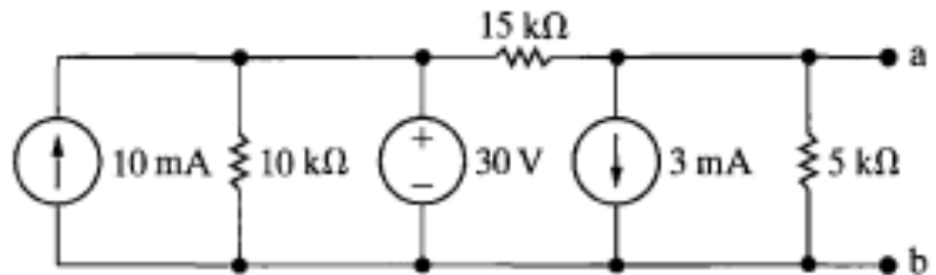Problem 4.64

Find the Norton equivalent with respect to the terminals a,b




Answer

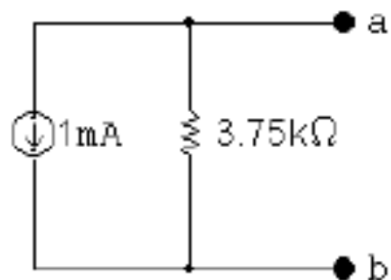

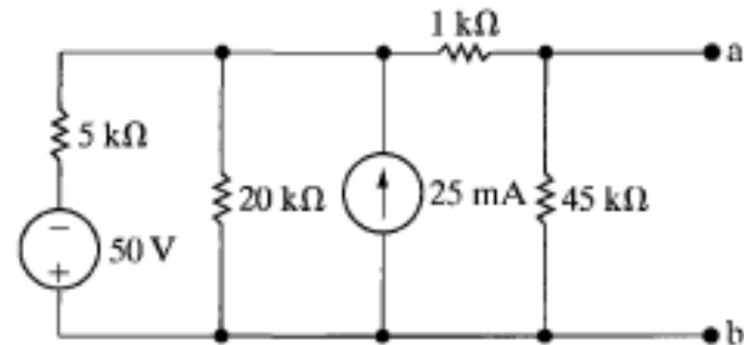Problem 4.71


A voltmeter with a resistance of $85.5 \text{ k}\Omega$ is used to measure the voltage v_{ab} in the circuit. What is the voltmeter reading?



Answer $\therefore v_{Th} = 54 \text{ V} \quad R_{Th} = 4.5 \text{ k}\Omega$

Maximum Power Transfer Theorem

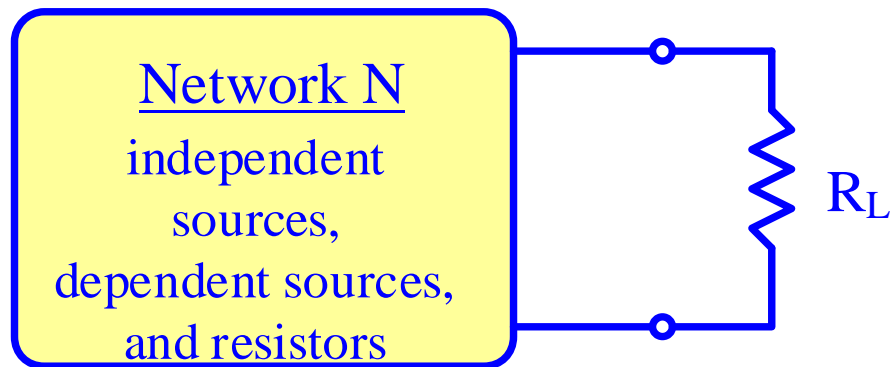Suppose that a general network N has a resistive load as shown below.



Now we might consider two questions:

- For what value of R_L is maximum power delivered to R_L ?
- What is the maximum power that can be delivered to R_L ?


To answer these questions (see next page),

- 1) Replace N by a Thevenin Equivalent Circuit
- 2) Determine a general expression for power to R_L
- 3) Solve $\frac{dP_L}{dR_L} = 0$ to find where P_L is maximum

Maximum Power Transfer Theorem

Show that: $R_L = R_{th}$ for maximum power

$$P_{\max} = \frac{V_{th}^2}{4R_{th}}$$

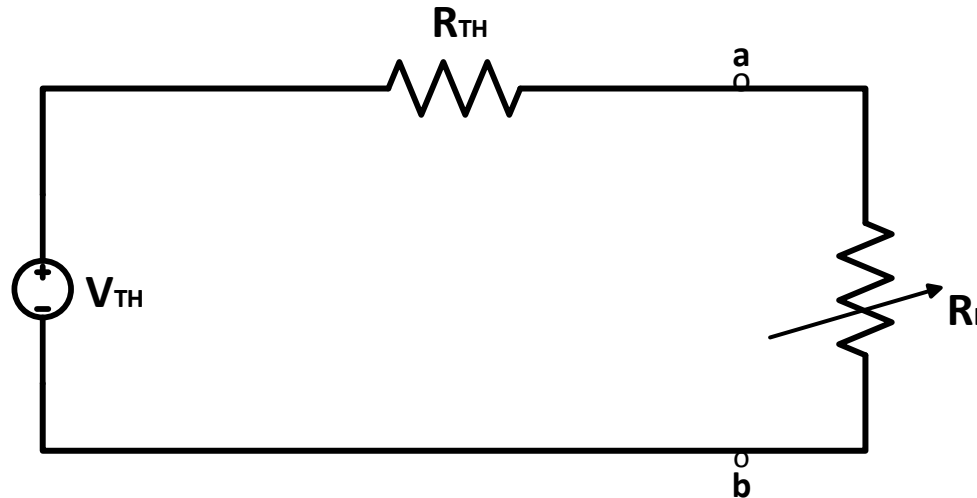


A load resistance will receive maximum power from a circuit when the resistance of the load is exactly the same as the Thevenin's resistance looking back at the circuit .

$$R_L = R_{TH}$$

$$P_L = \frac{V_L^2}{R_L}$$

$$V_L = \frac{R_L}{R_L + R_{TH}} \cdot V_{TH}$$

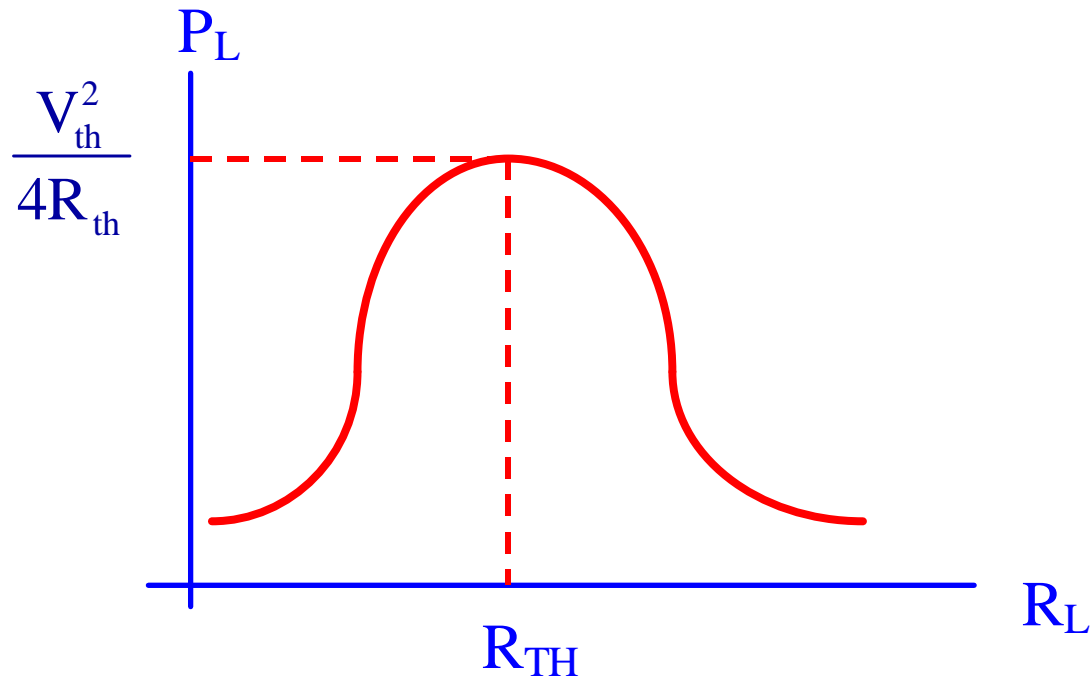The relationship between P_L and R_L can be illustrated by the graph shown below.



$$P_L = \frac{V_{TH}^2 \cdot R_L}{(R_L + R_{TH})^2}$$

$$\frac{\partial P_L}{\partial R_L} = \frac{V_{TH}^2 [(R_L + R_{TH})^2 - 2R_L(R_L + R_{TH})]}{(R_{TH} + R_L)^4}$$

$$\frac{\partial P_L}{\partial R_L} = 0$$

$$(R_L + R_{TH})^2 - 2R_L(R_L + R_{TH}) = 0$$

$$(R_L + R_{TH})[(R_L + R_{TH}) - 2R_L] = 0$$


$$\therefore R_{TH} - R_L = 0$$

$$\therefore R_L = R_{TH}$$


$$P_{L,max} = \frac{V_{TH}^2}{4 R_L} = \frac{V_{TH}^2}{4 R_{TH}}$$

Find the value of R_L for maximum power transfer in the circuit shown .

Find the maximum power .

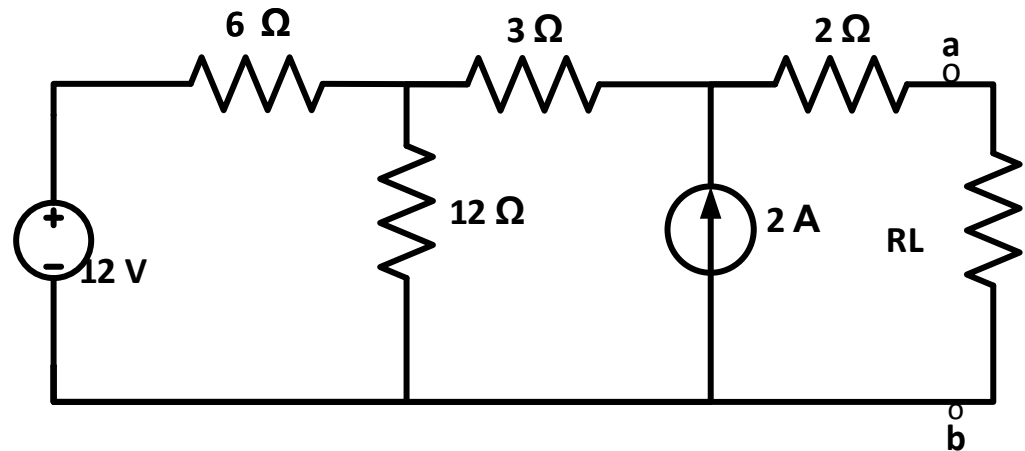

To find V_{TH}

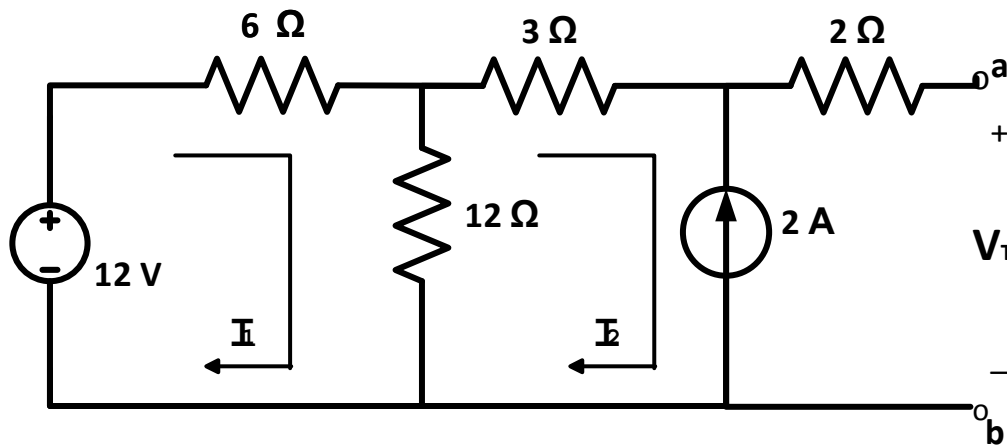

$$I_2 = -2 \text{ A} \quad \text{constrain equation}$$


$$12 = 18 I_1 - 12 I_2$$

$$\therefore I_1 = -\frac{2}{3} \text{ A}$$

$$V_{TH} = -3 I_2 - 6 I_1 + 12$$

$$\therefore V_{TH} = 22 \text{ V}$$

To find R_{TH}

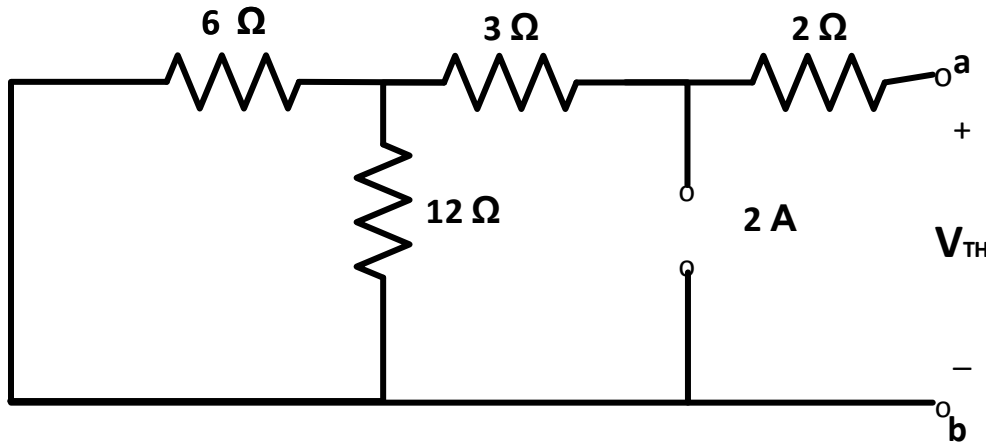


$$\begin{aligned} R_{TH} &= 2 + 3 + 6||12 \\ &= 2 + 3 + 4 \\ &= 9\ \Omega \end{aligned}$$

$$\therefore R_L = R_{TH} = 9\ \Omega$$


$$\therefore P_{L,max} = \frac{V_{TH}^2}{4 R_{TH}} = 13.44\ \text{W}$$

Find the value of R_L for maximum power transfer in the circuit shown .

Find the maximum power .

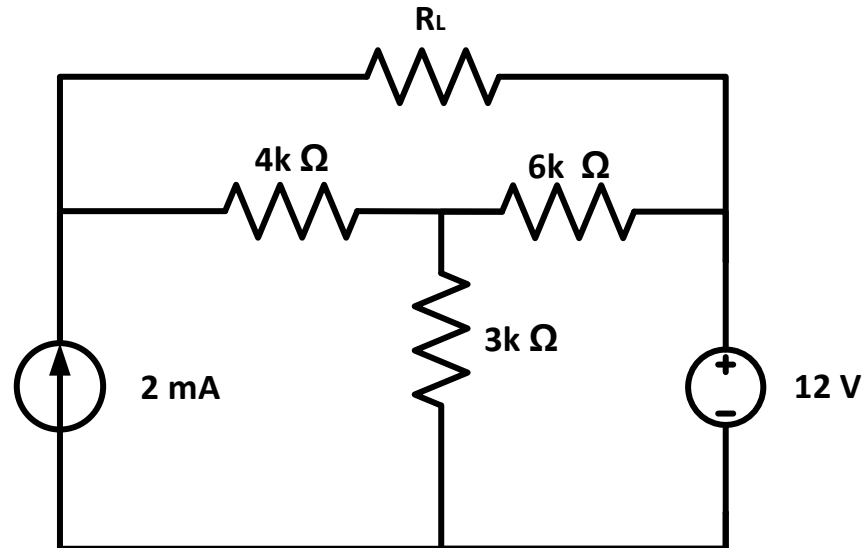

To find V_{TH}

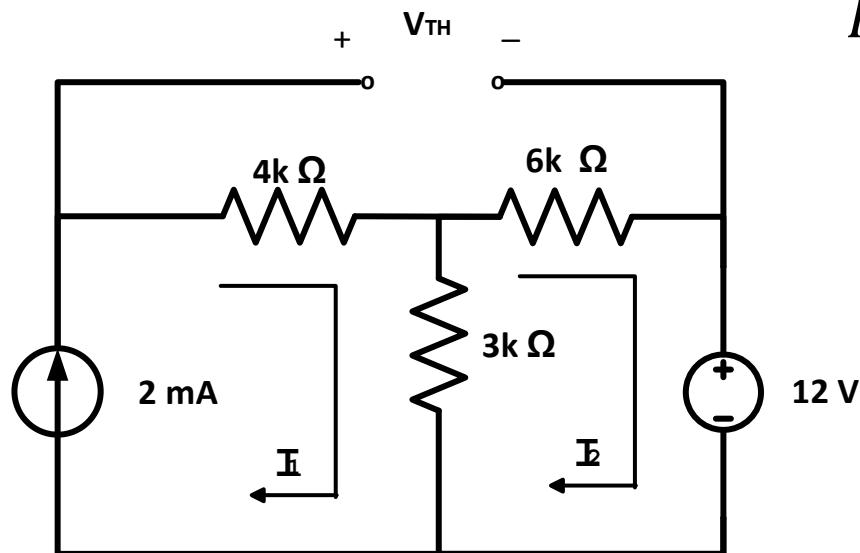

$I_1 = 2 \text{ mA}$ constrain equation


$$-12 = 9k I_2 - 3k I_1$$

$$\therefore I_2 = \frac{1}{3} \text{ mA}$$

$$V_{TH} = 4k I_1 + 6k I_2$$

$$V_{TH} = 10 \text{ V}$$

To find R_{TH}

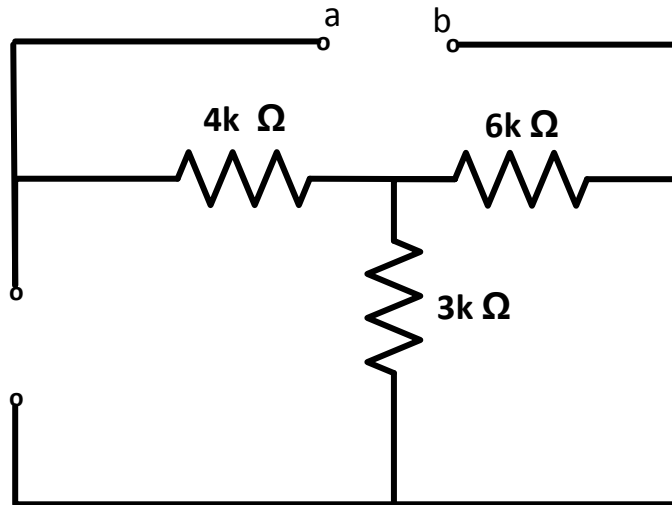

$$R_{TH} = 4k + 3k || 6k$$

$$= 4k + 2k$$


$$= 6k \Omega$$

$$\therefore R_L = R_{TH} = 6k \Omega$$

$$P_{L,max} = \frac{V_{TH}^2}{4 R_{TH}} = \frac{25}{6} \text{ mW}$$

Assessment 4.21

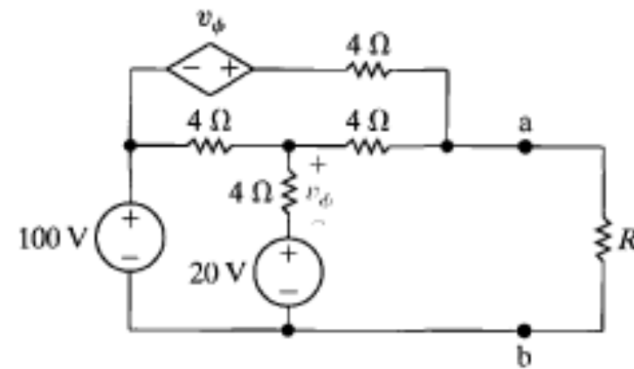
- a) Find the value of R that enables the circuit shown to deliver maximum power to the terminals a,b.
- b) Find the maximum power delivered to R .



Answer: (a) 30 ;
(b) 1.2 k Ω .

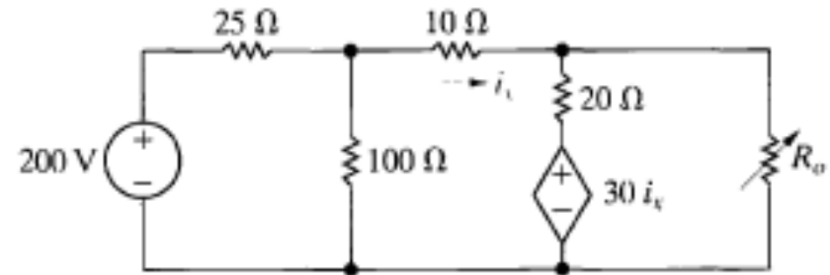Problem 4.83

The variable resistor (R_o) in the circuit adjusted until the power dissipated in the resistor is 250 W. Find the values of R_o that satisfy this condition.



Answer

$$R_o = 22.5 \Omega$$


or

$$R_o = 2.5 \Omega$$

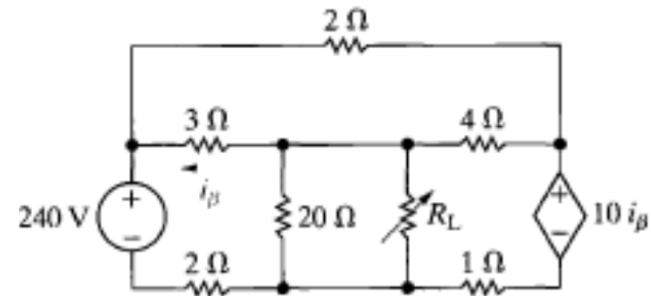Problem 4.87

The variable resistor (R_L) in the circuit adjusted for maximum power transfer

- Find the numerical value of R_L .
- Find the maximum power transferred to R_L .



Answer

$$R_L = R_{Th} = 6 \Omega$$

$$p_{\max} = \frac{12^2}{6} = 24 \text{ W}$$