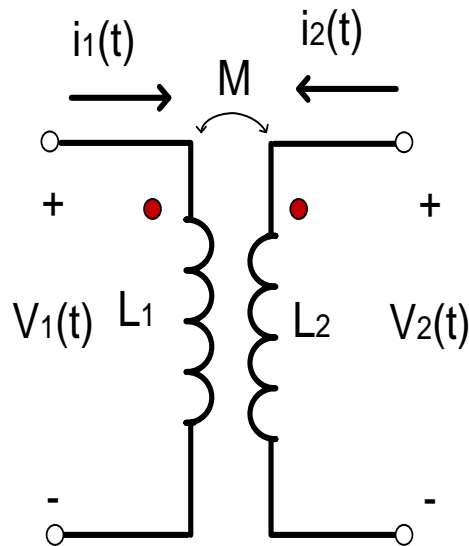


ENEE2301

Network Analysis 1




Transformers


Transformers

- **Transformers are used in a wide variety of applications.**
- **In electric power transmission and distribution systems they step up the voltage at the sending end to reduce transmission losses and step down at the receiving end to make it safer and easier to utilize.**
- **Transformers change voltages and currents to any desired amplitude, large or small.**
- **They transform impedances and match load impedances to source impedances for maximum power transfer.**

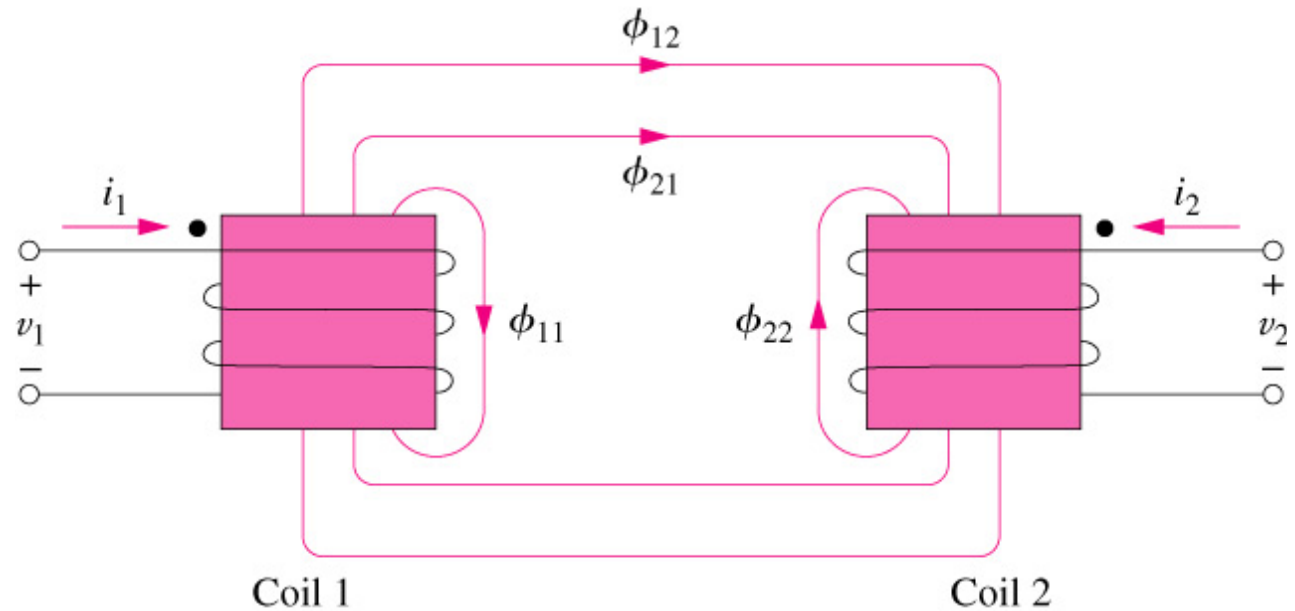
- **Transformers are constructed of two coils placed so that the Changing flux developed by one will link the other**
- **When two coils are placed close to each other, a changing flux in one coil will cause an induced voltage in the second coil.**



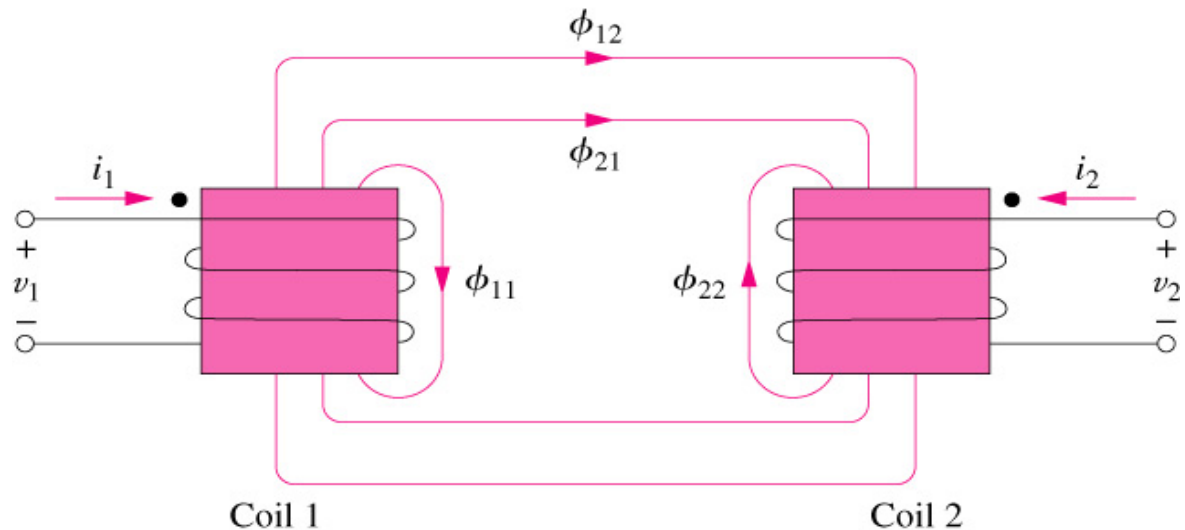- The coils are said to have mutual inductance M , which can either add or subtract from the total inductance depending on if the fields are aiding or opposing.
- The coil to which the source is applied is called the primary coil
- The coil to which the load is applied is called the secondary coil



Mutually coupled circuit

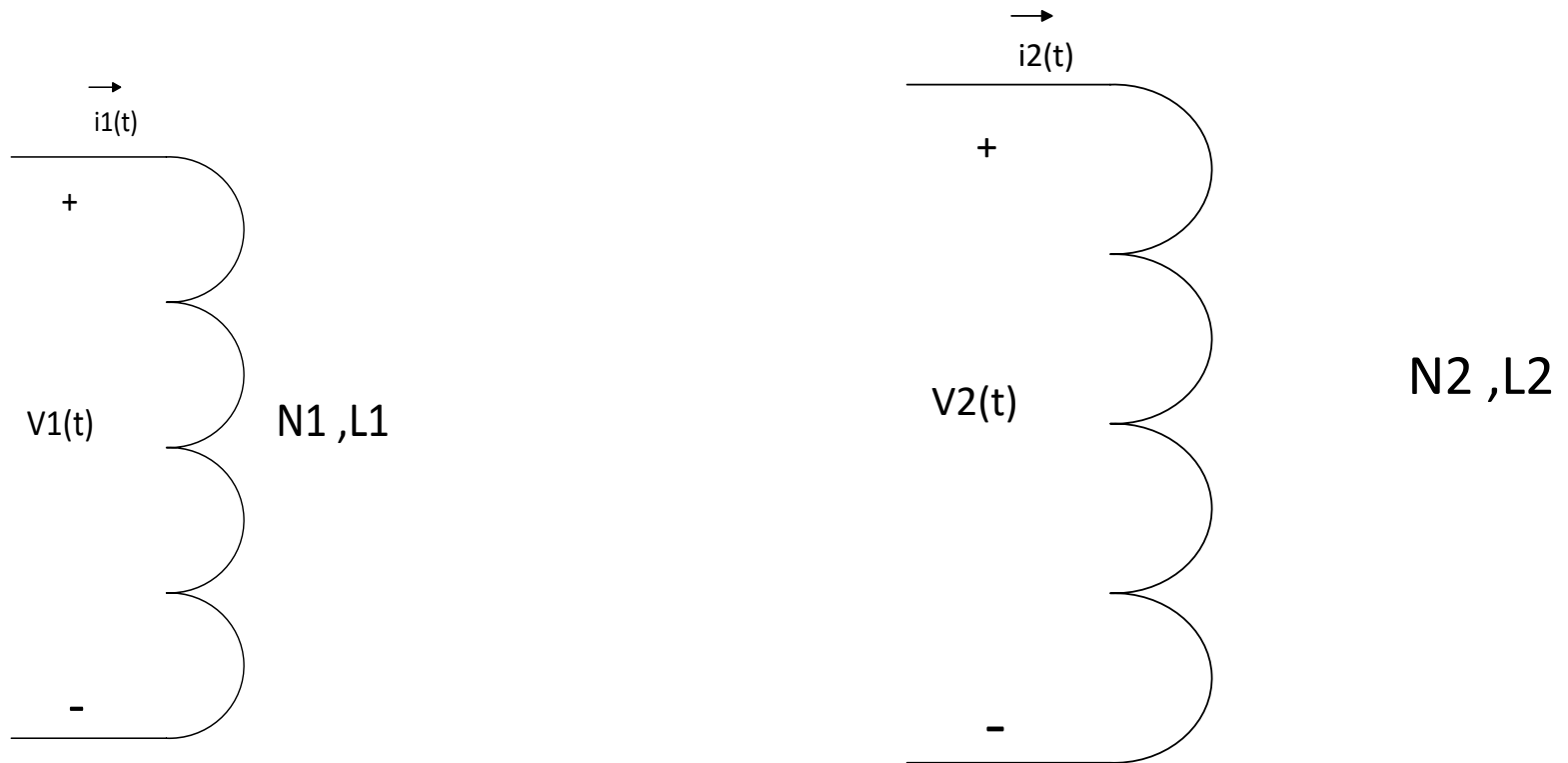

$$V_1(t) = N_1 \frac{d\Phi_1}{dt}$$

$$V_2(t) = N_2 \frac{d\Phi_2}{dt}$$

$$V_1(t) = N_1 \frac{d\Phi_1}{dt}$$

$$V_2(t) = N_2 \frac{d\Phi_2}{dt}$$

Φ_1 = The magnetic fluxes threading through the coil 1

Φ_2 = The magnetic fluxes threading through the coil 2

$$\Phi_1 = K_1 N_1 i_1(t)$$

$$\Phi_2 = K_2 N_2 i_2(t)$$

K_1, K_2 are constants related to the geometry of construction and the permeability of the material used for the coils.

$$V_1(t) = N_1 \frac{d\Phi_1}{dt}$$

$$V_2(t) = N_2 \frac{d\Phi_2}{dt}$$

$$V_1(t) = N_1 \frac{d}{dt} [K_1 N_1 i_1(t)]$$

$$V_2(t) = N_2 \frac{d}{dt} [K_2 N_2 i_2(t)]$$

$$V_1(t) = K_1 N_1^2 \frac{d[i_1(t)]}{dt}$$

$$V_2(t) = K_2 N_2^2 \frac{d[i_2(t)]}{dt}$$


Define $L_1 = K_1 N_1^2$

$$\therefore V_1(t) = L_1 \frac{d[i_1(t)]}{dt}$$

Define $L_2 = K_2 N_2^2$

$$\therefore V_2(t) = L_2 \frac{d[i_2(t)]}{dt}$$

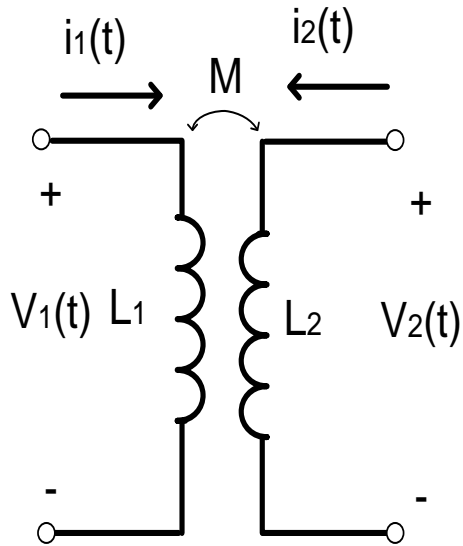Now if we bring the two coils close to each other




$$V_1(t) = N_1 \frac{d\Phi_1}{dt}$$

$$\phi_1 = \phi_{11} \pm \phi_{12}$$


$\phi_{11} \equiv$ the flux caused in coil 1 by current in coil 1

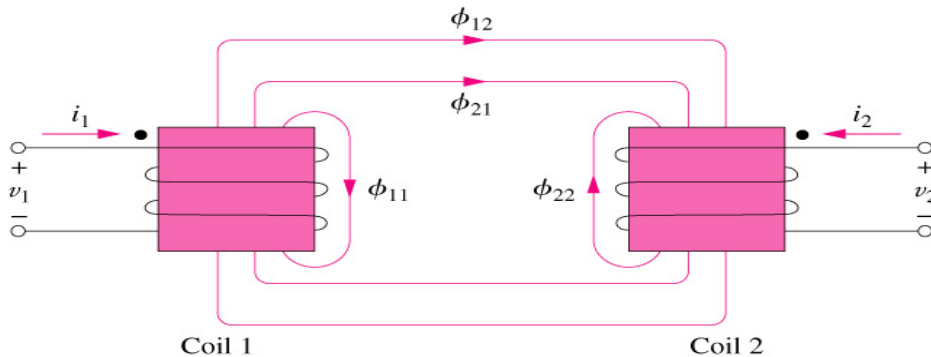$\phi_{12} \equiv$ the flux caused in coil 1 by current in coil 2



$$\phi_{11} = K_{11} N_1 i_1(t)$$

$$\phi_{12} = K_{12} N_2 i_2(t)$$

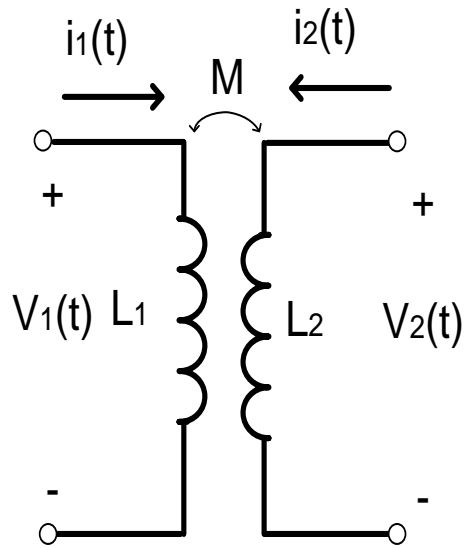


$$V_2(t) = N_2 \frac{d\Phi_2}{dt}$$

$$\Phi_2 = \Phi_{22} \pm \Phi_{21}$$

$\Phi_{22} \equiv$ the flux caused in coil 2 by current in coil 2

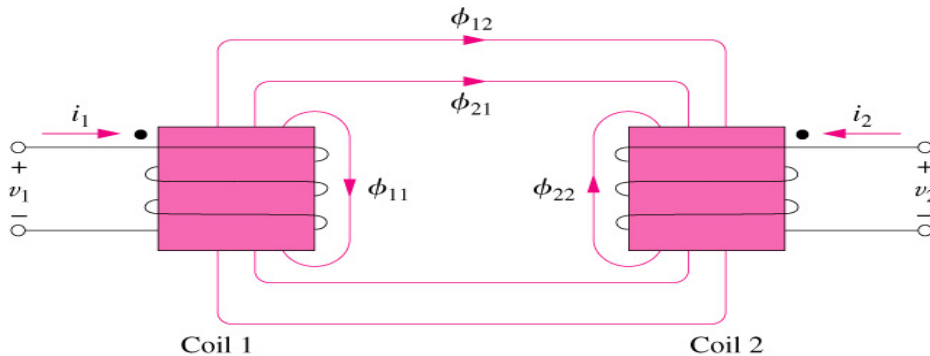
$\Phi_{21} \equiv$ the flux caused in coil 2 by current in coil 1



$$\Phi_{22} = K_{22} N_2 i_2(t)$$

$$\Phi_{21} = K_{21} N_1 i_1(t)$$

$$K_{12} = K_{21} = K_m$$

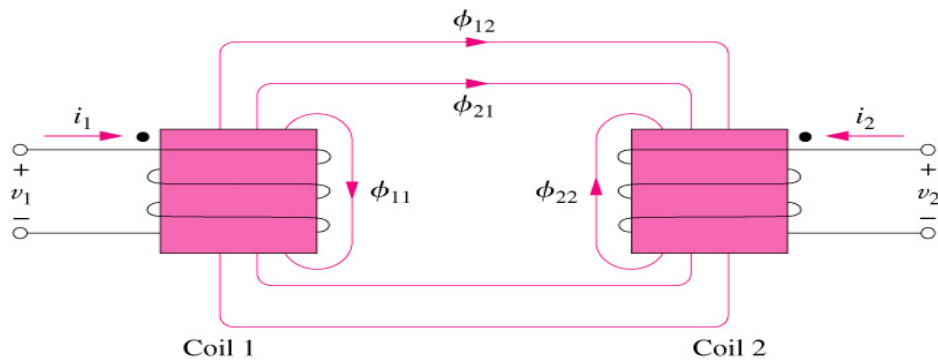

$$V_1(t) = N_1 \frac{d\Phi_1}{dt}$$

$$\phi_1 = \phi_{11} \pm \phi_{12}$$

$$K_{12} = K_{21} = K_m$$


$$V_1(t) = N_1 \frac{d}{dt} \left(\left[K_{11} N_1 i_1(t) \pm K_{12} N_2 i_2(t) \right] \right)$$

$$V_1(t) = K_{11} N_1^2 \frac{d}{dt} (i_1(t)) \pm K_{12} N_2 N_1 \frac{d}{dt} (i_2(t))$$

Let $L_1 = K_{11} N_1^2$; self-inductance of coil 1

$M = K_{12} N_1 N_2$; mutual inductance of coil 1 and 2
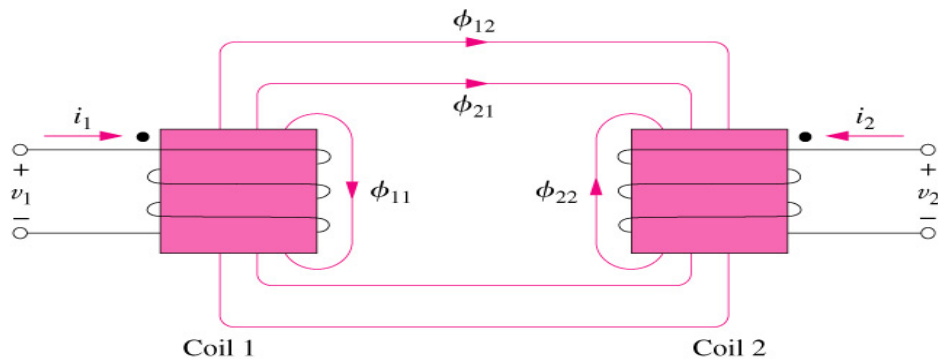
$$V_1(t) = L_1 \frac{d}{dt} (i_1(t)) \pm M \frac{d}{dt} (i_2(t))$$



$$V_2(t) = N_2 \frac{d\Phi_2}{dt}$$

$$\phi_2 = \phi_{22} \pm \phi_{21}$$

$$\mathbf{K}_{12} = \mathbf{K}_{21} = \mathbf{K}_m$$


$$V_2(t) = N_2 \frac{d}{dt} \left(\left[\mathbf{K}_{22} N_2 i_2(t) \pm \mathbf{K}_{21} N_1 i_1(t) \right] \right)$$

$$V_2(t) = \mathbf{K}_{22} N_2^2 \frac{d}{dt} (i_2(t)) \pm \mathbf{K}_{21} N_2 N_1 \frac{d}{dt} (i_1(t))$$

Let $L_2 = \mathbf{K}_{22} N_2^2$; self-inductance of coil 1

$M = \mathbf{K}_{21} N_1 N_2$; mutual inductance of coil 1 and 2
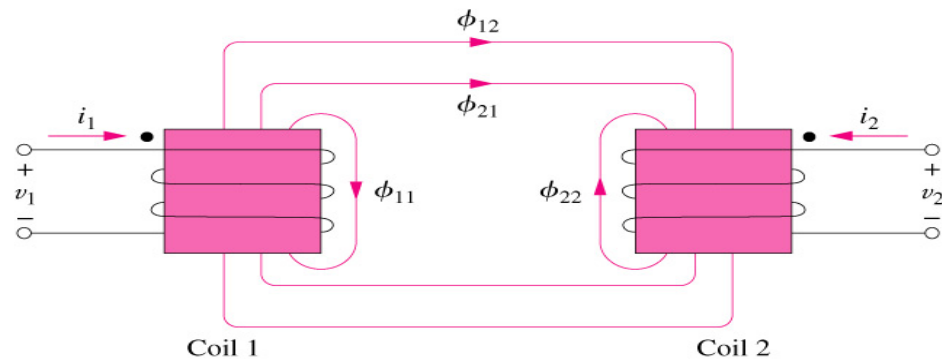
$$V_2(t) = L_2 \frac{d}{dt} (i_2(t)) \pm M \frac{d}{dt} (i_1(t))$$



$$M = K_{12} N_1 N_2$$

$$L_2 = K_{22} N_2^2$$

$$L_1 = K_{11} N_1^2$$

$$M = K_m \sqrt{\frac{L_1}{K_{11}}} \sqrt{\frac{L_2}{K_{22}}}$$

$$M = K_m \sqrt{\frac{L_1 L_2}{K_{11} K_{22}}}$$

$$M = K \sqrt{L_1 L_2}$$



$$K = \frac{K_m}{\sqrt{K_{11} K_{22}}}$$





coefficient of coupling

$$1 \geq k \geq 0$$


$$V_1(t) = L_1 \frac{d}{dt}(i_1(t)) \pm M \frac{d}{dt}(i_2(t))$$

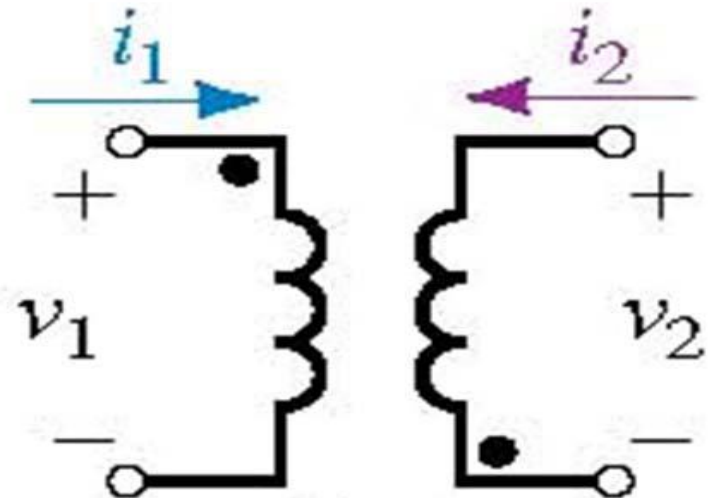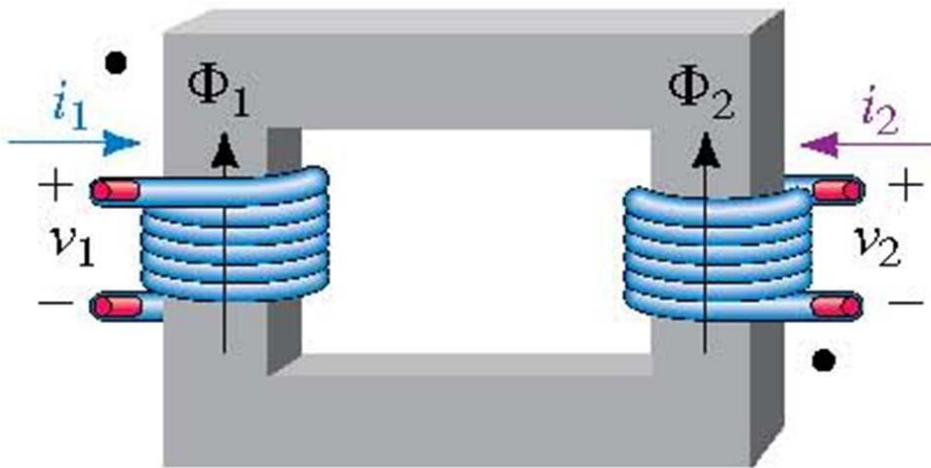- Depending on the direction of the coil winding and the relative position of the coils, the voltage due to the mutual inductance either aids or opposes the voltage due to the self-inductance.



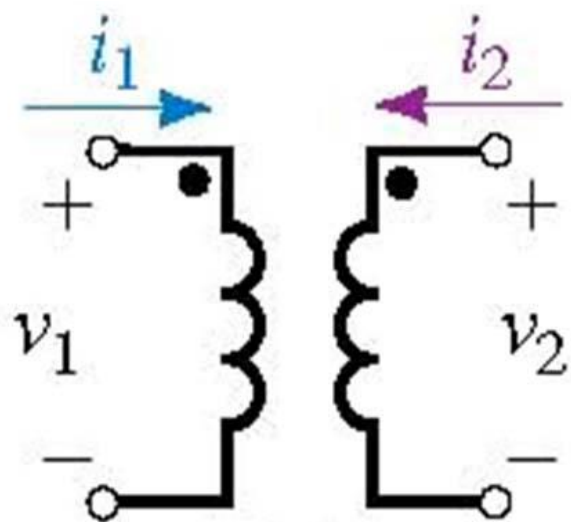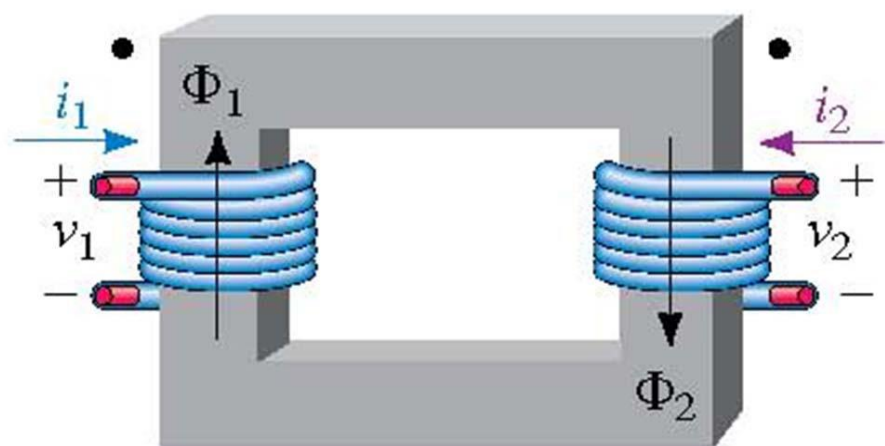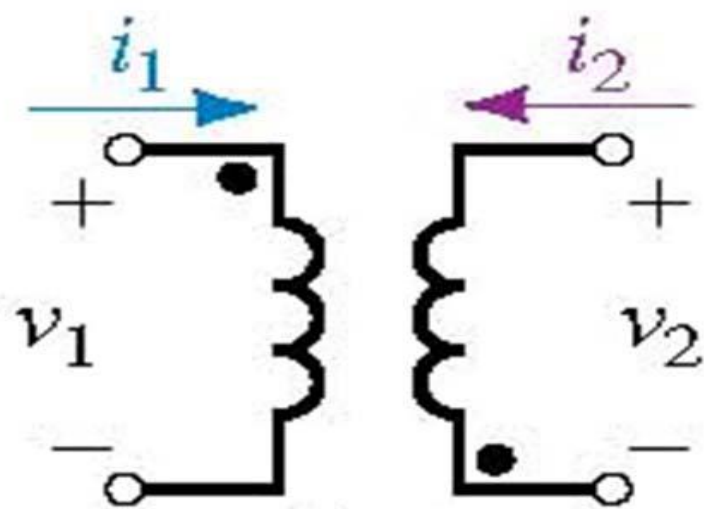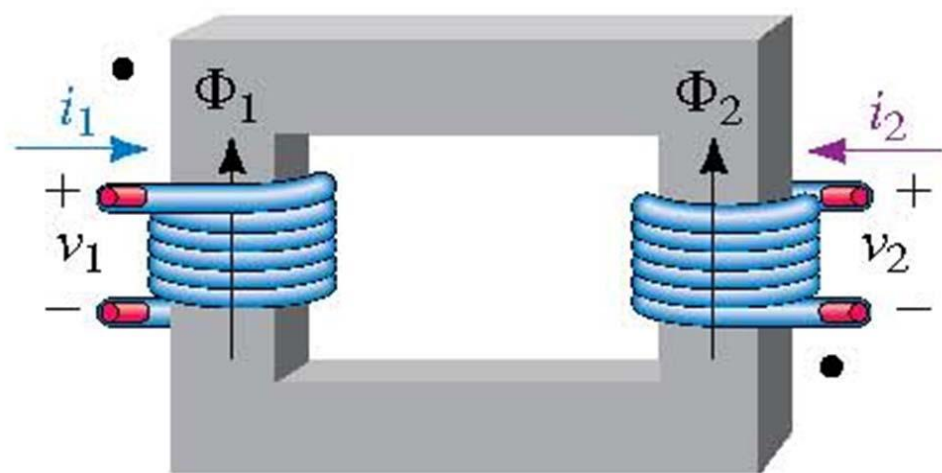

Dot Convention

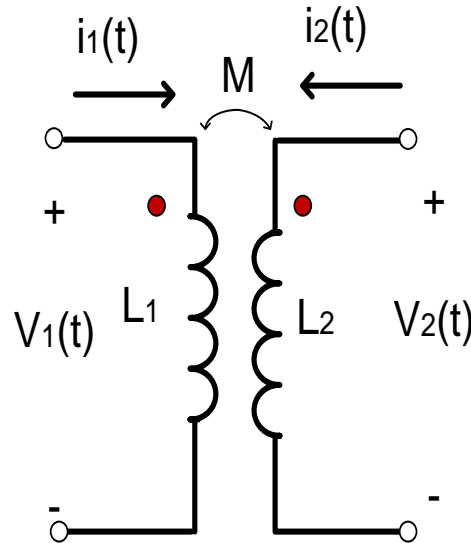


1-If both currents are directed into or away from **corresponding terminals**, the voltage due to the mutual inductance is of the same sign as the voltage due to self inductance

2-If one current enter **a dotted** terminal and the other enters an **un-dotted** terminal ,

Then voltage due to mutual and self inductance have opposite signs.


Important

Flux Direction

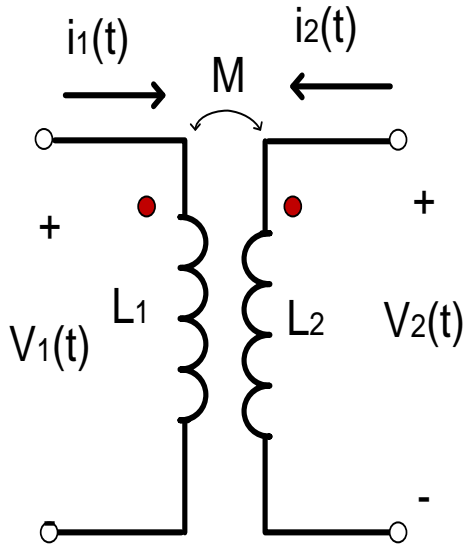


$$V_1(t) = L_1 \frac{d}{dt}(i_1(t)) + M \frac{d}{dt}(i_2(t))$$
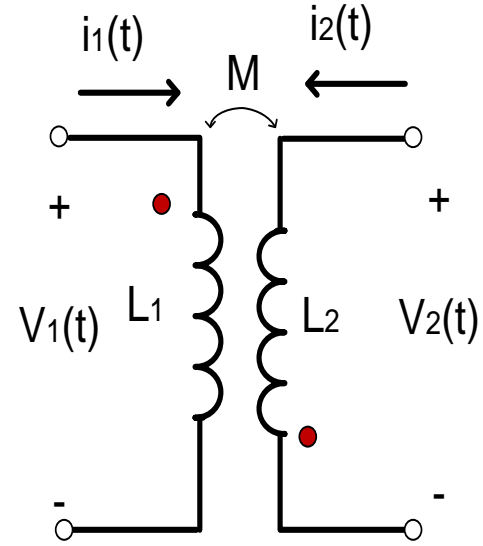
$$V_2(t) = L_2 \frac{d}{dt}(i_2(t)) + M \frac{d}{dt}(i_1(t))$$



$$V_1(t) = L_1 \frac{d}{dt}(i_1(t)) - M \frac{d}{dt}(i_2(t))$$

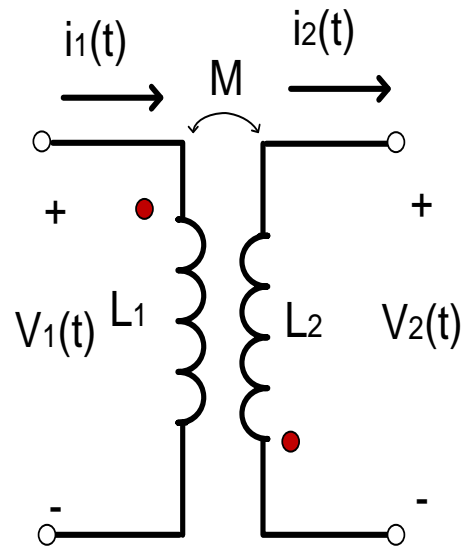
$$V_2(t) = L_2 \frac{d}{dt}(i_2(t)) - M \frac{d}{dt}(i_1(t))$$



$$V_1(t) = L_1 \frac{d}{dt}(i_1(t)) + M \frac{d}{dt}(i_2(t))$$

$$V_2(t) = -L_2 \frac{d}{dt}(i_2(t)) - M \frac{d}{dt}(i_1(t))$$

Example

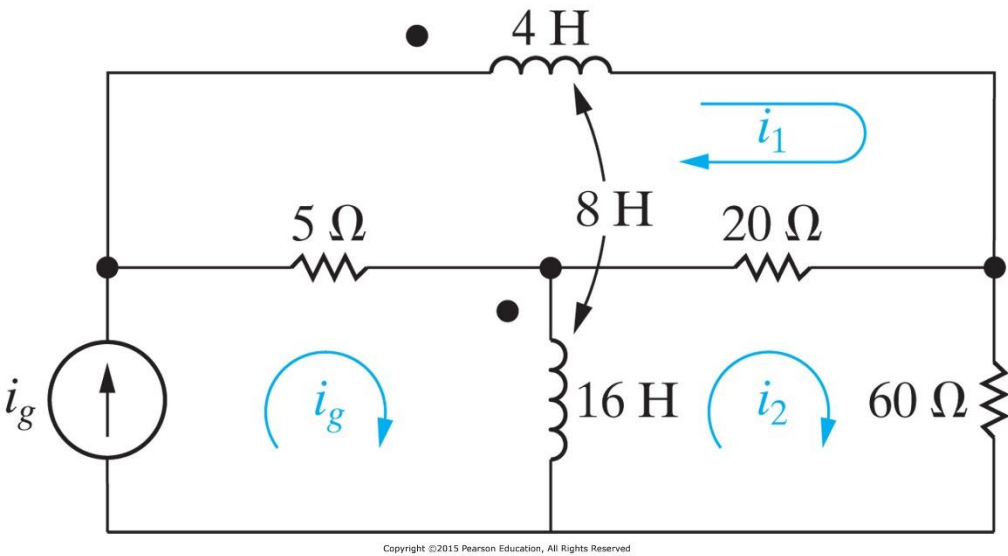


Mesh 1

$$0 = 4 \frac{d}{dt} (i_1) + 8 \frac{d}{dt} (i_g - i_2) + 20(i_1 - i_2) + 5(i_1 - i_g)$$

Mesh 2

$$0 = 20(i_2 - i_1) + 60(i_2) + 16 \frac{d}{dt} (i_2 - i_g) - 8 \frac{d}{dt} (i_1)$$

Example

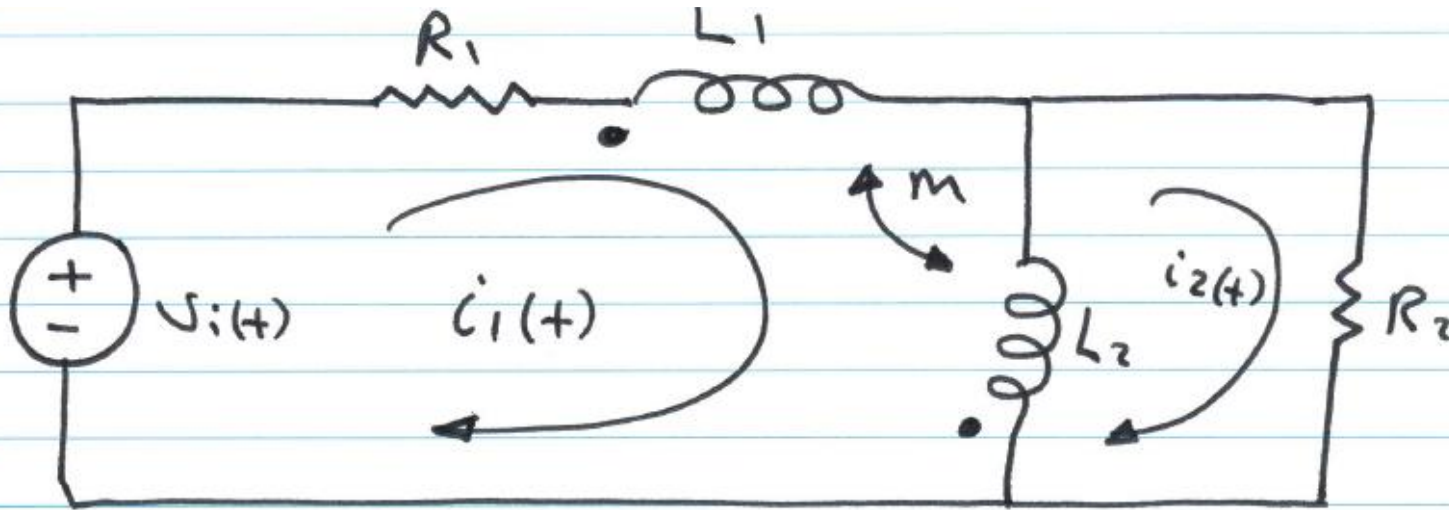


Mesh 1

$$V_i(t) = R_1 i_1(t) + L_1 \frac{d}{dt}(i_1(t)) - M \frac{d}{dt}(i_1 - i_2) + L_2 \frac{d}{dt}(i_1 - i_2) - M \frac{d}{dt}(i_1(t))$$

Mesh 2


$$0 = R_2 i_2(t) + L_2 \frac{d}{dt}(i_2 - i_1) + M \frac{d}{dt}(i_1(t))$$

Phasors and mutual inductance

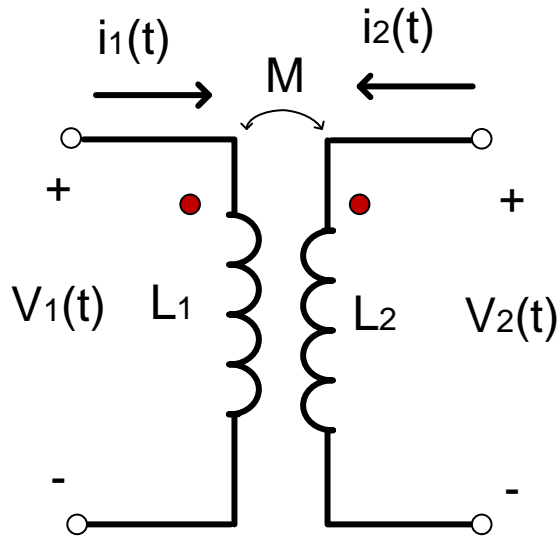

$$V_1(t) = L_1 \frac{d}{dt}(i_1(t)) + M \frac{d}{dt}(i_2(t))$$
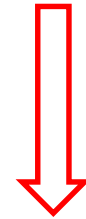
$$V_2(t) = L_2 \frac{d}{dt}(i_2(t)) + M \frac{d}{dt}(i_1(t))$$




$$V_1 = j\omega L_1 I_1 + j\omega M I_2$$

$$V_2 = j\omega M I_1 + j\omega L_2 I_2$$

Example

Find V_o

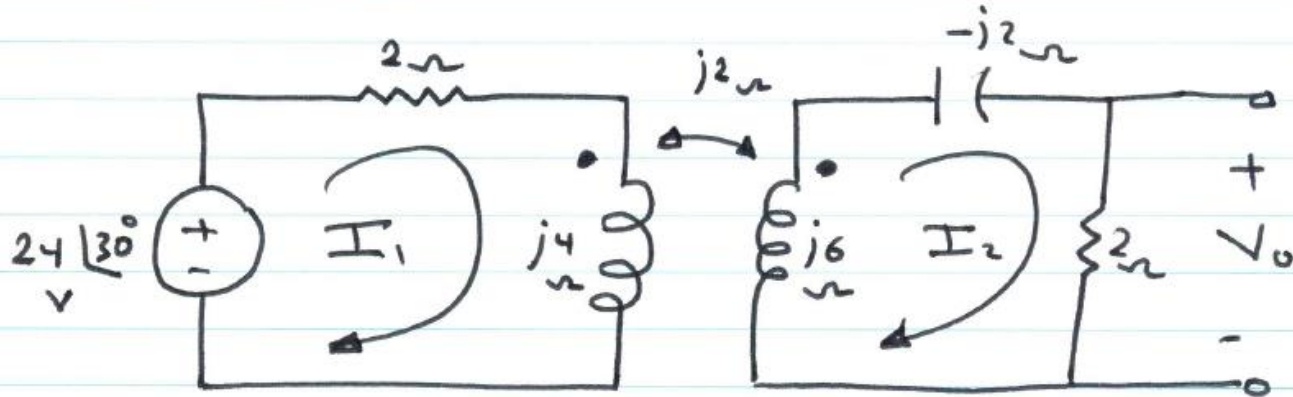

$$24 \angle 30^\circ = 2I_1 + j4I_1 - j2I_2$$


$$24 \angle 30^\circ = (2 + j4)I_1 - j2I_2 \dots \dots \dots (1)$$

$$0 = -j2I_2 + 2I_2 + j6I_2 - j2I_1$$

$$0 = -j2I_1 + (2 + j4)I_2 \dots \dots \dots (2)$$

Example

Find V_o

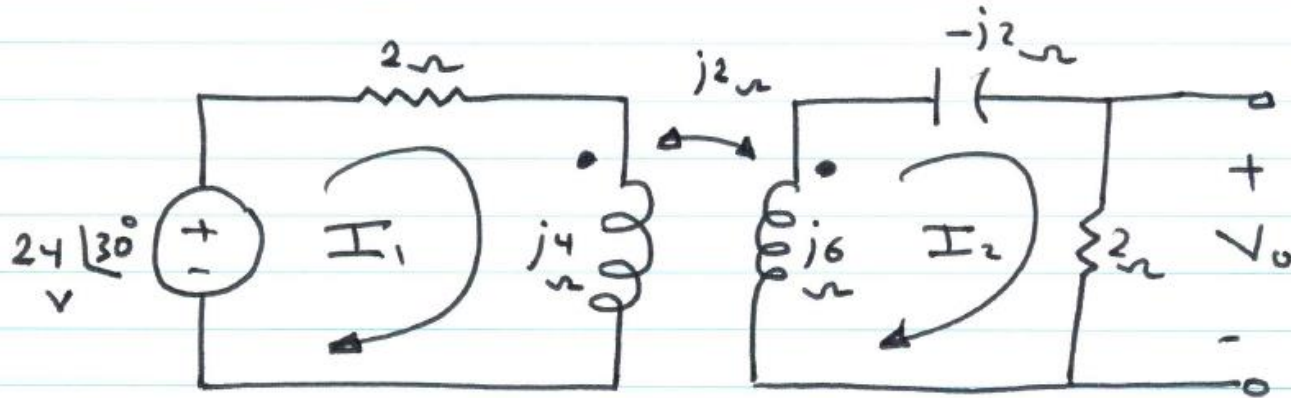

$$24 \angle 30^\circ = (2 + j4)I_1 - j2I_2 \dots \dots \dots (1)$$

$$0 = -j2I_1 + (2 + j4)I_2 \dots \dots \dots (2)$$


Solving (1) & (2) yields

$$I_2 = 2.685 \angle 3.24^\circ \text{ A}$$

$$V_o = 2I_2 = 5.37 \angle 3.24^\circ \text{ v}$$

Find V_o

Example

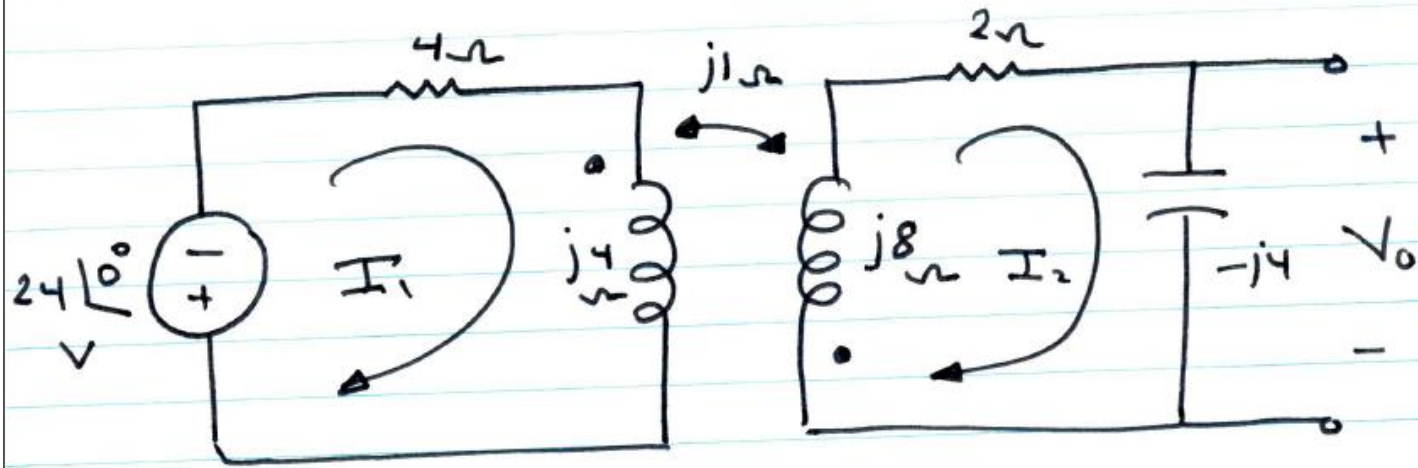

$$-24 \angle 0^\circ = (4 + j4)I_1 + j1I_2 \dots \dots \dots (1)$$

$$0 = 2I_2 - j4I_2 + j8I_2 + j1I_1$$


$$0 = j1I_1 + (2 + j4)I_2 \dots \dots \dots (2)$$

Solving (1) & (2) yields

$$I_2 = 0.96 \angle -16.26^\circ \text{ A}$$

$$V_o = -j4I_2 = 3.84 \angle -106.26^\circ \text{ V}$$

The ideal transformer

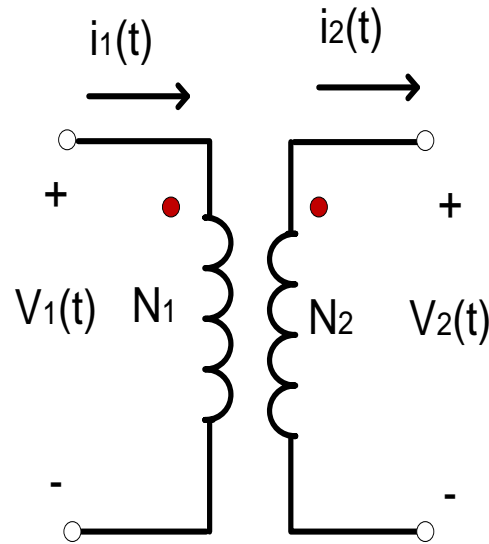

$$V_1(t) = N_1 \frac{d\Phi}{dt}$$

$$V_2(t) = N_2 \frac{d\Phi}{dt}$$


$$\frac{V_1(t)}{V_2(t)} = \frac{N_1}{N_2}$$

Assuming $P_1 = P_2$ (100% efficiency- no losses)

$$V_1(t)i_1(t) = V_2(t)i_2(t)$$

$$\therefore \frac{i_1(t)}{i_2(t)} = \frac{V_2(t)}{V_1(t)} = \frac{N_2}{N_1}$$

Ideal Transformer

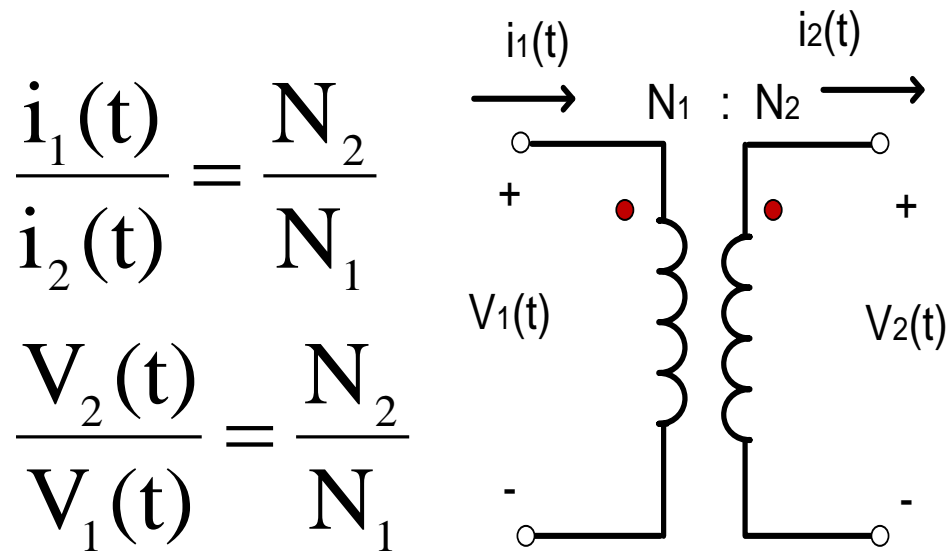

Since the equations are algebraic,
they are unchanged for phasors

$$\frac{I_1}{I_2} = \frac{V_2}{V_1} = \frac{N_2}{N_1}$$

Impedance Reflection



$$\mathbf{Z}_{\text{TH}} = \frac{V_1}{I_1} = \frac{\frac{N_1}{N_2} V_2}{\frac{N_2}{N_1} I_2}$$

$$\mathbf{Z}_{\text{TH}} = \frac{N_1^2}{N_2^2} \frac{V_2}{I_2}$$


$$\mathbf{Z}_{\text{TH}} = \frac{N_1^2}{N_2^2} \mathbf{Z}_L$$

Let $\frac{N_1}{N_2} = \mathbf{n}$

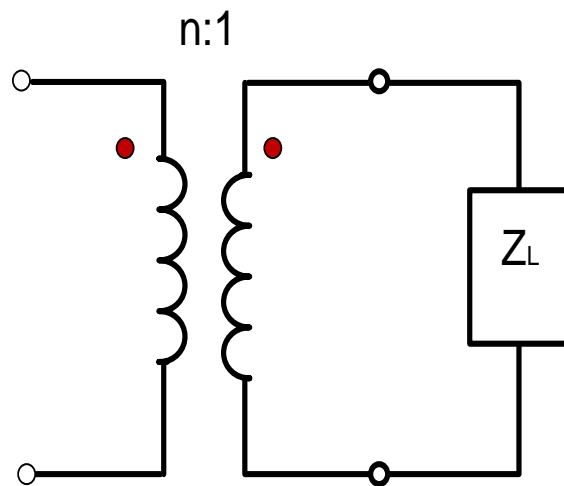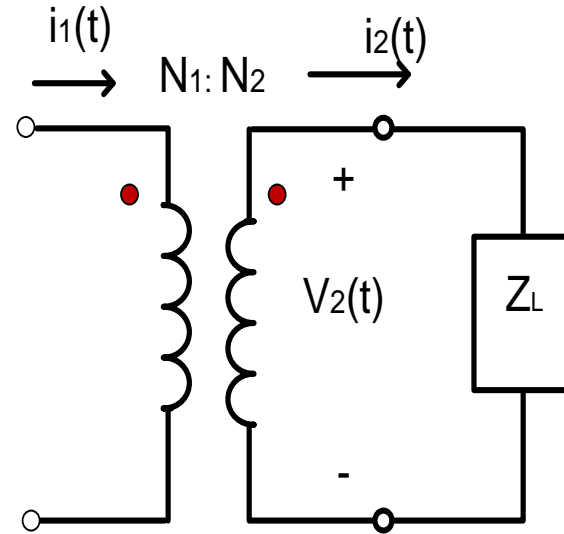
$$\mathbf{Z}_{\text{TH}} = \mathbf{n}^2 \mathbf{Z}_L$$



Example

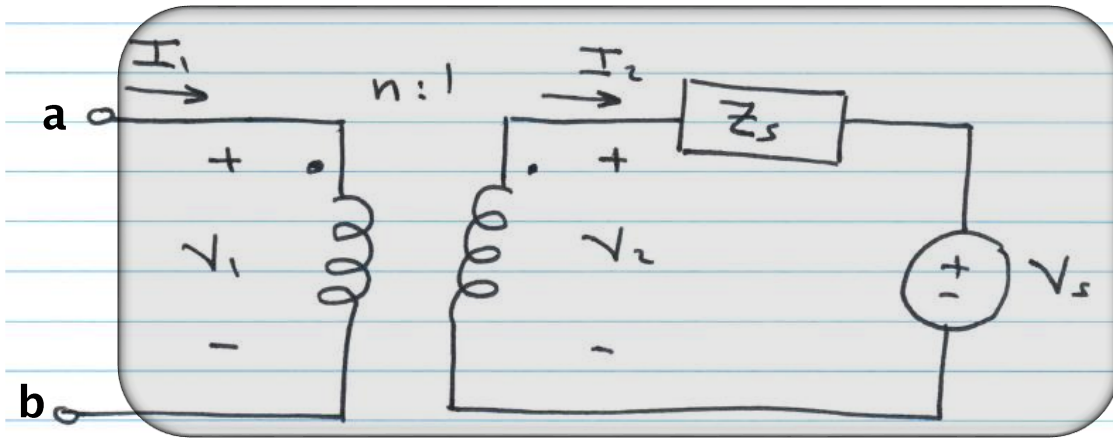


$$I_1 = I_2 = 0$$

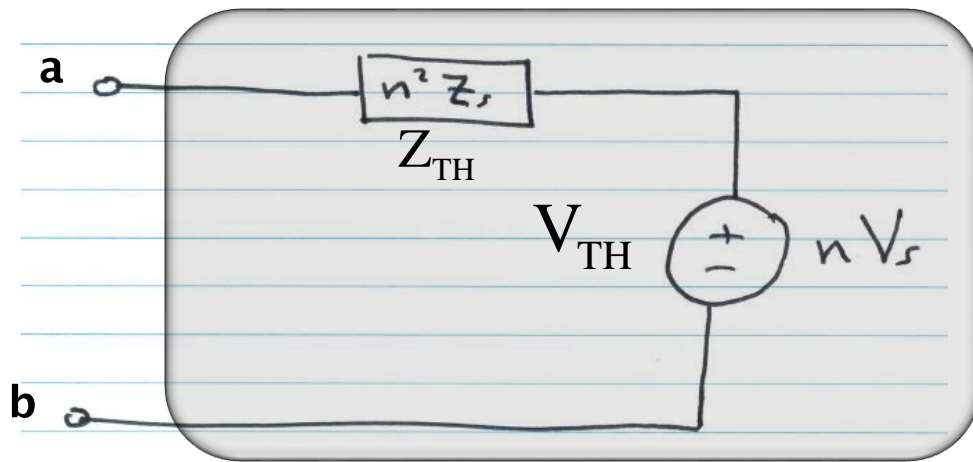

$$V_{TH} = V_1 = nV_2 = nV_S$$

$$Z_{TH} = n^2 Z_S$$

Find I_1 and I_2


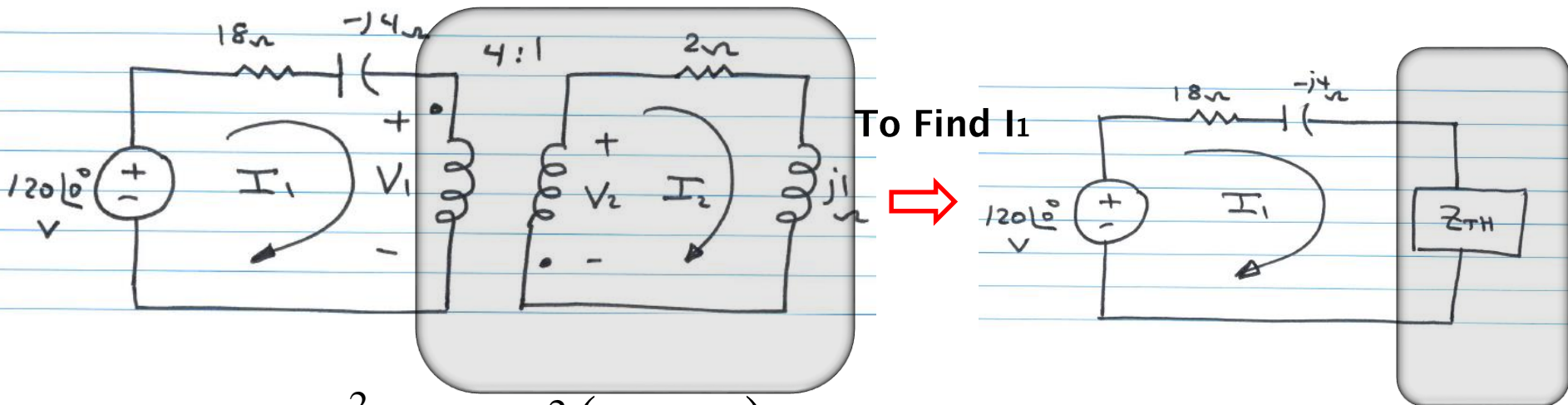


$$Z_{TH} = n^2 Z_L = 4^2 (2 + j1) = 32 + j16$$

$$I_1 = \frac{120\angle 0}{18 - j4 + 32 + j16} = \frac{120\angle 0}{50 + j12}$$

$$= 2.33\angle -13.5^\circ \text{ A}$$

Find I_1 and I_2

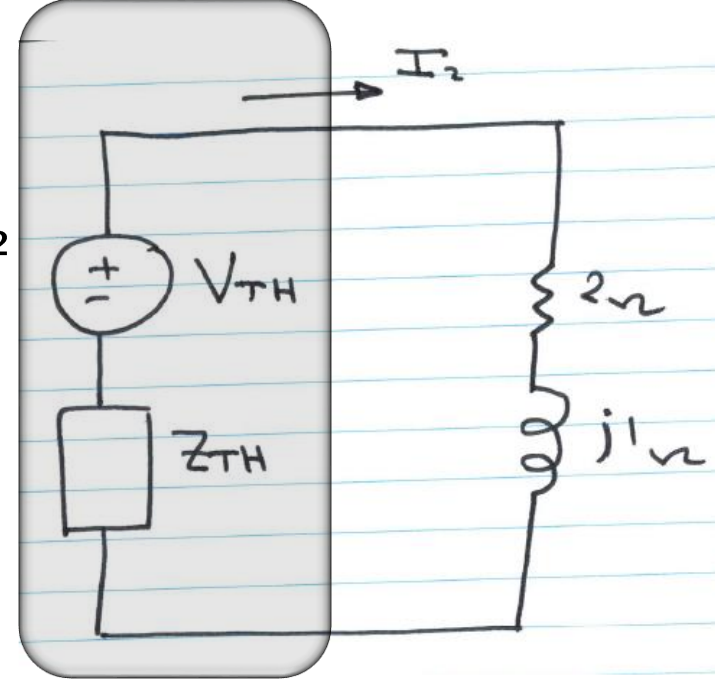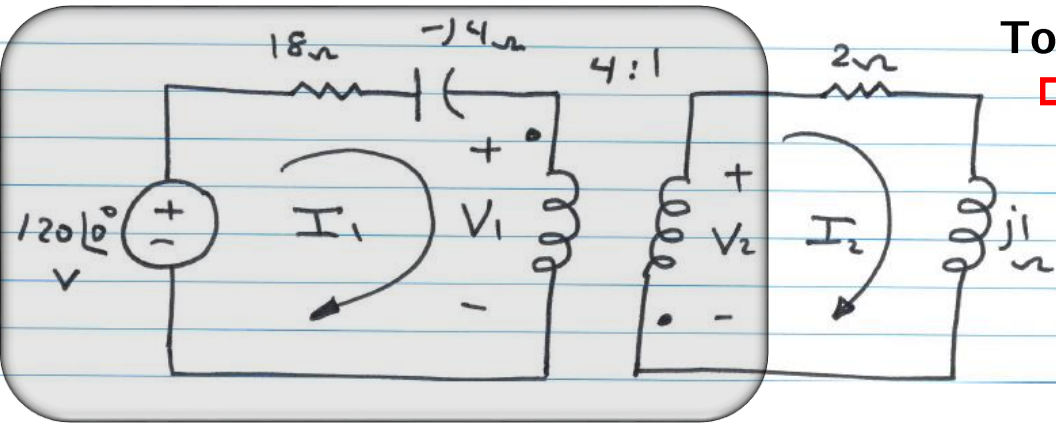


$$Z_{TH} = \frac{1}{n^2} Z_s = \frac{(18 - j4)}{4^2} = 1.125 - j0.25 \Omega$$

$$V_{TH} = -\frac{120 \angle 0}{4} = -30 \angle 0 \text{ V}$$


$$I_2 = \frac{V_{TH}}{Z_{TH} + 2 + j1}$$

$$= 9.335 \angle 166.5^\circ \text{ A}$$

Find V_1 and V_2

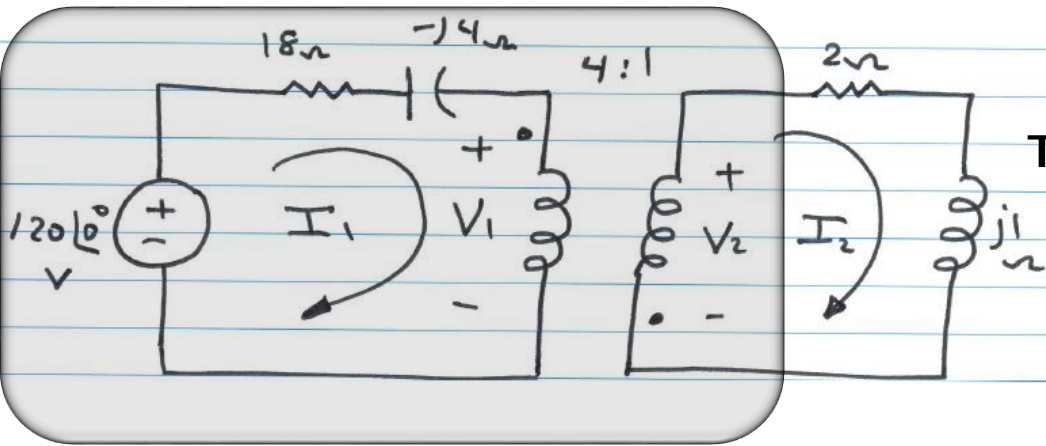

To Find I_2

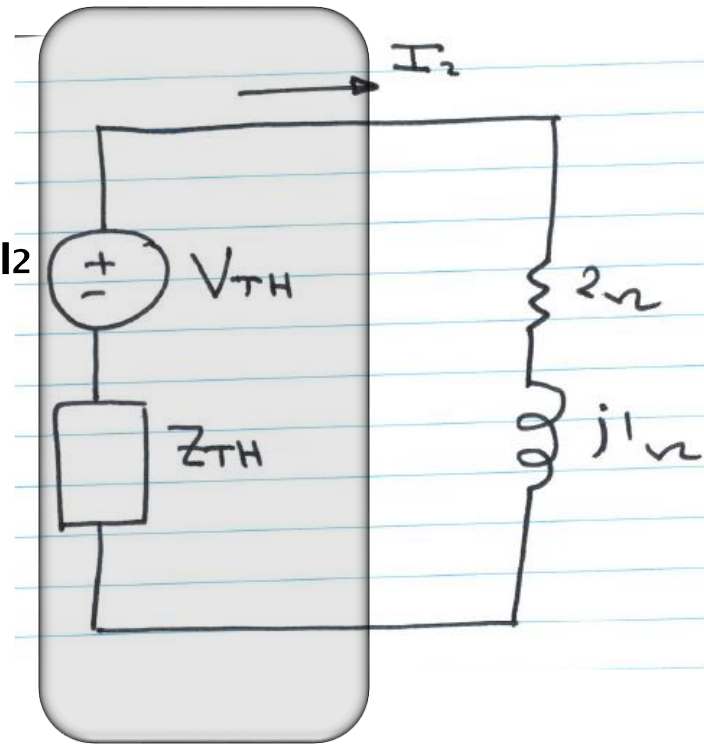


$$V_2 = I_2(2 + j1)$$

$$V_2 = 20.87 \angle 193.07^\circ \text{ V}$$

$$V_1 = -4V_2$$

$$= 83.49 \angle 3.07^\circ \text{ V}$$


Example

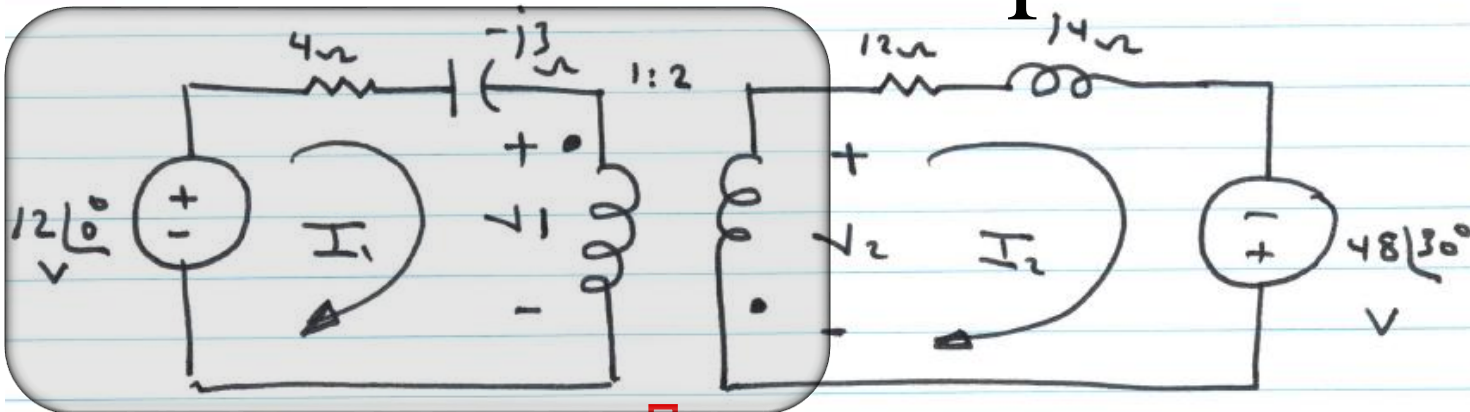


To Find I_2

$$V_{TH1} = -nV_1 = -2(12 \angle 0^\circ) = -24 \angle 0^\circ$$
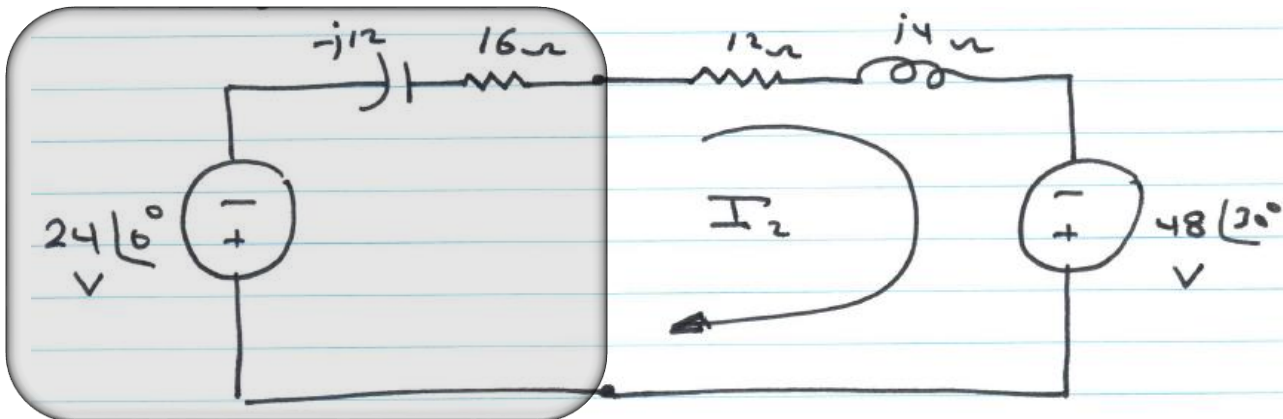
$$Z_{TH1} = n^2 Z_s = 2^2(4 - j3) = 16 - j12 \Omega$$




Example


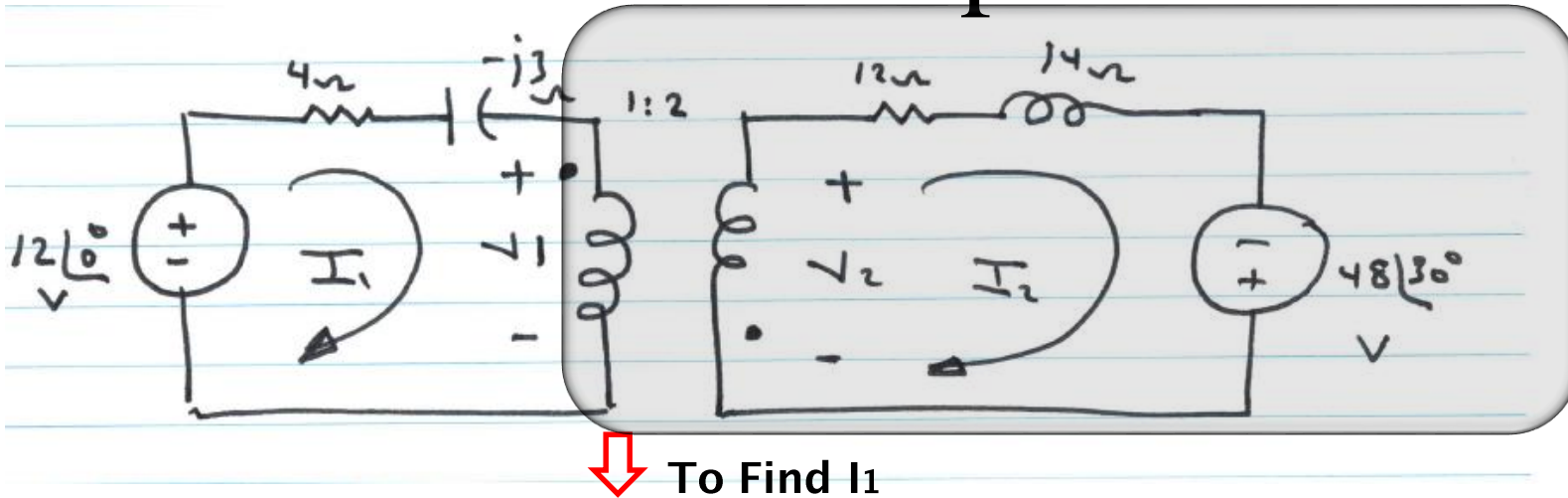


$$V_{TH2} = -\frac{1}{n} V_2 = -\frac{1}{2} (-48 \angle 30^\circ) = +24 \angle 30^\circ$$
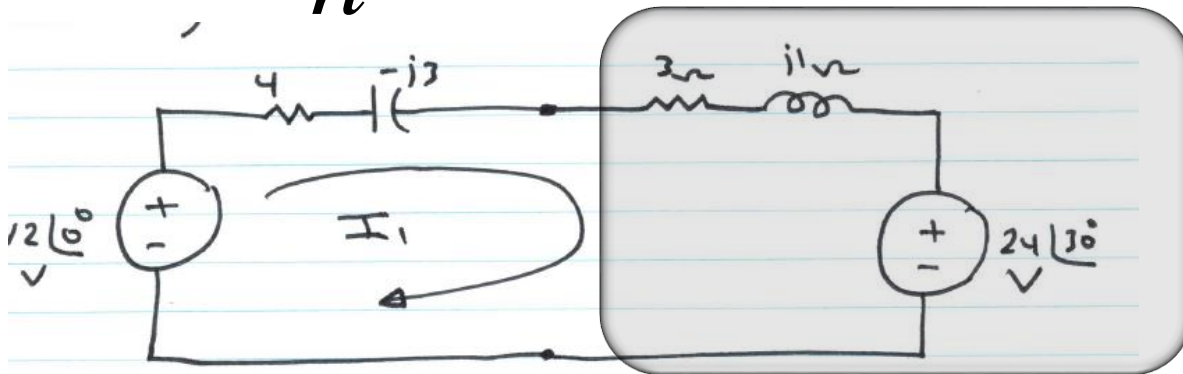
$$Z_{TH2} = \frac{1}{n^2} Z_L = \frac{(12 + j4)}{2^2} = 3 + j1 \Omega$$



Example: Find V_o

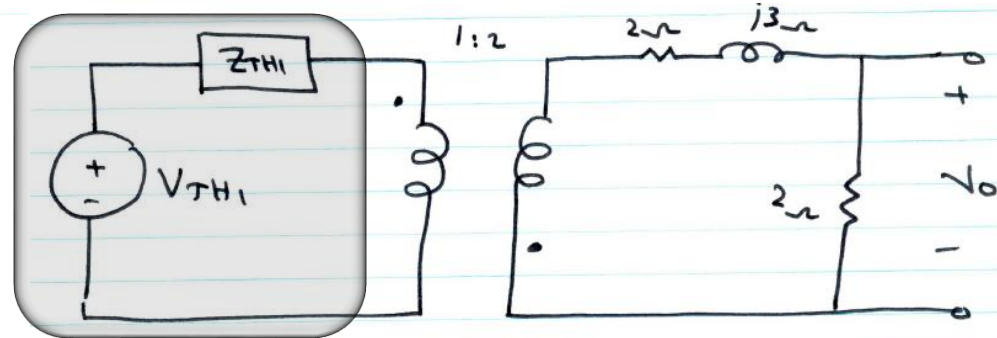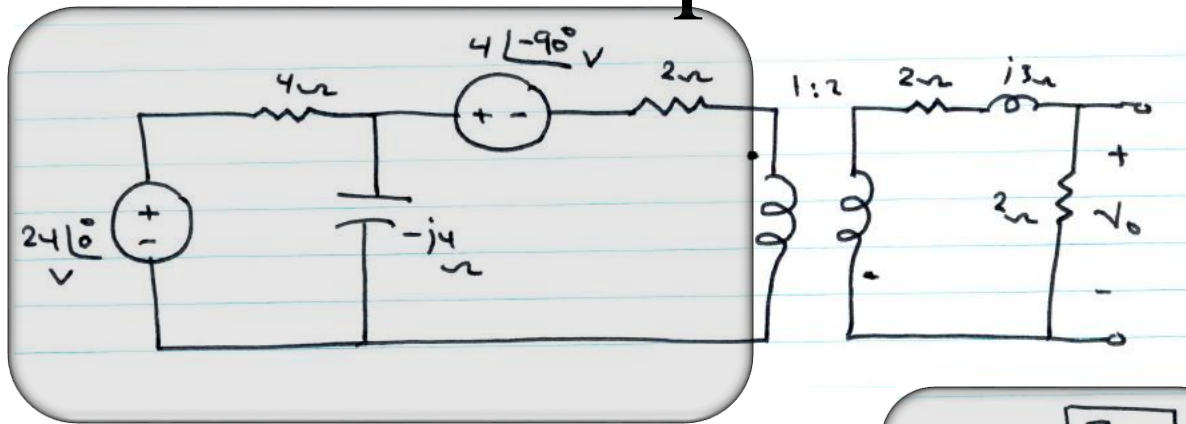


$$Z_{TH1} = 2 + (4 \parallel -j4)$$

$$= 2 + \left(\frac{-j16}{4 - j4} \right) \left(\frac{4 + j4}{4 + j4} \right) = 2 + \left(\frac{-j64 + 64}{32} \right)$$

$$= 2 + (2 - j2) = 4 - j2 \Omega$$


Example: Find V_o

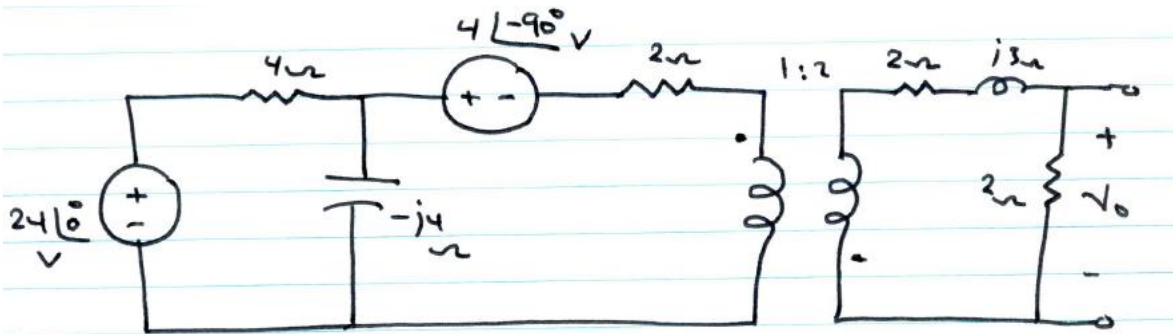


$$V_{TH1} = \frac{-j4}{4-j4} 24 \angle 0^\circ - 4 \angle -90^\circ$$

$$\frac{-j4}{4-j4} = \frac{-j4}{4-j4} \times \frac{4+j4}{4+j4} = \frac{-j16+16}{32} = \frac{1}{2} - j\frac{1}{2}$$
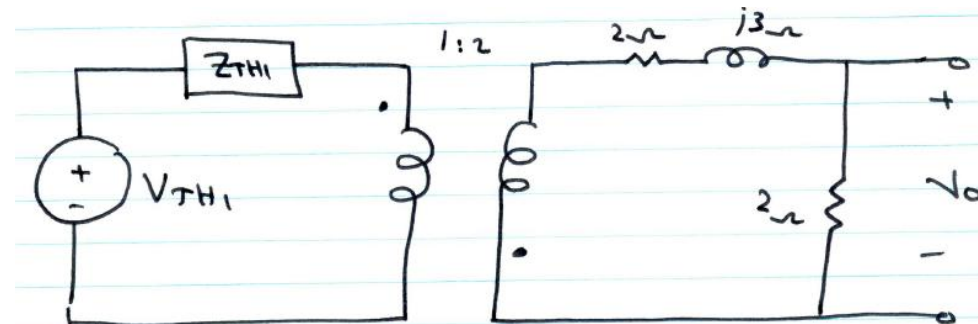
$$\begin{aligned} V_{TH1} &= \left(\frac{1}{2} - j\frac{1}{2} \right) 24 \angle 0^\circ - (-j4) \\ &= 12 - j12 + j4 = 12 - j8 \end{aligned}$$



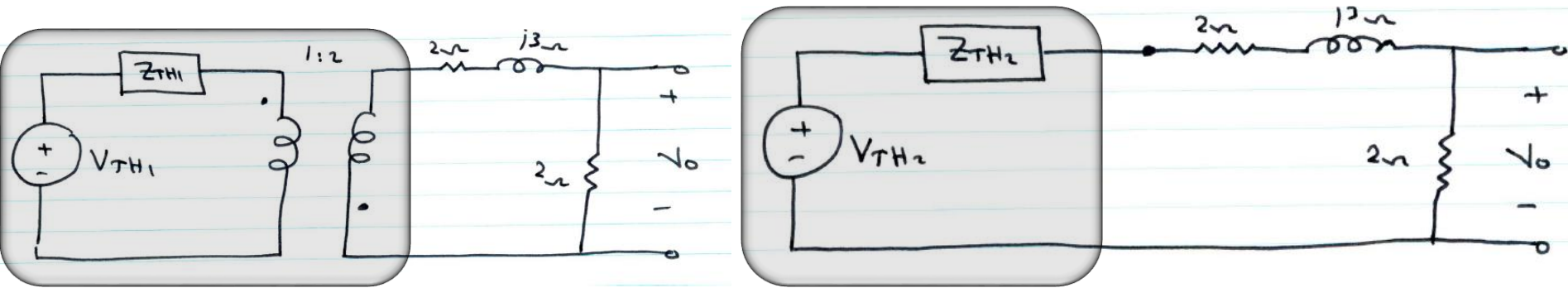
$$V_{TH1} = 14.42 \angle -33.69^\circ \text{ V}$$



$$Z_{TH2} = (2^2) Z_{TH1} = 4(4 - j2) = 16 - j8 \Omega$$

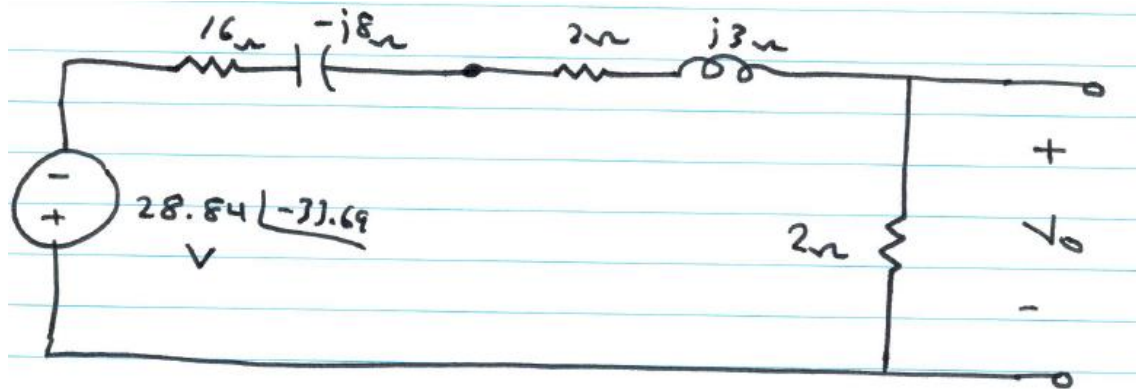
$$V_{TH2} = -2V_{TH1} = -28.84 \angle -33.69^\circ \text{ V}$$



$$V_o = \frac{2}{(2 + 2 + 16 + j3 - j8)} (-28.84 \angle -33.69^\circ)$$

$$V_o = 2.8 \angle 160.35^\circ \text{ V}$$

Example

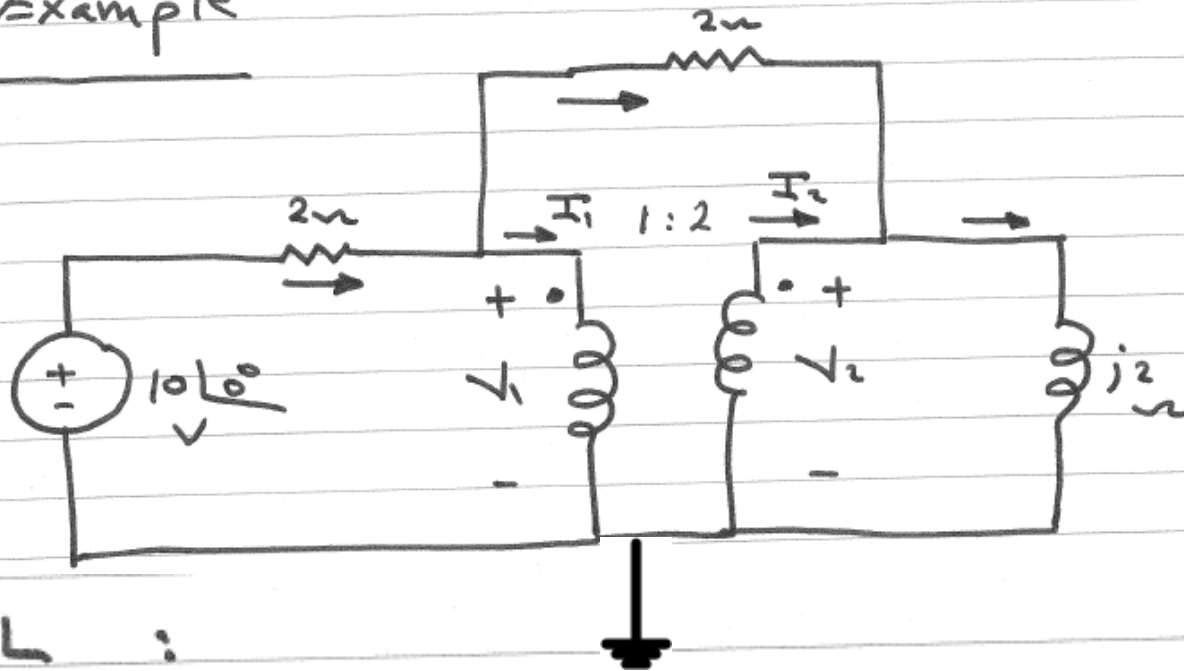


KCL :

$$\frac{10 - V_1}{2} = \frac{V_1 - V_2}{2} + I_1$$

KCL :

$$I_2 + \frac{V_1 - V_2}{2} = \frac{V_2}{j2}$$

Example

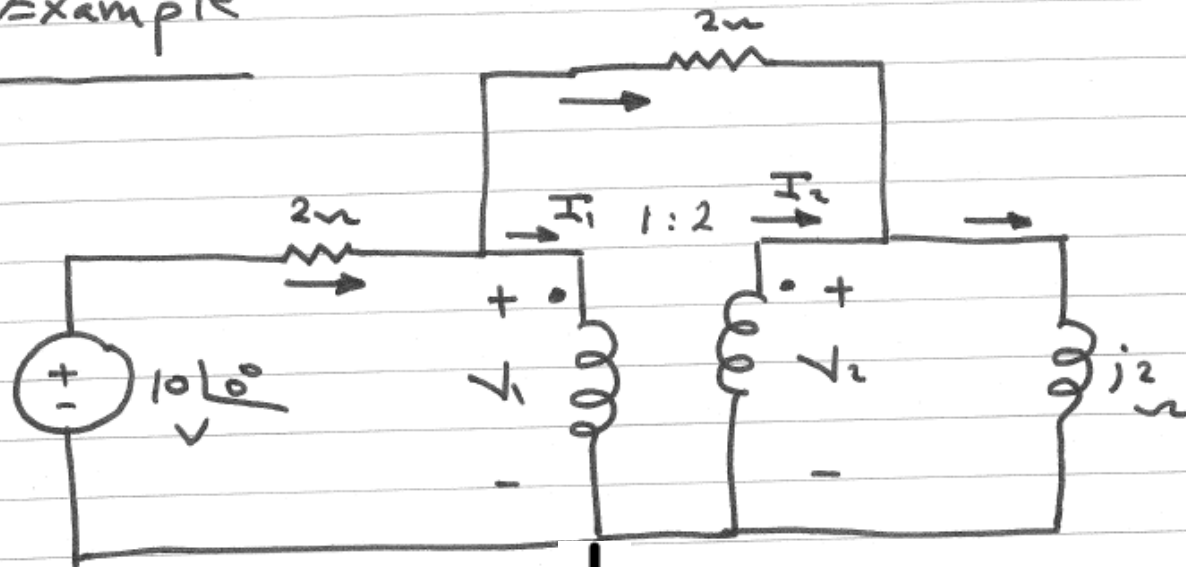

$$V_2 = 2V_1$$

$$I_1 = 2I_2$$


$$\therefore I_1 = 5 \angle 0^\circ \text{ A}$$

$$I_2 = 2.5 \angle 0^\circ \text{ A}$$

$$V_1 = \sqrt{5} \angle 63^\circ \text{ V}$$

$$V_2 = 2\sqrt{5} \angle 63^\circ \text{ V}$$

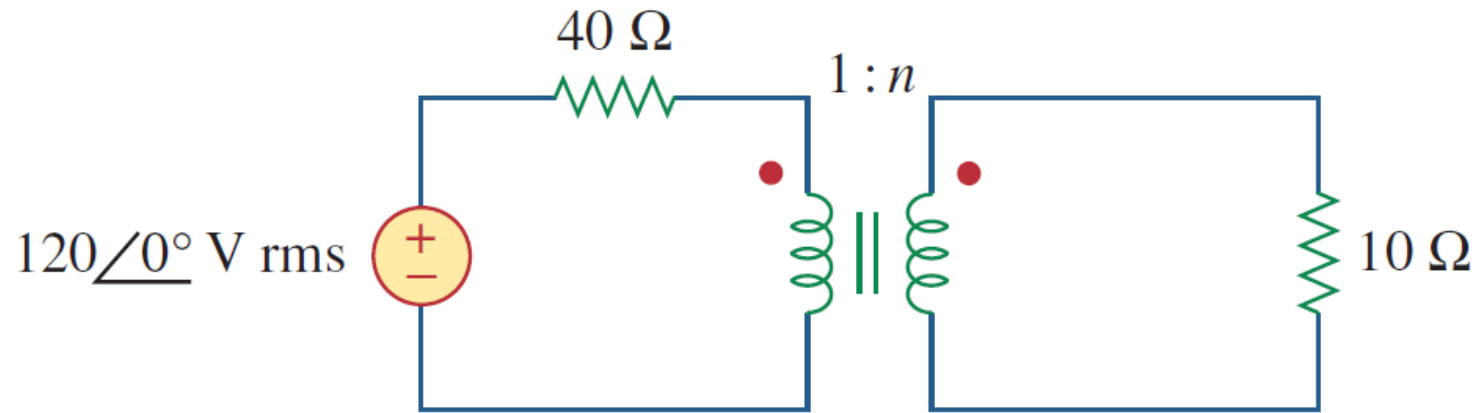For the circuit shown , determine the turns ratio n that will cause maximum average power transfer to the load . Calculate that maximum average power



For maximum average power transfer to the load : $Z_{th} = 10\Omega$

$$n^2 \cdot 40 = 10$$

$$\therefore n = 0.5$$

$$I = \frac{60\angle 0}{10 + 10} = 3\angle 0 \text{ Arms}$$

$$V_{th} = 60\angle 0 \text{ V rms}$$

$$P = I^2 \cdot R = 90 \text{ W}$$