

ENEE 230 |

Final Exam

Solutions



**BIRZEIT UNIVERSITY**

Electrical & Computer Engineering Department

ENEE2301-Network Analysis 1

Final Exam-January 19<sup>th</sup>, 2016

Instructors: M. Jubeh , N. Ismail & Khader Mohammad

Student Name:

ID:

Section:

Notes and Instructions:

- Read each question carefully before starting your solution and answer in the assigned space.
- Write neatly and clearly and leave only one answer for each question.
- Use of cell Phones is categorically prohibited so please make sure to turn them off.
- Percentage (%) of total mark is given for each question. Budget your time accordingly.
- The results of this exam will be evaluated according to ABET "a" and "e" student outcomes and the questions are designed for that.

**Part One:**


Problem1. ( 15 points) To assess "a" student outcome

Choose the correct Answer:

<p>1. The equivalent resistance <math>R_{eq}</math> between the two terminals A and B is</p> <p>(I) <math>2 \Omega</math>      (II) <math>2.8 \Omega</math>      (III) <math>1 \Omega</math>      (IV) <math>2.5 \Omega</math></p> <p>(V) <math>1.2 \Omega</math>      (VI) <math>3 \Omega</math>      (VII) <math>1.5 \Omega</math>      (VIII) <math>3.3 \Omega</math></p>	
<p>2. In the circuit shown below , the value of <math>V_x</math> is</p> <p>(I) <math>10 V</math>      (II) <math>-10 V</math>      (III) <math>4 V</math>      (IV) <math>-4 V</math></p> <p>(V) <math>-6 V</math>      (VI) <math>0 V</math>      (VII) <math>6 V</math>      (VIII) <math>5 V</math></p>	
<p>3. In the circuit shown below, the value of <math>i_s</math> and the power absorb by <math>R_1</math> are</p> <p>(I) <math>6A, -30W</math>      (II) <math>-6A, -30W</math>      (III) <math>6A, 30W</math>      (IV) <math>-6A, 30W</math></p> <p>(V) <math>3A, -30W</math>      (VI) <math>-6A, -60W</math>      (VII) <math>-3A, 60W</math>      (VIII) <math>3A, 60W</math></p>	


4. In the circuit shown below, the value of  $V_2$  is :

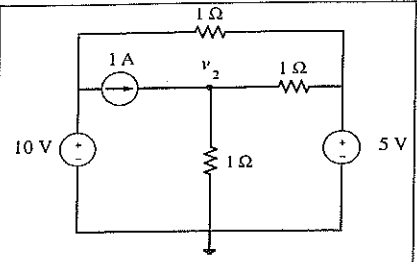- (I) 2 V      (II) -2 V      (III) -5 V      (IV) 5 V  
 (V) -3 V      (VI) 3 V      (VII) 0.5 V      (VIII) -0.5 V



5. In the circuit shown below, the value of  $i$  is

- (I)  $\frac{24}{5} A$       (II)  $-\frac{6}{5} A$       (III)  $\frac{6}{5} A$       (IV) 2 A  
 (V)  $-\frac{24}{5} A$       (VI) -8 A      (VII) 8 A      (VIII) -2 A

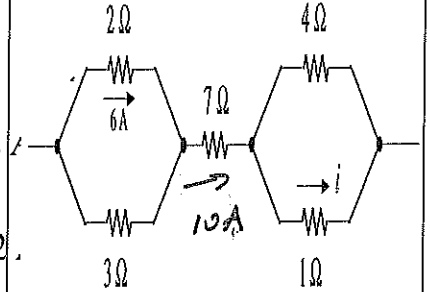

Problem2. ( 10 points) To assess "a" student outcome  
 For the circuit of Fig.(2) , determine  $V_x$  using Superposition.

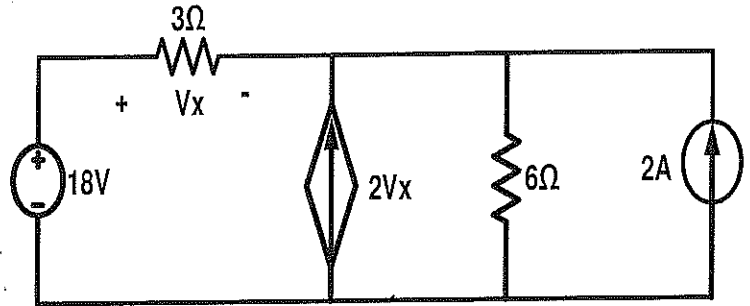


Fig.(2)

1) Kill 18V source

Nodal


$$2V_x' + 2 = V_1' \left( \frac{1}{6} + \frac{1}{3} \right)$$

$$V_x' = -V_1'$$

$$\therefore -2V_1' + 2 = V_1' \cdot \frac{3}{6}$$

$$-2.5V_1' = -2 \Rightarrow V_1' = 0.8 \text{ V}$$
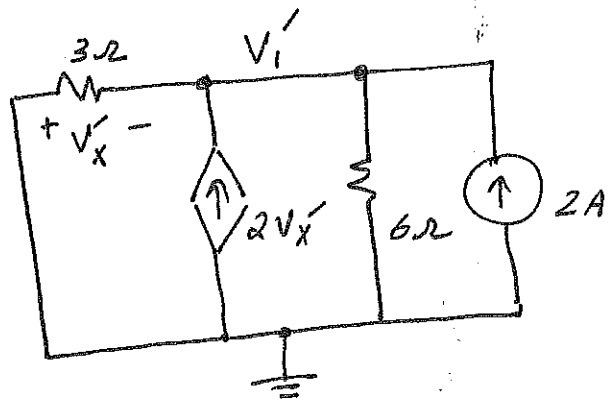
$$\boxed{\therefore V_x' = -0.8 \text{ V}}$$



2) Kill 2A source

$$2V_x'' = V_1'' \left( \frac{1}{6} + \frac{1}{3} \right) - 18V \times \frac{1}{3}$$


$$V_x'' = 18 - V_1''$$

$$2(18 - V_1'') = \frac{1}{2} V_1'' - 6$$

$$36 + 6 = 2.5 V_1''$$

$$\therefore V_1'' = \frac{42}{2.5} = 16.8 \text{ V}$$
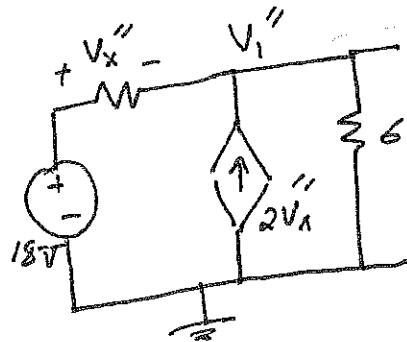
$$\boxed{V_x'' = 18 - 16.8 = 1.2 \text{ V}}$$



$$3) V_x = V_x' + V_x'' = -0.8 + 1.2 = 0.4 \text{ V}$$

Problem3: (10 points) To assess "a" student outcome  
 For the circuit of Fig.(3), find power dissipated in the  $0.2375 \Omega$  resistor.

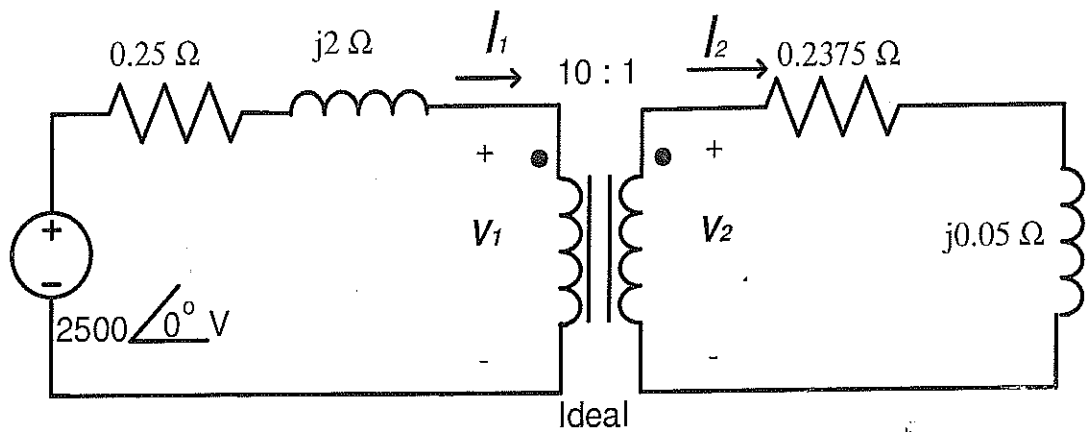


Fig.(3)

$$2500 \angle 0^\circ = (0.25 + j2) I_1 + V_1$$

$$V_1 = 10 V_2$$

$$V_2 = I_2 (0.2375 + j0.05)$$

$$V_1 = 10 \cdot I_2 (0.2375 + j0.05)$$

$$V_1 = 10 \cdot 10 I_1 (0.2375 + j0.05) \quad \dots (1)$$

$$V_1 = 2500 \angle 0^\circ - (0.25 + j2) I_1 \quad \dots (2)$$

equalizing (1) & (2)

$$100 I_1 (0.2375 + j0.05) = 2500 \angle 0^\circ - (0.25 + j2) I_1$$

$$((23.75 + 0.25) + j7) I_1 = 2500 \angle 0^\circ$$

$$I_1 = \frac{2500 \angle 0^\circ}{24 + j7} = \frac{2500 \angle 0^\circ}{25 \angle 16.26^\circ} = 100 \angle -16.26^\circ$$

$$I_2 = 10 I_1 = 1000 \angle -16.26^\circ$$

$$P_{0.2375 \Omega} = |I_{rms}|^2 \cdot R = \left(\frac{1000}{\sqrt{2}}\right)^2 \cdot R = 118.75 \text{ Watt}$$

Problem 4. (15 points) To assess "e" student outcome

The following three loads are connected in parallel to a 240Vrms 60 Hz Ac generator:

Load #1 has  $P_1 = 600\text{KW}$  and has a  $\text{pf}_1 = 0.8$  lagging.

Load #2 has  $P_2 = 400\text{KW}$  and has a  $|S_2| = 500\text{KVA}$  and has a lagging power factor.

Load #3 has  $Q_3 = -207\text{KVAR}$  and has a  $\text{pf}_3 = 0$  leading.

- Determine the total apparent power of the three loads.
- Determine the power factor of the combined load.
- Determine the value of capacitance or inductance that will need to be added in order to make the overall  $\text{pf} = 1.0$ , assuming that the voltage across the load is to be kept at 240Vrms (with  $\omega = 377\text{rad/sec}$ )


Solution

load 1

$$\theta_1 = \cos^{-1} \text{pf}_1 = \cos^{-1} 0.8 = 36.87^\circ$$

$$|S_1| = P_1 = \frac{P_1}{\text{pf}_1} = \frac{600}{0.8} = 750\text{KVA}$$

$$Q_1 = |S_1| \sin 36.87^\circ = 450\text{KVAR}$$

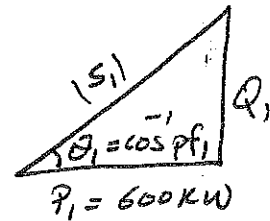

load 2

$$P_2 = 400\text{KW}$$

$$|S_2| = P_2 = 500\text{KVA}$$

$$Q_2 = |S_2| \sin 36.87^\circ = 300\text{KVAR}$$

load 3

$$P_3 = 0$$

$$Q_3 = -207\text{KVAR}$$

$$|S_3| = 207\text{KVA}$$

$$S_T = (P_1 + P_2 + P_3) + j(Q_1 + Q_2 + Q_3) = (1000 + j543)\text{KVA}$$

$$1) |S_T| = P_{AT} = \sqrt{1000^2 + 543^2} = 1138\text{KVA}$$

$$\theta_T = \tan^{-1} \left( \frac{543}{1000} \right) = 28.5^\circ$$

$$2) \text{pf}_T = \cos \theta_T = 0.878 \text{ lagging}$$

$$3) Q_C = -\omega C V_{\text{rms}}^2 = -543\text{KVAR}$$

$$\therefore C = \frac{543\text{KVAR}}{377 \times 240^2} \approx 25\text{mf}$$

ENEE2301-Network Analysis 1  
 Final Exam-January 19<sup>th</sup>, 2016  
 Instructors: M. Jubeh , N. Ismail & Khader Mohammad

Student Name: \_\_\_\_\_

ID: \_\_\_\_\_

Section: \_\_\_\_\_

**Part Two:**

**Problem5.** (15 points) *To assess "e" student outcome*  
 The switch in Fig.(5) has been in position (a) for a long time .  
 At  $t = 0$  , it moves to position (b).  
 Calculate  $i_x(t)$  for all  $t > 0$  .



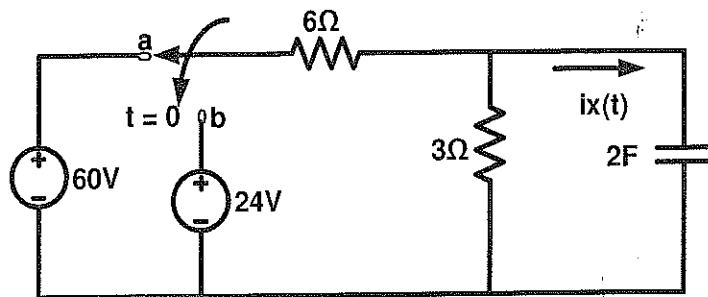


Fig.(5)

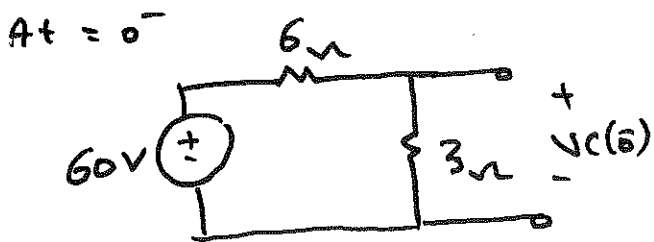

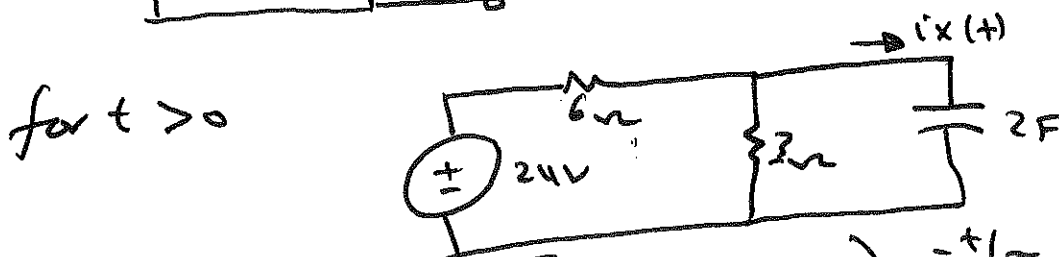
$$\therefore v_C(0^-) = \frac{3}{3+6} \cdot 60 = 20 \text{ V}$$



$$i_x(t) = i_x(\infty) + (i_x(0^+) - i_x(\infty)) e^{-t/\tau}$$

$$i_x(\infty) = 0$$

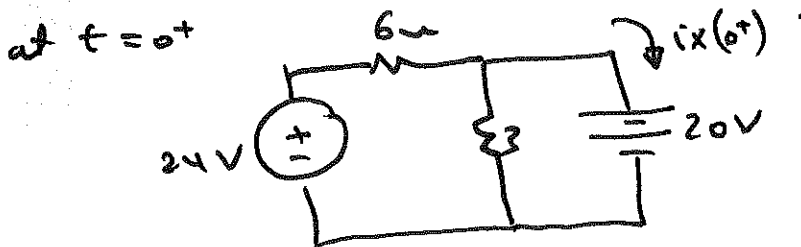

$$i_x(0^+) = \frac{24-20}{6} = \frac{20}{3}$$

$$i_x(0^+) = -6 \text{ A}$$

$$\tau = R_{TH} C \quad ; \quad R_{TH} = 6\Omega \parallel 3\Omega = 2\Omega \rightarrow \tau = \frac{4}{5}$$


$$\therefore i_x(t) = -6 e^{-t/4} \text{ A} \quad \text{for } t > 0$$

Problem 6. ( 10 points) To assess "a" student outcome

After being open for a long time, the switch in the circuit of Fig.(6) is closed at  $t = 0$ .


- Find  $v_C(0^-)$  and  $i_L(0^-)$ .
- Find the differential equation describing  $i_L(t)$ , for  $t > 0$ .
- Find the characteristic equation of the circuit of Fig.(6).

d) Find  $\frac{di_L(0^+)}{dt}$

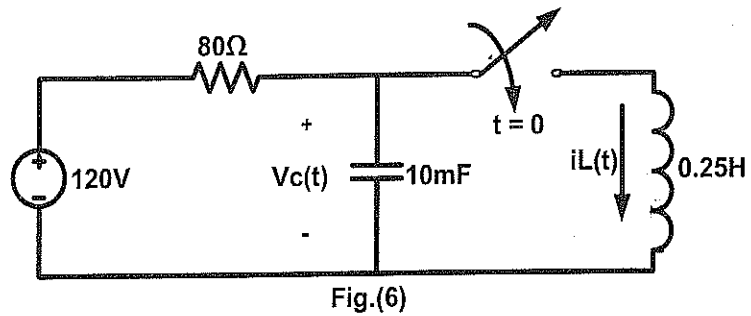

a)  $v_C(0^-) = 120V$ ,  $i_L(0^-) = 0$

b) for  $t > 0$

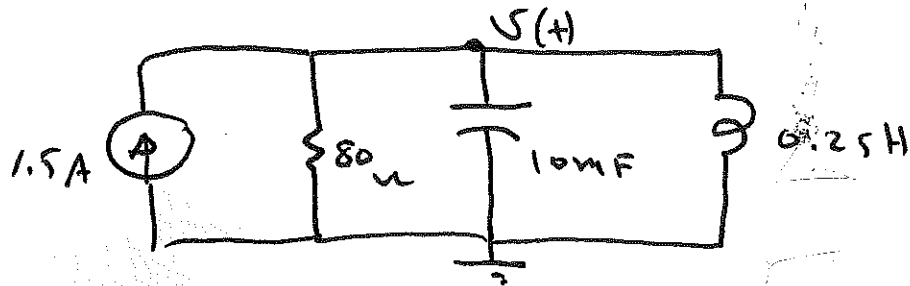

KCL :

$$1.5 = \frac{v(t)}{80} + 10 \times 10^{-3} \frac{dv(t)}{dt} + i_L(t)$$

$$v(t) = L \frac{di(t)}{dt} = 0.25 \frac{di(t)}{dt}$$

$$\therefore 1.5 = 2.5 \times 10^{-3} \frac{d^2 i(t)}{dt^2} + 3.125 \times 10^{-3} \frac{di(t)}{dt} + i(t)$$

c)  $0 = s^2 + 1.25s + 400$

d)  $v_C(0^+) = v_L(0^+) = L \frac{di(0^+)}{dt}$

$$\therefore \frac{di(0^+)}{dt} = \frac{v_C(0^+)}{L} = 480$$



Student Name: \_\_\_\_\_

ID: \_\_\_\_\_


Section: \_\_\_\_\_

**Part Three:**

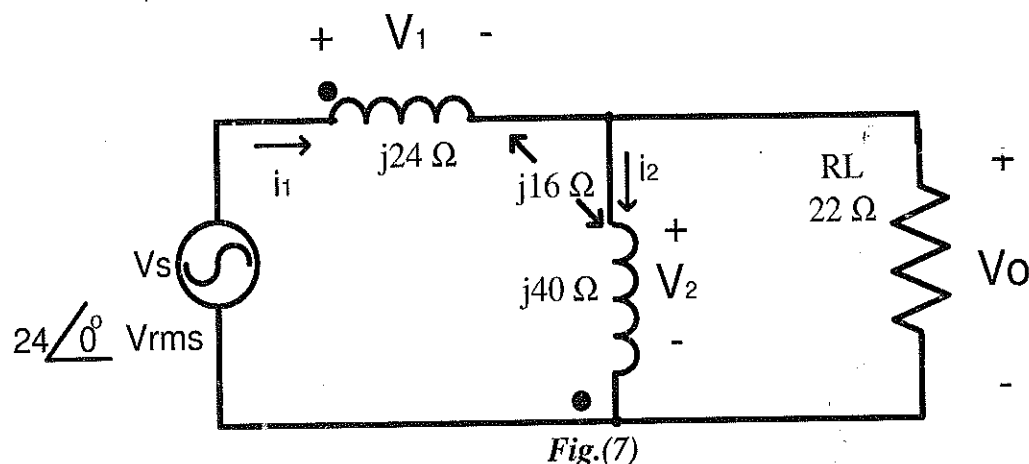**Problem7: ( 12 points) To assess "a" student outcome**

For the circuit of Fig.(7) , use the thevenin's equivalent circuit to find voltage  $V_o$

(note that the two inductors have a mutual inductance between them)



$V_{oc} = V_{th} = V_2$

$\bar{I}_1 = \bar{I}_2 = \bar{I}$

$V_1 = j24\bar{I}_1 - j16\bar{I}_2 = j8\bar{I}$

$V_2 = -j16\bar{I}_1 + j40\bar{I}_2 = j24\bar{I}$

also  $24\angle 0^\circ = V_1 + V_2 = j8\bar{I} + j24\bar{I}$

$\therefore \bar{I} = \frac{24}{j32} = -j0.75 \text{ Arms}$

$V_{oc} = V_2 = (j24) \cdot (-j\frac{3}{4}) = 18\angle 0^\circ \text{ Vrms}$

$I_{sc}$  :  $V_2 = 0 = -j16\bar{I}_1 + j40\bar{I}_2$   
 $\bar{I}_1 = \bar{I}_2$

$\therefore j16\bar{I}_1 = j40\bar{I}_2$

$\bar{I}_1 = 2.5\bar{I}_2 \dots (1)$



$V_s = j24\bar{I}_1 - j16\bar{I}_2$

$= j24(2.5\bar{I}_2) - j16\bar{I}_2$

$V_s = j60\bar{I}_2 - j16\bar{I}_2 \Rightarrow \bar{I}_2 = \frac{24}{j44} = -j\frac{6}{11}$

$I_{sc} = \bar{I}_1 - \bar{I}_2 = (2.5 - 1)\bar{I}_2 = 1.5\bar{I}_2 = 1.5(-j\frac{6}{11}) = -j0.818 \text{ Arms}$

$\therefore Z_{th} = \frac{V_{oc}}{I_{sc}} = \frac{18\angle 0^\circ}{0.818\angle -90^\circ} = 22\angle 90^\circ \Omega$  ;  $V_o = \frac{R_L}{R_L + Z_{th}} \cdot V_{th} = \frac{22}{22 + j22} \cdot 18 = 12.73 \angle 45^\circ \text{ V}$

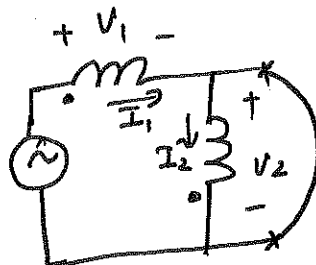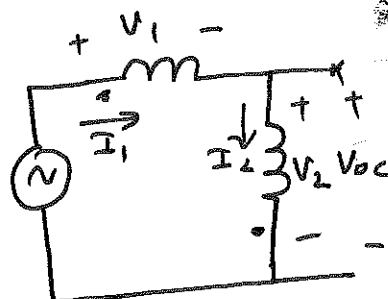

**Problem8: ( 13 points) To assess "a" student outcome**


For the following balanced three phase system shown in Fig.(8), the source is  $\Delta$ -connected positive sequence and the load consists of parallel  $\Delta$ -Y loads, given:

$$\bar{V}_{AB} = 380 \angle 30^\circ \text{ V}; Z_T = (0.1)\Omega; Z_Y = (-j1)\Omega; Z_\Delta = (6 + j9)\Omega$$

1) Calculate the phase currents of the delta connected load:  $\bar{I}_{AB\Delta}, \bar{I}_{BC\Delta}, \bar{I}_{CA\Delta}$

2) Calculate the phase currents of the Y - connected load:  $\bar{I}_{AN}, \bar{I}_{BN}, \bar{I}_{CN}$

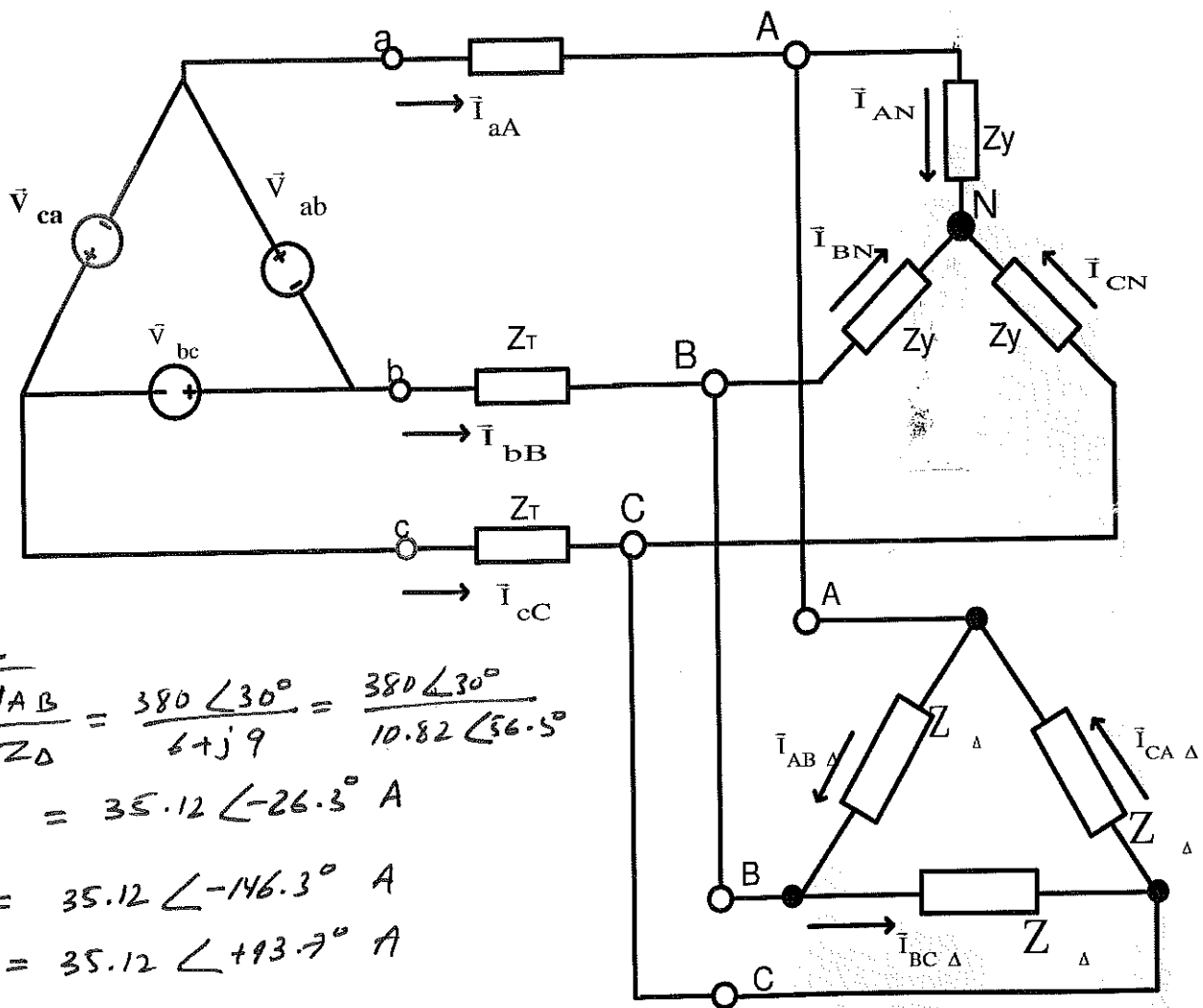3) Calculate the magnitude of the line current  $I_{aA}$



1)  $\Delta$  load

$$\bar{I}_{AB\Delta} = \frac{V_{AB}}{Z_\Delta} = \frac{380 \angle 30^\circ}{6 + j9} = \frac{380 \angle 30^\circ}{10.82 \angle 56.5^\circ} = 35.12 \angle -26.3^\circ \text{ A}$$

$$\bar{I}_{BC} = 35.12 \angle -146.3^\circ \text{ A}$$

$$\bar{I}_{CA} = 35.12 \angle +93.7^\circ \text{ A}$$

2) Y-load

$$\bar{I}_{AN} = \frac{V_{AN}}{Z_Y};$$


$$V_{AN} = \frac{V_{AB}}{\sqrt{3} \angle 30^\circ} = \frac{380 \angle 30^\circ}{\sqrt{3} \angle 30^\circ} = 219.4 \angle 0^\circ \text{ V}$$

$$\bar{I}_{AN} = \frac{219 \angle 0^\circ}{-j1} = \frac{219 \angle 0^\circ}{1 \angle -90^\circ} = 219.4 \angle 90^\circ \text{ A}, \bar{I}_{BN} = 219.4 \angle -50^\circ \text{ A}$$

$$\bar{I}_{CN} = 219.4 \angle 210^\circ \text{ A}$$

Fig.(8)

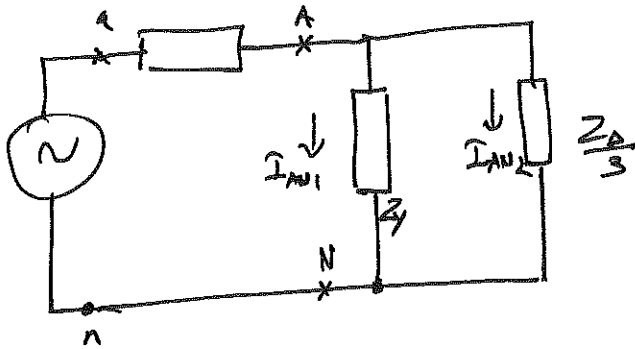3) To find  $I_{AA}$ , we construct single-phase equivalent circuit



$$I_{AA} = I_{AN1} + I_{AN2}$$

$$I_{AN1} = 219.4 \angle 90^\circ \quad (\text{calculated earlier})$$

$$I_{AN2} = \frac{\overline{V_{AN}}}{\frac{Z_D}{3}} = \frac{219.4 \angle 0^\circ}{\frac{6+j9}{3}} = \frac{219.4 \angle 0^\circ}{2+j3} = \frac{219.4 \angle 0^\circ}{3.606 \angle 56.3^\circ} = 60.84 \angle -56.3^\circ \text{ A}$$

$$\begin{aligned} I_{AA} &= 219.4 \angle 90^\circ + 60.84 \angle -56.3^\circ \\ &= j219.4 + 36.504 - j48.67 = 36.504 + j170.73 \\ &= 174.58 \angle 77.93^\circ \end{aligned}$$

OR

$$\begin{aligned} I_{AA} &= \frac{\overline{V_{AN}}}{Z_Y \parallel \frac{Z_D}{3}} = \frac{219.4 \angle 0^\circ}{-j1 \parallel 2+j3} = \frac{219 \angle 0^\circ}{1.275 \angle -78.7^\circ} \\ &= 172.1 \angle 78.7^\circ \end{aligned}$$

where

$$\begin{aligned} -j1 \parallel (2+j3) &= \frac{-j(2+j3)}{-j+(2+j3)} = \frac{3-j2}{2+j2} = \frac{3.605 \angle -33.7^\circ}{2.83 \angle 45^\circ} \\ &= 1.275 \angle -78.7^\circ \end{aligned}$$

GOOD LUCK

Mohammad Jubeh, Nasser Ismail & Khader Mohammad