


Electrical and Computer Engineering Department
Network Analysis I, ENEE2301

Name: First Exam 17/4/2018

No.: Sec:



The exam Five question for 90 min.

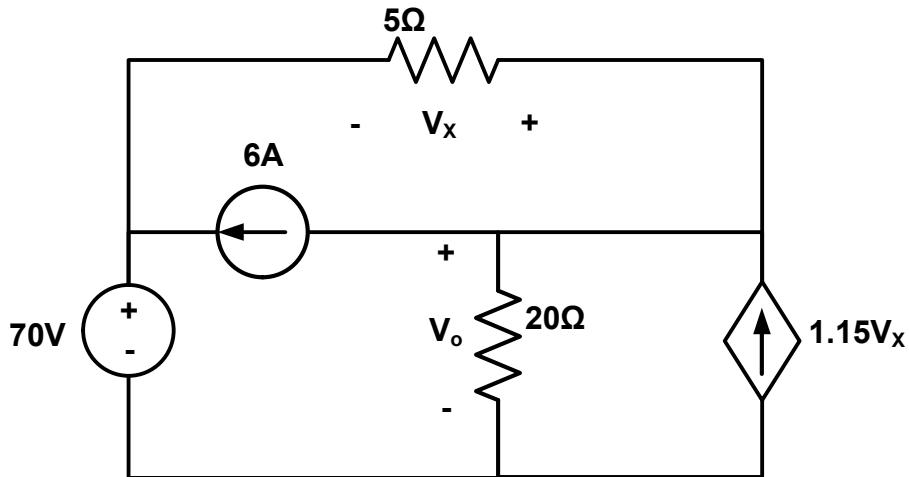Q1) Find V_o by Node-Voltage Method? (20 marks)



$$\begin{aligned}
 V_x &= V_o - 70 \\
 6 + \frac{V_o}{20} + \frac{V_o - 70}{5} - 1.15V_x &= 0 \\
 6 + \frac{V_o}{20} + \frac{V_o - 70}{5} - 1.15(V_o - 70) &= \\
 V_o &= \frac{6 - 14 + 80.5}{-0.05 - 0.2 + 1.15} = \frac{725}{9} = 80.56V
 \end{aligned}$$

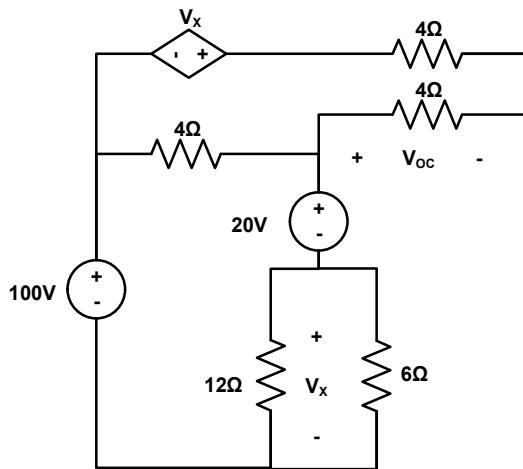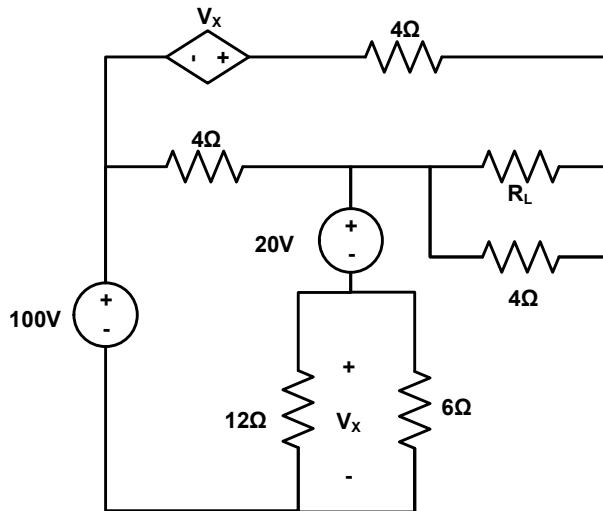
Q2) Find the maximum power delivered to the load R_L ? (20 marks)



$$\frac{V_{oc}}{4} + \frac{V_x + 20 - 100}{4} + \frac{V_x}{4} + \frac{V_x + 20}{4} = 0$$

$$V_x + 20 = 20V$$

$$V_{oc} = 40V$$

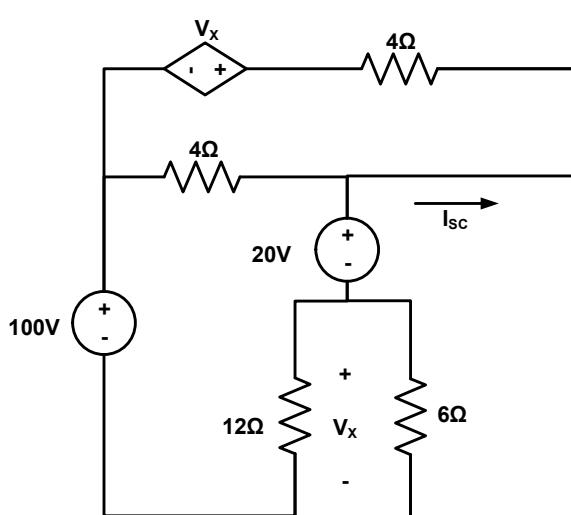



$$I_{sc} - \frac{100}{4} - \frac{20}{4} = 0$$

$$I_{sc} = 30A$$

$$R_L = \frac{V_{oc}}{I_{sc}} = \frac{4}{3} \Omega$$


$$P_{MAX} = \frac{V_{oc}^2}{4R_L} = \frac{40^2}{4 * \frac{4}{3}} = 300W$$

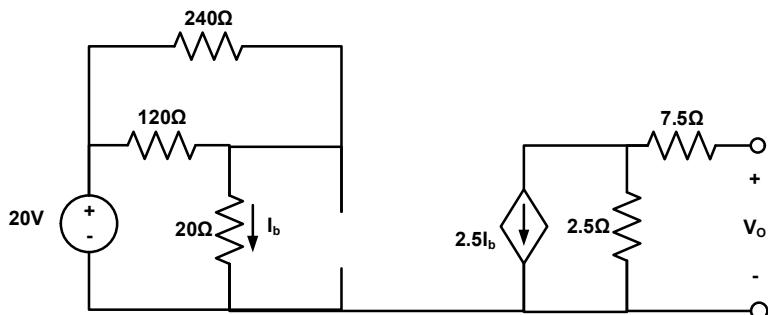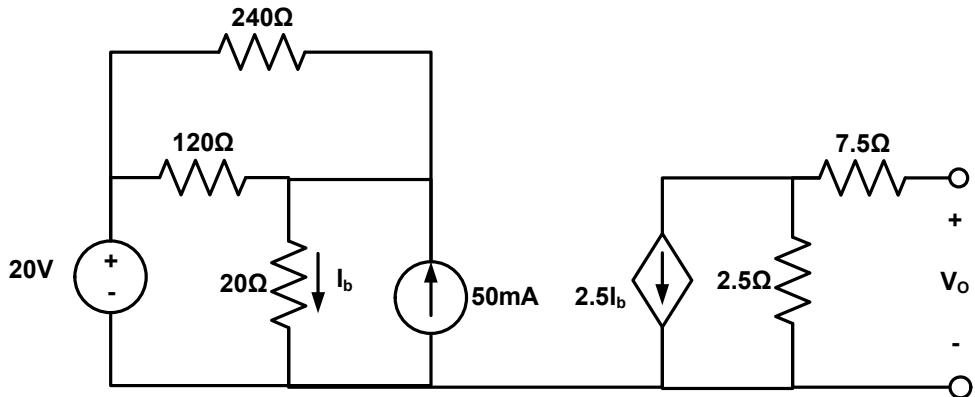Q3) Find V_o by Superposition Method? (20 marks)



$$I_b = \frac{20}{240//120 + 20} = 0.2A$$

$$V'_o = -2.5I_b * 2.5 = -1.25V$$


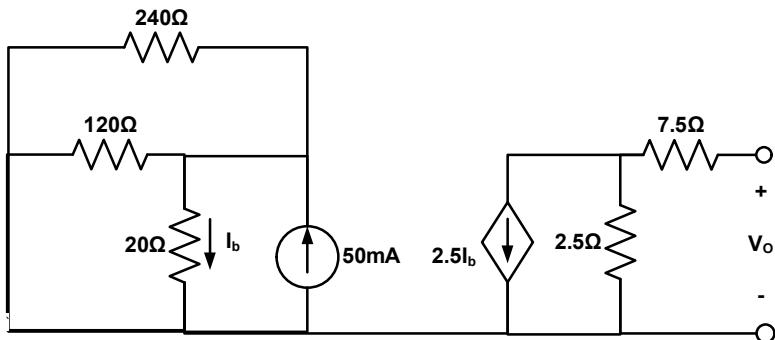


$$I_b = \frac{240//120}{240//120 + 20} 50m = 40m$$


$$V''_o = -2.5I_b * 2.5 = -0.25V$$

$$V_o = V'_o + V''_o = -1.5V$$

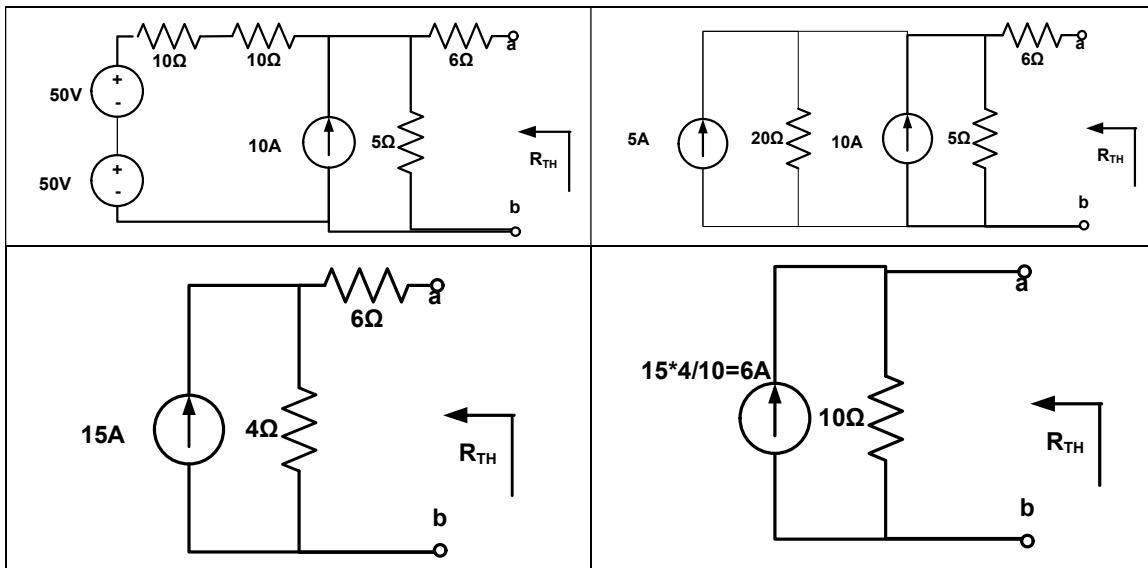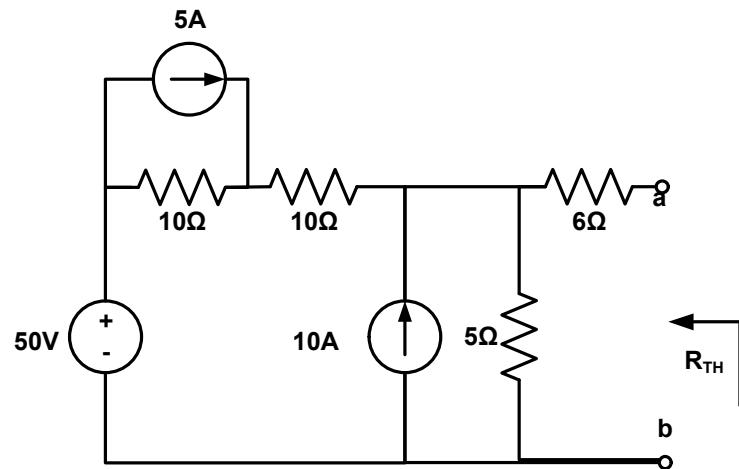Q4) Find Norton equivalent circuit between (a,b) ? (20 marks)



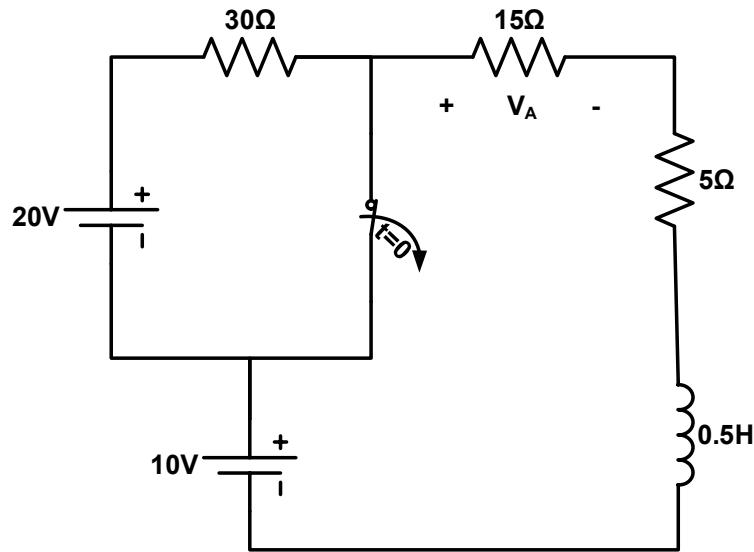Q5) The switch has been closed for a long time and then it was opened at $t=0$.
 Find V_A for $t>0$? (20 marks)



$$i_L(0) = \frac{10}{20} = 0.5A$$

$$i_L(\infty) = \frac{30}{50} = 0.6A$$

$$i_L(t) = 0.6 + (0.5 - 0.6)e^{-\frac{50}{0.5}t}$$

$$V_A(t) = 15 \left[0.6 - (0.1)e^{-\frac{50}{0.5}t} \right]$$

$$V_A(t) = 9 - 1.5e^{-100t}V$$

Good Luck