
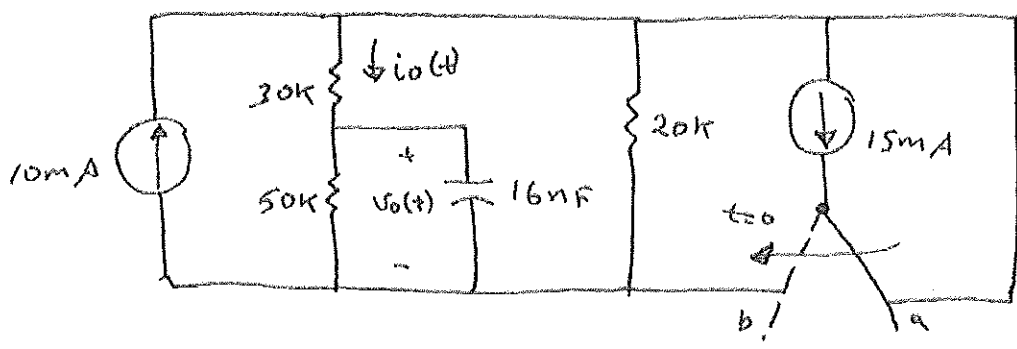


7.54 Q2

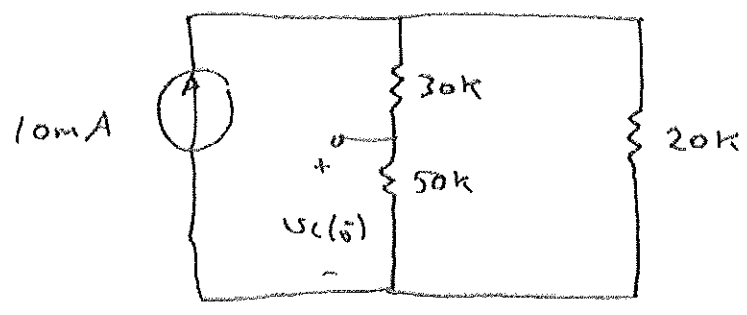


for $t < 0$



$$V_c(s) = (50k) \left(\frac{20k}{20k + 80k} \right) (10mA) = 100 \underline{\underline{V}}$$

at $t = \infty$

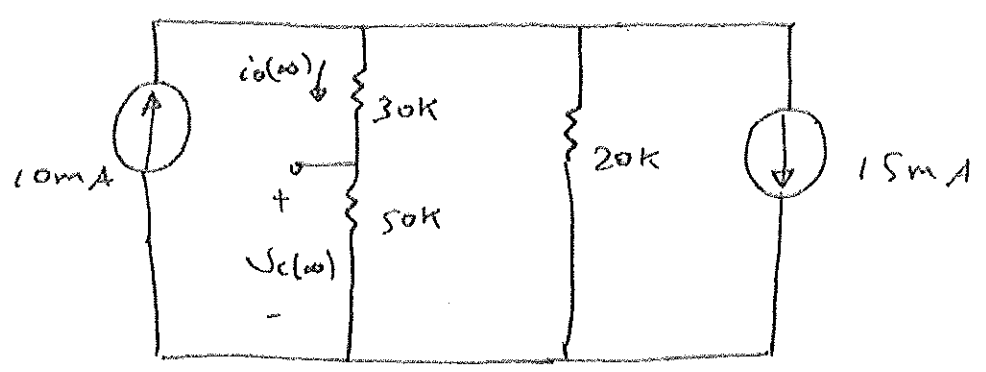


$$V_c(\infty) = (10mA - 15mA) \left(\frac{20k}{20k + 80k} \right) (50k) = -50 \underline{\underline{V}}$$

Q.2

$$i_0(\infty) = (10\text{mA} - 15\text{mA}) \left(\frac{20\text{k}}{20\text{k} + 80\text{k}} \right) = -1\text{mA}$$

at $t = 0^+$

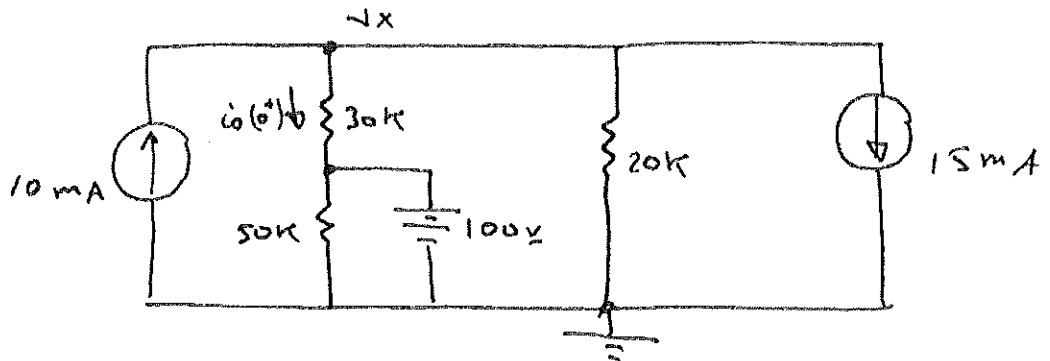

$$v_0(0^+) = 100 \text{ V}$$

$$10\text{mA} = \frac{v_x - 100}{30\text{k}} + 15\text{mA} + \frac{v_x}{20\text{k}}$$

$$v_x = -20 \text{ V}$$

$$i_0(0^+) = \frac{v_x - v_0(0^+)}{30\text{k}} = -4\text{mA}$$

$$\tau = R_{TH} C$$

$$R_{TH} = (30\text{k} + 20\text{k}) \parallel 50\text{k} = 25\text{k}$$

$$\tau = 0.4\text{ms}$$

$$i_0(t) = i_0(\infty) + (i_0(0^+) - i_0(\infty)) e^{-t/\tau} \quad t > 0$$


$$i_0(t) = - \left(1 + 3 e^{-2500t} \right) \text{ mA} \quad \text{for } t > 0$$

$$v_0(t) = v_0(\infty) + (v_0(0^+) - v_0(\infty)) e^{-t/\tau} \quad \text{for } t > 0$$



$$v_0(t) = \left(-50 + 150 e^{-2500t} \right) \text{ V} \quad \text{for } t > 0$$

Q3


Page 1

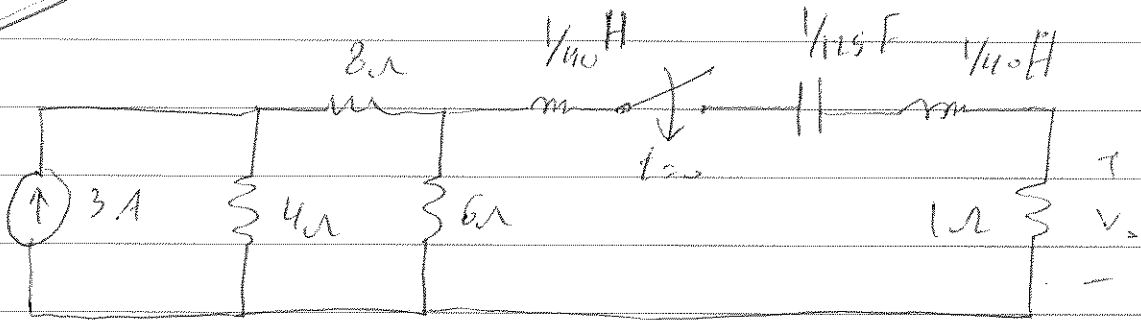

find V_o for $t < 0$

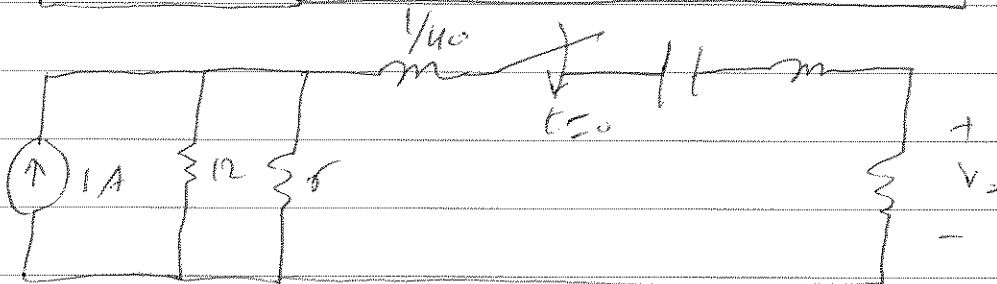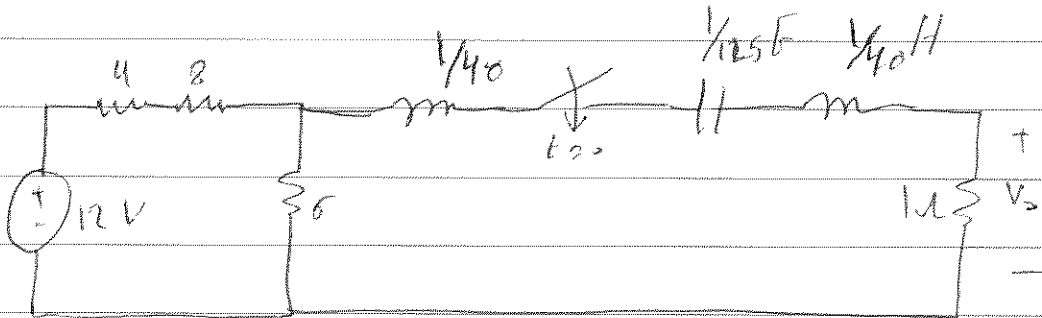

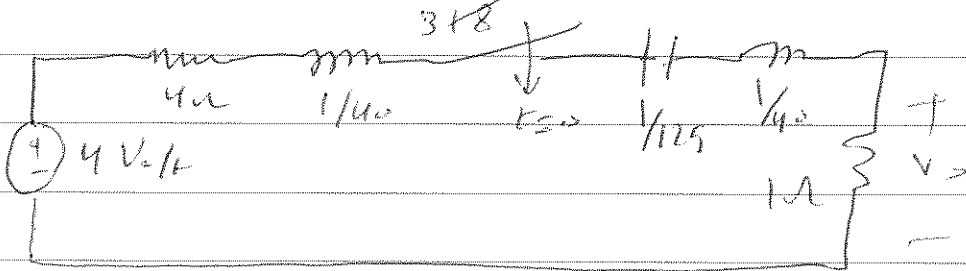
$$12 \parallel 6 = \frac{12 \times 6}{12 + 6} = 4 \Omega$$



for $t < 0$ or $t = 0^-$:

$$V_o(0^-) = 0 \text{ Volt} \quad i(0^-) = 0 \text{ A}$$

for $t > 0$

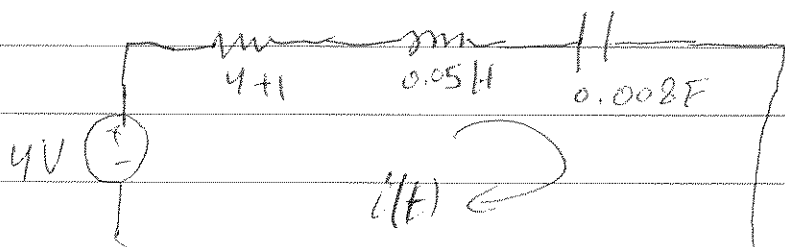

find $i(t)$ for $t > 0$

$$-V_s + R i(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int_0^t i(t) dt + V_c(0^-) = 0 \quad \text{--- (1)}$$

by differentiation:

$$R \frac{di(t)}{dt} + L \frac{d^2 i(t)}{dt^2} + \frac{1}{C} i(t) = 0 \quad \text{--- (2)}$$

$$\alpha = \frac{R}{2L} = \frac{5}{2(0.05)} = 50$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(0.05)(0.008)}} = 50$$

$\alpha = \omega_0$ (critical damped response)

$$i(t) = i_n(t) + i_p(t)$$

$i(t)$ Second order homogeneous differential equation:

i.e. $i(t) = i_n(t) \quad i_p(t) = 0$

$$i(t) = A_1 t e^{-\alpha t} + A_2 e^{-\alpha t} \quad \text{for } t > 0$$

$$i(t) = A_1 t e^{-50t} + A_2 e^{-50t}$$

To find A_1 & A_2 we need $i(0^+)$ & $\frac{di(0^+)}{dt}$

$$i(0^+) = i(0^-) = i_c(0^+) = 0$$

using eq (1) at $t=0^+$

$$-V_s + R i(0^+) + L \frac{di(0^+)}{dt} + \frac{1}{C} \int_0^{0^+} i(t) dt \neq 0 = 0$$

$$-4 + R(0) + 0.05 \frac{di(0^+)}{dt} + 0 = 0$$

$$\frac{di(0^+)}{dt} = \frac{4}{0.05} = 80$$

$$i(t) = A_1 t e^{-50t} + A_2 e^{-50t}$$

at $t = 0^+$

$$i(0^+) = A_1(0) + A_2(1) = 0$$

$$\Rightarrow A_2 = 0$$

$$\Rightarrow i(t) = A_1 t e^{-50t}$$

$$\frac{di(t)}{dt} = A_1 \left[t(-50) e^{-50t} + e^{-50t} (1) \right]$$

at $t = 0^+$

$$\frac{di(0^+)}{dt} = 80 = \left[A_1 \left((0) + 1 \right) \right] \Rightarrow A_1 = 80$$

$$\Rightarrow i(t) = 80 t e^{-50t}$$

$$v_L(t) = R i(t) = 80 t e^{-50t} \text{ for } t > 0$$