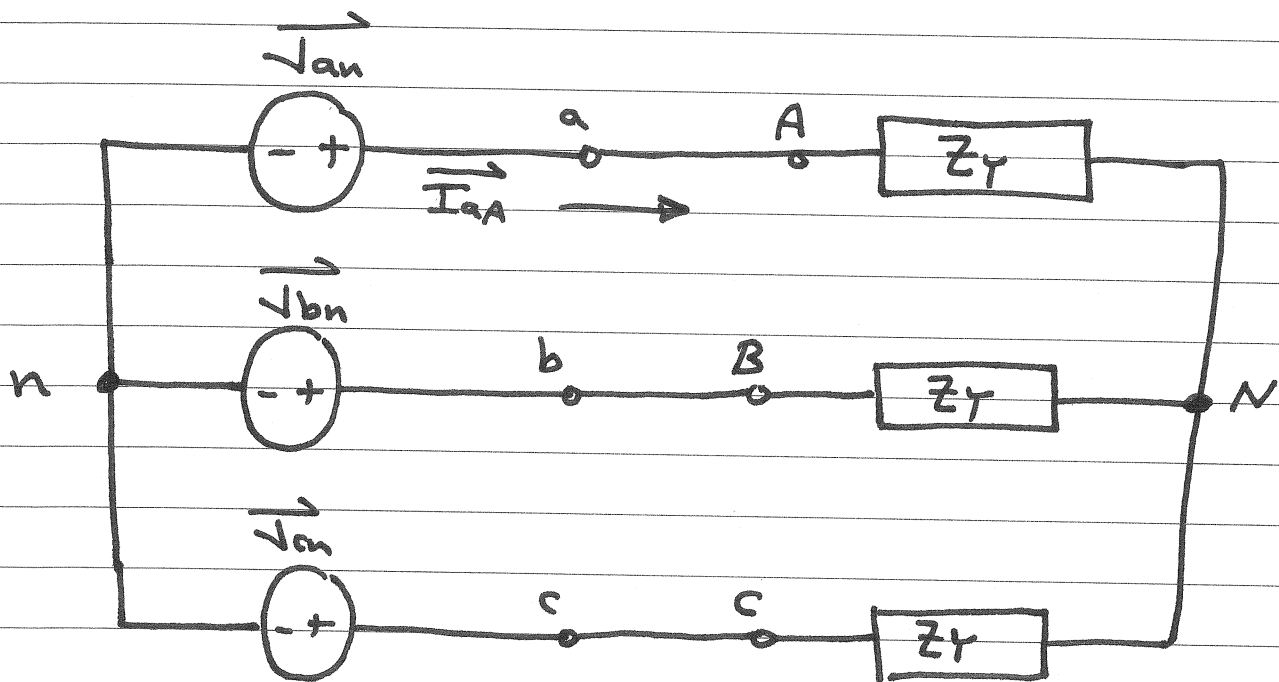


Power in a Balanced System



* The total instantaneous power in a balanced three phase system is Constant

$$v_{AN}(t) = \sqrt{2} V_p \cos \omega t$$

$$v_{BN}(t) = \sqrt{2} V_p \cos (\omega t - 120^\circ)$$

$$v_{CN}(t) = \sqrt{2} V_p \cos (\omega t + 120^\circ)$$

$$i_{aA}(t) = \sqrt{2} I_p \cos (\omega t - \theta)$$

$$i_{bB}(t) = \sqrt{2} I_p \cos (\omega t - \theta - 120^\circ)$$

$$i_{cC}(t) = \sqrt{2} I_p \cos (\omega t - \theta + 120^\circ)$$

$$P(t) = P_a(t) + P_b(t) + P_c(t)$$

$$P_a(t) = 2V_p I_p \cos \omega t \cos (\omega t - \Theta)$$

$$P_b(t) = 2V_p I_p \cos (\omega t - 120^\circ) \cos (\omega t - \Theta - 120^\circ)$$

$$P_c(t) = 2V_p I_p \cos (\omega t + 120^\circ) \cos (\omega t - \Theta + 120^\circ)$$


using $\cos A \cos B = \frac{1}{2} [\cos (A+B) + \cos (A-B)]$

$$P(t) = \sqrt{3} I_p [3 \cos \Theta]$$

$$P(t) = 3V_p I_p \cos \Theta$$

Power Calculation in a Balanced 3 ϕ Systems

1) Average Power in Balanced Y-Load

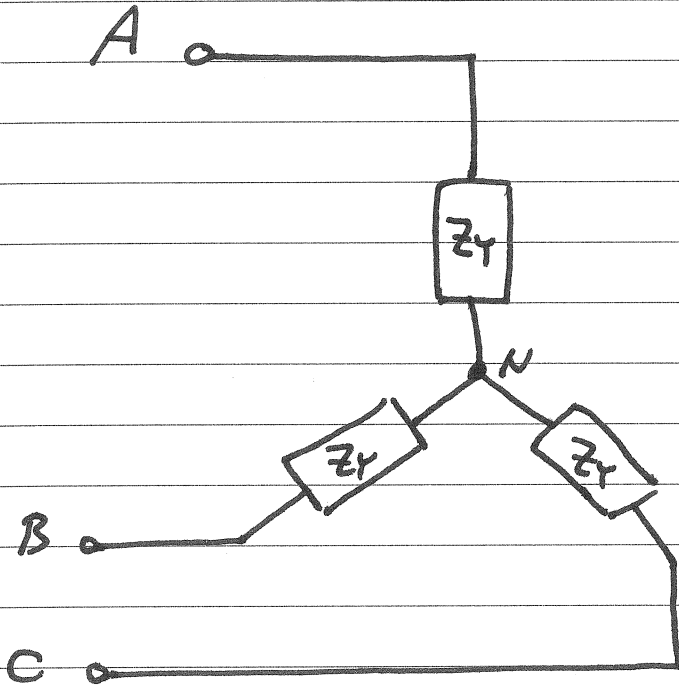

$$P_A = V_{AN} I_{AN} \cos (\theta_{V_A} - \phi_{i_A})$$

$$P_B = V_{BN} I_{BN} \cos (\theta_{V_B} - \phi_{i_B})$$

$$P_C = V_{CN} I_{CN} \cos (\theta_{V_C} - \phi_{i_C})$$

$$V_{AN} = V_{BN} = V_{CN} = V_{\phi}$$

$$I_{AN} = I_{BN} = I_{CN} = I_{\phi}$$

$$\theta_{V_A} - \phi_{i_A} = \theta_{V_B} - \phi_{i_B} = \theta_{V_C} - \phi_{i_C}$$

$$\therefore P_A = P_B = P_C = \sqrt{\phi} I_{\phi} \cos \theta$$

$$P_T = 3 \sqrt{\phi} I_{\phi} \cos \theta$$

$$\text{But } \sqrt{\phi} = \frac{V_L}{\sqrt{3}}$$

$$I_{\phi} = I_L$$

$$\therefore P_T = \sqrt{3} V_L I_L \cos \theta$$

2) Reactive Power in Balanced Y-load

$$Q_A = Q_B = Q_C = \sqrt{\phi} I_{\phi} \sin \theta$$

$$Q_T = 3 \sqrt{\phi} I_{\phi} \sin \theta$$

$$Q_T = \sqrt{3} V_L I_L \sin \theta$$


3) Complex Power in Balanced Y-load

$$\vec{S}_A = \vec{S}_B = \vec{S}_C = \sqrt{\phi} \cdot \vec{I}_{\phi}^* = P_{\phi} + j Q_{\phi}$$

$$\vec{S}_T = 3 \vec{S}_{\phi} = 3 \sqrt{\phi} \cdot \vec{I}_{\phi}^*$$

$$\vec{S}_T = \sqrt{3} V_L I_L \angle \theta$$

Power Calculation in Balanced Δ -load

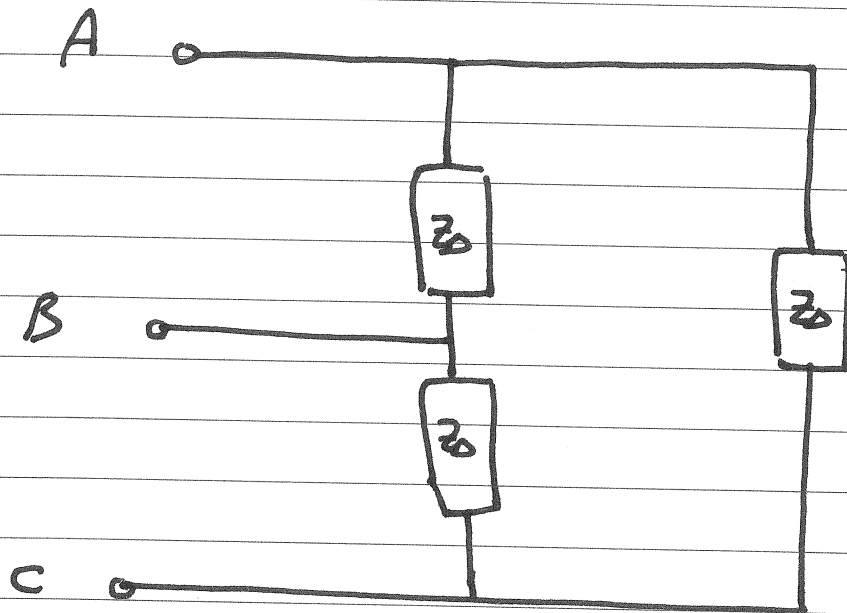

$$P_A = V_{AB} I_{AB} \cos (\theta_{V_{AB}} - \phi_{i_{AB}})$$

$$P_B = V_{BC} I_{BC} \cos (\theta_{V_{BC}} - \phi_{i_{BC}})$$

$$P_C = V_{CA} I_{CA} \cos (\theta_{V_{CA}} - \phi_{i_{CA}})$$

$$V_{AB} = V_{BC} = V_{CA}$$

$$I_{AB} = I_{BC} = I_{CA}$$

$$\theta_{V_{AB}} - \phi_{i_{AB}} = \theta_{V_{BC}} - \phi_{i_{BC}} = \theta_{V_{CA}} - \phi_{i_{CA}}$$

$$\therefore P_A = P_B = P_C = P_\phi = \sqrt{3} I_\phi \cos \theta$$

$$P_T = 3 P_\phi = 3 V_\phi I_\phi \cos \theta$$

$$V_\phi = V_L$$

$$I_\phi = \frac{I_L}{\sqrt{3}}$$

$$\therefore P_T = \sqrt{3} V_L I_L \cos \theta$$

$$Q_\phi = V_\phi I_\phi \sin \theta$$

$$Q_T = 3 Q_\phi = 3 V_\phi I_\phi \sin \theta$$

$$Q_T = \sqrt{3} V_L I_L \sin \theta$$

$$\vec{S}_T = 3 \vec{S}_\phi$$


$$\vec{S}_\phi = \vec{V}_\phi \vec{I}_\phi^* = P_\phi + j Q_\phi$$

$$\vec{S}_T = P_T + j Q_T$$

$$\vec{S}_T = \sqrt{3} V_L I_L \angle \theta$$

Comparing the Power Loss

a) a single phase system

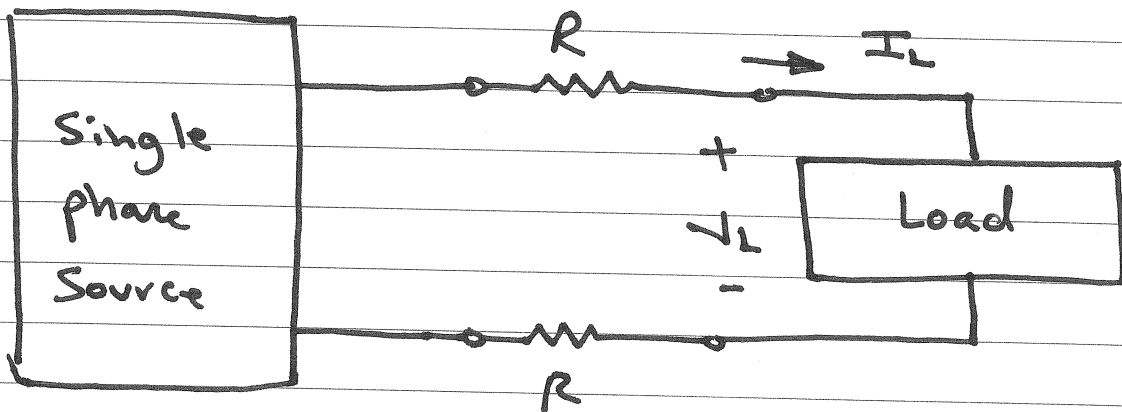


$$P_{Loss} = 2 I_L^2 \cdot R$$

$$I_L = \frac{P_L}{V_L \cdot Pf}$$

$$P_{Loss} = 2 \frac{P_L^2}{V_L^2 \cdot Pf^2} R$$

b) a three phase system

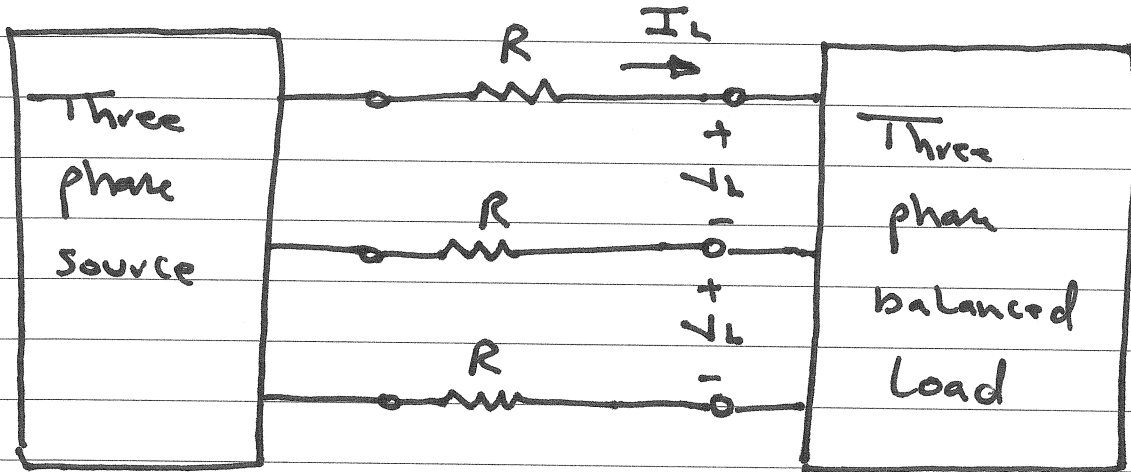

$$P_{Loss} = 3 I_L^2 \cdot R$$

$$I_L = \frac{P_L}{\sqrt{3} V_L \cdot Pf}$$

$$P_{Loss} = \frac{P_L^2}{\sqrt{3}^2 \cdot Pf^2} \cdot R$$


Example

A balanced 3 ϕ load requires 480 kW at a lagging power factor of 0.8.

The load is fed from a line having an impedance of $(0.005 + j0.025) \Omega/\phi$


The line voltage at the terminal of the load is 600 V rms

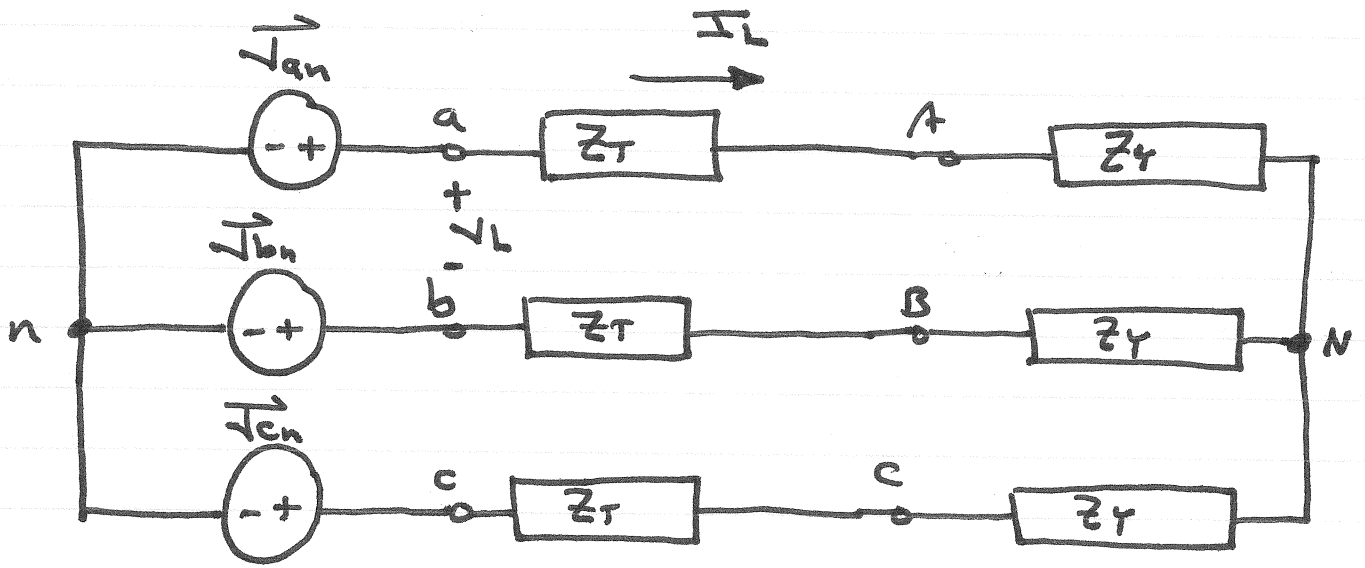- 1) Calculate the magnitude of the line current
- 2) Calculate the magnitude of the line voltage at the sending end of the line
- 3) Calculate the power factor at the sending end of the line.



Solution

Single phase representation

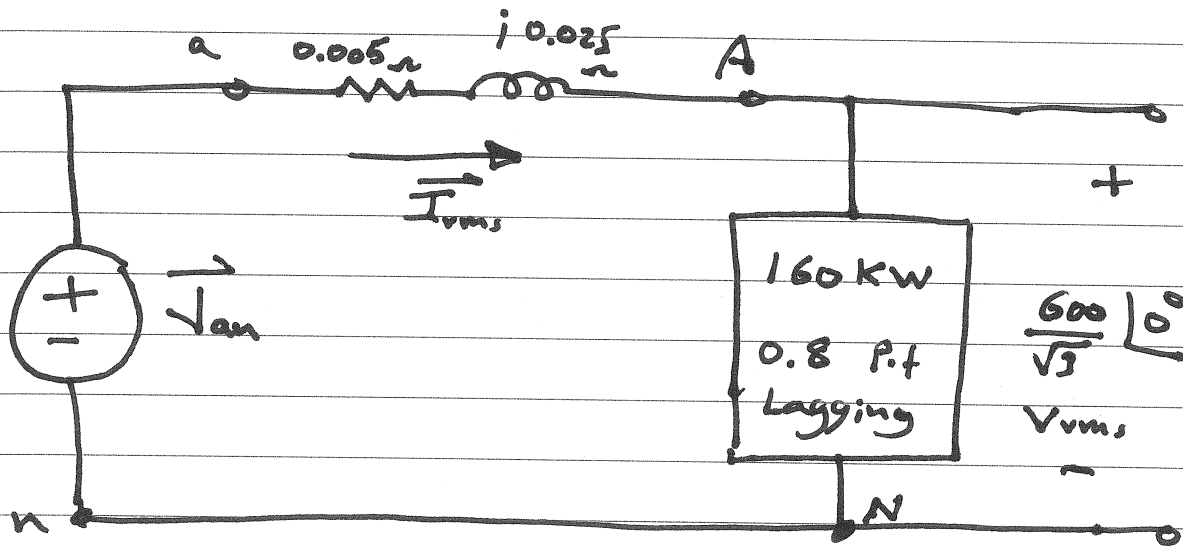

$$1) P_{av} = 160 \text{ kW}$$

$$Q = P_{av} \tan \cos^{-1} \text{P.f} = 120 \text{ KVAR}$$

$$\vec{S} = P_{av} + jQ$$

$$\vec{S} = 160 + j120 \text{ KVA}$$

$$\vec{S} = \vec{V}_{rms} \cdot \vec{I}_{rms}^*$$

$$\therefore \vec{I}_{rms} = 577.35 \angle -36.87^\circ \text{ A}_{rms}$$

$$\therefore I_L = 577.35 \text{ A}_{rms}$$

$$2) \vec{V}_{an} = (0.005 + j0.025) \vec{I}_{rms} + \frac{600}{\sqrt{3}} \angle 0^\circ$$

$$\vec{V}_{an} = 357.51 \angle 1.57^\circ \text{ V}_{rms}$$

$$\therefore V_{an} = 357.51 \text{ V}_{rms}$$

$$\therefore V_L = \sqrt{3} V_{an}$$

$$\therefore V_L = 619.23 \text{ V}_{rms}$$


$$3) P_f = \cos(\theta_r - \phi_i)$$

$$P_f = \cos(1.57^\circ + 36.87^\circ)$$

$$P_f = 0.783 \text{ Lagging}$$

Measuring Average Power in 3 ϕ system

The Two-Wattmeter method

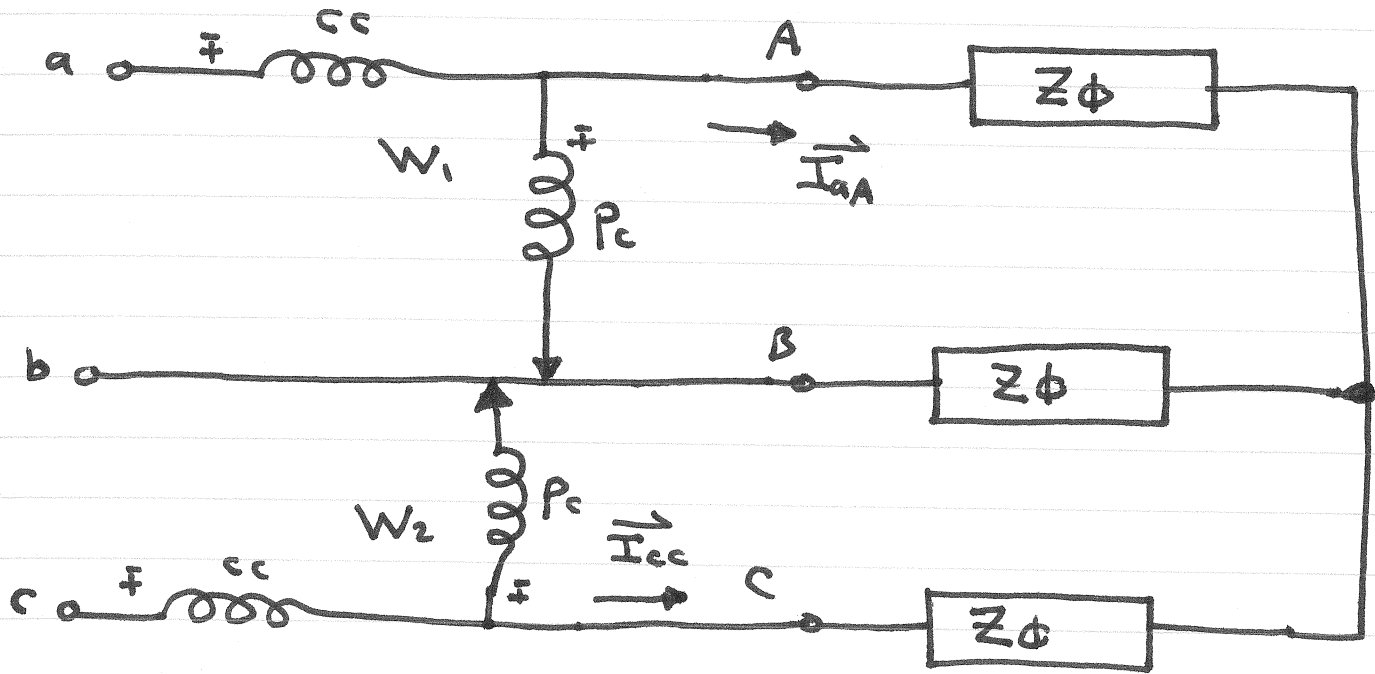

$$Z_{\phi} = |Z| \angle \theta_z ; \theta_z = \text{impedance angle}$$

$$W_1 = V_{AB} I_{aA} \cos \theta_1$$

$\theta_1 =$ The angle between \vec{V}_{AB} and \vec{I}_{aA}

$$\theta_1 = \theta_z + 30^\circ$$

$$\vec{V}_{AB} = \vec{V}_{AN} \sqrt{3} \angle 30^\circ$$

$$\vec{I}_{aA} = \vec{I}_{AN}$$

$$\therefore \theta_1 = \theta_z + 30^\circ$$

$$\therefore W_1 = \sqrt{L} I_L \cos (\theta_z + 30^\circ)$$

$$W_2 = \sqrt{V_B} I_{cc} \cos \Theta_2$$

$\Theta_1 =$ The angle between \vec{V}_{CB} and \vec{I}_{cc}

$$\Theta_2 = \Theta_1 - 30^\circ$$

$$\vec{V}_{CB} = -\vec{V}_{BC}$$

$$\vec{V}_{CB} = \vec{V}_{BC} \angle 180^\circ$$

$$\vec{V}_{CB} = \vec{V}_{CA} \angle -240^\circ \angle 180^\circ$$

$$\vec{V}_{CB} = \vec{V}_{CA} \angle -60^\circ$$

$$\vec{V}_{CB} = \sqrt{3} \vec{V}_{CN} \angle +30^\circ \angle -60^\circ$$

$$\vec{V}_{CB} = \sqrt{3} \vec{V}_{CN} \angle -30^\circ$$

$$\vec{I}_{cc} = \vec{I}_{cN}$$

$$\therefore \Theta_2 = \Theta_1 - 30^\circ$$

$$\therefore W_2 = \sqrt{V_L} I_L \cos (\Theta_1 - 30^\circ)$$

$$W_1 = V_L I_L \cos(\theta_2 + 30^\circ)$$

$$W_2 = V_L I_L \cos(\theta_2 - 30^\circ)$$

$$P_T = W_1 + W_2$$

$$\cos(\theta_2 + 30^\circ) = \cos\theta_2 \cos 30^\circ - \sin\theta_2 \sin 30^\circ$$

$$\cos(\theta_2 - 30^\circ) = \cos\theta_2 \cos 30^\circ + \sin\theta_2 \sin 30^\circ$$

$$\therefore W_1 + W_2 = V_L I_L (2 \cos\theta_2 \cos 30^\circ)$$

$$W_1 + W_2 = \sqrt{3} V_L I_L \cos\theta_2$$

Example

Calculate the reading of each wattmeter if the phase voltage at the load is $120\angle 0^\circ$ V rms

a) and $Z_\phi = (8 + j6) \Omega$

$$\vec{I}_{\phi A} = \frac{\vec{V}_{AN}}{Z_\phi} = 12 \angle -36.87^\circ \text{ A rms}$$

$$Z_\phi = 8 + j6 = 10 \angle 36.87^\circ \Omega$$

$$V_L = \sqrt{3} \cdot (120) \text{ V rms}$$

$$I_L = 12 \text{ A rms}$$

$$\theta_z = 36.87^\circ$$

$$W_1 = V_L I_L \cos(\theta_z + 30^\circ)$$
$$= (120\sqrt{3})(12) \cos(66.87^\circ)$$

$$W_1 = 979.75 \text{ Watt}$$

$$W_2 = V_L I_L \cos(\theta_z - 30^\circ)$$

$$W_2 = (120\sqrt{3})(12) \cos(6.87^\circ)$$

$$W_2 = 2476.25 \text{ Watt}$$

$$b) Z_{\phi} = 8 - j6 = 10 \angle -36.87^{\circ} \Omega$$

$$\therefore \theta_z = -36.87^{\circ}$$

$$W_1 = (120\sqrt{3})(12) \cos(-36.87^{\circ} + 30^{\circ})$$

$$W_1 = 2476.25 \text{ Watt}$$

$$W_2 = (120\sqrt{3})(12) \cos(-36.87^{\circ} - 30^{\circ})$$

$$W_2 = 979.75 \text{ Watt}$$

$$c) Z_{\phi} = 5 + j5\sqrt{3} = 10 \angle 60^{\circ}$$

$$\therefore \theta_z = 60^{\circ}$$

$$W_1 = (120\sqrt{3})(12) \cos(60 + 30)$$

$$W_1 = 0$$

$$W_2 = (120\sqrt{3})(12) \cos(60 - 30^{\circ})$$

$$W_2 = 2160 \text{ Watt}$$