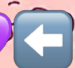











Huda AbuZayed

First Exam

بعرف انه الكل هلا ربح يبلش بيرس الفورمات على أمل انه بس ينجح بالمادة من كتر
ما سمع من الطلاب عن انها مادة صعبة ومعقدة وصعب يتجاب فيها علامات
بس قاية اذكيلكم انه صاعح المادة يمكن مش سهلة ولكن عادي يتجاب فيها علامات
انرا أعطيتها الجهد المطلوب ودرستوا صبح         وبتفهم بقيادة على اليوتيوب اسمها " Circuit-99 " انرا بتصيروا تحضروا المادة
الخطوية منكم بالامتحان منها وبعدها تروها للسيدات ربح تحسوا فالكم فاهمين
المادة وانه الامور بتسطت اكر من شرح الدكتور...
و بالتوفيق بالامتحان 

For a diode rectifier with filter, the output waveform has an average value = 20V as shown

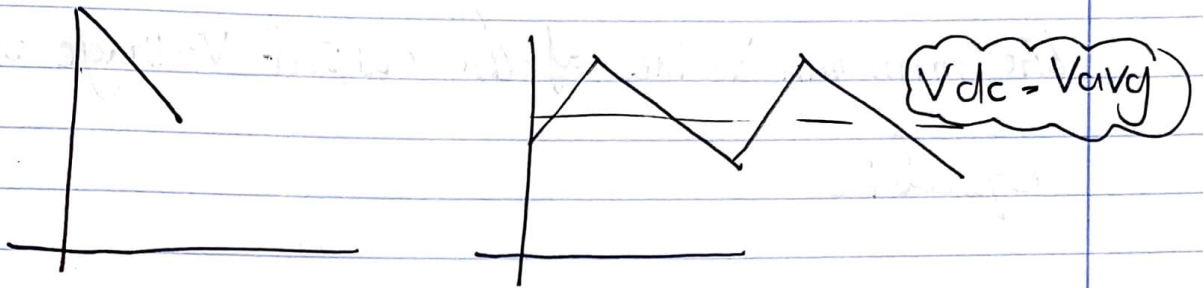& a ripple factor 5%, the minimum value of the output voltage is equal



$$V_{avg} = 20V$$

$$r = 5\%$$

$$V_{r, p-p} = V_{max} - V_{min}$$

$$r = \frac{V_{r, p-p}}{\frac{2\sqrt{3}}{V_{avg}}}$$

$$\frac{5}{100} = \frac{V_{r, p-p}}{\frac{2\sqrt{3}}{20}}$$

$$1 = \frac{V_{r, p-p}}{2\sqrt{3}}$$

$$2\sqrt{3} = V_{r, p-p}$$

$$V_{avg} = V_m - \frac{1}{2} V_{p-p}$$

$$20 = V_m - \frac{1}{2} \times 2\sqrt{3} = 20 + \sqrt{3} = V_m$$

$$V_{r, p-p} = V_m - V_{min}$$

$$2\sqrt{3} = 20 + \sqrt{3} - V_{min}$$

$$V_{min} = 18.27$$

$$V_{min} = V_m - \frac{2V_m}{\pi} \times \text{ripple factor}$$

قانون تانی

$$V_{min} = V_m - V_r$$

$$V_{avg} = V_m - \frac{V_r}{2}$$

$$V_m = 20\sqrt{2}$$

$$V_{min} = 20 - \frac{2 \times 20 \times \sqrt{2}}{\pi} \times \frac{5}{100}$$

For a diode rectifier with filter

the output wave form has an average


Value = 20V as shown & ripple = 2:1
Factor

the minimum Value of the output Voltage is
equal to

The circuit shown is to be designed so that $V_L, dc = 12V$ & $V_L, r-p-p = 2V$.

1) The required capacitor C is equal to

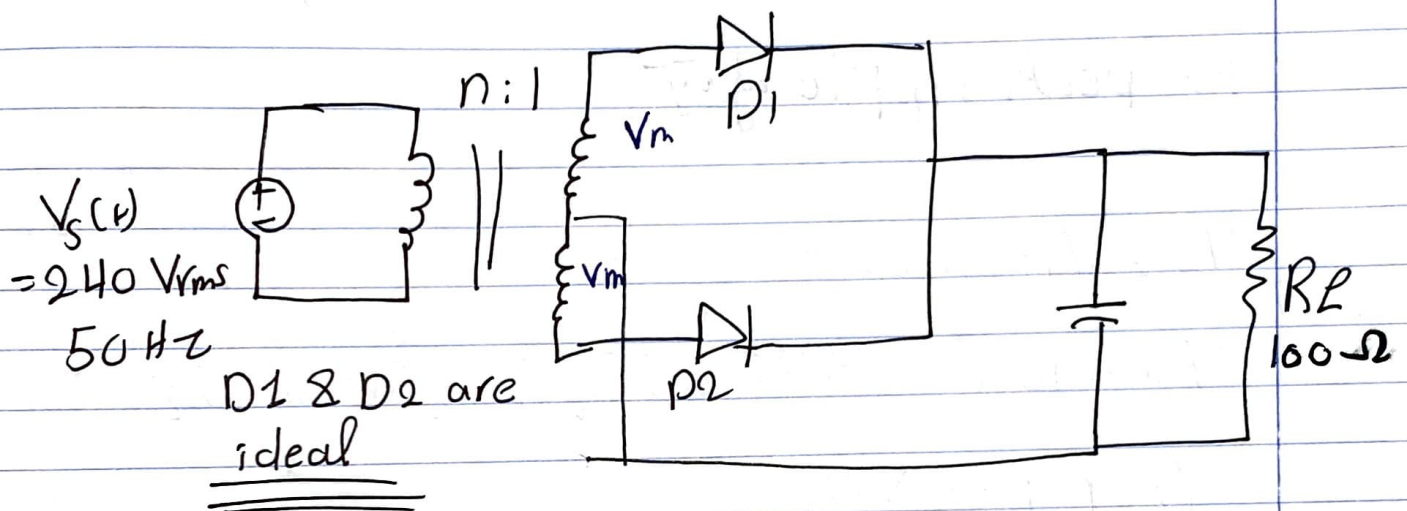2) The required turns ratio n is equal to



$$V_L, dc = 12, V_L, r-p-p = 2V$$

$$V_L, dc = V_m - \frac{1}{2} V_L, r-p-p$$

$$12 = V_m - \frac{1}{2} \times 2 \quad (V_m = 13V)$$

$$V_m = \sqrt{2} V_{m,rms}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$


$$V_L = \frac{V_m}{2f_0 R C} = \frac{13}{2 \times 50 \times 100 \times C}$$

$$C = 0.65 \mu F$$

$$V_m = \frac{N_s}{N_p} \cdot V_{mp}$$

$$13 = \frac{1}{n} \frac{240}{\sqrt{2}} \quad n = 26.1$$
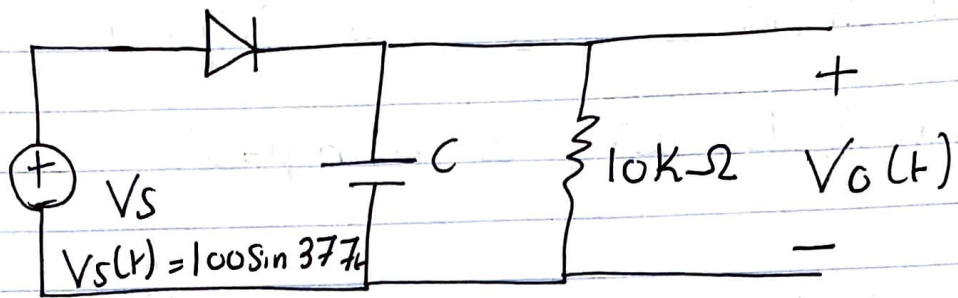
$$n = \frac{V_s(rms)}{\frac{V_m(rms)}{\sqrt{2}}} = \frac{240}{\frac{13}{\sqrt{2}}}$$



For the circuit shown, the value of the capacitor C that will result in a peak to peak ripple of $2V$

$$V_s = V_m \sin \omega t$$

$$V_m = 100 \quad 377 = 2\pi f_0 \quad f_0 = 60 \text{ Hz}$$

$$V_{R-P-P} = \frac{V_m}{f_0 RC}$$

$$2 = \frac{100}{60 \times C \times 10}$$

$$C = 83.3 \mu\text{f}$$

Full wave center-tapped rectifier has

$V_A(t) = 10 \sin \omega t \text{ V}$ & 4.7 k Load resistance

what is the dc Load current for the
Circuit V_{dc}

Assume $V_K = 0.7$

$V_A = 10 \sin \omega t \text{ V}$

$R = 4.7 \text{ k}\Omega$

for full wave
Rectifier

$I_{dc} = ?$

$V_K = 0.7 \text{ V}$


$$V_{dc} = 0.63 V_m$$

$$V_m = 10 - 0.7 = 9.3$$

$$V_{dc} \text{ Load} = 5.9148$$

$$\text{Load Current} = \frac{5.9148}{4.7 \text{ k}\Omega} = 1.258 \text{ mA}$$

Z_0

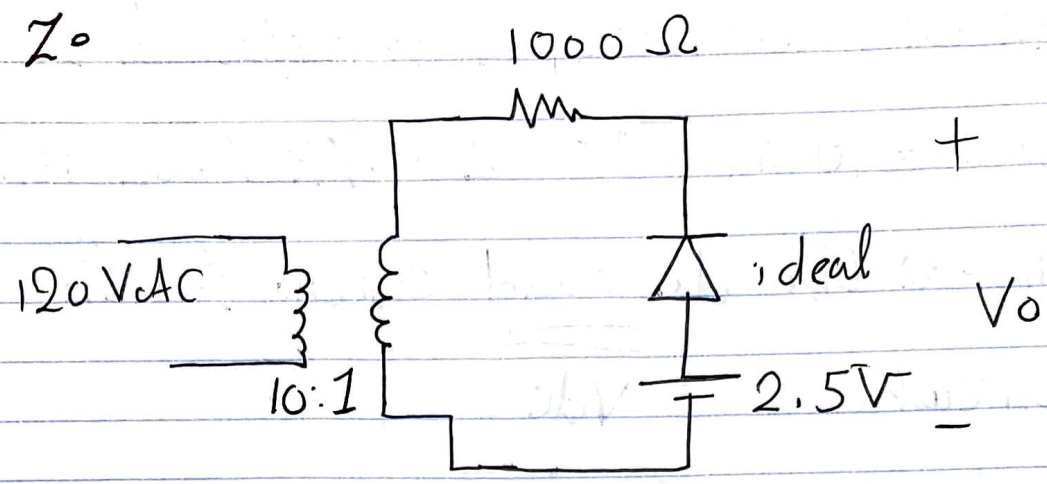



For the clipping circuit, what will be the maximum output voltage when the diode is conducting

Conducting \rightarrow The diode is o.c.v

$$\frac{V_S}{V_{in}} = \frac{10}{1}$$

$$V_S = 10 \times 120 = 1200V$$

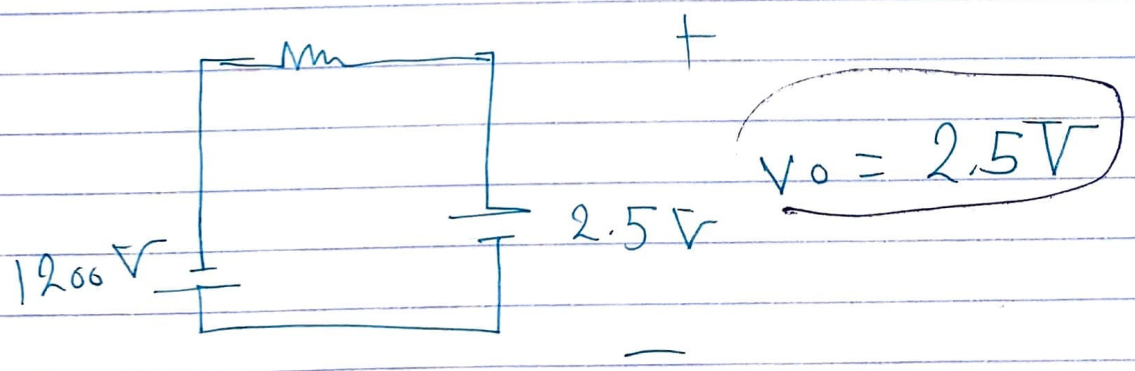


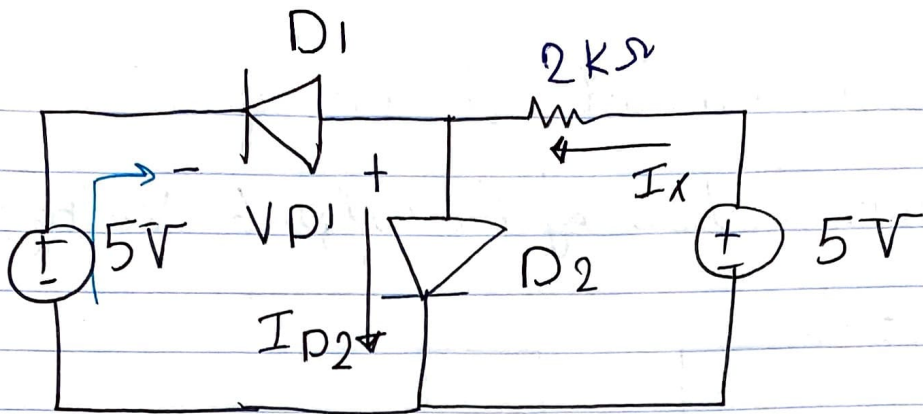

$$I_x =$$

$$V_{D1} = ?$$

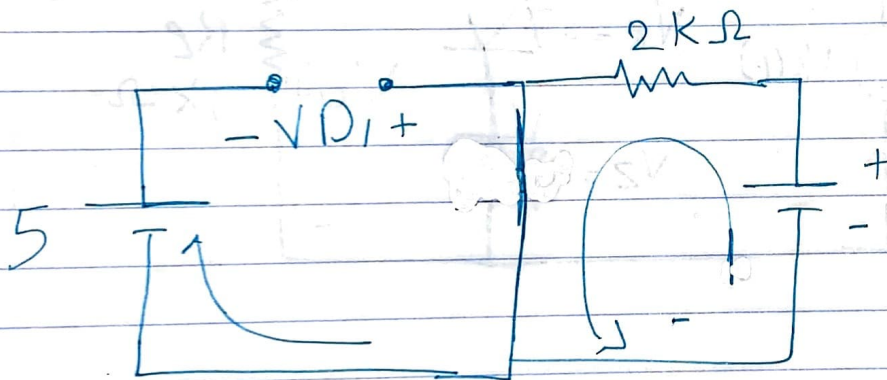\$D_1\$ is off & \$D_2\$ is on
 \$D_1\$ is o.c & \$D_2\$ is s.c





$$-5 + 2I_x = 0 \quad I_x = 2.5 \text{ mA}$$

$$-5 - V_{D1} = 0 \quad V_{D1} = -5 \text{ V}$$


وكانت تكون المقاومة = $3k\Omega$ تكون الـ $I_x = 1.66$

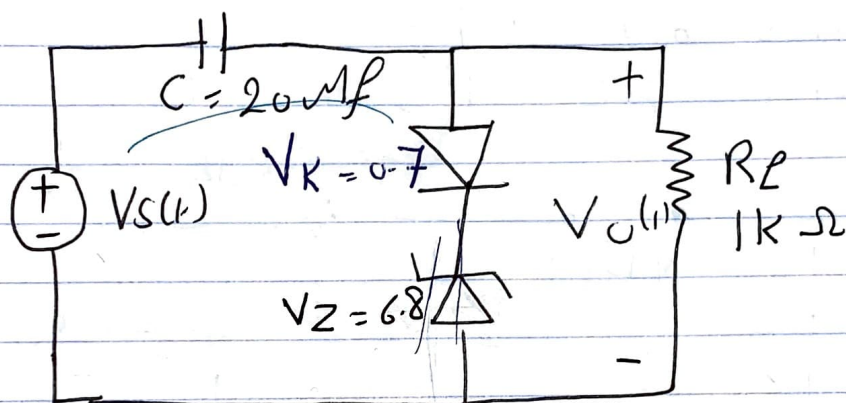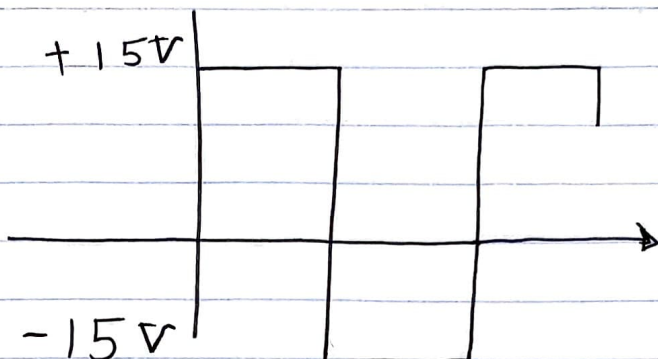For the circuit shown, what is the minimum value of the output voltage $V_o(t)$



+ve

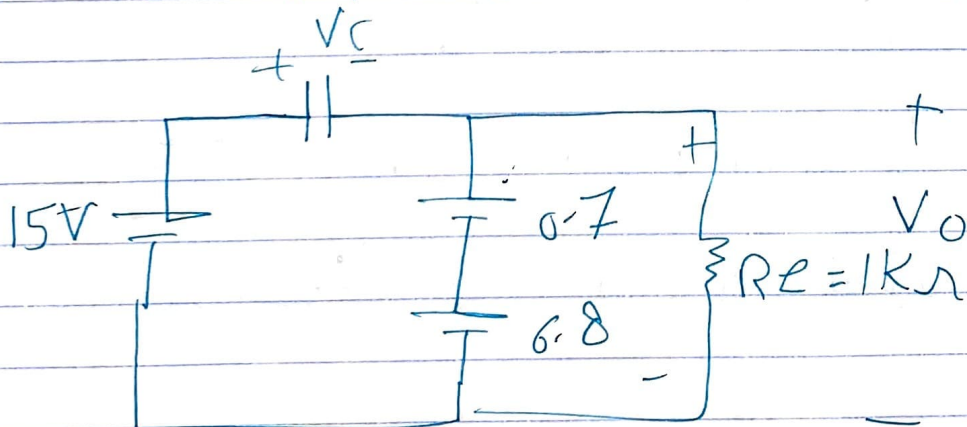
$V_s = 15V$ Diode is ON V_Z in Break down



$V_{o\max} = 7.5$

$$-15 + V_C + 7.5 = 0$$


$$V_C = 7.5V$$

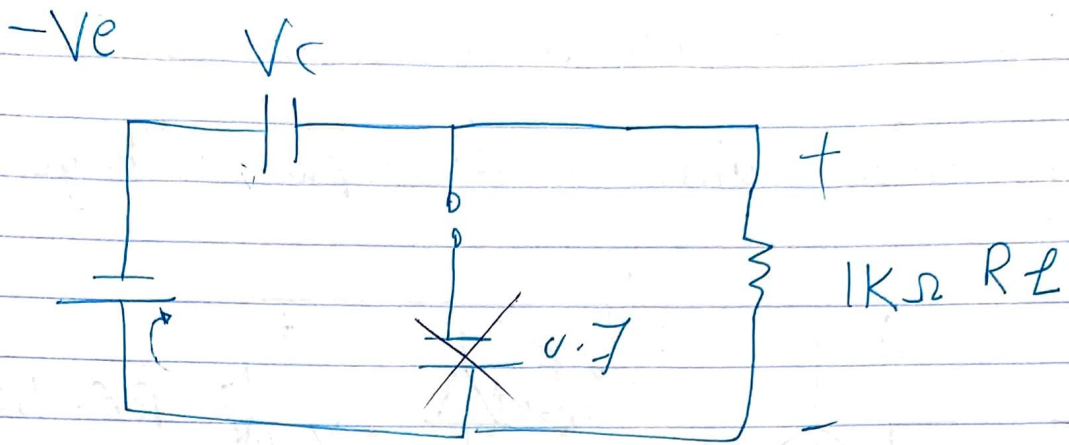

$$+15 + 7.5 + V_0 = 0$$


$$V_0 = -22.5$$

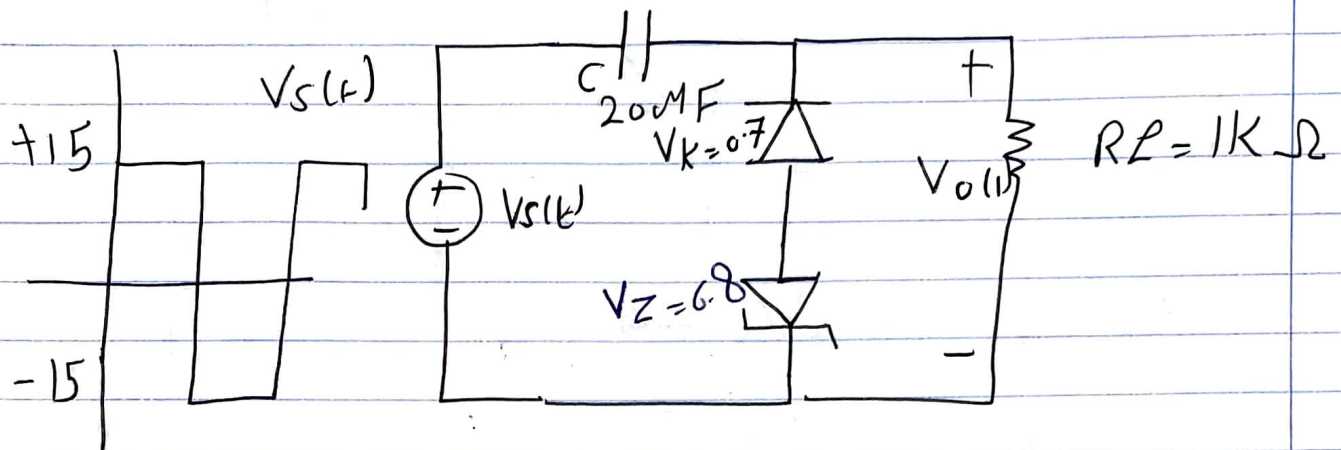For the circuit shown, what is the maximum value of the output voltage $V_o(t)$



when $V_s = 15V$

D_1 is off o.c & Zener is Diode o.w S.C

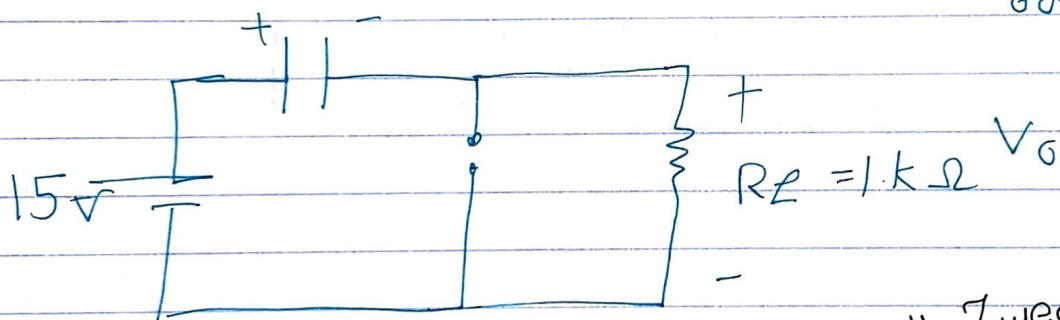


$$V_o - V_C + 15 = 0$$

$$V_o = 15 - V_C$$

Flucka AbuZayed

when $V_s = -15V$

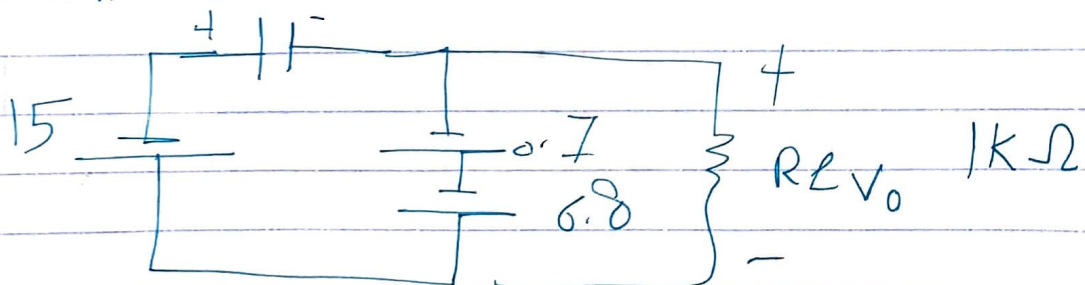

$V_{out} =$

$$-V_0 - 0.7 - 6.8 = 0$$

$$V_0 = -7.5$$

$$15 + V_C - 0.7 - 6.8 = 0$$



$$15 + V_C - 7.5 = 0$$

$$V_C + 7.5 = 0$$

$$V_C = -7.5$$

$$V_0 = 15 + 7.5 = 22.5$$

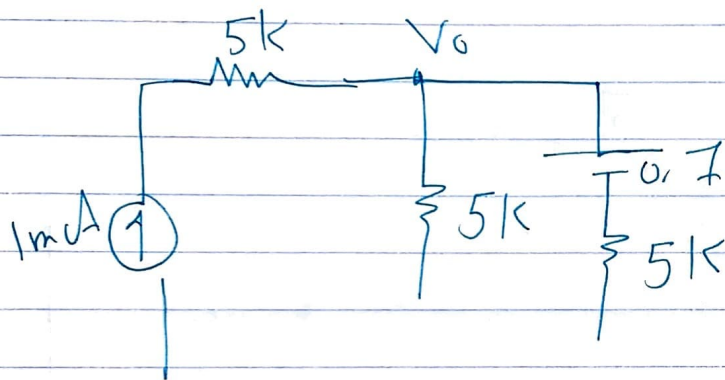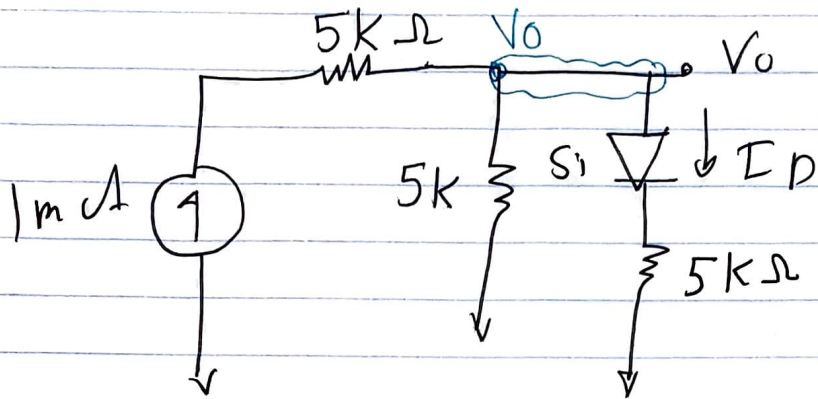
For the circuit shown, using the knee voltage model find V_0



$$\frac{V_0}{5} + \frac{V_0 - 0.7}{5} = 1$$

$$2V_0 = 5.7 \quad V_0 = 2.85V$$

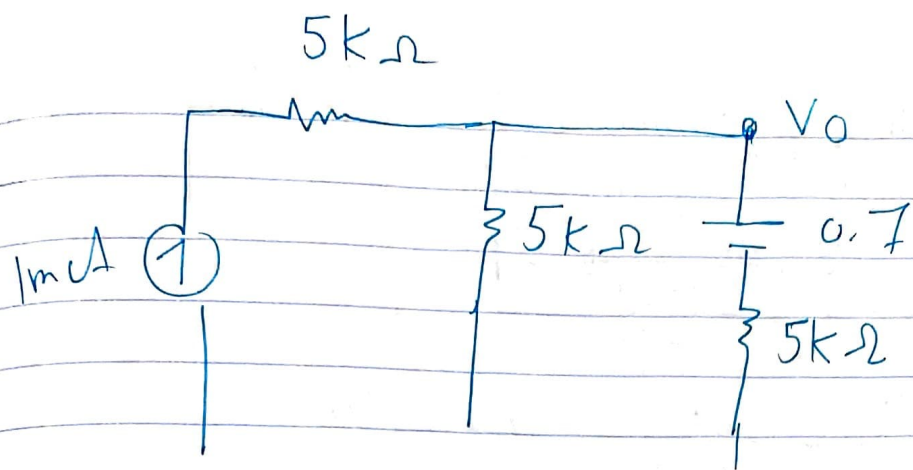
$$1 = V_0 \left(\frac{1}{5} + \frac{1}{5} \right) - \frac{0.7}{5}$$



Apply Kcl

$$-1\text{mA} + \frac{V_0}{5\text{K}} + \frac{V_0 - 0.7}{5\text{K}}$$




$$V_0 = 2.85$$

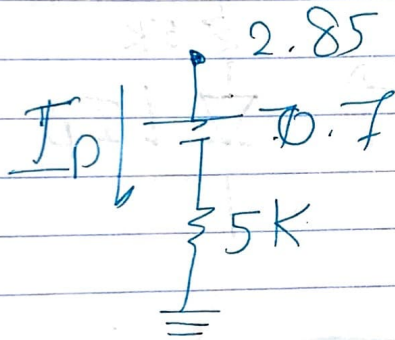

$$-2.85 + 0.7 + 5I_P = 0$$

$$I_P = 0.43\text{mA}$$

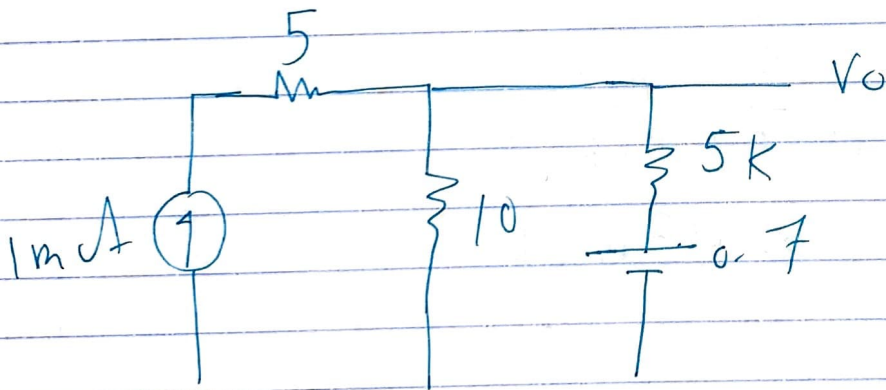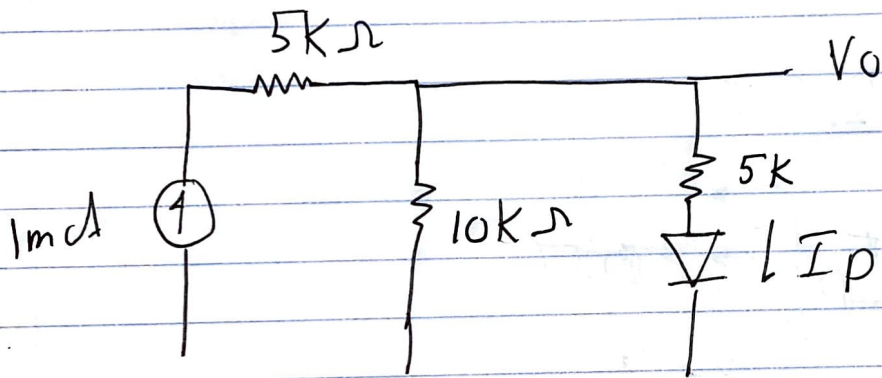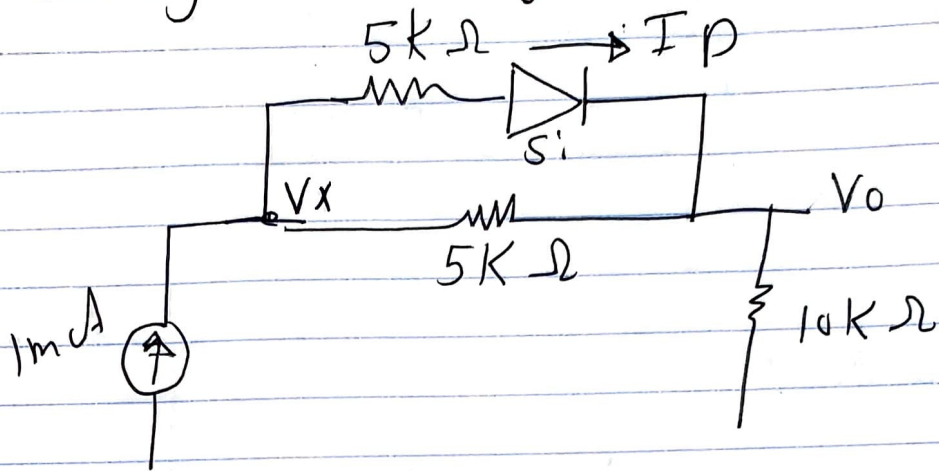For the circuit shown, using the knee voltage model find I_D




$$-1\text{mA} + \frac{V_0}{10} + \frac{V_0 - 0.7}{5\text{k}} = 0$$

$$V_0 \left[\frac{1}{5} + \frac{1}{10} \right] = \frac{0.7}{5} + 1\text{mA}$$

$$0.14 + 1 = 1.14$$

$$V_0 = 3.8$$

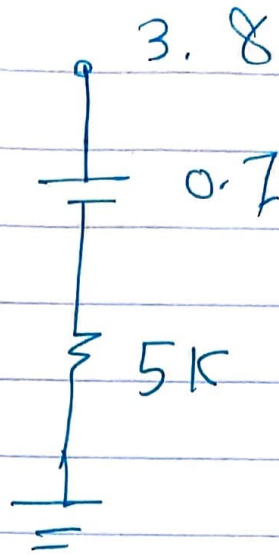


$$-3.8 + 0.7 + 5k I_k$$


$$3.1 = 5I_D$$

$$= 0.62 \text{ None of the Listed}$$

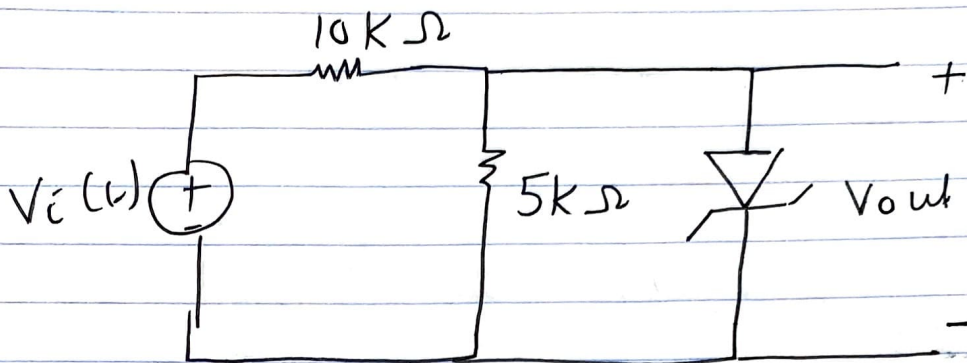
For the circuit shown, for what range will the diode be in the break down



V-I characteristic curve

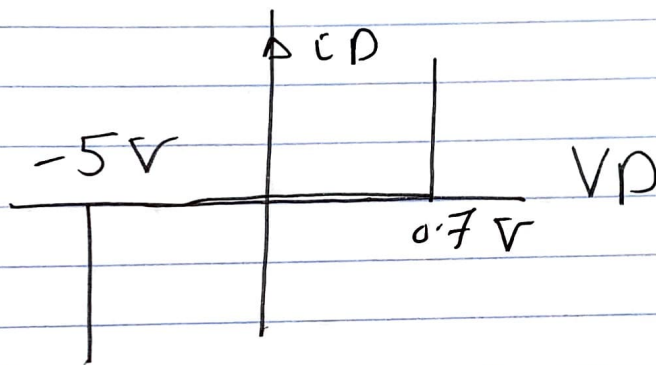

SI in the break down when $V_P < -5$

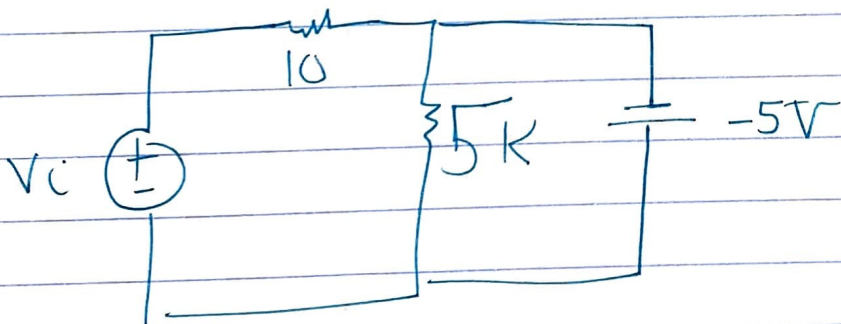


voltage divider

$$\frac{V_i \times 5}{15} < -5$$

$$V_i < -15 \text{ Less than } 15$$

S2) when Zener diode is disconnected

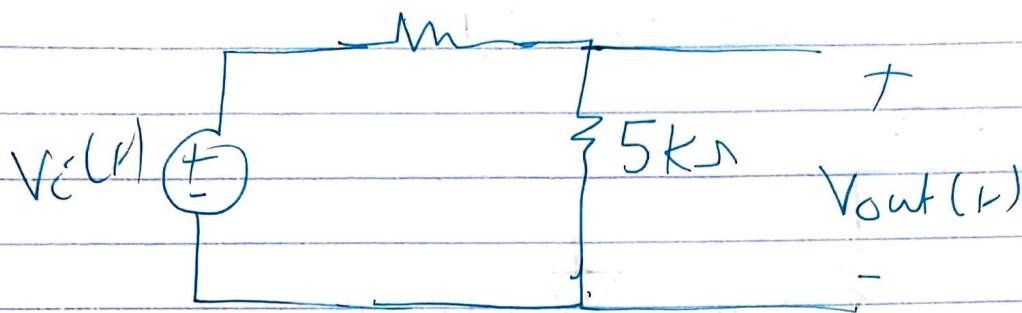


$$V = \frac{5}{15} \times V_i (V) = \frac{1}{3} V_i (V)$$

Zener is in break down $V_o (V) \leq 5V$


$$\frac{1}{3} V_i \leq -5$$

$$V_i \leq -15$$

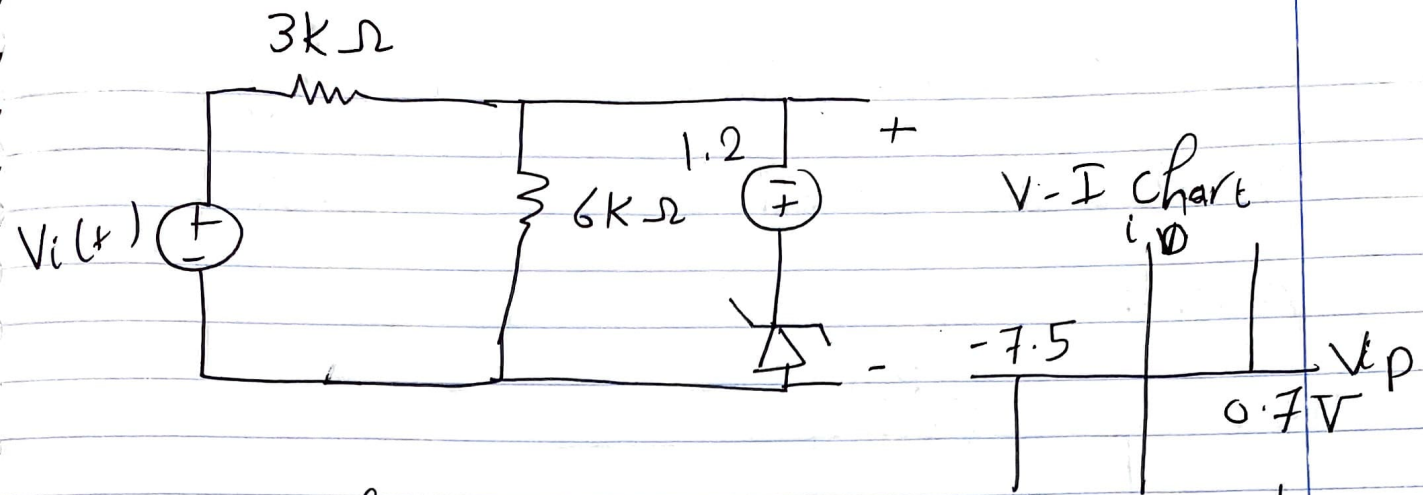


For what range of $V_i(t)$ will the diode be in the breakdown region.

when $V_D < -7.5$

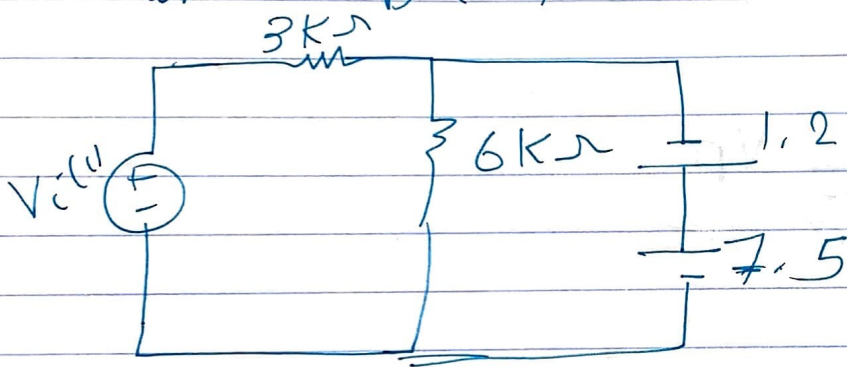



$$V_{out} = 7.5 - 1.2 = 6.3$$

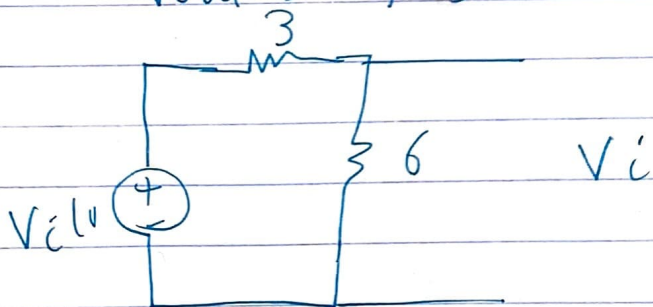


$$V_{out} = 6 \times V_i$$

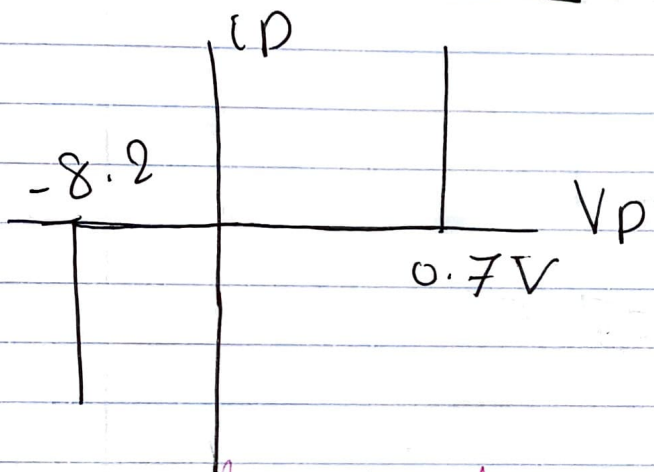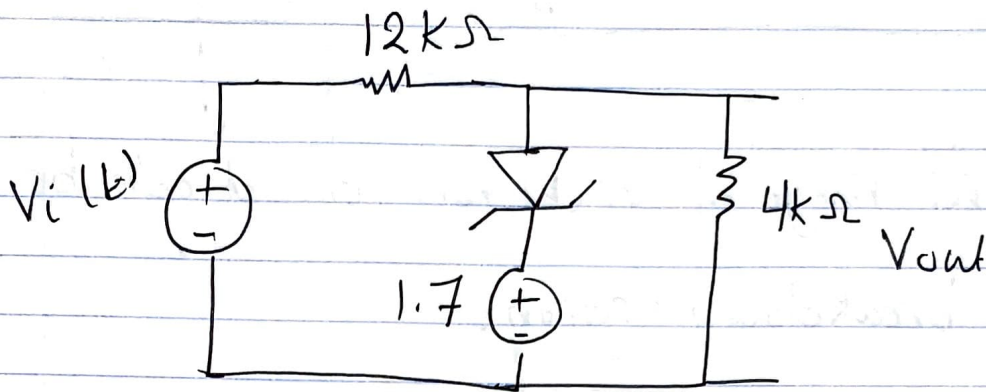9.45^9 greater than

For the circuit shown, for what range of $V_i(k)$ will the diode be in the break down region



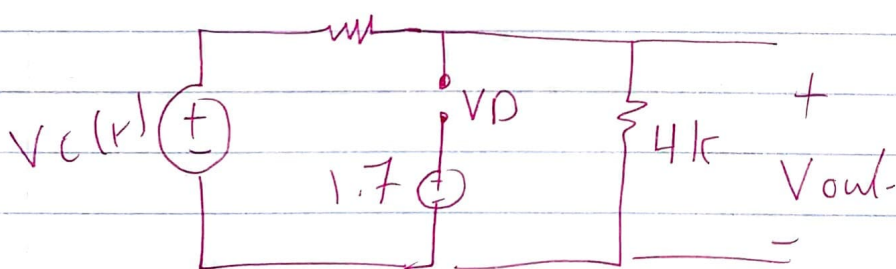Before breakdown $i_D = 0$ — open circuit



$$V_o = V_c \times \frac{4}{12+4}$$

$$V_o = \frac{V_c}{4}$$

$$V_D = \frac{V_C}{4} \quad \text{Voltage at positive terminal}$$

$$V_- = 1.7 = \text{Voltage at negative terminal}$$

Voltage across the diode


$$V_D = \frac{V_C}{4} - 1.7$$

$$V_D < -8.2$$

$$\frac{V_C}{4} - 1.7 < -8.2$$

$$< -6.5$$

$$V_C < -26$$

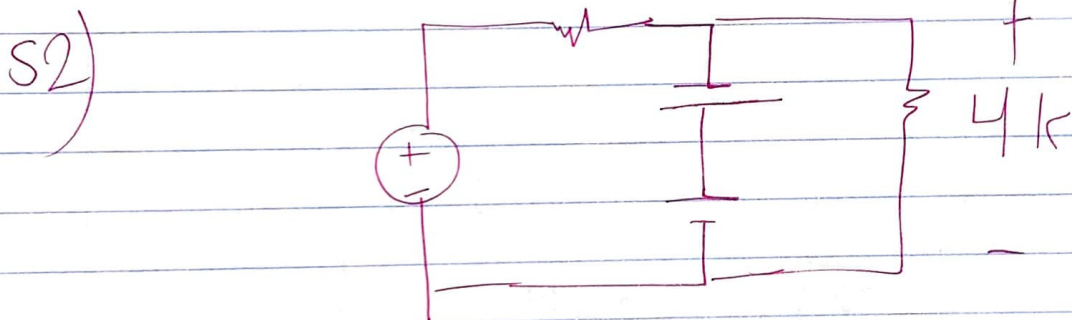


$$\rightarrow V_D - 8.2 + 1.7 = 0$$
$$V_D < 6.5$$



$$\frac{V_C \times 4}{12} < 6.5$$

$$V_C < -26 \text{ V}$$

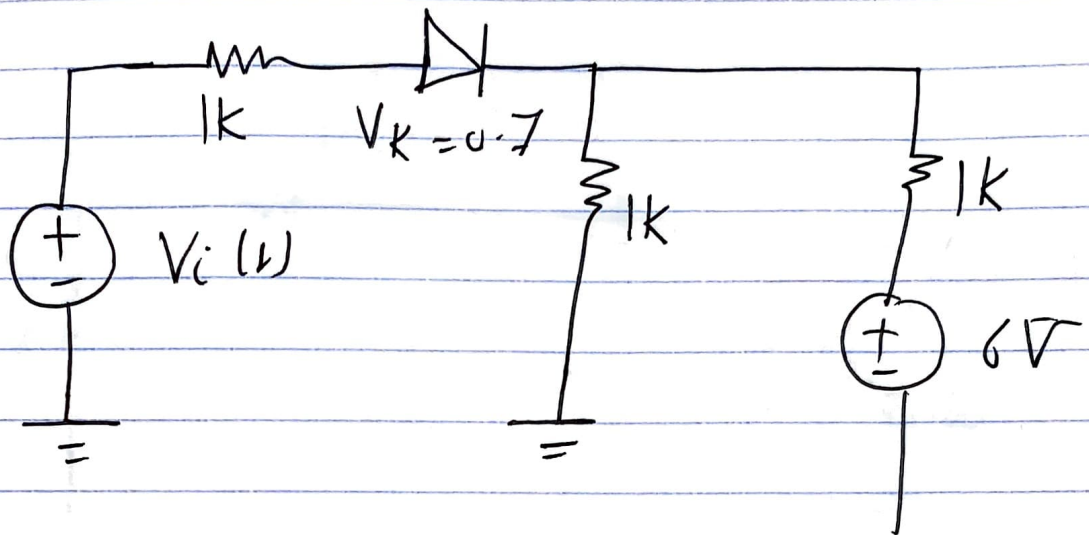For the circuit shown, for what range of $V_i(t)$ will the diode be off



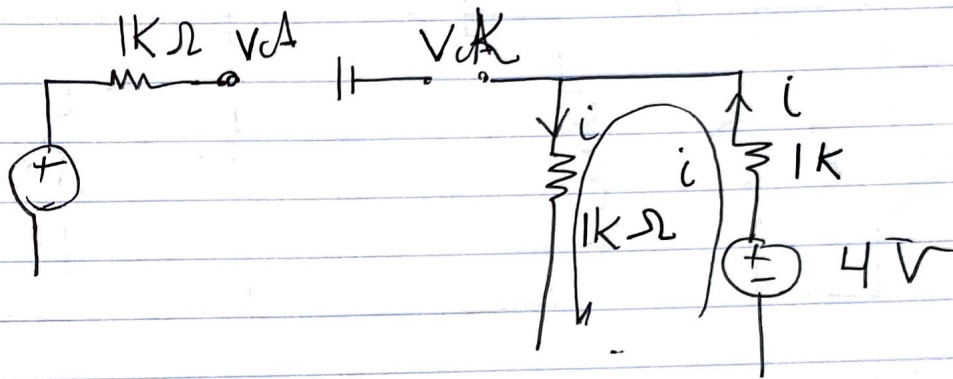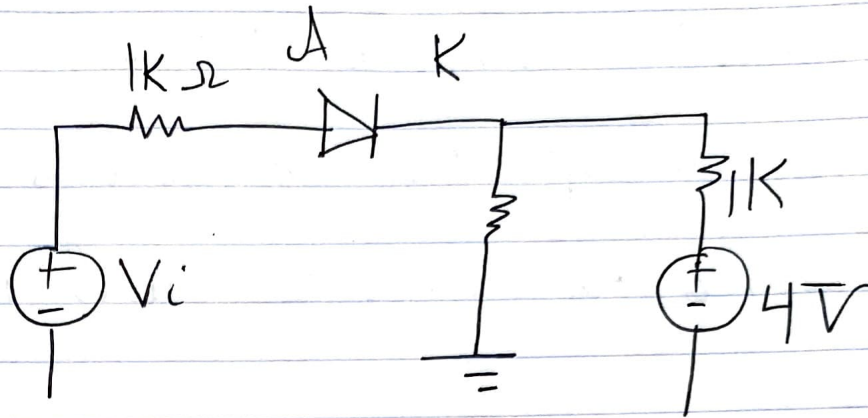For what range of $V_i(t)$ will the diode be off



$$V_A = V_i(t)$$

$$V_K = 1 \times i$$

$$= 1 \times \frac{4-0}{2} = 2V$$

To turn off the diode

$$V_A - 0.7 < V_K$$


$$V_i(t) - 0.7 < 2$$

$$V_i < 2.7$$

The circuit shown is to be designed so that

$$V_{L, dc} = 12V \quad V_{Lr, p-p} = 4V$$

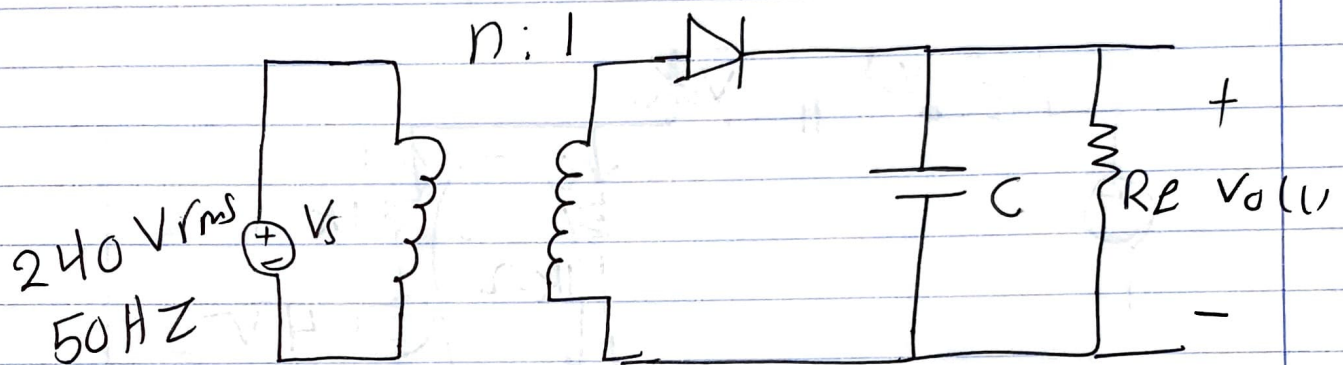- 1) The required capacitor C is equal to
- 2) The required turns ratio n is equal to



$$V_p = \sqrt{2} \times 240$$

$$V_p = 339.41$$

$$V_s = 12V$$

$$\frac{V_s}{V_p} = \frac{n_s}{n_p}$$

$$n_p = 28$$

$$a) \quad C = I \frac{\Delta V}{\Delta V} \quad t = \frac{1}{f}$$

$$f = 50 \text{ Hz}$$

$$C = 0.7$$

$$V_L, dc = 12 \text{ V}$$

30

$$V_L = V_m - \frac{1}{2} V_L r_p - \rho$$

$$V_m = 14 \text{ V}$$

$$V_L - r_p - \rho = \frac{V_m}{f_0 RC}$$

$$4 = \frac{14}{50 \times 100 \times C}$$

$$C = 7 \times 10^{-4}$$

$$V_m = \frac{cNs}{Np} \cdot V_{mp}$$

$$14 = \frac{1}{n} \times \frac{240}{\sqrt{2}}$$

$$n = 12.12$$