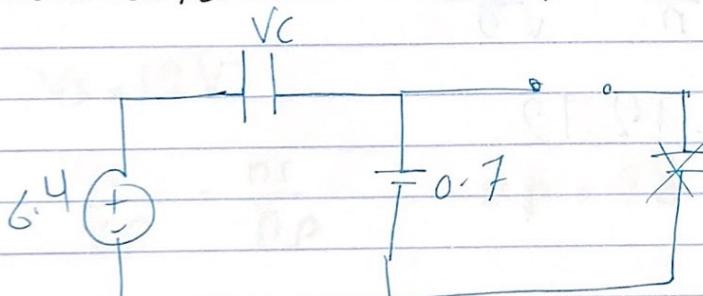



For the diode circuit shown, what will the output voltage V_o be in V if the input voltage V_i is a sine wave with an amplitude equal 6.4? Assume that when a diode is turned on the voltage across it will be 0.7V




$$-6.4 + V_C + 0.7 = 0$$

$$V_C = 5.7$$


$$+6.4 + 5.7 - 0.7 + V_o = 0$$

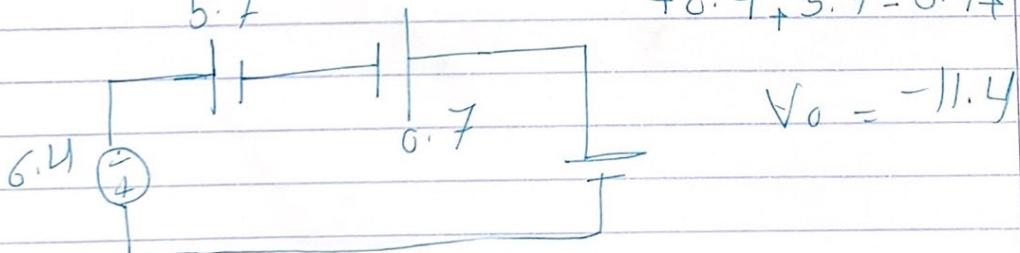


$$V_o = -11.4$$

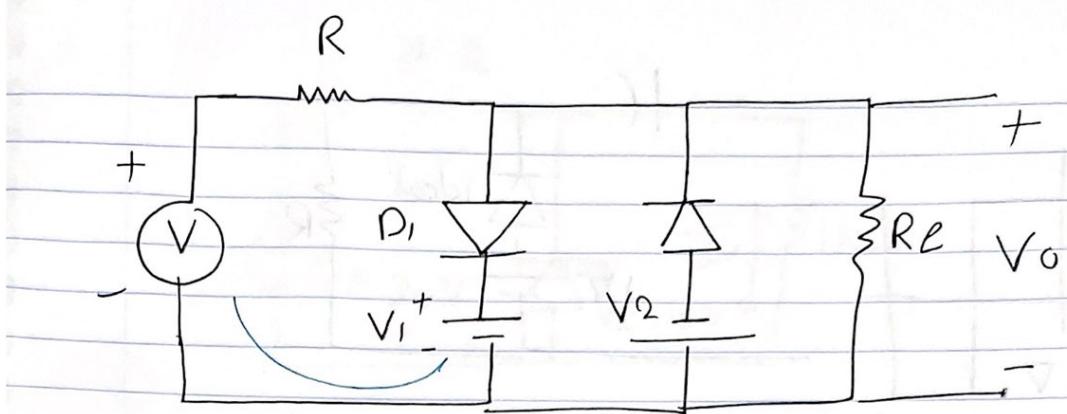

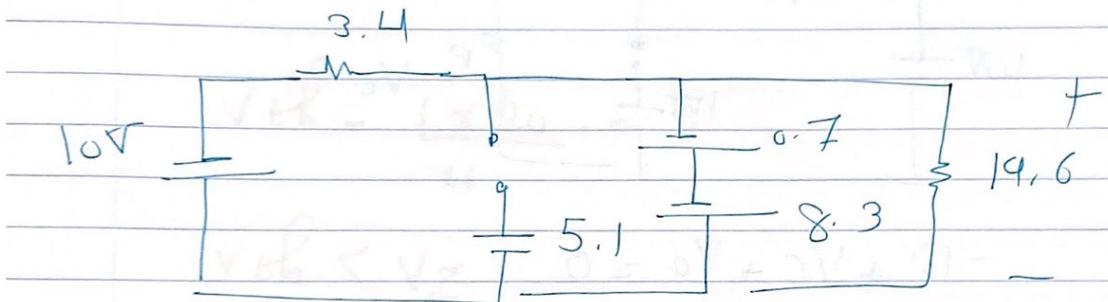
For the diode circuit shown, what will the output voltage, V_o , be in V if the input voltage V is equal to -10V ? Assume that when a diode is turned on the voltage across it will be 0.7V , & for the batteries use $V_1 = 5.1\text{V}$ & $V_2 = 8.3\text{V}$. $R = 3.4\text{k}\Omega$, $R_L = 19.6\text{k}\Omega$



$$V_o = -0.7 - 8.3 = -9\text{V}$$

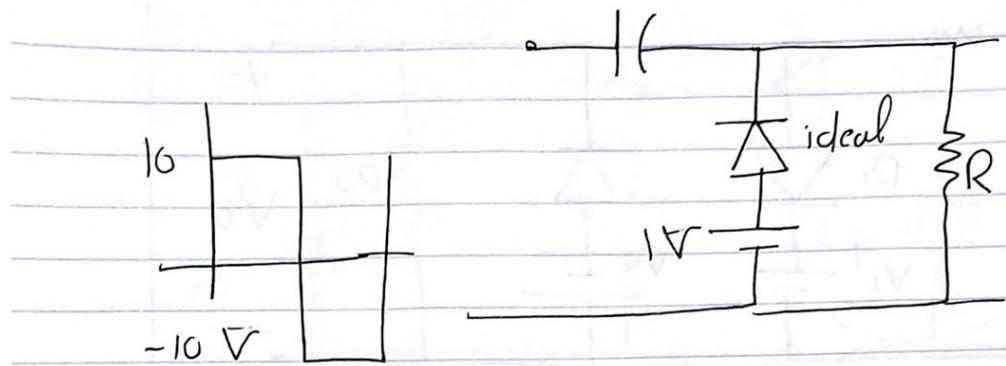

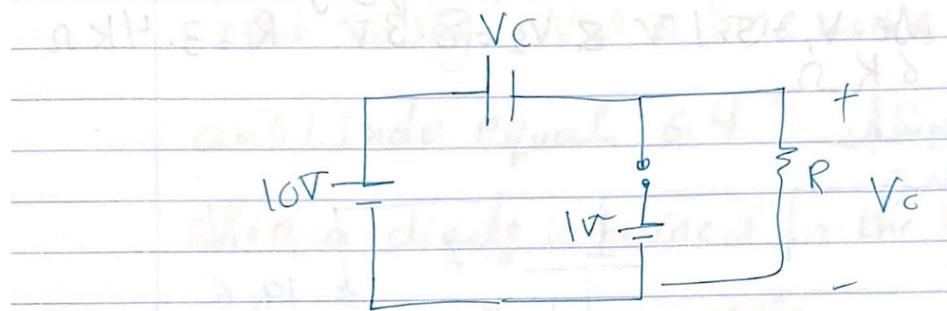
what is the maximum output voltage for
this clamping circuit




$$-10 + V_C + V_o = 0$$

-ve cycle
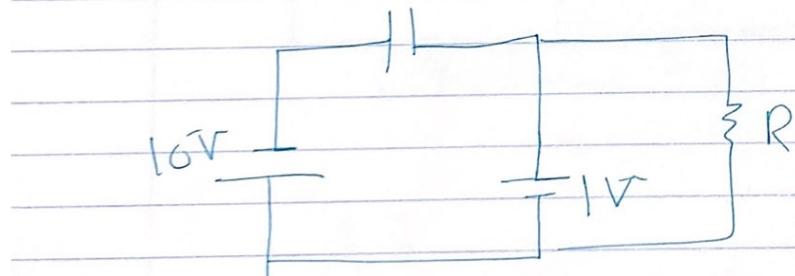
$$\Rightarrow -10 + -11 + V_o = 0 \\ V_o = 21 \text{ V}$$




$$10 + V_C + 1 = 0 \\ V_C = -11$$

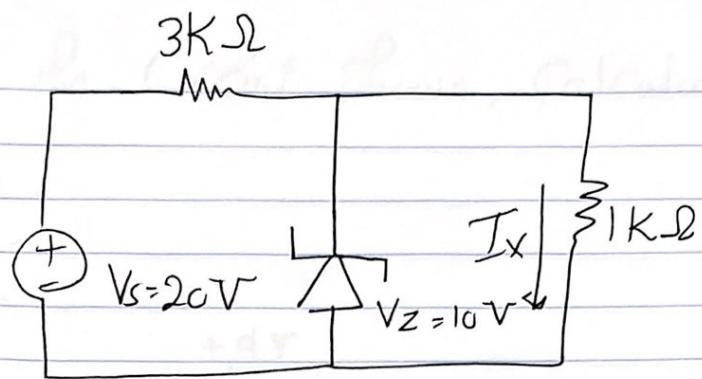

$$I_x = ??$$

فابيو سليمان
V_{th} = 5V

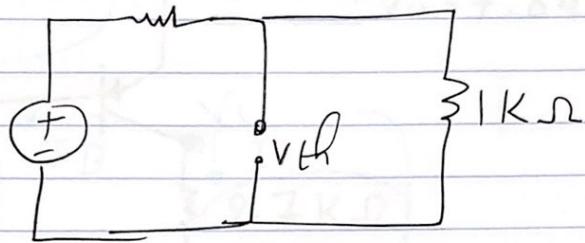

$$V_{th} = \frac{1 \times 20}{4} = 5$$

Fluxus
Abu Zayed

$$V_{th} < V_z$$

$5 < 10$ open circuit.


$$I_L = \frac{V_L}{R_L} = 5mA$$

For the Circuit Shown, Calculate the following

$$I_B =$$

$$I_C =$$

$$V_C =$$

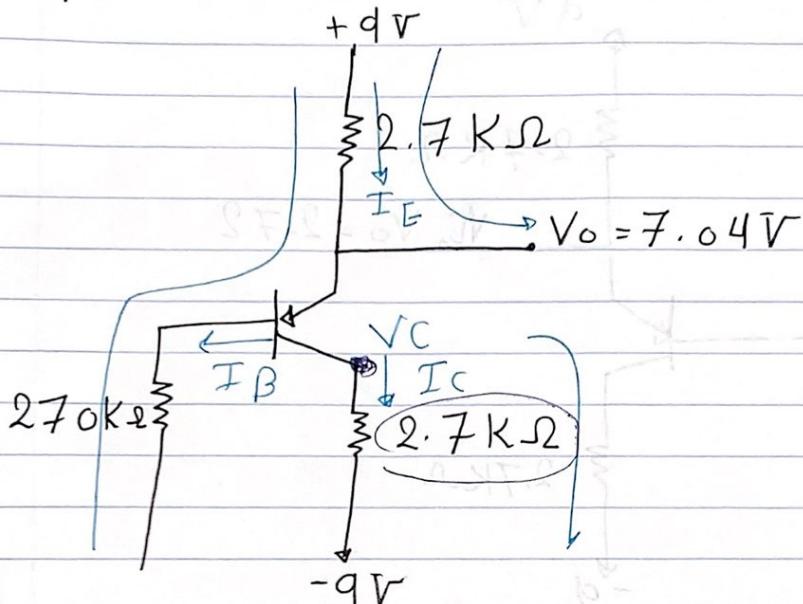

$$-9 + 2.7 I_E + 7.04 = 0$$

$$I_E = \frac{1.92}{2.7} = 0.725$$

$$-9 + 2.7 I_E + V_{EB} + 270 I_B = 0$$

$$I_B = 0.023$$

$$\text{or } I_E = (\beta + 1) I_B \quad \beta = 31.52 \\ \beta = 30.52$$


$$I_C = \beta I_B = 0.702$$

$$-V_C + 2.7 I_C + 9 = 0 \quad V_C = -7.104$$

$$I_B =$$

$$I_C =$$

$$V_C =$$

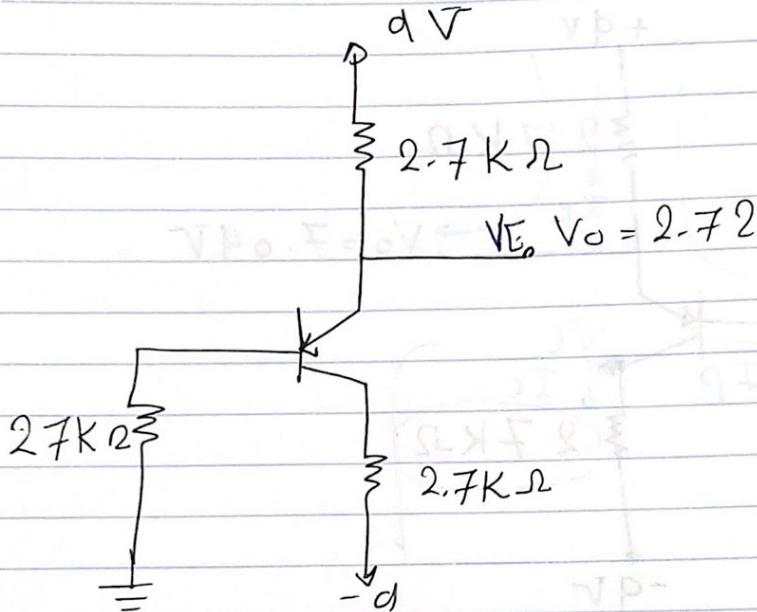

$$V_E = V_O = 2.72 \text{ V}$$

$$V_{EB} = 0.7$$

$$V_E - V_B = 0.7$$

$$V_O - 0.7 = V_B$$

$$V_B = 2.72 - 0.7$$


$$V_B = I_B R_B$$

$$I_B = \frac{2.02}{27} = 0.07481$$


$$q - 2.7 I_E = 2.72$$

$$I_E = 2.325$$

$$V_C = -2.72 \text{ V}$$

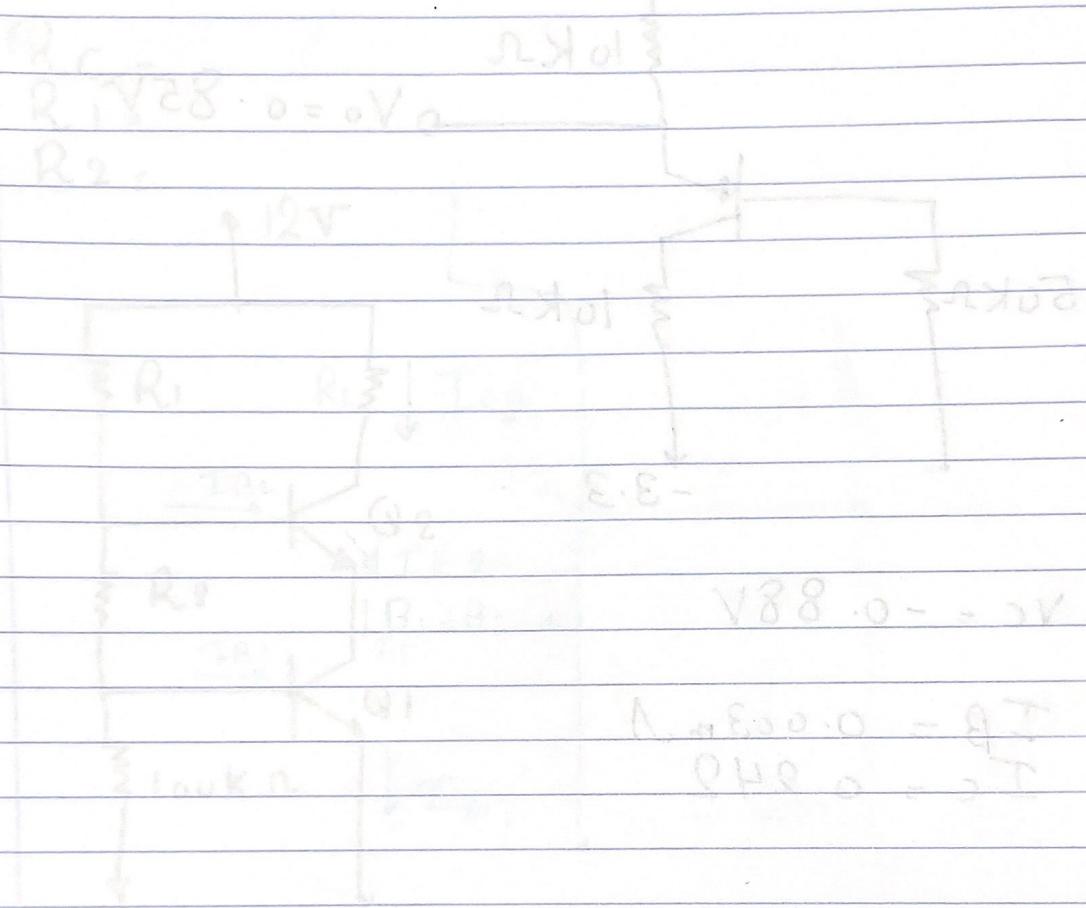

3.3

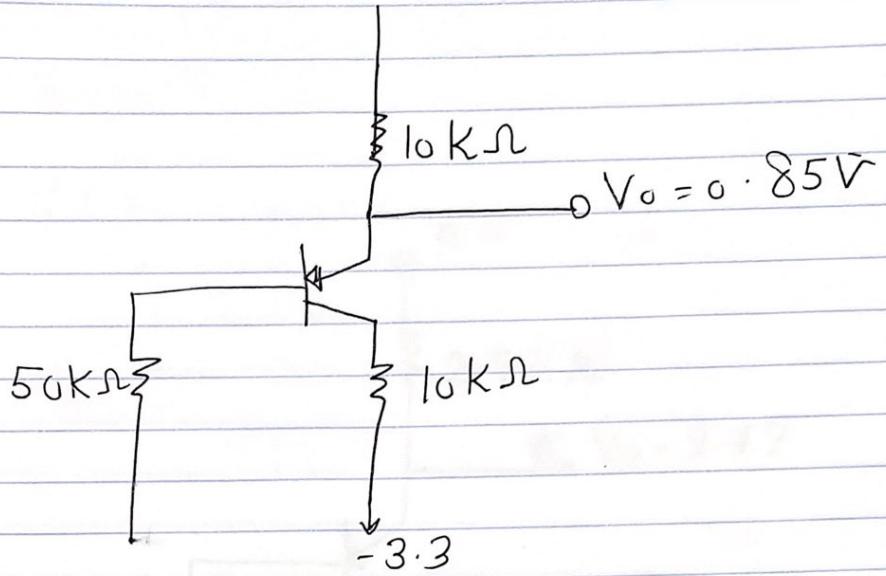

$$V_C = -0.88V$$

$$I_B = 0.003\text{ mA}$$


$$I_C = 0.242$$

For the circuit shown $I_{C2} = 1 \text{ mA}$ $V_{CE1} = 3 \text{ V}$
 $V_{CE2} = 6 \text{ V}$

$$R_C =$$

$$R_1 =$$

$$R_2 =$$

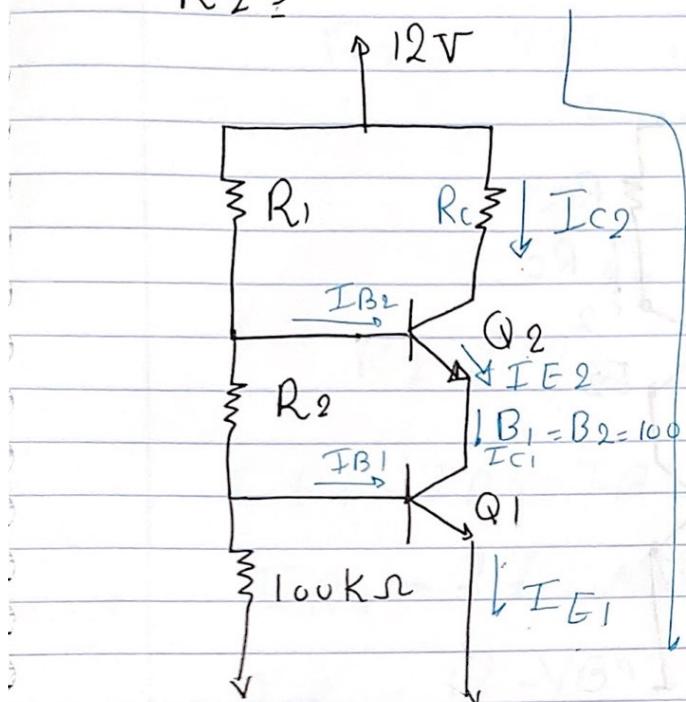

$$-12 + I_{C2} R_C + V_{CE2} + V_{CE1}$$

$$-12 + 1 R_C + 6 + 3 = 0$$

$$(R_C = 3 \text{ k}\Omega)$$

$$I_{B1} = \frac{I_{C1}}{\beta} = \frac{10}{100} = 0.1 \text{ mA}$$

$$(I_{C1} = I_{E2})$$

$$I_{B2} = \frac{I_{C2}}{\beta} = \frac{1 \text{ mA}}{100} = 0.01 \text{ mA}$$

$$I_{E2} = I_{B2} + I_{C2} = 0.01 + 1 = 1.01 \text{ mA}$$