

# Diode-Large-Signal- Applications Diode

Clipping at two independent levels

Clamping Circuits

Voltage Multipliers

# Clipping at two independent levels

$D_1, D_2$  are ideal

1) Assume  $D_1$  on, and  $D_2$  off

$$V_o(t) = 5 V$$



$$i_{D1}(t) = \frac{V_i(t) - 5}{10k} > 0$$

$$\therefore V_i(t) - 5 > 0$$

$$\therefore V_i(t) > 5 V$$

$$V_{D2}(t) = -5 - 5 = -10 V$$

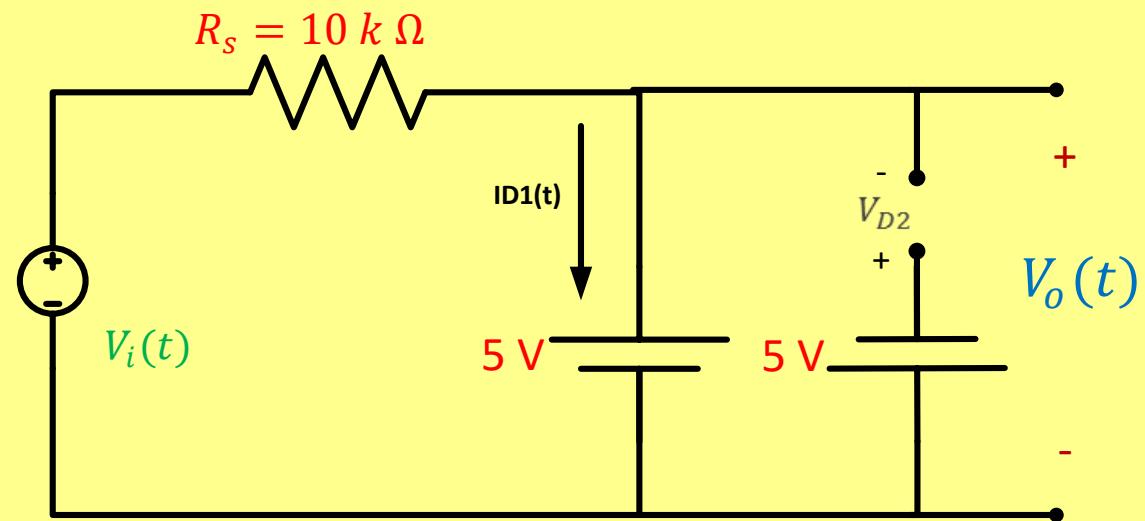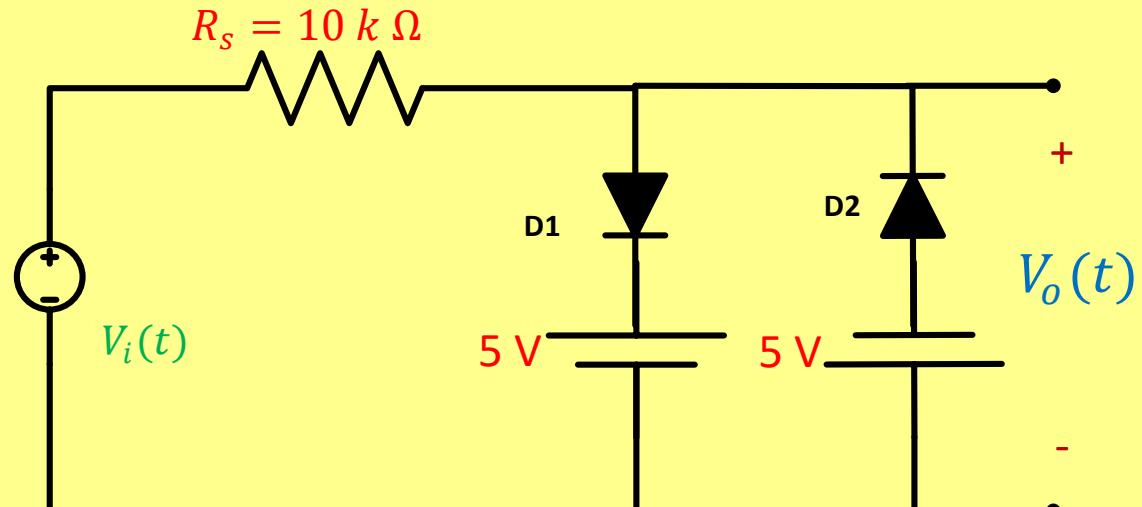$\therefore$  When  $V_i(t) > 5 V$ ,  $V_o(t) = 5 V$



► 2) Assume  $D_2$  on, and  $D_1$  off


$$V_o(t) = -5 \text{ v}$$

$$i_{D2}(t) = \frac{-V_i(t) - 5}{10k} > 0$$

$$-V_i(t) - 5 > 0$$

$$\therefore V_i(t) < -5 \text{ V}$$

$$V_{D1}(t) = -5 - 5 = -10 \text{ V}$$

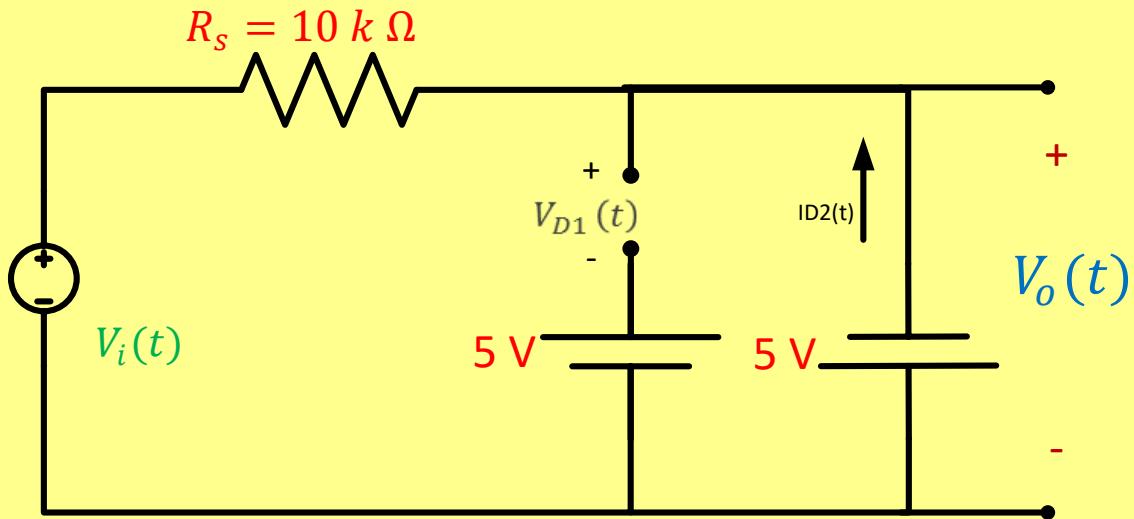


$\therefore$  When  $V_i < -5v$ ,  $V_o(t) = -5V$

- 3) Assume that  $D_1$  and  $D_2$  are on

$$V_o = -5 \text{ v}$$

also  $V_o = +5\text{v} ??$

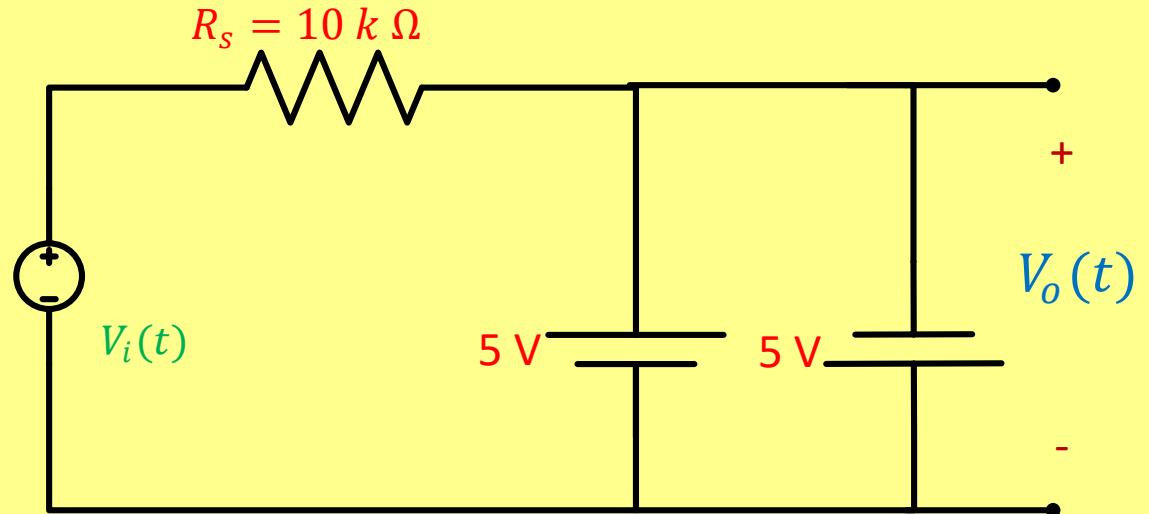


This case is **not valid**

**Impossible**


- 4) Assume that  $D_1$  , and  $D_2$  are off

- When  $+5 > V_i(t) > -5$

$$V_o(t) = V_i(t)$$

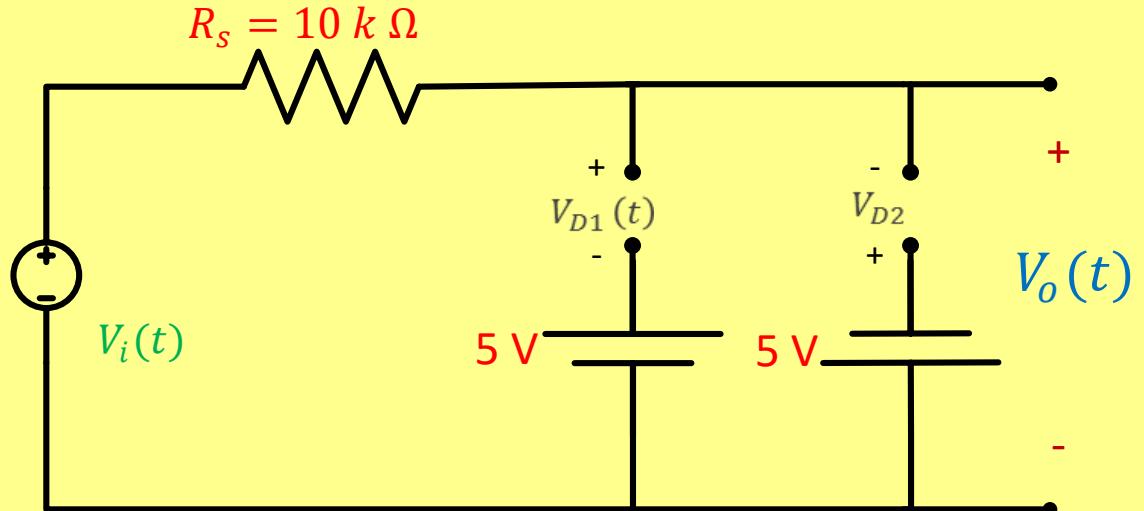


# Clipping at two independent levels


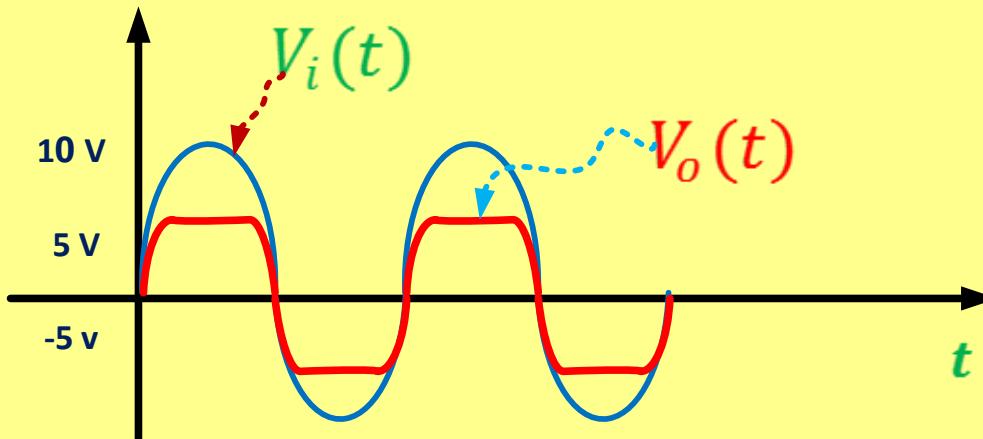


Limiter

For protection

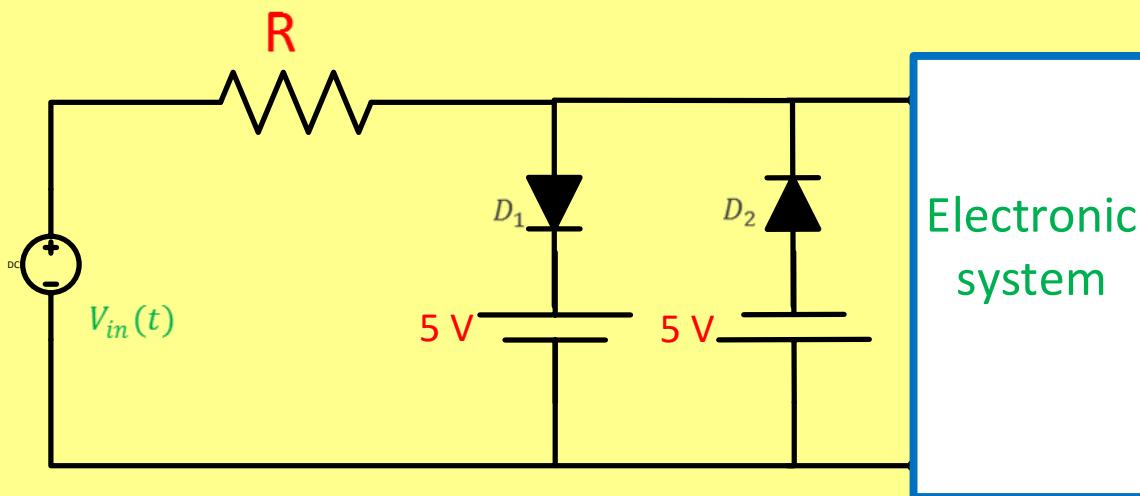

## 2) Clamping circuit

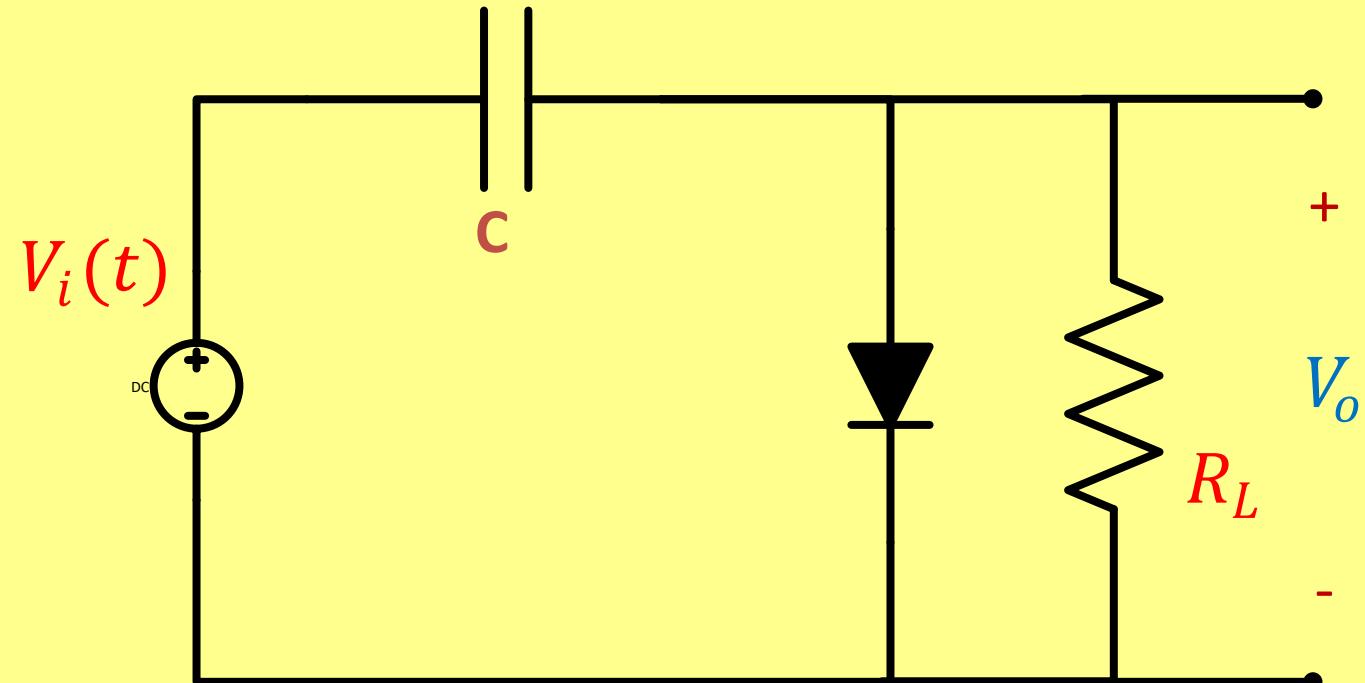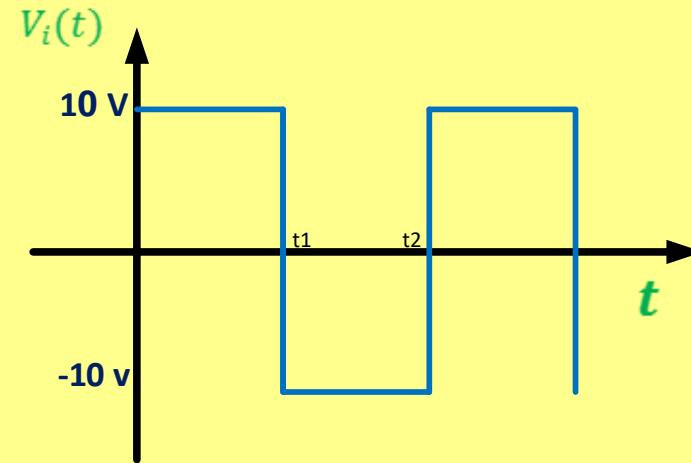


Diode is ideal ,  $V_c(0^-) = 0$

1) at  $t= 0^+$

$$V_i(0^+) = 10V ; V_c(0^+) = V_c(0^-) = 0$$


$$\therefore V_D(0^+) = 10V ,$$

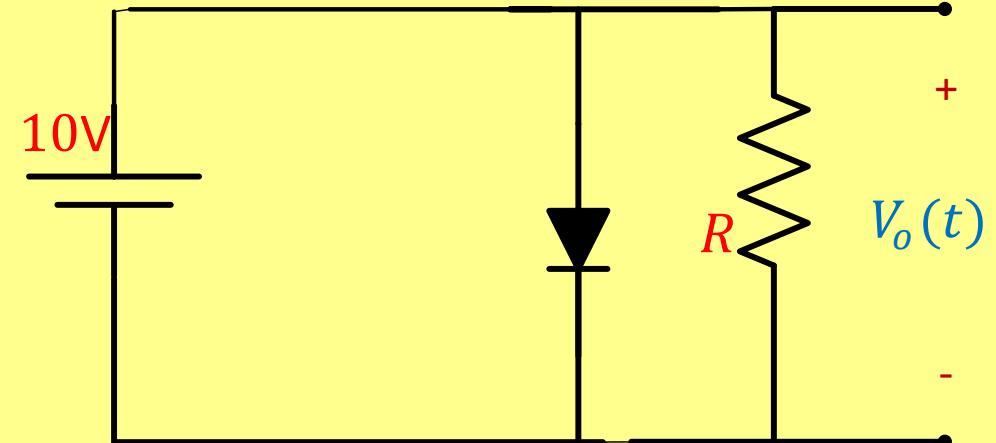$\therefore$  Diode is on and then replaced with short circuit




In the interval  $t_1 > t > 0^+$

- $V_i = 10 V$ , Diode is on (short)

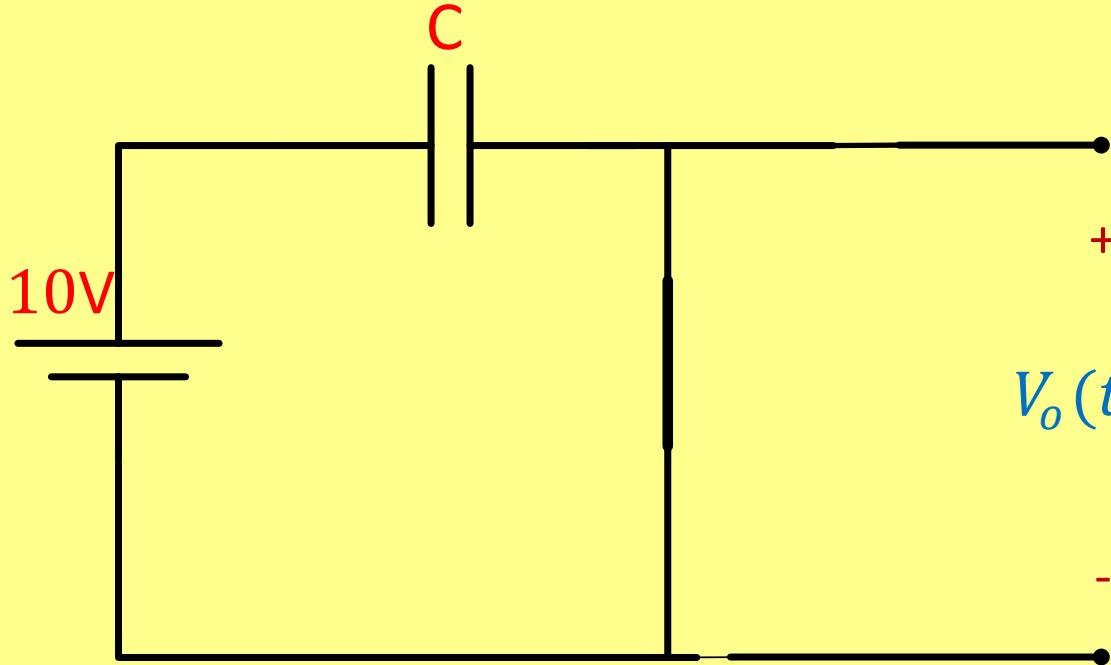

$$V_o(t) = 0$$

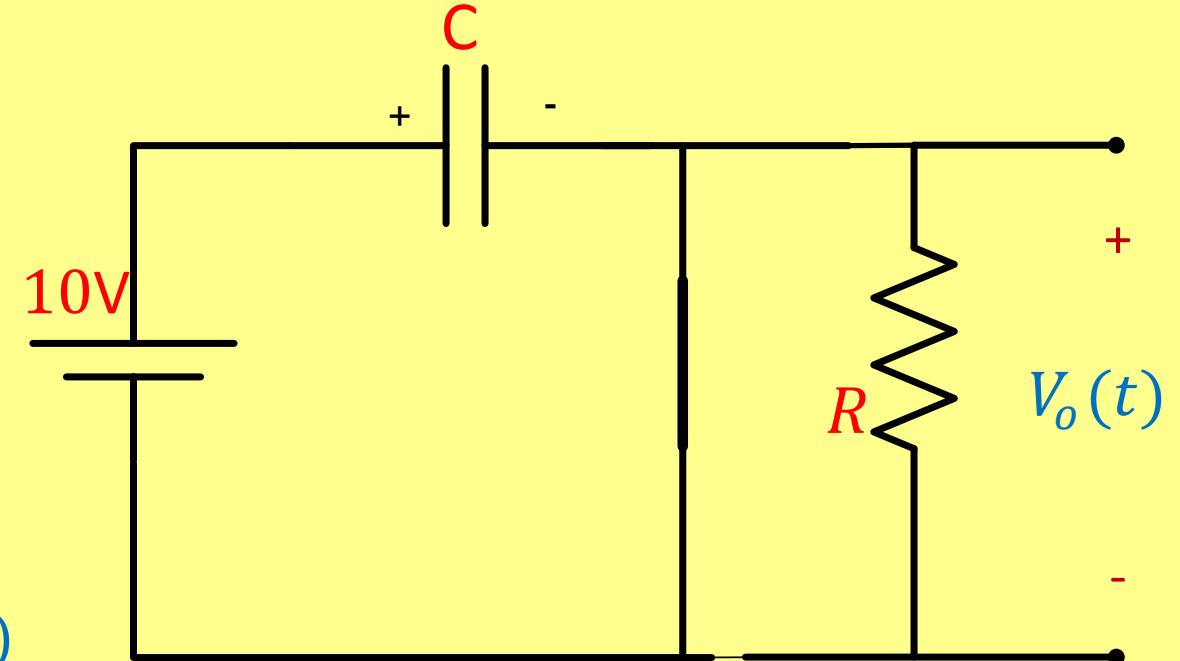

and the capacitor charges toward  $+10V$  in  $5\tau = 5R_{eq}C = 0$

In the interval  $t_2 > t > t_1$

$$V_i = -10 \text{ V}$$



The diode is off and replaced  
with open circuit

►  $\therefore V_0(t) = -V_c(t) - 10$



►  $V_0(t) = -10 - 10$

$$V_0(t) = -20 \text{ V}$$


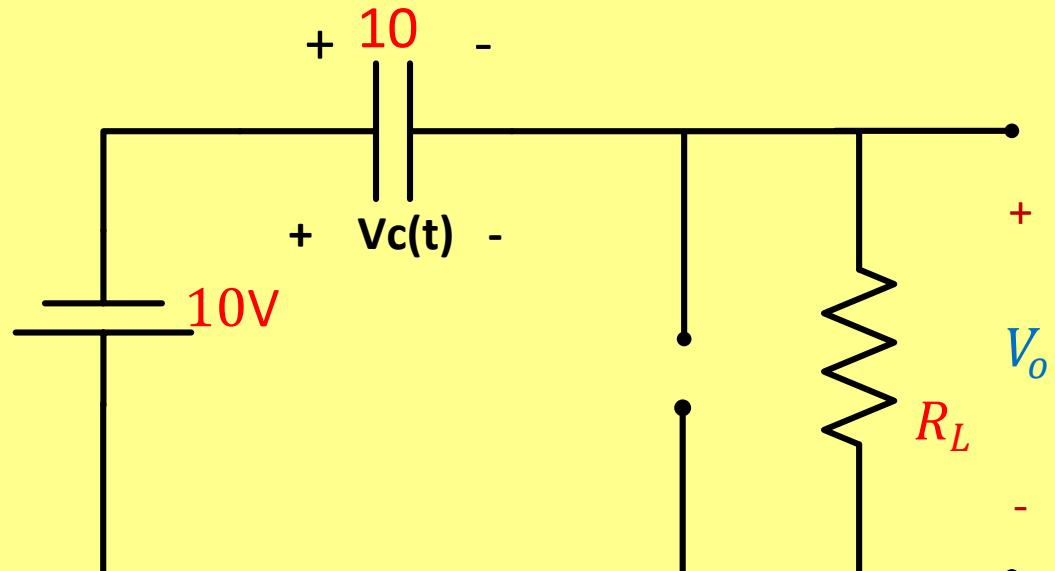
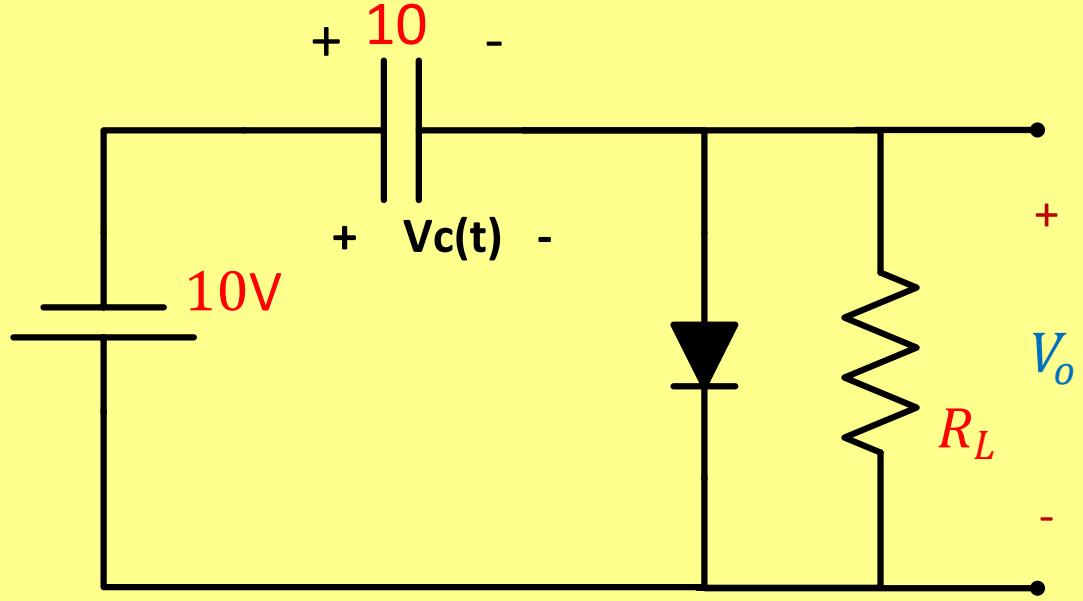
We must choose  $RC \gg (t_2 - t_1)$   
so that  $V_c(t) \equiv 10 \text{ V}$  in this interval



# The output

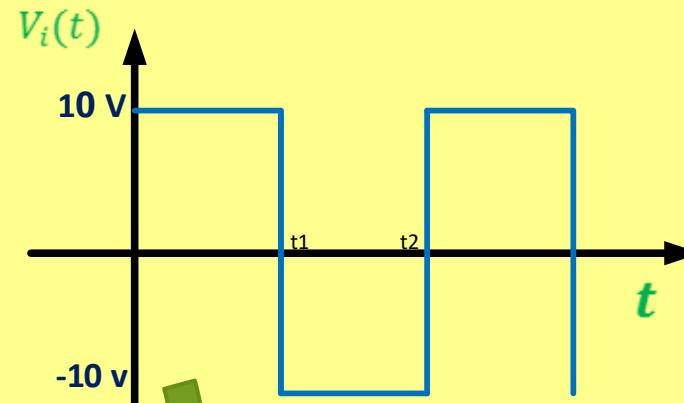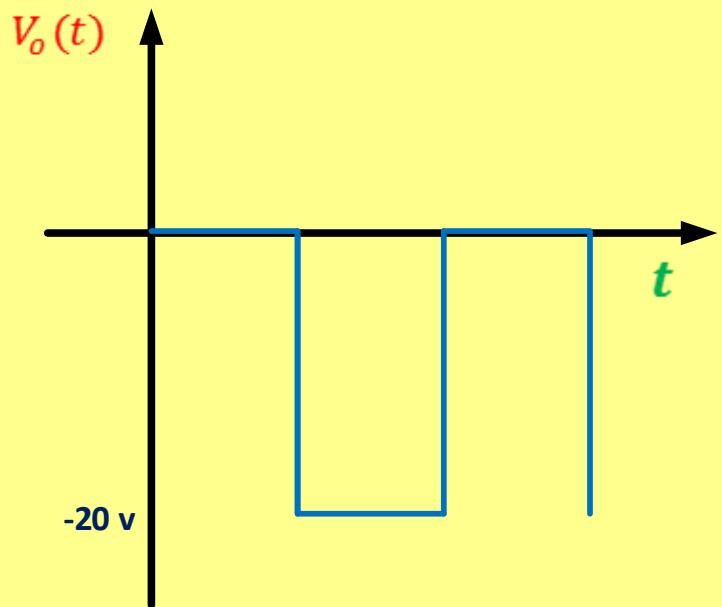

# Biased clamping circuit

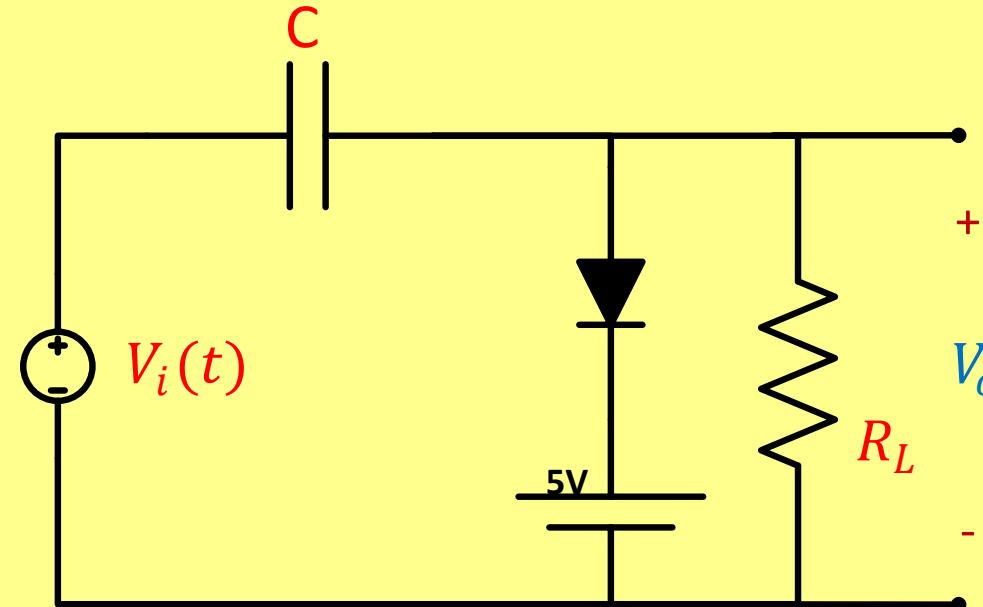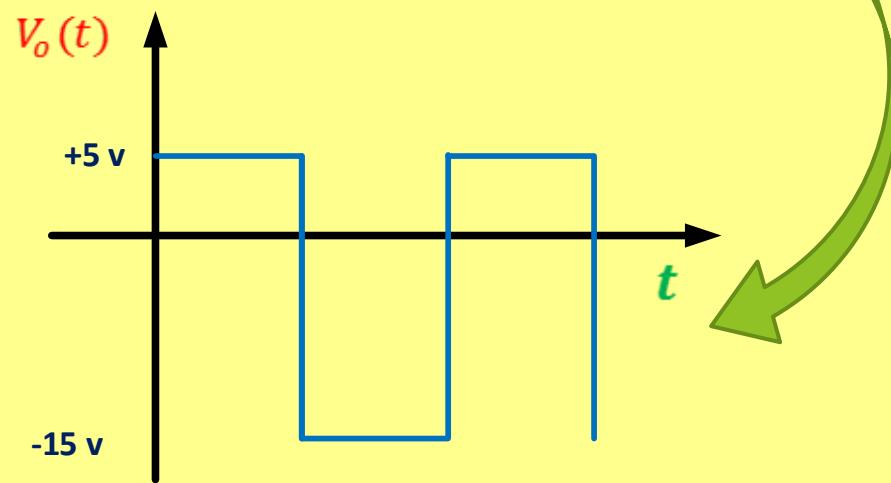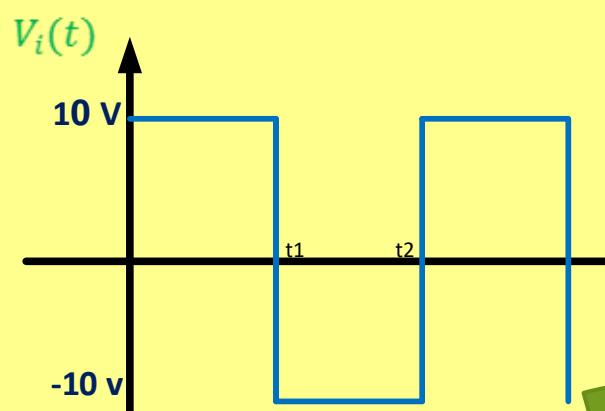

### 3) Voltage Multiplier

$D_1$ , and  $D_2$  are ideal




$$V_{c1}(0^-) = V_{c2}(0^-) = 0$$


A) at  $t = 0^+$

$$V_i(0^+) > 0 \quad V_{c1}(0^+) = V_{c2}(0^+) = 0$$

$$V_{D1}(0^+) > 0V \quad \therefore D_1 \text{ on}$$
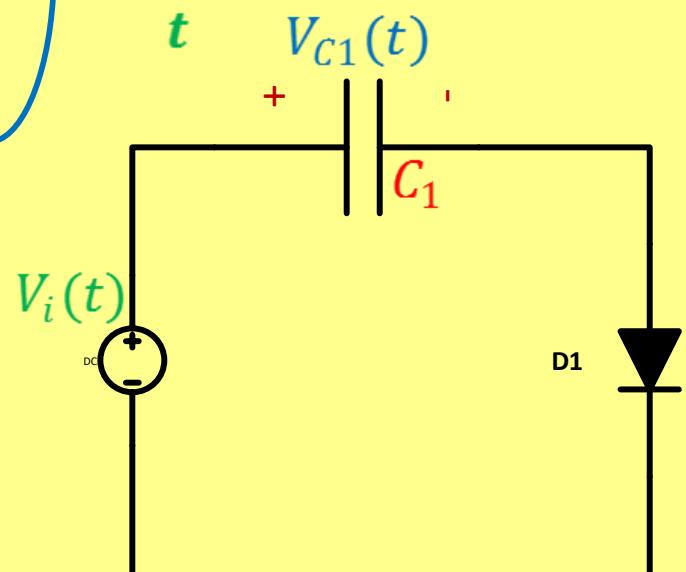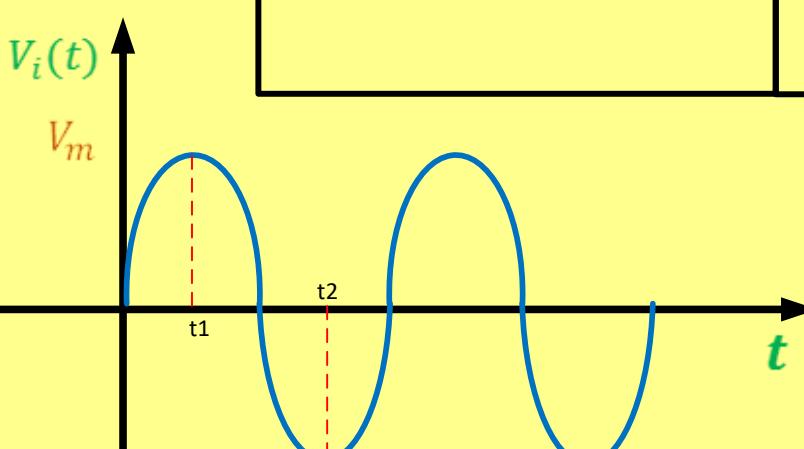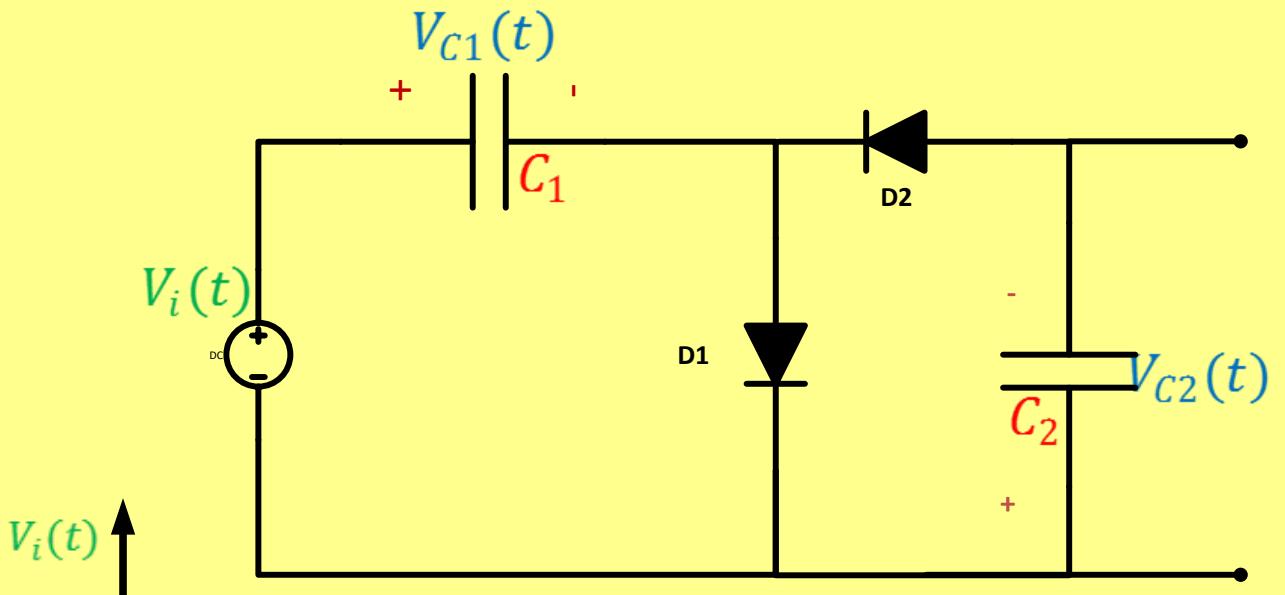
$$\text{and } V_{D2}(0^+) < 0V \quad \therefore D_2 \text{ off}$$




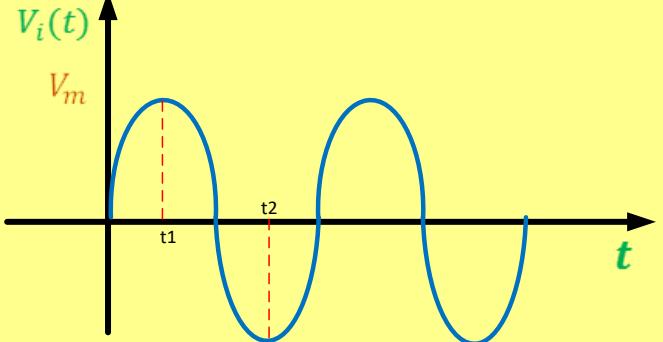

► C) at  $t = t_1^+$

$$V_{c1}(t_1^+) = V_m$$

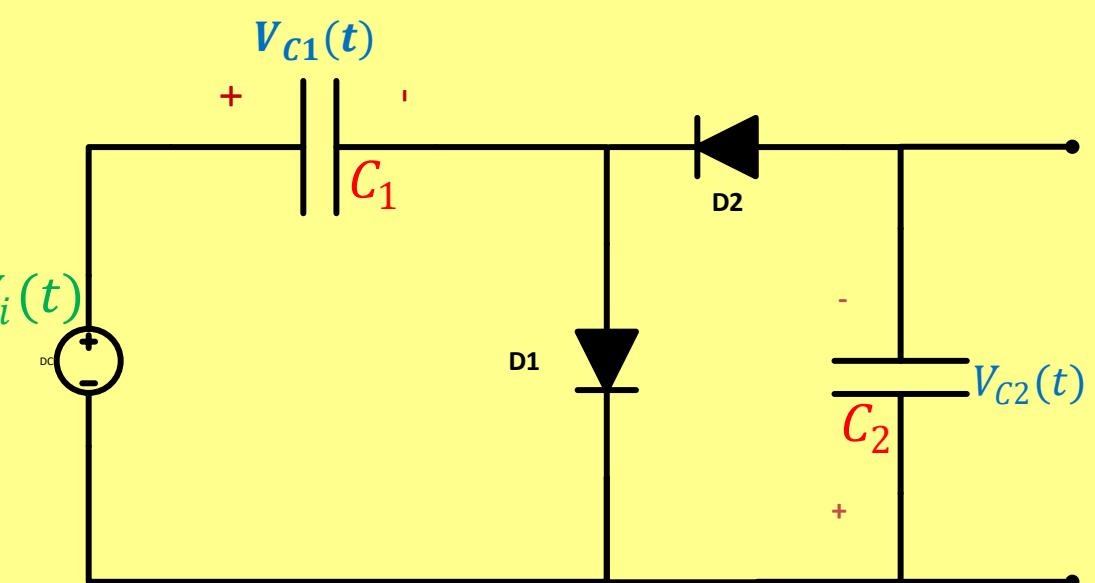$V_i(t_1^+) < V_m \therefore D_1$  is off , and  $D_2$  is on



► D) in the interval  $t_2 > t > t_1$


$C_2$  charges toward  $2V_m$

at  $t = t_2$

$$V_{c2}(t_2) = 2V_m$$

$$V_{c2}(t_2) = -V_i(t_2) + V_m$$

$$V_{c2}(t_2) = V_m + V_m = 2V_m$$

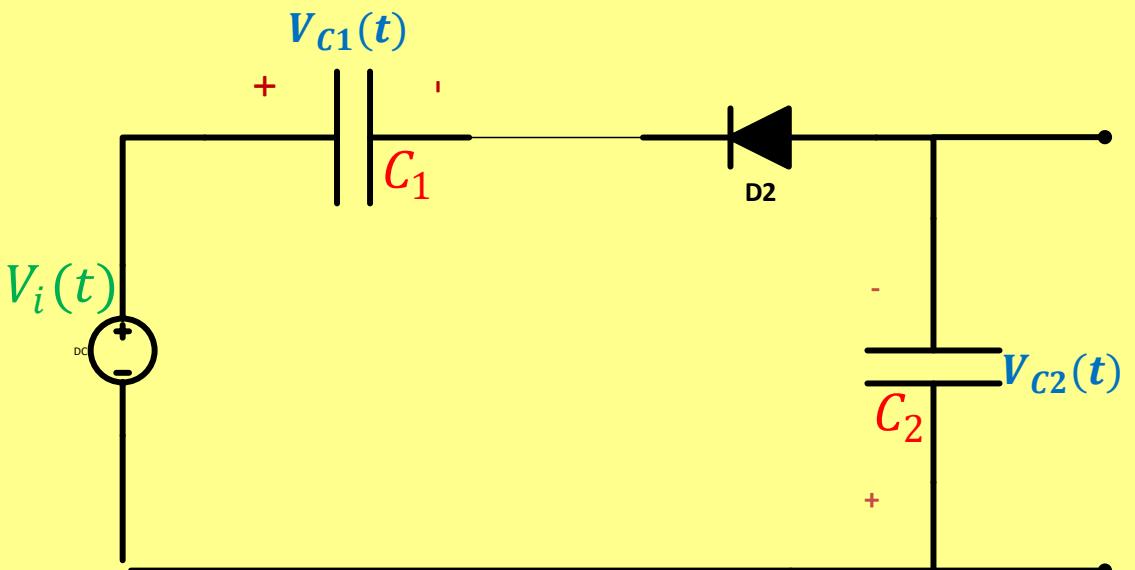


► E) at  $t = t_2^+$

$D_2$  is off,  $D_1$  is off

$$V_{c1}(t_2^+) = V_m$$

$$V_{c2}(t_2^+) = 2V_m$$

## Voltage Tripler

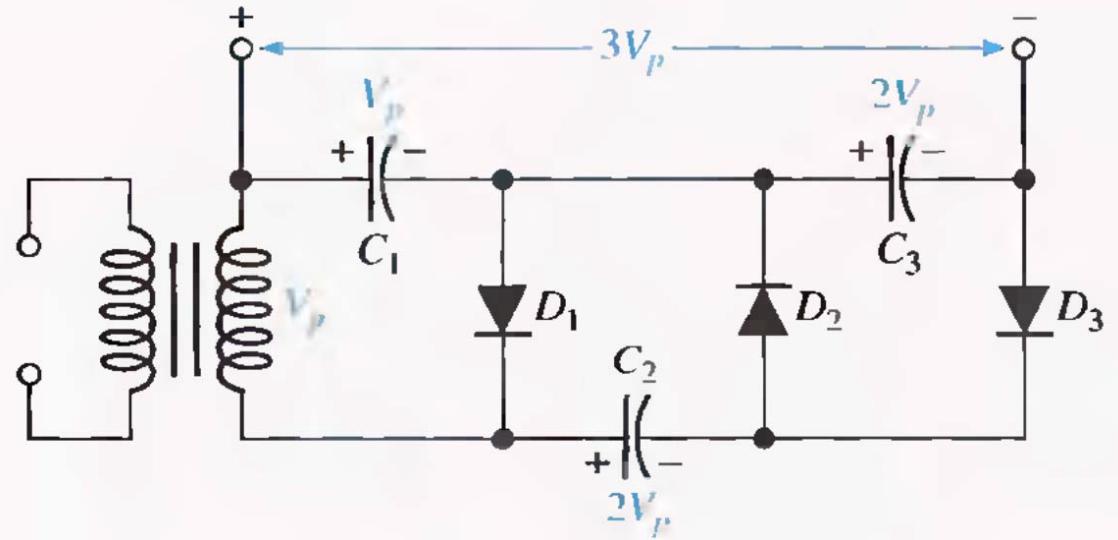

## Voltage Quadrupler

