






Dc Power Supply




half wave rectifier
center tapped transformer

Dc Power Supply



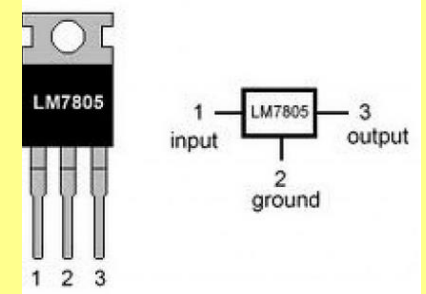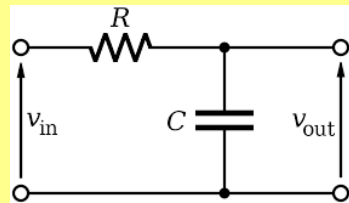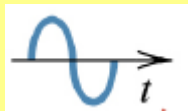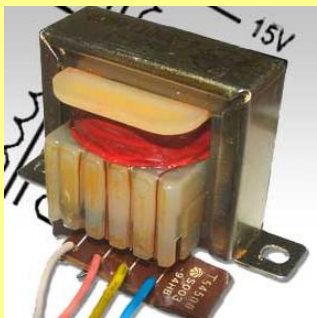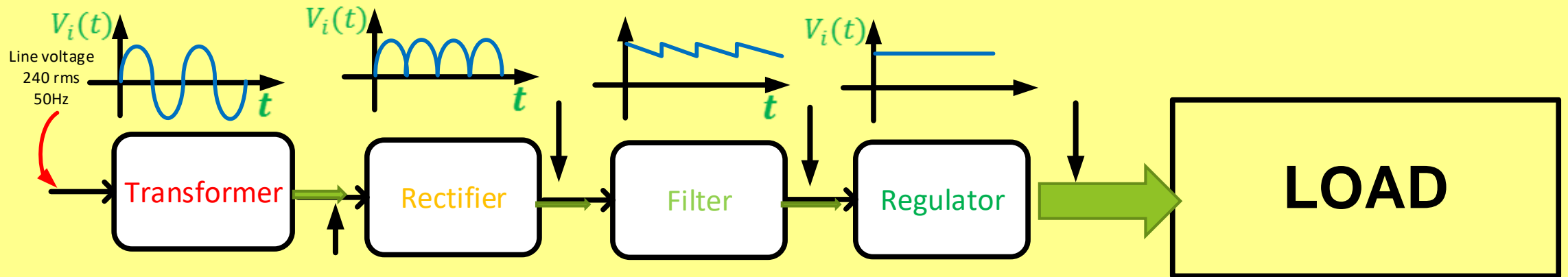- ▶ All electronic circuits and systems require a stable source of dc voltage and current (or dc power) to operate correctly.



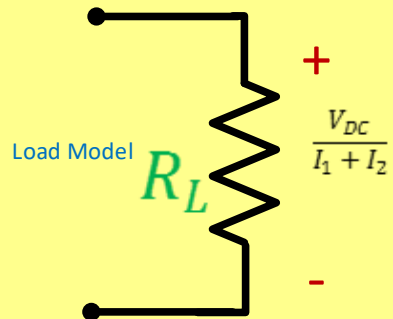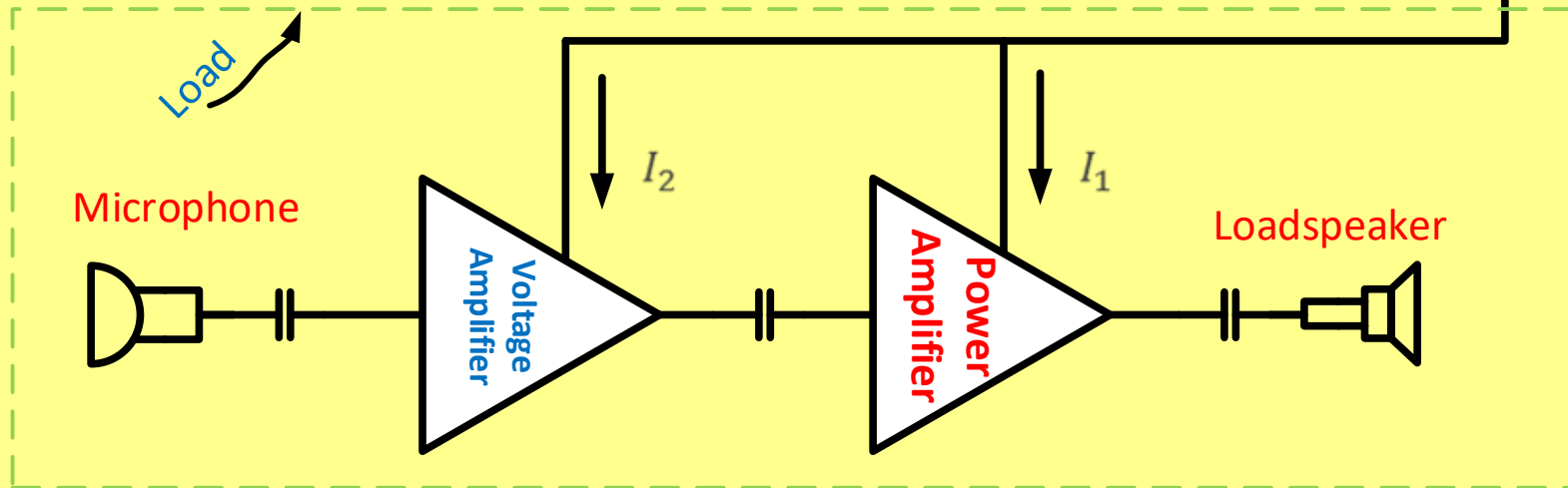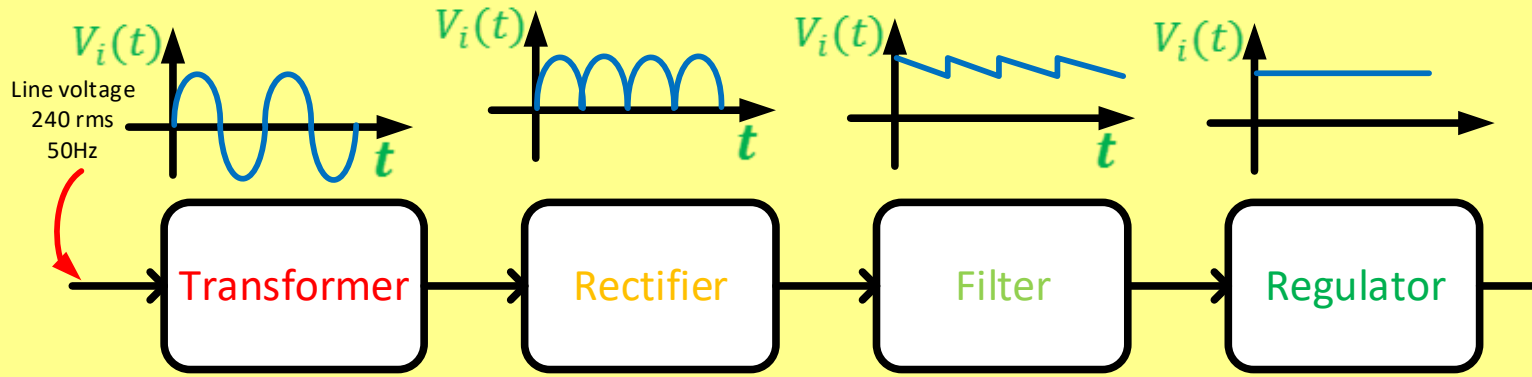


Dc Power Supply



- ▶ The basic power supply consists of a transformer, rectifier, filter, and a regulator.
- ▶ **Transformer:** Used to increase or decrease the amplitude of the line voltage

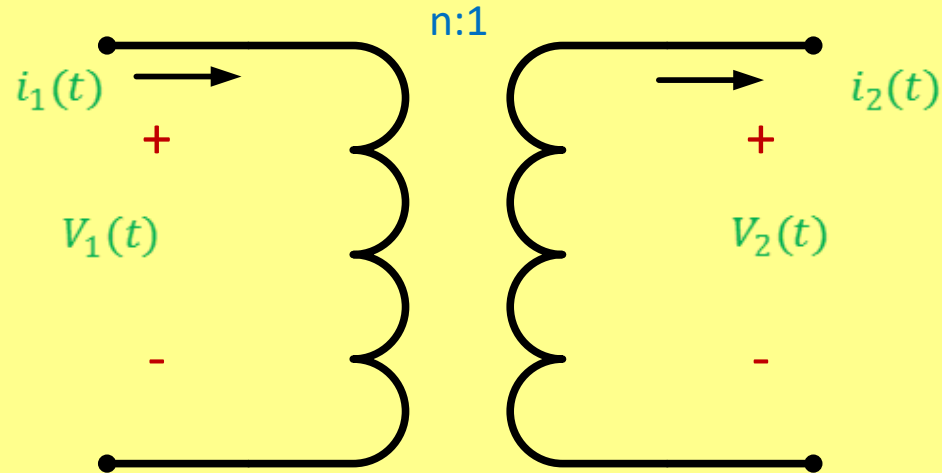- ▶ $V_2(t) = \frac{1}{n} V_1$
 $i_2(t) = n i_1(t)$



Dc Power Supply

- **Rectifier**: used to convert the ac voltage (zero- average value) into either positive and negative pulsating dc.


- 1) Half- Wave Rectifier

- $V_i(t) = \frac{V_s(t)}{n}$

- **A)** when $V_i(t) > 0$, Diode is on (short circuit)

- $\therefore V_o(t) = V_i(t)$



- $\therefore V_D(t) = 0$




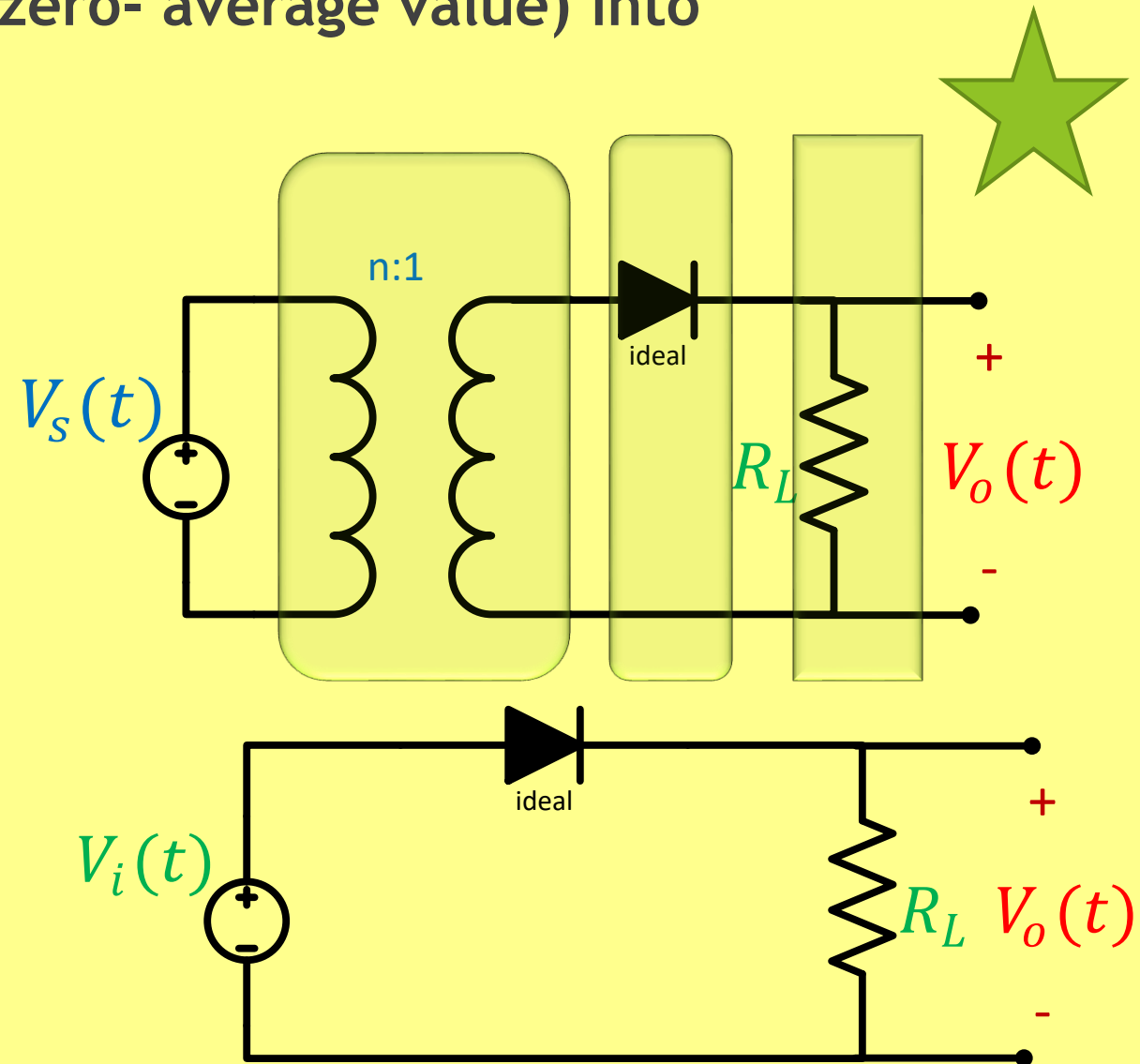


B) when $V_i(t) < 0$, Diode is off (open circuit)

$$\therefore V_o(t) = 0$$

$$\therefore V_D(t) = V_i(t)$$

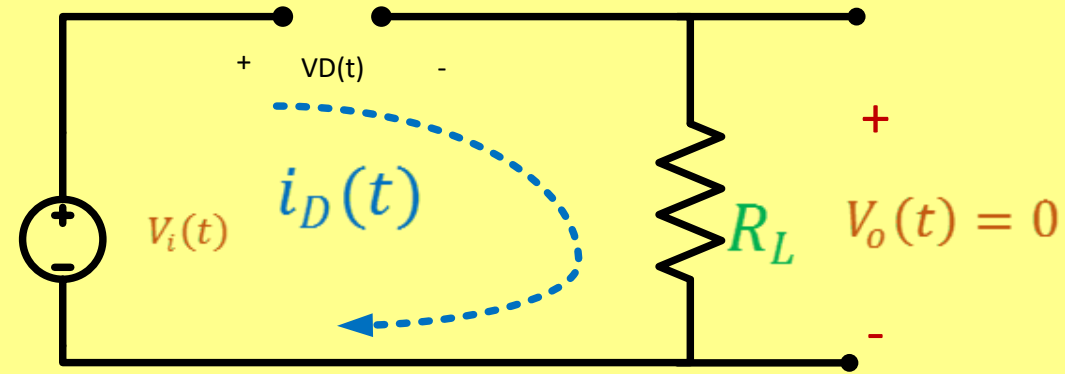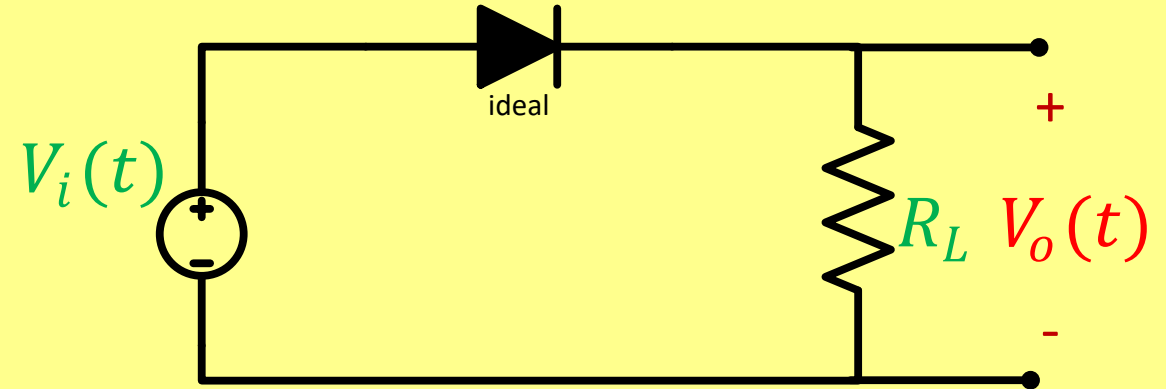

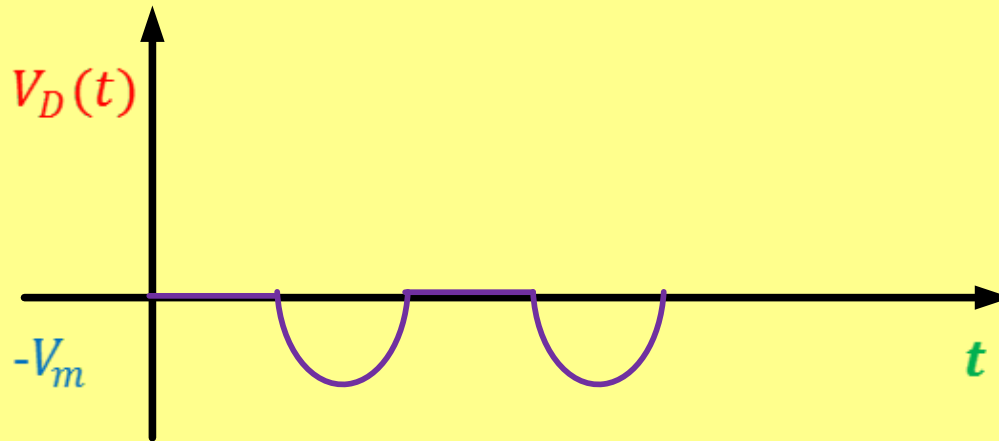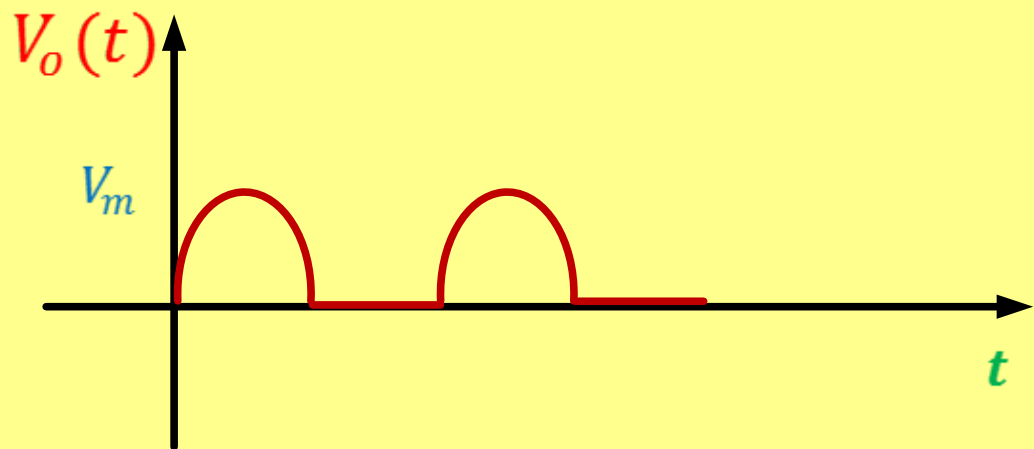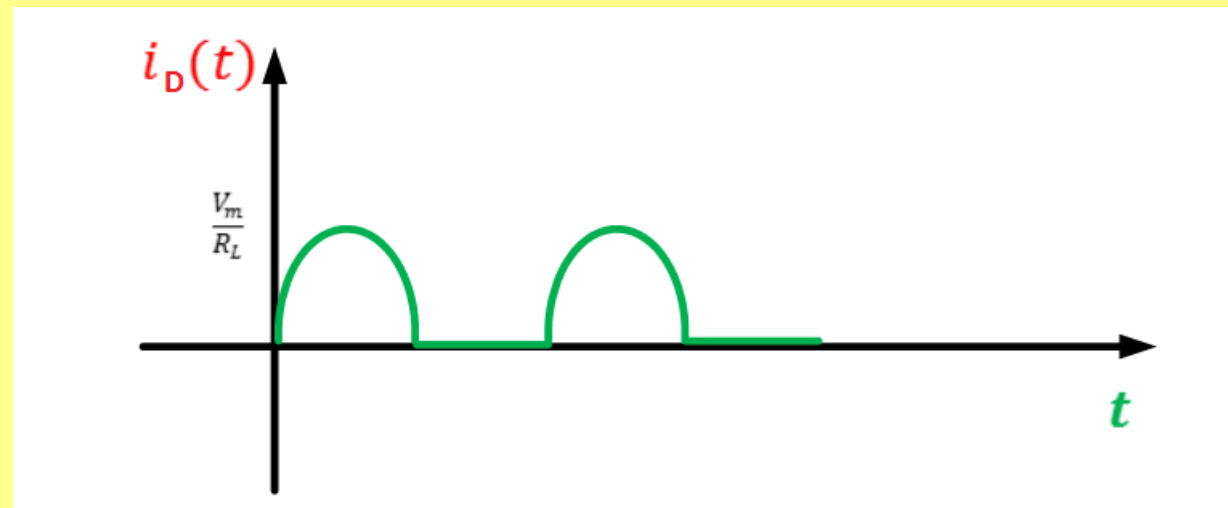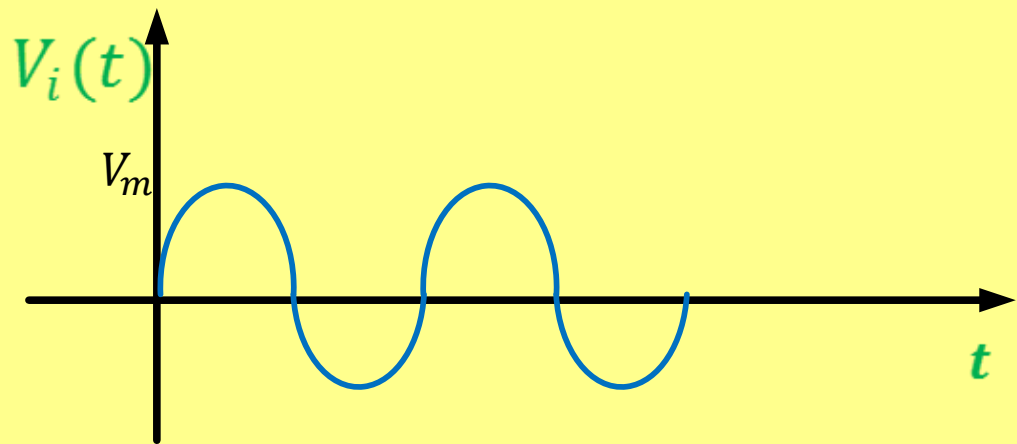




$$\begin{aligned} \blacktriangleright V_{o,av} &= \frac{1}{T} \int_0^T V_o(t) dt \\ &= \frac{V_m}{2\pi} \int_0^\pi \sin \theta d\theta \end{aligned}$$

$$\blacktriangleright V_{o,av} = \frac{V_m}{\pi}$$

$$\blacktriangleright T = T_o$$


$$\blacktriangleright f = f_o$$
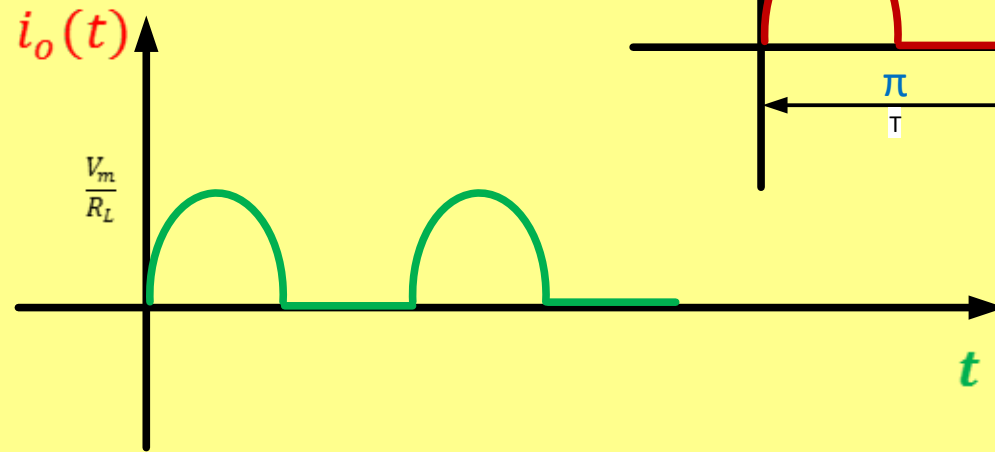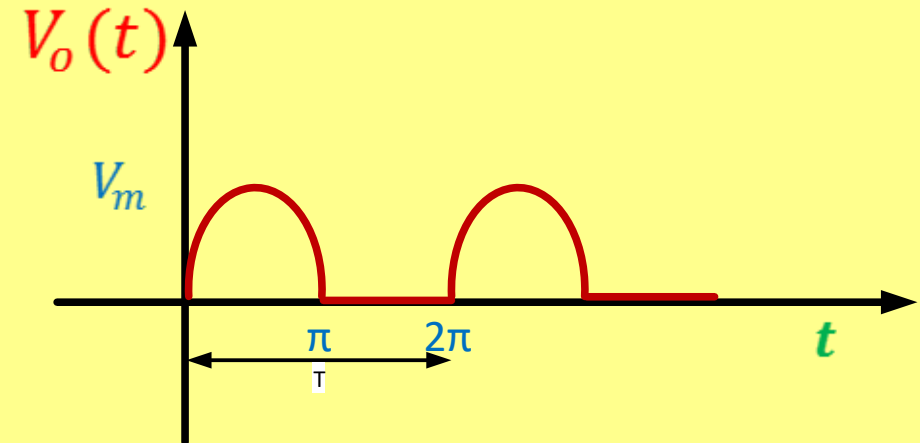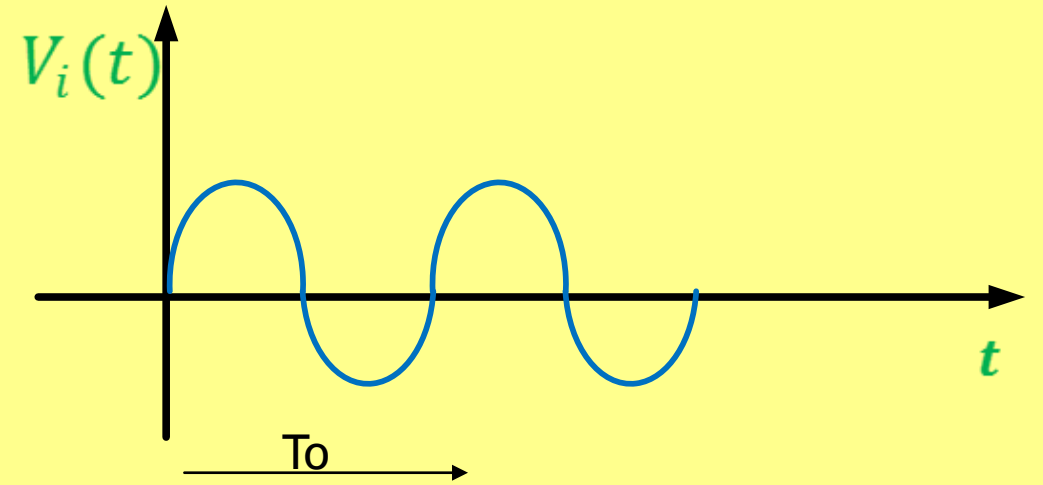
$$\blacktriangleright i_{D(t),av} = \frac{V_m}{\pi R_L}$$



Important Electrical Ratings

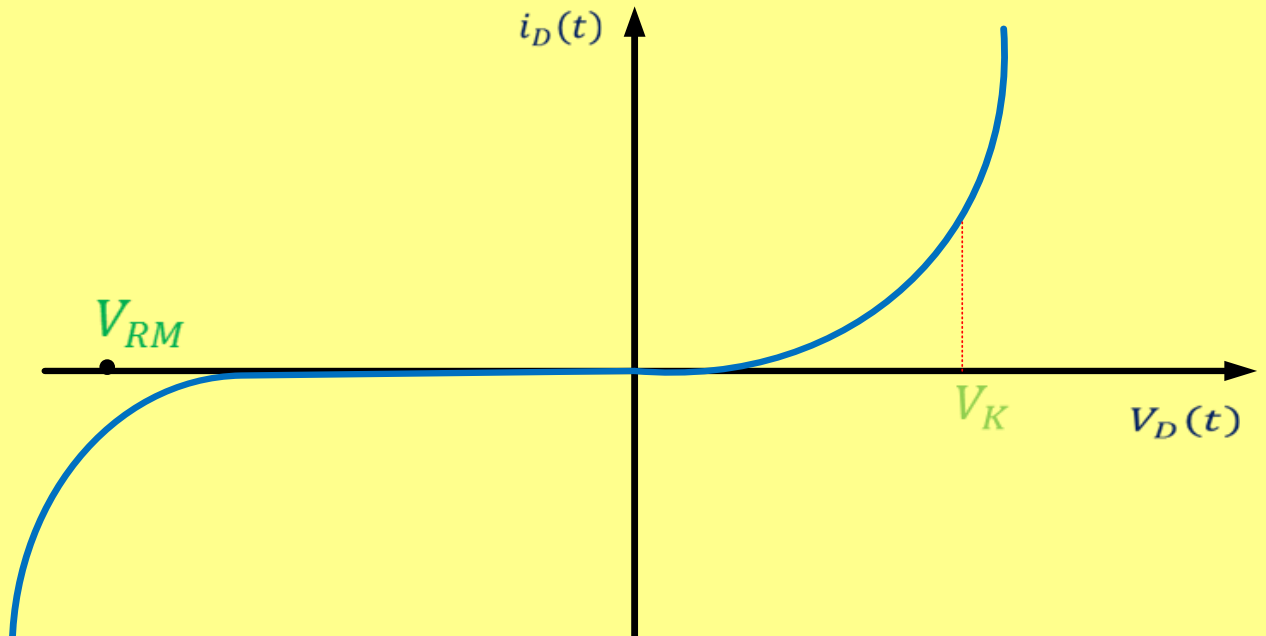- ▶ I_{FM} = Maximum Forward Current
- ▶ I_{FM} = Maximum average current that can safely be sustained by the diode when it is forward biased
- ▶ V_{RM} = Maximum Reverse Voltage
- ▶ V_{RM} = Maximum voltage that can be applied to the diode in the Reverse bias polarity before voltage break down occur
- ▶ PIV \equiv Peak Inverse Voltage
- ▶ PIV = V_{RM}



► ∴ For the half-wave rectifier


$$V_{o,av} = \frac{V_m}{\pi}$$

$$I_{FM} = \frac{V_m}{\pi R_L}$$

$$\text{PIV} = -V_m \quad \text{Prove ???}$$

To calculate PIV

When $V_i(t) < 0$, Diode is off

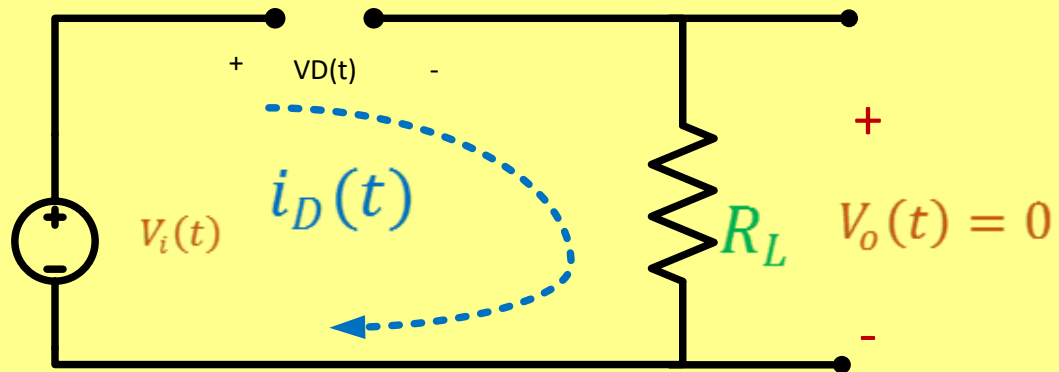


► $V_D(t) = V_i(t) < 0$

$$V_{D(t),max} = -V_m$$

Full-Wave Rectifier

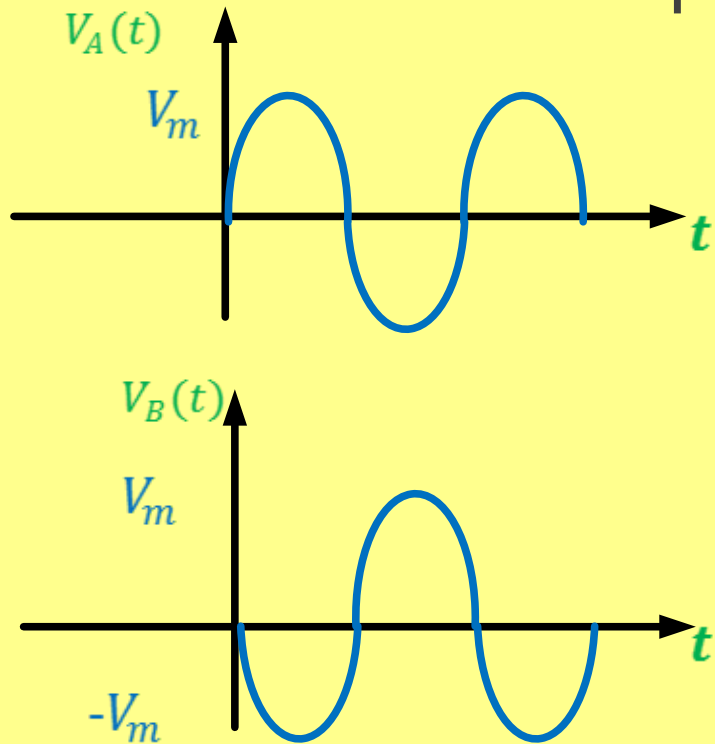
- ▶ A) Center-tapped transformer full-wave Rectifier
- ▶ V_A , V_B have the same amplitude but 180° out of phase



$$V_A(t) = - V_B(t)$$

$$V_A(t) = \frac{1}{n} V_s(t)$$

$$V_B(t) = - \frac{1}{n} V_s(t)$$

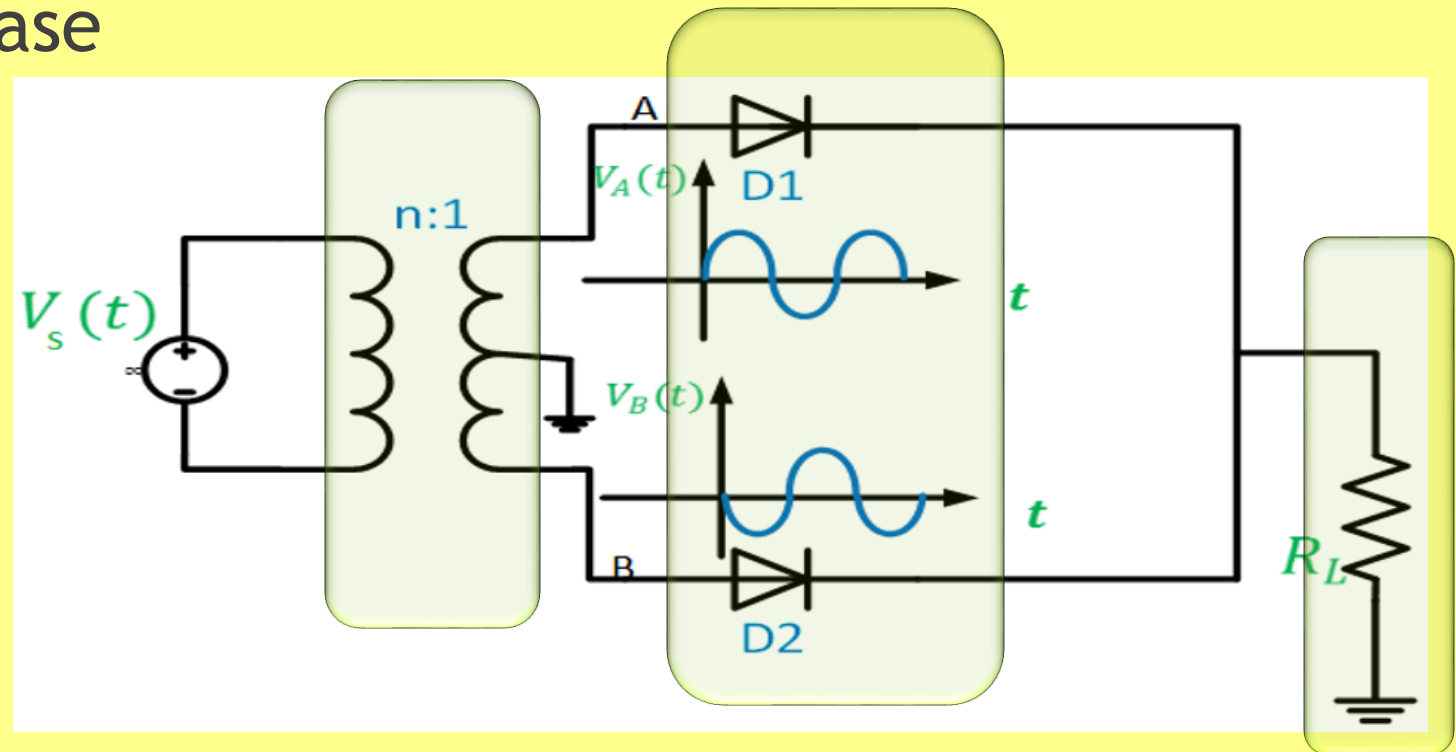

D_1 and D_2 are ideal

Simplified Circuit




D_1 and D_2 are ideal

► 1) when $V_s(t) > 0$

$V_A(t) > 0$, D_1 is on

$V_B(t) < 0$, D_2 is off

► $V_o(t) = V_A(t)$

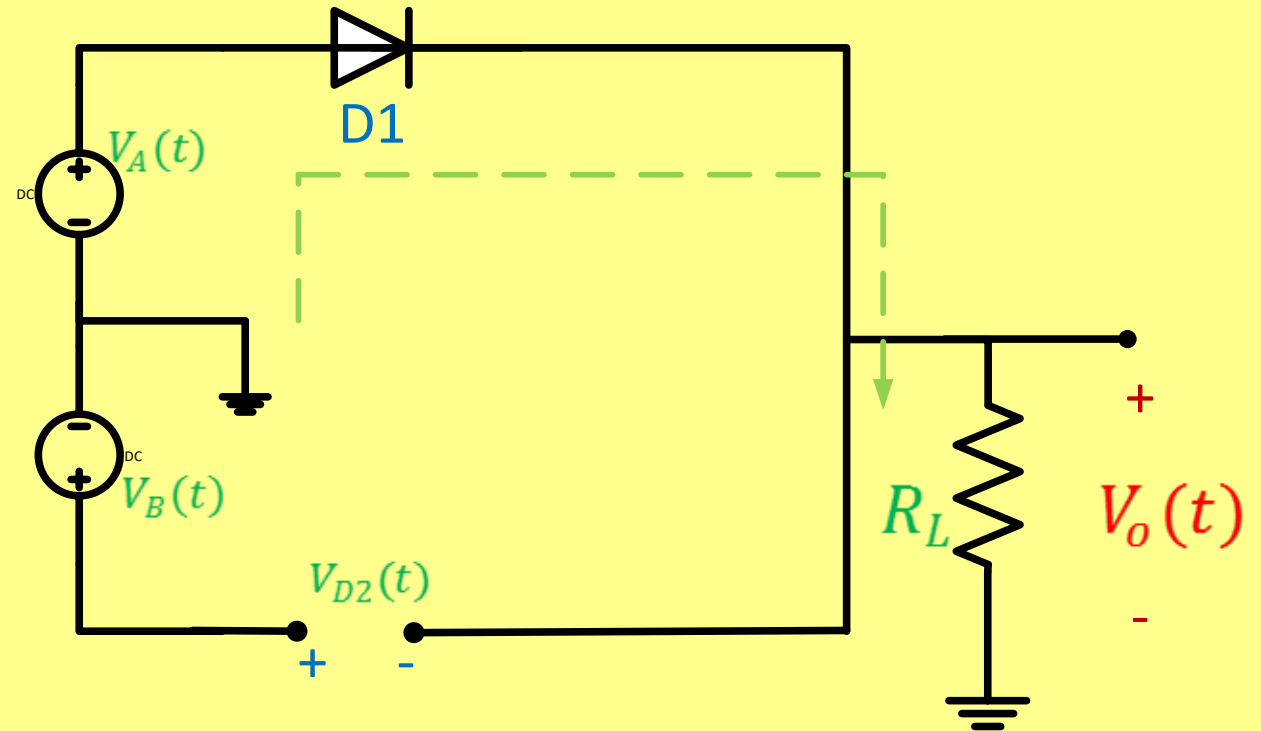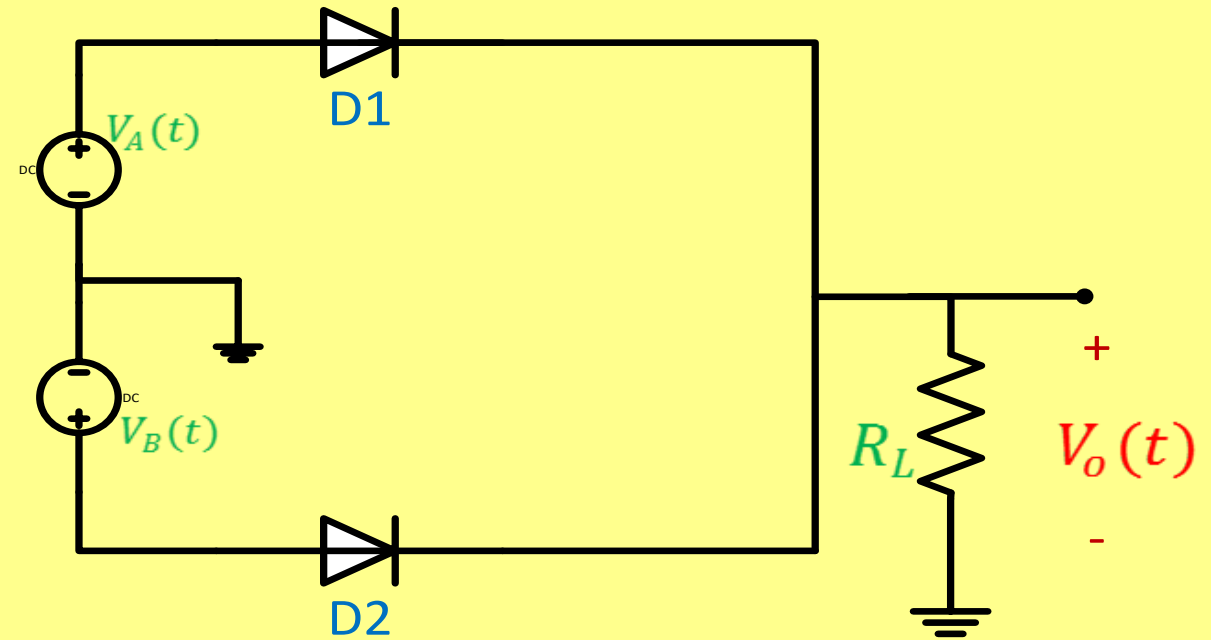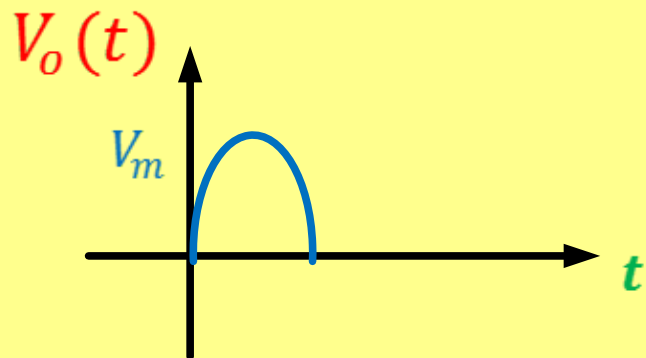


► 2) when $V_s(t) < 0$



$V_A < 0$; D_1 is off

$V_B > 0$; D_2 is on

► $\therefore V_o(t) = V_B(t) > 0$

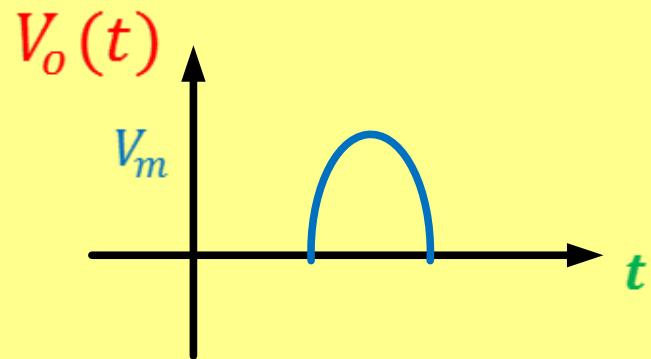

For a complete cycle of $V_s(t)$

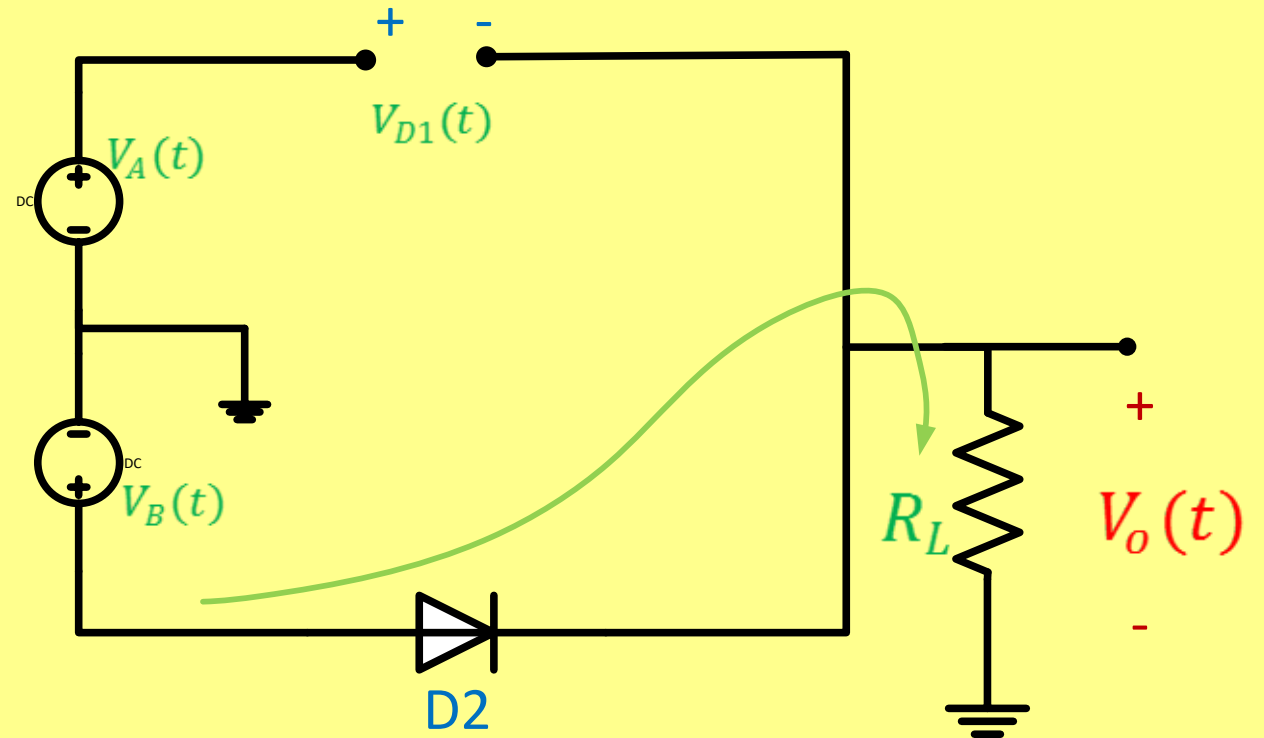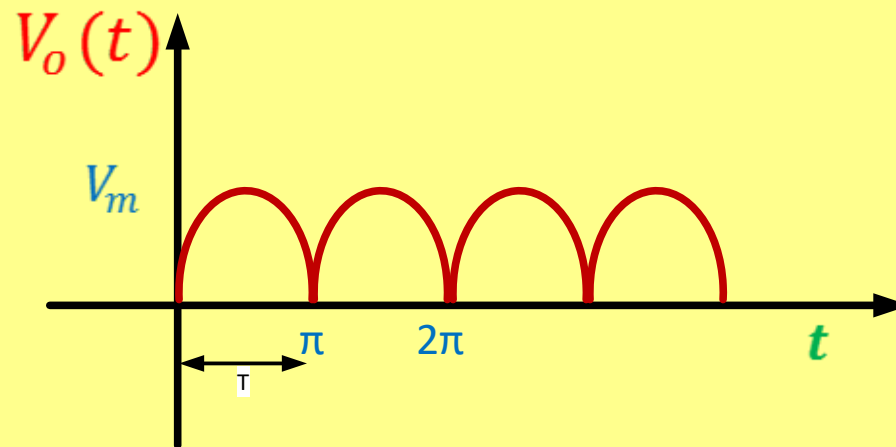


To calculate PIV

$$V_{D2}(t) = V_B(t) - V_A(t)$$

$$V_{D2}(t)_{,max} = -V_m - V_m$$

$$V_{D2}(t)_{,max} = -2V_m$$

$$\therefore \text{PIV} = -2V_m$$



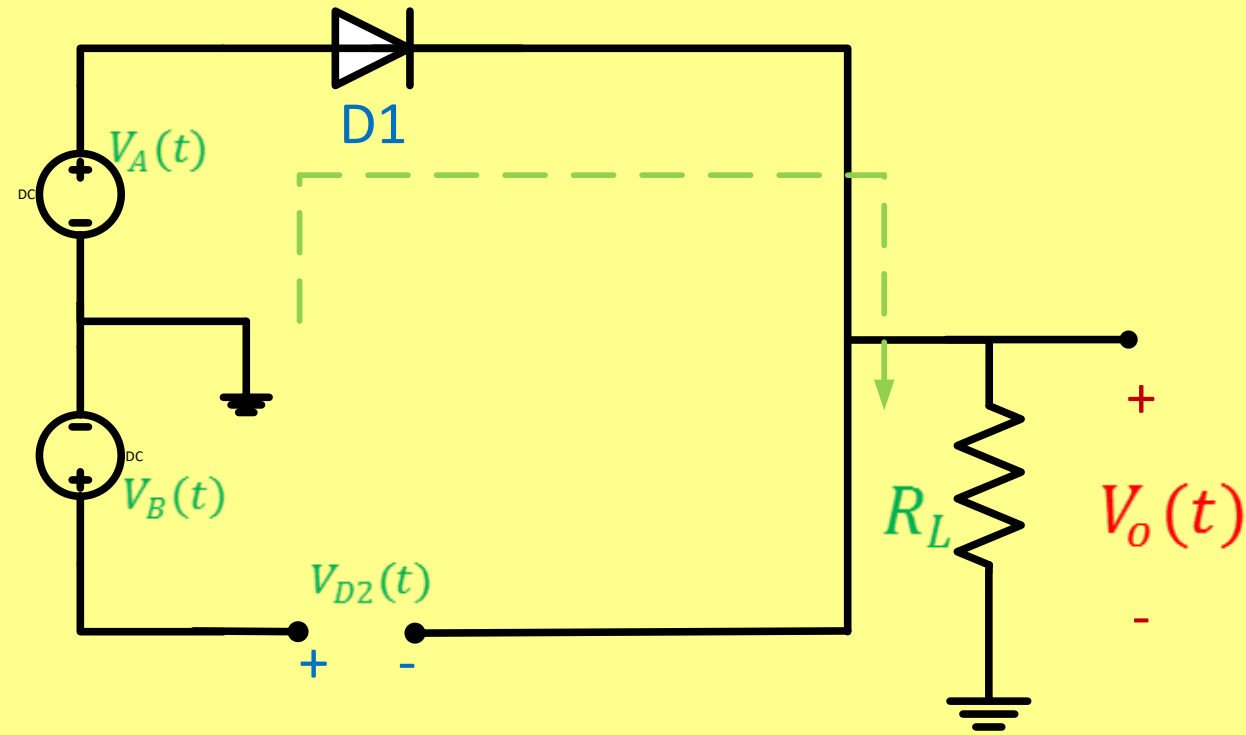


$V_A(t) > 0$, D_1 is on

$V_B(t) < 0$, D_2 is off

- ▶ $V_{o,av} = \frac{2V_m}{\pi}$
- ▶ $PIV = -2V_m$
- ▶ $T = \frac{1}{2}T_o$
- ▶ $f = 2f_o$

Diodes currents

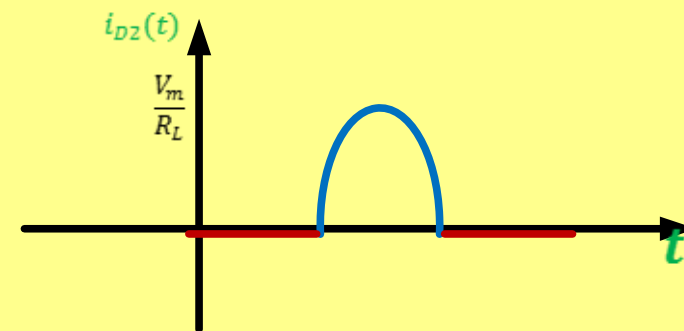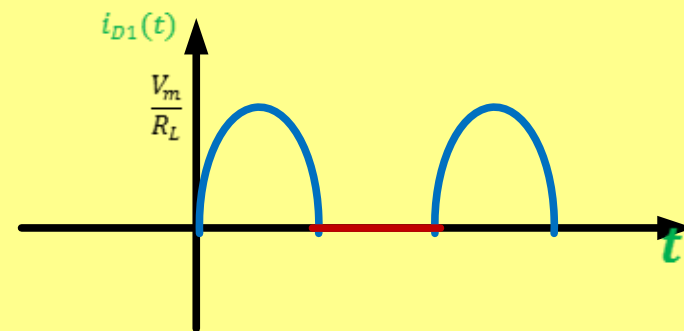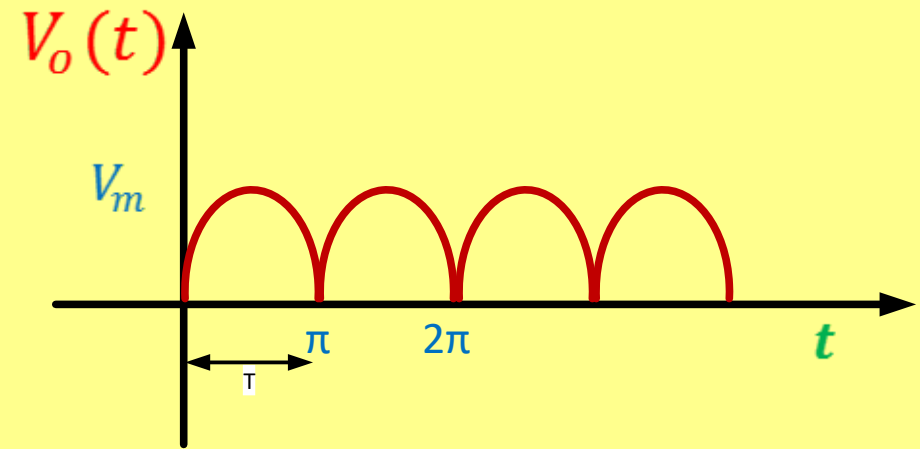

If the diodes have V_k

