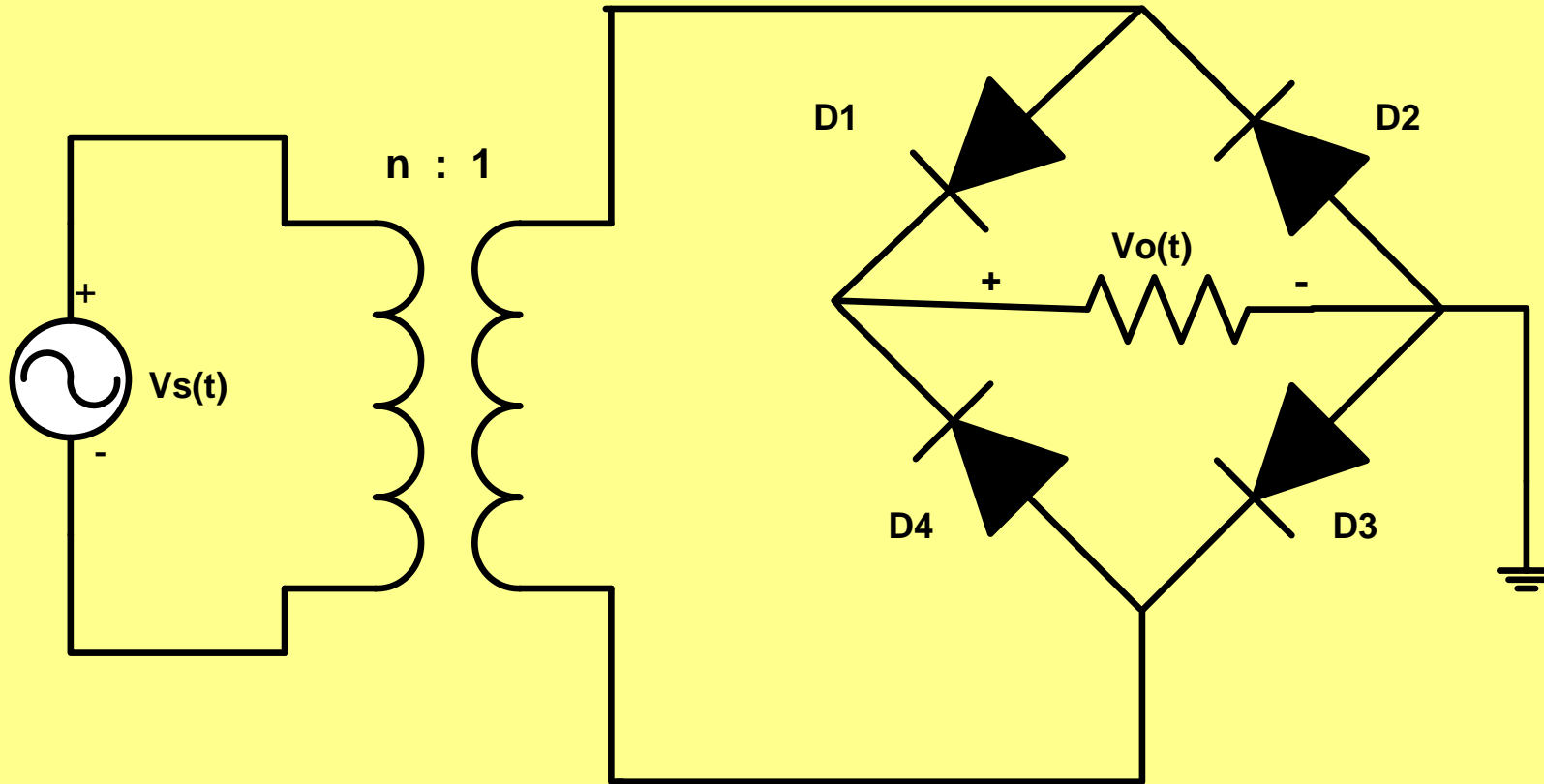


Dc Power Supply

Bridge Full Wave Rectifier


Filter

b) Bridge full-wave rectifier



b) Bridge full-wave rectifier

► Simplified circuit

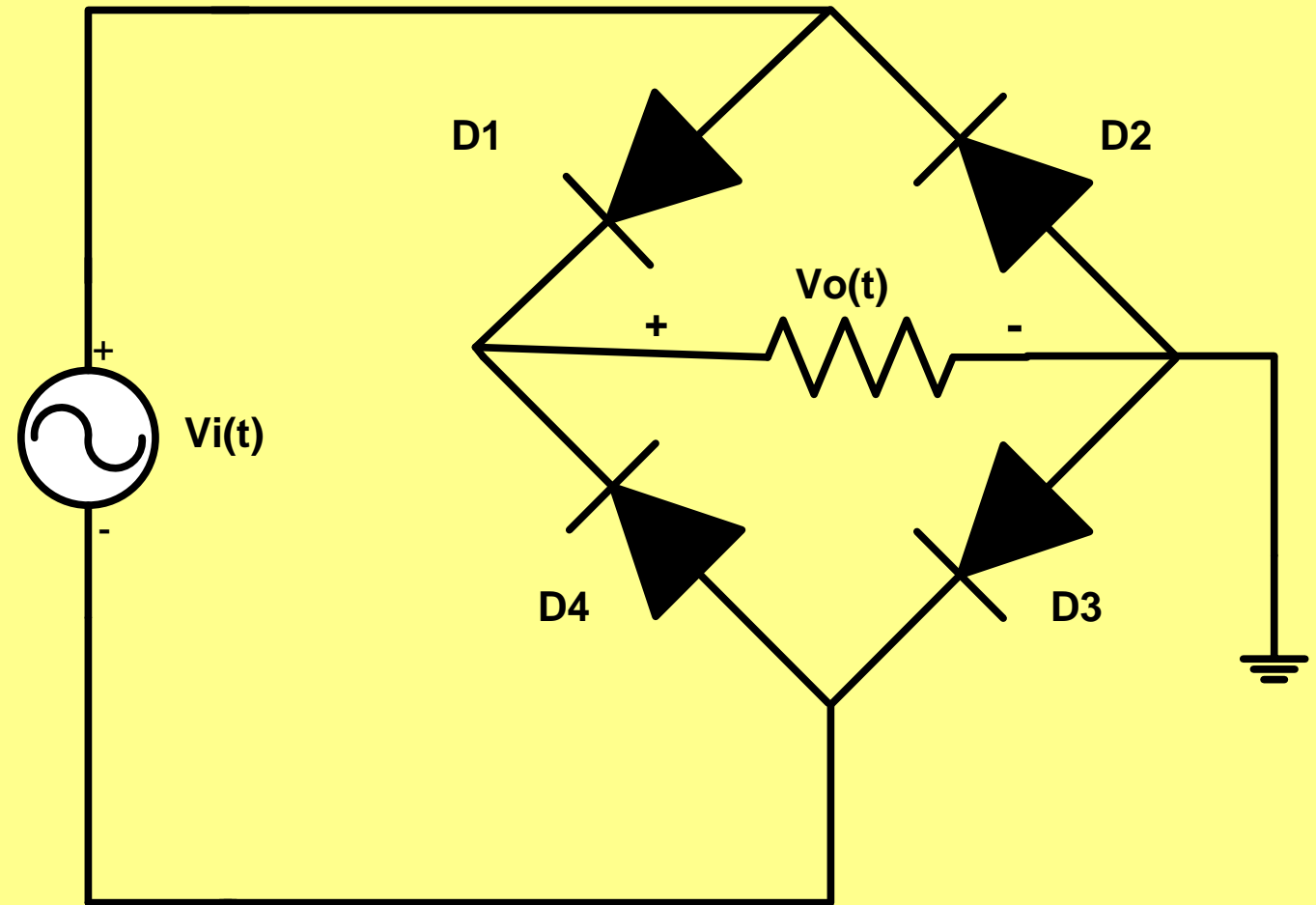

b) Bridge full-wave rectifier



► 1) when $V_s(t) > 0$

$$\therefore V_i(t) > 0$$

$\therefore D_1$ and D_3 are on

$\therefore D_2$ and D_4 are off

► $V_o(t) = V_i(t)$

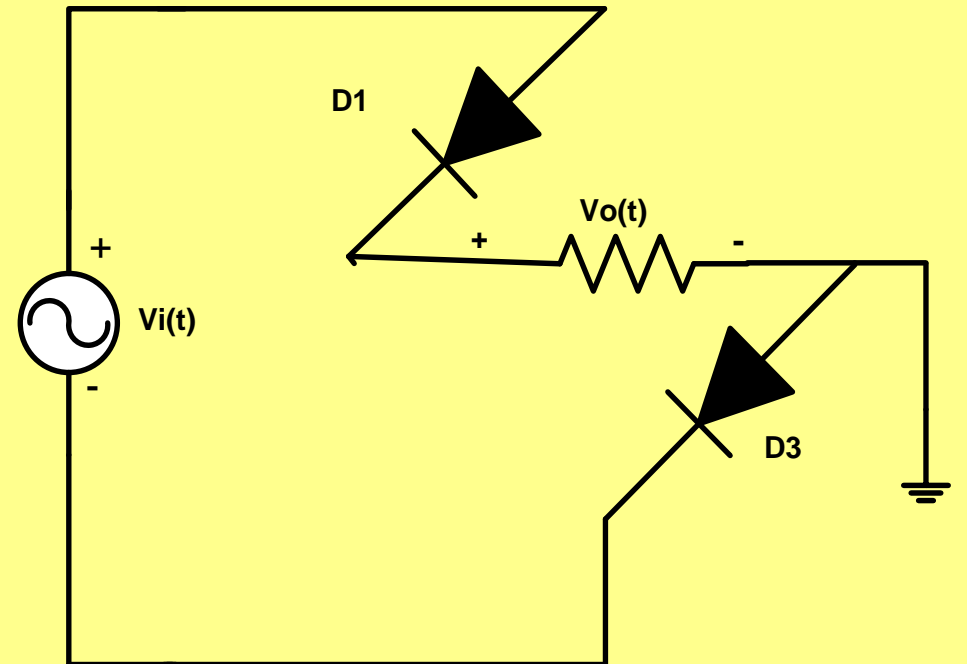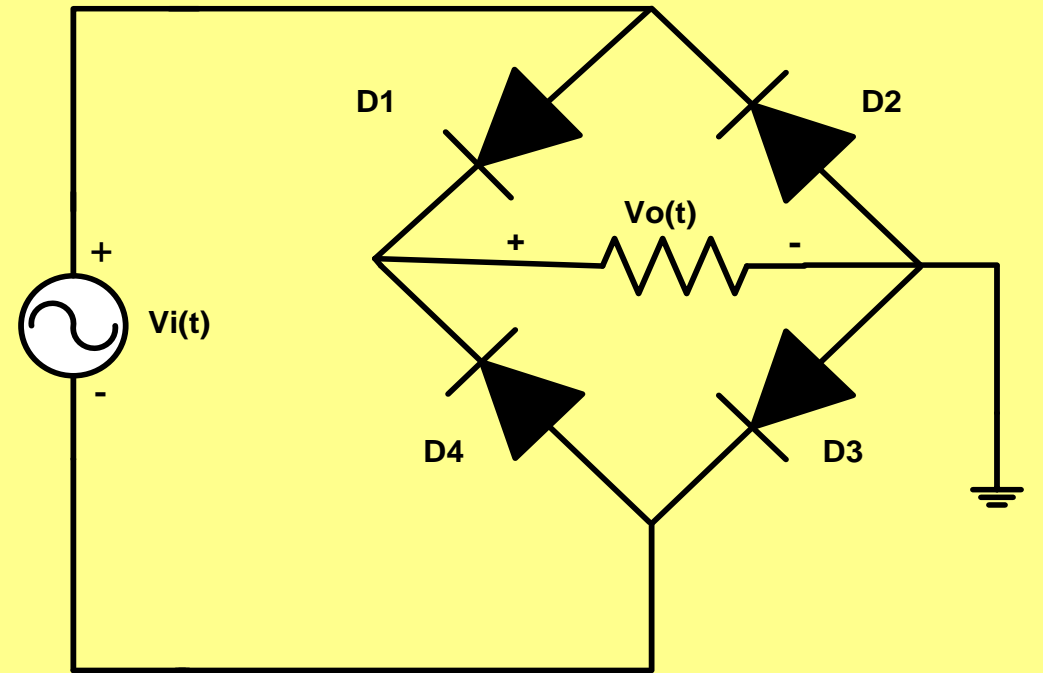

► 2) when $V_s(t) < 0$




$$\therefore V_i(t) < 0$$

$\therefore D_1$ and D_3 are off

$\therefore D_2$ and D_4 are on

$$\therefore V_o(t) = -V_i(t)$$

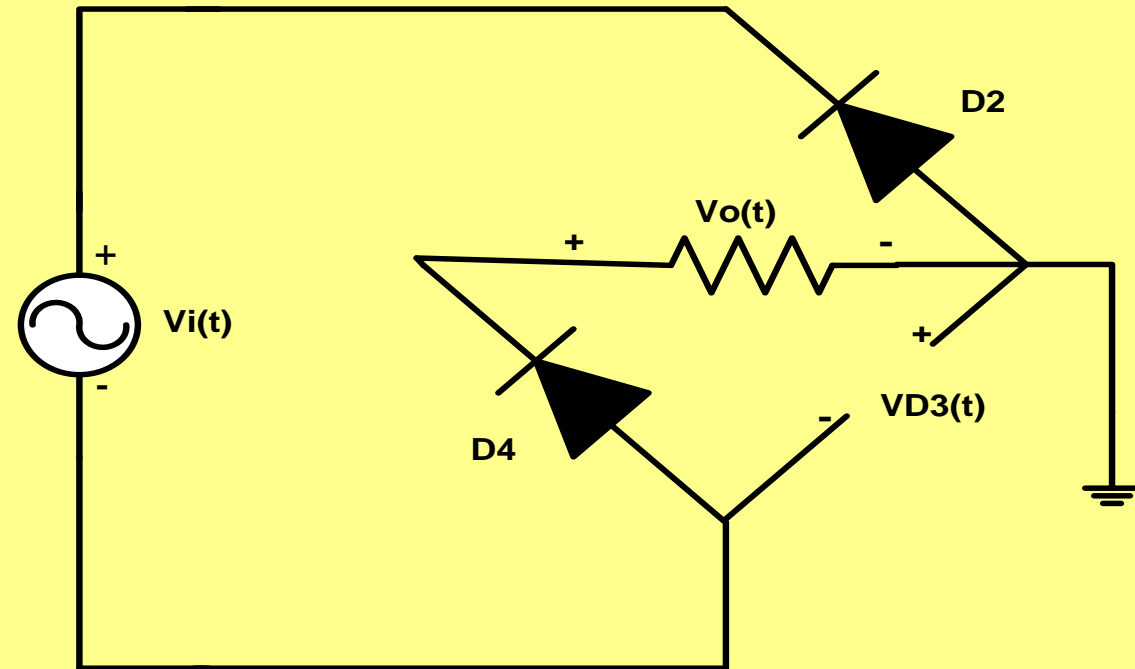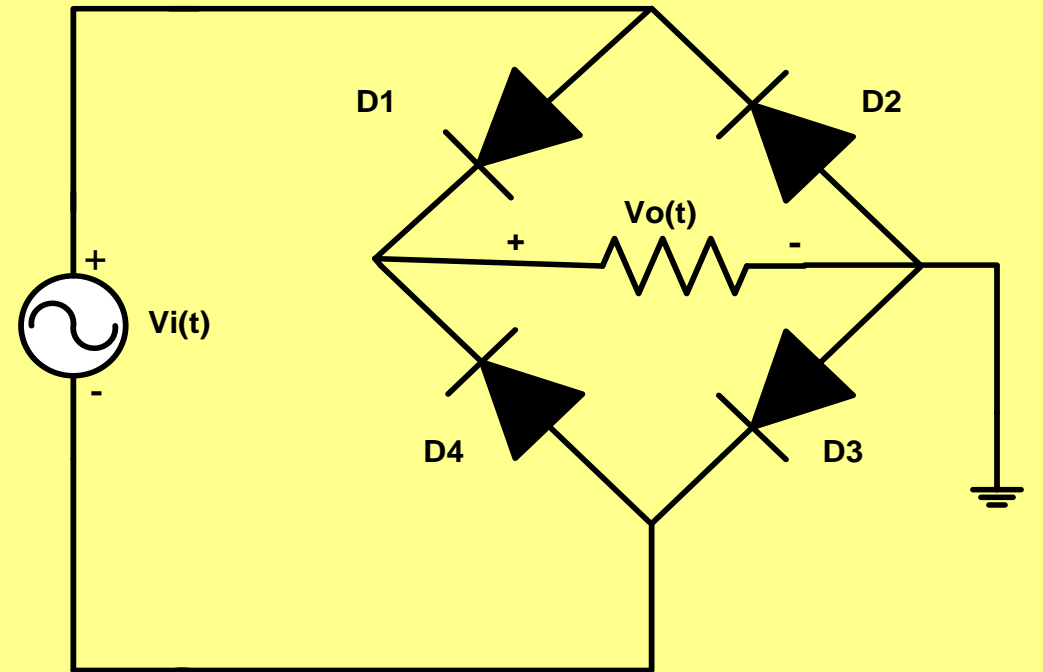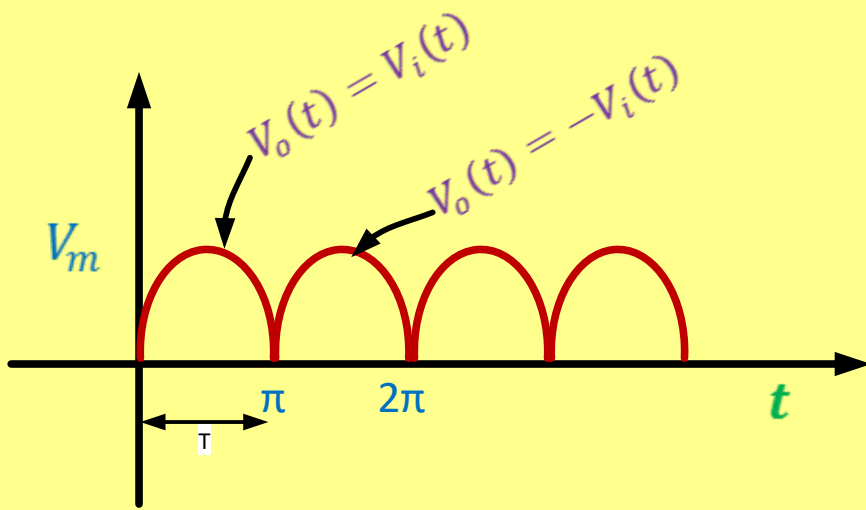\therefore For the complete cycle of $V_i(t)$



► ∴ For Bridge full-wave rectifier

► $V_{o,av} = \frac{1}{T} \int_0^T V_o(t) dt$

$$V_{o,av} = \frac{2V_m}{\pi}$$

► $T = \frac{1}{2} T_o$



► $f = 2f_o$

► To calculate the PIV of the D3

► $V_i(t) < 0$


$$V_{D3}(t) = V_i(t)$$

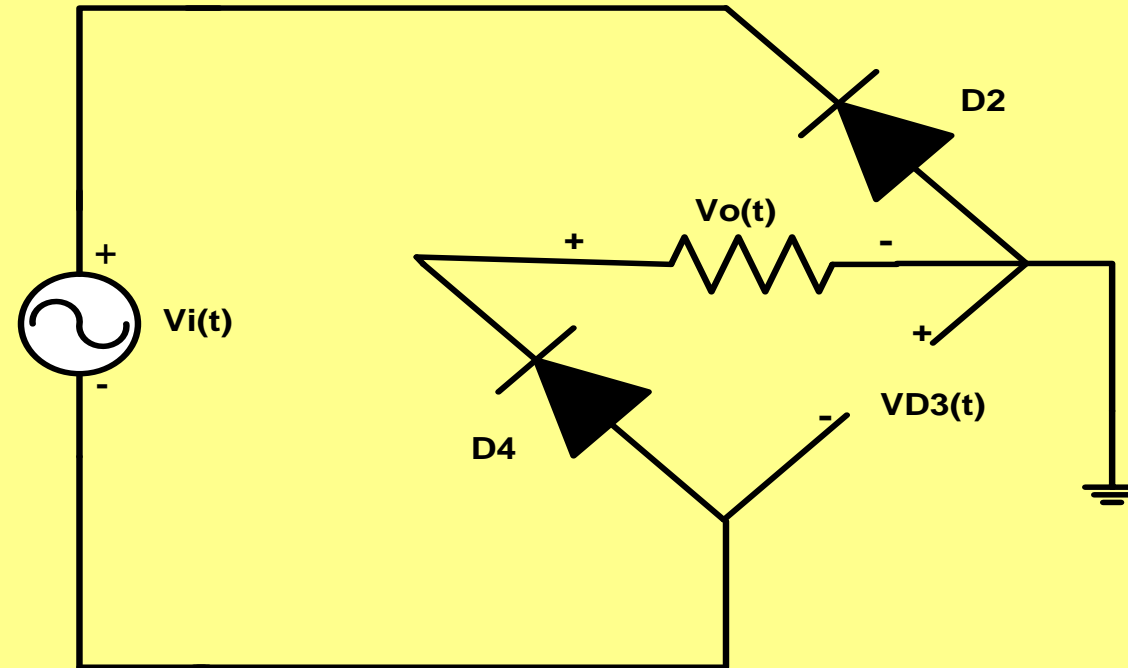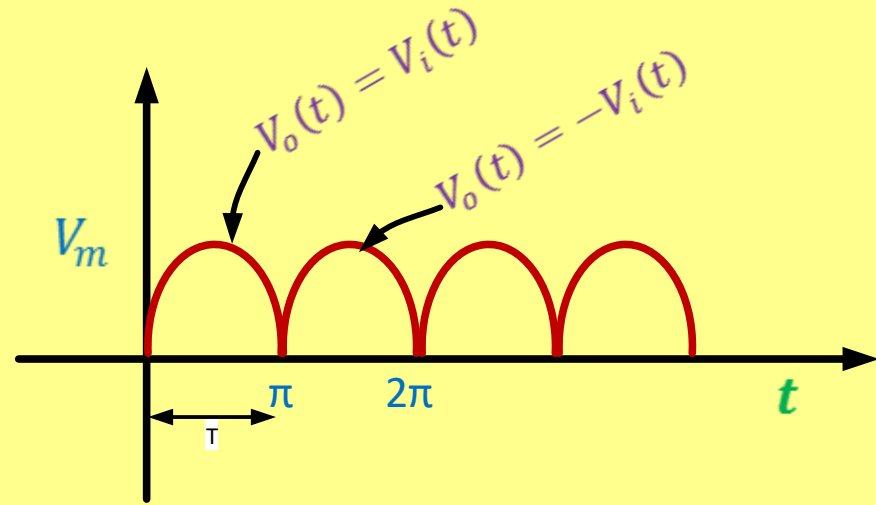∴ $V_{D3}(t)_{max} = -V_m$ ∴ PIV = $-V_m$




Filter

The Fourier Series of Selected Waveforms

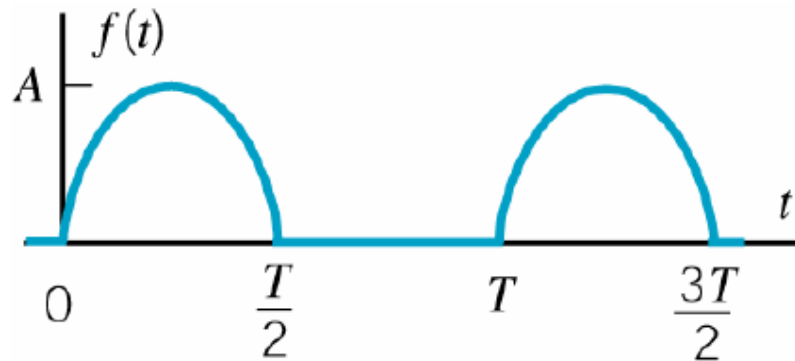

Half wave rectified sine wave: $\omega_0 = \frac{2\pi}{T}$

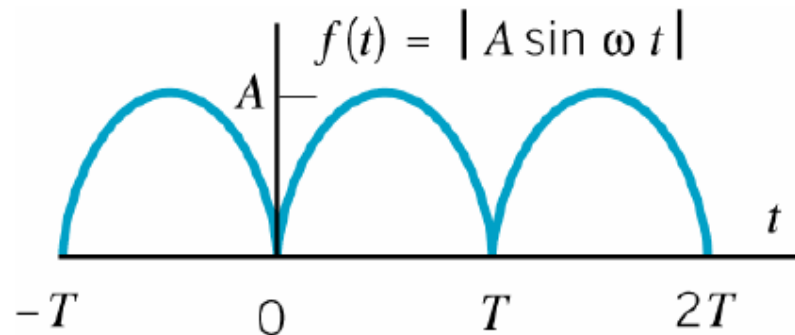
$$f(t) = \frac{A}{\pi} + \frac{A}{2} \sin \omega_0 t - \frac{2A}{\pi} \sum_{n=1}^{\infty} \frac{\cos(2n\omega_0 t)}{4n^2 - 1}$$



Full wave rectified sine wave: $\omega_0 = \frac{2\pi}{T}$

$$f(t) = \frac{2A}{\pi} - \frac{4A}{\pi} \sum_{n=1}^{\infty} \frac{\cos(n\omega_0 t)}{4n^2 - 1}$$

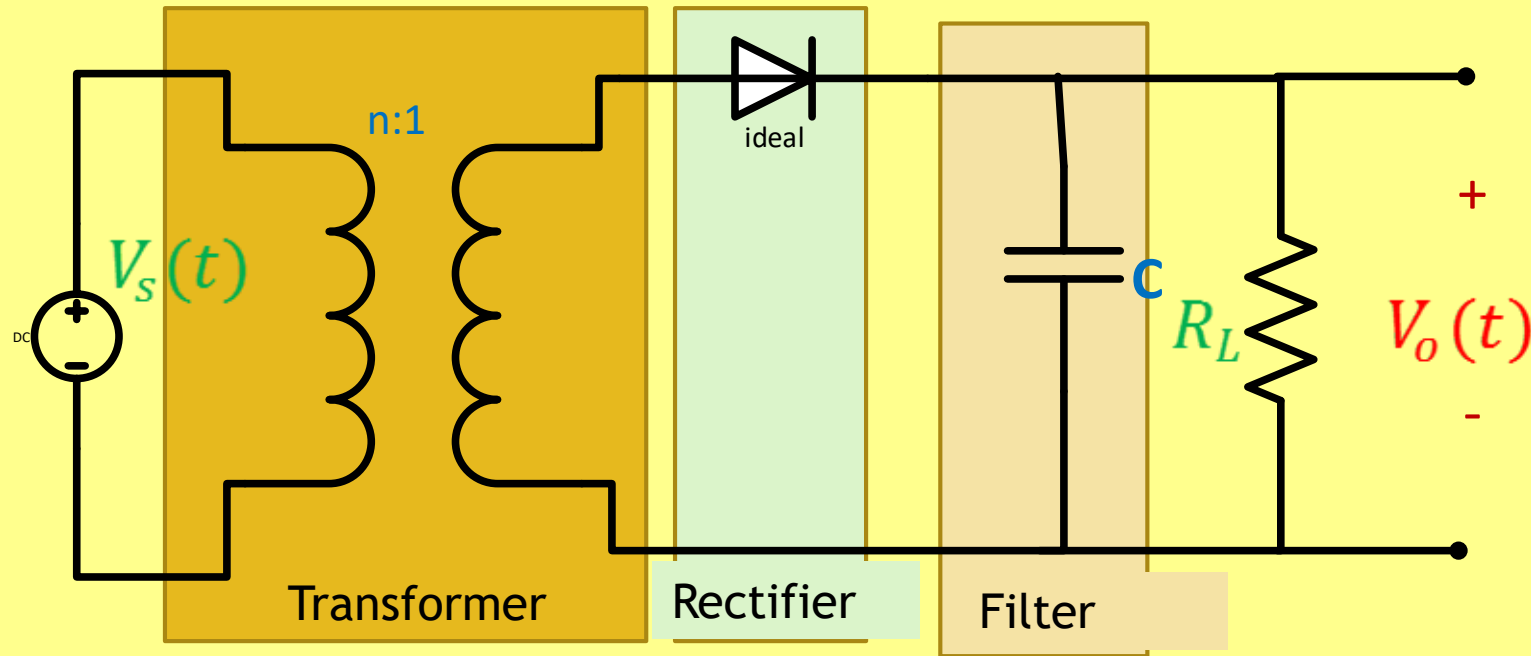- **Filter:** used to smooth out the pulsating dc produced by the rectifier by removing its ac ripple contents and passing its dc component (average value)




Simplified Circuit

▶ A) when $V_i(t) > V_c(t)$
Diode is on and



▶ $V_L(t) = V_c(t) = V_i(t)$

▶ B) when $V_i(t) < V_c(t)$

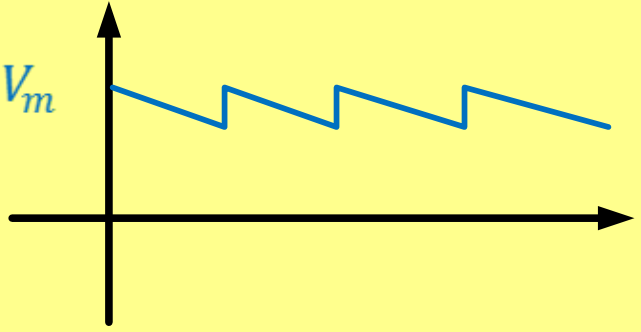Diode is off and the capacitor starts discharging



Approximated


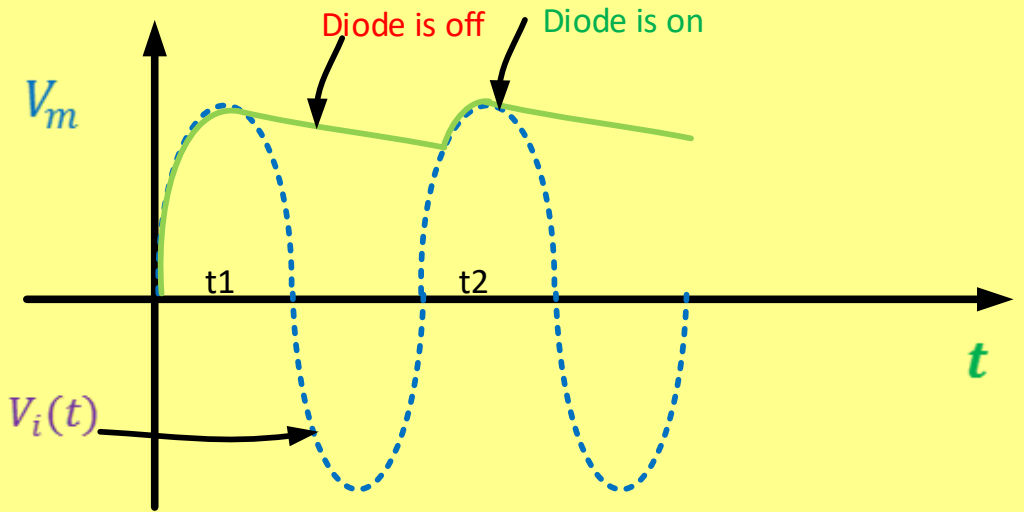
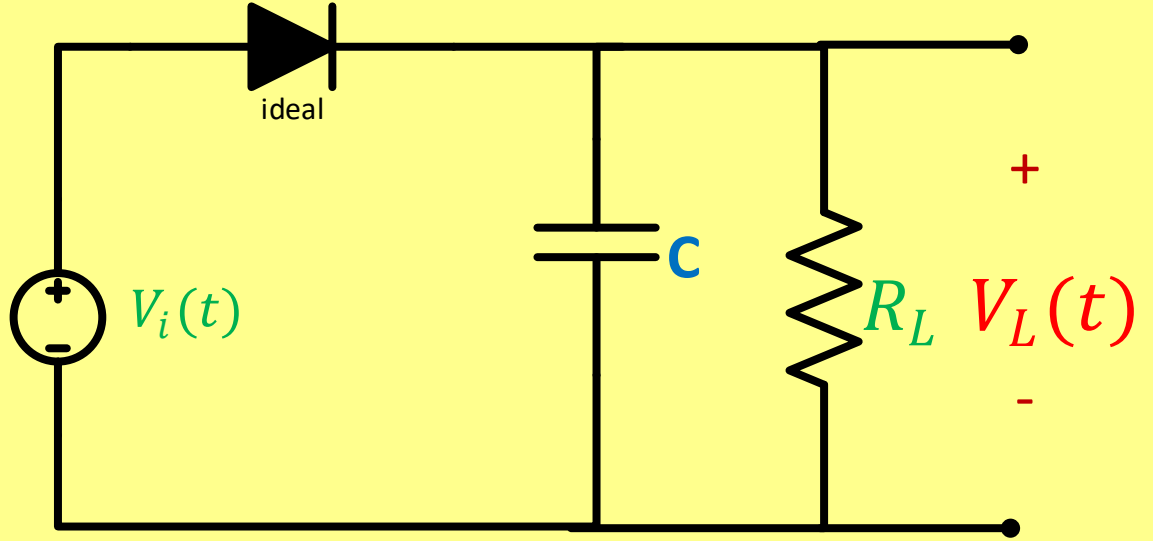


- ▶ Ripple factor is an indicator for the effectiveness of the filter

$$r = \frac{RMS(ripple\ voltage)}{Average\ value\ of\ the\ output\ signal} \times 100\%$$

- ▶ The output signal can be approximated as shown

$$V_L(t) = V_{L,dc} + V_{Lr}(t)$$

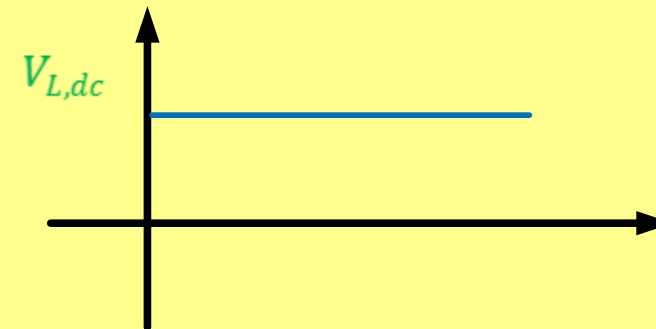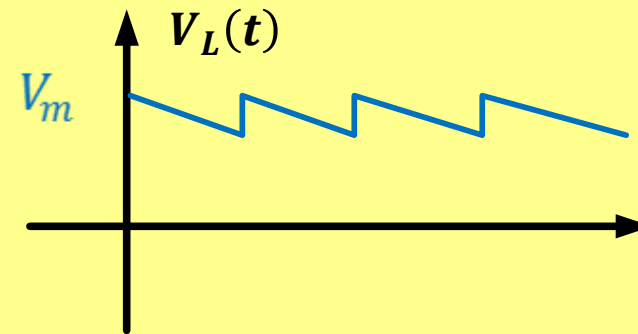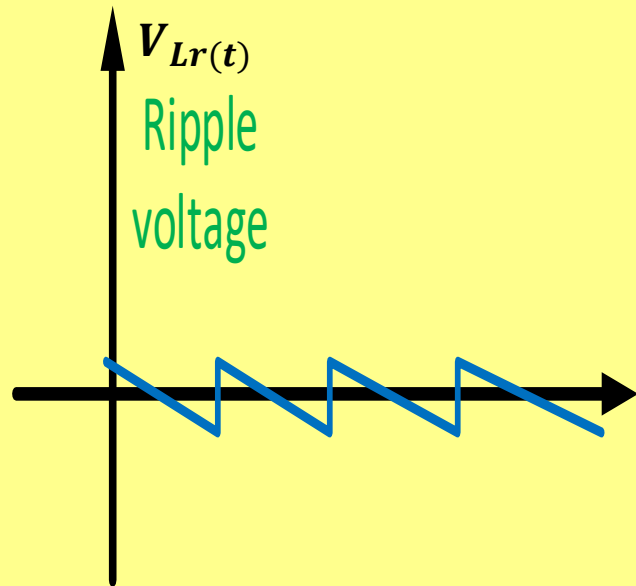

Example

$$\blacktriangleright V_{L,dc} = V_{L,av} = \frac{1}{T} \int_0^T V_L(t) dt$$

$$V_{L,dc} = \frac{1}{T} \cdot \text{area}$$

$$= \frac{1}{T} \left(8T + \frac{2 \cdot T}{2} \right)$$

$$V_{L,dc} = 9 V$$


OR

$$\blacktriangleright V_{L,dc} = V_m - \frac{1}{2} V_{Lr,p-p}$$

$$\text{where } V_m = 10 V$$

$$V_{Lr,p-p} = 2 V \text{ p-p}$$
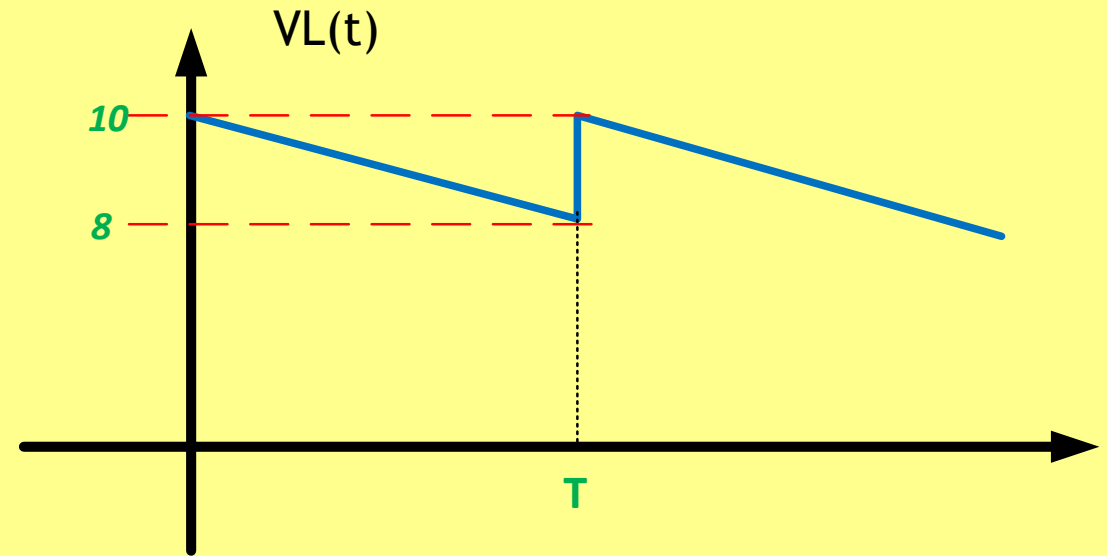
$$\therefore V_{L,dc} = 10 - \frac{1}{2} (2) = 9V$$



► Also for a triangle signal, the *RMS value* = $\frac{\text{Peak Value}}{\sqrt{3}}$

$$\text{or } \textit{RMS value} = \frac{\text{Peak-to-peak Value}}{2\sqrt{3}}$$

$$= \frac{V_{Lr,p-p}}{2\sqrt{3}}$$

$$\therefore r = \frac{\frac{V_{Lr,p-p}}{2\sqrt{3}}}{V_m - \frac{1}{2}V_{Lr,p-p}} \times 100\%$$

∴ To determine the ripple factor we need to find $V_{Lr,p-p}$

Ripple Factor

► For $t_2 > t > t_1$

► $V_L(t) = V_m e^{-(t-t_1)/RC}$

► $V_{Lr,p-p} = V_L(t_1) - V_L(t_2)$


► $V_{Lr,p-p} = V_m - V_m e^{-(t_2-t_1)/RC}$

► $V_{Lr,p-p} = V_m (1 - e^{-(t_2-t_1)/RC})$

Using $e^{-x} \cong 1 - x$

► $V_{Lr,p-p} = \frac{V_m(t_2-t_1)}{RC}$

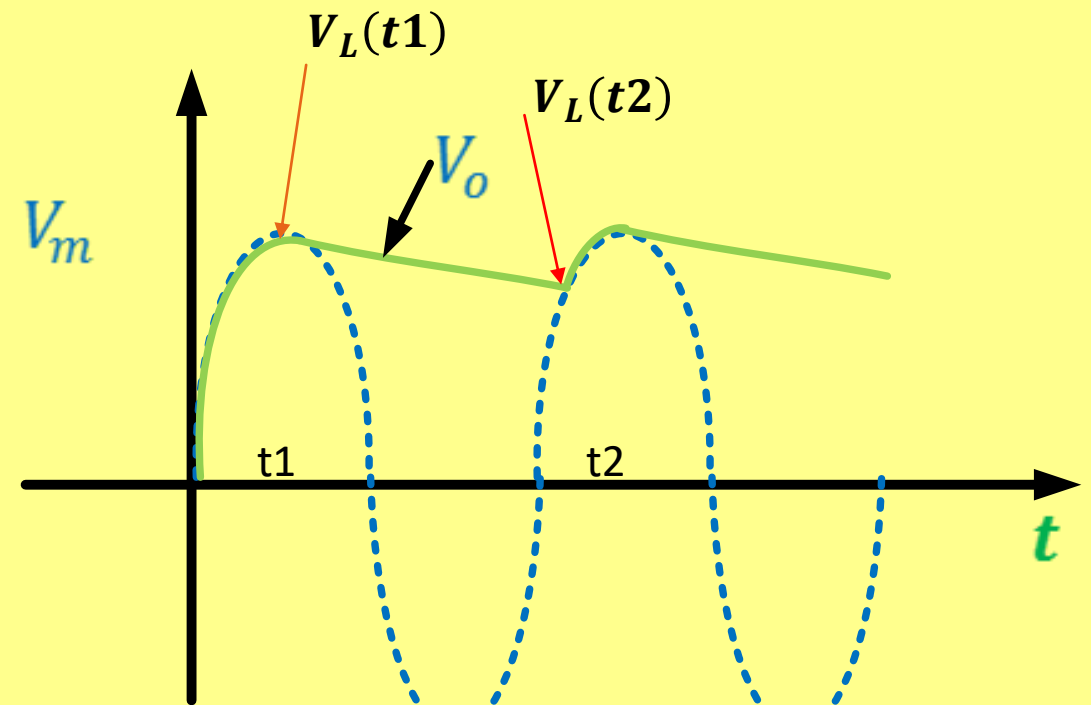► $V_{L,dc} = V_m - \frac{1}{2} V_{Lr,p-p}$



► For half-wave rectifier

► $t_2 - t_1 \approx T_o = \frac{1}{f_o}$

$$\therefore V_{Lr,p-p} = V_m \frac{1}{f_o RC}$$


► $V_{L,dc} = V_m \left(1 - \frac{1}{2f_o RC}\right)$

► $(V_{L,r})_{rms} = \frac{V_{Lr,p-p}}{2\sqrt{3}}$

$$(V_{L,r})_{rms} = \frac{V_m}{2\sqrt{3} f_o RC}$$

► $r = \frac{(V_{L,r})_{rms}}{V_{L,dc}} \times 100\%$
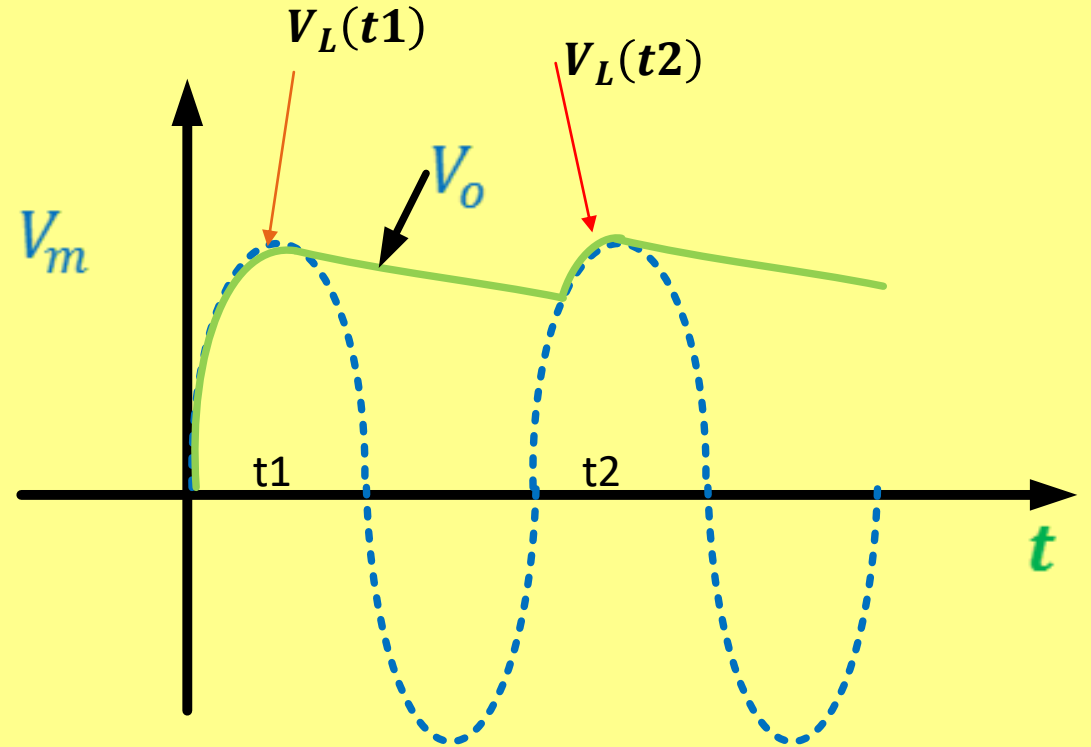
$$r = \frac{1}{\sqrt{3} (2f_o RC - 1)} \times 100\%$$




► For full-wave rectifier

► $t_2 - t_1 \approx \frac{1}{2} T_o = \frac{1}{2f_o}$

$$\therefore V_{Lr,p-p} = V_m \frac{1}{2f_o RC}$$

► $V_{L,dc} = V_m \left(1 - \frac{1}{4f_o RC} \right)$
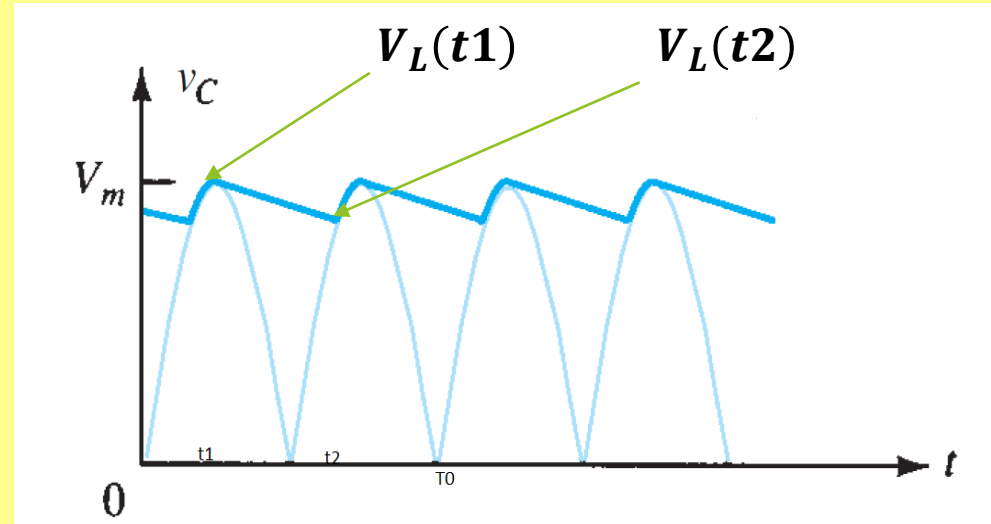
$$(V_{L,r})_{rms} = \frac{V_m}{4\sqrt{3} f_o RC}$$



$$r = \frac{1}{\sqrt{3} (4f_o RC - 1)} \times 100\%$$

Example

- Find the ripple factor r

$$V_m = 30\sqrt{2} = 42.43 \text{ V}$$

- $V_{L,dc} = V_m - \frac{V_m}{4f_o R_L C} = 41.54 \text{ V}$

- $V_{Lr,p-p} = \frac{V_m}{2f_o R_L C} = 1.7677 \text{ V}$

- RMS (ripple voltage) = $\frac{V_{Lr,p-p}}{2\sqrt{3}} = 0.51 \text{ V rms}$

$$\therefore r = \frac{0.51}{41.54} \times 100\%$$

$$r = 1.2277 \%$$

