
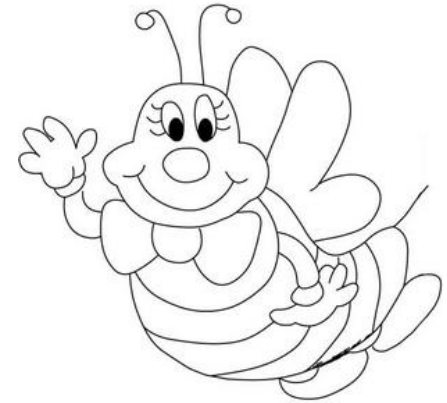


Multistage Amplifiers

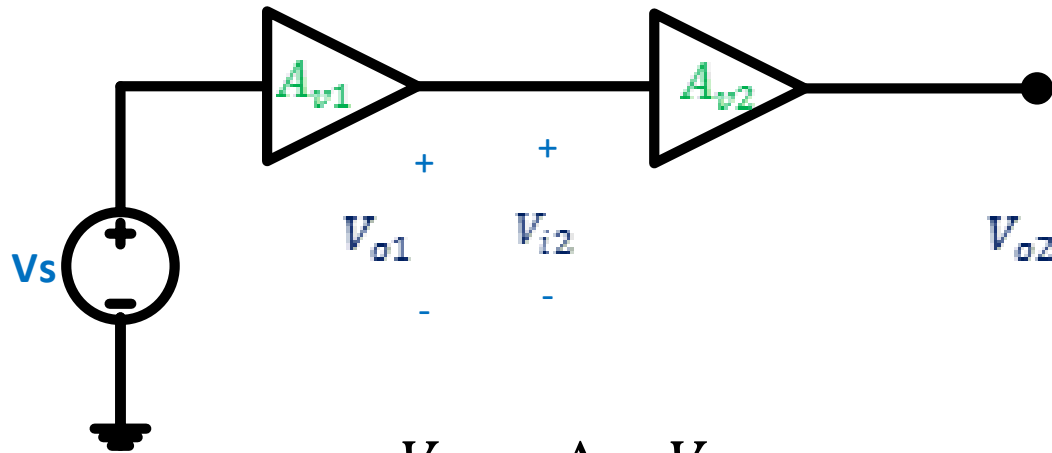

- 1) Additional Amplification can be required .
- 2) Improving the performance of the amplifier (**high input impedance ,high gain , small output impedance**) .
- 3) Increasing the Bandwidth .

Multistage Amplifiers



$$V_{O2} = A_{v2} V_{i2}$$


$$V_{i2} = V_{O1}$$

$$V_{O1} = A_{v1} V_s$$

$$\frac{V_{O2}}{V_s} = A_{v1} \cdot A_{v2}$$



Multistage Amplifiers

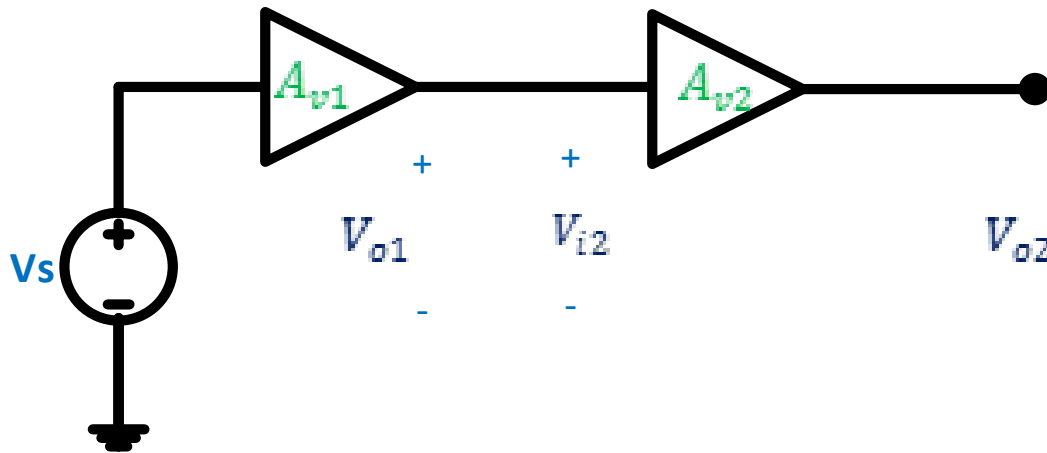

- ❖ When the output of one amplifier stage is connected to the input of another, the amplifier stages are said to be in **cascade**.
- ❖ $A_{v_T} = A_{v_1} \cdot A_{v_2} \cdot A_{v_3} \dots \dots \dots A_{v_n}$
 A_{v_1} , A_{v_2} , and A_{v_n} are the in-circuit gains.

Multistage Amplifiers

Methods of Coupling:


- **Capacitor Coupling.**
- **Direct Coupling.**
- **Transformer Coupling.**



Capacitor Coupled Multistage Amplifier

Advantages:

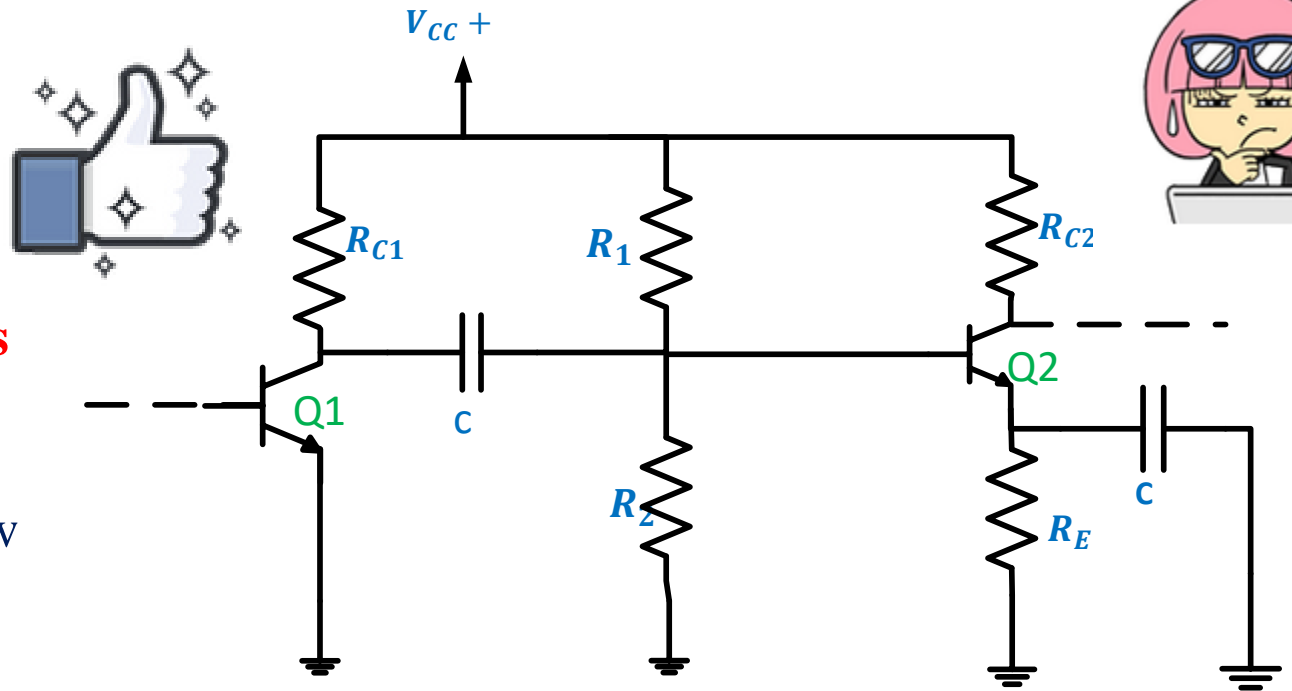
- ❖ the coupling capacitor **blocks** the flow of **DC** current while it **permits** the flow of **Ac** signal between stages .



- ❖ It makes it possible to have a dc bias voltage at the output of one stage that is different from the dc bias voltage at the input to the next stage (**stage isolation**)


Capacitor Coupled Multistage Amplifier

Disadvantages:

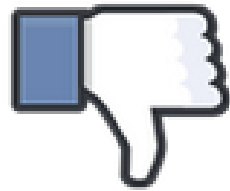


❖ It affects the low – frequency response of the amplifier .

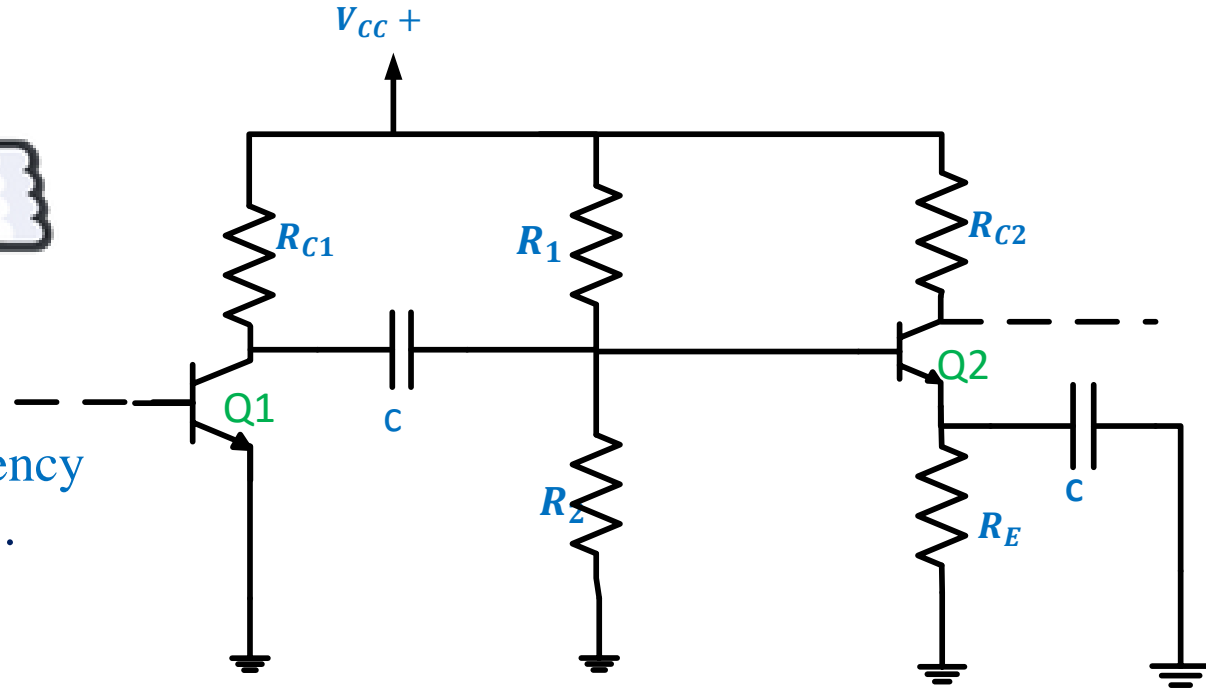❖ It **not** used in integrated circuit , **because** it is difficult and uneconomical to fabricate capacitors on a chip .



Capacitor Coupled Multistage Amplifier

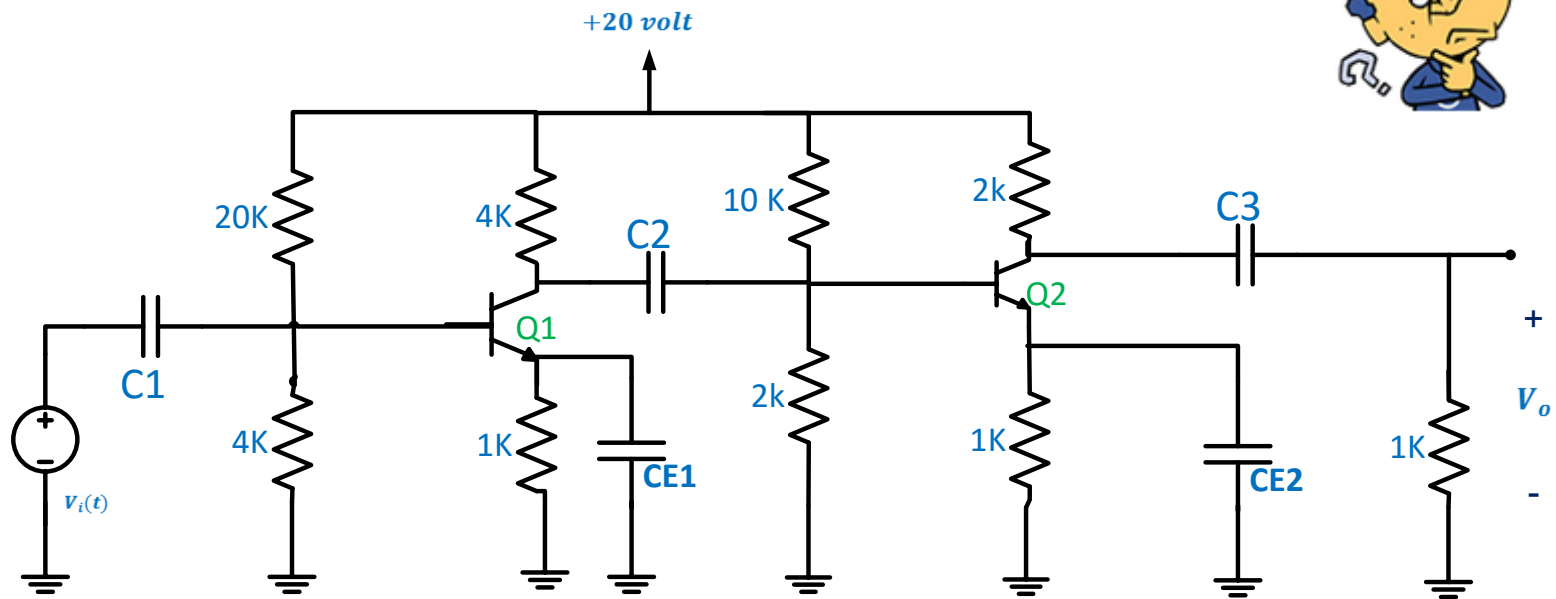Example: find the gain of the multistage amplifier




$$\beta_1 = \beta_2 = 50$$

Capacitor Coupled Multistage Amplifier

Solution:



DC Analysis:

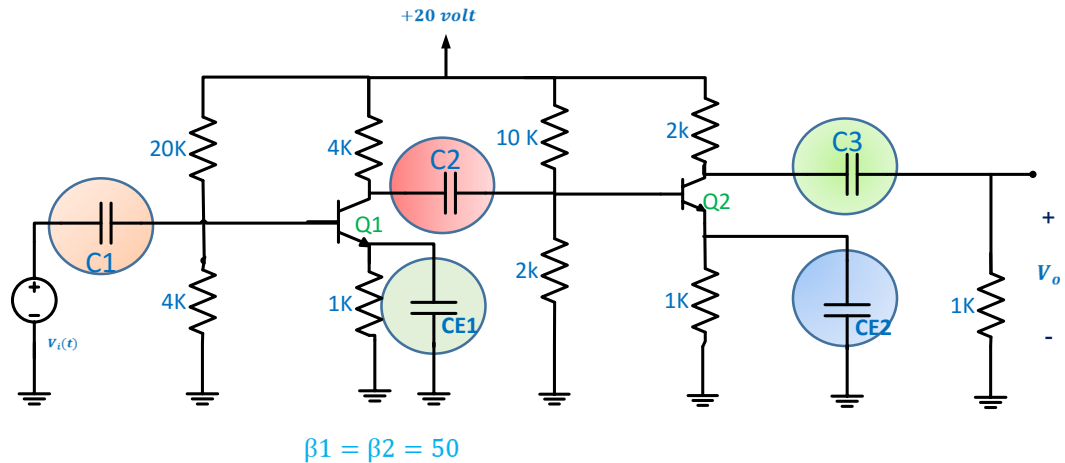

$$R_{TH1} = 4K \parallel 20K = 3.33K$$

$$V_{TH1} = \frac{4K}{4K+20K} (20) = 3.33v$$




Open Circuit!

$$I_{E1} = 2.47 \text{ mA} \quad \therefore h_{ie1} = 0.51K$$

$$R_{TH2} = 2K \parallel 10K = 1.67 K$$


$$V_{TH2} = \frac{2K}{2K+10K} (20) = 3.33v$$
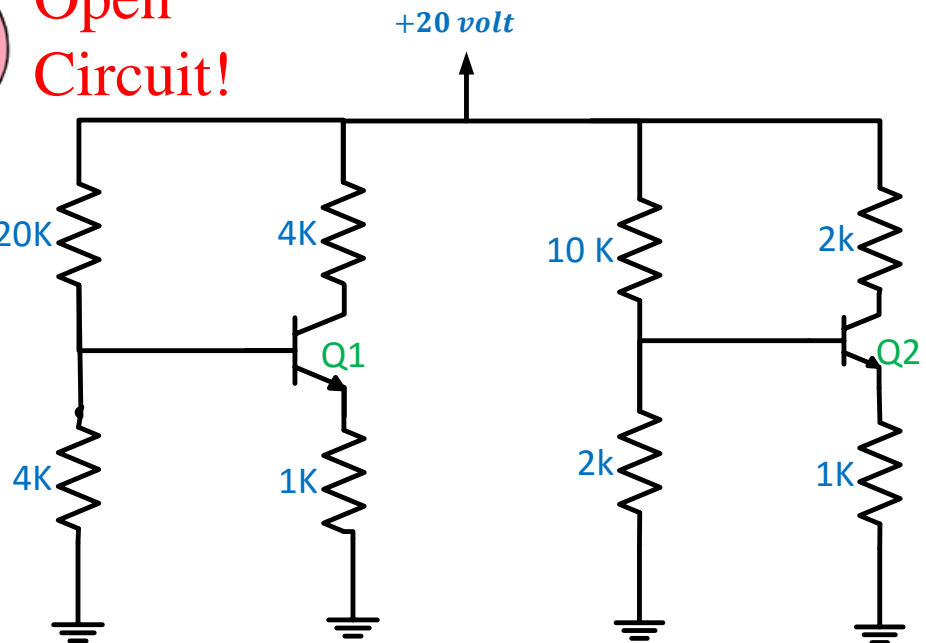
$$I_{E2} = 2.55 \text{ mA} \quad \therefore h_{ie2} \approx 0.51K$$



Capacitor Coupled Multistage Amplifier

Ac small signal equivalent circuit

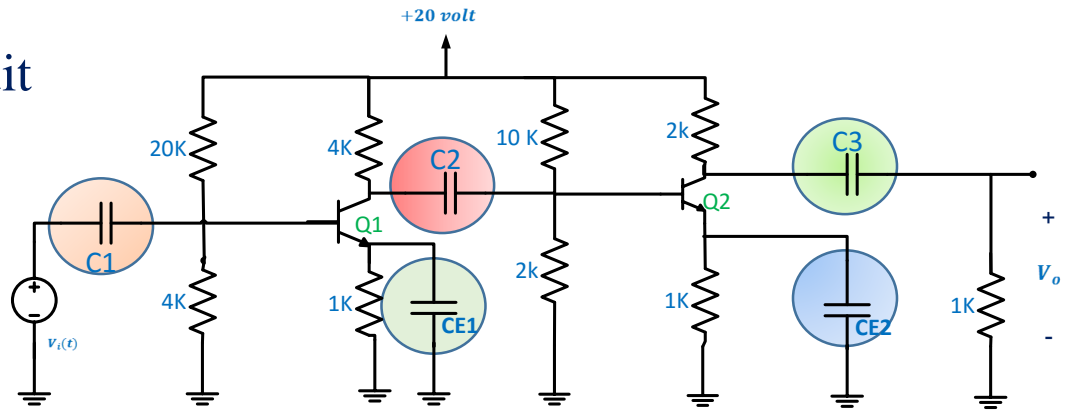


$$\beta_1 = \beta_2 = 50$$




Short
Circuit

Capacitor Coupled Multistage Amplifier

Ac small signal equivalent circuit

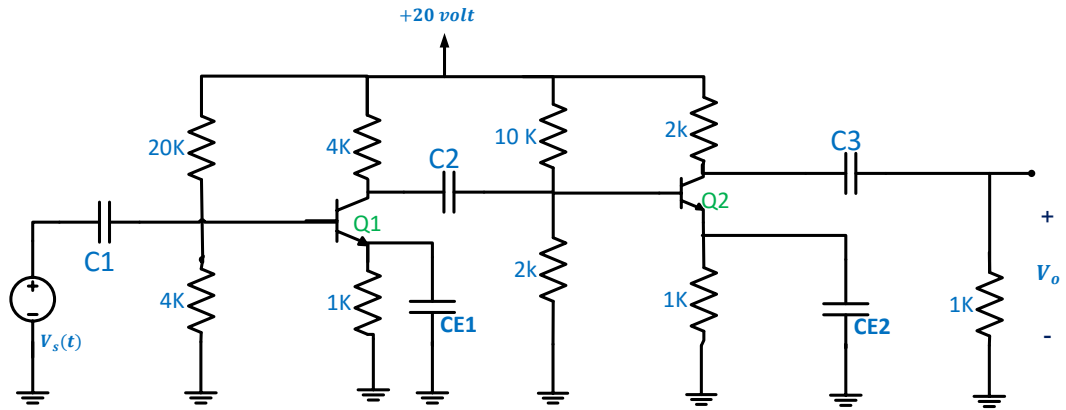


$$\beta_1 = \beta_2 = 50$$

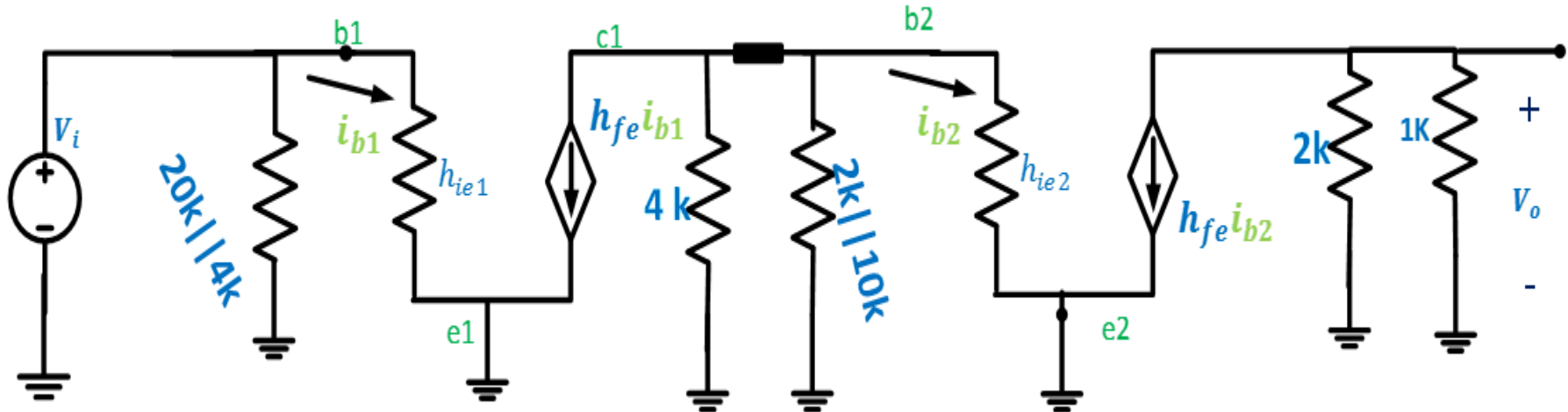

Capacitor Coupled Multistage Amplifier

$$Av_T = Av_1 \cdot Av_2$$

- $$Av_1 = \frac{V_{O1}}{V_i}$$

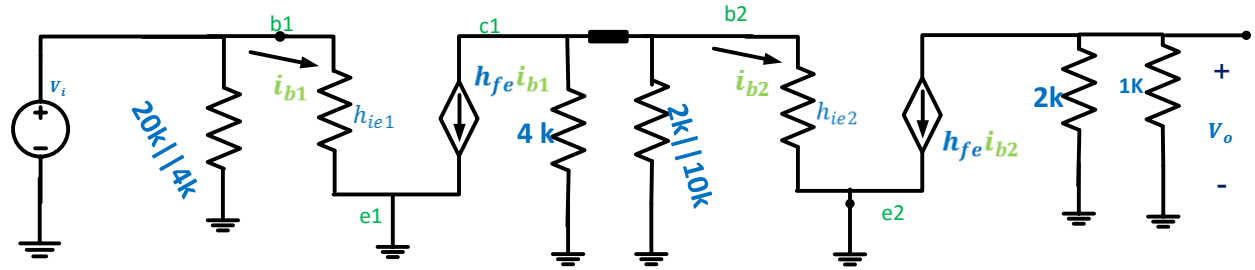

$$V_{O1} = -h_{fe1} i_{b1} (4k || 2k || 10k || h_{ie2})$$

$$i_{b1} = \frac{V_i}{h_{ie1}}$$

- $$Av_1 = -34.14$$

- $$Av_2 = \frac{V_{O2}}{V_{i2}} = \frac{V_o}{V_{i2}}$$

$$V_{O2} = -h_{fe2} i_{b2} (1k || 2k)$$

$$i_{b2} = \frac{V_{i2}}{h_{ie2}}$$

- $$Av_2 = -66.66$$

$$Av_T = Av_1 \cdot Av_2$$

- $$\diamond Av_T = 2342$$