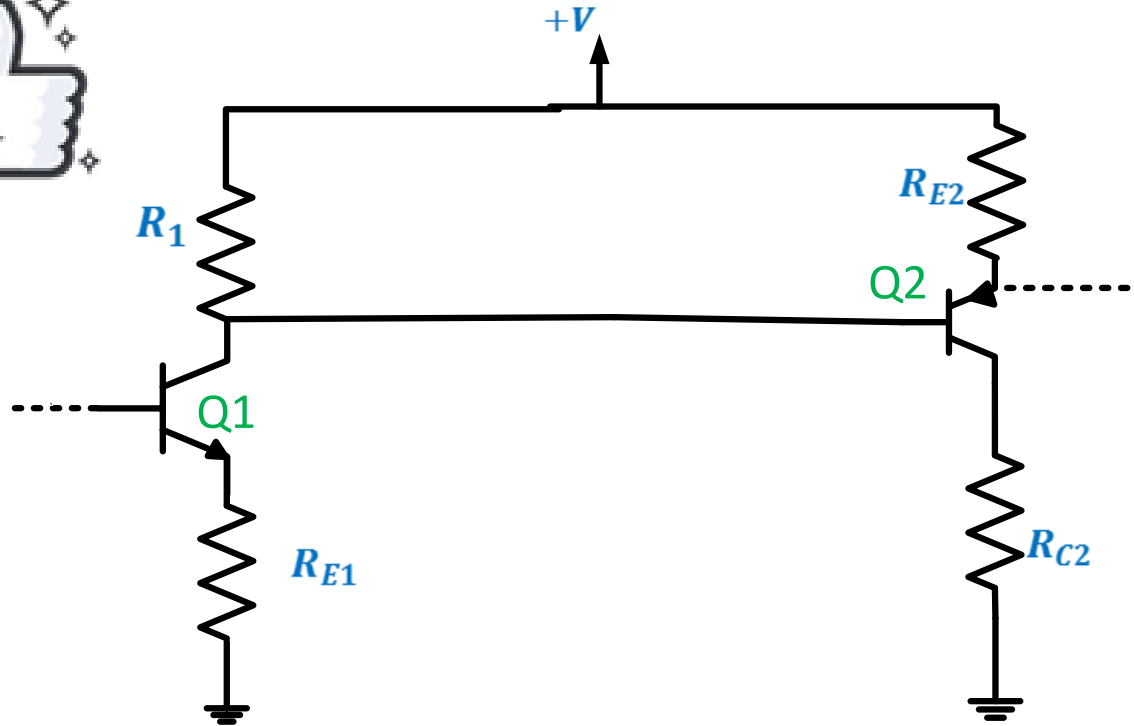


2) Direct – coupled multistage Amplifier

Advantages



- ❖ Used in differential and operational amplifier .
- ❖ Used in low and high frequency applications .



Darlington compound configuration

DC Analysis :




$$V_{CC} = R_B I_{B1} + V_{BE1} + V_{BE2} + R_E I_{E2}$$

$$I_{E2} = (\beta_2 + 1) I_{B2}$$

$$I_{B2} = I_{E1}$$



$$I_{E1} = (\beta_1 + 1) I_{B1}$$
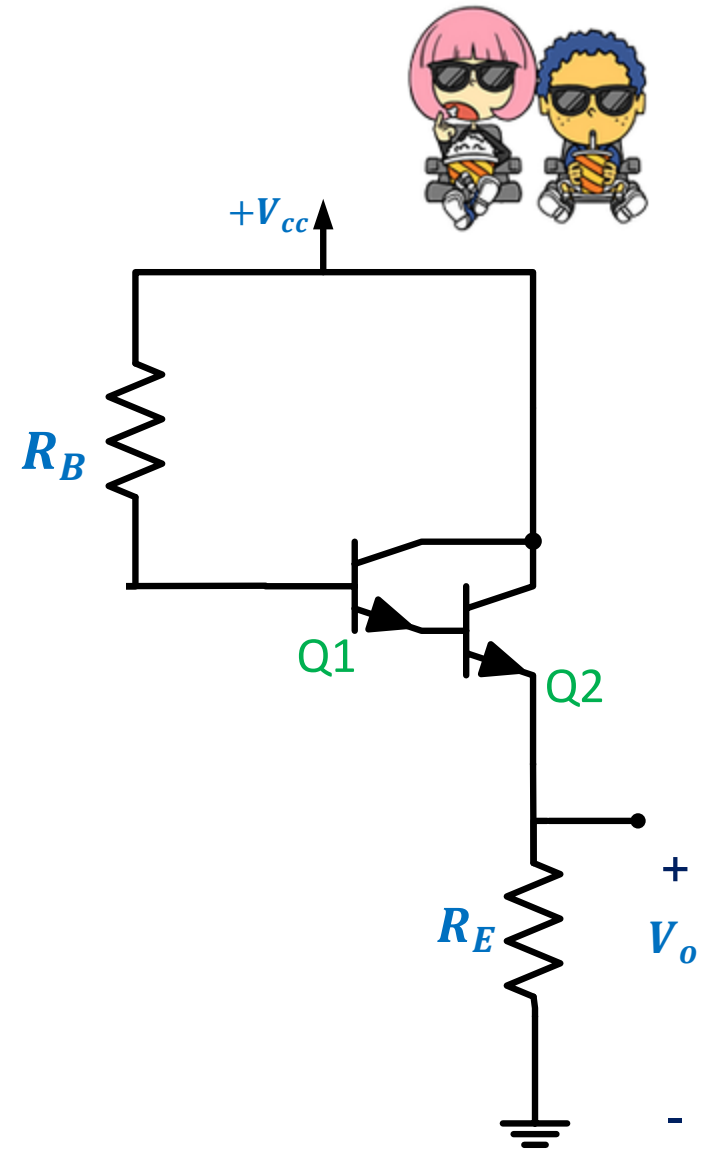
$$\therefore I_{E2} = (\beta_2 + 1) (\beta_1 + 1) I_{B1}$$



Darlington compound configuration

Ac small signal equivalent circuit

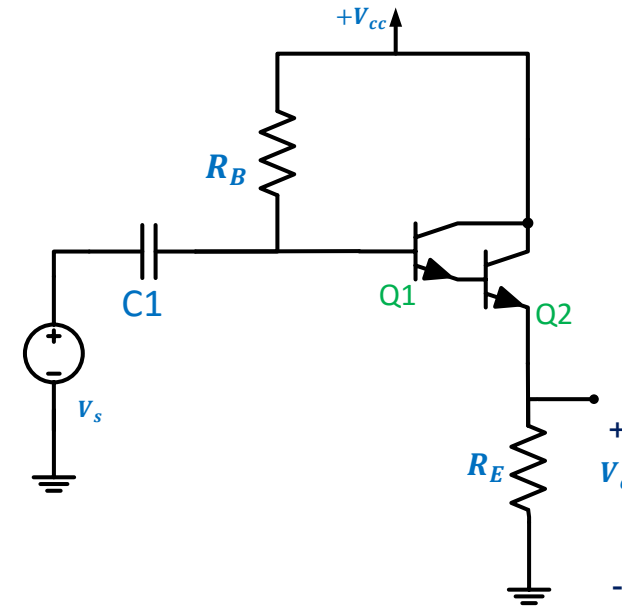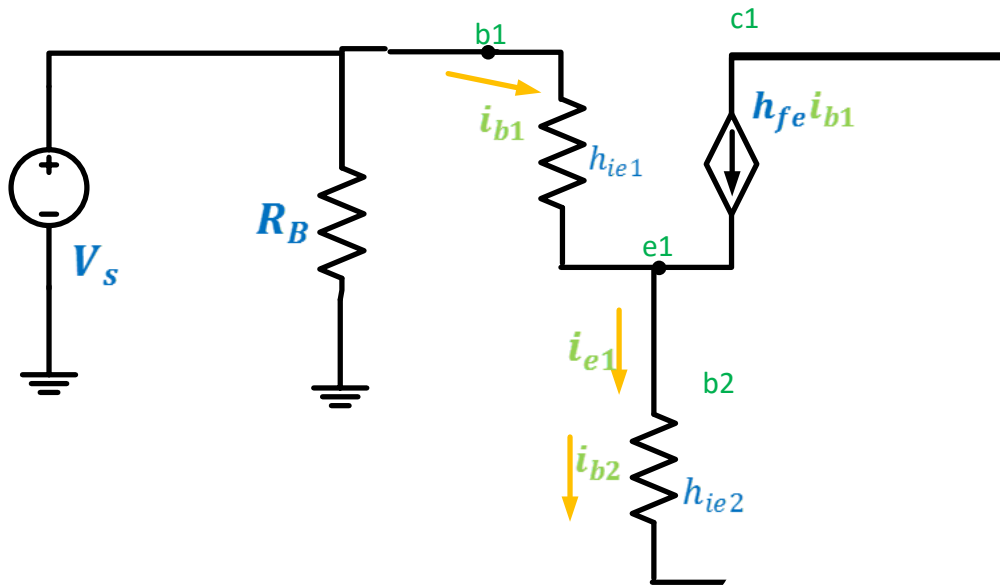

Darlington compound configuration

$$A_i = \frac{i_o}{i_{b1}} = \frac{i_{e2}}{i_{b1}}$$

$$i_{e2} = (1 + h_{fe2}) i_{b2}$$

$$i_{b2} = i_{e1}$$


$$i_{e1} = (1 + h_{fe1}) i_{b1}$$

$$A_i = \frac{i_o}{i_{b1}} = (1 + h_{fe2}) (1 + h_{fe1})$$

$$A_v = \frac{V_o}{V_s}$$





$$V_o = R_E i_o$$
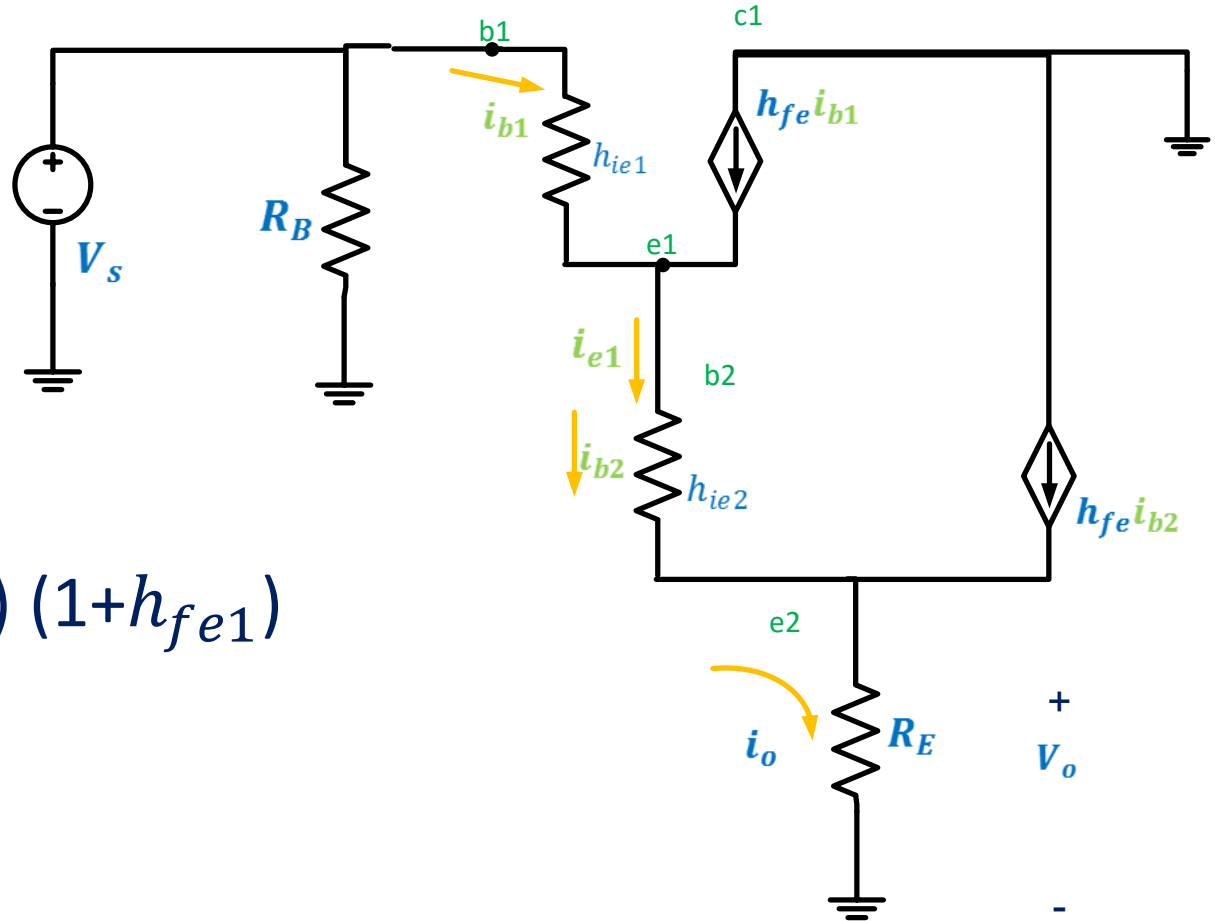
$$i_o = (1 + h_{fe2}) (1 + h_{fe1}) i_{b1}$$




Darlington compound configuration

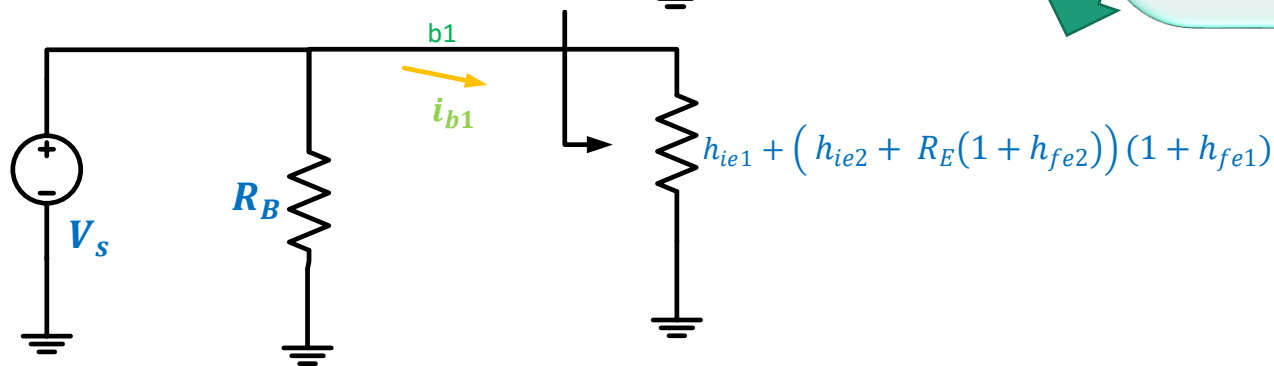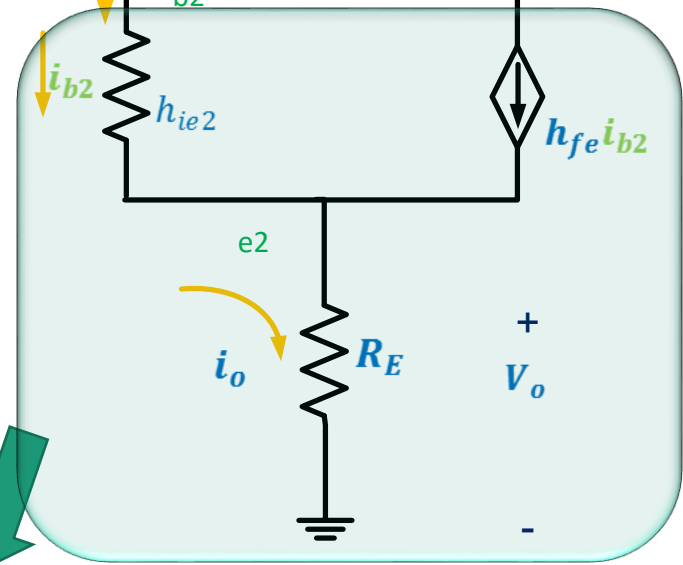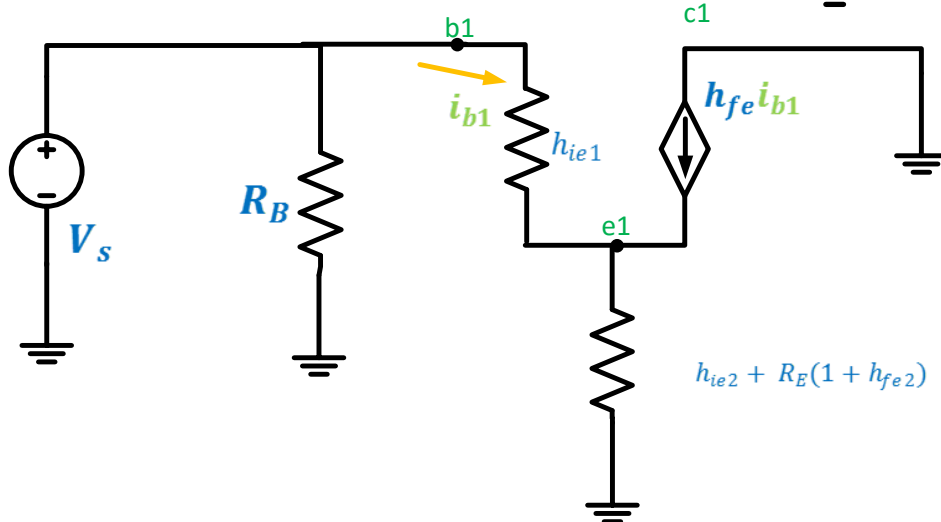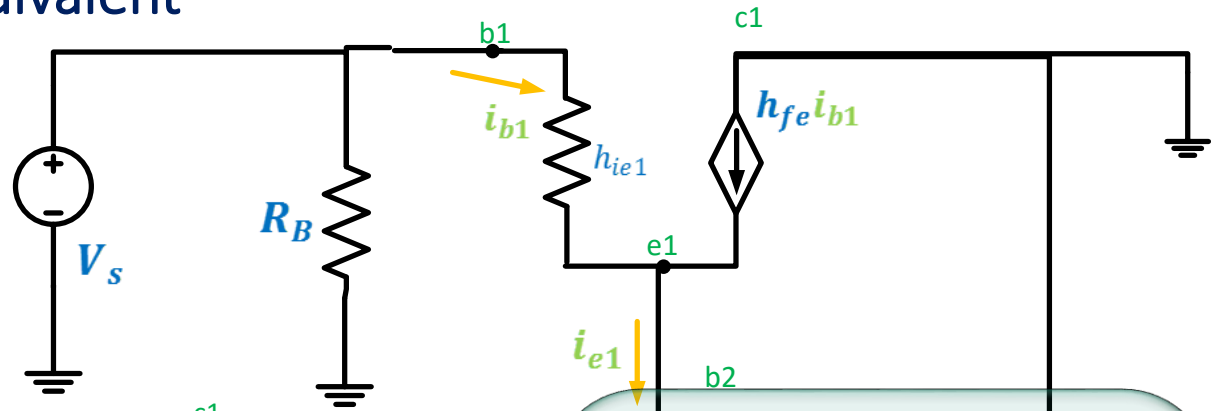To find $i_{b1} \rightarrow$ base equivalent




Darlington compound configuration

$$i_{b1} = \frac{V_S}{Z_i}$$

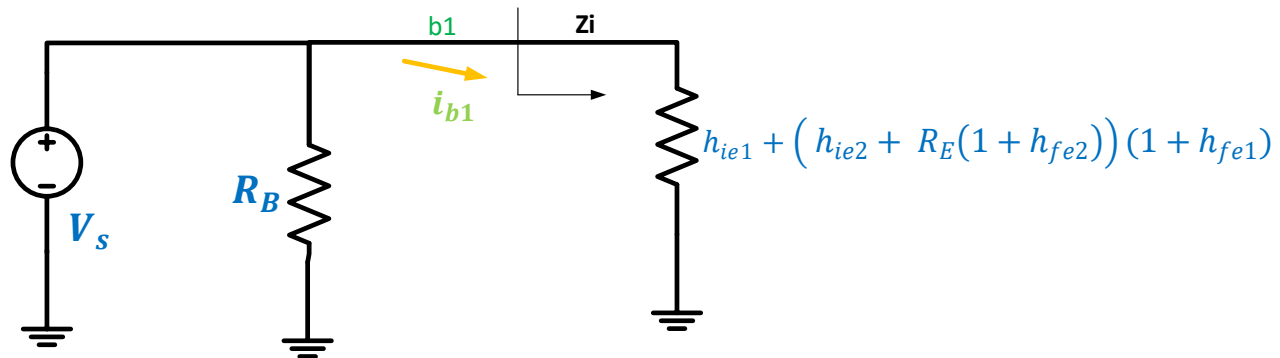
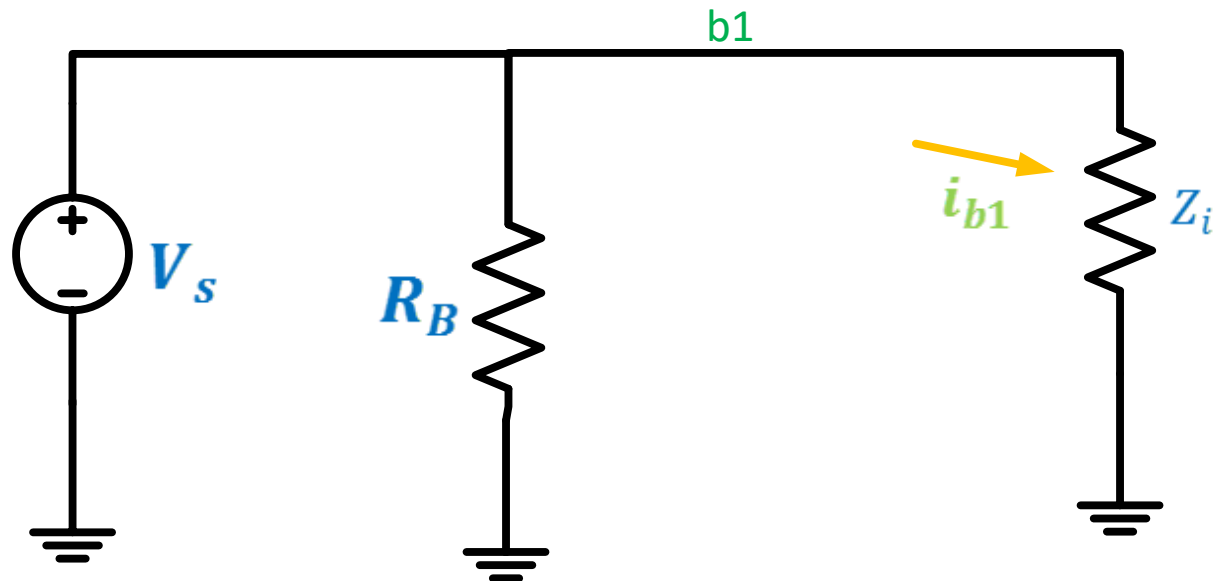
$$Z_i = h_{ie1} + (h_{ie2} + R_E(1 + h_{fe2}))(1 + h_{fe1})$$




Darlington compound configuration

$$A_v = \frac{R_E(1+h_{fe2})(1+h_{fe1})}{h_{ie1}+(R_E(1+h_{fe2})+h_{ie2})(1+h_{fe1})} < 1$$

To find Z_O , set $V_S = 0$

$$Z_O = \left(\frac{\frac{h_{ie1}}{1+h_{fe1}} + h_{ie2}}{1+h_{fe2}} \right) || R_E$$

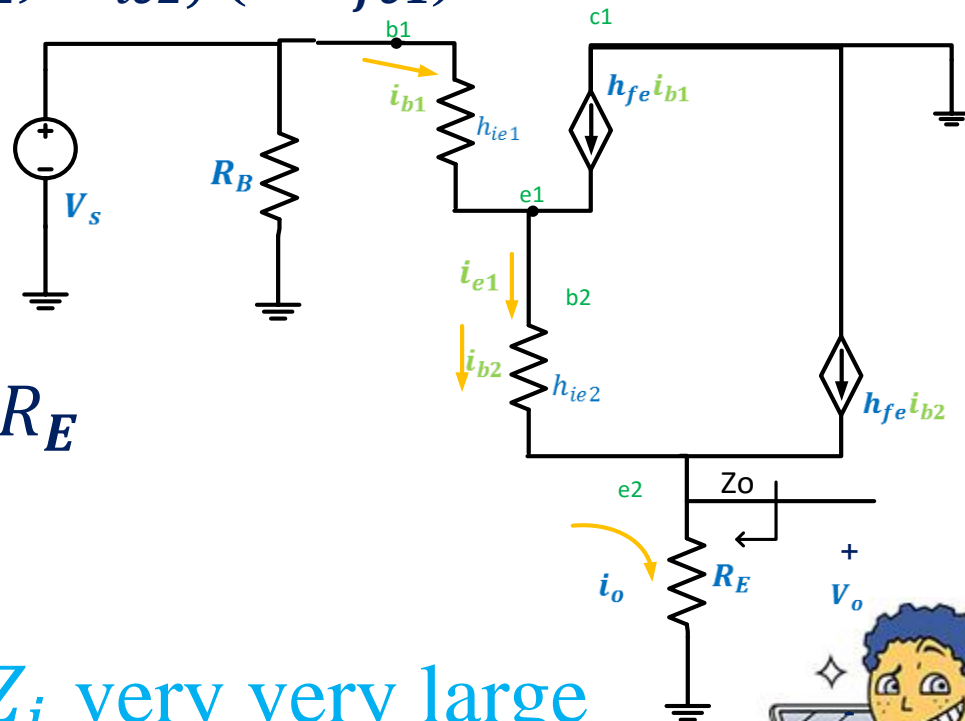

$$\therefore A_i > 1$$

$$A_v < 1$$

Z_i very very large


Z_O very very small

modified buffer




Darlington compound configuration

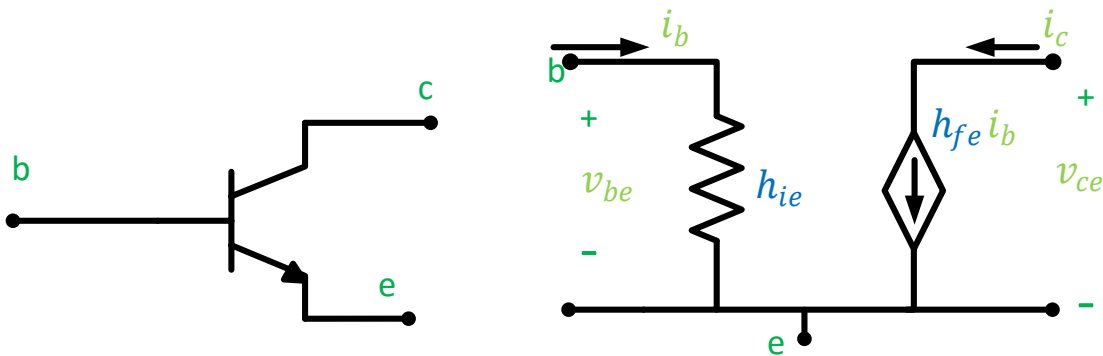
Ac small signal equivalent circuit of the BJT



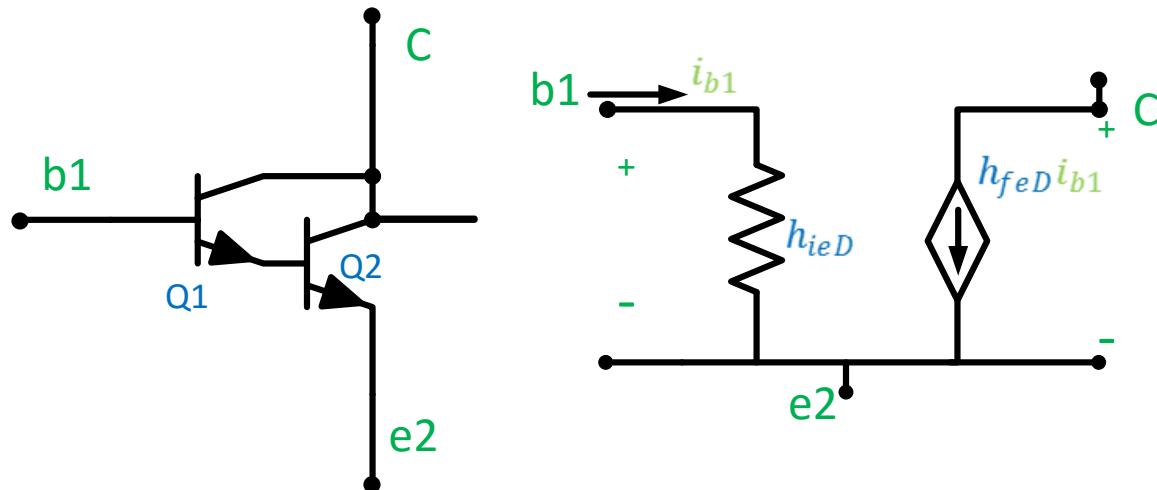Ac small signal equivalent circuit of the Darlington



Darlington compound configuration

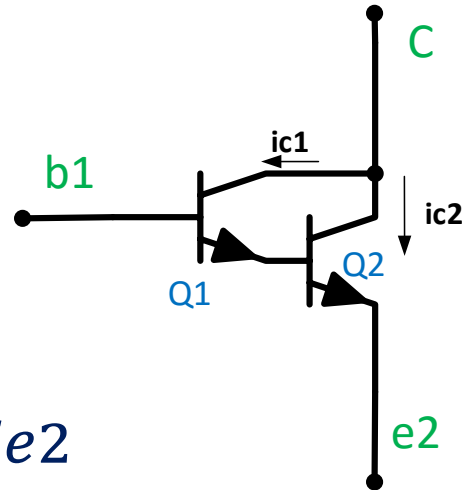


$$h_{ieD} = 2 h_{ie1}$$

$$h_{feD} = h_{fe1} \cdot h_{fe2}$$

$$h_{feD} = \frac{i_c}{i_{b1}}$$

$$h_{ieD} = Z_i \text{ with } R_E = 0$$

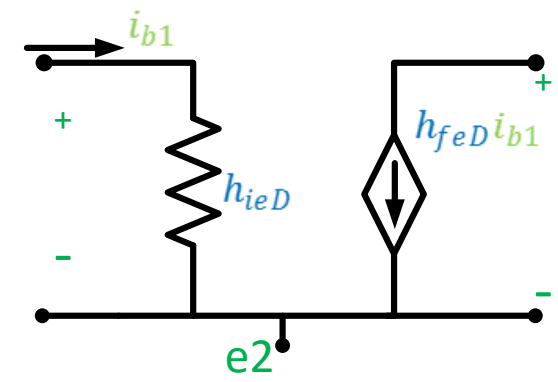

Darlington compound configuration

$$h_{feD} = \frac{i_c}{i_{b1}}$$

$$i_c = i_{c1} + i_{c2}$$

$$i_c = h_{fe1} i_{b1} + h_{fe2} i_{b2}$$



$$i_c = h_{fe1} i_{b1} + h_{fe2} i_{e1}$$

$$i_c = h_{fe1} i_{b1} + h_{fe2} (1 + h_{fe1}) i_{b1}$$

$$i_c = (h_{fe1} + h_{fe2} + h_{fe2} h_{fe1}) i_{b1}$$

$$h_{feD} = h_{fe1} + h_{fe2} + h_{fe2} h_{fe1}$$

$$h_{feD} \approx h_{fe2} h_{fe1}$$

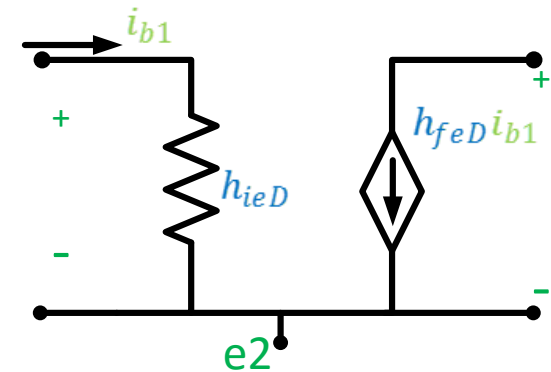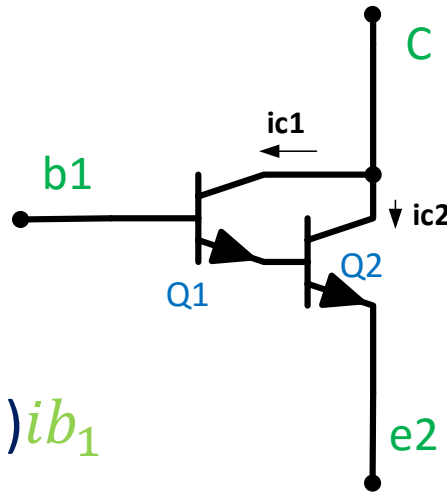

Darlington compound configuration

$$h_{ieD} = Z_i \Big|_{R_E=0}$$




- $Z_i = h_{ie1} + (R_E (1+h_{fe2})+h_{ie2})(1+h_{fe1})$

$$\therefore h_{ieD} = h_{ie1} + (1+h_{fe1}) h_{ie2}$$

$$= h_{ie1} + (1+h_{fe1}) \frac{(1+h_{fe2})V_T}{I_{E2}}$$

$$= h_{ie1} + (1+h_{fe1}) \frac{(1+h_{fe2})V_T}{(1+h_{fe2})I_{E1}}$$

Darlington compound configuration

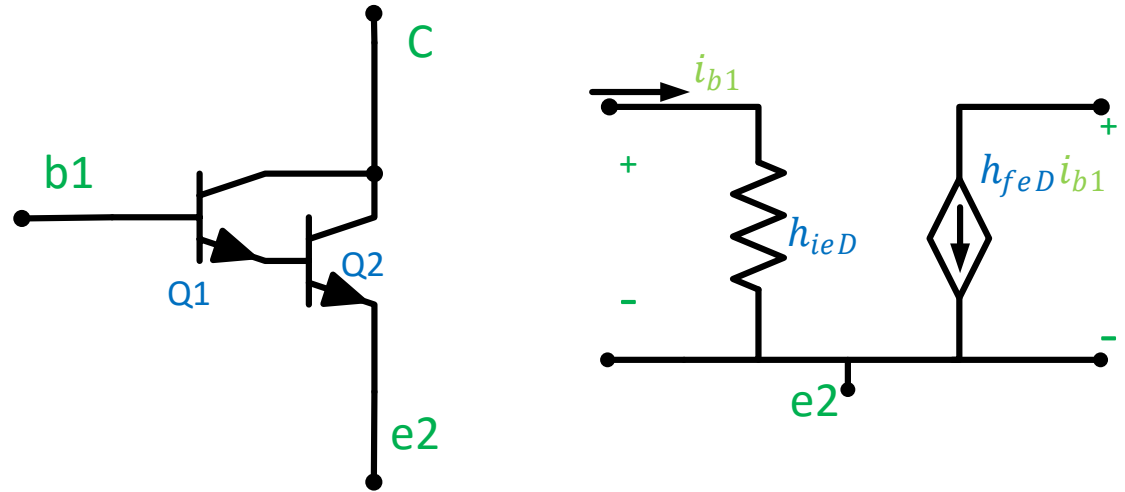


$$\begin{aligned}\therefore h_{ieD} &= h_{ie1} + \frac{(1+h_{fe1})V_T}{I_{E1}} \\ h_{ieD} &= h_{ie1} + h_{ie1} \\ &= 2h_{ie1}\end{aligned}$$





Cascode Amplifier

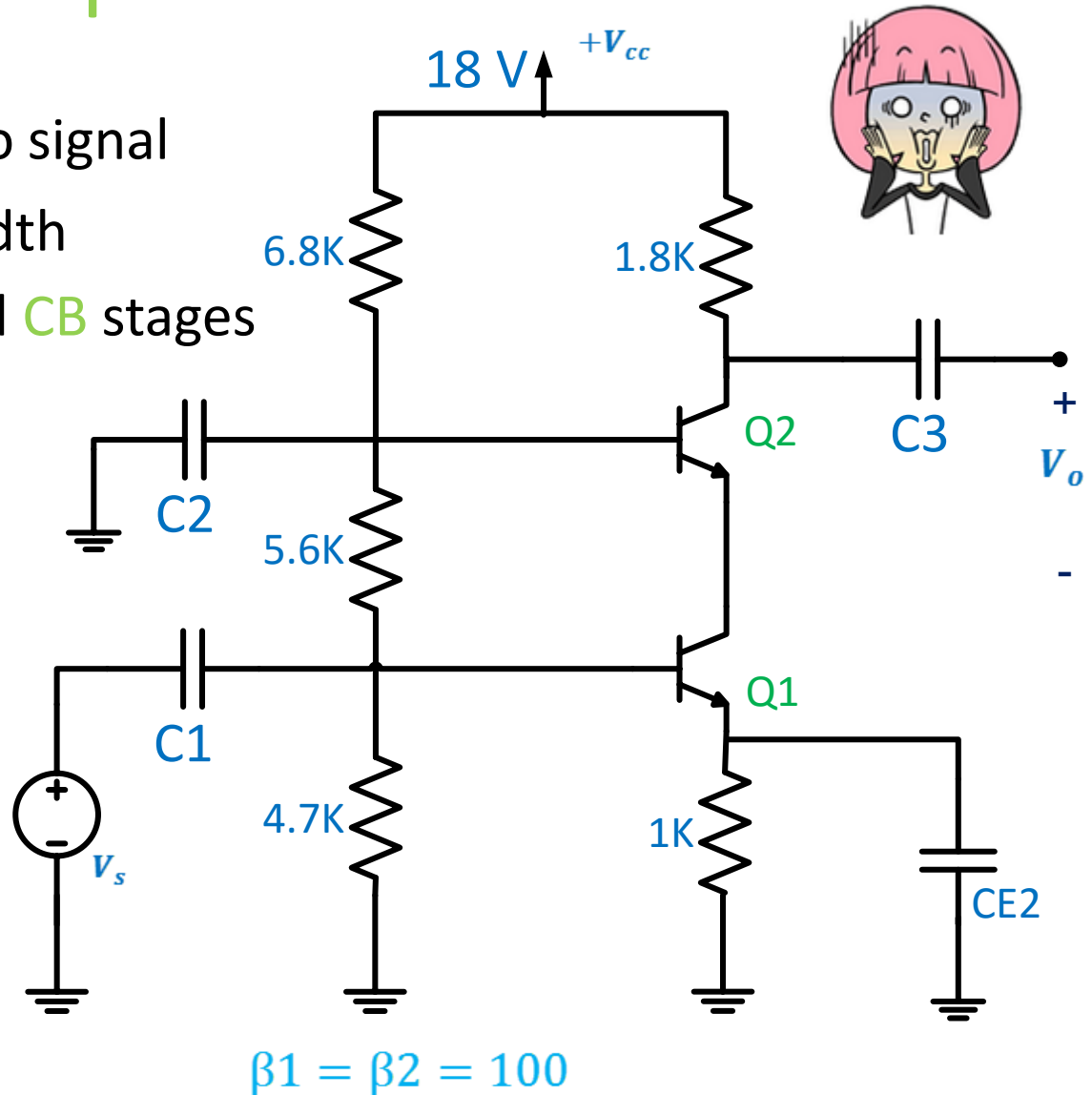- ◆ Used to amplify video signal
- ◆ It has a wide bandwidth
- ◆ It consists of a CE and CB stages or CS and CG stages .



Cascode Amplifier

DC Analysis :

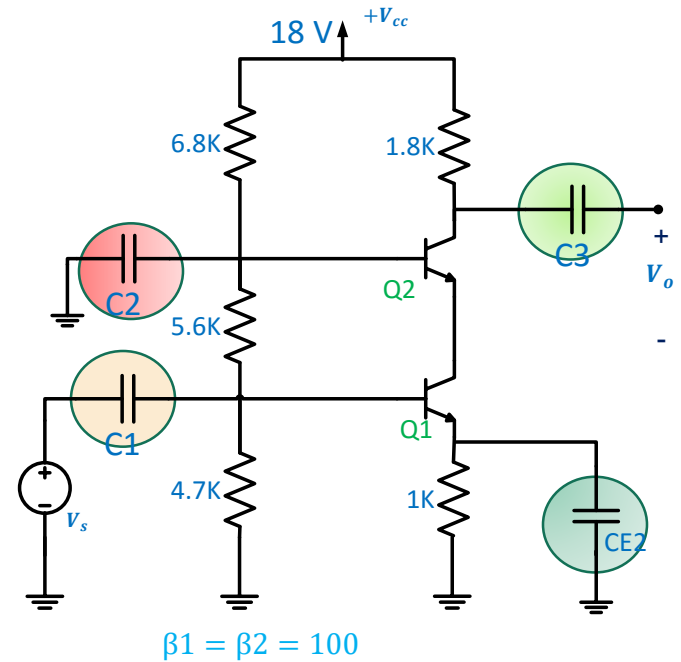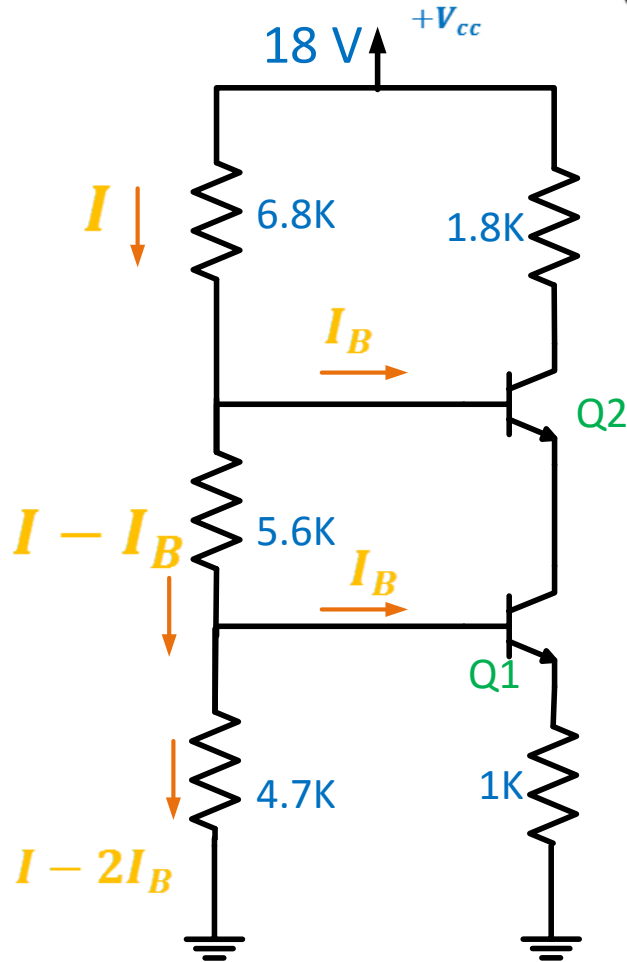

Open
Circuit!



$$I_{C1} = I_{E2} \approx I_{C2}$$

$$\text{Since } \beta_1 = \beta_2$$

$$I_{B1} = I_{B2} = I_B$$

Cascode Amplifier

DC Analysis :

$$I_{C1} = I_{E2} = I_{C2}$$


And since $\beta_1 = \beta_2$

$$I_{B1} = I_{B2} = I_B$$

$$18 = 6.8k I + 5.6k(I - I_B) + 4.7k(I - 2I_B)$$

$$18 = 6.8k I + 5.6k(I - I_B) + V_{BE1} + 1kI_{E1}$$

Solving for $I_E = 4mA$

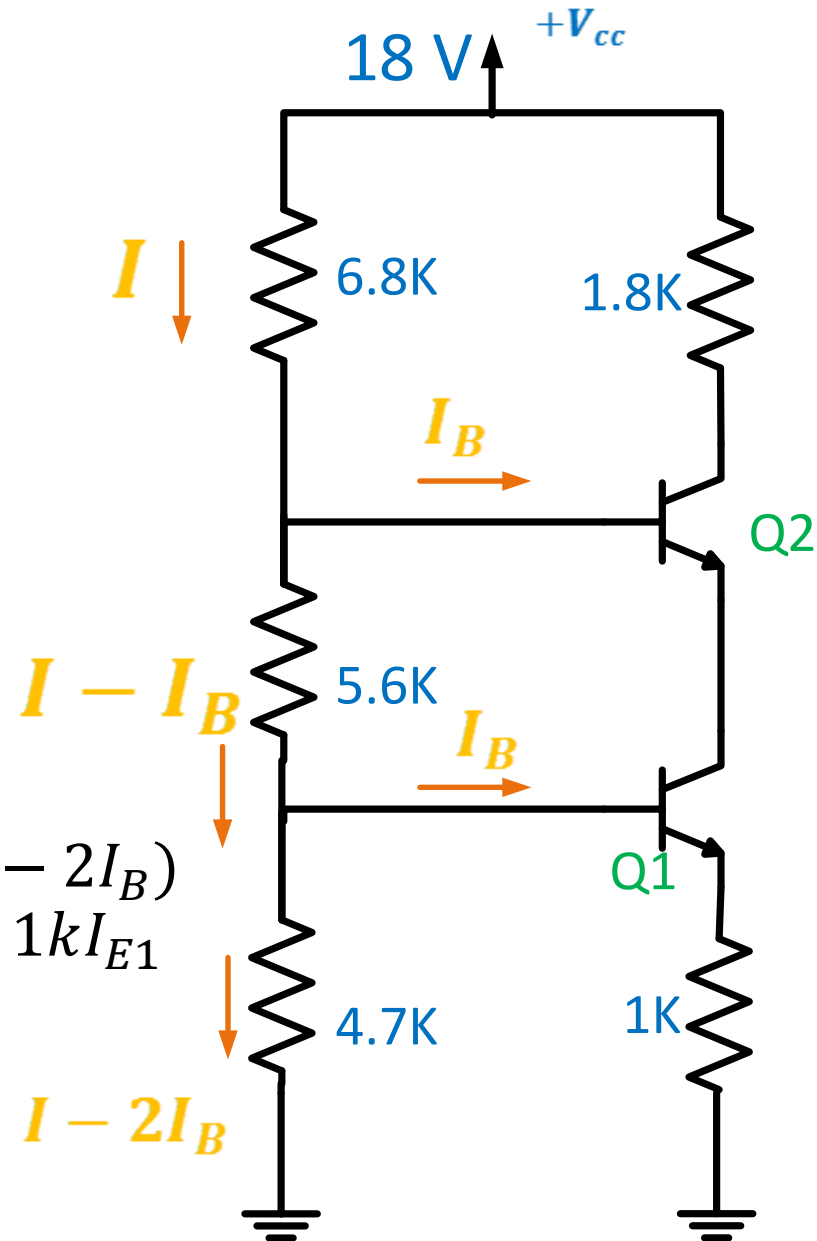

Cascode Amplifier



Ac small signal analysis

$$V_O = -h_{fb} i_{e2} (1.8K)$$

$$i_{e2} = h_{fe1} i_{b1}$$

$$i_{b1} = \frac{V_s}{h_{ie1}}$$

$$\therefore A_v = -294$$

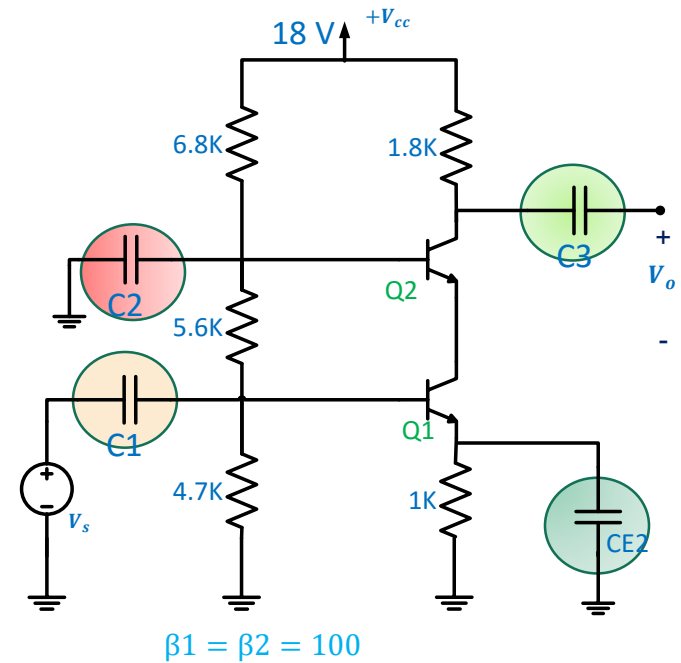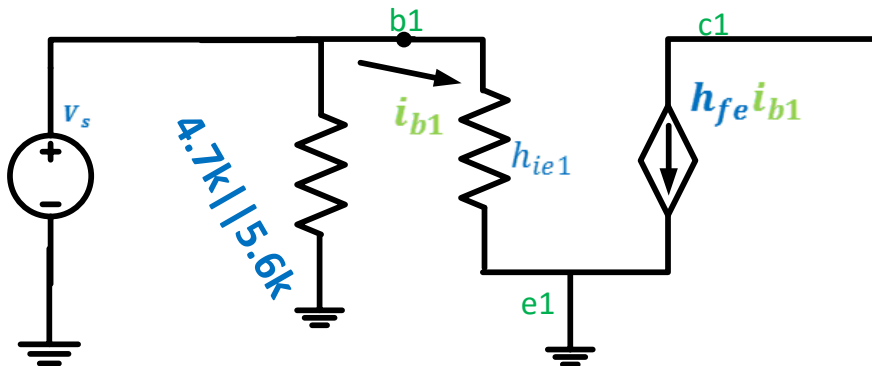

Short
Circuit!

