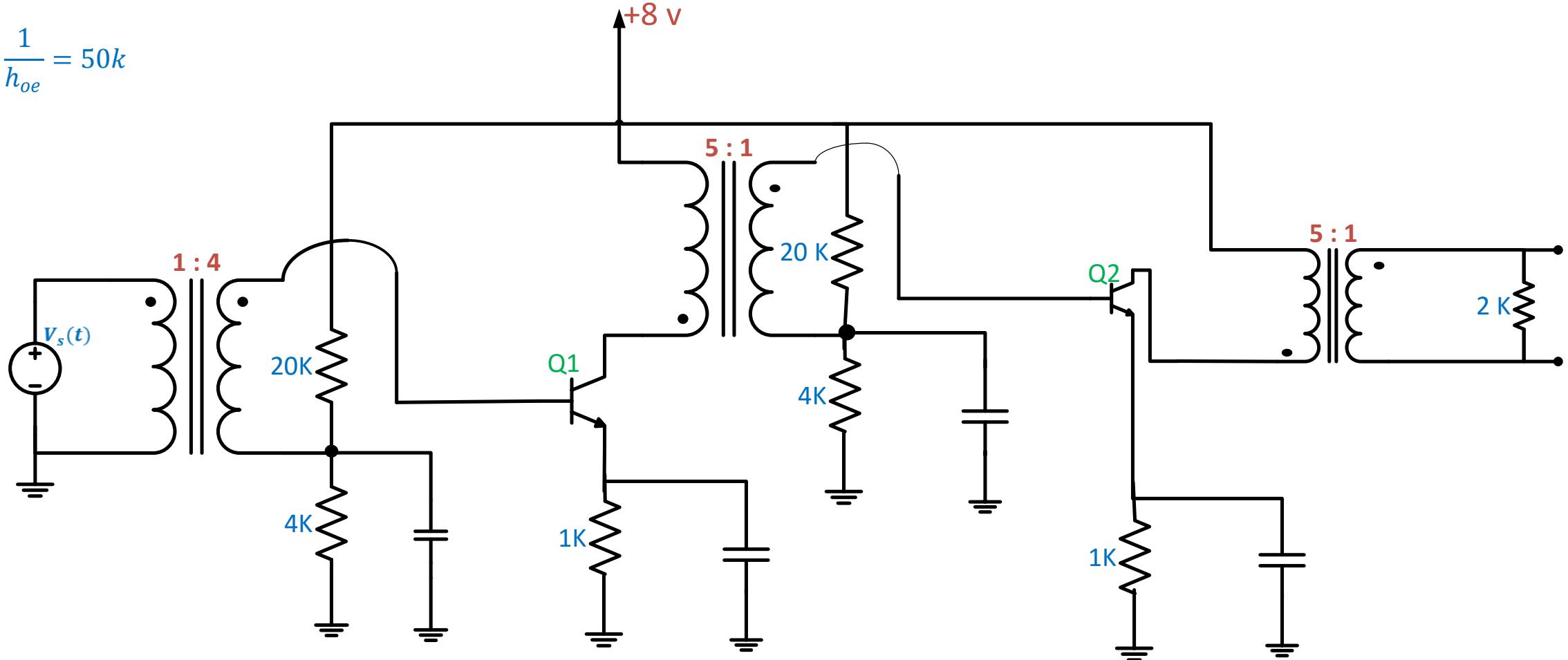


3) Transformer coupled multistage amplifier

$$h_{fe} = 50$$

$$\frac{1}{h_{oe}} = 50k$$



3) Transformer coupled multistage amplifier

Advantages:




1) The coupling transformer is used to pass the ac signal from one stage to the next , while blocking the DC voltages .

2) DC isolation .

3) matching for maximum power transfer .

4) low dc power dissipation ($R_C = 0$) .

Disadvantages

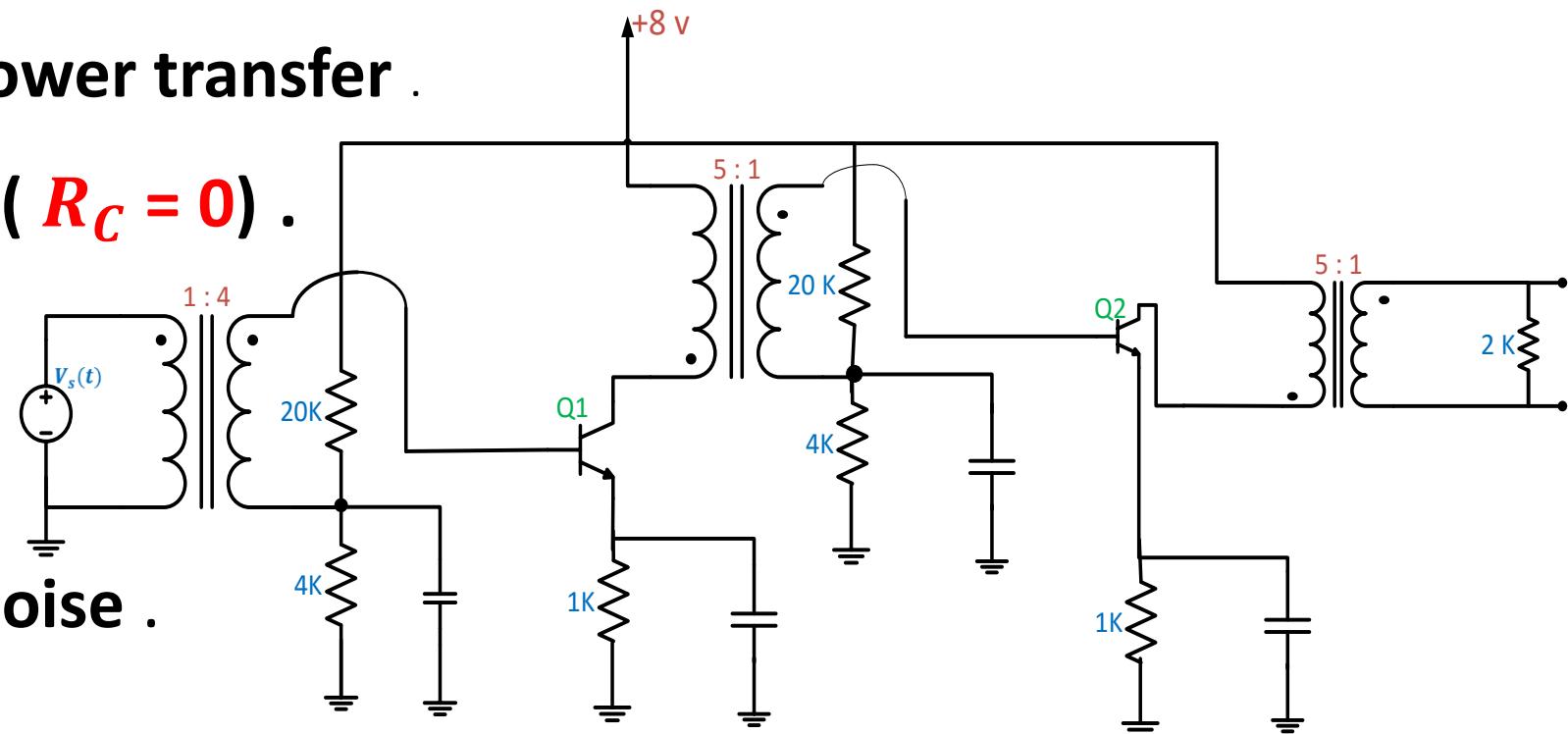

1) cost , weight , size , and noise .

2) poor frequency response .

3) Transformer coupled multistage amplifier


DC Analysis:

$$R_{TH1} = R_{TH2} = 4K \parallel 20K = 3.33K$$

$$V_{TH1} = V_{TH2} = \frac{4K}{4K+20K} (+8) = 1.33 V$$



$$I_{E1} = I_{E2} = \frac{4K}{\frac{R_{TH}}{\beta+1} + 1K} = 0.595 \text{ mA}$$

$$\therefore h_{ie1} = h_{ie2} = 2K$$

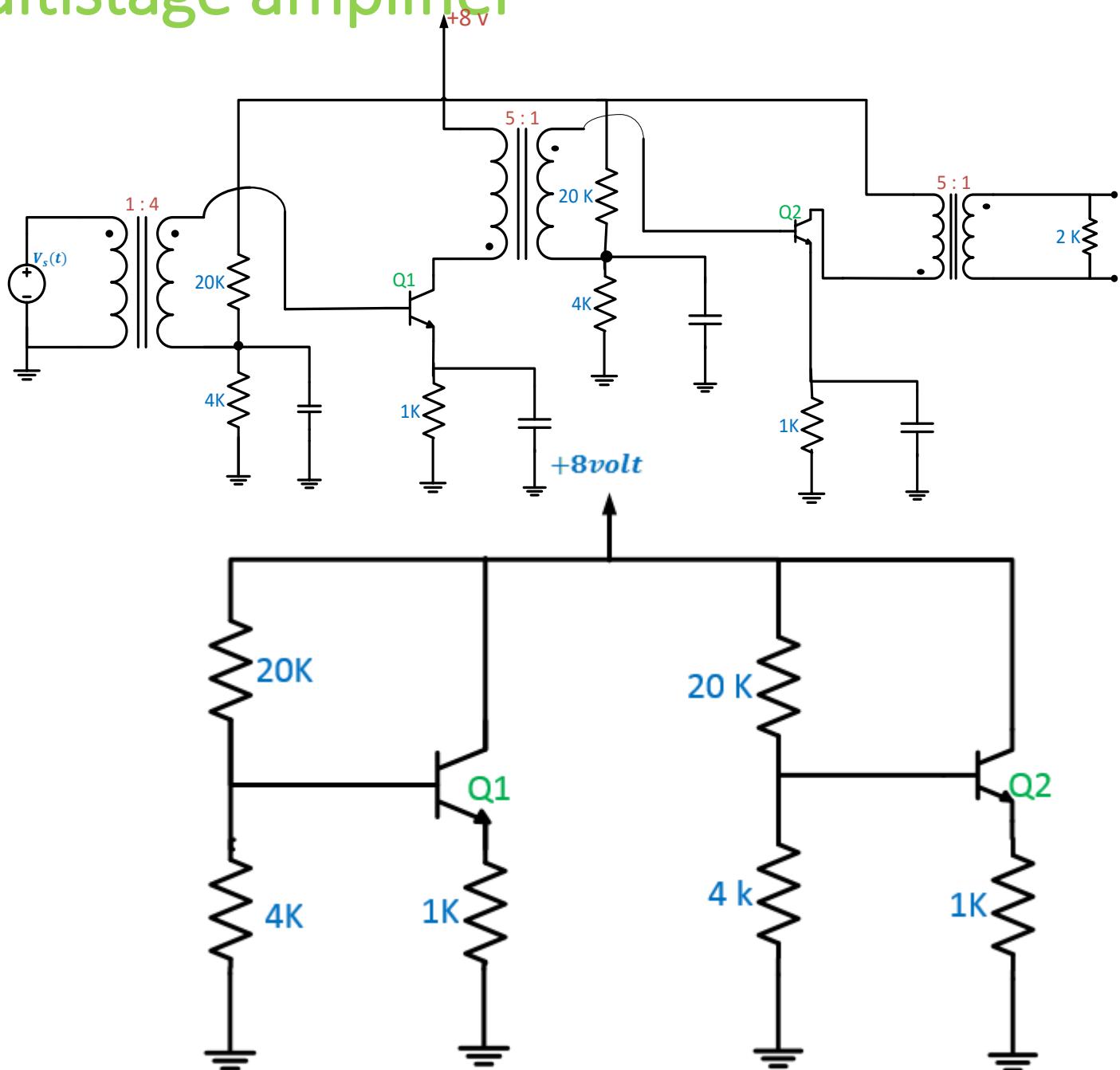




3) Transformer coupled multistage amplifier

Ac small signal equivalent circuit

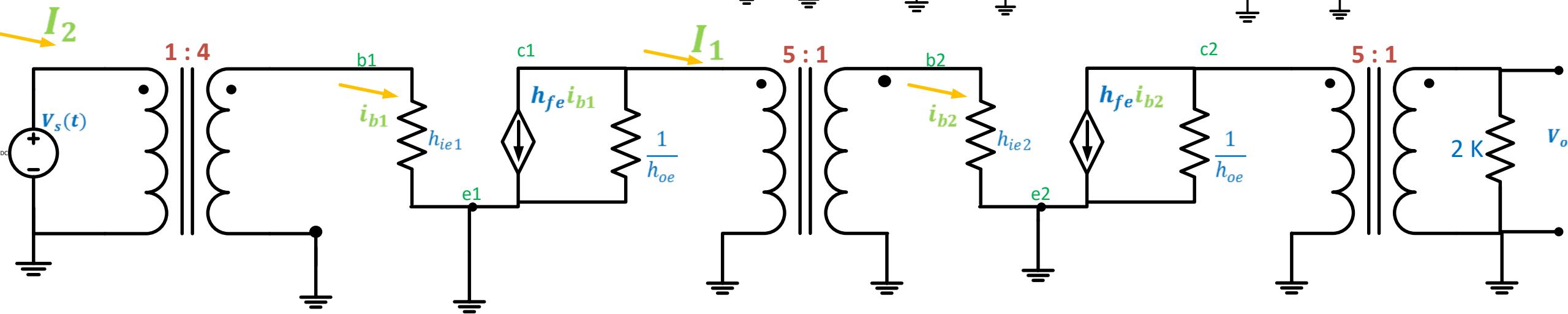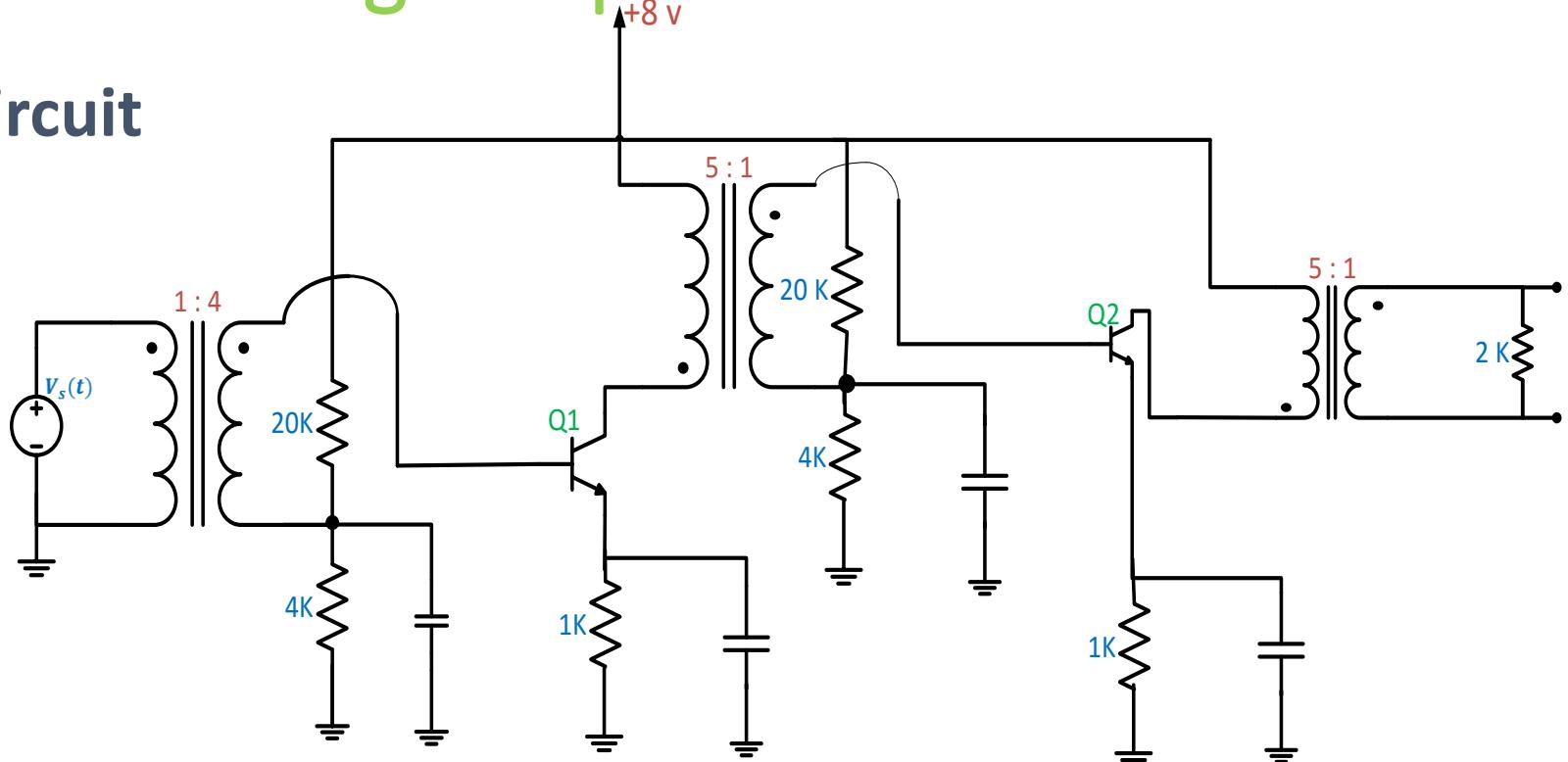

3) Transformer coupled multistage amplifier


Transformation

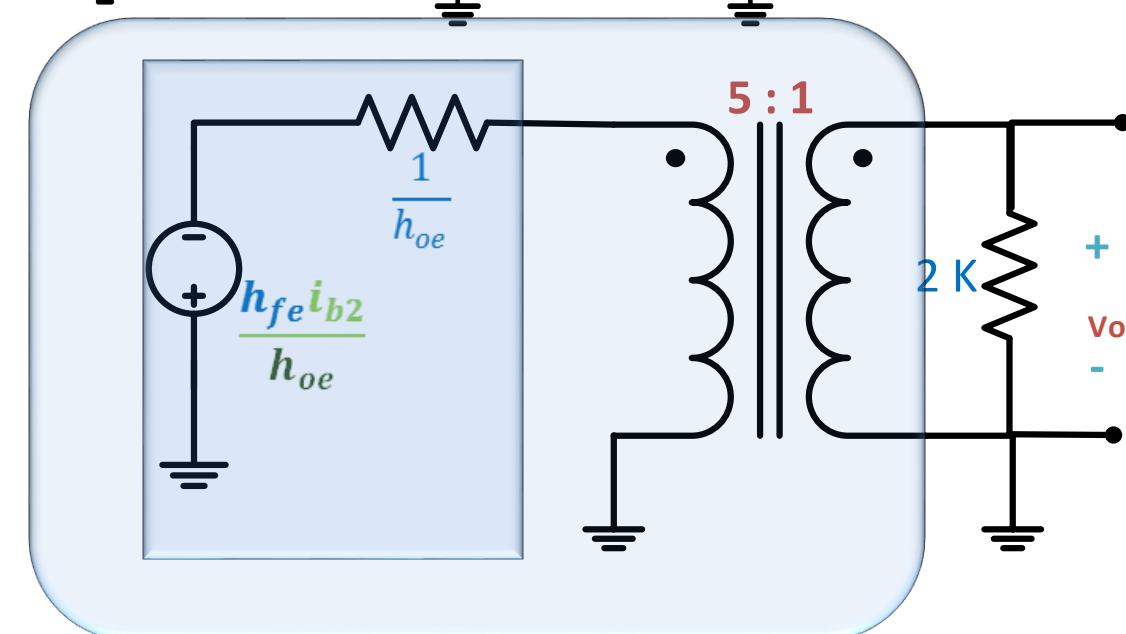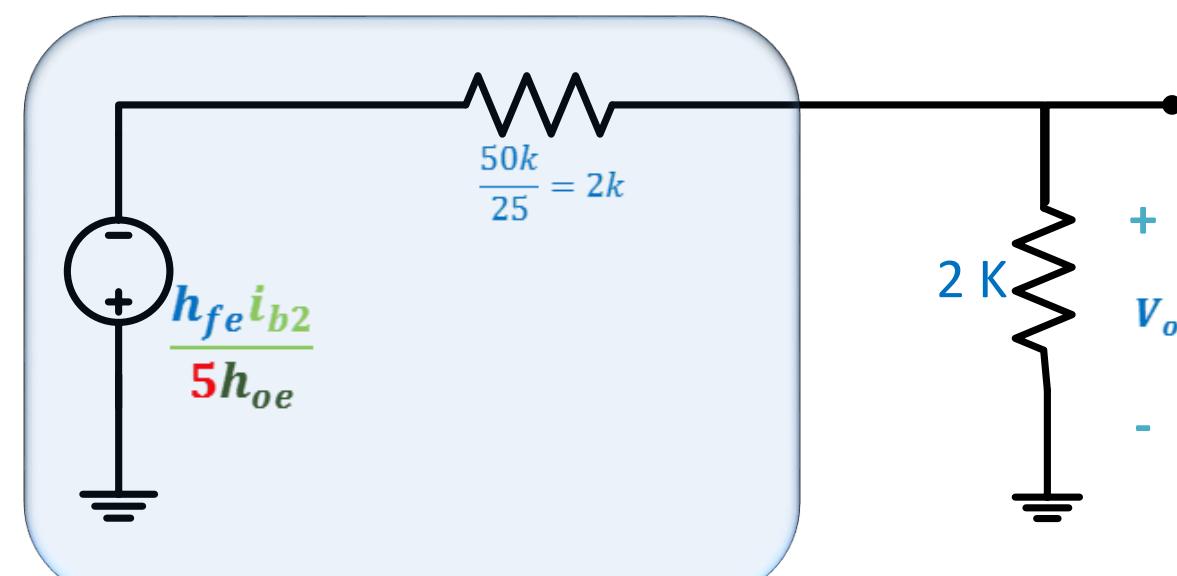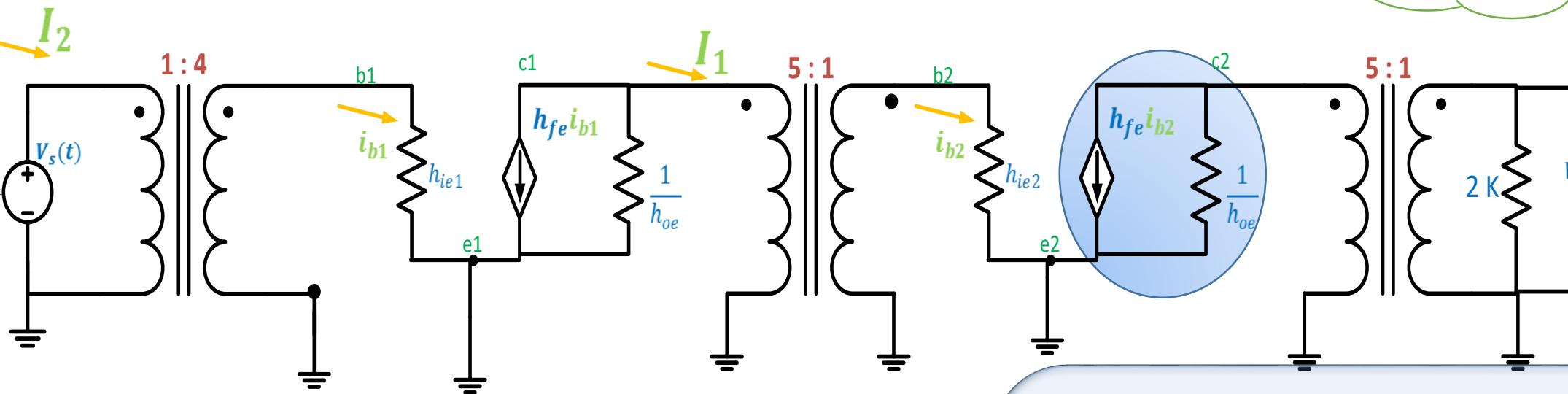

$$V_o = -\frac{2K}{2K+2K} \frac{h_{fe} i_{b2}}{5h_{oe}}$$

3) Transformer coupled multistage amplifier


To find $i_b 2$

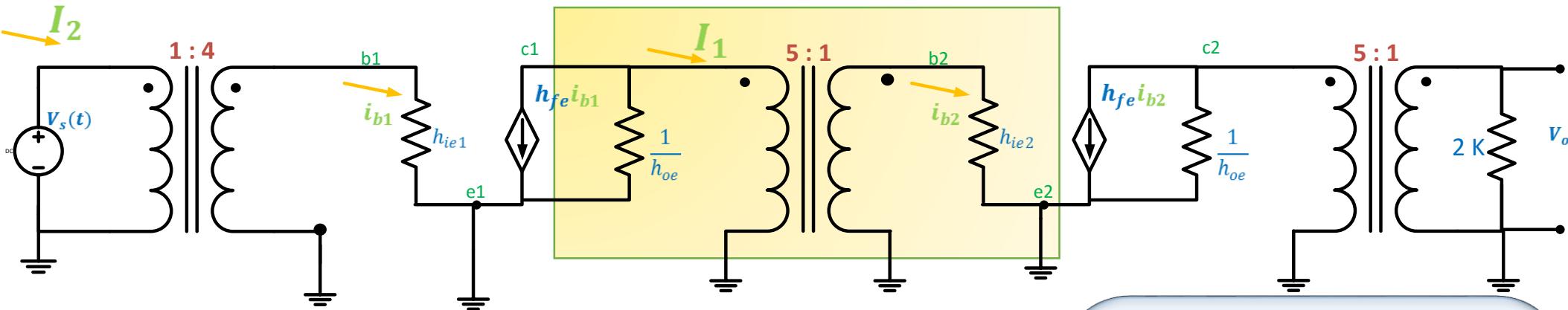

$$i_b 2 = 5I_1$$

To find I_1

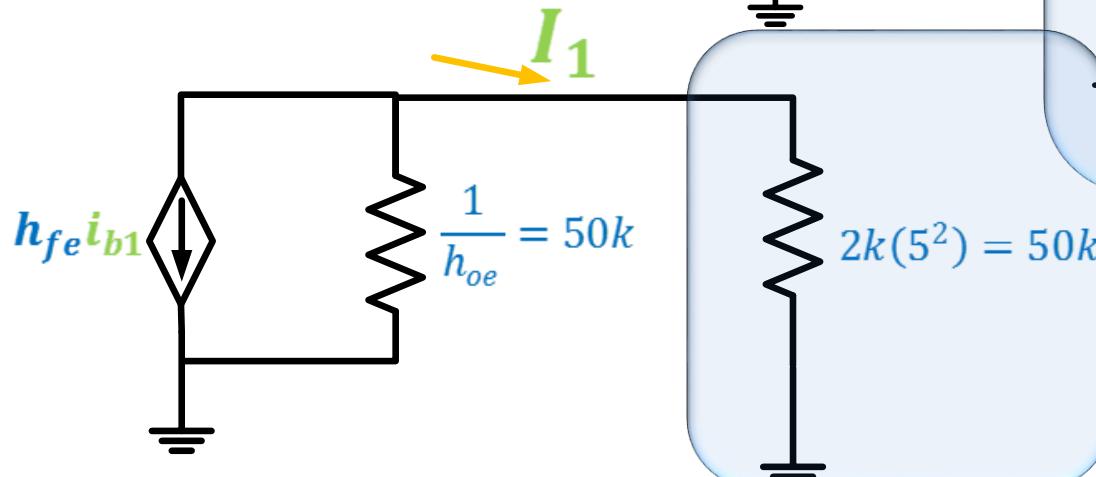
$$I_1 = -h_{fe} i_{b1} \frac{50K}{50K+50K}$$



3) Transformer coupled multistage amplifier

To find i_{b1}

$$i_{b1} = + \frac{1}{4} I_2$$

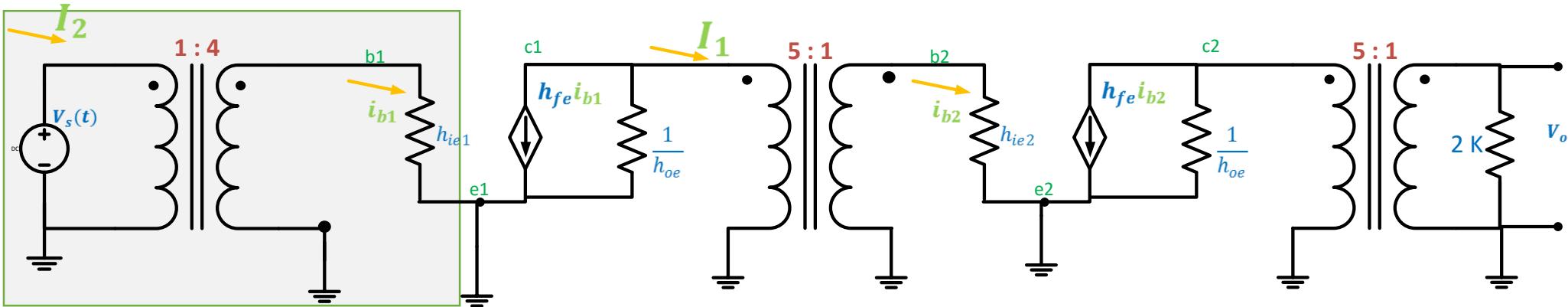

To find I_2

$$I_2 = \frac{V_S}{\frac{h_{ie1}}{16}}$$

$$\therefore A_v = \frac{V_o}{V_S} = +62.5$$

