




Frequency Response



Frequency Response

ω_L Lower cut off frequency

ω_H Upper cut off frequency

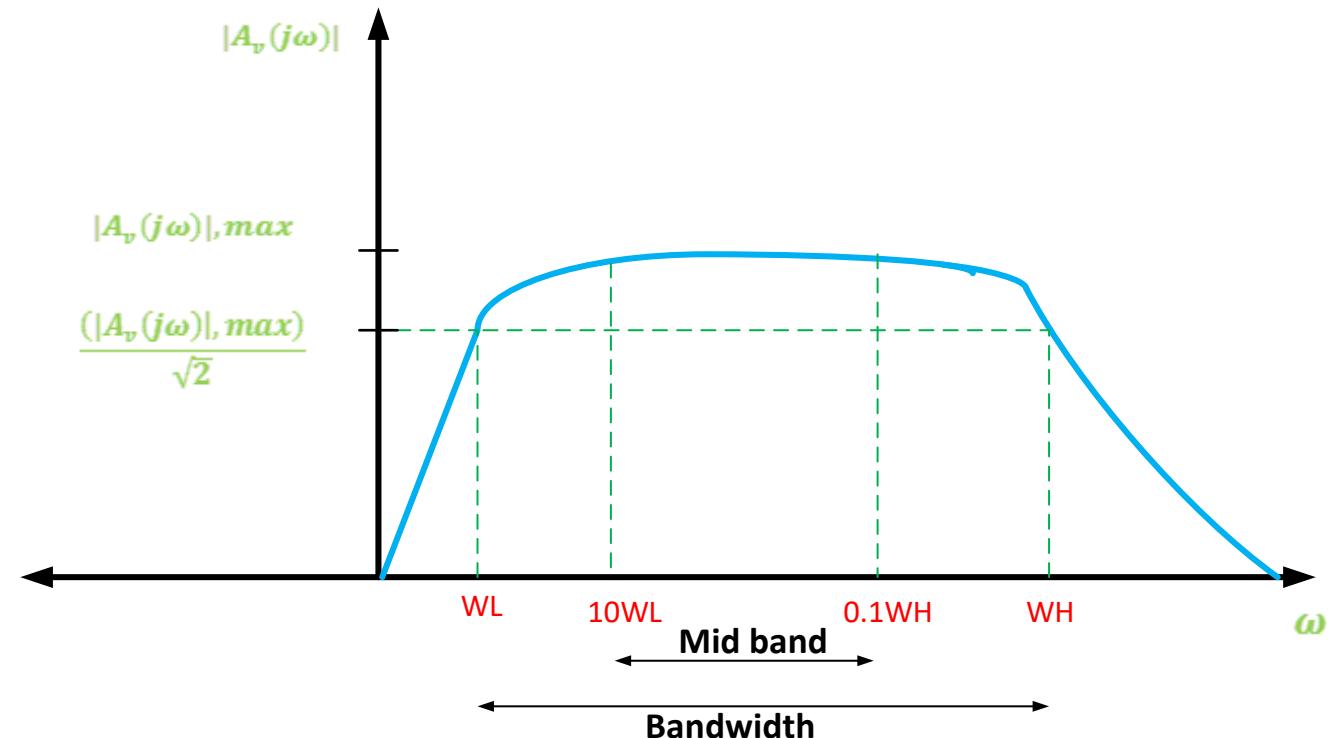

$$|A_v(j\omega)|_{\omega=\omega_L} = \frac{|A_v(j\omega)|_{max}}{\sqrt{2}} = \frac{|A_v|_{mid}}{\sqrt{2}}$$

$$\text{Bandwidth} = \omega_H - \omega_L$$



$$\text{Mid band range} = 0.1\omega_H - 10\omega_L$$

Frequency Response

- The signal passed through an AC amplifier is usually a complex waveform containing many different frequency components, rather than a single frequency sine wave.
- For example, audio- frequency signal such as speech and music are combination of many different sine waves accruing simultaneously with different amplitude and different frequencies in the range from $20H_z$ to $20kH_z$.
- In order for an output to be an amplified version of the input, an amplifier must amplify every frequency component in the signal by the same amount.
- Bandwidth must cover the entire range of frequency components if undistorted amplification is to be achieved.

Series Capacitance and low-frequency Response

1) at mid band range

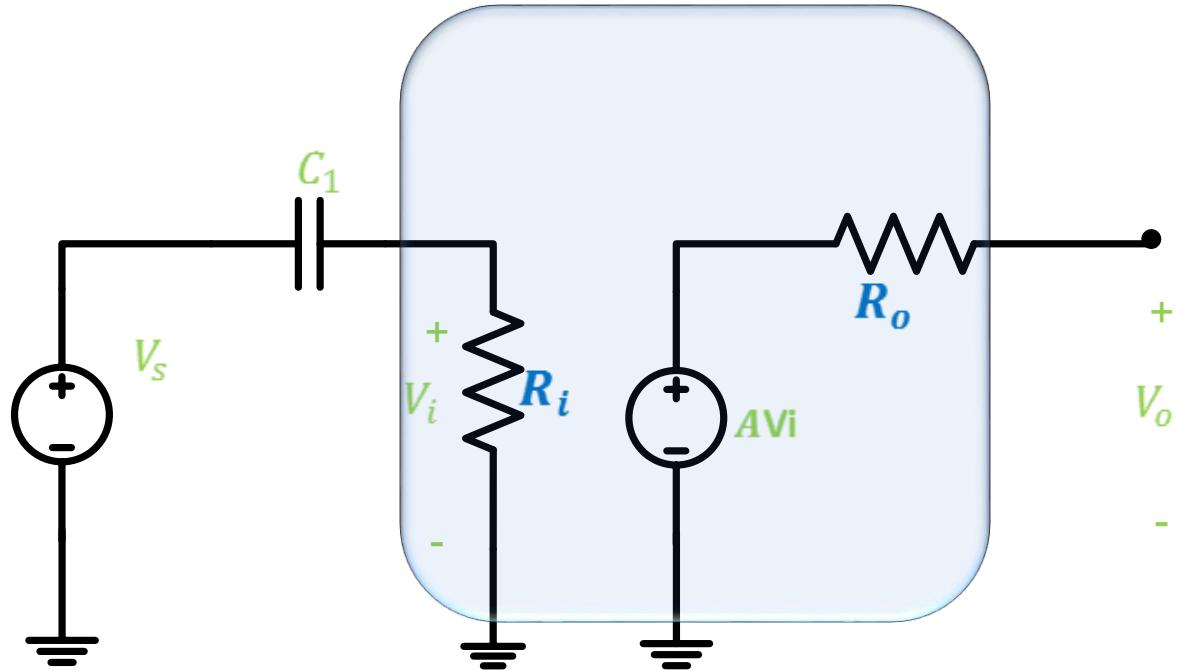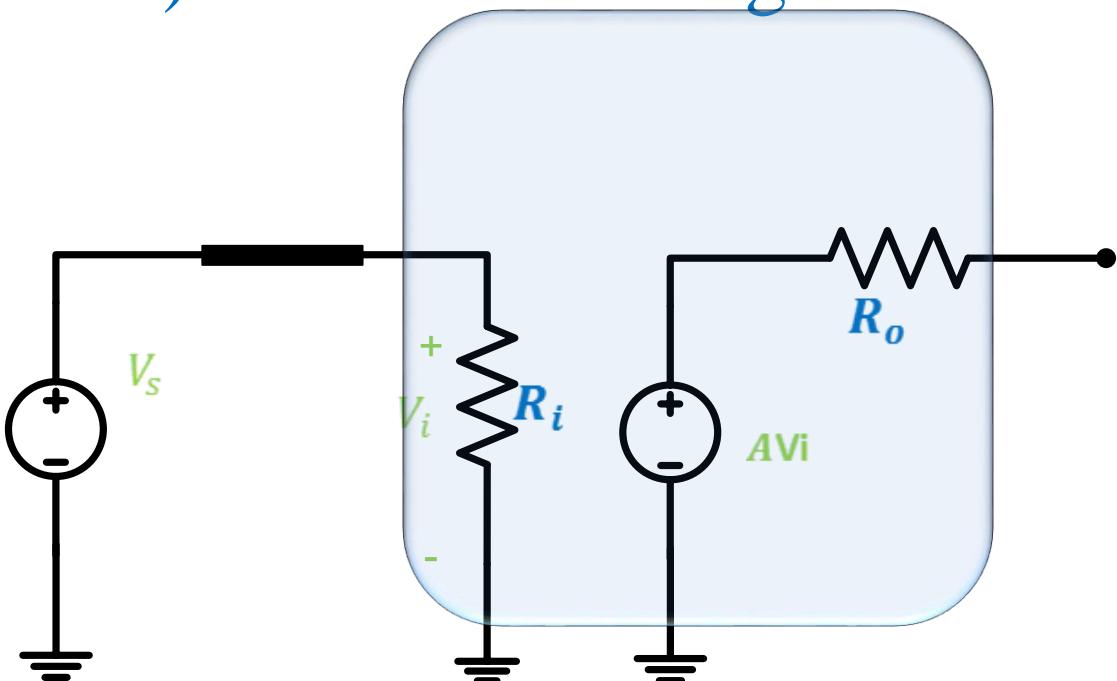

$$V_o = AV_i$$
$$V_i = V_s$$

$$\therefore \frac{V_o}{V_s} = A = A_{v(mid)}$$

Series Capacitance and low-frequency Response

2) At Low Frequency


$$V_o = A V_i$$

$$V_i = \frac{R_i}{R_i + \frac{1}{j\omega C_1}} V_s$$

$$\frac{V_o}{V_s} = A_v(j\omega) = A \frac{R_i}{R_i + \frac{1}{j\omega C_1}}$$

$$A_v(j\omega) = A \frac{1}{1 + \frac{1}{jR_i\omega C_1}}$$

$$|A_v(j\omega)| = A \frac{1}{\sqrt{1 + (\frac{1}{R_i\omega C_1})^2}}$$

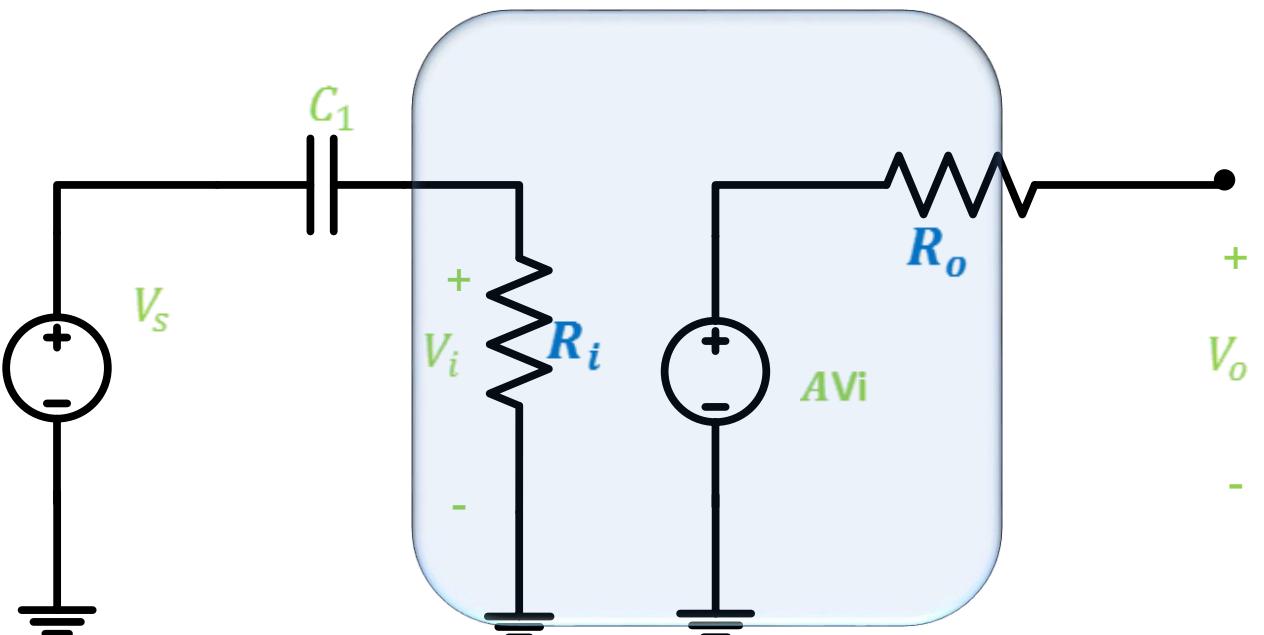

a) If $\omega \rightarrow 0 ; |A_v(j\omega)| \rightarrow 0$

b) If $\omega \rightarrow \infty ; |A_v(j\omega)| \rightarrow A$

c) If $\omega = \frac{1}{R_i C_1} ; |A_v(j\omega)| \rightarrow \frac{A}{\sqrt{2}}$

Series Capacitance and low-frequency Response

$$\therefore \omega_L = \frac{1}{R_i C_1}$$

$$\text{Let } \omega_{c1} = \frac{1}{R_{TH} C_1}$$

Where ω_{c1} is the corner frequency of C_1


$$\omega_{c1} = \frac{1}{R_i C_1}$$

$$\therefore \omega_L = \omega_{c1}$$

a) If $\omega \rightarrow 0 ; |A_v(j\omega)| \rightarrow 0$

b) If $\omega \rightarrow \infty ; |A_v(j\omega)| \rightarrow A$

c) If $\omega = \frac{1}{R_i C_1} ; |A_v(j\omega)| \rightarrow \frac{A}{\sqrt{2}}$

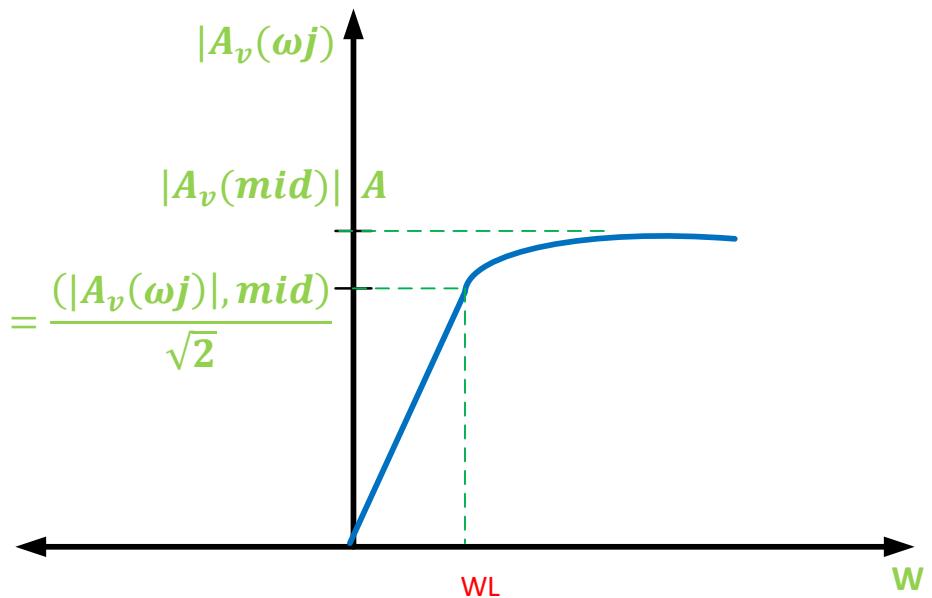



Input and output coupling capacitors

1. At mid band range

$$V_o = \frac{R_L}{R_L + R_o} A V_i$$

$$V_i = V_s$$
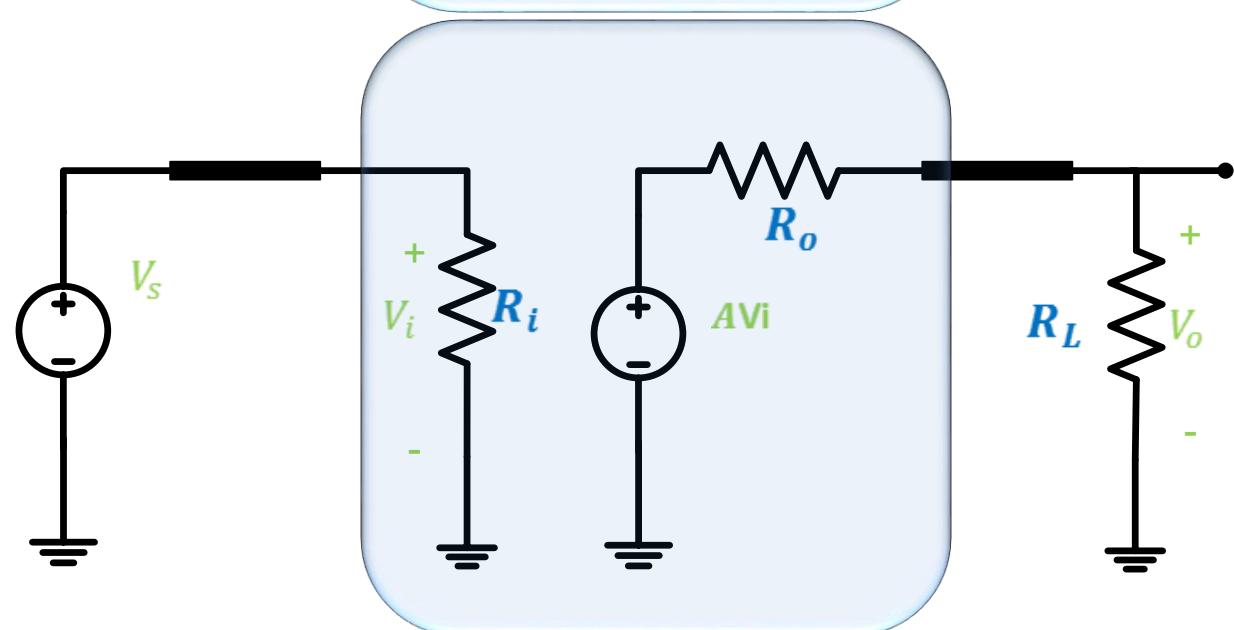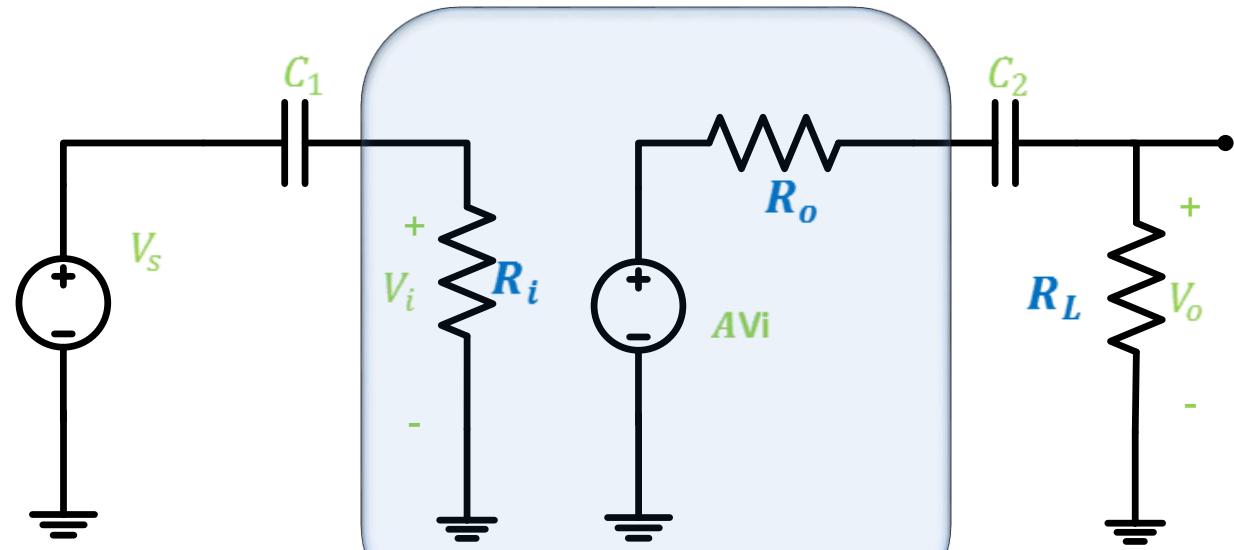
$$A_{v(mid)} = \frac{V_o}{V_s} = A \frac{R_L}{R_L + R_o}$$



Input and output coupling capacitors

2. At low frequency:

$$V_o = \frac{R_L}{R_L + R_o + \frac{1}{j\omega C_2}} A V_i$$




$$V_i = \frac{R_i}{R_i + \frac{1}{j\omega C_1}} V_s$$

$$A_{v(j\omega)} = \frac{V_o}{V_s} = A \frac{R_L}{R_L + R_o} \left(\frac{1}{1 + \frac{\omega_{c1}}{j\omega}} \right) \left(\frac{1}{1 + \frac{\omega_{c2}}{j\omega}} \right)$$

$$\therefore A_{v(j\omega)} = A_{v(mid)} \left(\frac{1}{1 + \frac{\omega_{c1}}{j\omega}} \right) \left(\frac{1}{1 + \frac{\omega_{c2}}{j\omega}} \right)$$

$$|A_{v(j\omega_L)}| = \frac{A_{v(mid)}}{\sqrt{2}}$$

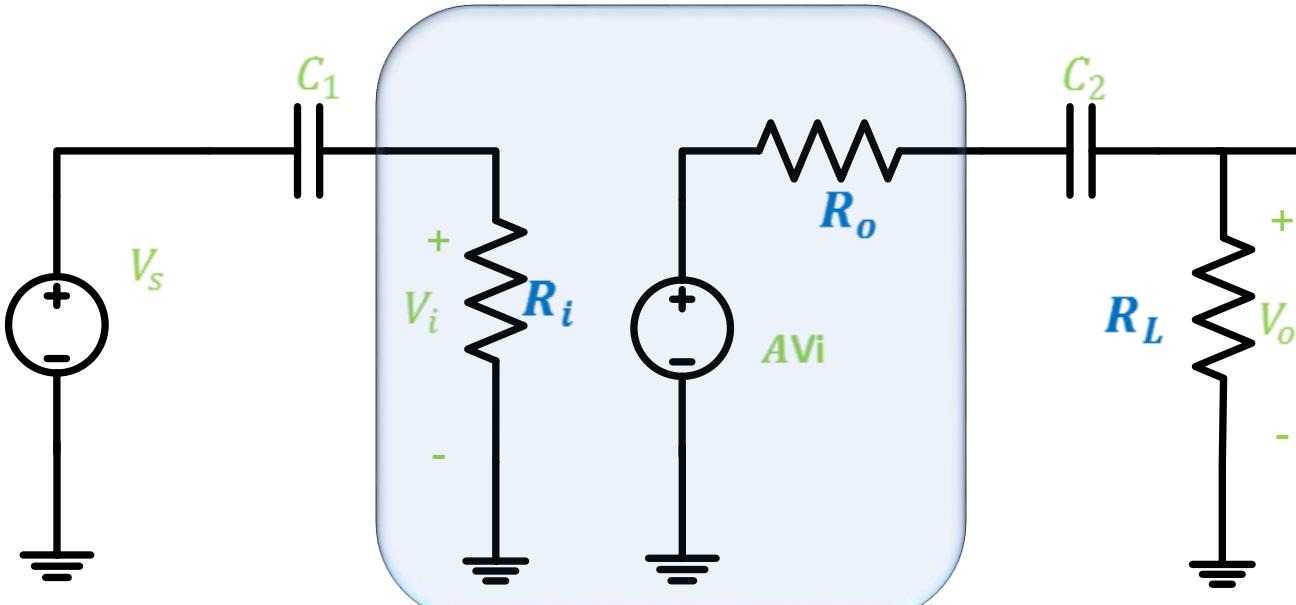

Where

$$\omega_{c1} = \frac{1}{R_i C_1}$$

$$\omega_{c2} = \frac{1}{(R_o + R_L) C_2}$$

Input and output coupling capacitors

$$|A_v(j\omega_L)| = \frac{A_{v(mid)}}{\left|(1 + \frac{\omega_{c1}}{j\omega_L})(1 + \frac{\omega_{c2}}{j\omega_L})\right|}$$

$$\therefore \left|(1 + \frac{\omega_{c1}}{j\omega_L})(1 + \frac{\omega_{c2}}{j\omega_L})\right| = \sqrt{2}$$

$$\therefore \omega_L^2 = \frac{\omega_{c1}^2 + \omega_{c2}^2}{2} + \frac{\sqrt{(\omega_{c1}^4 + \omega_{c2}^4 + 6\omega_{c1}^2\omega_{c2}^2)}}{2}$$

$$\therefore A_{v(j\omega)} = A_{v(mid)} \left(\frac{1}{1 + \frac{\omega_{c1}}{j\omega}} \right) \left(\frac{1}{1 + \frac{\omega_{c2}}{j\omega}} \right)$$
$$|A_v(j\omega_L)| = \frac{A_{v(mid)}}{\sqrt{2}}$$

- A) Let $\omega_{c1} = 616 \text{ r/s}$
 $\omega_{c2} = 17.86 \text{ r/s}$
 $\therefore \omega_L = 616.517 \text{ r/s}$

- B) Let $\omega_{c1} = 200 \text{ r/s}$
 $\omega_{c2} = 750 \text{ r/s}$
 $\therefore \omega_L = 798 \text{ r/s}$
 $\therefore \text{if } \omega_{c1} > \omega_{c2} > \omega_{c3}$
 $\therefore \omega_{c1} + \omega_{c2} + \omega_{c3} > \omega_L > \omega_{c1}$



$$A_{v(j\omega)} = A_{v(mid)} \frac{1}{(1 + \frac{\omega_{c1}}{j\omega})(1 + \frac{\omega_{c2}}{j\omega})} \quad \therefore \left| (1 + \frac{\omega_{c1}}{j\omega_L})(1 + \frac{\omega_{c2}}{j\omega_L}) \right| \approx \left| (1 + \frac{\omega_{c1}}{j\omega_L}) \right|$$

Let $\omega_{c1} > \omega_{c2}$; $\omega_L > \omega_{c1}$

$$|A_{v(j\omega_L)}| = \frac{A_{v(mid)}}{\left| (1 + \frac{\omega_{c1}}{j\omega_L})(1 + \frac{\omega_{c2}}{j\omega_L}) \right|}$$



$$\therefore \left| (1 + \frac{\omega_{c1}}{j\omega_L}) \right| \approx \sqrt{2}$$

$$\sqrt{1 + (\frac{\omega_{c1}}{\omega_L})^2} = \sqrt{2}$$

$$|A_{v(j\omega_L)}| = \frac{A_{v(mid)}}{\sqrt{2}}$$

$$\therefore \left| (1 + \frac{\omega_{c1}}{j\omega_L})(1 + \frac{\omega_{c2}}{j\omega_L}) \right| = \sqrt{2}$$

$$\therefore \omega_{c1} = \omega_L \quad (\text{Lower limit})$$

Since $\omega_{c1} > \omega_{c2}$ and $\omega_L > \omega_{c1}$

$$\therefore \frac{\omega_{c1}}{\omega_L} < 1 \quad \text{and} \quad \frac{\omega_{c2}}{\omega_L} \ll 1$$

To find the upper limit



$$\left| \left(1 + \frac{\omega_{c1}}{j\omega_L}\right) \left(1 + \frac{\omega_{c2}}{j\omega_L}\right) \right| = \sqrt{2}$$

$$\left| 1 + \frac{\omega_{c1} + \omega_{c2}}{j\omega_L} - \frac{\omega_{c1}}{\omega_L} \cdot \frac{\omega_{c2}}{\omega_L} \right| = \sqrt{2}$$

$$\left| 1 + \frac{\omega_{c1} + \omega_{c2}}{j\omega_L} - \frac{\omega_{c1}}{\omega_L} \cdot \frac{\omega_{c2}}{\omega_L} \right| \approx \sqrt{\left(1 + \left(\frac{\omega_{c1} + \omega_{c2}}{\omega_L}\right)^2\right)}$$

$$\sqrt{\left(1 + \left(\frac{\omega_{c1} + \omega_{c2}}{\omega_L}\right)^2\right)} = \sqrt{2}$$

But $\frac{\omega_{c1}}{\omega_L} < 1$ and $\frac{\omega_{c2}}{\omega_L} \ll 1$

$$\therefore \frac{\omega_{c1} + \omega_{c2}}{\omega_L} = 1$$

$\therefore \omega_L = \omega_{c1} + \omega_{c2}$ Upper limit

$$\therefore \frac{\omega_{c1}}{\omega_L} \cdot \frac{\omega_{c2}}{\omega_L} \ll \ll 1$$

$$\therefore \text{let } \frac{\omega_{c1}}{\omega_L} \cdot \frac{\omega_{c2}}{\omega_L} \rightarrow 0$$



$\therefore \text{if } \omega_{c1} > \omega_{c2}$

$$\omega_{c1} + \omega_{c2} > \omega_L > \omega_{c1}$$

CE Amplifier low-frequency Analysis



$$h_{ie} = 10.45k, h_{fe} = 350, R_1 \parallel R_2 = 16.67k$$

$$R_c = 5k, R_L = 2k, R_E = 5k, R_s = 1k$$

$$C_1 = 3\mu F, C_2 = 8\mu F, \text{ and } C_E = 50\mu F$$

Estimate ω_L

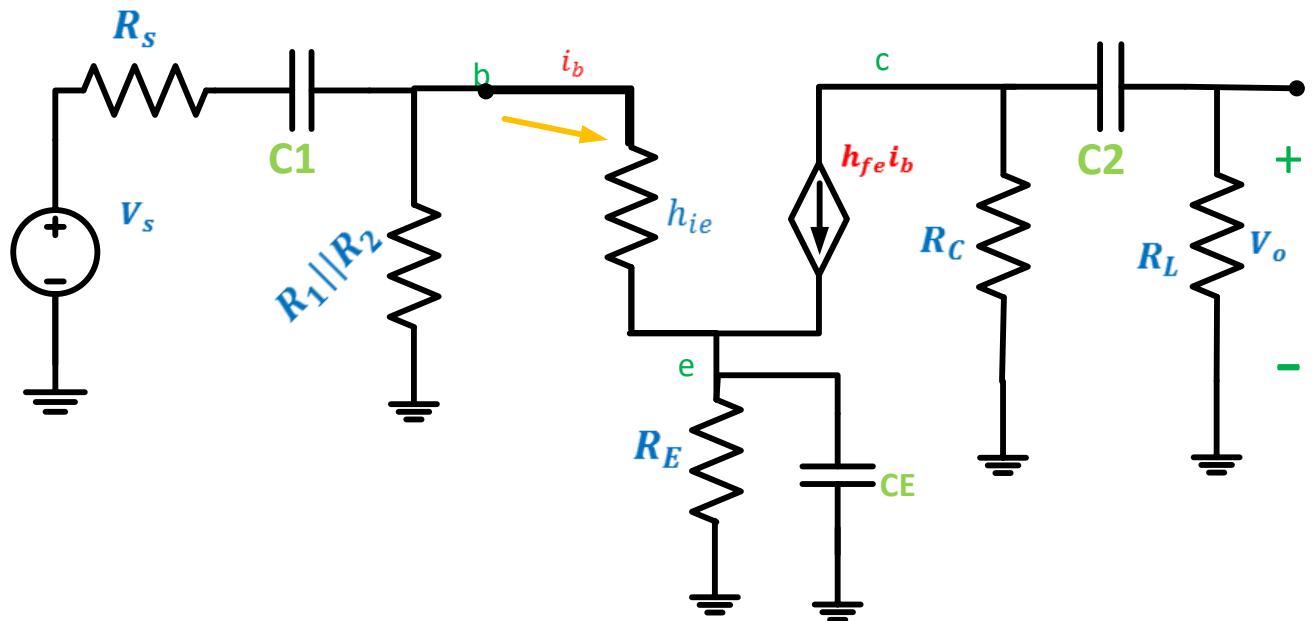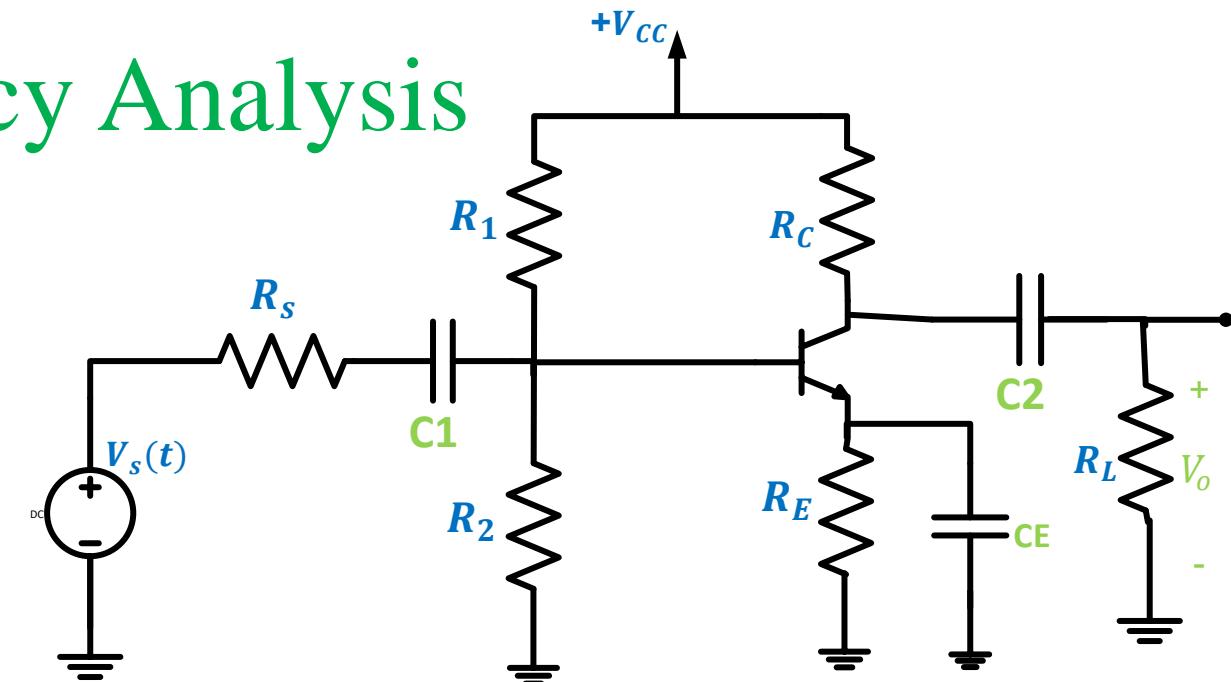Ac small signal low- frequency equivalent C_{KT}





CE Amplifier low-frequency Analysis

1) To find ω_{c1} , set C_E and C_2 short

$$\omega_{c1} = \frac{1}{R_{TH1} C_1}$$

$$R_{TH1} = R_s + R_1 \parallel R_2 \parallel h_{ie}$$
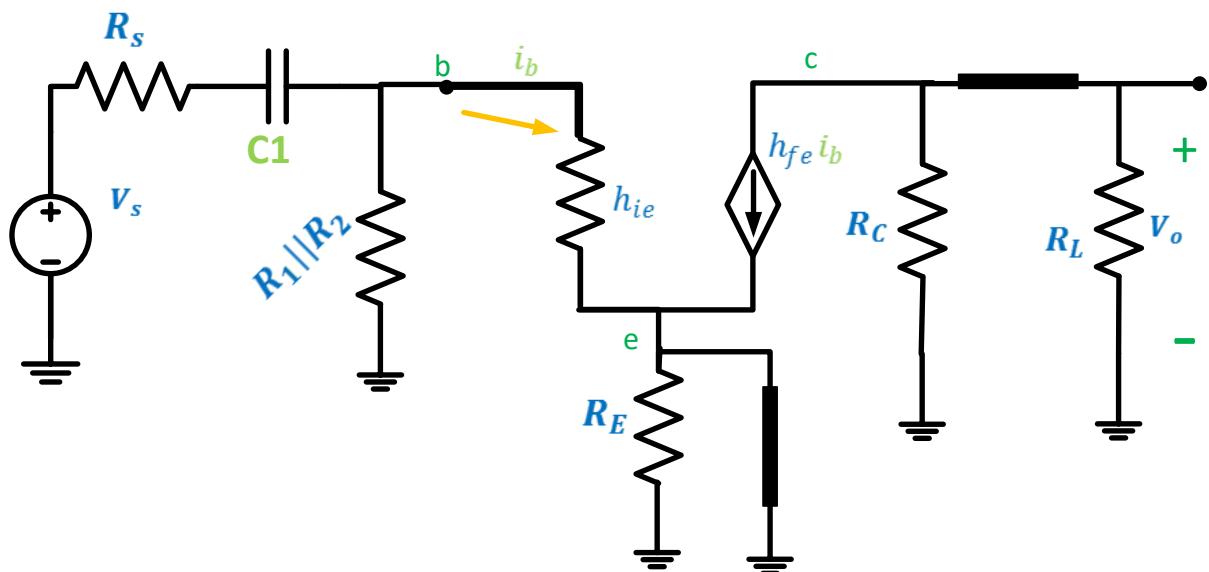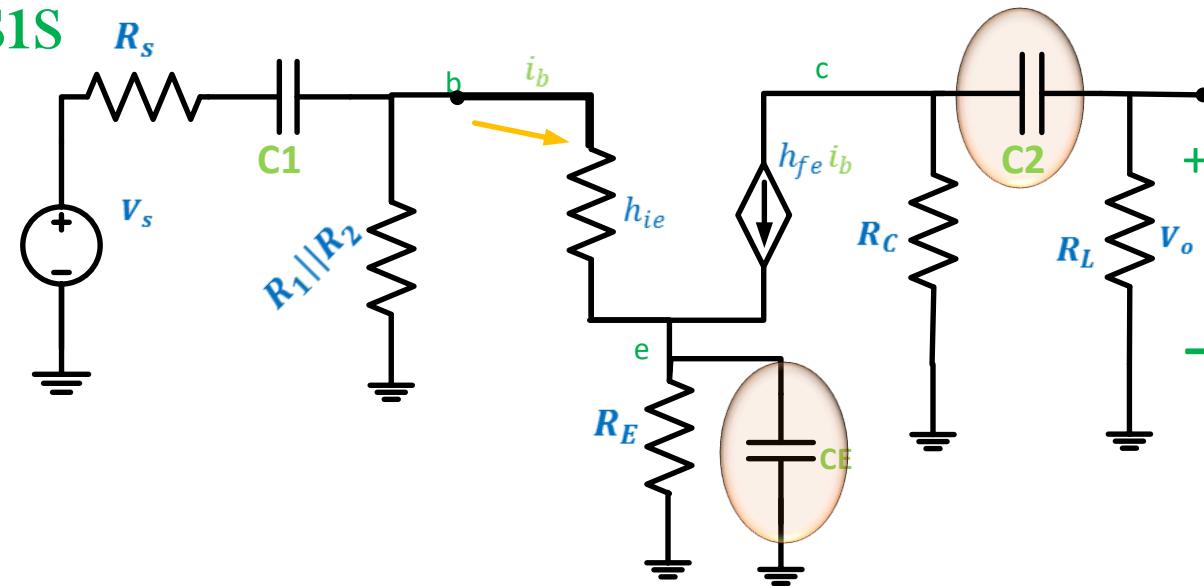
$$\therefore \omega_{c1} = 44.9 \text{ r/s}$$




CE Amplifier low-frequency Analysis

- 2) To find ω_{c2} , set C_1 and C_E short

$$\omega_{c2} = \frac{1}{R_{TH_2} C_2}$$

$$R_{TH_2} = R_L + R_c$$

$$\omega_{c2} = 17.86 \text{ r/s}$$

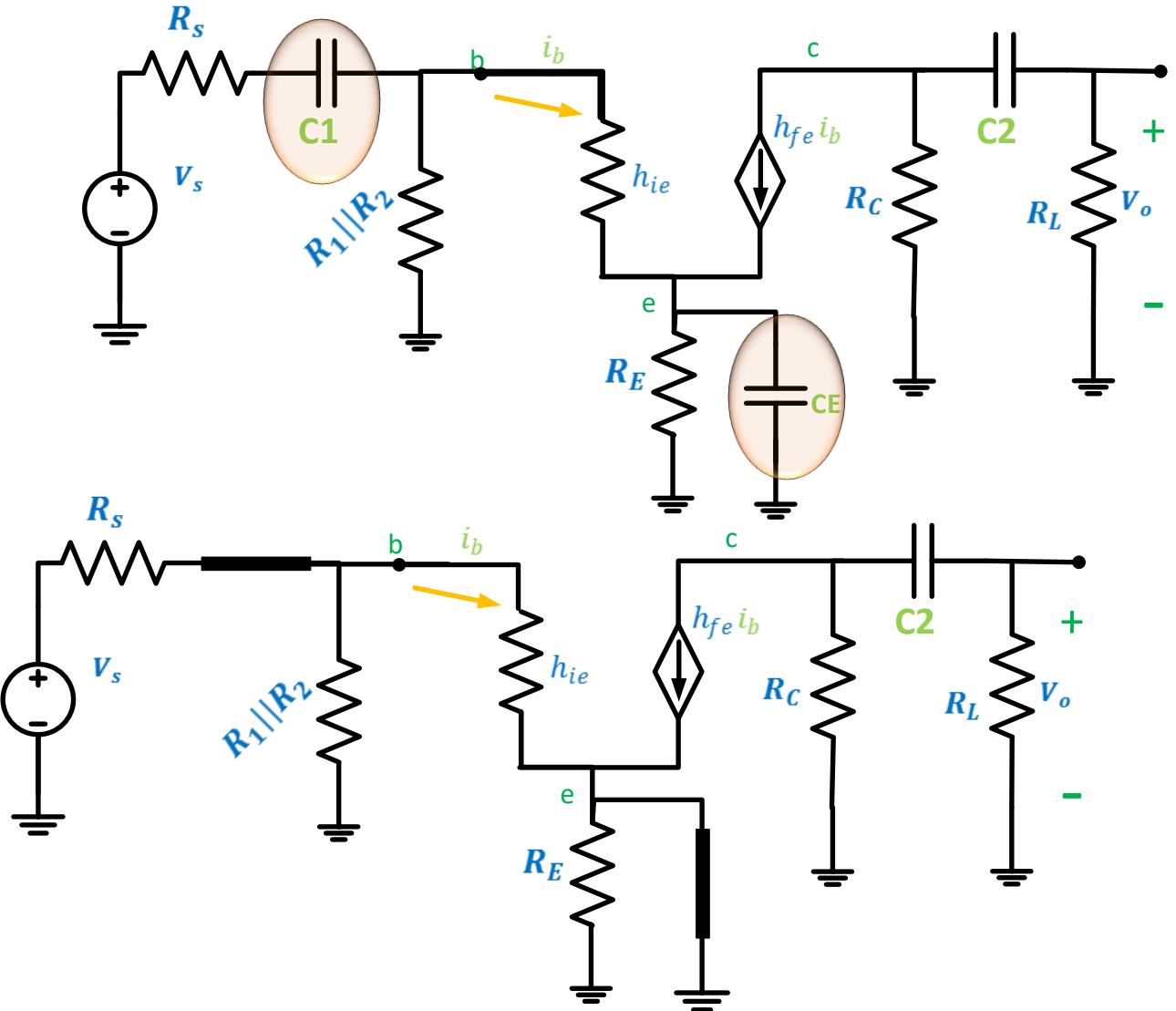

CE Amplifier low-frequency Analysis

3) To find ω_{CE} , set C_1 and C_2 short

$$\omega_{CE} = \frac{1}{R_{TH_3} C_E}$$

$$R_{TH_3} = R_E \parallel \left(\frac{R_s IIR_1 IIR_2 + h_{ie}}{h_{fe} + 1} \right)$$



$$\therefore \omega_{CE} = 616 \text{ r/s}$$

But $\omega_{C2} = 17.86 \text{ r/s}$ and $\omega_{C1} = 44.9 \text{ r/s}$

$$\omega_{C1} + \omega_{C2} + \omega_{CE} > \omega_L > \omega_{CE}$$

$$679 \text{ r/s} > \omega_L > 616 \text{ r/s}$$
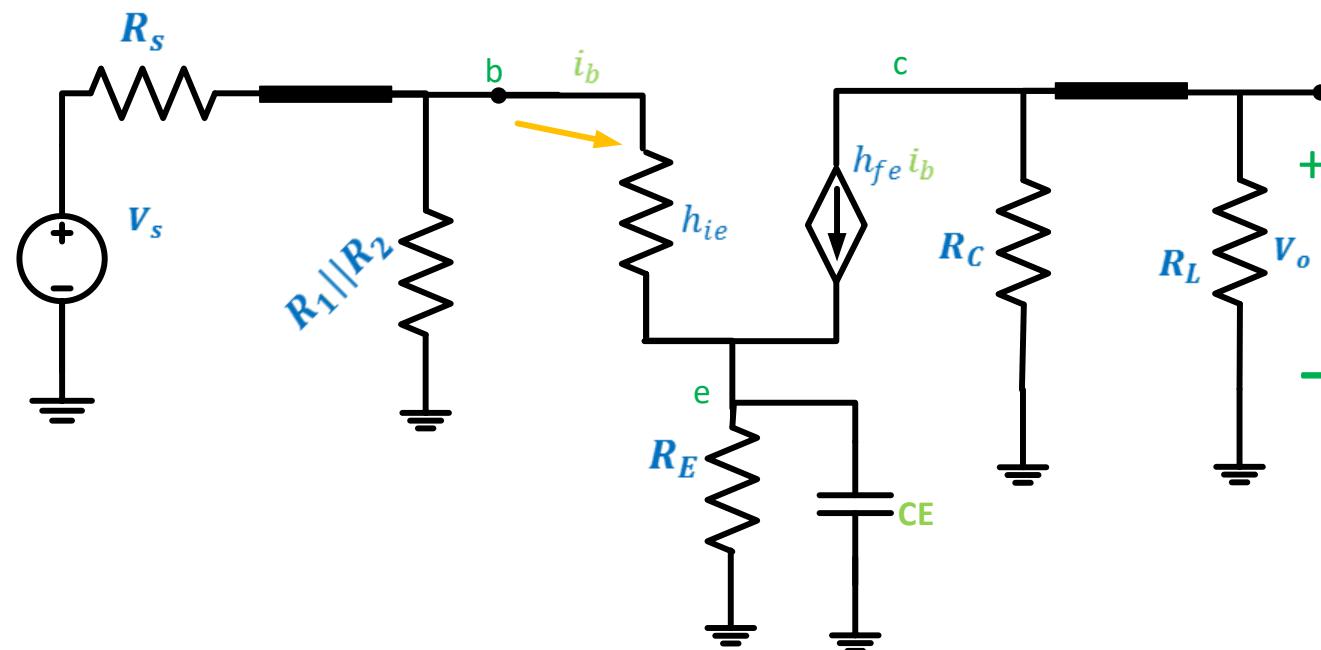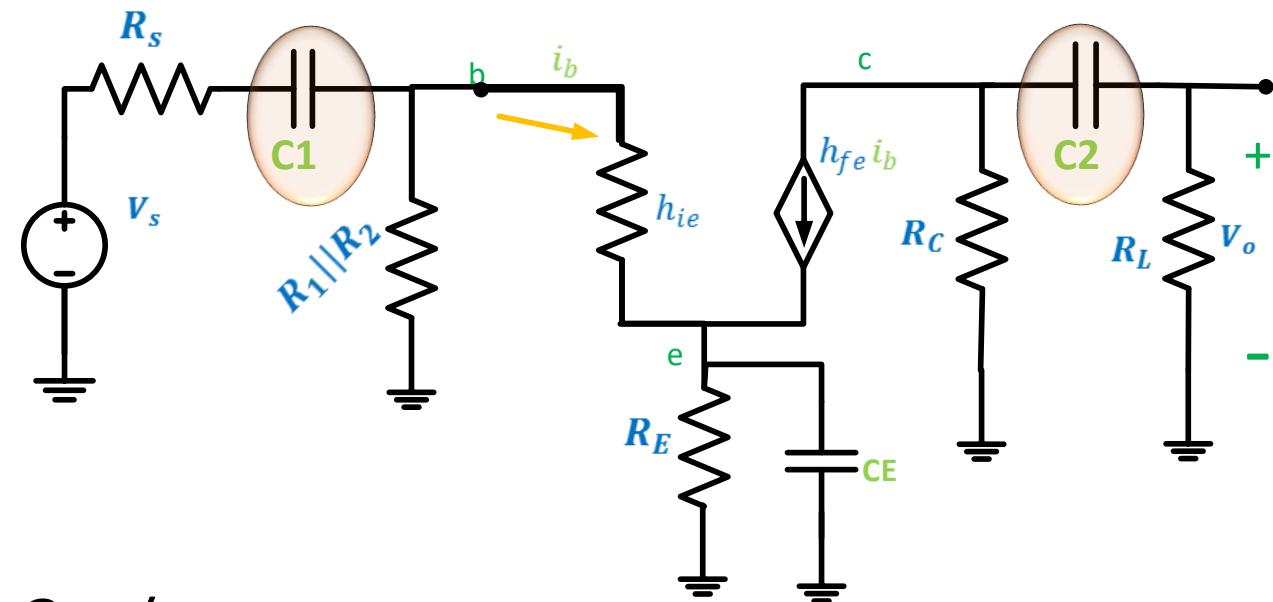
$$\omega_L \equiv 645 \text{ r/s} \quad \text{exact}$$



CE Amplifier low-frequency Design

Complete the design so that $W_L = 1000 \text{ r/s}$

$$\omega_{C1} + \omega_{C2} + \omega_{CE} = \omega_l = 1000 \text{ r/s}$$


$$\omega_{CE} \geq 70\% \omega_L$$

$$\omega_{CE} \geq 0.7 \omega_L$$

$$\omega_{CE} = 850 \text{ r/s}$$

$$\omega_{C2} = 50 \text{ r/s}$$

$$\omega_{C1} = 100 \text{ r/s}$$

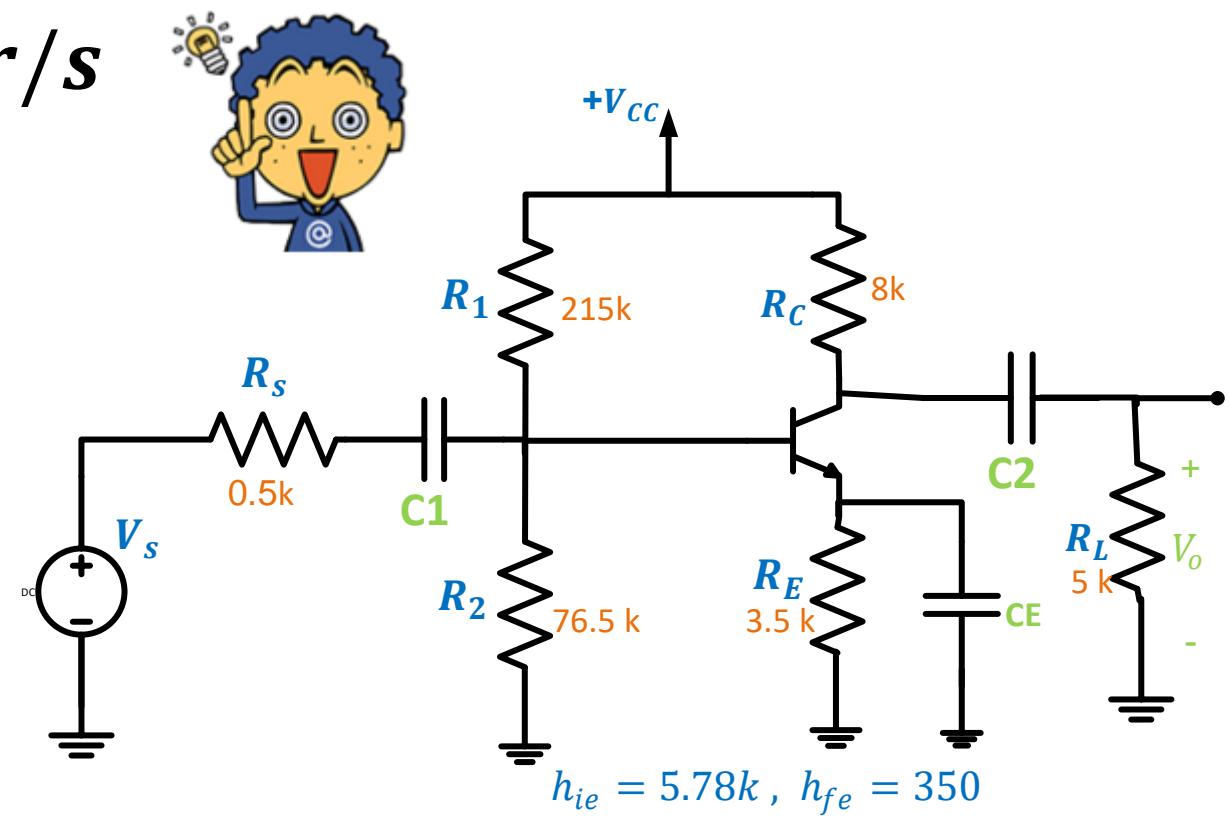

CE Amplifier low-frequency Design

$$\omega_{CE} = \frac{1}{R_E II \left\{ \frac{R_s II R_1 II R_2 + h_{ie}}{1 + h_{fe}} \right\} C_E} = 850 \text{ r/s}$$

$$\therefore C_E = 65.9 \mu F$$



$$\omega_{c1} = \frac{1}{[R_s + R_1 II R_2 II h_{ie}] C_1} = 100 \text{ r/s}$$

$$\therefore C_1 = 1.74 \mu F$$



Choose $C_E = 80 \mu F$

$$C_1 = C_2 = 2 \mu F$$

$$\omega_{c2} = \frac{1}{[R_C + R_L] C_2} = 50 \text{ r/s}$$

$$\therefore C_2 = 1.54 \mu F$$



$$\therefore \omega_L = 982 \text{ r/s}$$

$$\omega_{CE} = 850 \text{ r/s}$$


$$\omega_{C2} = 50 \text{ r/s}$$

$$\omega_{C1} = 100 \text{ r/s}$$




CS Low- Frequency Analysis

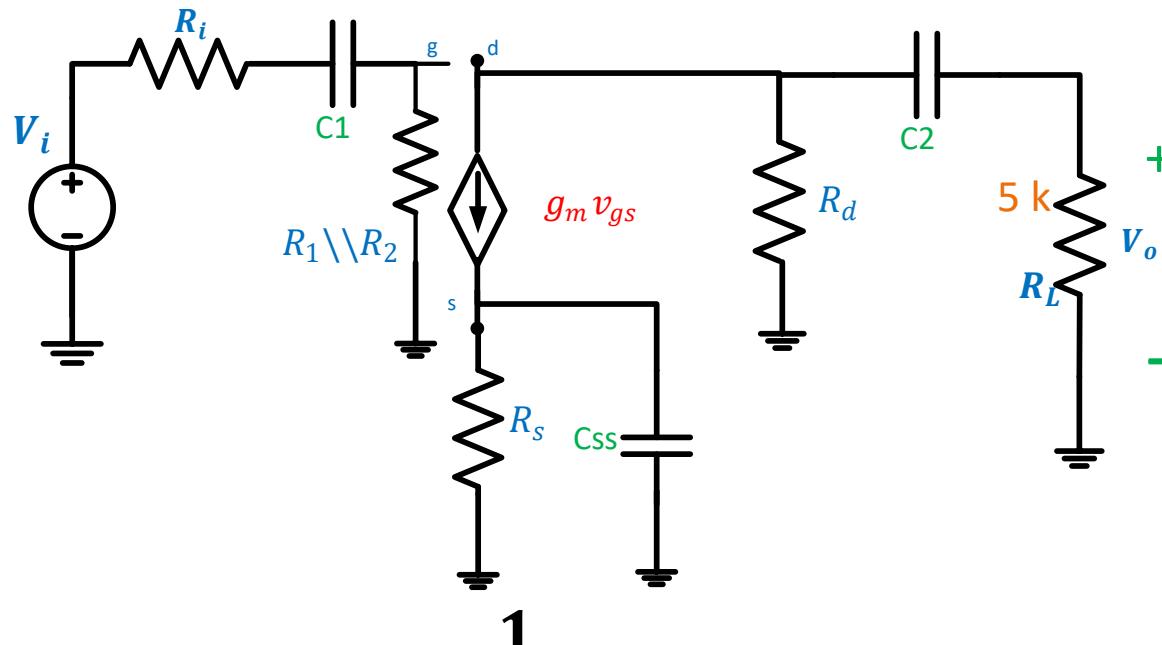Ac small signal low-frequency equivalent circuit:



$$\omega_{c1} = \frac{1}{C_1[R_i + R_1 \parallel R_2]} = 49.9 \text{ r/s}$$
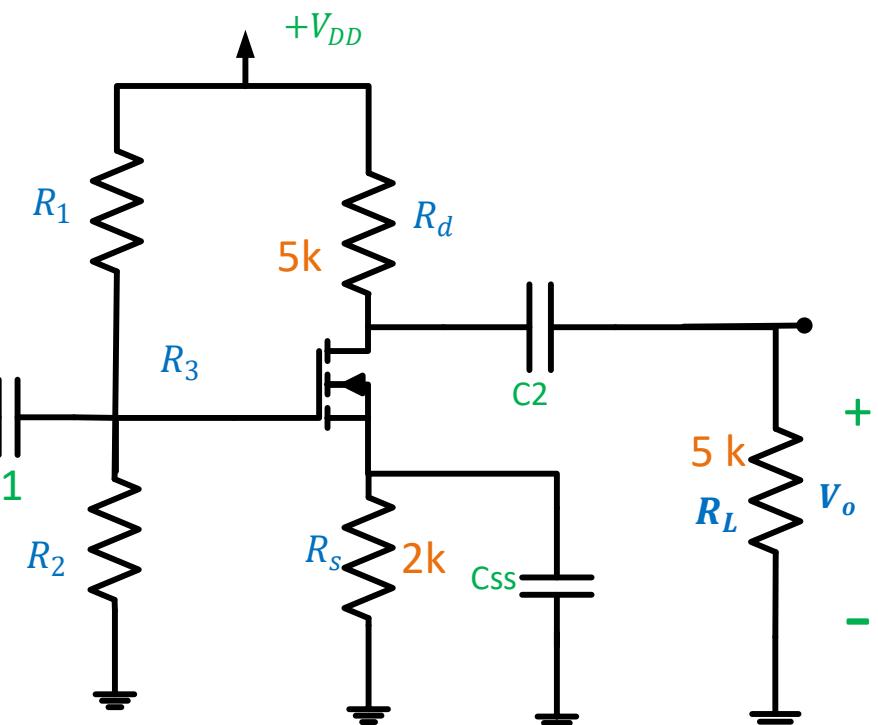
$$\omega_{c2} = \frac{1}{C_2[R_L + R_d]} = 100 \text{ r/s}$$



$$R_1 \parallel R_2 = 100k, g_m = 10 \text{ mV}$$


$$C_1 = 0.2 \mu\text{F}, C_2 = 1 \mu\text{F}, C_{ss} = 10 \mu\text{F}$$

$$\omega_{css} = \frac{1}{C_{ss} \left[R_s II \frac{1}{g_m} \right]} = 1050 \text{ r/s}$$

$$\omega_{c1} + \omega_{c2} + \omega_{css} > \omega_L > \omega_{css}$$

$$1199.9 \text{ r/s} > \omega_L > 1050 \text{ r/s}$$


$$\omega_L = 1059.4 \text{ r/s}$$

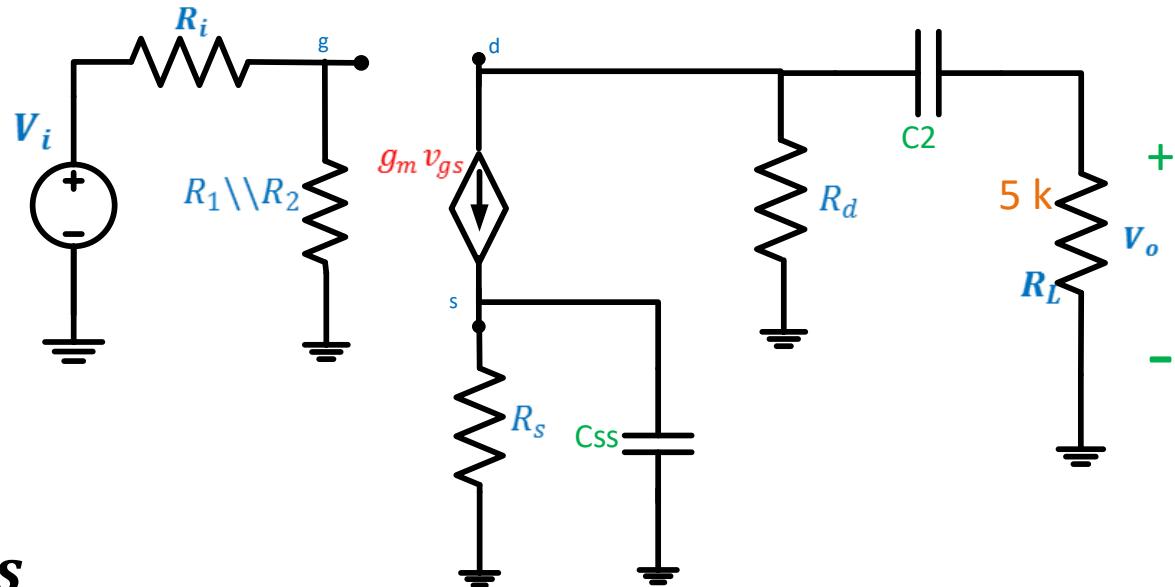

$$\omega_{c1} = \frac{1}{C_1 [R_i + R_1 IIR_2]} = 49.9 \text{ r/s}$$

$$\omega_{c2} = \frac{1}{C_2 [R_L + R_d]} = 100 \text{ r/s}$$


The Amplifier Frequency Response

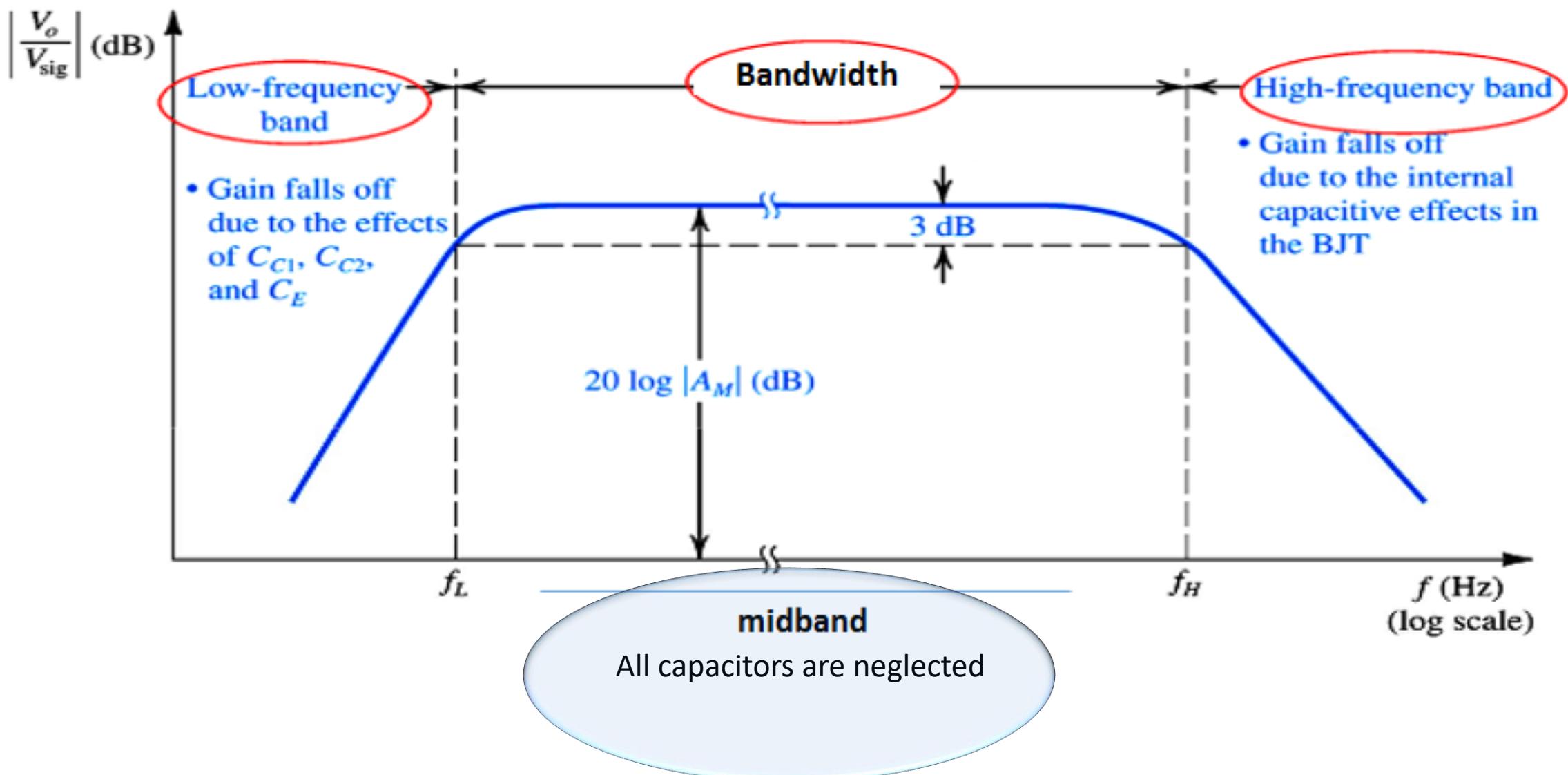

Shunt Capacitance and the high-frequency Response


1) At mid band

$$V_o = A V_i$$

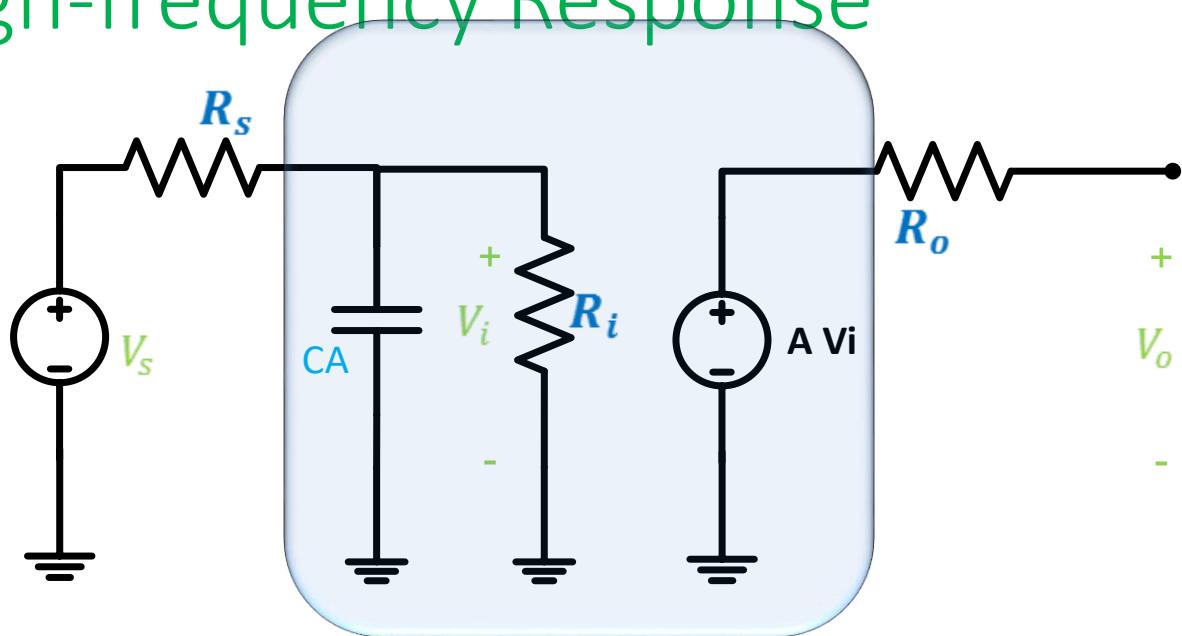

$$V_i = \frac{R_i}{R_i + R_s} V_s$$
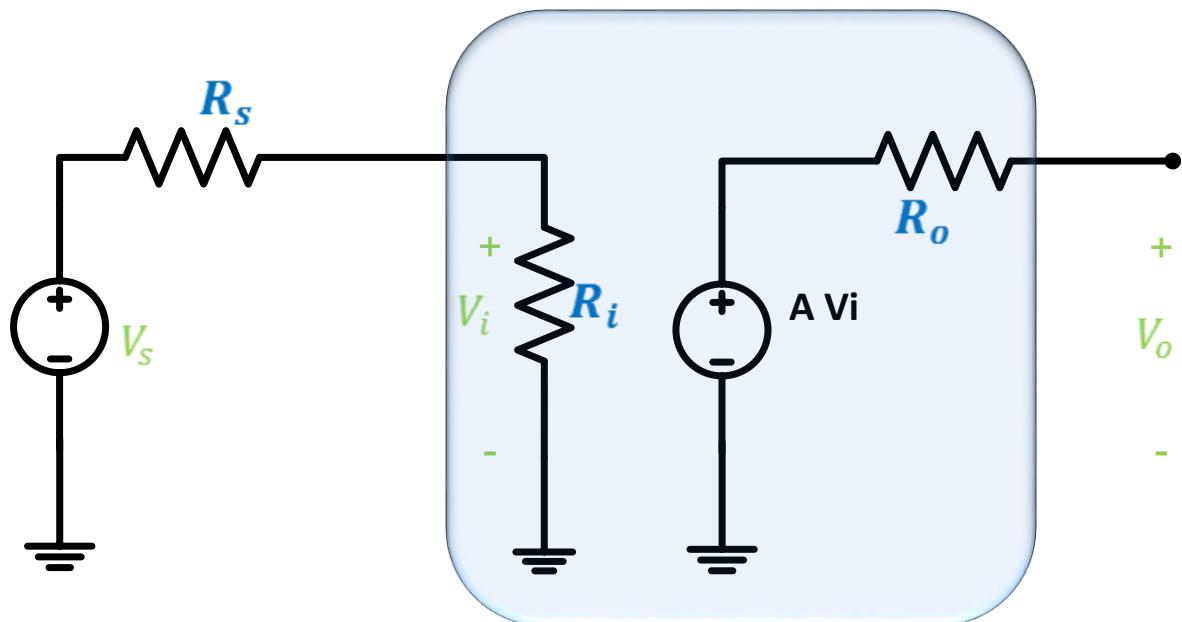
$$\therefore A_{v(mid)} = \frac{V_o}{V_s} = A \frac{R_i}{R_i + R_s}$$



2) At high- frequency


$$V_o = A V_i$$

$$V_i = \frac{R_i || \frac{1}{j\omega C_A}}{R_i || \frac{1}{j\omega C_A} + R_s} V_s$$

$$\therefore A_{v(j\omega)} = \frac{V_o}{V_s}$$

$$\therefore A_{v(j\omega)} = A \frac{R_i}{R_i + R_s} \frac{1}{1 + j\omega C_A (R_s || R_i)}$$

$$\therefore A_{v(j\omega)} = A_{v(mid)} \frac{1}{1 + j\omega C_A (R_s || R_i)}$$

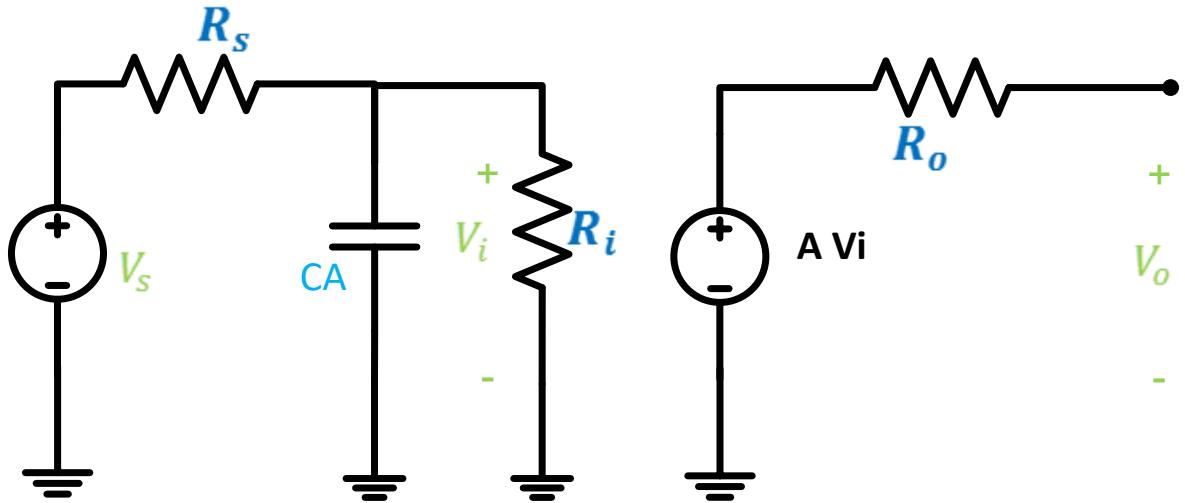

$$|A_{v(j\omega)}| = A_{v(mid)} \frac{1}{\sqrt{1 + [\omega C_A (R_s || R_i)]^2}}$$

A) for small ω ; $|A_{v(j\omega)}| = A_{v(mid)}$

B) for large ω ; $|A_{v(j\omega)}| = 0$

C) for $\omega = \frac{1}{C_A (R_s || R_i)}$; $|A_{v(j\omega)}| = \frac{A_{v(mid)}}{\sqrt{2}}$

$$\therefore \omega_H = \frac{1}{c_A(R_s || R_i)}$$

$$\text{But } \omega_{CA} = \frac{1}{c_A R_{TH}}$$

$$\omega_{CA} = \frac{1}{c_A(R_s || R_i)}$$

$$\therefore \omega_H = \omega_{CA}$$

ω_H : The upper cut off frequency of the C_{KT}

ω_{CA} : The corner frequency of C_A


$$A_v(j\omega) = A_{v(mid)} \frac{1}{1 + j\omega c_A(R_s || R_i)}$$

$$\omega_{CA} = \frac{1}{c_A(R_s || R_i)}$$

$$\therefore A_v(j\omega) = A_{v(mid)} \frac{1}{1 + \frac{j\omega}{\omega_{CA}}}$$



- A) for small ω ; $|A_{v(j\omega)}| = A_{v(mid)}$
- B) for large ω ; $|A_{v(j\omega)}| = 0$
- C) for $\omega = \frac{1}{c_A(R_s || R_i)}$; $|A_{v(j\omega)}| = \frac{A_{v(mid)}}{\sqrt{2}}$

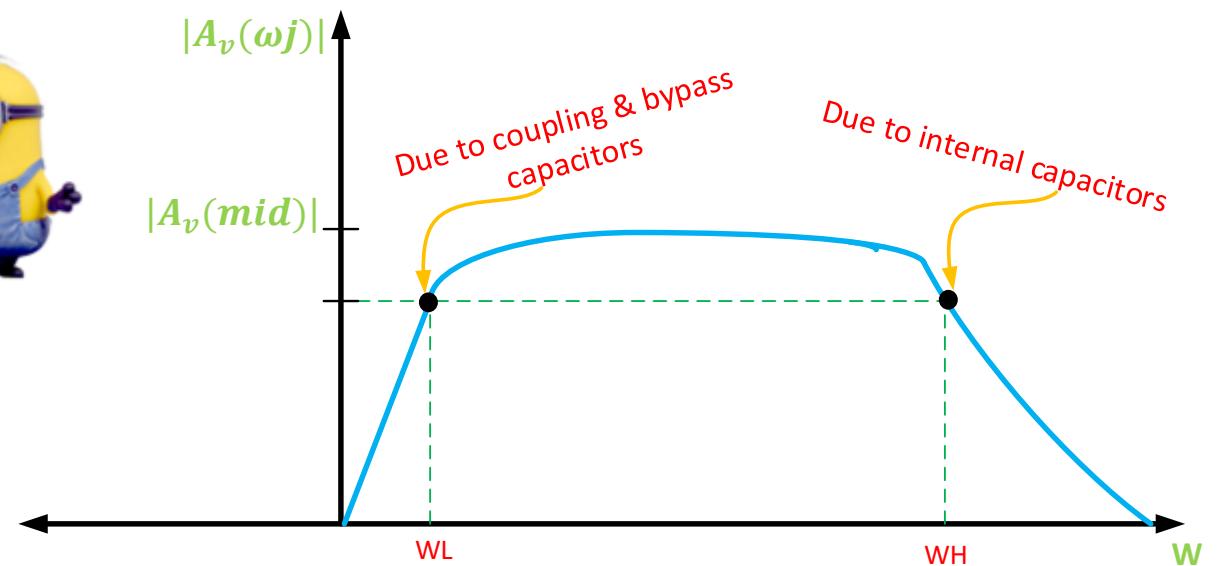

If we have two internal capacitors :



$$A_{v(j\omega)} = A_{v(mid)} \frac{1}{\left(1 + \frac{j\omega}{\omega_A}\right) \left(1 + \frac{j\omega}{\omega_B}\right)}$$

If $\omega_A = 1 \text{ M r/s}$, and $\omega_B = 5 \text{ M r/s}$

$$\omega_H = 0.964 \text{ M r/s}$$

\therefore if $\omega_A < \omega_B$; $\omega_H < \omega_A$

$$|A_{v(j\omega)}| = \frac{|A_{v(mid)}|}{\left|\left(1 + \frac{j\omega}{\omega_A}\right) \left(1 + \frac{j\omega}{\omega_B}\right)\right|}$$

assuming $\omega_A < \omega_B$

$$|A_{v(j\omega_H)}| = \frac{|A_{v(mid)}|}{\left|\left(1 + \frac{j\omega_H}{\omega_A}\right) \left(1 + \frac{j\omega_H}{\omega_B}\right)\right|} = \frac{|A_{v(mid)}|}{\sqrt{2}}$$

$$\therefore \left| \left(1 + \frac{j\omega_H}{\omega_A}\right) \left(1 + \frac{j\omega_H}{\omega_B}\right) \right| = \sqrt{2}$$

Since $\omega_H < \omega_A$, and $\omega_H \ll \omega_B$

$$\therefore \frac{j\omega_H}{\omega_B} \rightarrow 0$$

$$\therefore \left| \left(1 + \frac{j\omega_H}{\omega_A}\right) \right| \approx \sqrt{2}$$

$$\omega_H = \omega_A$$

To find the lower limit

$$\left| \left(1 + \frac{j\omega_H}{\omega_A} \right) \left(1 + \frac{j\omega_H}{\omega_B} \right) \right| = \sqrt{2}$$

$$\left| 1 + j\omega_H \left(\frac{1}{\omega_A} + \frac{1}{\omega_B} \right) + \frac{\omega_H}{\omega_A} \frac{\omega_H}{\omega_B} \right| = \sqrt{2}$$

Since $\omega_H < \omega_A$, and $\omega_H \ll \omega_B$

$$\frac{\omega_H}{\omega_A} < 1 \text{ and } \frac{\omega_H}{\omega_B} \ll 1$$

$$\frac{\omega_H}{\omega_A} \quad \frac{\omega_H}{\omega_B} \quad \xrightarrow{\hspace{1cm}} \quad 0$$

$$\therefore \omega_H = \frac{1}{\left(\frac{1}{\omega_A} + \frac{1}{\omega_B} \right)}$$

$$\left| \left(1 + \frac{j\omega_H}{\omega_A} \right) \left(1 + \frac{j\omega_H}{\omega_B} \right) \right| \approx \left| \left(1 + j\omega_H \left(\frac{1}{\omega_A} + \frac{1}{\omega_B} \right) \right) \right| = \sqrt{2}$$

\therefore if $\omega_A < \omega_B$

$$\frac{1}{\frac{1}{\omega_A} + \frac{1}{\omega_B}} < \omega_H < \omega_A$$

If $\omega_A = 1 \text{ M r/s}$, $\omega_B = 5 \text{ M r/s}$

$$\omega_H \equiv 0.964 \text{ M r/s}$$

$$\frac{1}{\frac{1}{\omega_A} + \frac{1}{\omega_B}} < \omega_H < \omega_A$$

$$0.83 \text{ M r/s} < \omega_H < 1 \text{ M r/s}$$



$$0.83 \text{ M r/s} < 0.964 \text{ M r/s} < 1 \text{ M r/s}$$

FET High-Frequency Analysis

1) Common Source Amplifier


$$R_i = 0.3k, R_1 \parallel R_2 = 100k, R_d = R_L = 5k$$

$$R_s = 1k, g_m = 10 m\text{U}$$


$$C_{gd} = 2 \text{ pF and } C_{gs} = 5 \text{ pF}$$



Estimate ω_H

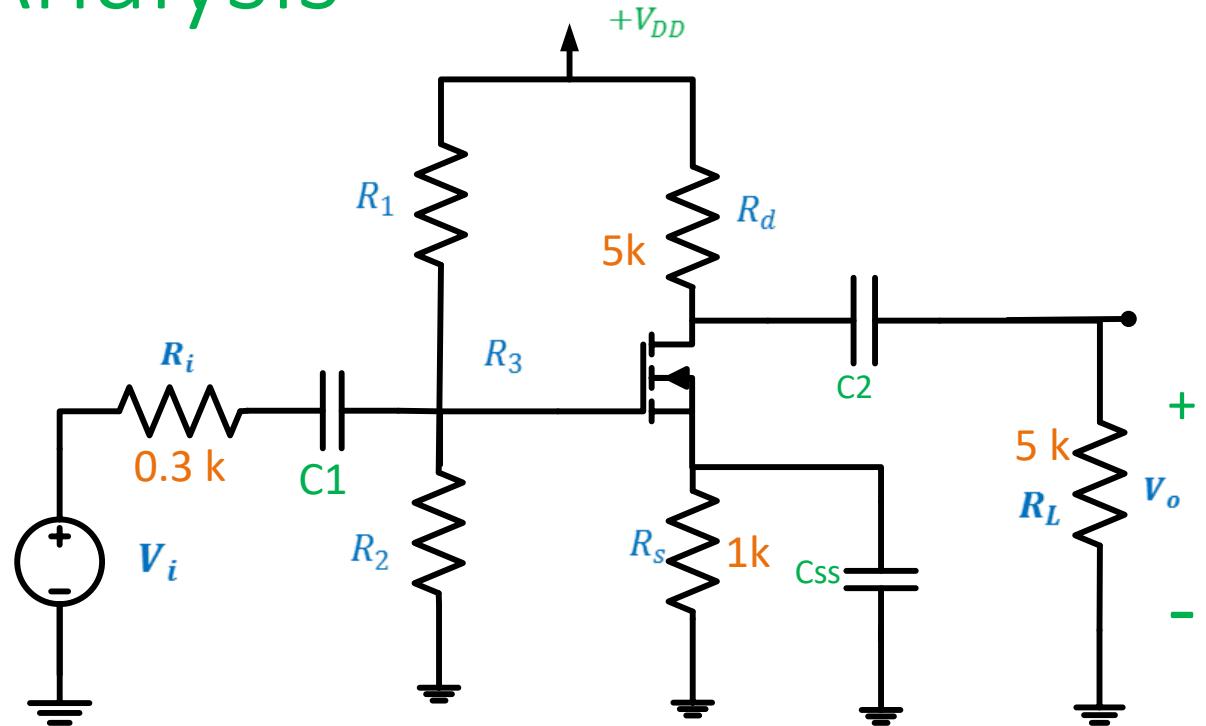

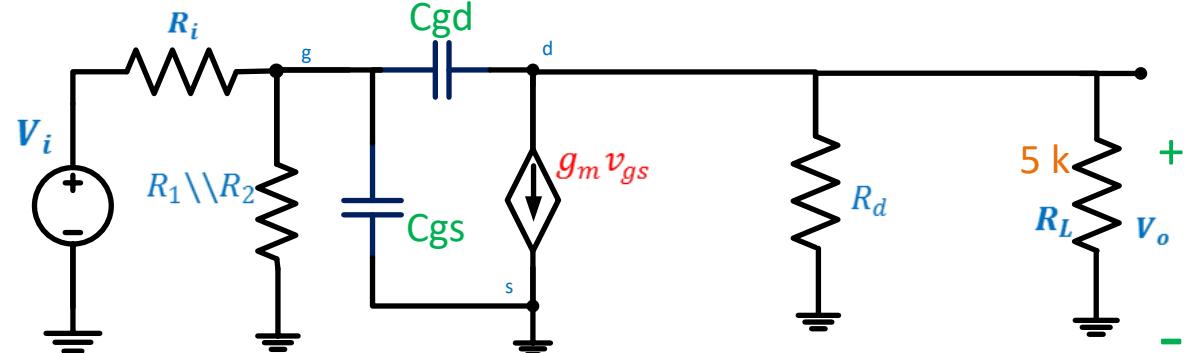Ac small signal high-frequency equivalent C_{KT}





1) To find τ_{gs} ; set C_{gd} open circuit

$$\tau_{gs} = C_{gs} R_{gs}$$

$$R_{gs} = R_i \parallel R_1 \parallel R_2$$

$$\therefore \tau_{gs} = 1.496 \text{ ns}$$
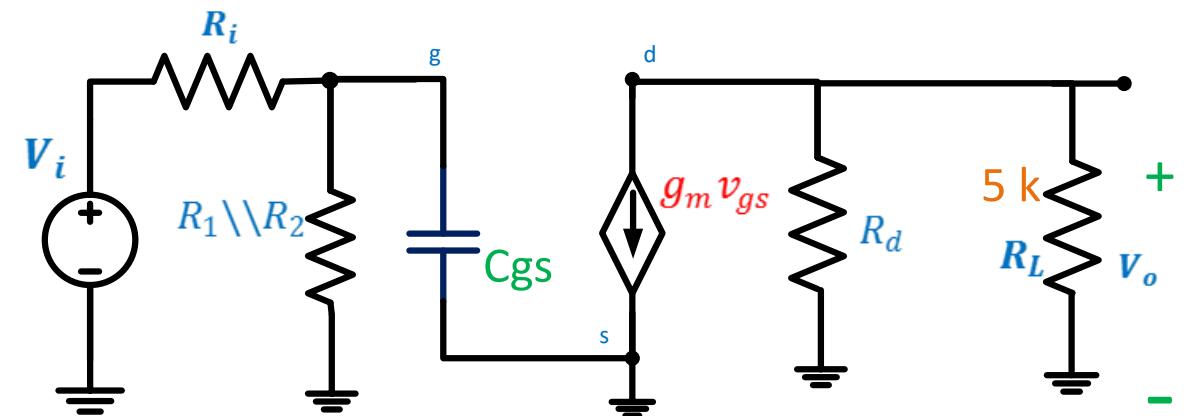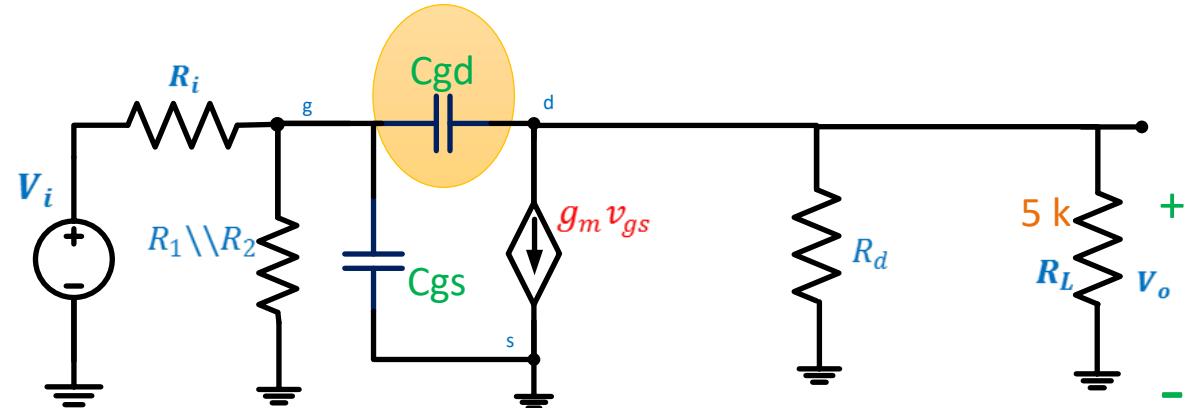
$$\therefore \omega_{gs} = \frac{1}{\tau_{gs}} = 668.45 \text{ Mr/s}$$



2) To find τ_{gd} ; set C_{gs} open circuit

$$\tau_{gd} = C_{gd} R_{gd}$$

To find R_{gd}

$$R_L^- (I_T + g_m V_{gs}) + R_s^- I_T = V_T$$




$$V_{gs} = V_g - V_s = V_g = R_s^- I_T$$

$$\therefore \frac{V_T}{I_T} = R_s^- + R_L^- + g_m R_L^- R_s^- = R_{gd}$$


$$\tau_{gd} = C_{gd} R_{gd}$$

$$\tau_{gd} = 20.6 \text{ ns}$$
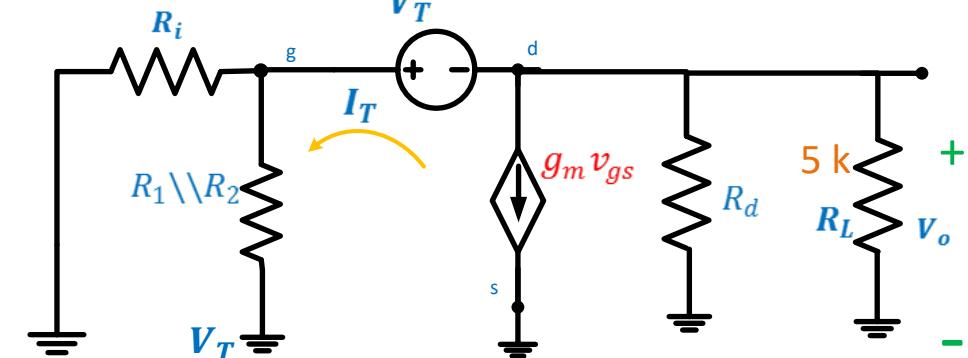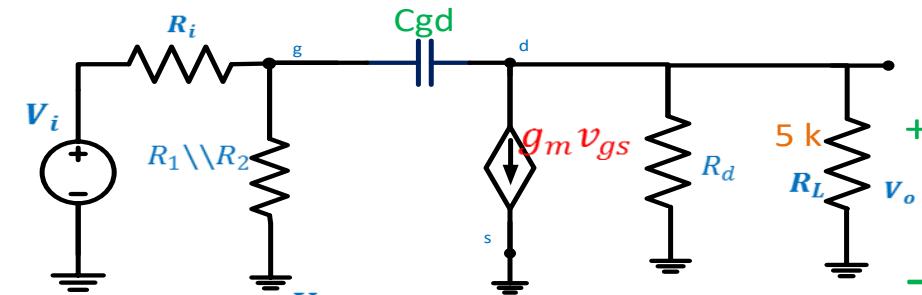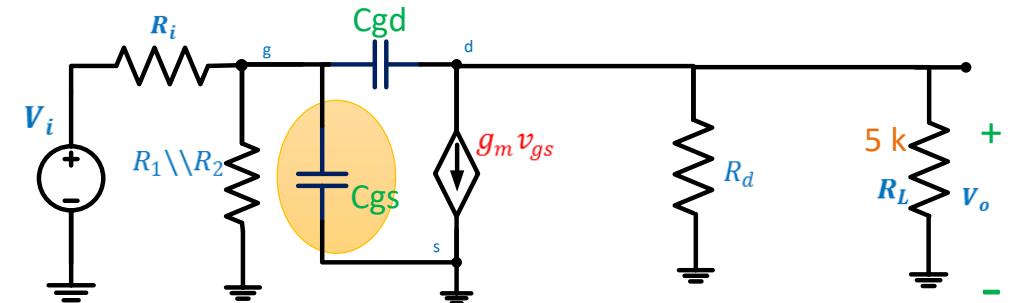
$$\therefore \omega_{gd} = 48.54 M \text{ r/s}$$


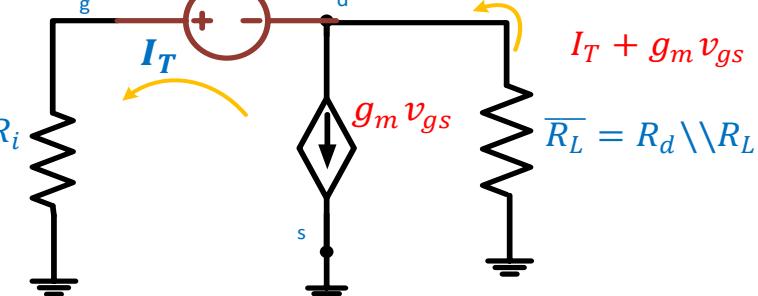
$$\overline{R_S} = R_1 \parallel R_2 \parallel R_i$$



$$\overline{R_L} = R_d \parallel R_L$$

$$\frac{1}{\tau_{gd} + \tau_{gs}} < \omega_H < 48.54 \text{ Mr/s}$$

$$\therefore \omega_{gd} = 48.54 \text{ Mr/s}$$

$$45.3 \text{ Mr/s} < \omega_H < 48.54 \text{ Mr/s}$$

$$\omega_H \equiv 48.4 \text{ Mr/s}$$

$$\therefore \omega_{gs} = \frac{1}{\tau_{gs}} = 668.45 \text{ Mr/s}$$

$$\tau_{gd} = 20.6 \text{ ns} ; \tau_{gs} = 1.496 \text{ ns}$$

\therefore To increase the bandwidth, we must decrease τ_{gd}

$$\tau_{gd} = C_{gd}R_L^- + C_{gd}R_s^- + C_{gd}g_m R_L^- R_s^-$$

$$\tau_{gd} = 5 \text{ ns} + 0.6 \text{ ns} + 15 \text{ ns} = 20.6 \text{ ns}$$

And to decrease τ_{gd} ; we need to decrease $g_m R_L^- \approx A_{v(mid)}$

Thus increasing bandwidth is usually achieved by reducing the midband gain

\therefore The product of gain and bandwidth tends to be constant.


2) Common gate amplifier

$$R_i = 0.3k, R_1 \parallel R_2 = 100k, R_d = R_L = 5k$$


$$R_s = 1k, g_m = 10 m\Omega$$

$$C_{gd} = 2 pF \text{ and } C_{gs} = 5 pF$$

Estimate ω_H

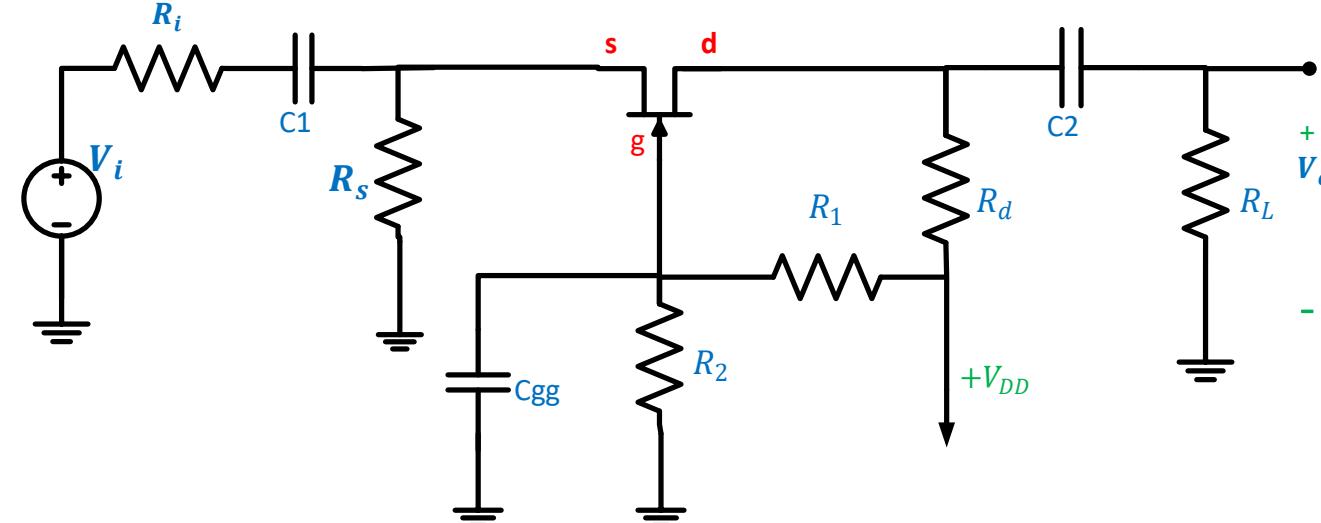

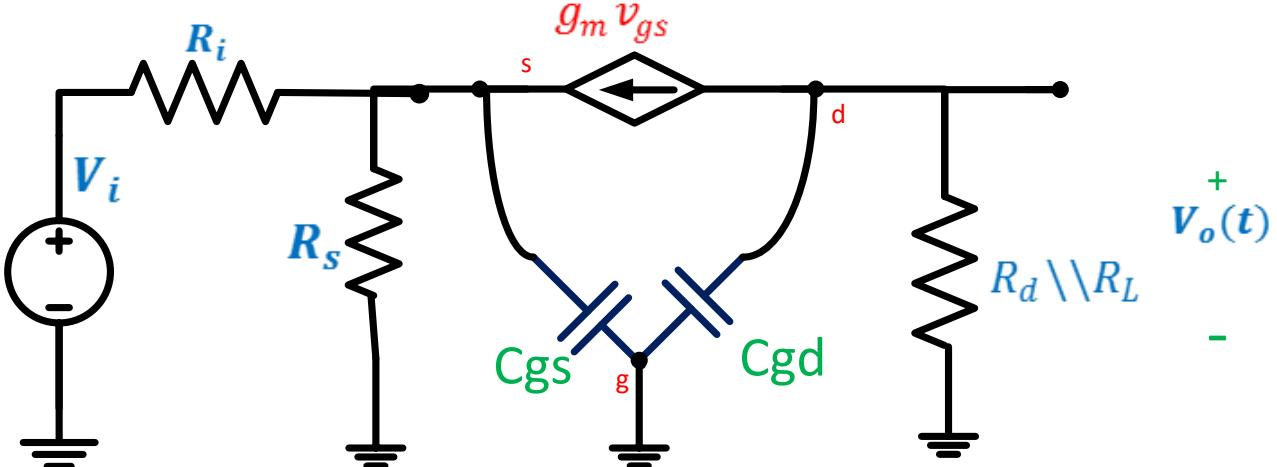Ac small signal high-frequency equivalent C_{KT}




1) To find τ_{gs} ; set C_{gd} open circuit

$$\tau_{gs} = C_{gs} R_{gs}$$

$$R_{gs} = R_s \parallel R_i \parallel \frac{1}{g_m}$$

$$\therefore \tau_{gs} = 0.349 \text{ ns}$$
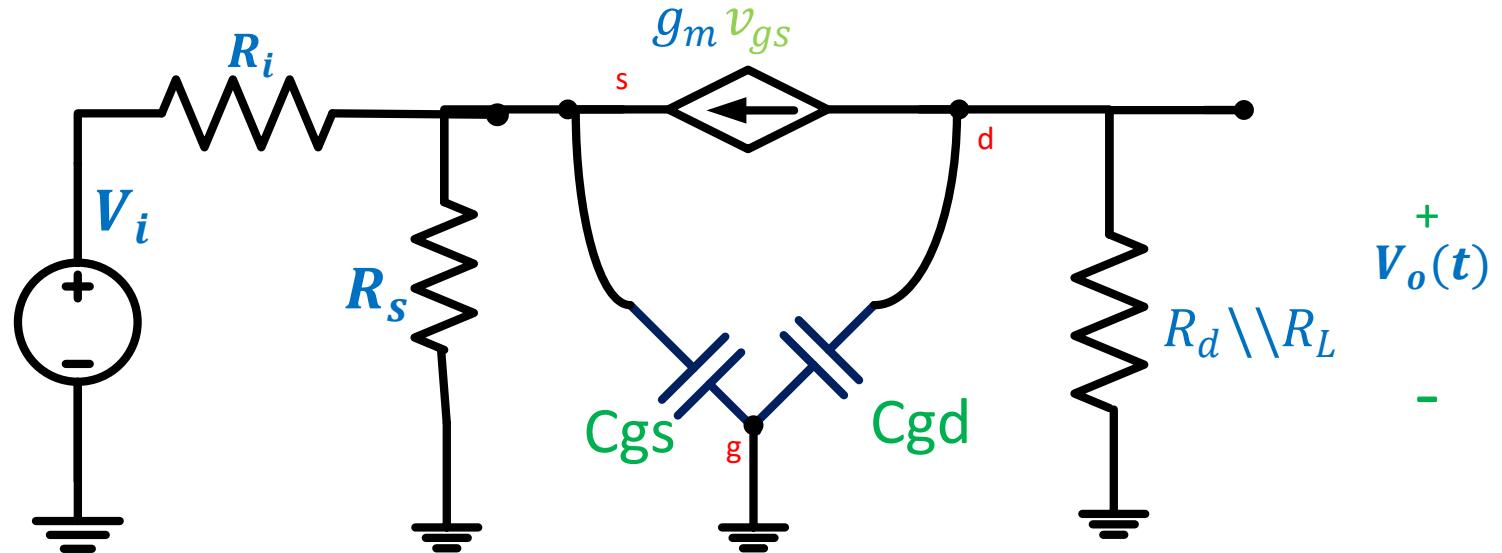
$$\therefore \omega_{gs} = 2865 \text{ Mr/s}$$



2) To find τ_{gd} ; set C_{gs} open circuit

$$\tau_{gd} = C_{gd} R_{gd}$$

$$R_{gd} = R_L \parallel R_d$$

$$\therefore \tau_{gd} = 5 \text{ ns}$$

$$\therefore \omega_{gs} = 200 \text{ Mr/s}$$

$$\frac{1}{\tau_{gd} + \tau_{gs}} < \omega_H < 200 \text{ Mr/s}$$

$$187 \text{ Mr/s} < \omega_H < 200 \text{ Mr/s}$$



BJT small signal high-frequency equivalent C_{KT}

1) Common Emitter and Common Collector



$$r_{bb}^- = (20\Omega - 200\Omega)$$

$$r_{cc}^- = r_{ee}^- = (1\Omega - 2\Omega) \rightarrow 0\Omega$$
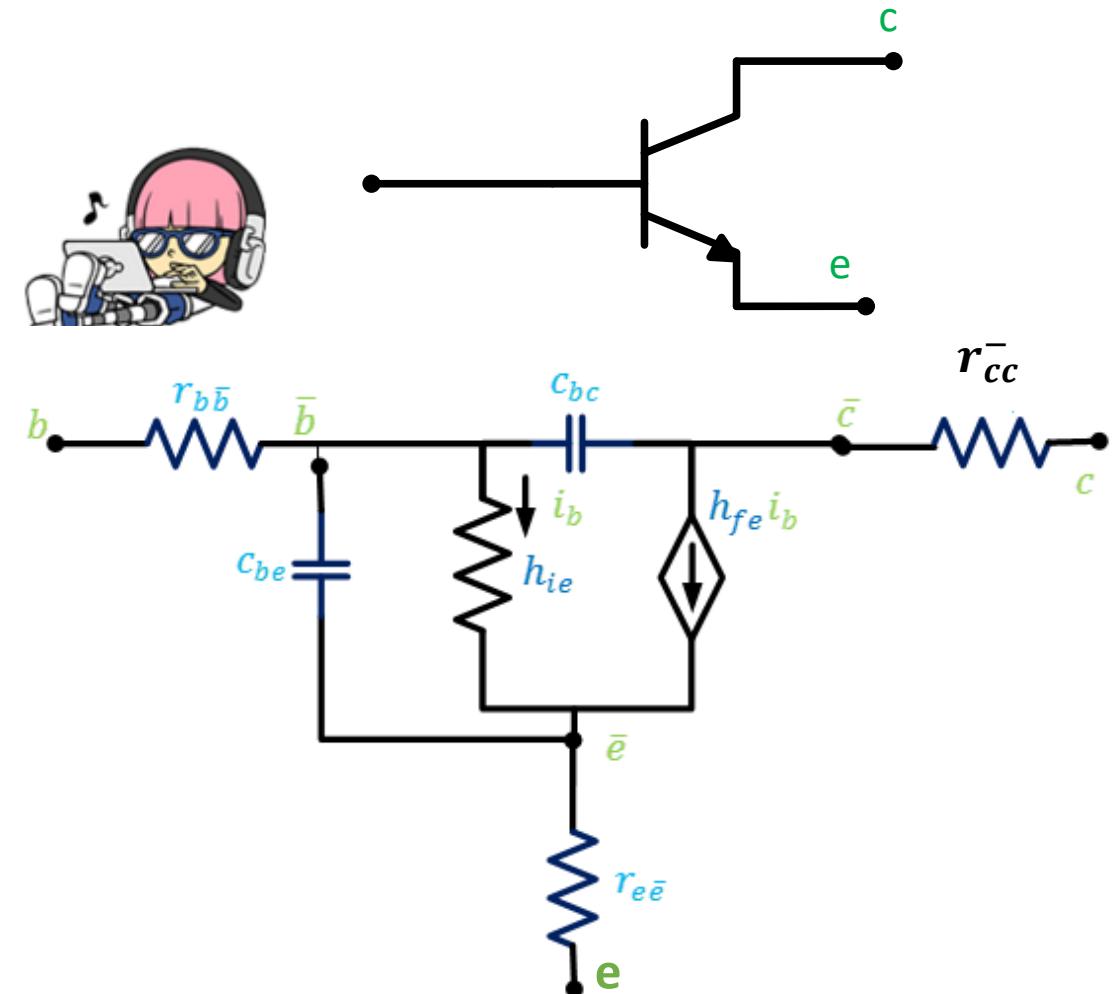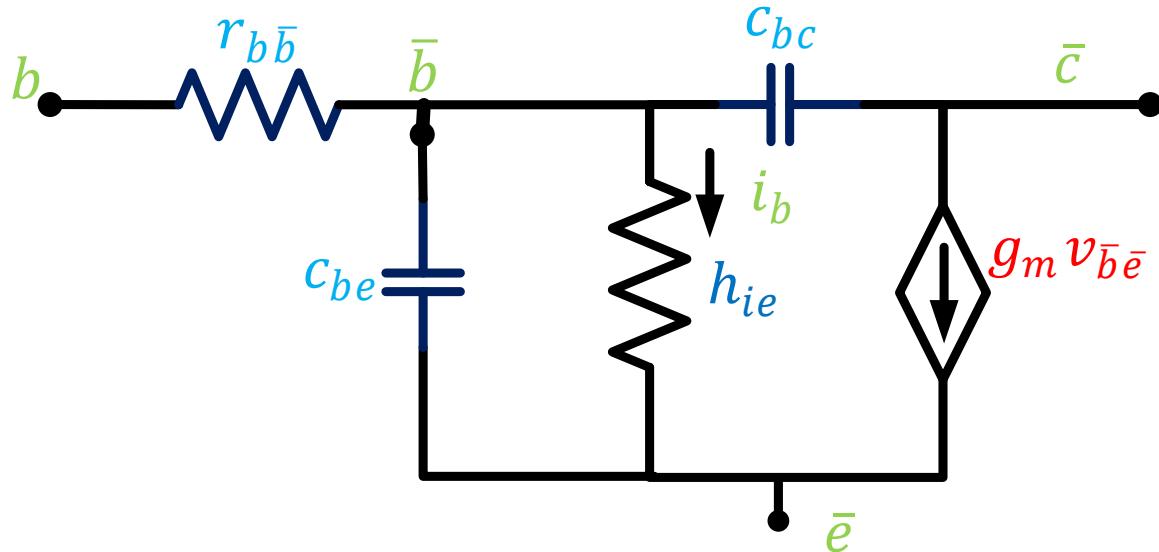
$$h_{fe} i_b = h_{fe} \frac{v_{b\bar{e}}}{h_{ie}} = \frac{h_{fe}}{h_{ie}} v_{b\bar{e}} = g_m v_{b\bar{e}}$$



2) Common Base

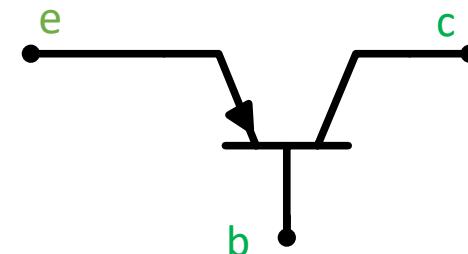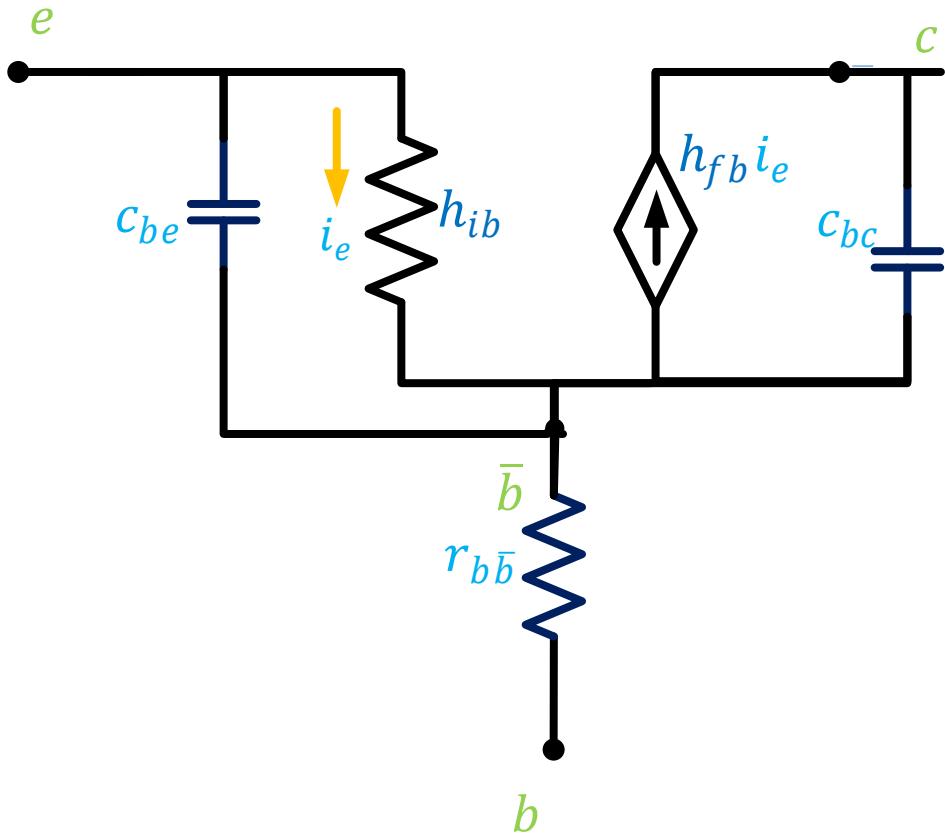


Common Emitter Amplifier High-Frequency Analysis

$$g_m = 33.5 \text{ mV/V}, h_{ie} = 8.78k$$


$$R_1 \parallel R_2 = 16.67k \Omega, R_s = 1k \Omega, R_c = 5k \Omega$$

$$R_L = 2k \Omega, R_e = 1k \Omega, r_{bb}^- = 50\Omega$$
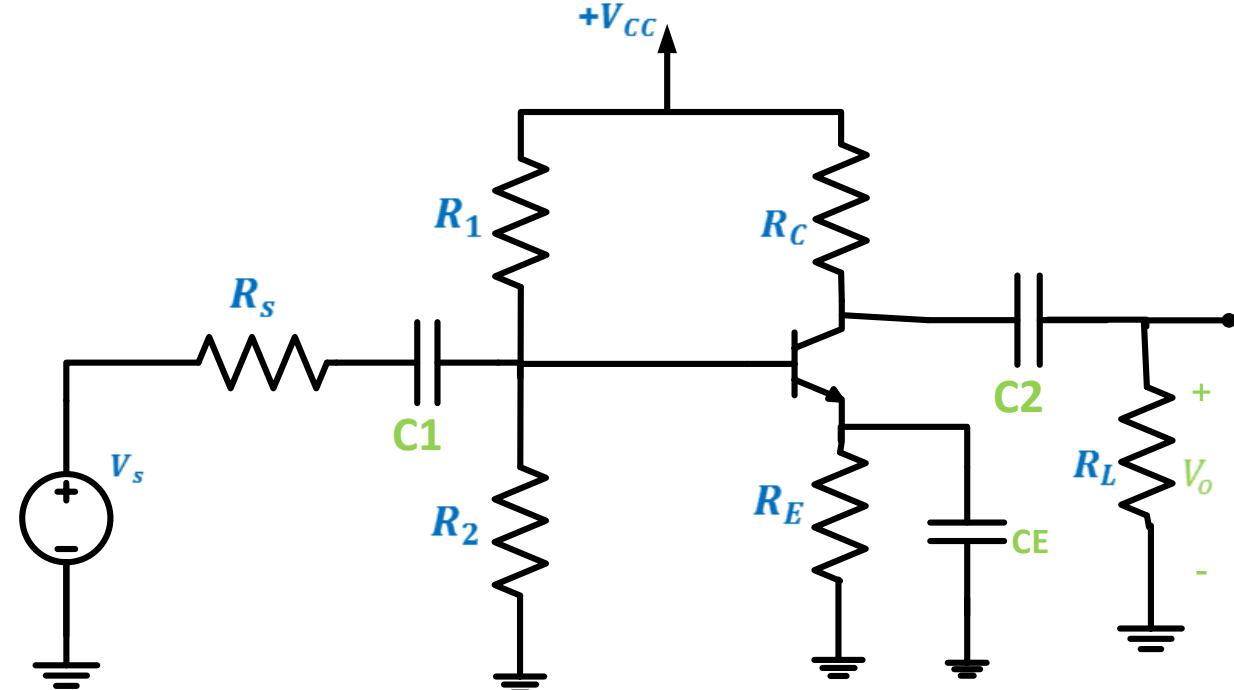
$$C_{be} = 17.25 \text{ pF}, \text{ and } C_{bc} = 1.8 \text{ pF}$$



Estimate ω_H

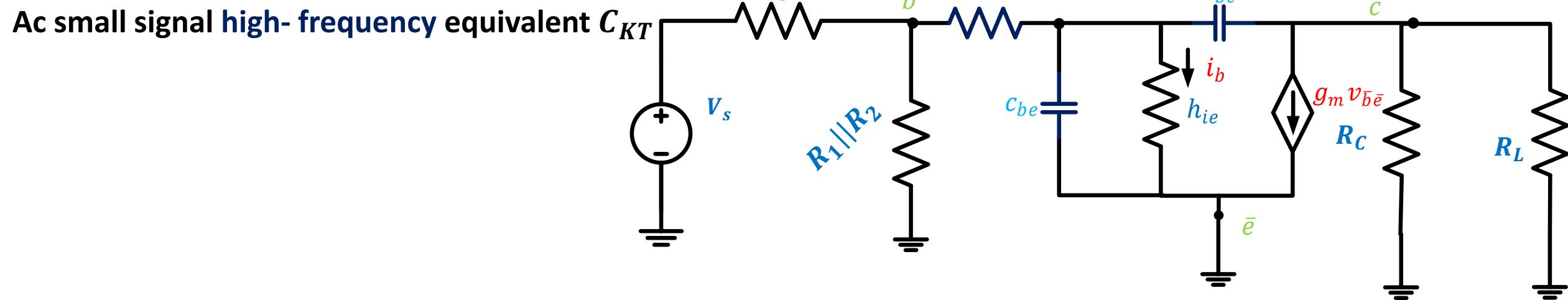


1) To find τ_{be} , set C_{bc} open circuit

$$\tau_{be} = C_{be} R_{be}$$

$$R_{be} = (R_s || R_1 || R_2 + r_{bb}) \parallel h_{ie}$$

$$\tau_{be} = 14.98 \text{ ns}$$

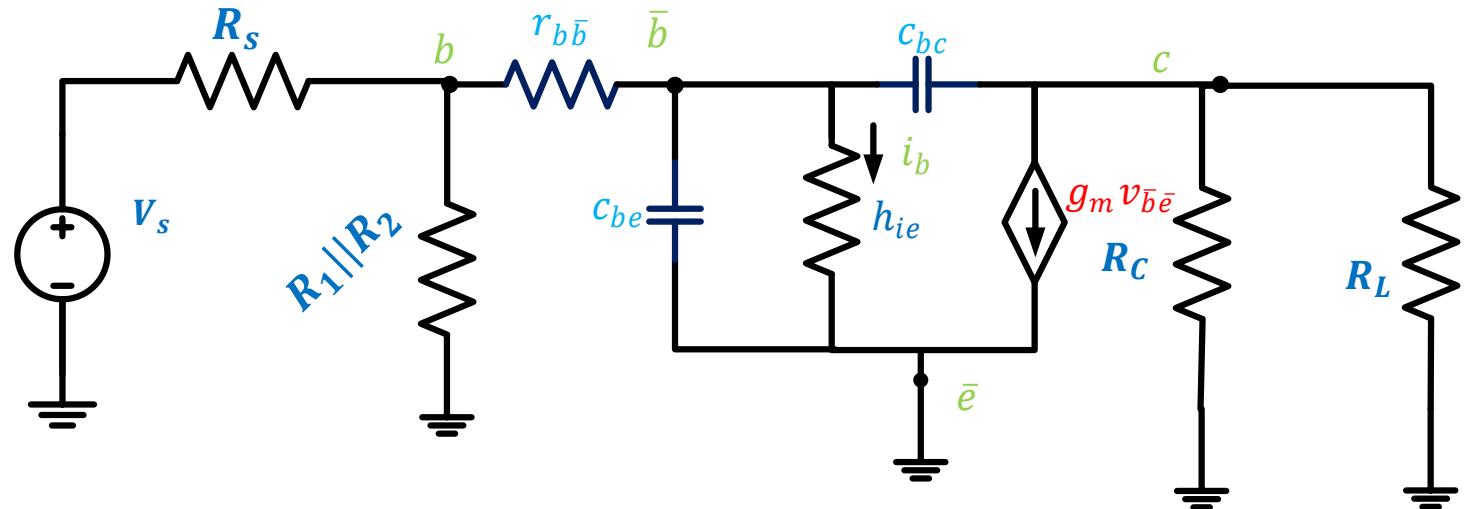
$$\therefore \omega_{be} = 66.76 \text{ Mr/s}$$



2) To find τ_{bc} , set C_{be} open circuit

$$\tau_{bc} = C_{bc} R_{bc}$$

To find R_{bc}

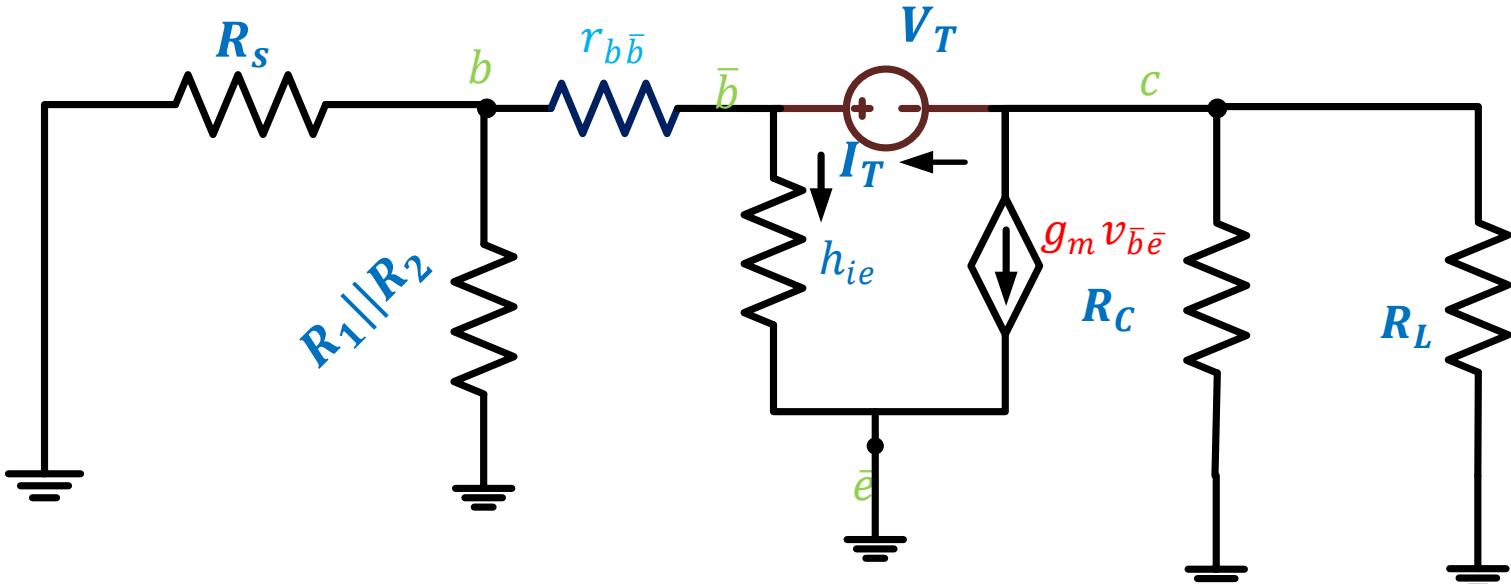


To find R_{bc}

$$R_s^- = \{(R_s || R_1 || R_2 + r_{bb})\} || h_{ie}$$

$$R_L^- \cdot (I_T + g_m v_{be}) + R_s^- I_T = V_T$$

$$v_{be} = R_s^- I_T$$

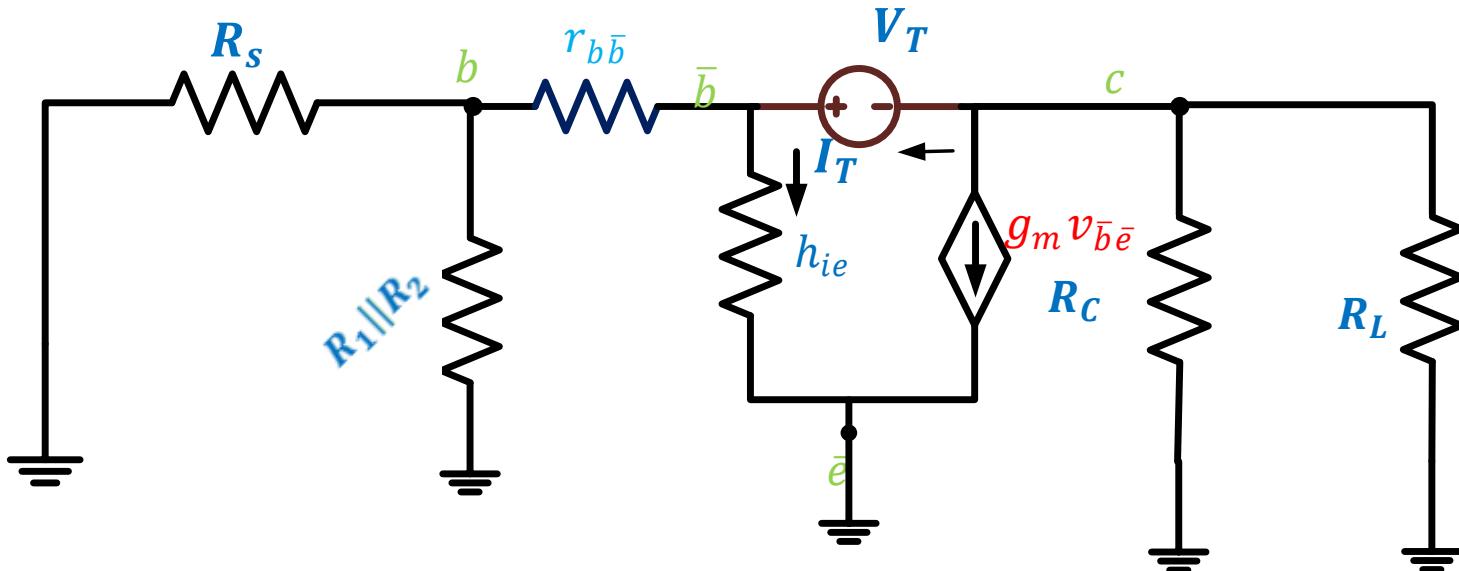

$$\therefore \frac{V_T}{I_T} = R_{bc} = R_s^- + R_L^- + g_m R_L^- R_s^-$$


$$\therefore \tau_{bc} = 78.9 \text{ ns}$$

$$\therefore \omega_{bc} = 12.67 \text{ Mr/s}$$

$$\frac{1}{\tau_{be} + \tau_{bc}} < \omega_H < 12.67 \text{ Mr/s}$$

$$10.65 \text{ Mr/s} < \omega_H < 12.67 \text{ Mr/s}$$

$$\omega_H \equiv 10.7 \text{ Mr/s}$$

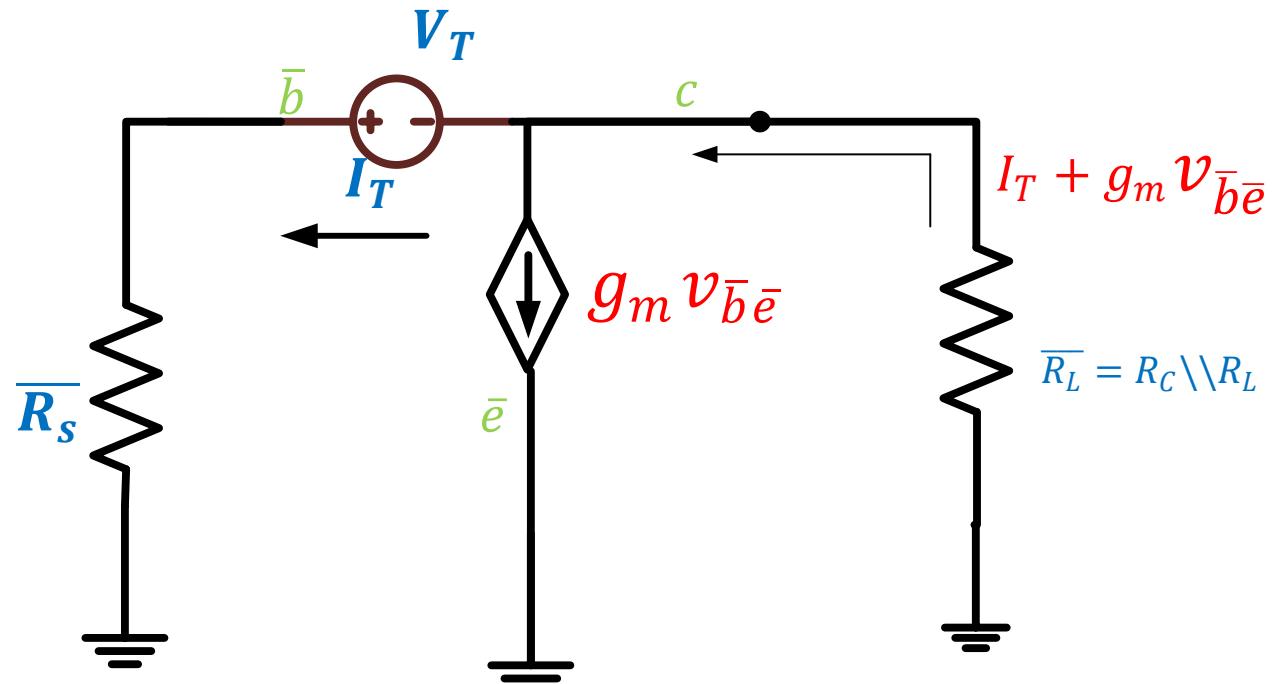

$$\omega_{be} = 66.76 \text{ Mr/s}$$


Common base amplifier

$$R_s = 0.1k \Omega, R_e = 1k \Omega, R_c = 10k \Omega, R_L = 10k \Omega$$


$$R_1 \parallel R_2 = 16.67k \Omega, h_{ib} = 0.026k \Omega, r_{bb}^{-} = 0$$

$$C_{be} = 20 \text{ pF}, \text{ and } C_{bc} = 2 \text{ pF}$$

Estimate ω_H

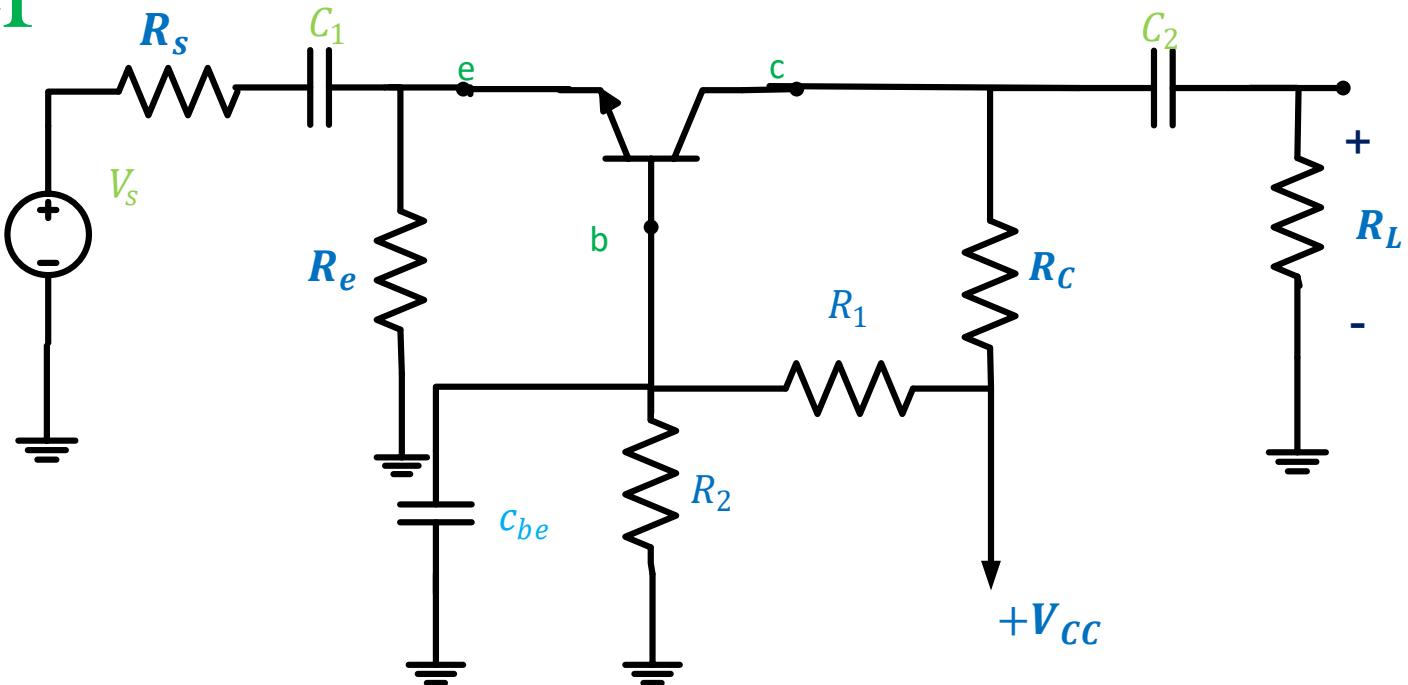

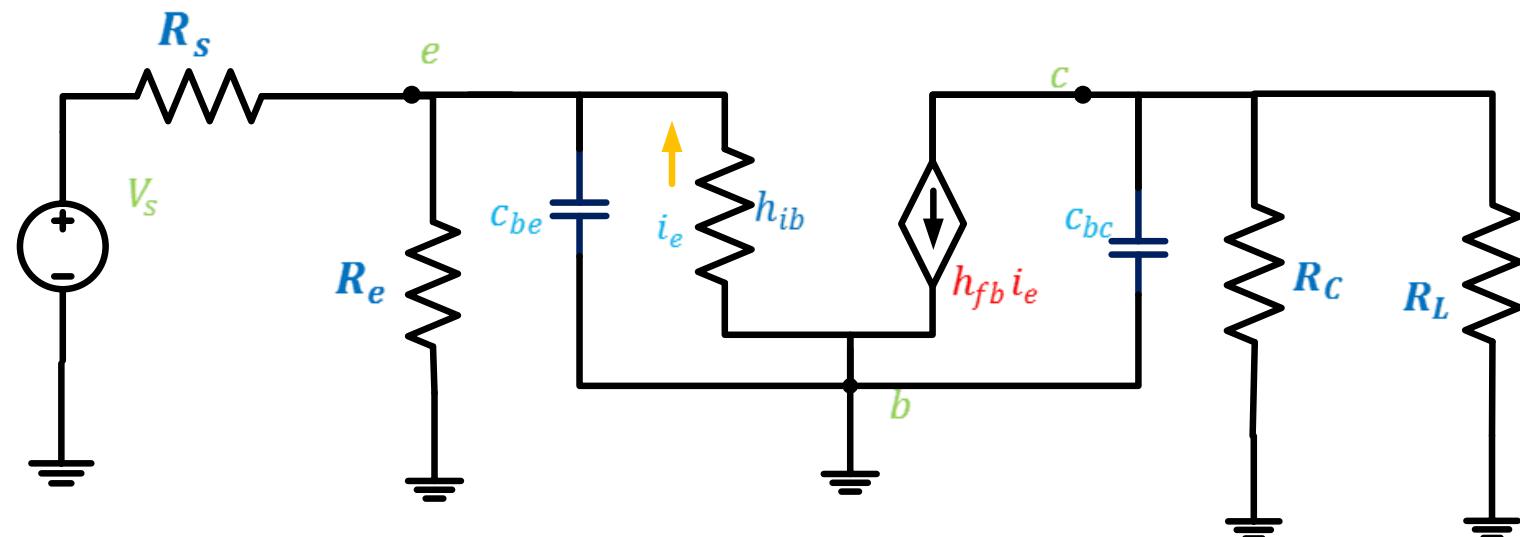Ac small signal high-frequency equivalent C_{KT}



1) To find τ_{be} , set C_{bc} open circuit

$$\tau_{be} = C_{be} R_{be}$$

$$R_{be} = R_s \parallel R_e \parallel h_{ib}$$

$$\therefore \tau_{be} = 0.40797 \text{ ns}$$

$$\therefore \omega_{be} = 2451 \text{ Mr/s}$$



2) To find τ_{bc} , set C_{be} open circuit

$$\tau_{bc} = C_{bc} R_{bc}$$


$$R_{bc} = R_c \parallel R_L$$

$$\therefore \tau_{bc} = 10 \text{ ns}$$

$$\therefore \omega_{be} = 100 \text{ Mr/s}$$

$$96.1 \text{ Mr/s} < W_H < 100 \text{ Mr/s}$$



$$\omega_H \equiv 99.8 \text{ Mr/s}$$

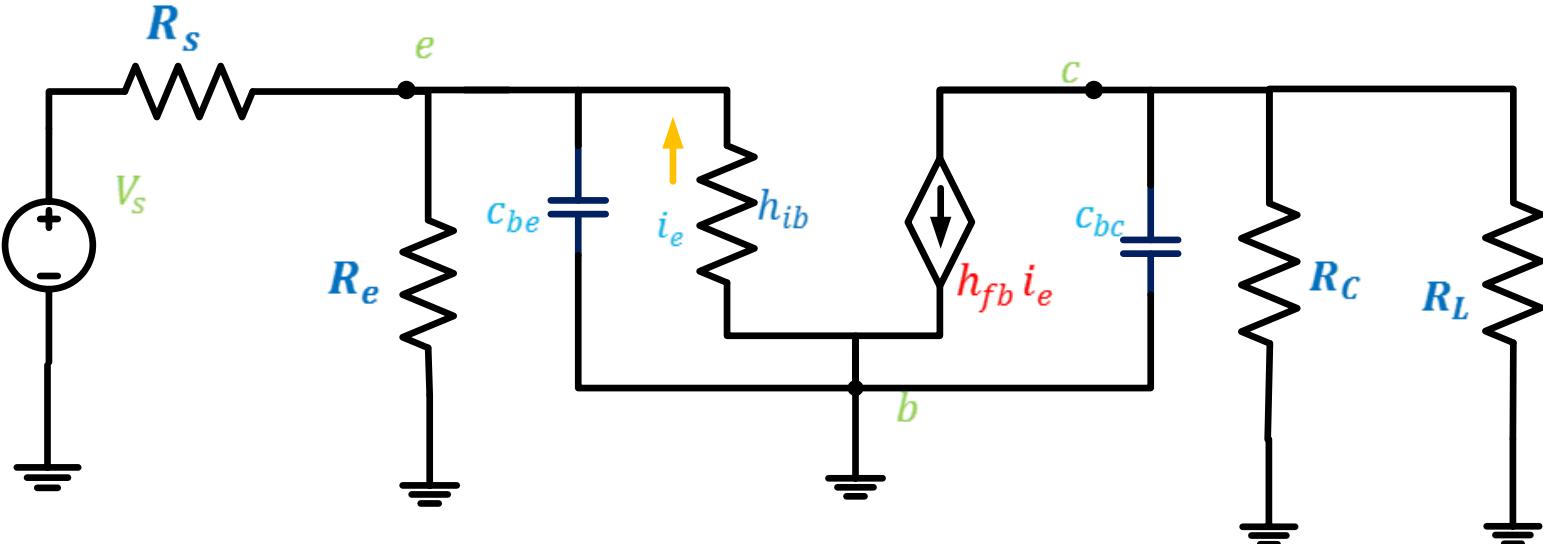

Miller Effect Capacitor

$$C_{im} = C(1 - A_{v(mid)})$$
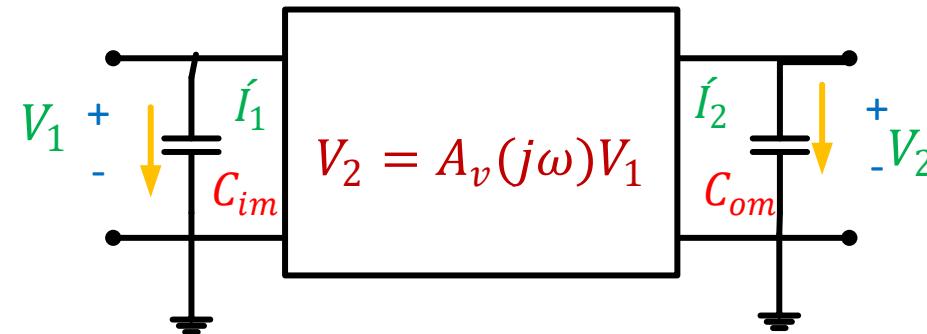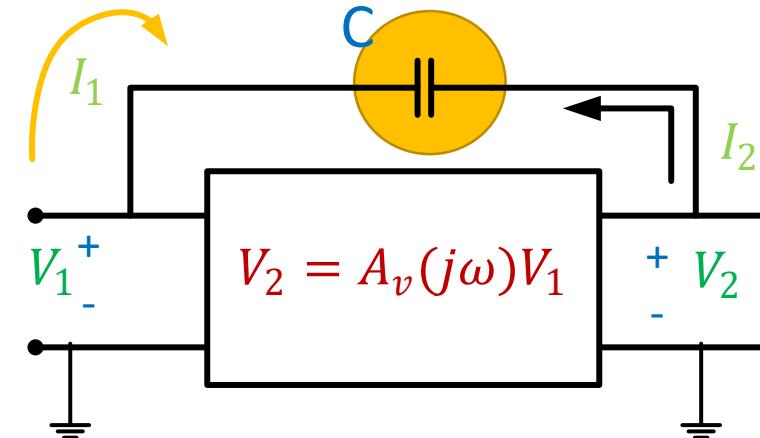
$$C_{om} = C \left(\frac{A_{v(mid)} - 1}{A_{v(mid)}} \right)$$



Miller Effect Capacitor

$$I_1 = \frac{V_1 - V_2}{j\omega C} = j\omega c(V_1 - V_2)$$



$$I_1 = j\omega c(V_1 - A_{v(jw)}V_1)$$

$$I_1 = j\omega cV_1(1 - A_{v(jw)})$$



$$I_1 \approx j\omega cV_1(1 - A_{v(mid)})$$

But $I_1^- = j\omega C_{im}V_1$

For the two circuit to be equivalent

$$I_1 = I_1^-$$
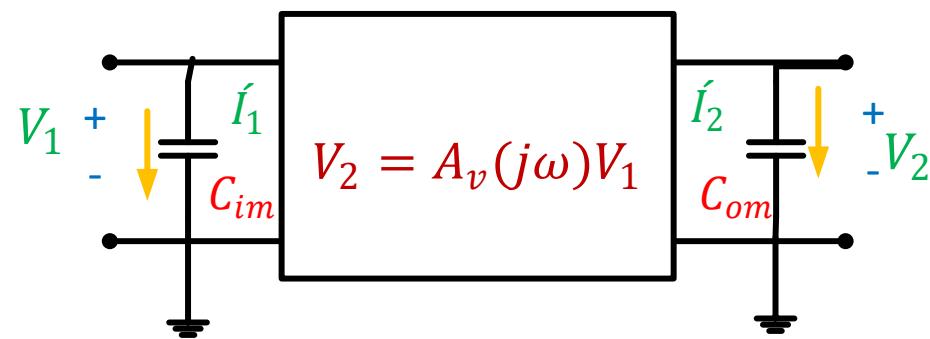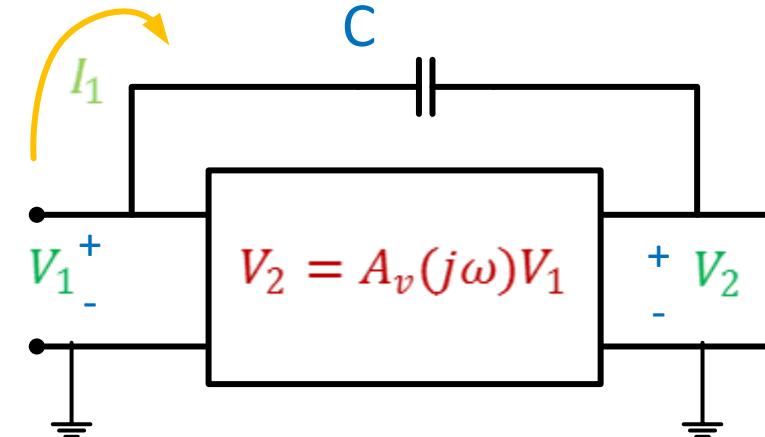
$$\therefore C_{im} = C(1 - A_{v(mid)})$$



Miller Effect Capacitor

$$I_2 = j\omega c(V_2 - V_1)$$



$$I_2 = j\omega c(V_2 - \frac{V_2}{A_{v(j\omega)}})$$

$$I_2 = j\omega cV_2(1 - \frac{1}{A_{v(j\omega)}})$$

$$I_2 \cong j\omega cV_2(\frac{A_{v(mid)} - 1}{A_{v(mid)}})$$

But $I_2^- = j\omega C_{om}V_2$
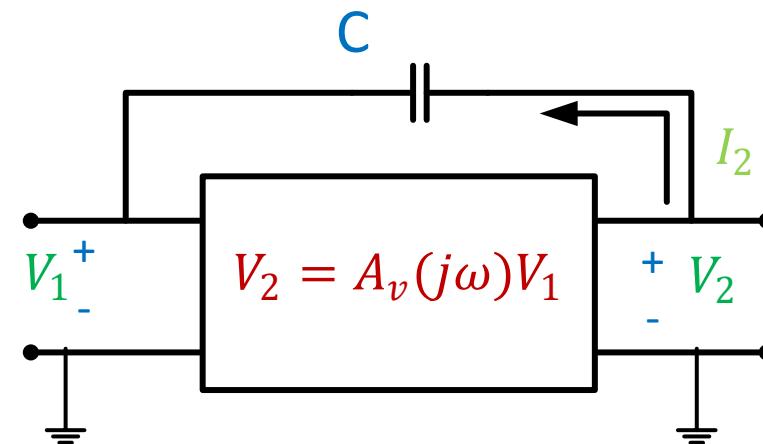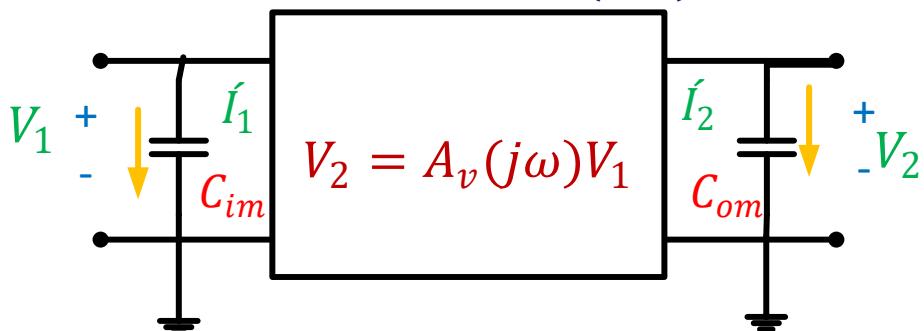
$$\therefore C_{om} = C \left(\frac{A_{v(mid)} - 1}{A_{v(mid)}} \right)$$




If $|A_{v(mid)}| \gg 1$

$$C_{om} \cong C$$

Common Emitter High-Frequency Analysis




Using Miller-effect Capacitor

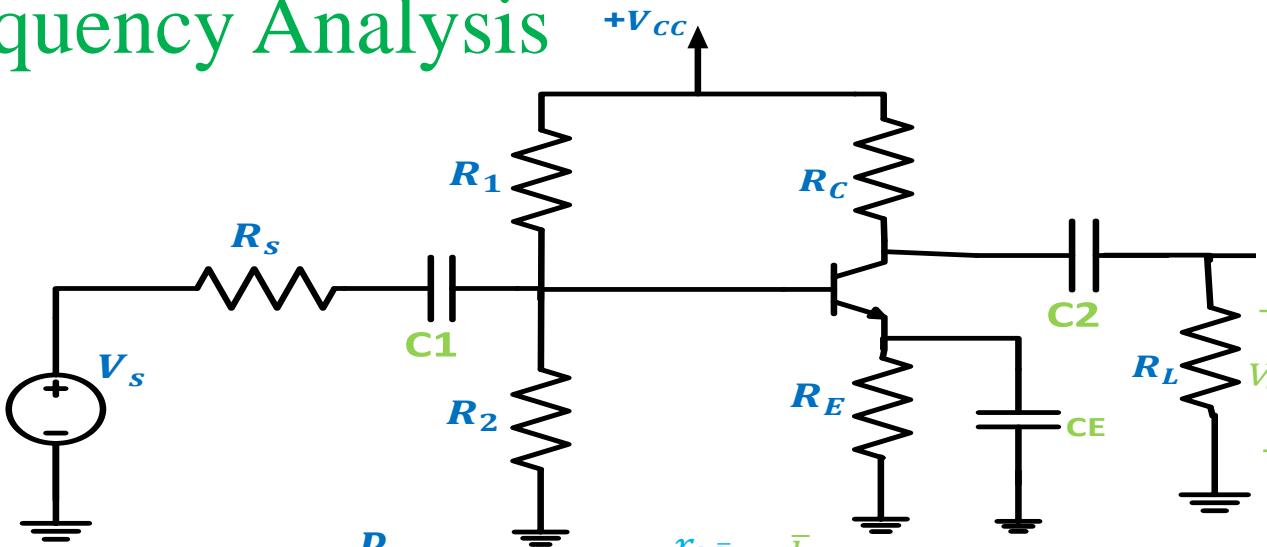

$$C_{im} = C_{bc}(1 - A_{v(mid)})$$

$$C_{iT} = C_{be} + C_{im}$$


$$C_{om} = C_{bc}$$

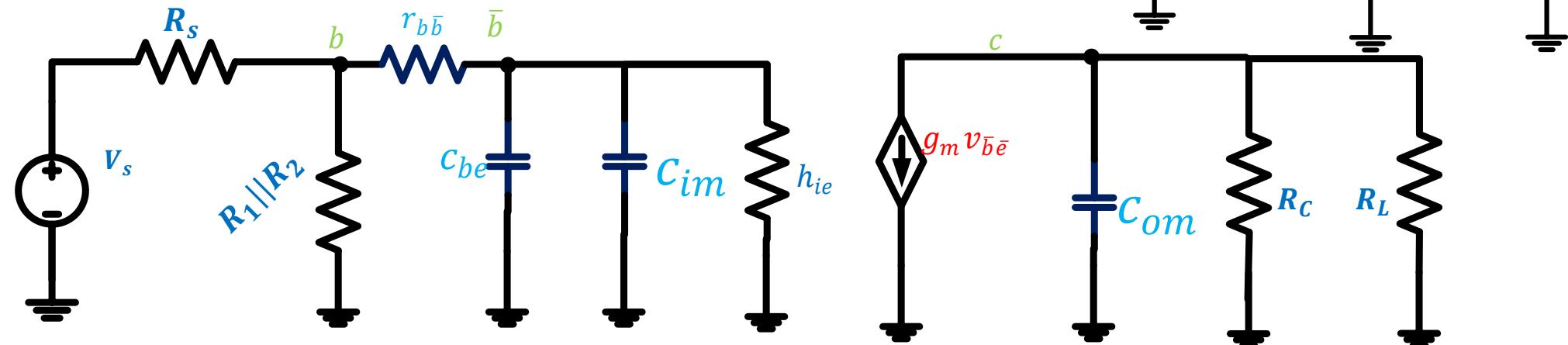

Common Emitter High-Frequency Analysis

To find τ_{CiT} , set C_{om} open

$$\tau_{CiT} = C_{iT} \cdot R_{TH_1}$$

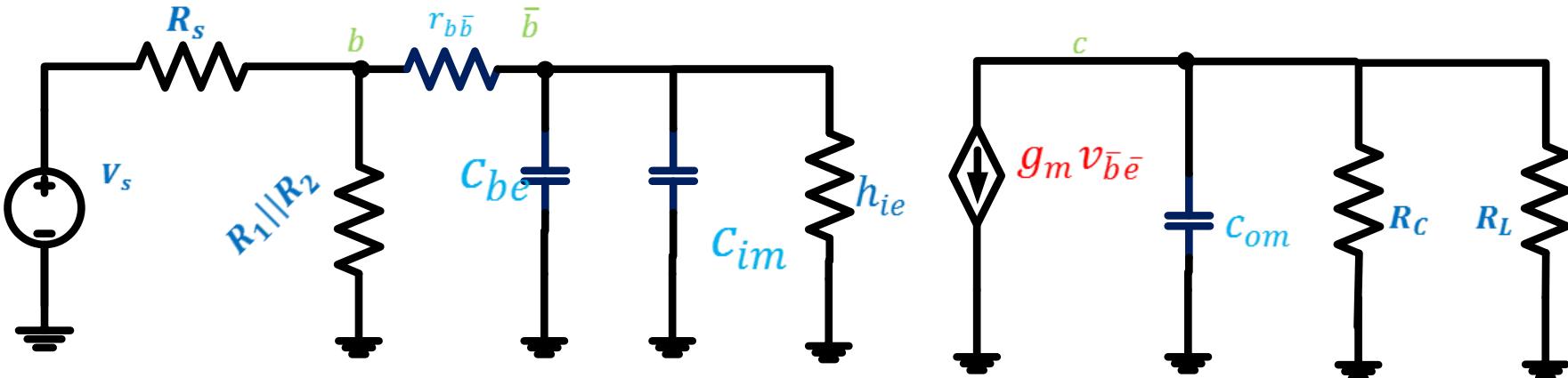

$$R_{TH_1} = h_{ie} || (r_{bb} + R_s || R_1 || R_2)$$

$$C_{iT} = C_{be} + C_{im}$$

$$C_{im} = C_{bc}(1 - A_{v(mid)})$$


$$A_{v(mid)} = -g_m(R_c || R_L)$$

$$\therefore C_{im} = 87.97 \text{ PF}$$


$$\therefore C_{iT} = 105.2 \text{ PF}$$

$$\therefore \tau_{CiT} = 91.3 \text{ ns}$$
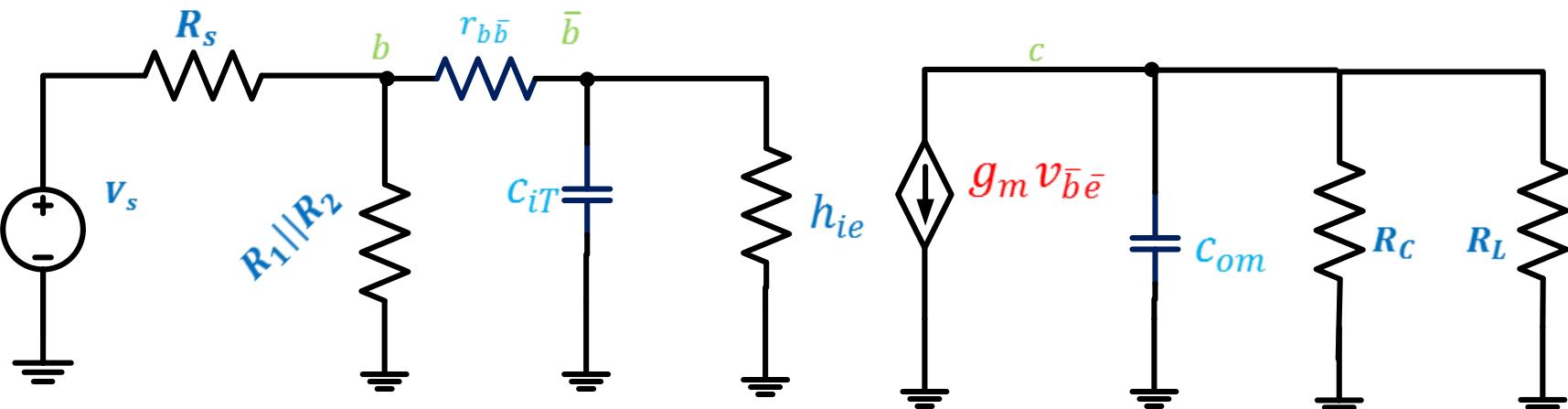
$$\therefore \omega_{CiT} = 10.95 \text{ Mr/s}$$



Common Emitter High-Frequency Analysis

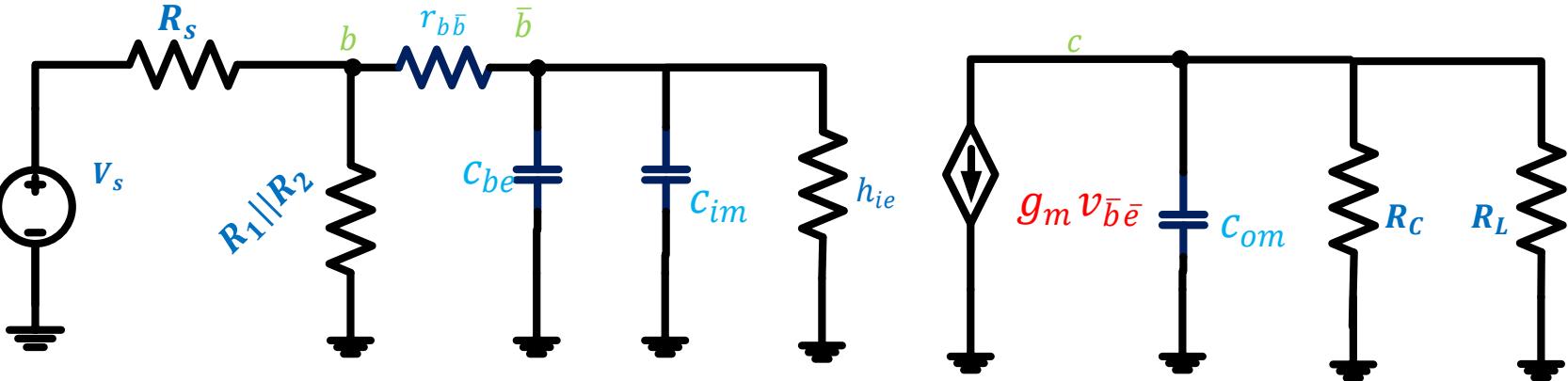


2) To find τ_{com} , set C_{IT} open

$$\tau_{com} = C_{om} R_{TH_2}$$

$$R_{TH_2} = R_c || R_L$$

$$\therefore \tau_{com} = 2.57 \text{ ns}$$

$$\omega_{com} = 388.9 \text{ Mr/s}$$

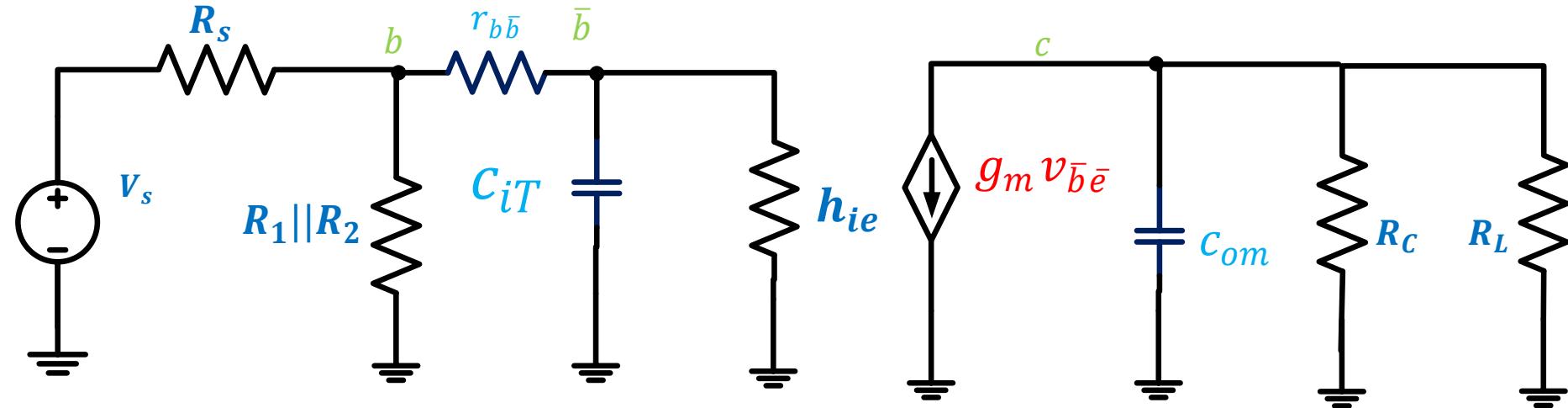

$$10.65M \text{ r/s} < W_H < 10.95 M\text{r/s}$$

$$\omega_H \equiv 10.7 \text{ Mr/s}$$

$$\therefore \omega_{C_{IT}} = 10.95 \text{ Mr/s}$$

The End