

# Thyristors and other Devices

## Thyristors


- Devices constructed of four semiconductor

### Layers

- They act as open circuits capable of withstanding a certain rated voltage until they are triggered

- When triggered, they turn on and become low-resistance current path, and remains on, even after the trigger is removed, until the current is reduced to a certain level or they are triggered off, depending on the type of the device
- Thyristors can be used to control the amount of ac power to a load
- They are used in lamp dimmers, motor speed controls and charging circuits.

# The Shockley Diode

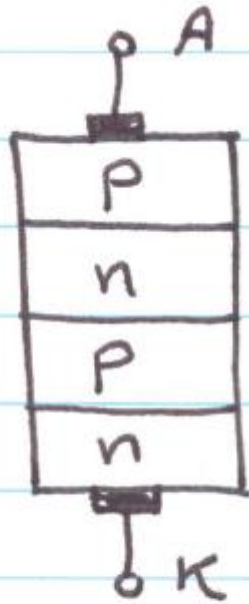

Basic  
Construction



Circuit  
Symbol




Equivalent  
Circuit


- The basic 4-layer device
- It is a two terminal device
- It acts as a switch

- It remain off until the forward voltage reaches a certain value ; then it turns on and conducts current.

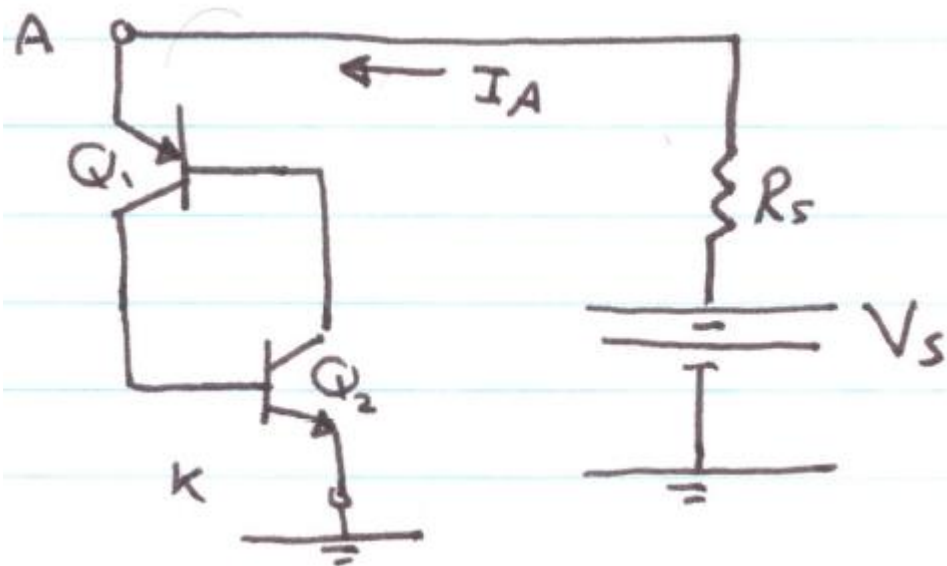- Conduction continue until the current is reduced below a specified value



# Characteristic Curve

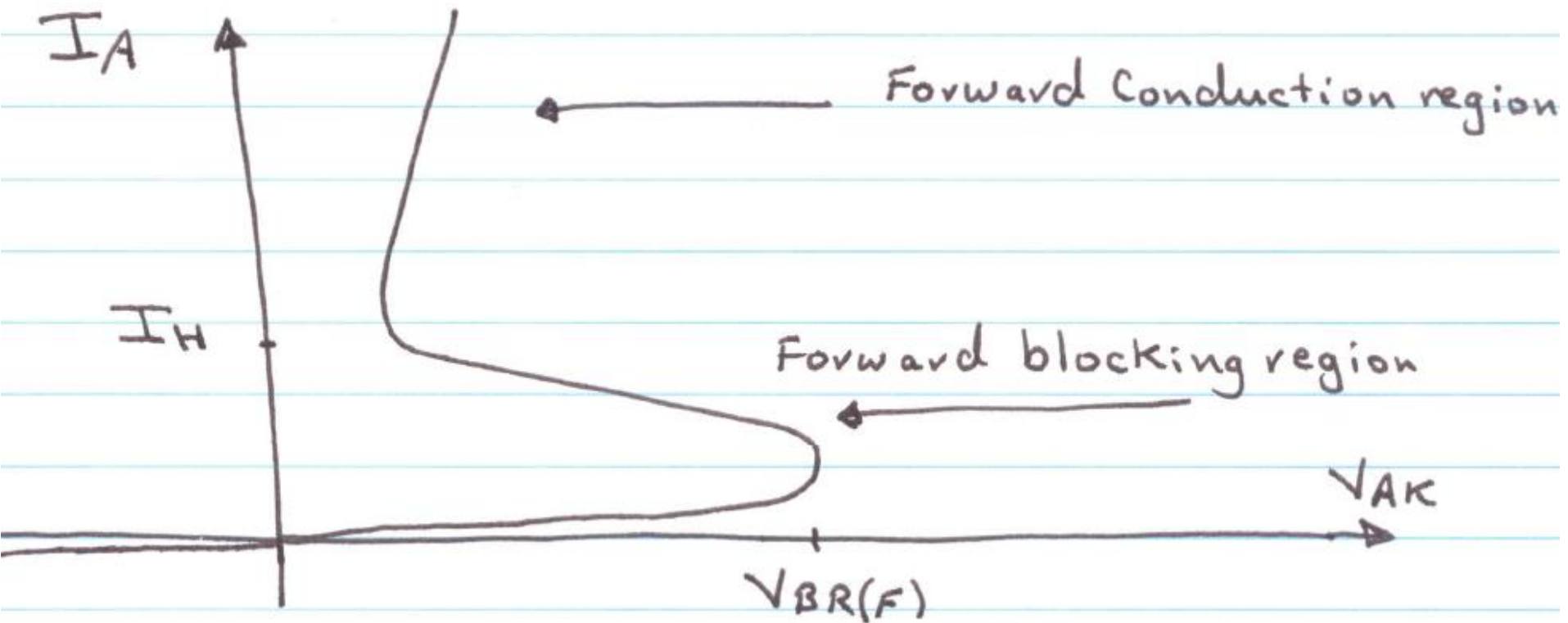


$V_{BR(F)} \equiv$  Forward breakover voltage

$I_H \equiv$  Holding Current


\* When  $V_s > V_{BR(F)}$ ; the device is in the on

state and acts as a closed switch

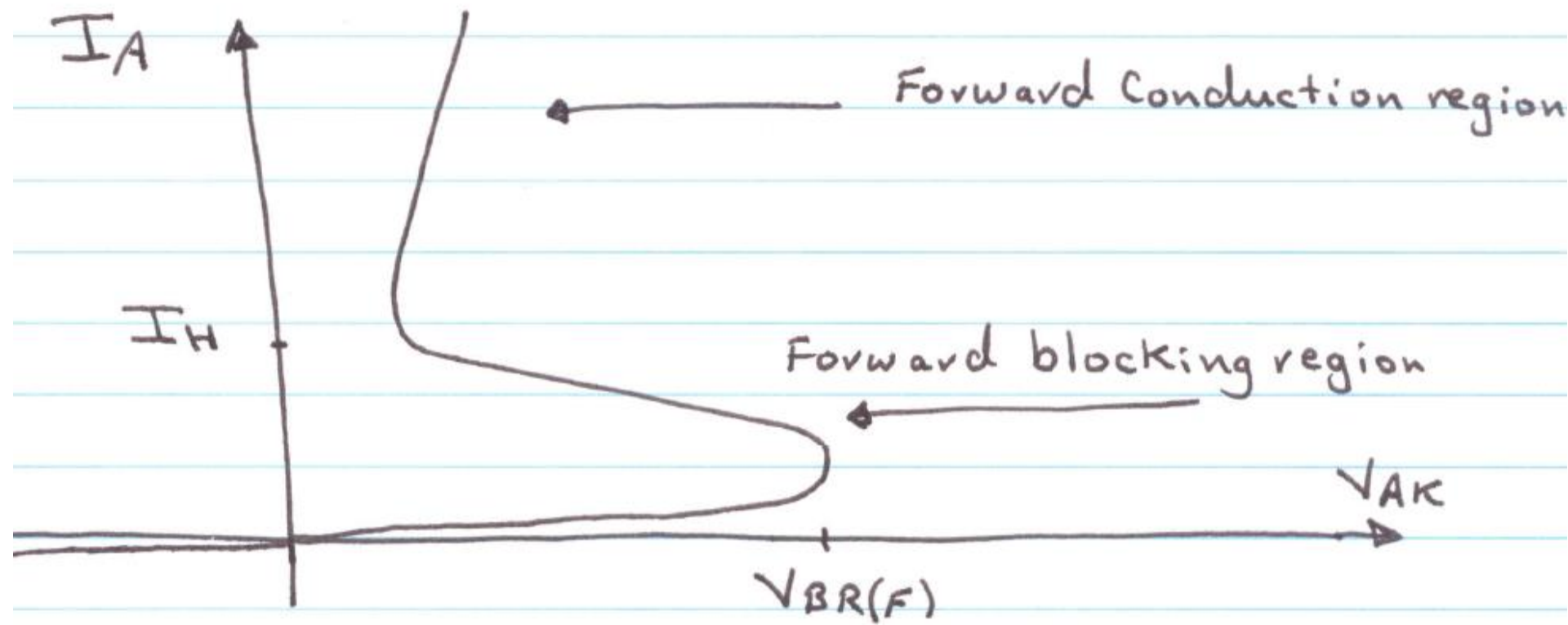

\* When the anode current  $I_A$  drops back below the holding value  $I_H$ , the device turns OFF (open circuit)

# Application : Relaxation Oscillator

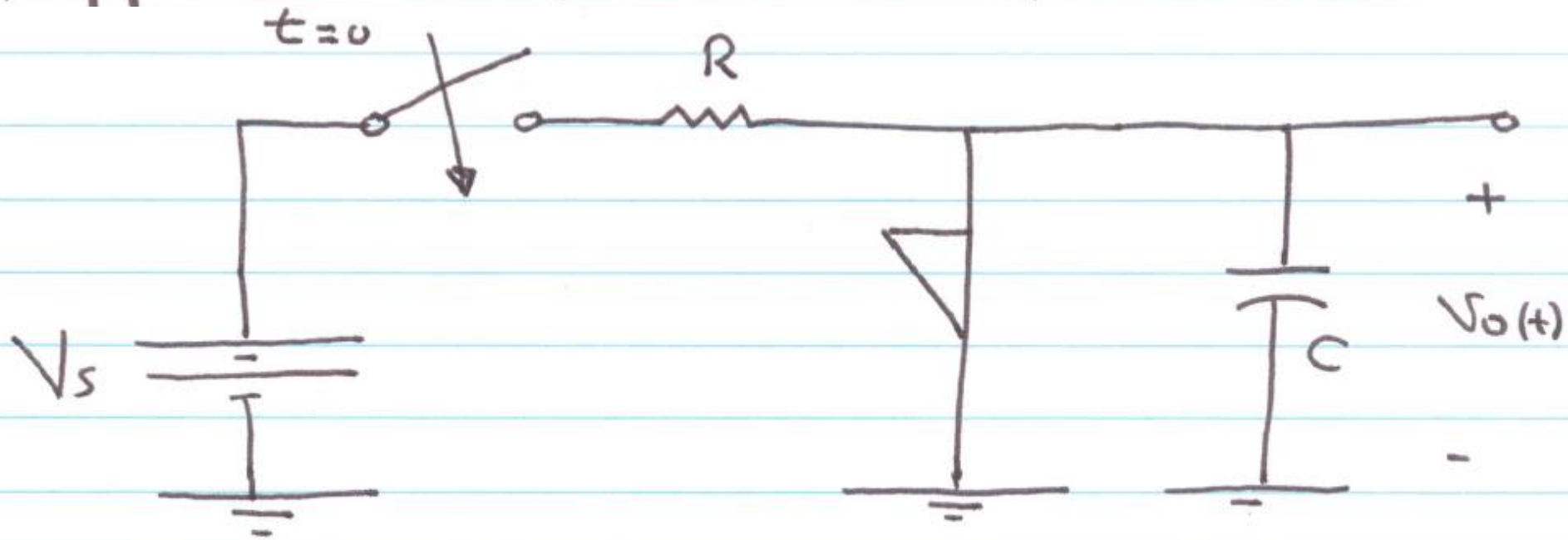


$$V_c(0) = 0$$

- At  $t = 0^+$ ,  $V_c(0^+) = V_{AK}(0^+) = 0$ ; the device

is OFF (open circuit)

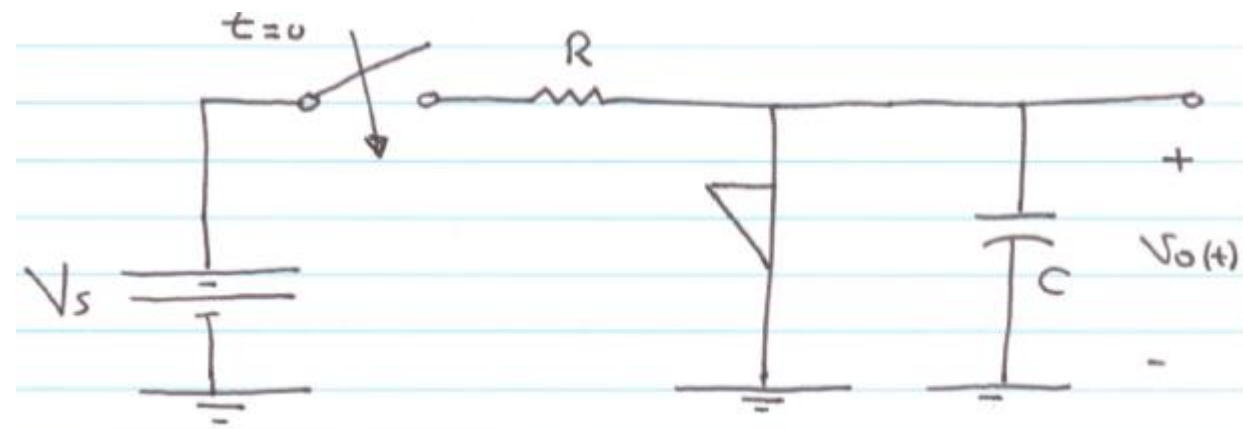
- The device switch into conduction (short circuit)



The Capacitor rapidly discharge through




the device until  $I_A < I_H$

The device switch back to the OFF state

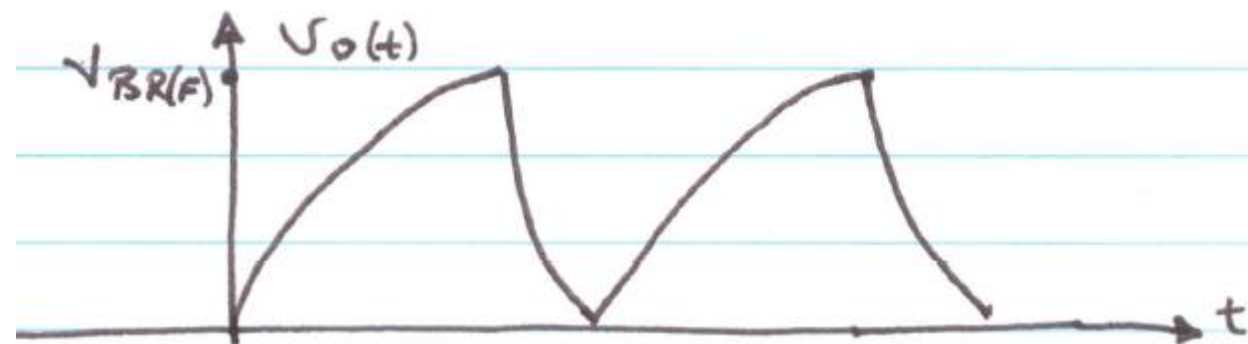



# The Silicon Controlled Rectifier . SCR

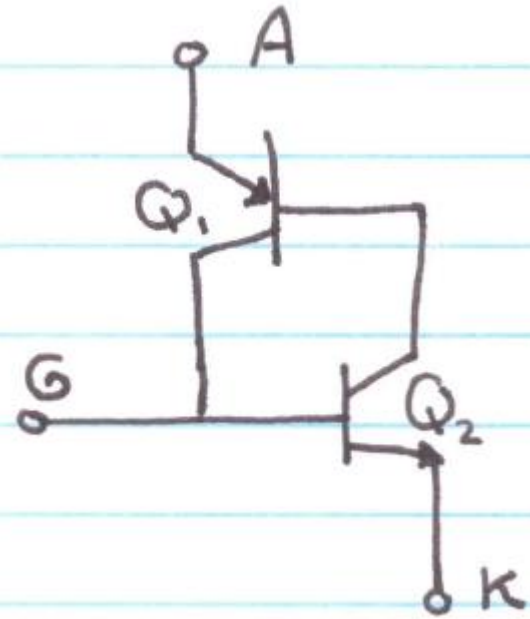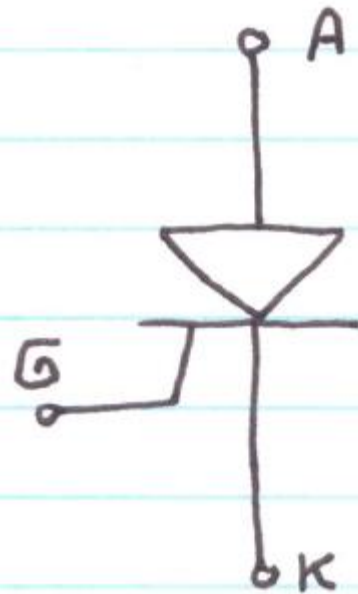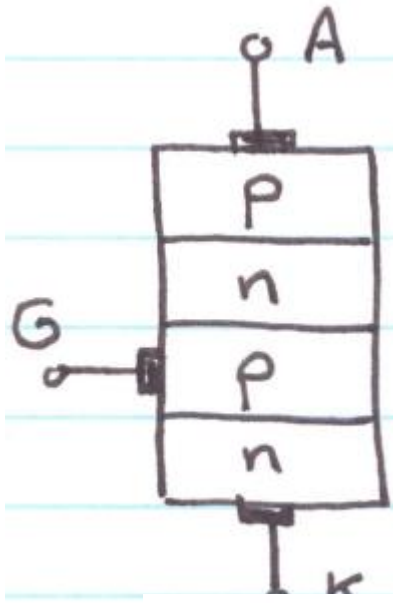

- It is a three terminal device





- It is four Layer pnpn device

- It acts as a switch

- In the off state ; it acts as an open circuit

between Anode and Cathode

# Turning the SCR On

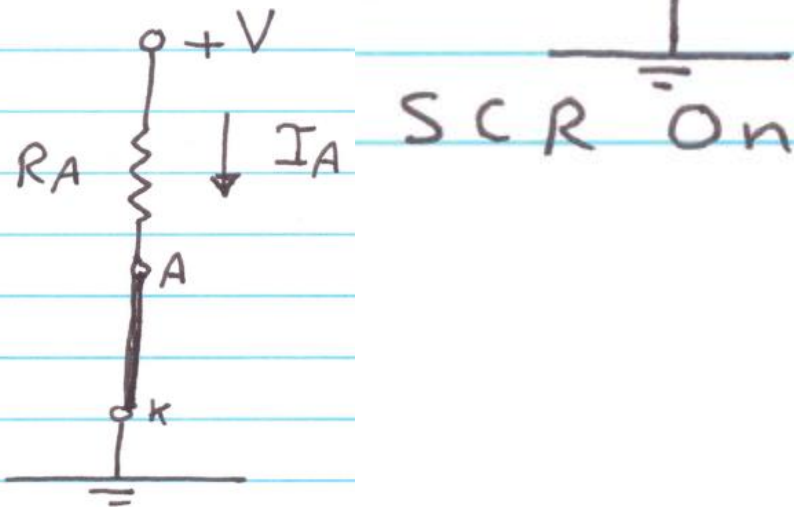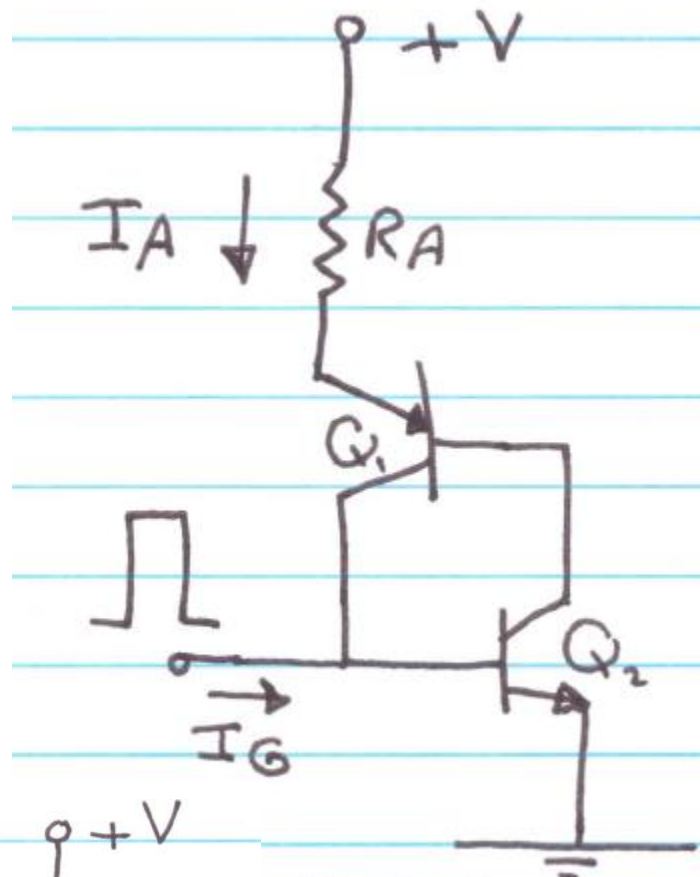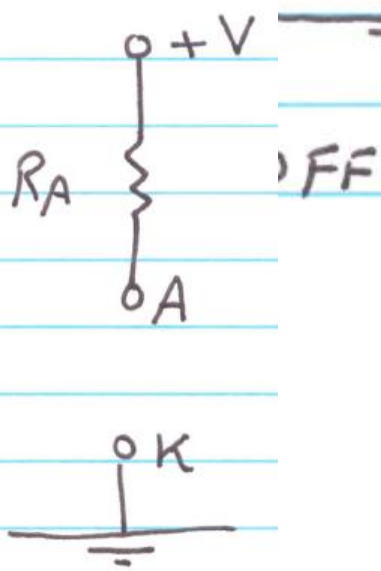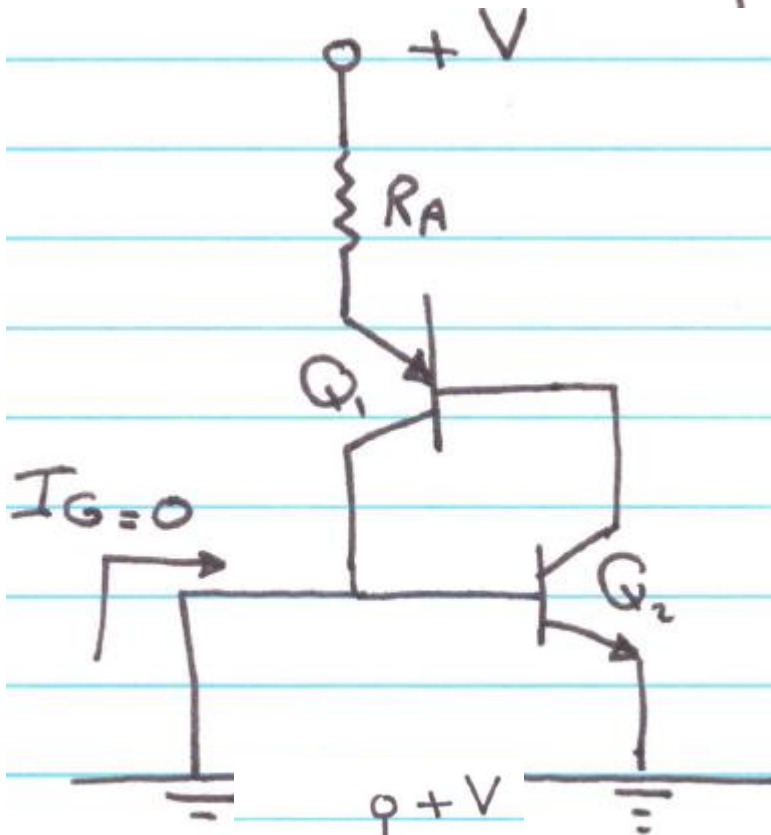

- When  $I_G = 0$ ; it acts as the Schottky diode in the off state (open circuit)
- When a positive pulse of current (trigger) is applied to the gate, both transistors turn on
- The SCR stays on (latches) once it is triggered on
- In this state, SCR can be approximated by a closed switch.


- Like the Schottky diode, an SCR can also be turned on without gate triggering by increasing  $V_{AK}$  to a value exceeding  $V_{BR}(F_0)$

## Turning the SCR OFF


When the gate returns to  $0V$ , after the trigger pulse is removed, the SCR can not turn off

It stays in the on state until the anode current  $I_A$  drop below  $I_H$

# SCR Characteristic Curves

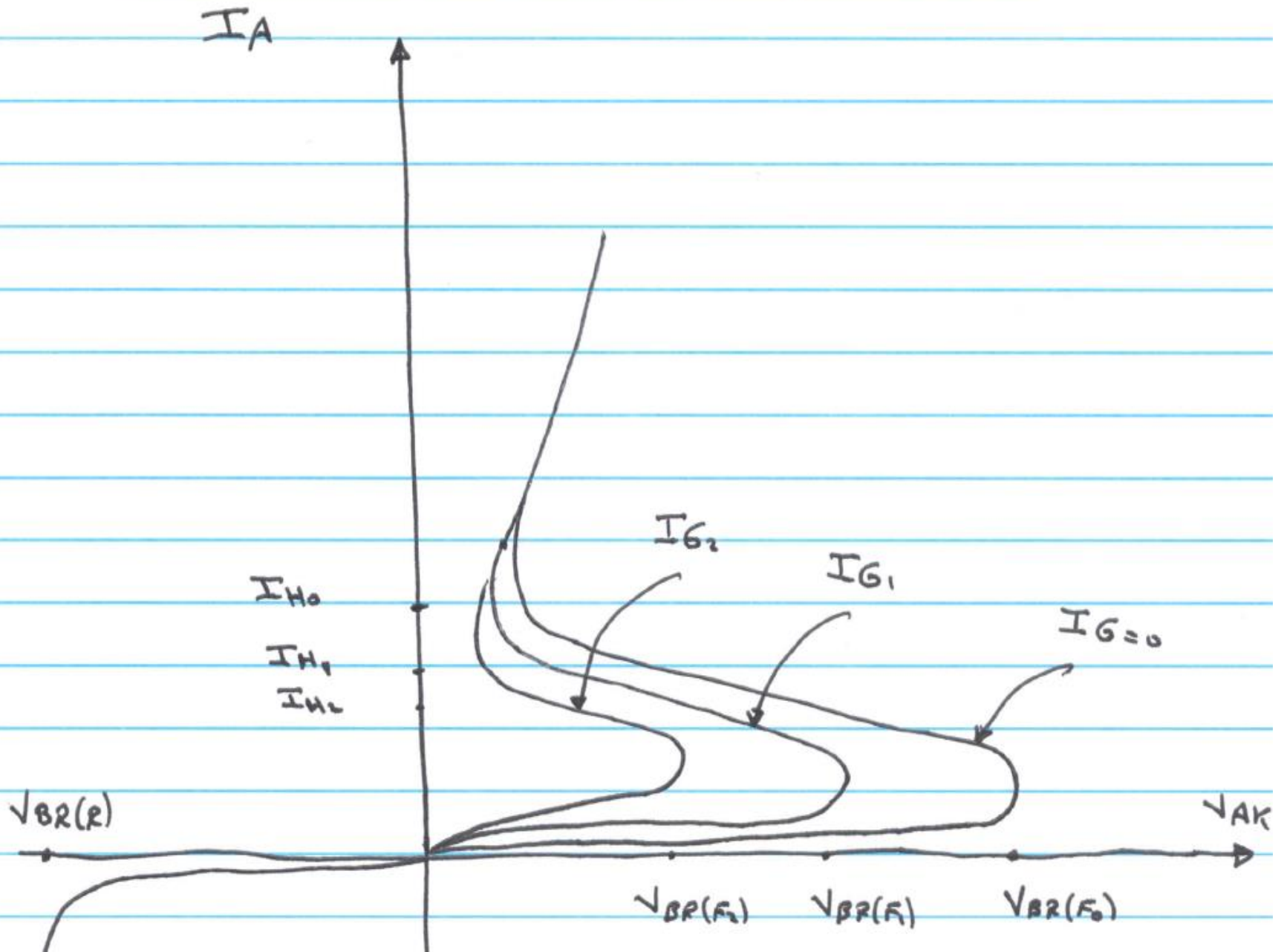

# SCR Characteristics and ratings

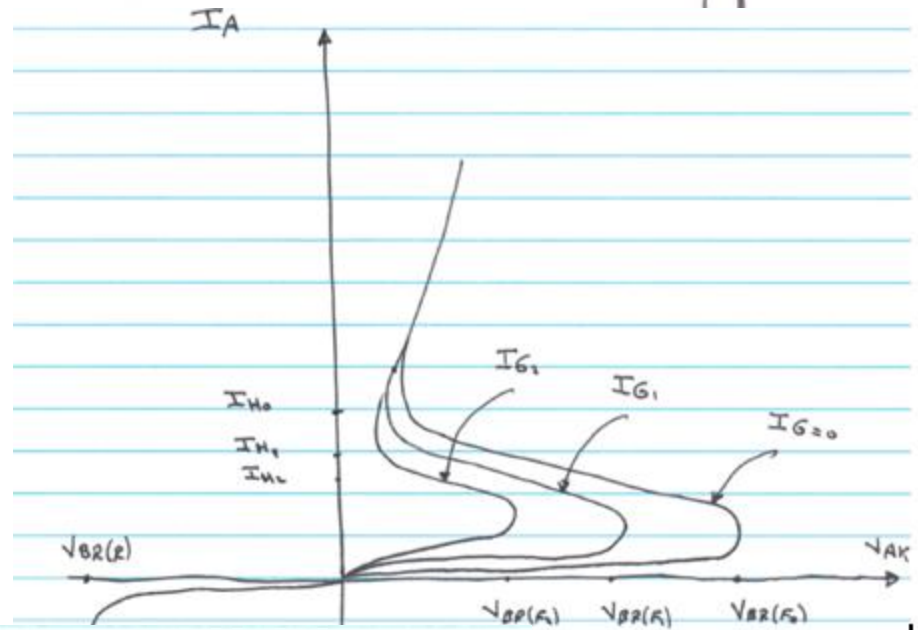


1) Forward breakover voltage :  $V_{BR(F)}$

This is the voltage at which the SCR enters the forward conduction region.

$V_{BR(F)}$  is maximum when  $I_G = 0$ .

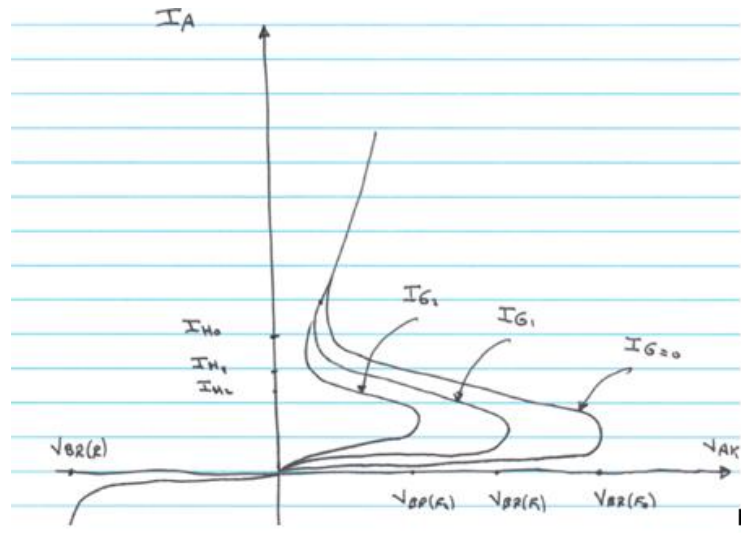When  $I_G$  increases,  $V_{BR(F)}$  decreases.




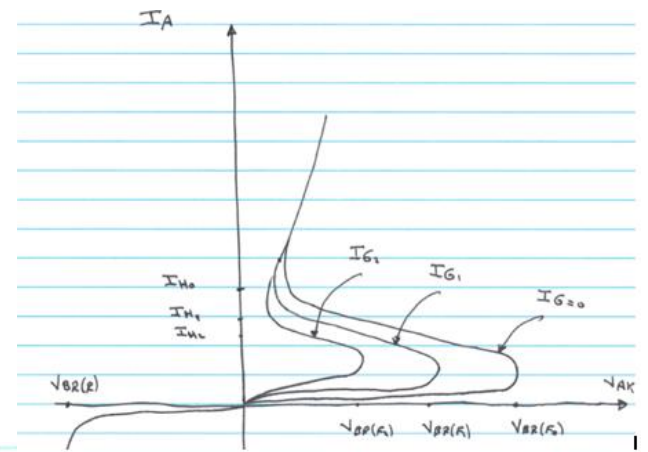2) Holding Current :  $I_H$

This is the value of anode current below which the SCR switches from the forward conduction region to the forward blocking region

$$I_H \downarrow \text{ as } I_G \uparrow$$






3) Gate triggering Current :  $I_{GT}$

This is the value of gate current necessary to switch the SCR from the forward blocking region to the forward conduction region

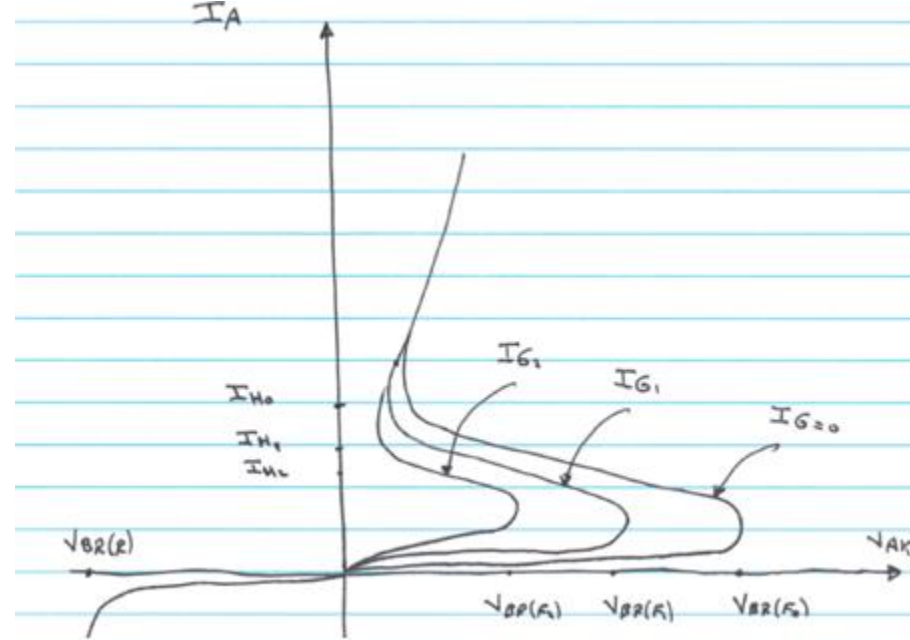4) Forward conduction region :



This region corresponds to the on condition of the SCR where there is forward current from Anode to Cathode.






5) Forward blocking region :

This region correspond to the OFF condition of the SCR where the forward current from anode to cathod is blocked by the open circuit of the SCR.

# SCR Application

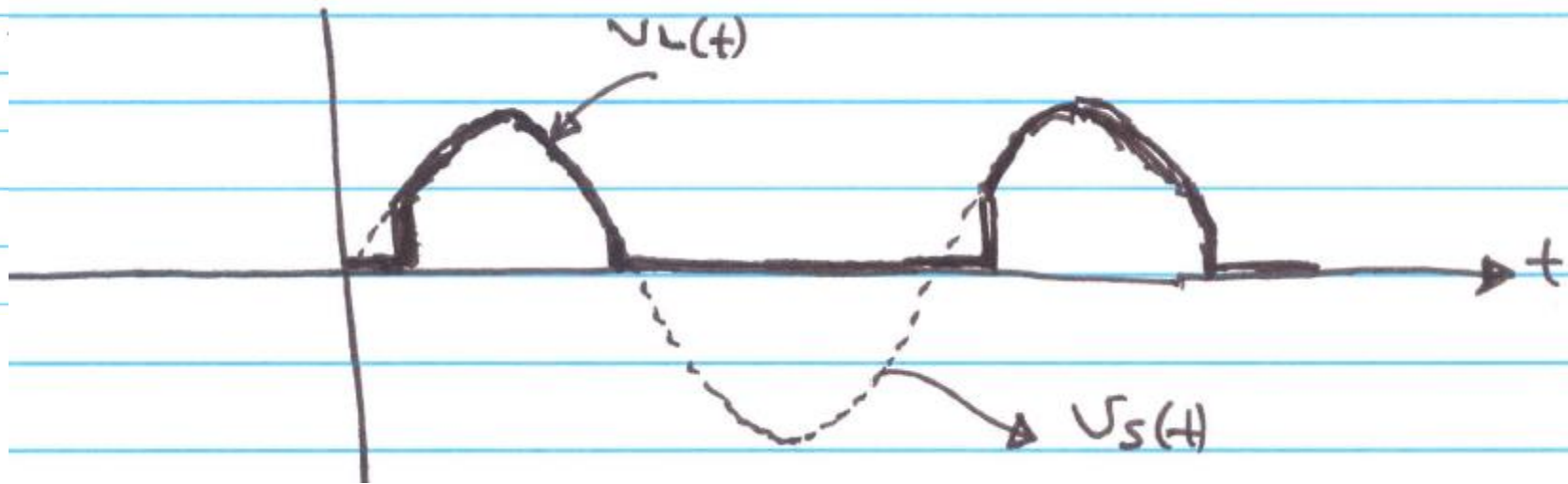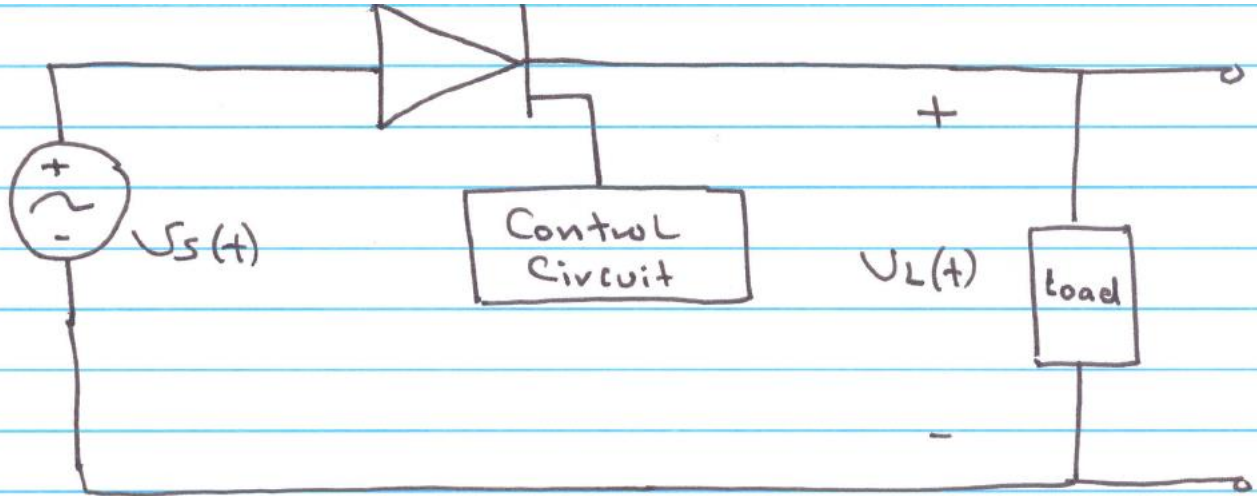


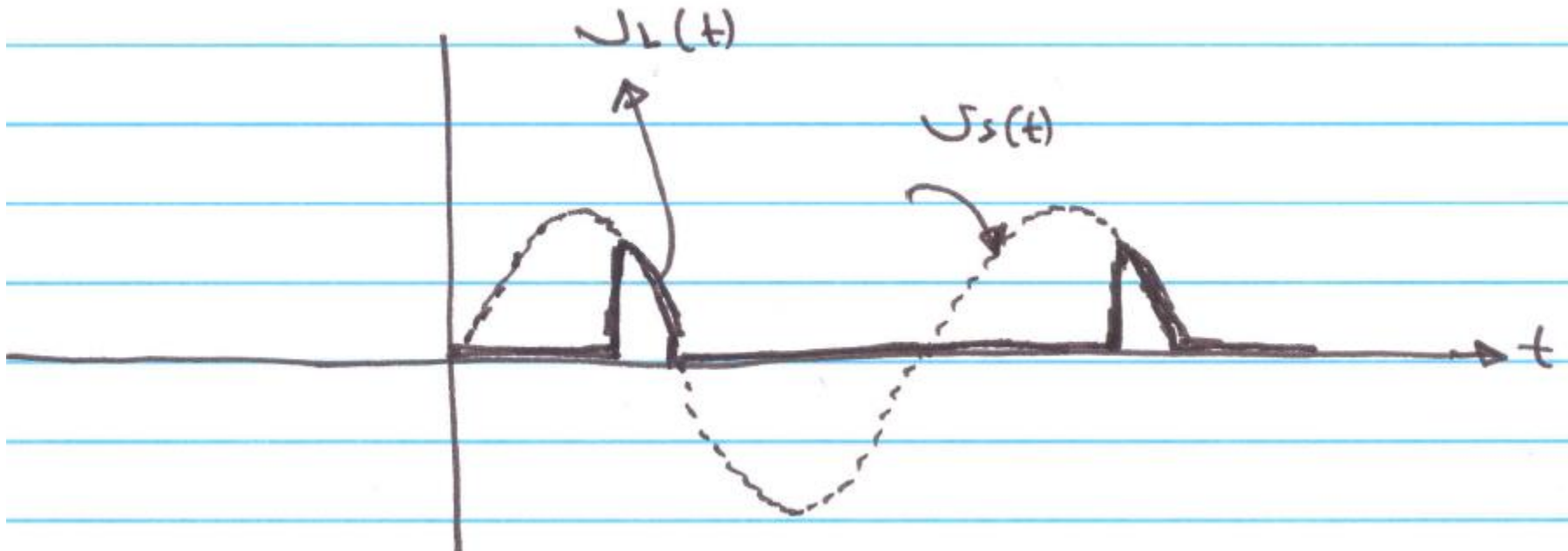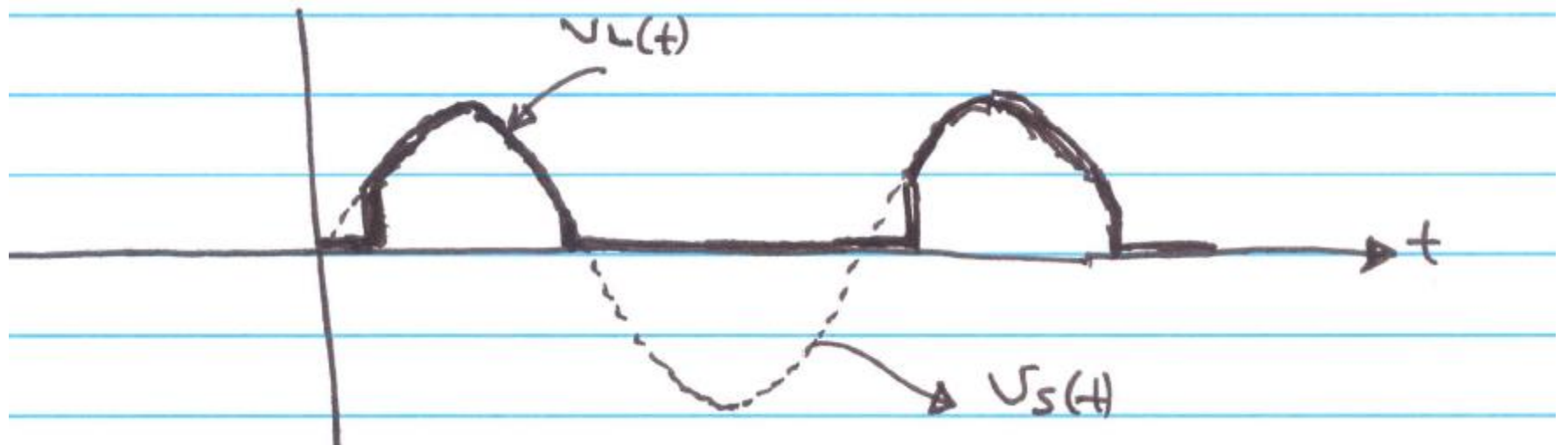

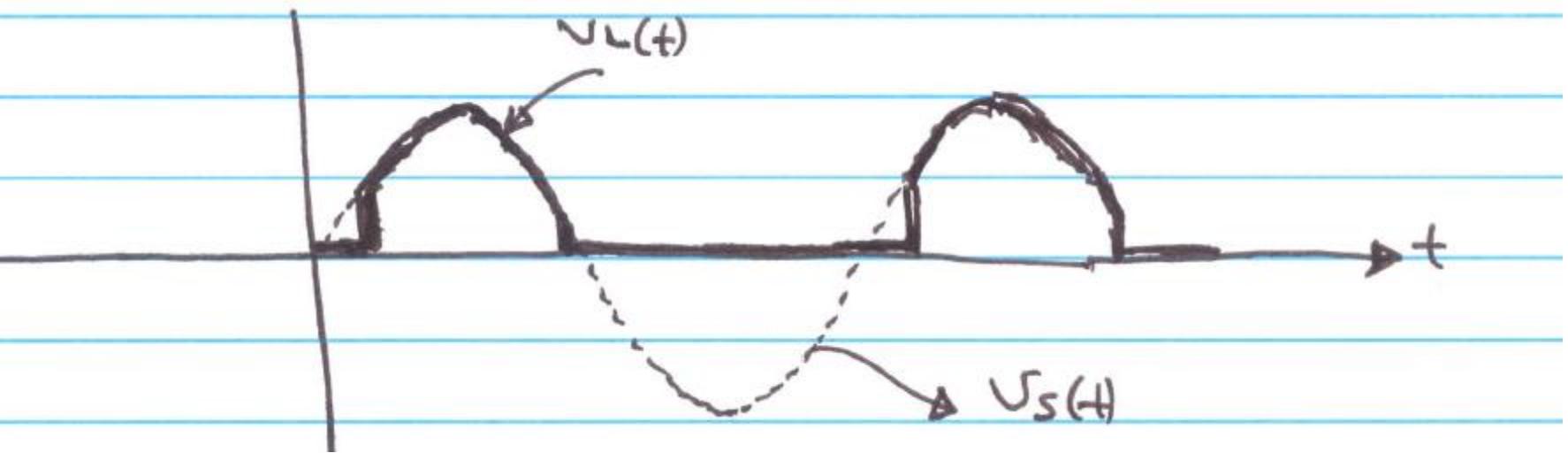

Conduction angle : is the number of Degrees  
of an ac cycle during which the SCR is  
turned on

$$\text{Conduction angle} = 135$$

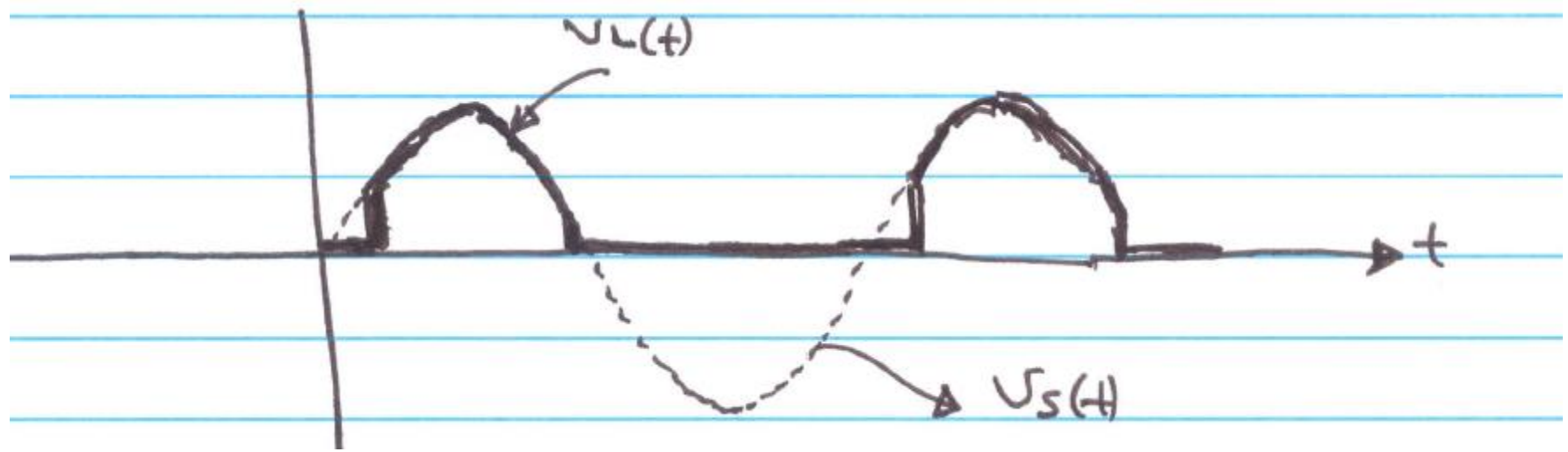


Firing delay angle : is the number of Degrees of an ac cycle elapses before the SCR is turned on. Firing delay angle = 45

The SCR spends a certain portion of the ac cycle time in the on state, and the remainder of the time is in the off state.


The amount of time spent in each state is controlled by the gate.

The SCR can not be turned on more than half the time.

# Typical Gate Control Circuits

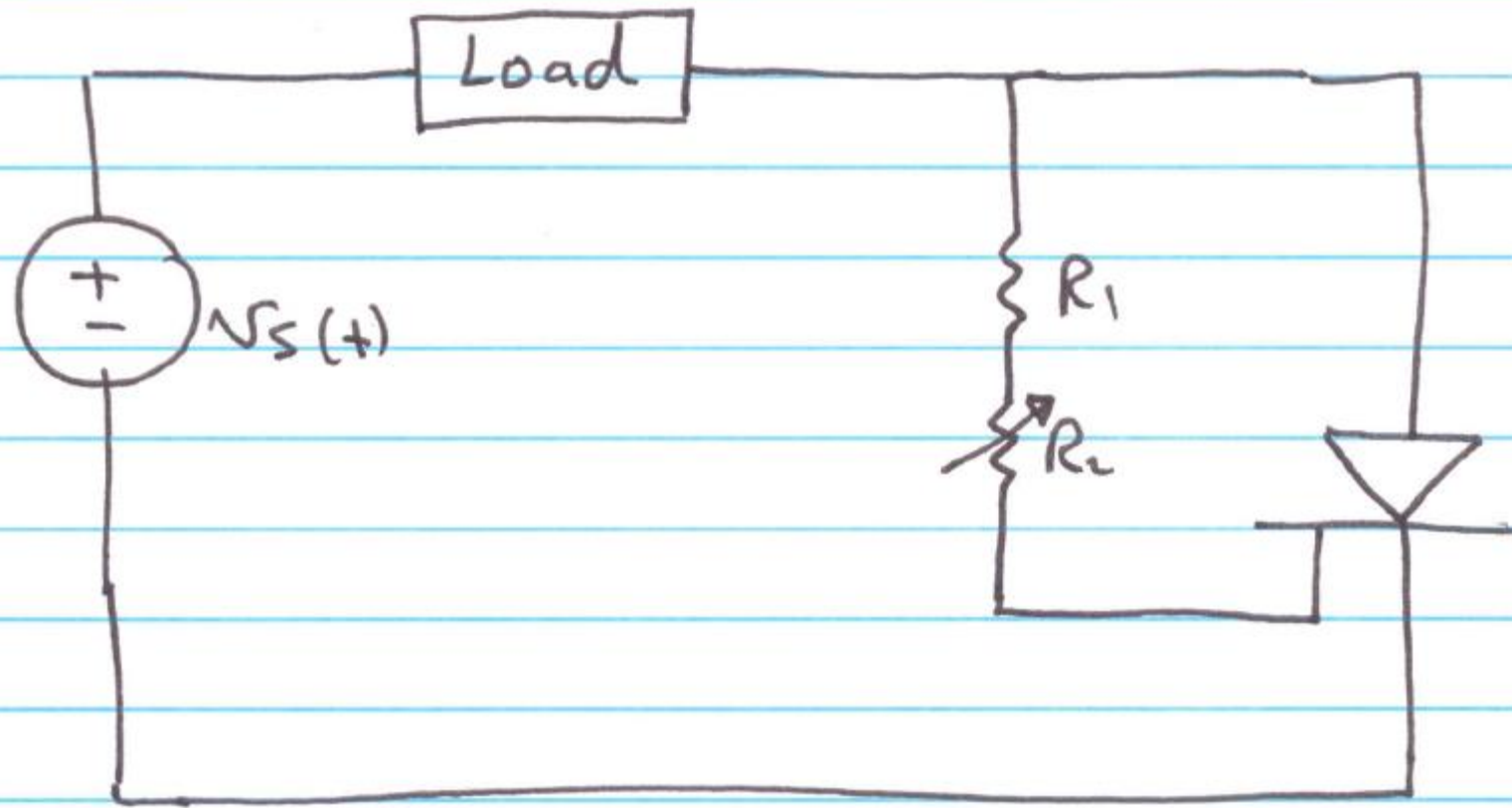




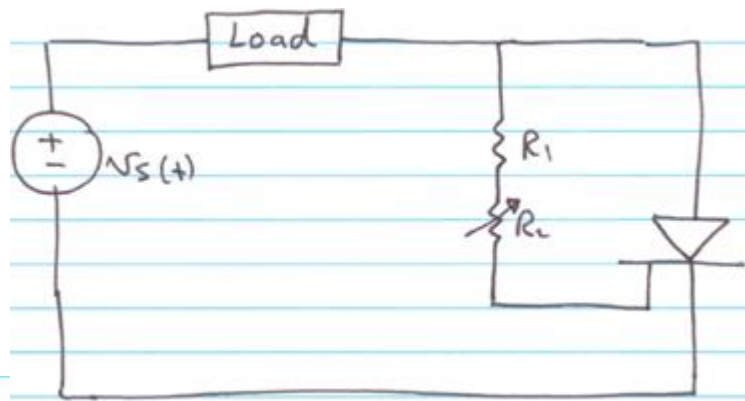

- The Same voltage supply  $V_s(t)$  is used to power both the gate Control and the Load
- When the Supply voltage  $V_s(t)$  is positive and Large enough so that  $I_G > I_{GT}$ ; the SCR turns on
- The firing angle is determined by the setting of  $R_2$
- $90 > \alpha > 0$


## Other Gate Control Circuit

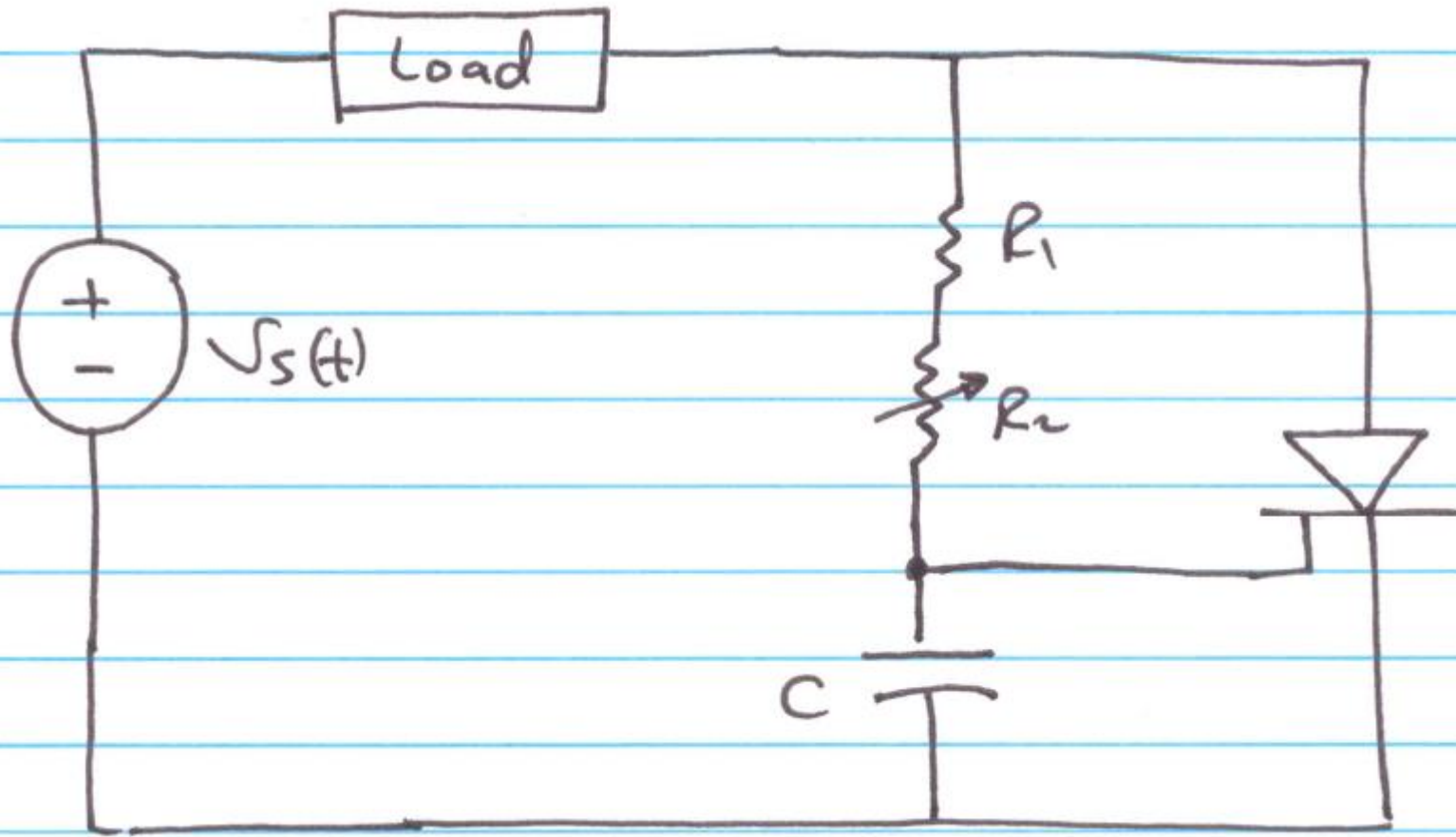

Firing delay angle could be greater than  $90^\circ$

$R_2 \uparrow$ ,  $\tau \uparrow$ ,  $\theta \uparrow$

# The Diac

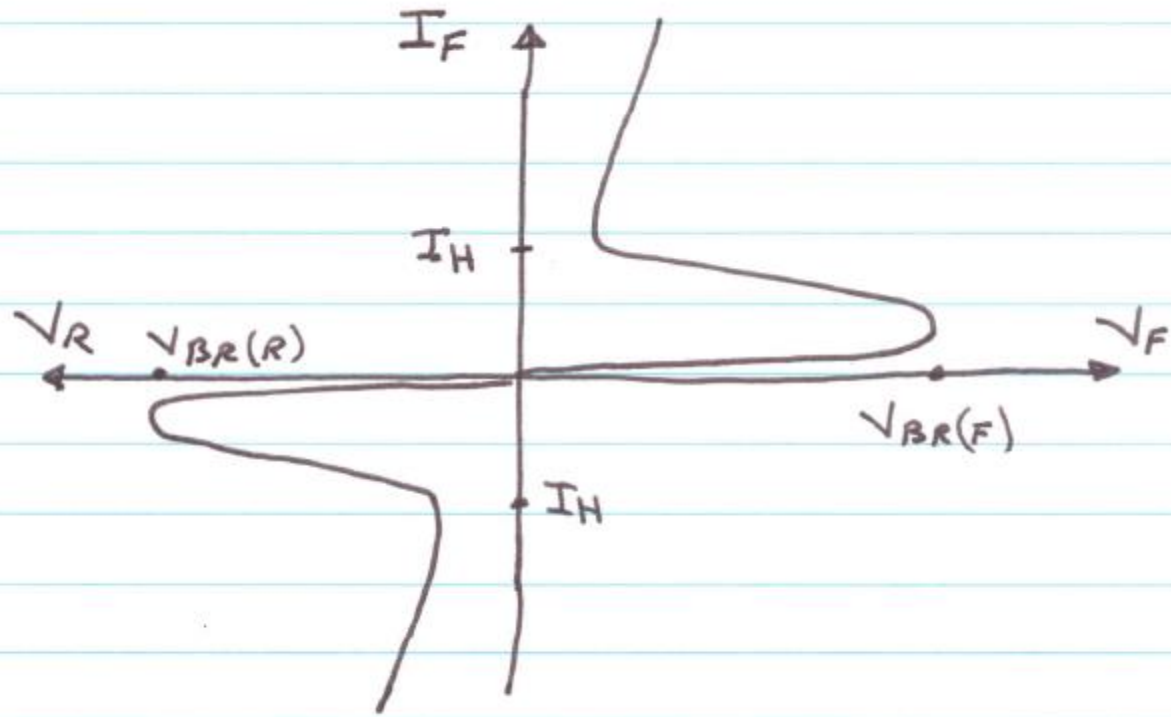

Circuit Symbol

Characteristic Curve


- It is a two terminal device
- It can conduct current in either direction

when properly activated

Conduction occurs when the breakover voltage

is reached with either polarity




# The Diac

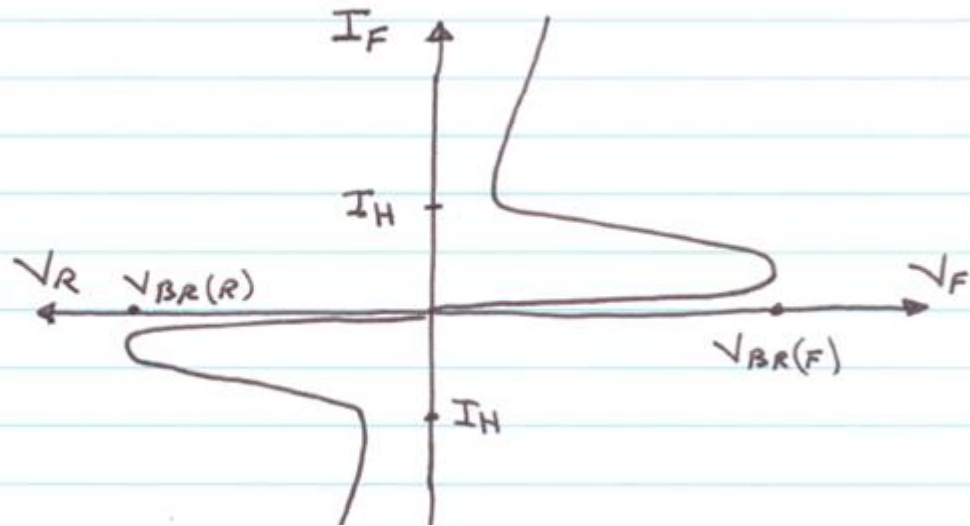


The device turns off when the current drops below the holding value ( $I_H$ )

The device functions like two parallel Shockley diodes turned in opposite direction


# The Diac

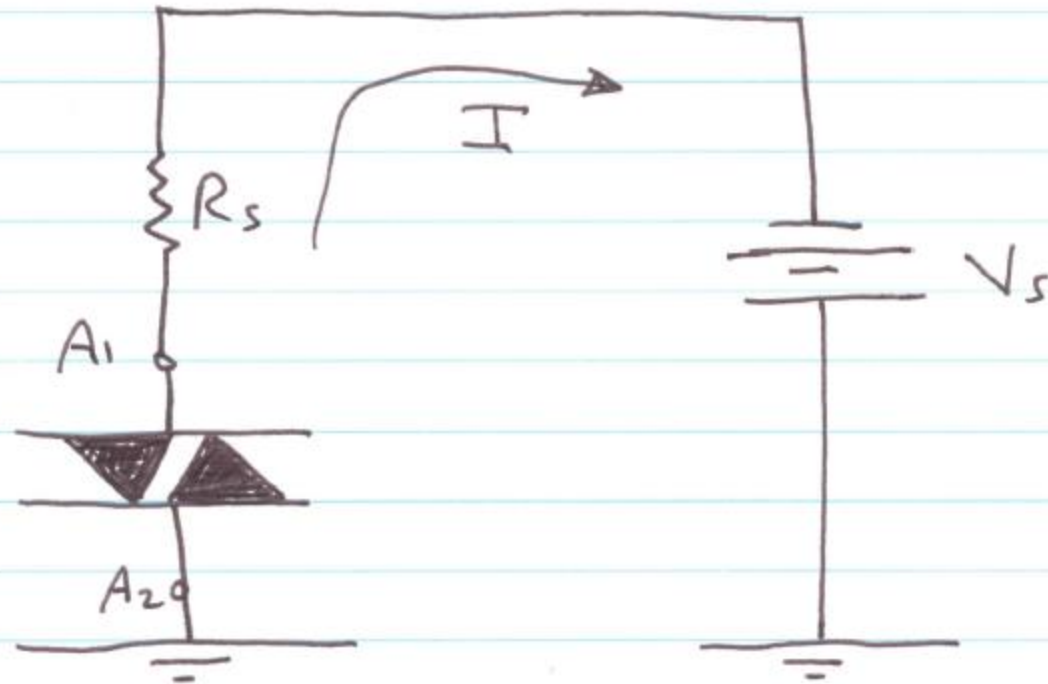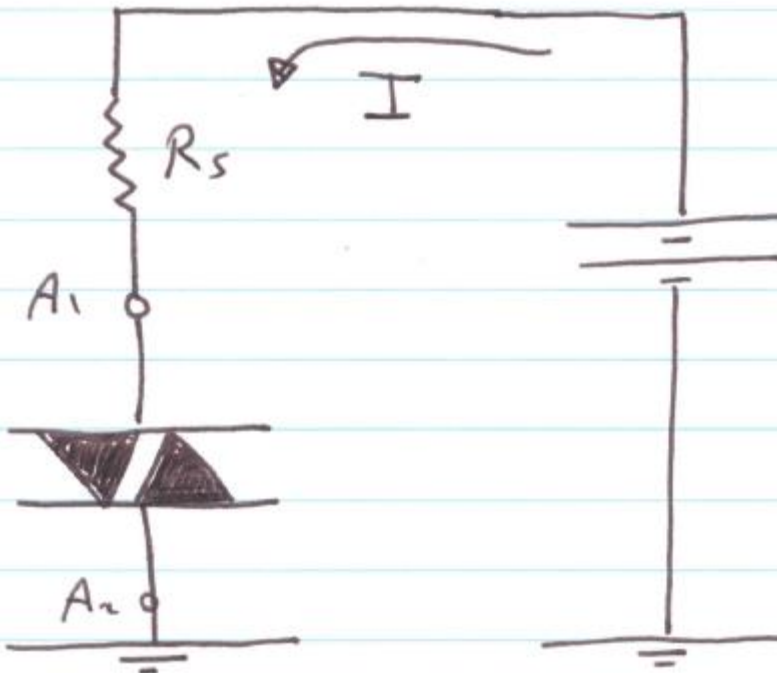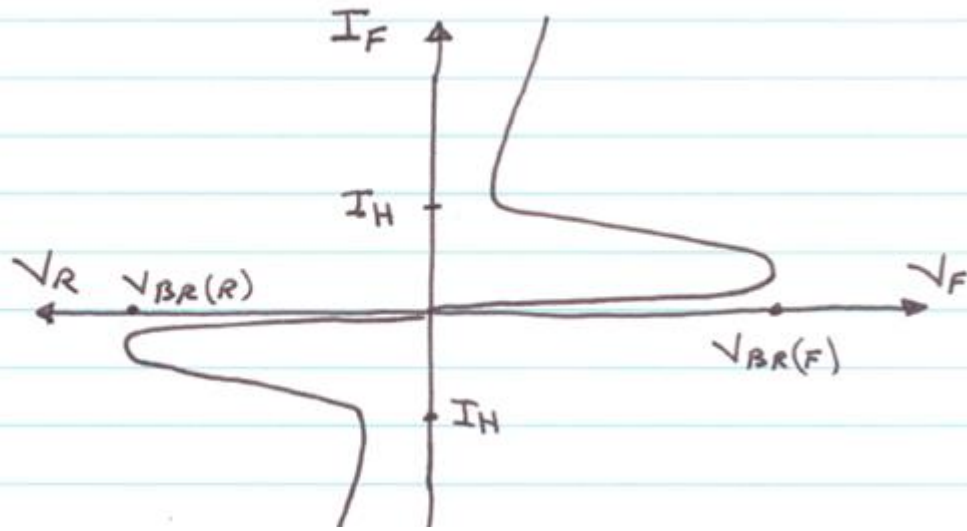

# The Triac

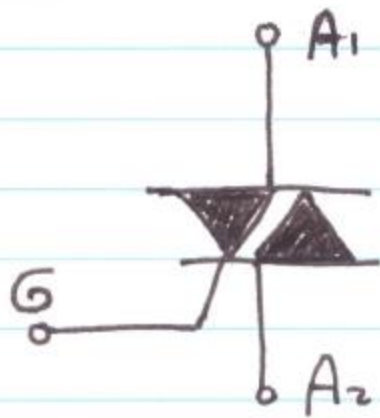


Circuit  
Symbol

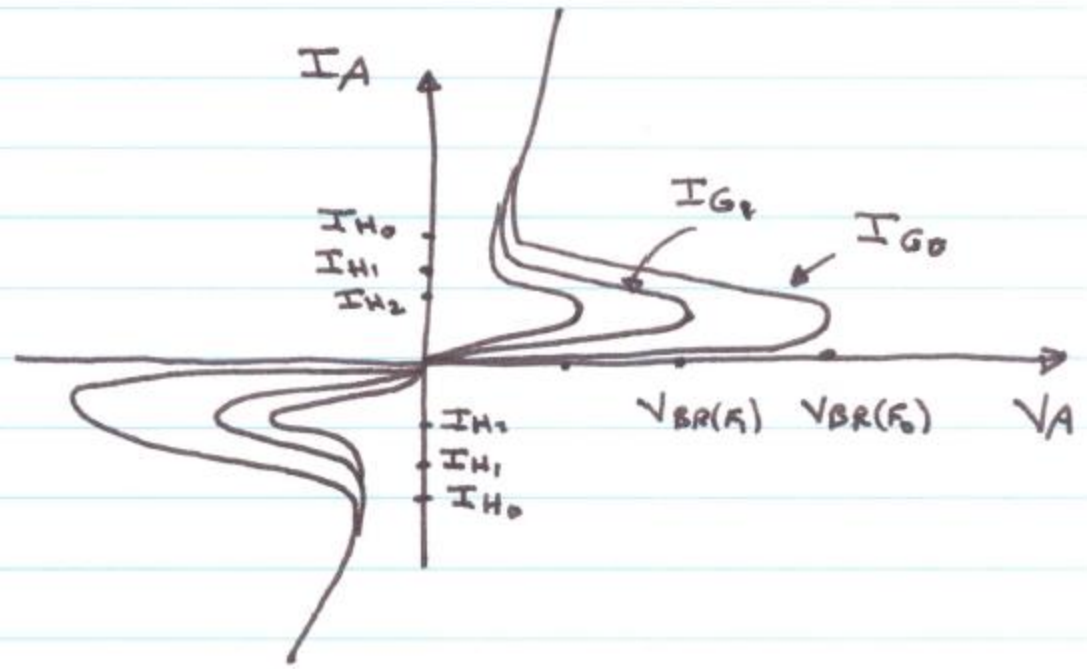


characteristic Curves

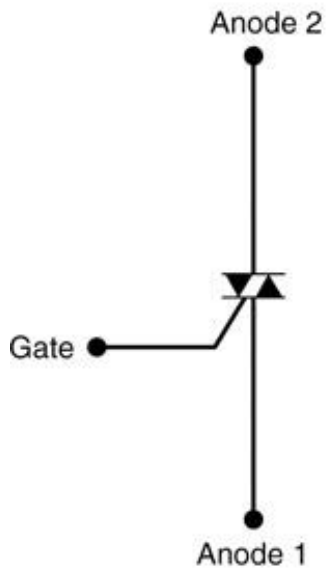- A triac is like a diac with a gate
- The triac functions like two SCR connected in parallel and in opposite direction with a common gate terminal.




(a)

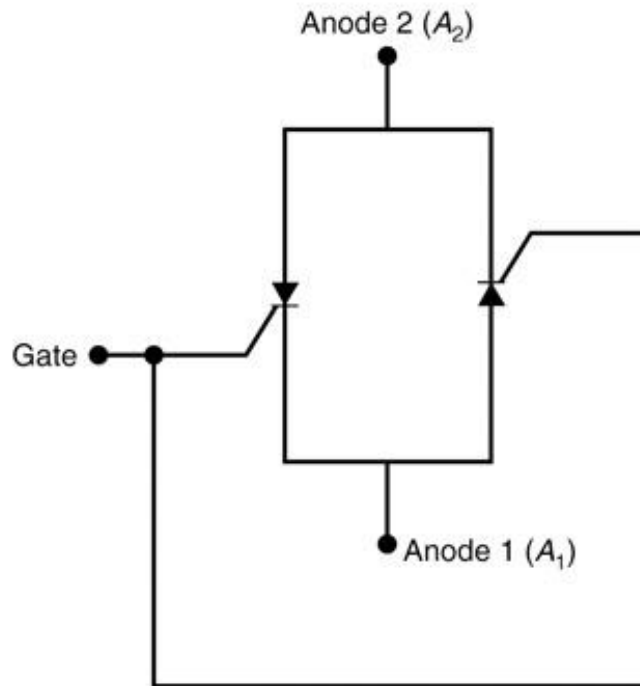


(b)

# The Triac

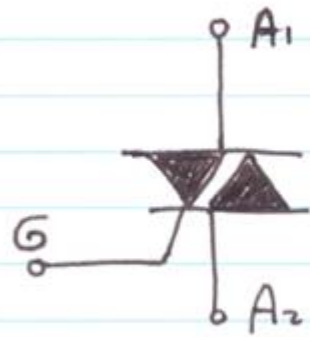

Circuit  
Symbol

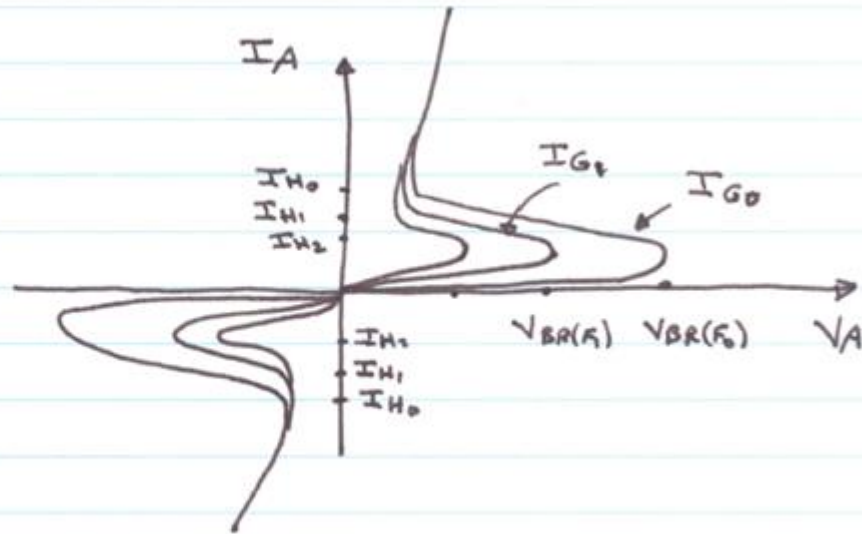


Characteristic Curves

The triac can conduct current in either direction when it is triggered on, depending on the polarity of the voltage across its  $A_1$  and  $A_2$  terminals.

The triac turns off when the current drops below the holding value ( $I_H$ ).



# Triac Application

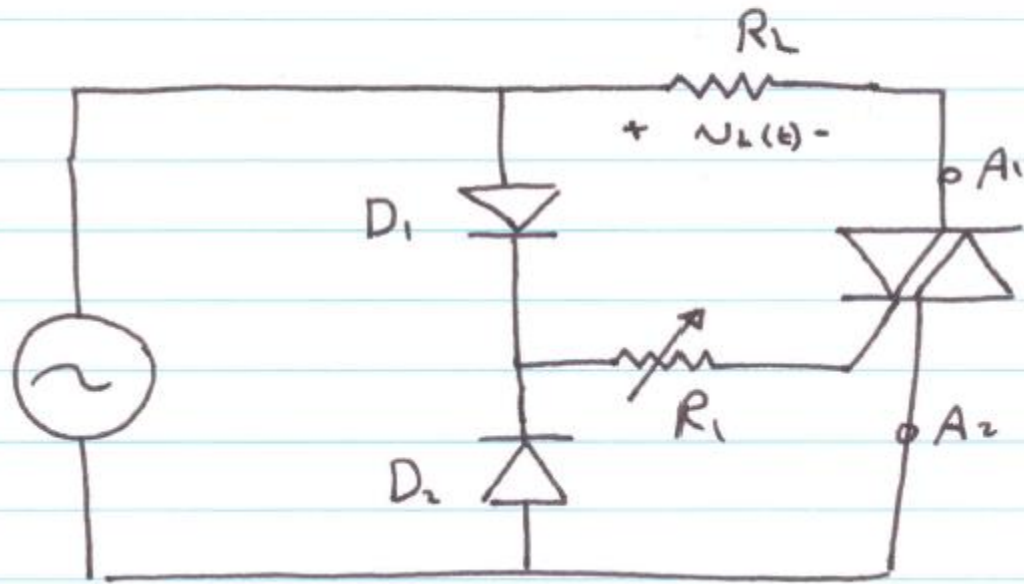


- Diode  $D_1$  conducts during the positive

half-cycle


- The value of  $R_1$  sets the point on the positive

half cycle at which the triac triggers


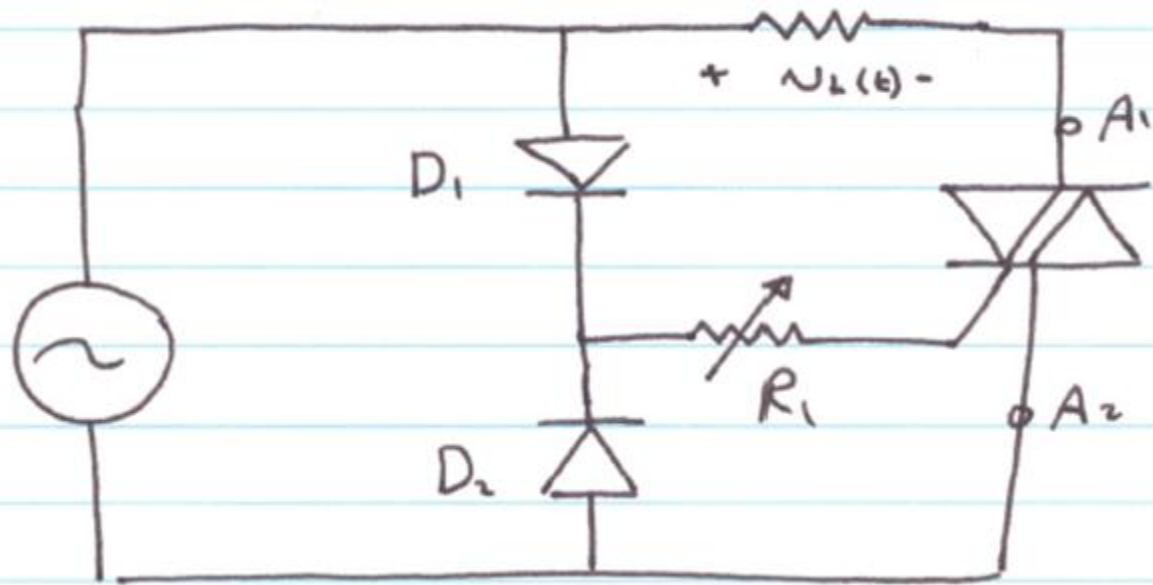


- Diode  $D_2$  Conducts during the negative half cycle

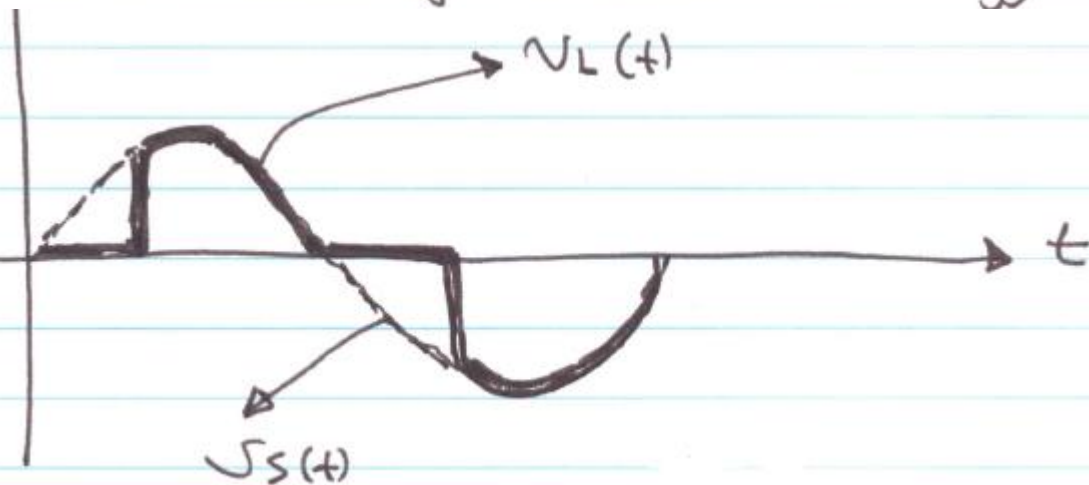
- The value of  $R_1$  sets the trigger point



# Unijunction Transistor (UJT)

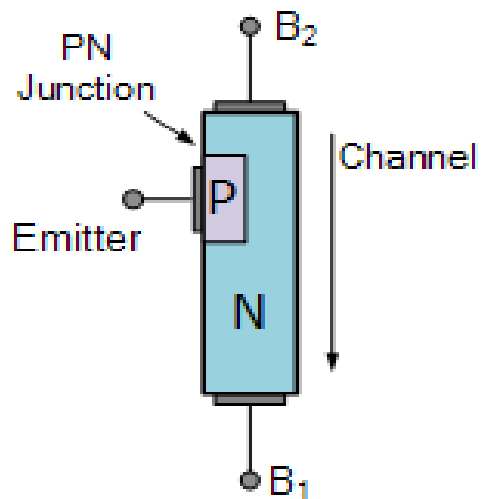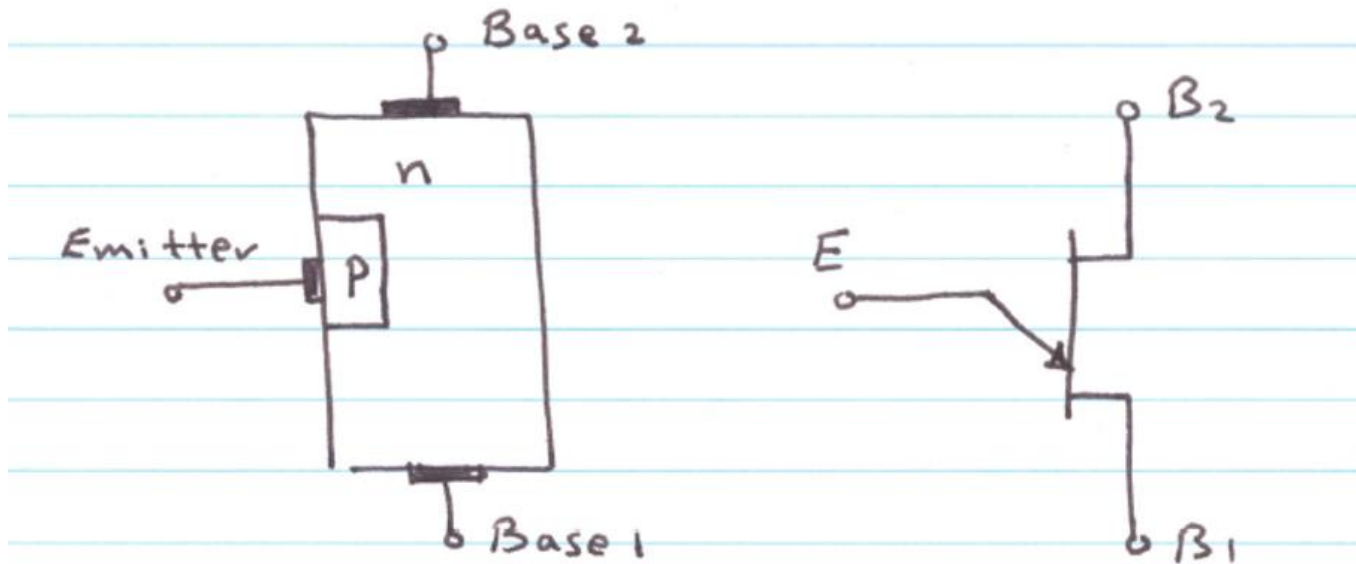



Construction

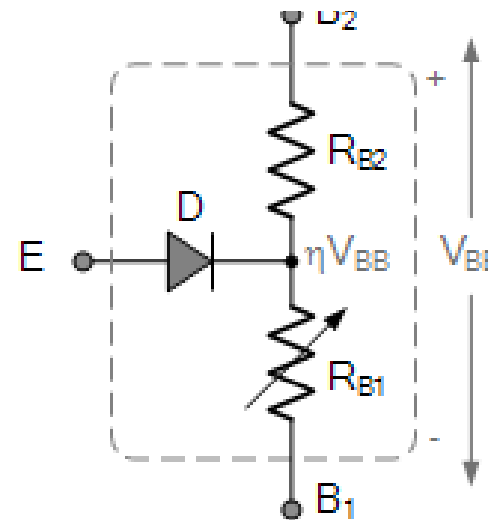

Simplified Equivalent Circuit
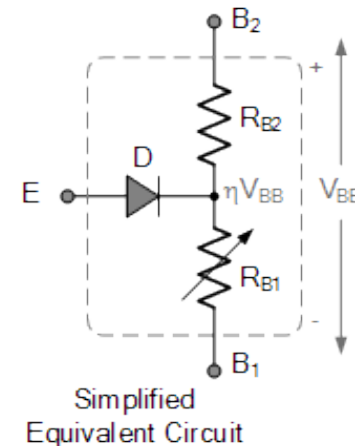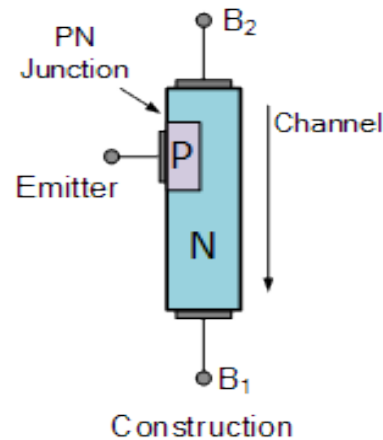
# Unijunction Transistors

- The **unijunction transistor (UJT)** is a three-terminal semiconductor device that has only one p-n junction.
- The unijunction transistor (UJT) has two base leads,  $B_1$  and  $B_2$  and an emitter (E) lead.
- The interbase resistance,  $R_{BB}$  of a UJT is the resistance of its n-type silicon bar.
- The ratio  $R_{B1}/(R_{B1} + R_{B2})$  is called the intrinsic standoff ratio, designated  $\eta$ .




# Unijunction Transistor (UJT)

- For a Unijunction transistor, the resistive ratio of  $R_{B1}$  to  $R_{B2}$  is called the **intrinsic stand-off ratio** ( $\eta$ ).


$$\eta = \frac{R_{B1}}{R_{B1} + R_{B2}}$$

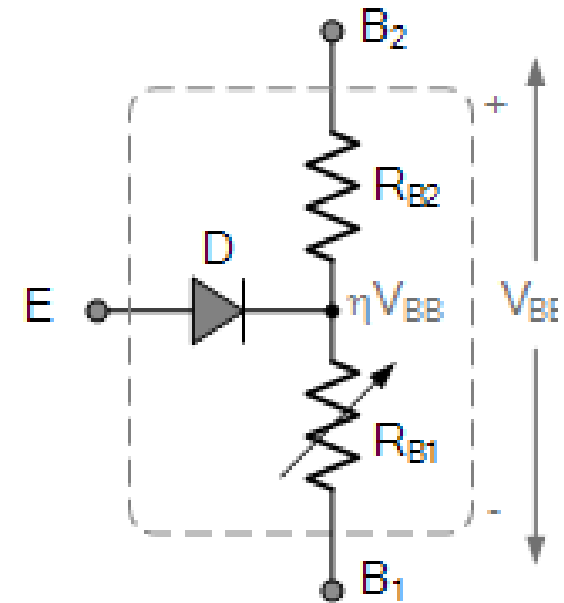- Typical standard values of  $\eta$  range from 0.5 to 0.8 for most common UJT's.**



Simplified  
Equivalent Circuit

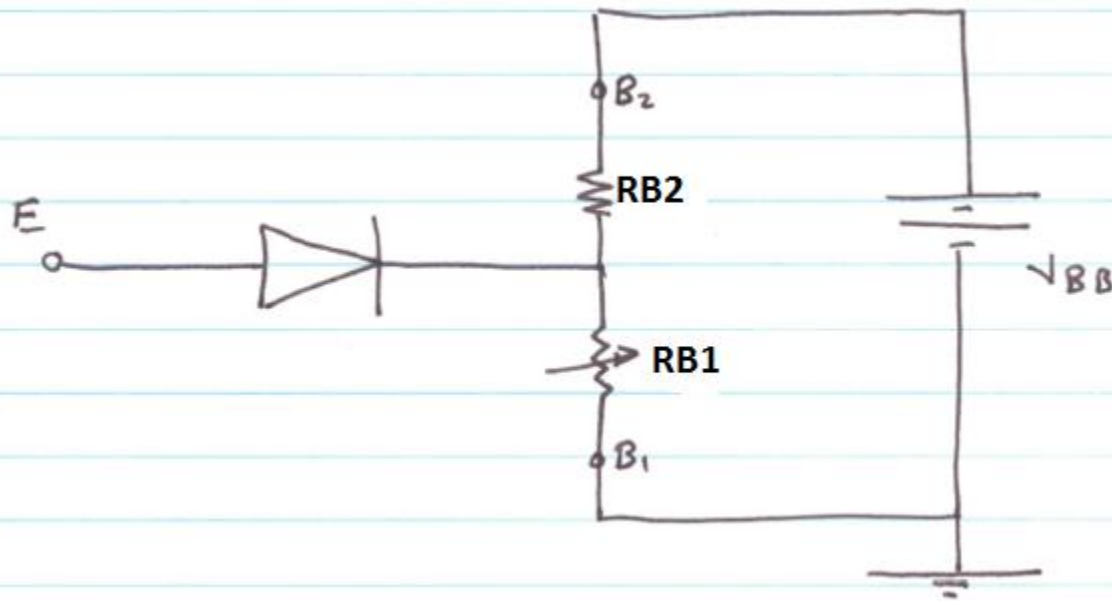**UJTs are used in conjunction with SCRs and Triacs to control their conduction angle**



To fire the UJT

$$V_{EB1} \geq V_D + \frac{RB1}{RB1+RB2} V_{BB} = V_p$$

$$V_{EB1} \geq V_D + \frac{RB1}{R_{BB}} V_{BB} = V_p$$

$$V_{EB_1} \gg V_D + \eta V_{BB} = V_p$$

$$\eta = \frac{R_{B1}}{R_{BB}} \equiv \text{standoff ratio}$$

$V_p \equiv$  peak point voltage

As long as the applied emitter voltage  $V_{EB_1}$  is less than  $V_p$ ; there is no emitter

current because the pn junction is not forward biased

- When  $V_{EB_1}$  reaches  $V_p$ , the pn junction

becomes forward biased and  $I_E$  begins.

- Holes are injected into the n-type bar


from the p-type emitter

$r_B$  decreases

After turn on, the UJT operates in a negative resistance region up to a certain value of  $I_E$ .

After the peak point ( $V_E = V_p$  and  $I_E = I_p$ )

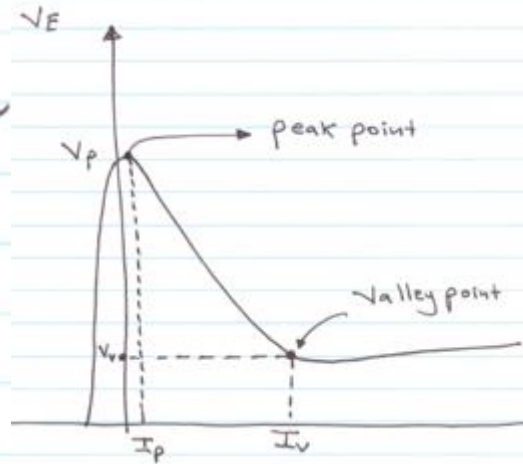$V_E$  decreases as  $I_E$  continues to increase, thus producing the negative resistance characteristic.




Beyond the valley point ( $V_E = V_v$  and  $I_E = I_v$ )

, the device is in saturation



# UJT Characteristic Curve

---

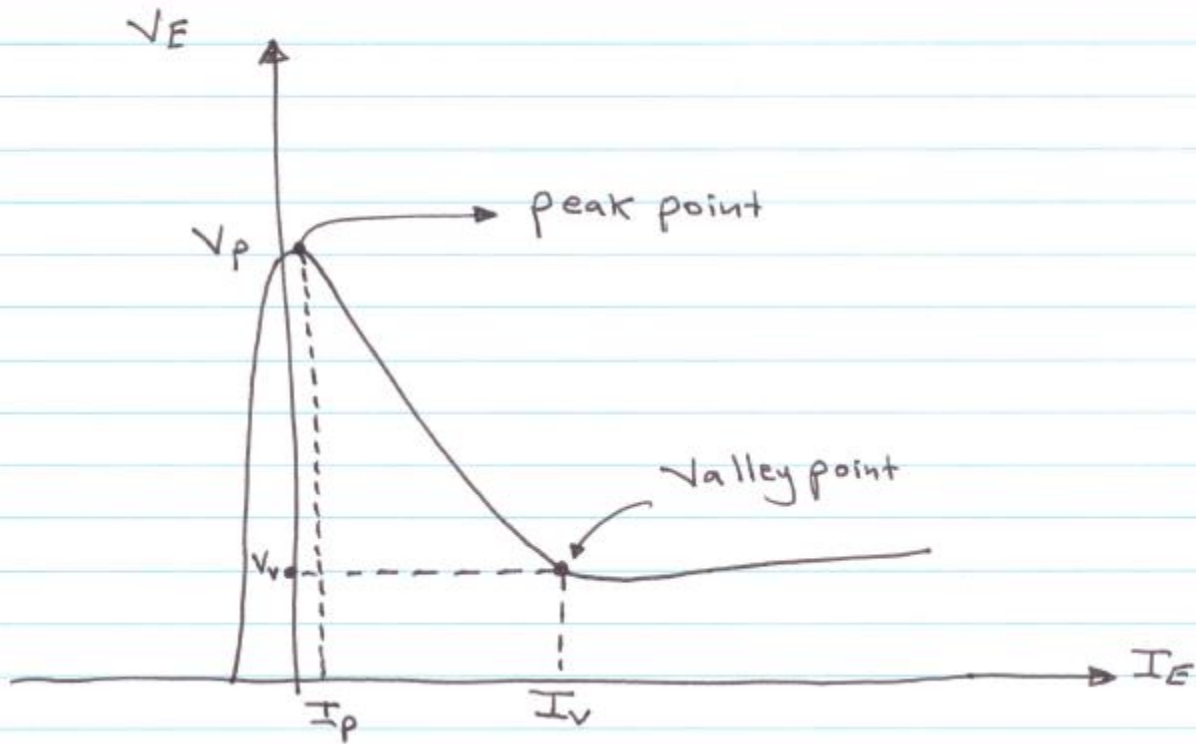



$V_v \equiv$  Valley Voltage

$I_v \equiv$  Valley Current



# A UJT Application

## Relaxation Oscillator

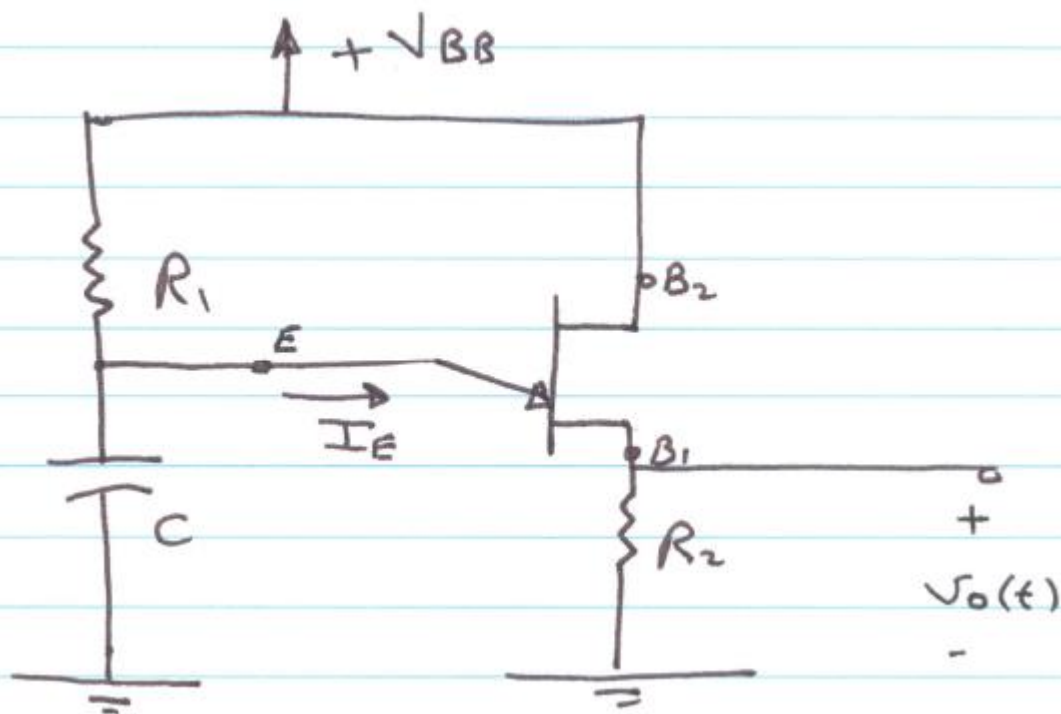


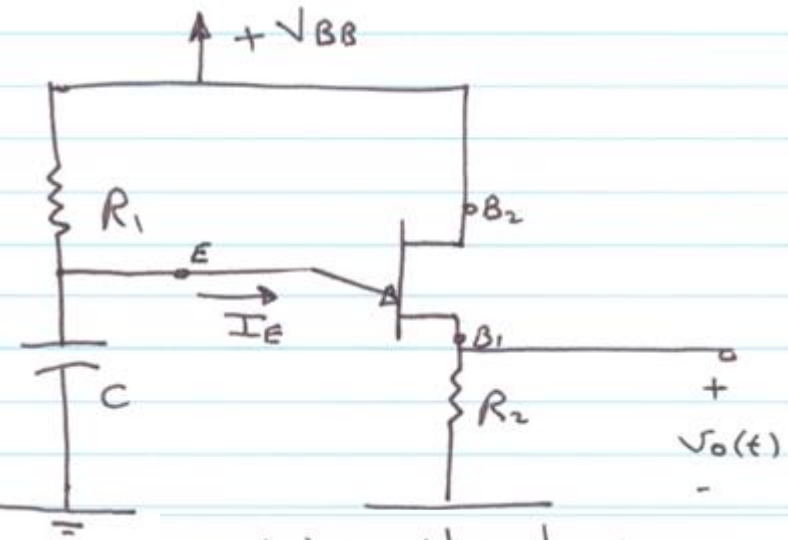

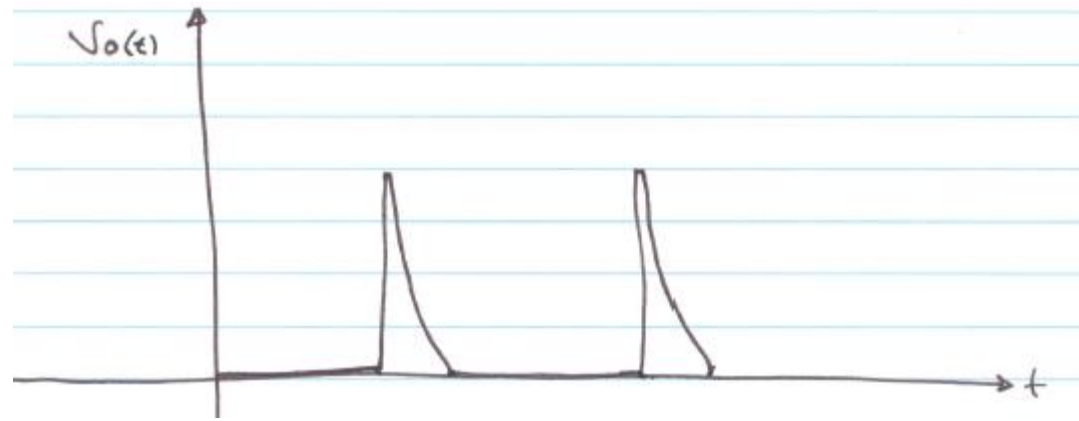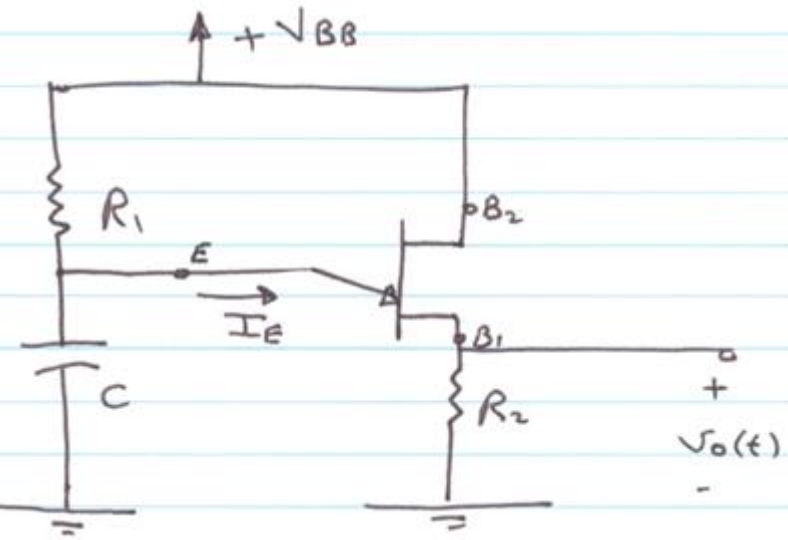- When the dc power supply is applied, the Capacitor  $C$  charges through  $R_1$  until it reaches  $V_p$
- At this point, the pn junction becomes forward biased and  $I_E$  conducts, and  $v_{B_1}$  decreases
- The Capacitor then quickly discharge through  $R_2$  and  $v_{B_1}$
- When the Capacitor voltage decreases to the valley voltage, the UJT turns OFF



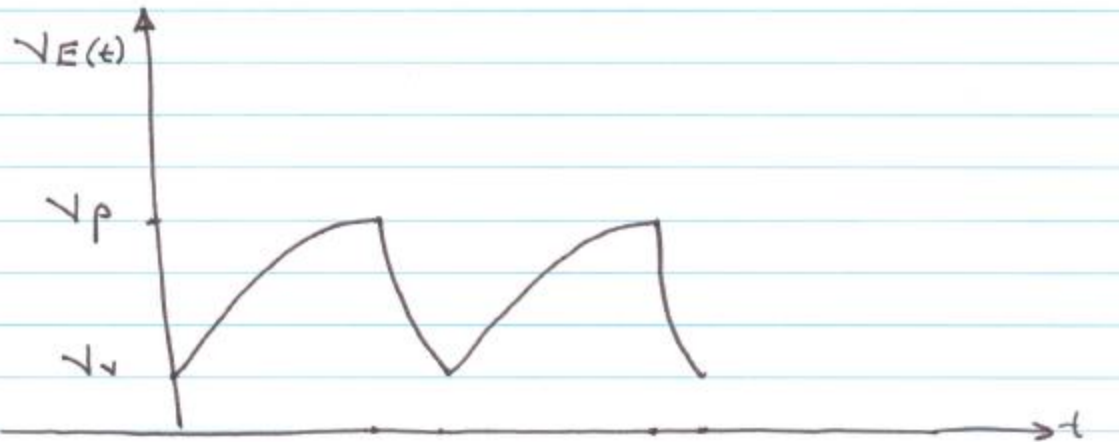- The Capacitor begins to charge again and the cycle is repeated.



# UJT Relaxation Oscillator

