



For instructor's Use

لاستعمال المدرّس

السؤال Question	العلامة Grade
1	
2	
3	
4	
5	
6	
7	
8	
9	
10	
11	
12	
Total	

ENEE 2305
Circuit Analysis II

Exam BOOKLET

دفتر امتحان

Student:	المطالِب:
Number: Midterm Exam Solution	الرقم:
Division:	المادة:
Department:	الكلية:
Instructor:	المدرّس:
Date:	التاريخ:

Question 1

30 marks

30/30

(a) $T_U(s) = -\frac{500(s+100)}{s(s+150)}$, RC & only 1 OPAMP
use 1 μF Cap.

$T_U(s) = \underbrace{\left(-\frac{500}{s}\right)}_{1^{\text{st}} \text{ stage}} \underbrace{\left(\frac{s+100}{s+150}\right)}_{2^{\text{nd}} \text{ stage}}$

1st stage Inv. op. amp.


$$\text{gain} = -\frac{Z_2(s)}{Z_1(s)} = -\frac{500}{s} = -\frac{500/s}{1}$$

$$Z_2(s) = -\frac{500}{s} \Omega \Rightarrow C_2 = \frac{1}{500} = 2 \times 10^{-3} \text{ F} \quad (6)$$

$$Z_1(s) = 1 \Omega \Rightarrow R_1 = 1 \Omega$$

$$K_f = \frac{C_{\text{old}}}{C_{\text{new}}} = \frac{2 \times 10^{-3}}{1 \times 10^{-6}} = 2000$$
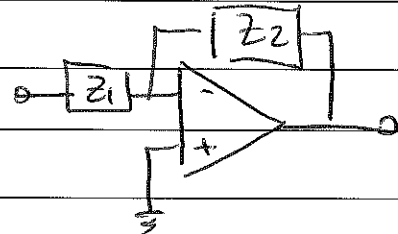
$$C_1 = 1 \mu\text{F} \quad R_1 = 2 \text{ k}\Omega$$



2nd stage

$$T_{U2}(s) = \frac{s+100}{s+150} = \frac{1 + \frac{100}{s}}{1 + \frac{150}{s}} = \frac{Z_2'(s)}{Z_1'(s) + Z_2'(s)}$$

$$Z_2'(s) = 1 + \frac{100}{s}$$


$$Z_1'(s) = 1 + \frac{150}{s} \Rightarrow Z_2'(s) = \frac{50}{s}$$

$$C_2' = \frac{1}{100} = 0.01 \text{ F} \quad \& \quad C_1' = \frac{1}{50} = 0.02 \text{ F} \quad (6)$$

$$k_f' = \frac{C_{old}}{C_{new}} = \frac{0.01}{1 \times 10^{-6}} = \boxed{10000}$$

$$C_2' = 1 \mu F, \quad R_2' = 10 k\Omega$$
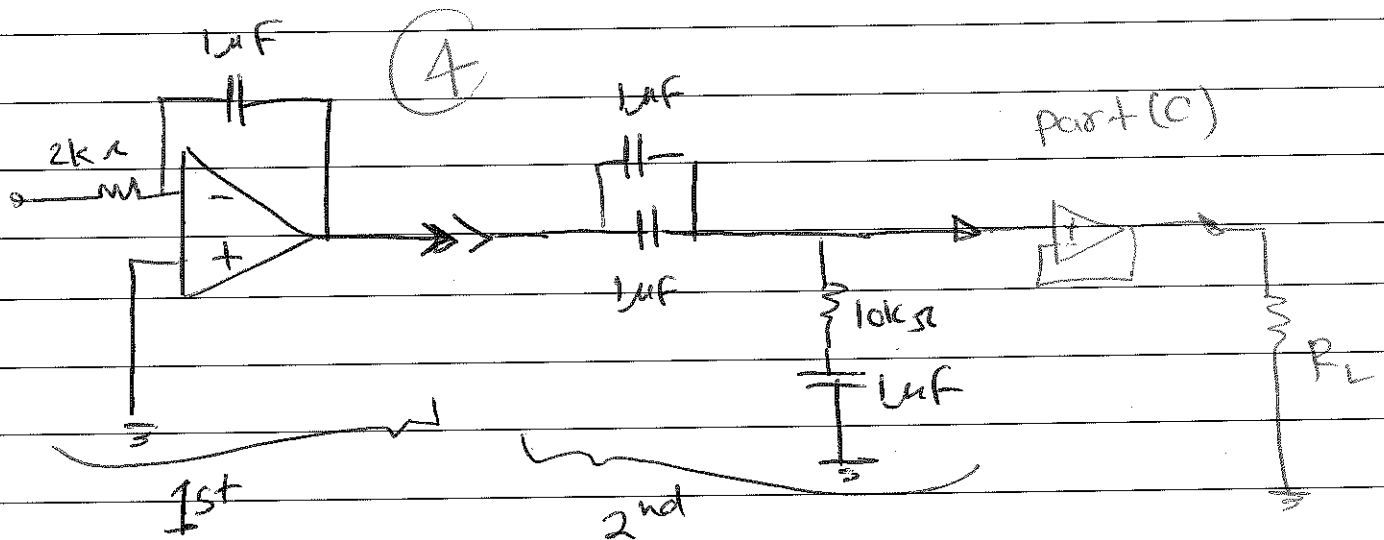
$$C_1' = \frac{0.02}{10,000} = 2 \times 10^{-6} F$$



(b) No loading, since Z_{out} of the first stage equals zero.

(c) if R_L is connected to the output part, then the circuit will involve loading!!



→ to eliminate the loading effect, use voltage follower as shown in the above figure.

Question 2 | 20 marks

20/20

find $V_o(t)$ using Nodal Analysis

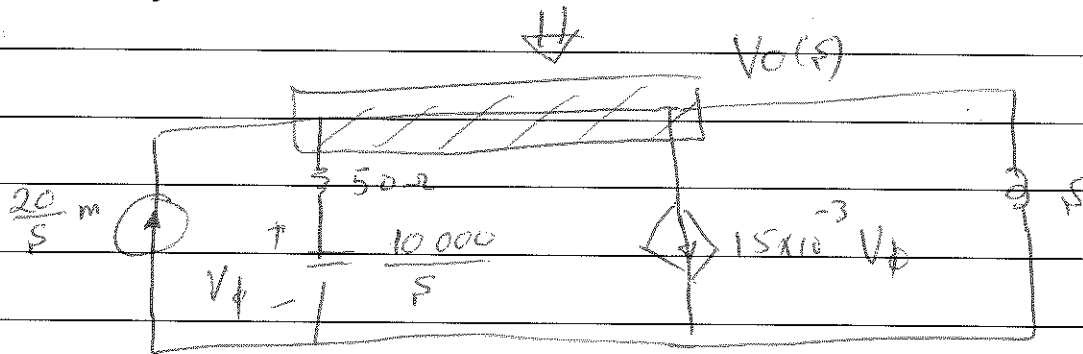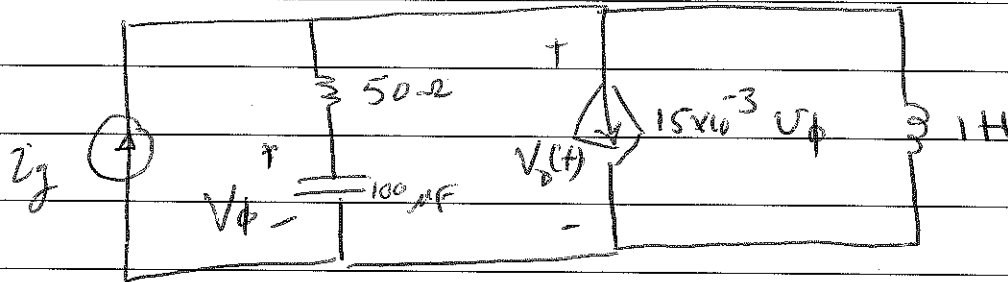$i_g(t) = 20 \text{ (u)(t) mA}$. No energy stored @ $t=0$



(A)

4/5

$$\frac{-20 \times 10^{-3}}{s} + \frac{V_o}{50 + \frac{10^4}{s}} + 15 \times 10^{-3} V_\phi + \frac{V_o}{s} = 0 \quad \text{(A)}$$

(A)

But $V_\phi = \frac{\frac{10^4}{s}}{\frac{10^4}{s} + 50} V_o = \frac{10^4}{10^4 + 50s} V_o$ → sub in (A)

(2)

4/5

$$\frac{20 \times 10^{-3}}{s} = \frac{V_o}{50 + \frac{10^4}{s}} + \frac{150}{10^4 + 50s} V_o + \frac{V_o}{s}$$

$$\frac{20 \times 10^{-3}}{s} = \left(\frac{s + 150}{10^4 + 50s} \right) V_o + \frac{V_o}{s}$$

$$20 \times 10^{-3} = \left(\frac{s(s + 150)}{50s + 10^4} + 1 \right) V_o$$

$$20 \times 10^{-3} = \frac{s^2 + 150s + 50s + 10^4}{50s + 10^4} V_o$$

$$\therefore V_o = \frac{20 \times 10^{-3} (50s + 10^4)}{s^2 + 200s + 10^4}$$

$$V_o = \frac{s + 200}{s^2 + 200s + 10^4} \quad (2)$$

$$\frac{s + 200}{s^2 + 200s + 10^4} = \frac{s + 200}{(s + 100)(s + 100)} = \frac{s + 200}{(s + 100)^2}$$

$$\frac{s + 200}{(s + 100)^2} = \frac{k_1}{(s + 100)^2} + \frac{k_2}{s + 100} \quad (2)$$

$$k_1 = 100$$


$$k_2 = 1$$

$$= V_o(s) = \frac{100}{(s + 100)^2} + \frac{1}{s + 100} \quad (A)$$

$$= V_o(t) = \left[100t e^{-100t} + e^{-100t} \right] u(t) \text{ Volt}$$

Question 3

20 marks.

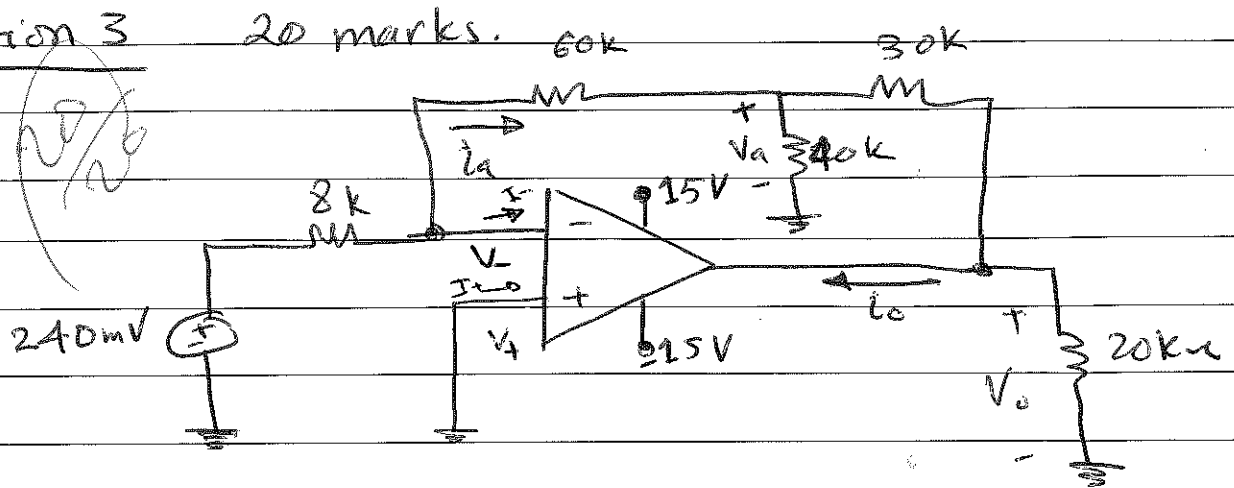

$$V_+ = V_- = 0$$

$$I_+ = I_- = 0$$

[a] $i_a = ??$

$$\frac{0 - 240\text{m}}{8\text{k}} + I_a = 0$$

5

$$\therefore I_a = \frac{240\text{m}}{8\text{k}} = 3 \times 10^{-5} = 30\text{ }\mu\text{A}$$

[b] $V_a = ?$

$$i_a = \frac{V_- - V_a}{60\text{k}} = \frac{0 - V_a}{60\text{k}}$$


5

$$\therefore V_a = -i_a \times 60\text{k}$$
$$= -3 \times 10^{-5} \times 60 \times 10^3$$

$$= -1.8 \text{ Volt}$$

(c) $V_o = ??$

KCL

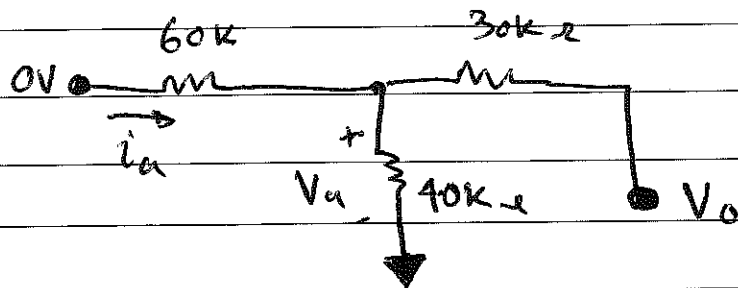

$$\frac{V_a - 0}{60k} + \frac{V_a}{40k} + \frac{V_a - V_o}{30k} = 0$$

$$\therefore V_a = -1.8 \text{ Volt}$$

$$\therefore V_o = 2.25 V_a$$

$$= -4.05 \text{ Volt.}$$

(d) $i_o = ?$

for ideal op amp $i_o = 0$

But

KCL

$$i_o + \frac{V_o}{20k} + \frac{V_o - V_a}{30k} = 0$$

$$i_o = \frac{4.05}{20k} + \frac{-4.05 + 1.8}{30k} = 0$$

$$i_o = 2.775 \times 10^{-4} = 0$$

$$i_o = 2.775 \times 10^{-4} \text{ A}$$

$$i_o = 277.5 \mu\text{A}$$