

$$\left. \begin{aligned} V_1 &= Z_{11} I_1 + Z_{12} I_2 \quad \text{--- (1)} \\ V_2 &= Z_{21} I_1 + Z_{22} I_2 \quad \text{--- (2)} \end{aligned} \right\}$$

$$\left. \begin{aligned} V_1 &= V_g - I_1 Z_g \quad \text{--- (3)} \\ V_2 &= -Z_L I_2 \quad \text{--- (4)} \end{aligned} \right\}$$

$$\boxed{1} \quad Z_{in} = \frac{V_1}{I_1}$$

$$\text{eq (2)} \quad V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$\text{(4)} \quad -Z_L I_2 = Z_{21} I_1 + Z_{22} I_2$$

$$-(Z_L + Z_{22}) I_2 = Z_{21} I_1$$

$$\boxed{I_2 = \frac{-Z_{21}}{Z_L + Z_{22}} I_1} \quad \text{--- (A)}$$

$$\begin{aligned} \text{eq (1)} \quad V_1 &= Z_{11} I_1 + Z_{12} I_2 && \text{sub (A) in (1)} \\ &= Z_{11} I_1 + \frac{-Z_{12} Z_{21}}{Z_L + Z_{22}} I_1 \end{aligned}$$

$$\therefore \boxed{Z_{in} = \frac{V_1}{I_1} = Z_{11} - \frac{Z_{12} Z_{21}}{Z_{22} + Z_L}}$$

$$\boxed{2} \quad I_2 = ??$$

$$\text{from (A)} \quad \boxed{I_1 = -\frac{Z_L + Z_{22}}{Z_{21}} I_2} \quad \text{--- (B)}$$

$$\text{eq (1)} \quad V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$\text{eq (3) in (1)}$$

$$V_g - I_1 Z_g = Z_{11} I_1 + Z_{12} I_2$$

$$Z_{12} I_2 = V_g - (Z_g + Z_{11}) I_1 \quad \text{sub (B)}$$

$$\frac{Z_{21} Z_{12} I_2}{Z_{21}} = \frac{V_g + (Z_g + Z_{11})(Z_L + Z_{22}) I_2}{Z_{21}} I_2$$

$$\left(\frac{Z_{12} Z_{21} - (V_g + Z_{11})(Z_L + Z_{22})}{Z_{21}} \right) I_2 = V_g$$

$$\therefore \boxed{I_2 = \frac{Z_{21} V_g}{Z_{12} Z_{21} - (V_g + Z_{11})(Z_L + Z_{22})}}$$

$$\boxed{3} \quad V_{Th} = ??$$

$$V_{Th} = V_2 \Big|_{I_2=0}$$

$$\therefore \text{eq (1)} \quad V_1 = Z_{11} I_1 \quad \text{--- (C)}$$

$$\text{eq (2)} \quad V_2 \Big|_{I_2=0} = Z_{21} I_1 \quad \text{--- (D)}$$

Sub (C) in (D)

$$\Rightarrow V_{Th} = \frac{Z_{21}}{Z_{11}} V_1 \quad \leftarrow$$

from (3) $V_1 = V_g - I_1 Z_g$ sub in V_{Th}

$$V_{Th} = \frac{Z_{21}}{Z_{11}} (V_g - I_1 Z_g) \quad \leftarrow$$

$$= \frac{Z_{21}}{Z_{11}} \left(V_g - \frac{V_{Th}}{Z_{21}} Z_g \right) \quad \leftarrow \begin{array}{l} \downarrow \text{from D} \\ \end{array}$$

$$\therefore V_{Th} \left(1 + \frac{Z_{21}}{Z_{11}} \frac{Z_g}{Z_{21}} \right) = \frac{Z_{21}}{Z_{11}} V_g$$

$$V_{Th} \left(\frac{Z_{11} + Z_g}{Z_{11}} \right) = \frac{Z_{21}}{Z_{11}} V_g$$

$$\boxed{V_{Th} = \frac{Z_{21}}{Z_{11} + Z_g} V_g}$$

OR

$$V_1 = Z_{11} I_1$$

$$V_g - I_1 Z_g = Z_{11} I_1$$

$$\therefore \boxed{I_1 = \frac{V_g}{Z_{11} + Z_g}}$$

$$\rightarrow V_{Th} = \frac{Z_{21}}{Z_{11}} \left(V_g - \frac{Z_g V_g}{Z_{11} + Z_g} \right)$$

$$= V_g \left(\frac{Z_{21}}{Z_{11}} - \frac{Z_{21} Z_g}{Z_{11} (Z_{11} + Z_g)} \right)$$

$$= \frac{Z_{21}}{Z_{11}} V_g \left(1 - \frac{Z_g}{Z_{11} + Z_g} \right)$$

$$= \frac{Z_{21}}{Z_{11}} V_g \left(\frac{Z_{11}}{Z_{11} + Z_g} \right)$$

$$\boxed{V_{Th} = \frac{Z_{21}}{Z_{11} + Z_g} V_g}$$

[4] Thev. impedance = output impedance

$$Z_{Th} = \left. \frac{V_2}{I_2} \right|_{V_g=0} \quad V_g \text{ is S.C.}$$

When $V_g=0$, eq (3) becomes

$$V_1 = -I_1 Z_g$$

sub in (1)

$$-I_1 Z_g = Z_{11} I_1 + Z_{12} I_2$$

$$I_1 (Z_{11} + Z_g) = -Z_{12} I_2$$

$$I_1 = -\frac{Z_{12}}{Z_{11} + Z_g} I_2 \quad \text{--- (E)}$$

sub (E) in (2)

$$\left. V_2 \right|_{V_g=0} = Z_{21} I_1 + Z_{22} I_2$$

$$= \left(\frac{-Z_{21} Z_{12}}{Z_{11} + Z_g} + Z_{22} \right) I_2$$

$$\therefore \left. \frac{V_2}{I_2} \right|_{V_g=0} = Z_{Th} = Z_{22} - \frac{Z_{12} Z_{21}}{Z_{11} + Z_g}$$

[5] Current gain $\frac{I_2}{I_1}$

Directly from (A) OR (B)

$$\frac{I_2}{I_1} = \frac{-Z_{21}}{Z_L + Z_{22}}$$

5 Voltage current gain $\left(\frac{V_2}{V_1}\right)$

from (2) $V_2 = Z_{21} I_1 + Z_{22} I_2$

from (4)

$$I_2 = \frac{-V_2}{Z_L} \quad \text{--- (X)}$$

Sub X in (2)

$$V_2 = Z_{21} I_1 - \frac{Z_{22}}{Z_L} V_2 \quad \text{--- (F)}$$

from (1)

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

Sub X in (1)

$$V_1 = Z_{11} I_1 - \frac{Z_{12}}{Z_L} V_2$$

$$I_1 = \frac{V_1}{Z_{11}} + \frac{Z_{12}}{Z_{11} Z_L} V_2 \quad \text{--- (G)}$$

Sub (G) in (F)

$$V_2 = Z_{21} \left(\frac{V_1}{Z_{11}} + \frac{Z_{12}}{Z_{11} Z_L} V_2 \right) - \frac{Z_{22}}{Z_L} V_2$$

$$= \frac{Z_{21}}{Z_{11}} V_1 + \frac{Z_{12} Z_{21}}{Z_{11} Z_L} V_2 - \frac{Z_{22}}{Z_L} V_2$$

$$V_2 \left(1 - \frac{Z_{12} Z_{21}}{Z_{11} Z_L} + \frac{Z_{22}}{Z_L} \right) = \frac{Z_{21}}{Z_{11}} V_1$$

$$V_2 \left(\frac{Z_{11} Z_L - Z_{12} Z_{21} + Z_{11} Z_{22}}{Z_{11} Z_L} \right) = \frac{Z_{21}}{Z_{11}} V_1$$

$$V_2 \left(\frac{Z_{11} Z_L + Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{11} Z_L} \right) = \frac{Z_{21}}{Z_{11}} V_1$$

$$\frac{V_2}{V_1} = \frac{Z_{21} Z_L}{Z_{11} Z_L + \underbrace{Z_{11} Z_{22} - Z_{12} Z_{21}}_{\Delta Z}}$$
$$= \frac{Z_{21} Z_L}{Z_{11} Z_L + \Delta Z}$$

7 The Voltage ratio $\frac{V_2}{V_g}$

Combine (1), (3), (4) to find I_1

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_g - I_1 Z_g = Z_{11} I_1 + Z_{12} \left(\frac{-V_2}{Z_L} \right)$$

$$I_1 (Z_g + Z_{11}) = V_g + \frac{Z_{12}}{Z_L} V_2$$

$$I_1 = \frac{V_g}{Z_g + Z_{11}} + \frac{Z_{12}}{Z_L (Z_g + Z_{11})} V_2 \quad \text{--- (H)}$$

Combine (4) & (H) with (2)

eq(2) $V_2 = Z_{21} I_1 + Z_{22} I_2$

$$V_2 = \frac{Z_{21}}{Z_g + Z_{11}} V_g + \frac{Z_{12} Z_{21}}{Z_L (Z_g + Z_{11})} V_2 - \frac{Z_{22}}{Z_L} V_2$$

$$V_2 \left(1 + \frac{Z_{22} (Z_g + Z_{11})}{Z_L (Z_g + Z_{11})} - \frac{Z_{12} Z_{21}}{Z_L (Z_g + Z_{11})} \right) = \frac{Z_{21}}{Z_g + Z_{11}} V_g$$

$$V_2 \left(\frac{Z_L (Z_g + Z_{11}) + Z_{22} (Z_g + Z_{11}) - Z_{12} Z_{21}}{Z_L (Z_g + Z_{11})} \right) = \frac{Z_{21}}{(Z_g + Z_{11})} V_g$$

$$\frac{V_2}{V_g} = \frac{Z_{21} Z_L}{Z_L (Z_g + Z_{11}) + Z_{22} (Z_g + Z_{11}) - Z_{12} Z_{21}}$$

OR

$$\frac{V_2}{V_g} = \frac{Z_{21} Z_L}{(Z_{11} + Z_g)(Z_{22} + Z_L) - Z_{12} Z_{21}}$$