

JAMES W. NILSSON
&
SUSAN A. RIEDEL

ELECTRIC
CIRCUITS
EIGHTH EDITION



CHAPTER 18

Two-Port Circuits Part 2

© 2008 Pearson Education


CONTENTS

- 18.1 The Terminal Equations
- 18.2 The Two-Port Parameters
- 18.3 Analysis of the Terminated Two-Port Circuit
- 18.4 Interconnected Two-Port Circuits

© 2008 Pearson Education

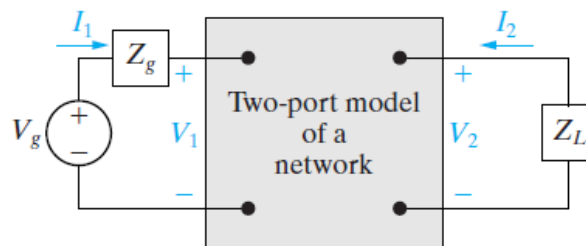18.3 Analysis of the Terminated Two-Port Circuit

- In the typical application of a two-port model, the circuit is driven at port 1 and loaded at port 2.
- The goal is to solve $\{V_1, I_1, V_2, I_2\}$ as functions of given parameters V_g , Z_g , Z_L , and matrix elements of the two-port circuit.



18.3 Analysis of the Terminated Two-Port Circuit

- Six characteristics of the terminated two-port circuit define its terminal behavior:
 1. the input impedance $Z_{in} = V_1/I_1$, or the admittance $Y_{in} = I_1/V_1$.
 2. the output current I_2 .
 3. the Thévenin voltage and impedance (V_{TH}, Z_{TH}) with respect to port 2
 4. the current gain I_2/I_1
 5. the voltage gain V_2/V_1
 6. the voltage gain V_2/V_g

Analysis in terms of $[Z]$

- Four equations are needed to solve the four unknowns $\{V_1, I_1, V_2, I_2\}$.

$$\left\{ \begin{array}{l} V_1 = z_{11}I_1 + z_{12}I_2 \cdots (1) \\ V_2 = z_{21}I_1 + z_{22}I_2 \cdots (2) \end{array} \right. \text{Two-Port equations}$$


$$\left\{ \begin{array}{l} V_1 = V_g - I_1 Z_g \cdots (3) \\ V_2 = -I_2 Z_L \cdots (4) \end{array} \right. \text{Constraint equations due to terminations}$$

Analysis in terms of $[Z]$

$$\Rightarrow \begin{bmatrix} -1 & 0 & z_{11} & z_{12} \\ 0 & -1 & z_{21} & z_{22} \\ 1 & 0 & Z_g & 0 \\ 0 & 1 & 0 & Z_L \end{bmatrix} \times \begin{bmatrix} V_1 \\ V_2 \\ I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ V_g \\ 0 \end{bmatrix}, \quad \{V_1, I_1, V_2, I_2\} \text{ are derived by inverse matrix method.}$$

Thévenin equivalent circuit with respect to port 2

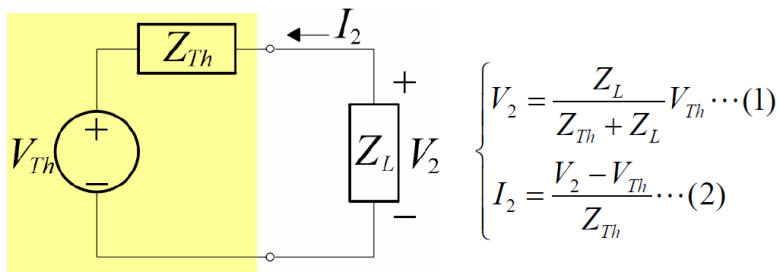- Once $\{V_1, I_1, V_2, I_2\}$ are solved, $\{V_{Th}, Z_{Th}\}$ can be determined by Z_L and $\{V_2, I_2\}$:




$$\Rightarrow \begin{bmatrix} Z_L & -V_2 \\ 1 & I_2 \end{bmatrix} \times \begin{bmatrix} V_{Th} \\ Z_{Th} \end{bmatrix} = \begin{bmatrix} V_2 Z_L \\ V_2 \end{bmatrix}; \quad \begin{bmatrix} V_{Th} \\ Z_{Th} \end{bmatrix} = \begin{bmatrix} Z_L & -V_2 \\ 1 & I_2 \end{bmatrix}^{-1} \times \begin{bmatrix} V_2 Z_L \\ V_2 \end{bmatrix}.$$

Terminal behavior (1)

- The terminal behavior of the circuit can be described by manipulations of $\{V_1, I_1, V_2, I_2\}$:
- Input impedance: $Z_{in} \equiv \frac{V_1}{I_1} = z_{11} - \frac{z_{12}z_{21}}{z_{22} + Z_L}$;
- Output current: $I_2 = \frac{-z_{21}V_g}{(z_{11} + Z_g)(z_{22} + Z_L) - z_{12}z_{21}}$;
- Current gain: $\frac{I_2}{I_1} = -\frac{z_{21}}{z_{22} + Z_L}$;
- Voltage gains: $\begin{cases} \frac{V_2}{V_1} = \frac{z_{21}Z_L}{z_{11}Z_L + \Delta z} \\ \frac{V_2}{V_g} = \frac{z_{21}Z_L}{(z_{11} + Z_g)(z_{22} + Z_L) - z_{12}z_{21}} \end{cases}$;

Terminal behavior (2)

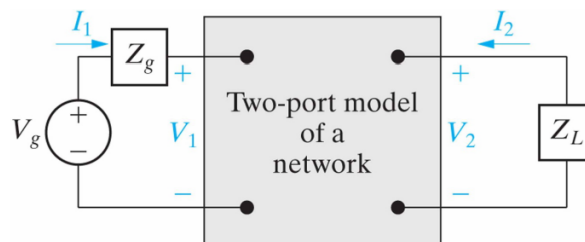- Thévenin voltage: $V_{Th} = \frac{z_{21}}{z_{11} + Z_g} V_g$;
- Thévenin impedance: $Z_{Th} = z_{22} - \frac{z_{12}z_{21}}{z_{11} + Z_g}$;



Analysis in term of a two-port matrix $[T] \neq [Z]$

- If the two-port circuit is modeled by $[T] \neq [Z]$...

$$T = \{Y, A, B, H, G\},$$

the terminal behavior can be determined by two methods:

1. Use the 2 two-port equations of $[T]$ to get a new 4X4 matrix in solving $\{V_1, I_1, V_2, I_2\}$ (Table 18.2);
2. Transform $[T]$ into $[Z]$ by Table 18.1, borrow the formulas derived by analysis in terms of $[Z]$.

TABLE 18.1 Parameter Conversion Table

$$z_{11} = \frac{y_{22}}{\Delta y} = \frac{a_{11}}{a_{21}} = \frac{b_{22}}{b_{21}} = \frac{\Delta h}{h_{22}} = \frac{1}{g_{11}}$$

$$z_{12} = -\frac{y_{12}}{\Delta y} = \frac{\Delta a}{a_{21}} = \frac{1}{b_{21}} = \frac{h_{12}}{h_{22}} = -\frac{g_{12}}{g_{11}}$$

$$z_{21} = \frac{-y_{21}}{\Delta y} = \frac{1}{a_{21}} = \frac{\Delta b}{b_{21}} = \frac{h_{21}}{h_{22}} = \frac{g_{21}}{g_{11}}$$

$$z_{22} = \frac{y_{11}}{\Delta y} = \frac{a_{22}}{a_{21}} = \frac{b_{11}}{b_{21}} = \frac{1}{h_{22}} = \frac{\Delta g}{g_{11}}$$

$$y_{11} = \frac{z_{22}}{\Delta z} = \frac{a_{22}}{a_{12}} = \frac{b_{11}}{b_{12}} = \frac{1}{h_{11}} = \frac{\Delta g}{g_{22}}$$

$$y_{12} = -\frac{z_{12}}{\Delta z} = -\frac{\Delta a}{a_{12}} = -\frac{1}{b_{12}} = -\frac{h_{12}}{h_{11}} = \frac{g_{12}}{g_{22}}$$

$$y_{21} = -\frac{z_{21}}{\Delta z} = -\frac{1}{a_{12}} = -\frac{\Delta b}{b_{12}} = -\frac{h_{21}}{h_{11}} = -\frac{g_{21}}{g_{22}}$$

$$y_{22} = \frac{z_{11}}{\Delta z} = \frac{a_{11}}{a_{12}} = \frac{b_{22}}{b_{12}} = \frac{\Delta h}{h_{11}} = \frac{1}{g_{22}}$$

$$a_{11} = \frac{z_{11}}{z_{21}} = \frac{y_{22}}{y_{21}} = \frac{b_{22}}{\Delta b} = \frac{\Delta h}{h_{21}} = \frac{1}{g_{21}}$$

$$a_{12} = \frac{\Delta z}{z_{21}} = -\frac{1}{y_{21}} = \frac{b_{12}}{\Delta b} = -\frac{h_{11}}{h_{21}} = \frac{g_{22}}{g_{21}}$$

$$a_{21} = \frac{1}{z_{21}} = -\frac{\Delta y}{y_{21}} = \frac{b_{21}}{\Delta b} = -\frac{h_{22}}{h_{21}} = \frac{g_{11}}{g_{21}}$$

$$a_{22} = \frac{z_{22}}{z_{21}} = -\frac{y_{11}}{y_{21}} = \frac{b_{11}}{\Delta b} = -\frac{1}{h_{21}} = \frac{\Delta g}{g_{21}}$$

$$b_{11} = \frac{z_{22}}{z_{12}} = \frac{y_{11}}{y_{12}} = \frac{a_{22}}{\Delta a} = \frac{1}{h_{12}} = -\frac{\Delta g}{g_{12}}$$

$$b_{12} = \frac{\Delta z}{z_{12}} = -\frac{1}{y_{12}} = \frac{a_{12}}{\Delta a} = \frac{h_{11}}{h_{12}} = -\frac{g_{22}}{g_{12}}$$

$$b_{21} = \frac{1}{z_{12}} = \frac{\Delta y}{y_{12}} = \frac{a_{21}}{\Delta a} = \frac{h_{22}}{h_{12}} = \frac{g_{11}}{g_{12}}$$

$$b_{22} = \frac{z_{11}}{z_{12}} = \frac{y_{22}}{y_{12}} = \frac{a_{11}}{\Delta a} = \frac{\Delta h}{h_{12}} = -\frac{1}{g_{12}}$$

TABLE 18.1 Parameter Conversion Table

$$\begin{aligned}
 h_{11} &= \frac{\Delta z}{z_{22}} = \frac{1}{y_{11}} = \frac{a_{12}}{a_{22}} = \frac{b_{12}}{b_{11}} = \frac{g_{22}}{\Delta g} \\
 h_{12} &= \frac{z_{12}}{z_{22}} = -\frac{y_{12}}{y_{11}} = \frac{\Delta a}{a_{22}} = \frac{1}{b_{11}} = -\frac{g_{12}}{\Delta g} \\
 h_{21} &= -\frac{z_{21}}{z_{22}} = \frac{y_{21}}{y_{11}} = -\frac{1}{a_{22}} = -\frac{\Delta b}{b_{11}} = -\frac{g_{21}}{\Delta g} \\
 h_{22} &= \frac{1}{z_{22}} = \frac{\Delta y}{y_{11}} = \frac{a_{21}}{a_{22}} = \frac{b_{21}}{b_{11}} = \frac{g_{11}}{\Delta g} \\
 g_{11} &= \frac{1}{z_{11}} = \frac{\Delta y}{y_{22}} = \frac{a_{21}}{a_{11}} = \frac{b_{21}}{b_{22}} = \frac{h_{22}}{\Delta h} \\
 g_{12} &= -\frac{z_{12}}{z_{11}} = \frac{y_{12}}{y_{22}} = -\frac{\Delta a}{a_{11}} = -\frac{1}{b_{22}} = -\frac{h_{12}}{\Delta h} \\
 g_{21} &= \frac{z_{21}}{z_{11}} = -\frac{y_{21}}{y_{22}} = \frac{1}{a_{11}} = \frac{\Delta b}{b_{22}} = -\frac{h_{21}}{\Delta h} \\
 g_{22} &= \frac{\Delta z}{z_{11}} = \frac{1}{y_{22}} = \frac{a_{12}}{a_{11}} = \frac{b_{12}}{b_{22}} = \frac{h_{11}}{\Delta h}
 \end{aligned}$$

$$\begin{aligned}
 \Delta z &= z_{11}z_{22} - z_{12}z_{21} \\
 \Delta y &= y_{11}y_{22} - y_{12}y_{21} \\
 \Delta a &= a_{11}a_{22} - a_{12}a_{21} \\
 \Delta b &= b_{11}b_{22} - b_{12}b_{21} \\
 \Delta h &= h_{11}h_{22} - h_{12}h_{21} \\
 \Delta g &= g_{11}g_{22} - g_{12}g_{21}
 \end{aligned}$$

TABLE 18.2 Terminated Two-Port Equations

<u>z Parameters</u>	<u>y Parameters</u>
$Z_{in} = z_{11} - \frac{z_{12}z_{21}}{z_{22} + Z_L}$	$Y_{in} = y_{11} - \frac{y_{12}y_{21}Z_L}{1 + y_{22}Z_L}$
$I_2 = \frac{-z_{21}V_g}{(z_{11} + Z_g)(z_{22} + Z_L) - z_{12}z_{21}}$	$I_2 = \frac{y_{21}V_g}{1 + y_{22}Z_L + y_{11}Z_g + \Delta yZ_gZ_L}$
$V_{Th} = \frac{z_{21}}{z_{11} + Z_g}V_g$	$V_{Th} = \frac{-y_{21}V_g}{y_{22} + \Delta yZ_g}$
$Z_{Th} = z_{22} - \frac{z_{12}z_{21}}{z_{11} + Z_g}$	$Z_{Th} = \frac{1 + y_{11}Z_g}{y_{22} + \Delta yZ_g}$
$\frac{I_2}{I_1} = \frac{-z_{21}}{z_{22} + Z_L}$	$\frac{I_2}{I_1} = \frac{y_{21}}{y_{11} + \Delta yZ_L}$
$\frac{V_2}{V_1} = \frac{z_{21}Z_L}{z_{11}Z_L + \Delta z}$	$\frac{V_2}{V_1} = \frac{-y_{21}Z_L}{1 + y_{22}Z_L}$
$\frac{V_2}{V_g} = \frac{z_{21}Z_L}{(z_{11} + Z_g)(z_{22} + Z_L) - z_{12}z_{21}}$	$\frac{V_2}{V_g} = \frac{y_{21}Z_L}{y_{12}y_{21}Z_gZ_L - (1 + y_{11}Z_g)(1 + y_{22}Z_L)}$

TABLE 18.2 Terminated Two-Port Equations

<i>a</i> Parameters	<i>b</i> Parameters
$Z_{in} = \frac{a_{11}Z_L + a_{12}}{a_{21}Z_L + a_{22}}$	$Z_{in} = \frac{b_{22}Z_L + b_{12}}{b_{21}Z_L + b_{11}}$
$I_2 = \frac{-V_g}{a_{11}Z_L + a_{12} + a_{21}Z_gZ_L + a_{22}Z_g}$	$I_2 = \frac{-V_g\Delta b}{b_{11}Z_g + b_{21}Z_gZ_L + b_{22}Z_L + b_{12}}$
$V_{Th} = \frac{V_g}{a_{11} + a_{21}Z_g}$	$V_{Th} = \frac{V_g\Delta b}{b_{22} + b_{21}Z_g}$
$Z_{Th} = \frac{a_{12} + a_{22}Z_g}{a_{11} + a_{21}Z_g}$	$Z_{Th} = \frac{b_{11}Z_g + b_{12}}{b_{21}Z_g + b_{22}}$
$\frac{I_2}{I_1} = \frac{-1}{a_{21}Z_L + a_{22}}$	$\frac{I_2}{I_1} = \frac{-\Delta b}{b_{11} + b_{21}Z_L}$
$\frac{V_2}{V_1} = \frac{Z_L}{a_{11}Z_L + a_{12}}$	$\frac{V_2}{V_1} = \frac{\Delta bZ_L}{b_{12} + b_{22}Z_L}$
$\frac{V_2}{V_g} = \frac{Z_L}{(a_{11} + a_{21}Z_g)Z_L + a_{12} + a_{22}Z_g}$	$\frac{V_2}{V_g} = \frac{\Delta bZ_L}{b_{12} + b_{11}Z_g + b_{22}Z_L + b_{21}Z_gZ_L}$

TABLE 18.2 Terminated Two-Port Equations

<i>h</i> Parameters	<i>g</i> Parameters
$Z_{in} = h_{11} - \frac{h_{12}h_{21}Z_L}{1 + h_{22}Z_L}$	$Y_{in} = g_{11} - \frac{g_{12}g_{21}}{g_{22} + Z_L}$
$I_2 = \frac{h_{21}V_g}{(1 + h_{22}Z_L)(h_{11} + Z_g) - h_{12}h_{21}Z_L}$	$I_2 = \frac{-g_{21}V_g}{(1 + g_{11}Z_g)(g_{22} + Z_L) - g_{12}g_{21}Z_g}$
$V_{Th} = \frac{-h_{21}V_g}{h_{22}Z_g + \Delta h}$	$V_{Th} = \frac{g_{21}V_g}{1 + g_{11}Z_g}$
$Z_{Th} = \frac{Z_g + h_{11}}{h_{22}Z_g + \Delta h}$	$Z_{Th} = g_{22} - \frac{g_{12}g_{21}Z_g}{1 + g_{11}Z_g}$
$\frac{I_2}{I_1} = \frac{h_{21}}{1 + h_{22}Z_L}$	$\frac{I_2}{I_1} = \frac{-g_{21}}{g_{11}Z_L + \Delta g}$
$\frac{V_2}{V_1} = \frac{-h_{21}Z_L}{\Delta hZ_L + h_{11}}$	$\frac{V_2}{V_1} = \frac{g_{21}Z_L}{g_{22} + Z_L}$
$\frac{V_2}{V_g} = \frac{-h_{21}Z_L}{(h_{11} + Z_g)(1 + h_{22}Z_L) - h_{12}h_{21}Z_L}$	$\frac{V_2}{V_g} = \frac{g_{21}Z_L}{(1 + g_{11}Z_g)(g_{22} + Z_L) - g_{12}g_{21}Z_g}$

Example 18.4 Analyzing a Terminated Two-Port Circuit

The two-port circuit shown in Fig. 18.8 is described in terms of its b parameters, the values of which are

$$\begin{aligned} b_{11} &= -20, & b_{12} &= -3000 \Omega, \\ b_{21} &= -2 \text{ mS}, & b_{22} &= -0.2. \end{aligned}$$

- Find the phasor voltage \mathbf{V}_2 .
- Find the average power delivered to the $5 \text{ k}\Omega$ load.
- Find the average power delivered to the input port.
- Find the load impedance for maximum average power transfer.
- Find the maximum average power delivered to the load in (d).

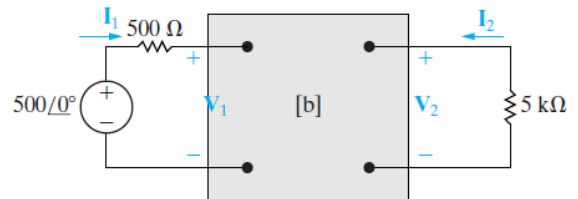


Figure 18.8 ▲ The circuit for Example 18.4.

Solution

- a) To find \mathbf{V}_2 , we have two choices from the entries in Table 18.2. We may choose to find \mathbf{I}_2 and then find \mathbf{V}_2 from the relationship $\mathbf{V}_2 = -\mathbf{I}_2 Z_L$, or we may find the voltage gain $\mathbf{V}_2/\mathbf{V}_g$ and calculate \mathbf{V}_2 from the gain. Let's use the latter approach. For the b -parameter values given, we have

$$\begin{aligned} \Delta b &= (-20)(-0.2) - (-3000)(-2 \times 10^{-3}) \\ &= 4 - 6 = -2. \end{aligned}$$

From Table 18.2,

$$\begin{aligned} \frac{\mathbf{V}_2}{\mathbf{V}_g} &= \frac{\Delta b Z_L}{b_{12} + b_{11} Z_g + b_{22} Z_L + b_{21} Z_g Z_L} \\ &= \frac{(-2)(5000)}{-3000 + (-20)500 + (-0.2)5000 + [-2 \times 10^{-3}(500)(5000)]} \\ &= \frac{10}{19}. \end{aligned}$$

Then,

$$\mathbf{V}_2 = \left(\frac{10}{19}\right)500 = 263.16 \angle 0^\circ \text{ V.}$$

- b) The average power delivered to the 5000Ω load is

$$P_2 = \frac{263.16^2}{2(5000)} = 6.93 \text{ W.}$$

- c) To find the average power delivered to the input port, we first find the input impedance Z_{in} . From Table 18.2,

$$\begin{aligned} Z_{in} &= \frac{b_{22} Z_L + b_{12}}{b_{21} Z_L + b_{11}} \\ &= \frac{(-0.2)(5000) - 3000}{-2 \times 10^{-3}(5000) - 20} \\ &= \frac{400}{3} = 133.33 \Omega. \end{aligned}$$

Now \mathbf{I}_1 follows directly:

$$\mathbf{I}_1 = \frac{500}{500 + 133.33} = 789.47 \text{ mA.}$$

The average power delivered to the input port is

$$P_1 = \frac{0.78947^2}{2}(133.33) = 41.55 \text{ W.}$$

d) The load impedance for maximum power transfer equals the conjugate of the Thévenin impedance seen looking into port 2. From Table 18.2,

$$\begin{aligned} Z_{\text{Th}} &= \frac{b_{11}Z_g + b_{12}}{b_{21}Z_g + b_{22}} \\ &= \frac{(-20)(500) - 3000}{(-2 \times 10^{-3})(500) - 0.2} \\ &= \frac{13,000}{1.2} = 10,833.33 \, \Omega. \end{aligned}$$

Therefore $Z_L = Z_{\text{Th}}^* = 10,833.33 \, \Omega$.

e) To find the maximum average power delivered to Z_L , we first find V_2 from the voltage-gain expression V_2/V_g . When Z_L is $10,833.33 \, \Omega$, this gain is

$$\frac{V_2}{V_g} = 0.8333.$$

Thus

$$V_2 = (0.8333)(500) = 416.67 \, \text{V},$$

and

$$\begin{aligned} P_L(\text{maximum}) &= \frac{1}{2} \frac{416.67^2}{10,833.33} \\ &= 8.01 \, \text{W}. \end{aligned}$$


Section 18.4 Interconnected Two-Port Circuits

- Why interconnected?

Design of a large system is simplified by first designing subsections (usually modeled by two-port circuits), then interconnecting these units to complete the system.

Section 18.4 Interconnected Two-Port Circuits

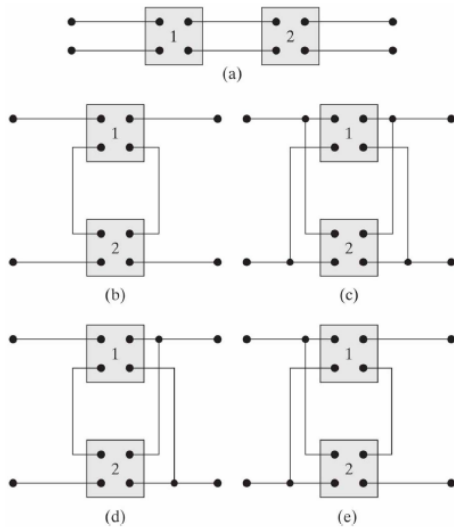Five types of interconnections of two-port circuits



a. Cascade: Better use $[A]$.

b. Series: $[Z]$

c. Parallel: $[Y]$


d. Series-parallel: $[H]$.

e. Parallel-series: $[G]$.

Section 18.4 Interconnected Two-Port Circuits

Analysis of cascade connection

- Goal: Derive the overall matrix $[A]$ of two cascaded two-port circuits with known transmission matrixes $[A']$ and $[A'']$.

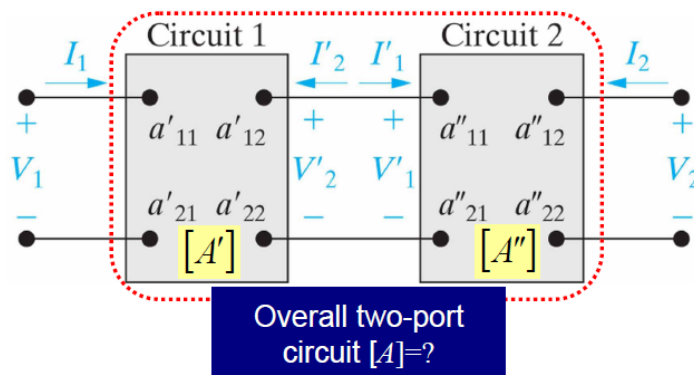

Section 18.4 Interconnected Two-Port Circuits

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = [A'] \times \begin{bmatrix} V_2' \\ I_2' \end{bmatrix} = [A'] \times \begin{bmatrix} V_1' \\ -I_1' \end{bmatrix} \dots (1)$$

$$\begin{bmatrix} V_1' \\ I_1' \end{bmatrix} = [A''] \times \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} a''_{11} & -a''_{12} \\ a''_{21} & -a''_{22} \end{bmatrix} \times \begin{bmatrix} V_2 \\ I_2 \end{bmatrix},$$

$$\Rightarrow \begin{bmatrix} V_1' \\ -I_1' \end{bmatrix} = \begin{bmatrix} a''_{11} & -a''_{12} \\ -a''_{21} & a''_{22} \end{bmatrix} \times \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = [A''] \times \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} \dots (2)$$

$$\text{By (1), (2), } \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = [A'] \times [A''] \times \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = [A] \times \begin{bmatrix} V_2 \\ I_2 \end{bmatrix},$$

$$\Rightarrow [A] = [A'] \times [A''], \begin{bmatrix} a_{11} & -a_{12} \\ a_{21} & -a_{22} \end{bmatrix} = \begin{bmatrix} a'_{11}a''_{11} + a'_{12}a''_{21} & -(a'_{11}a''_{12} + a'_{12}a''_{22}) \\ a'_{21}a''_{11} + a'_{22}a''_{21} & -(a'_{21}a''_{12} + a'_{22}a''_{22}) \end{bmatrix}$$

Section 18.4 Interconnected Two-Port Circuits

Key points

- How to calculate the 6 possible 2X2 matrices of a two-port circuit?
- How to find the 4 simultaneous equations in solving a terminated two-port circuit?
- How to find the total 2X2 matrix of a circuit consisting of interconnected two-port circuits?

Example 18.5 Analyzing Cascaded Two-Port Circuits

Two identical amplifiers are connected in cascade, as shown in Fig. 18.11. Each amplifier is described in terms of its h parameters. The values are $h_{11} = 1000 \Omega$, $h_{12} = 0.0015$, $h_{21} = 100$, and $h_{22} = 100 \mu\text{S}$. Find the voltage gain V_2/V_g .

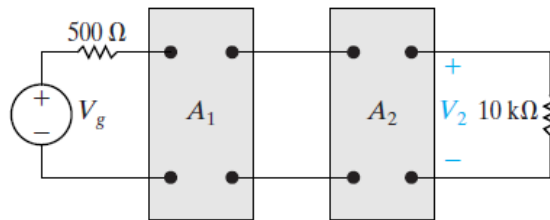


Figure 18.11 ▲ The circuit for Example 18.5.

Solution

The first step in finding V_2/V_g is to convert from h parameters to a parameters. The amplifiers are identical, so one set of a parameters describes the amplifiers:

$$a'_{11} = \frac{-\Delta h}{h_{21}} = \frac{+0.05}{100} = 5 \times 10^{-4},$$

$$a'_{12} = \frac{-h_{11}}{h_{21}} = \frac{-1000}{100} = -10 \Omega,$$

$$a'_{21} = \frac{-h_{22}}{h_{21}} = \frac{-100 \times 10^{-6}}{100} = -10^{-6} \text{ S},$$

$$a'_{22} = \frac{-1}{h_{21}} = \frac{-1}{100} = -10^{-2}.$$

Next we use Eqs. 18.74–18.77 to compute the a parameters of the cascaded amplifiers:

$$\begin{aligned} a_{11} &= a'_{11}a'_{11} + a'_{12}a'_{21} \\ &= 25 \times 10^{-8} + (-10)(-10^{-6}) \\ &= 10.25 \times 10^{-6}, \end{aligned}$$

$$\begin{aligned} a_{12} &= a'_{11}a'_{12} + a'_{12}a'_{22} \\ &= (5 \times 10^{-4})(-10) + (-10)(-10^{-2}) \\ &= 0.095 \Omega, \end{aligned}$$

$$\begin{aligned} a_{21} &= a'_{21}a'_{11} + a'_{22}a'_{21} \\ &= (-10^{-6})(5 \times 10^{-4}) + (-0.01)(-10^{-6}) \\ &= 9.5 \times 10^{-9} \text{ S}, \end{aligned}$$

$$\begin{aligned} a_{22} &= a'_{21}a'_{12} + a'_{22}a'_{22} \\ &= (-10^{-6})(-10) + (-10^{-2})^2 \\ &= 1.1 \times 10^{-4}. \end{aligned}$$

From Table 18.2,

$$\begin{aligned} \frac{V_2}{V_g} &= \frac{Z_L}{(a_{11} + a_{21}Z_g)Z_L + a_{12} + a_{22}Z_g} \\ &= \frac{10^4}{[10.25 \times 10^{-6} + 9.5 \times 10^{-9}(500)]10^4 + 0.095 + 1.1 \times 10^{-4}(500)} \\ &= \frac{10^4}{0.15 + 0.095 + 0.055} \\ &= \frac{10^5}{3} \\ &= 33,333.33. \end{aligned}$$

Thus an input signal of $150 \mu\text{V}$ is amplified to an output signal of 5 V. For an alternative approach to finding the voltage gain V_2/V_g , see Problem 18.41.