
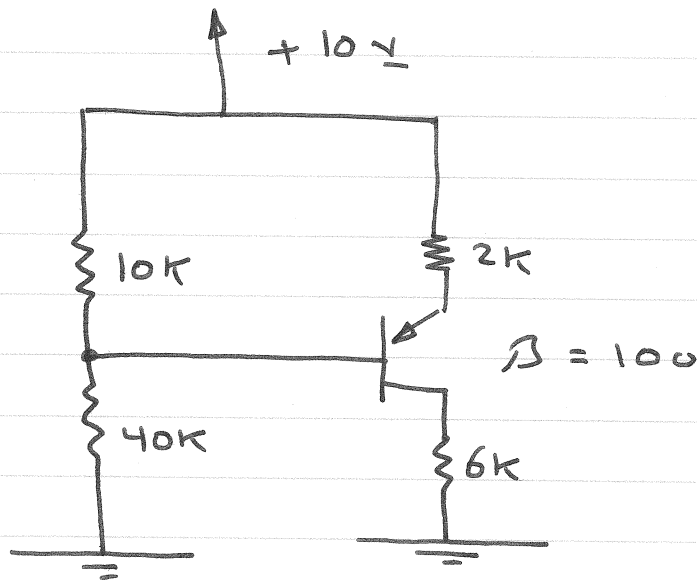


Circuit using pnp Transistor

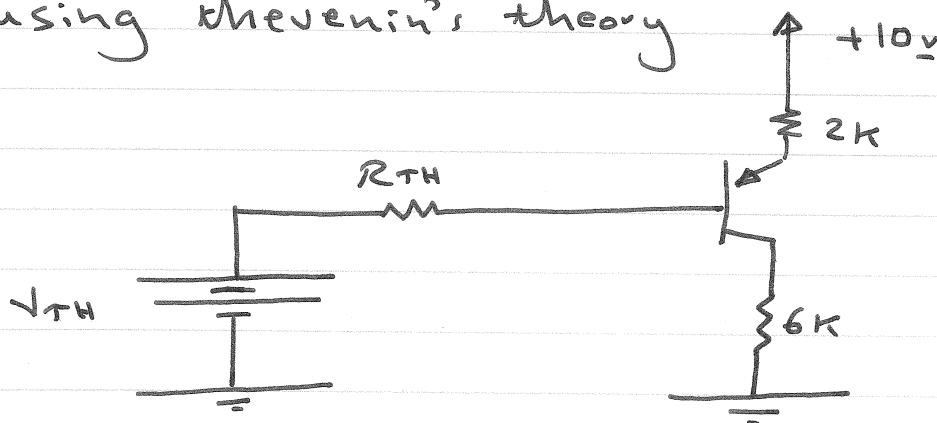

using Thevenin's theory



$$R_{TH} = 10k \parallel 40k = 8k$$

$$V_{TH} = \frac{40k}{10k + 40k} \cdot 10 = 8V$$

$$KVL: \quad 10 = 2k I_E + V_{EB} + R_{TH} I_B + V_{TH}$$

$$\therefore I_E = 0.625 \text{ mA}$$

$$KVL: \quad 10 = 2k I_E + V_{EC} + 6k I_C$$


$$\therefore V_{EC} = 5V$$

Example

Design the given circuit so that

$$I_{CQ} = 2 \text{ mA}, \text{ and } V_C = 5 \text{ V}$$

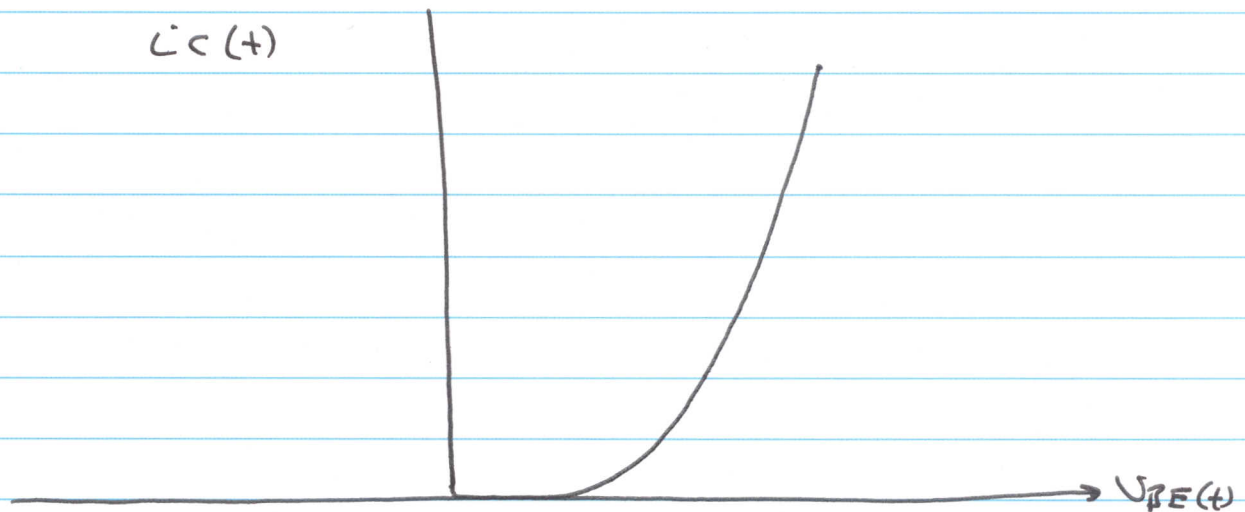given that $V_{BE} = 0.7 \text{ V}$ @ $I_C = 1 \text{ mA}$
 $\beta = \infty$



$$I_C(t) \approx I_S e^{\frac{V_{BE}(t)}{V_T}}$$

$$I_C \approx I_S e^{\frac{V_{BE}}{V_T}}$$

$$V_{BE} = V_T \ln \frac{I_C}{I_S}$$

in our circuit $I_C = 2 \text{ mA}$, we must

find the corresponding V_{BE}

$$V_{BE} = ? \text{ @ } I_C = 2 \text{ mA}$$

$$V_{BE1} = 0.7 = V_T \ln \frac{1mA}{I_S}$$

$$V_{BE2} = ? = V_T \ln \frac{2mA}{I_S}$$

$$V_{BE2} - V_{BE1} = V_T \ln \frac{I_{C2}}{I_{C1}}$$


$$V_{BE2} = V_{BE1} + V_T \ln \frac{2mA}{1mA}$$


$$\therefore V_{BE2} = 0.717 \text{ V}$$

∴

$$V_{BE} = 0.717 \text{ V} @ I_C = 2mA$$

The circuit that to be designed is

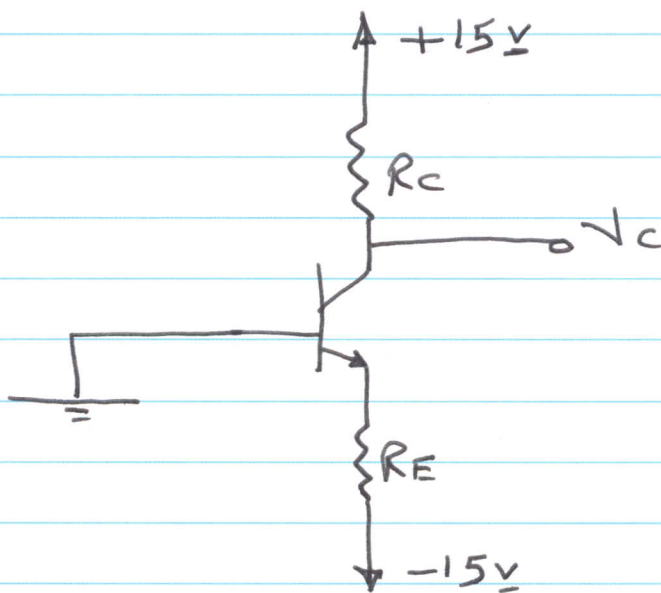

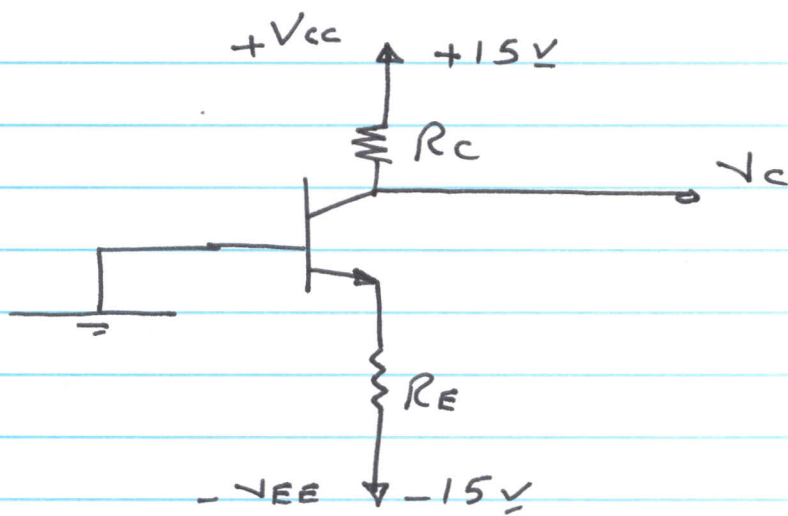

$$V_C = V_{CC} - R_C I_C$$

$$\therefore R_C = \frac{V_{CC} - V_C}{I_C}$$



$$R_C = \frac{15 - 5}{2\text{mA}} = 5\text{k}$$

KVL :

$$V_{BE} + R_E I_E - 15 = 0$$

$$\therefore R_E = \frac{15 - V_{BE}}{I_E} = 7\text{k}$$

Example

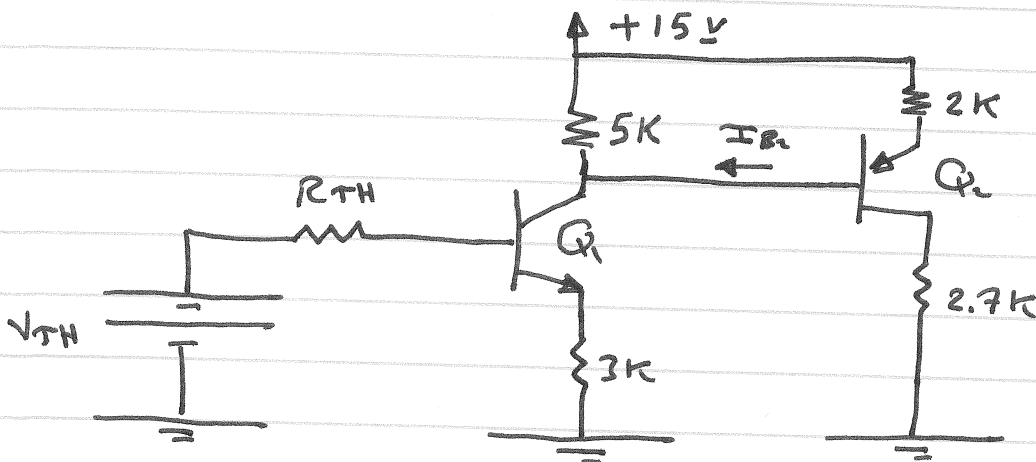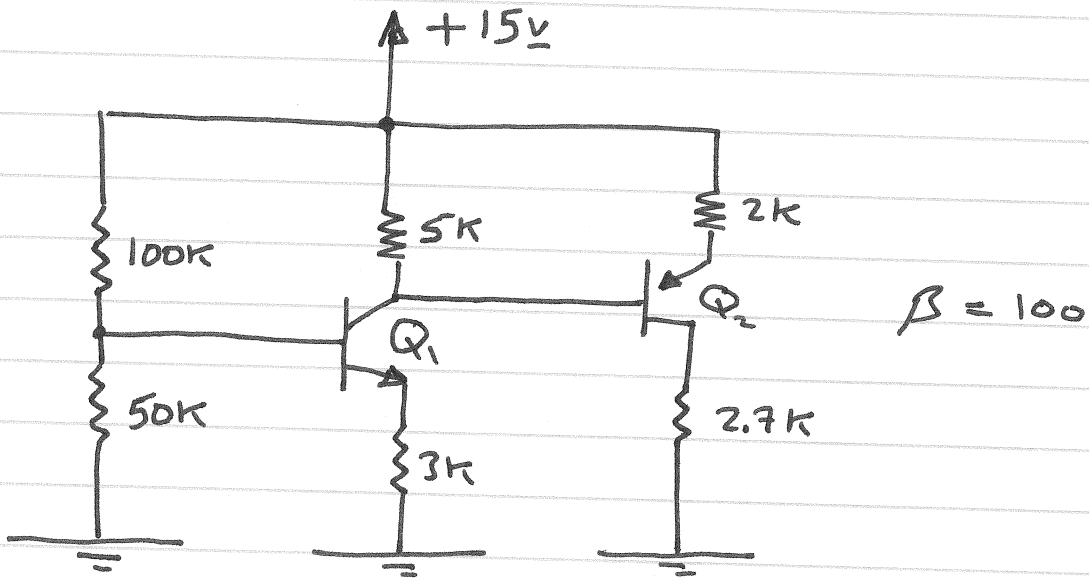

$$R_{TH} = 50k \parallel 100k = 33.3k$$

$$V_{TH} = \frac{50k}{50k+100k} \cdot 15 = 5V$$

$$KVL : I_{E1} = \frac{V_{TH} - 0.7}{\frac{R_{TH}}{\beta+1} + 3k} = 1.28mA$$

$$KVL : 2k I_{E2} + V_{EB} - 5k (I_{C1} - I_{B2}) = 0$$

$$\therefore I_{E2} = 2.78mA$$

Automatic Light Controller

In day time

R_{pe} is small, so that

$$V_{BE} < 0.7V$$

- ∴ Transistor is in cutoff
- ∴ Relay is deenergized
- ∴ Switch is open
- ∴ Lamp is OFF

At night

R_{pe} becomes large, so that

$$V_{BE} \approx 0.7V$$

- ∴ The Transistor is ON
- ∴ Relay is energized
- ∴ Switch is close
- ∴ Lamp is On

