
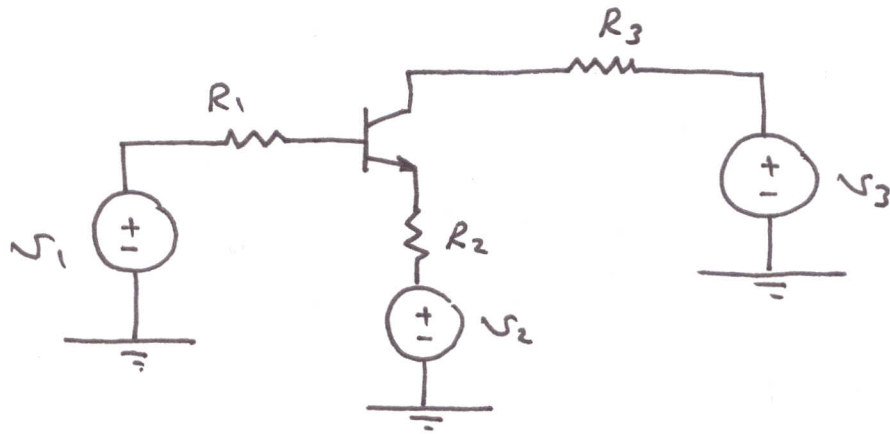


Impedance reflection :

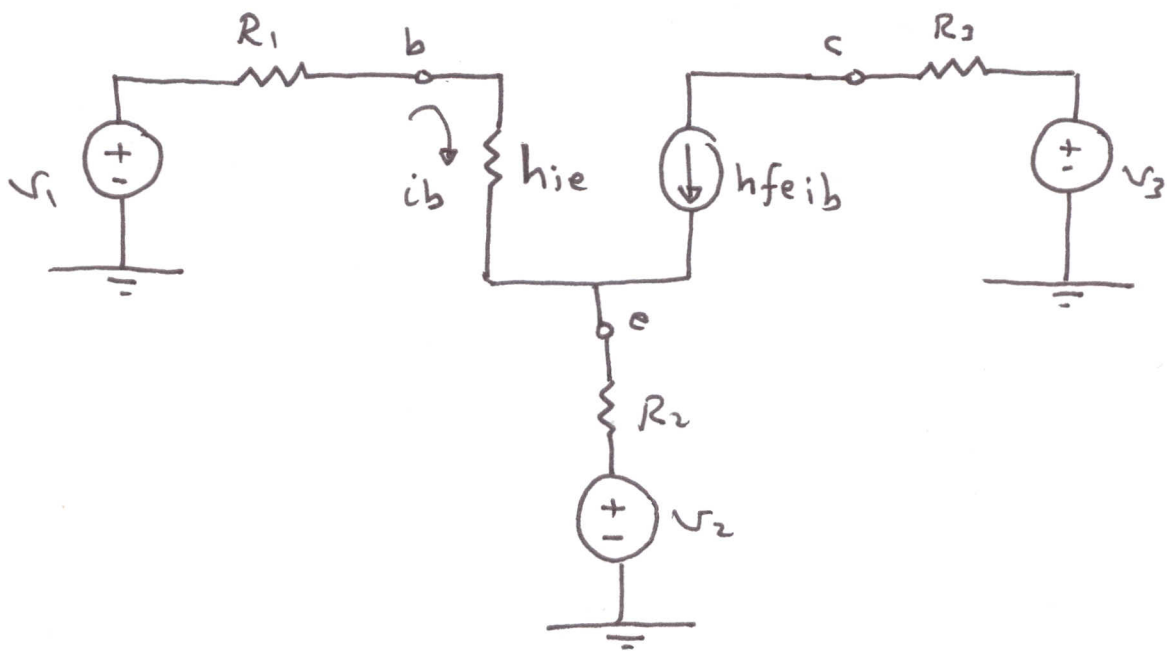


ac Small signal equivalent circuit :




base equivalent circuit
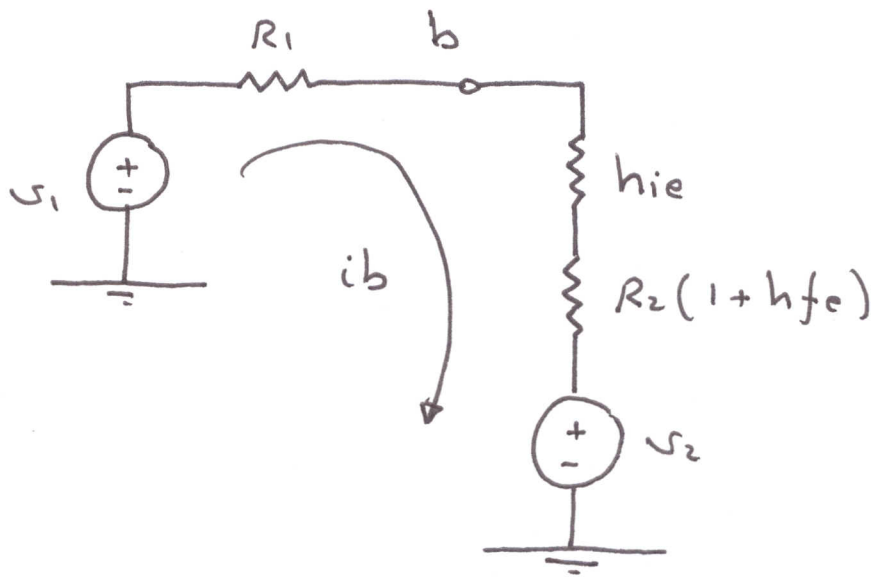
$$i_b = \frac{V_1 - V_2}{R_2(1+h_{fe}) + R_1 + h_{ie}}$$




Emitter equivalent circuit

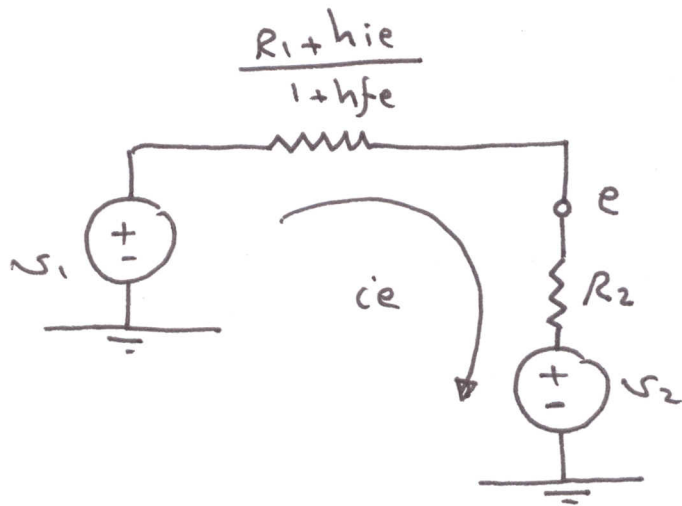
$$i_e = \frac{v_1 - v_2}{R_2 + \frac{R_1 + h_{ie}}{1 + h_{fe}}}$$




Collector equivalent circuit

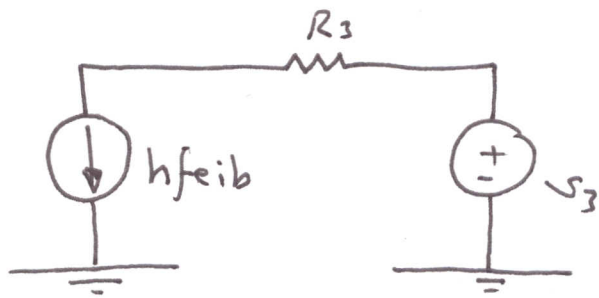

3) Common Collector amplifier

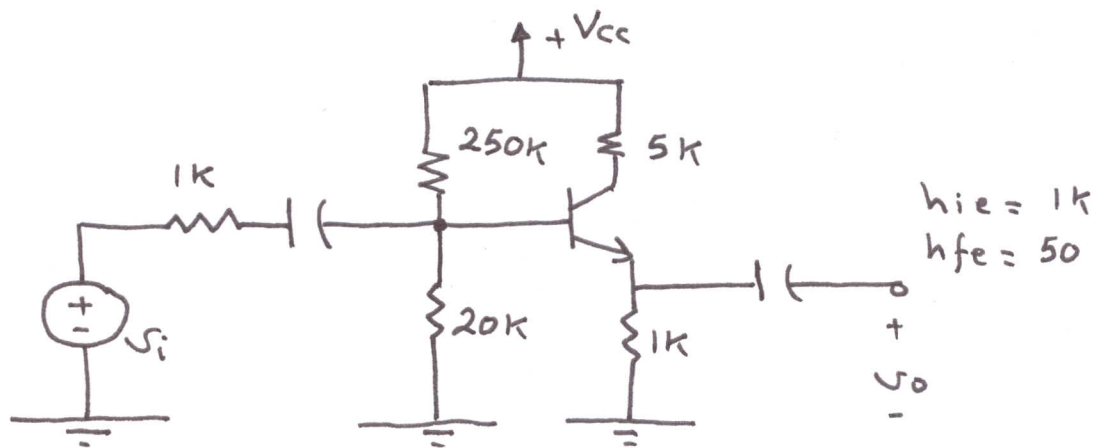

ac small signal equivalent circuit :

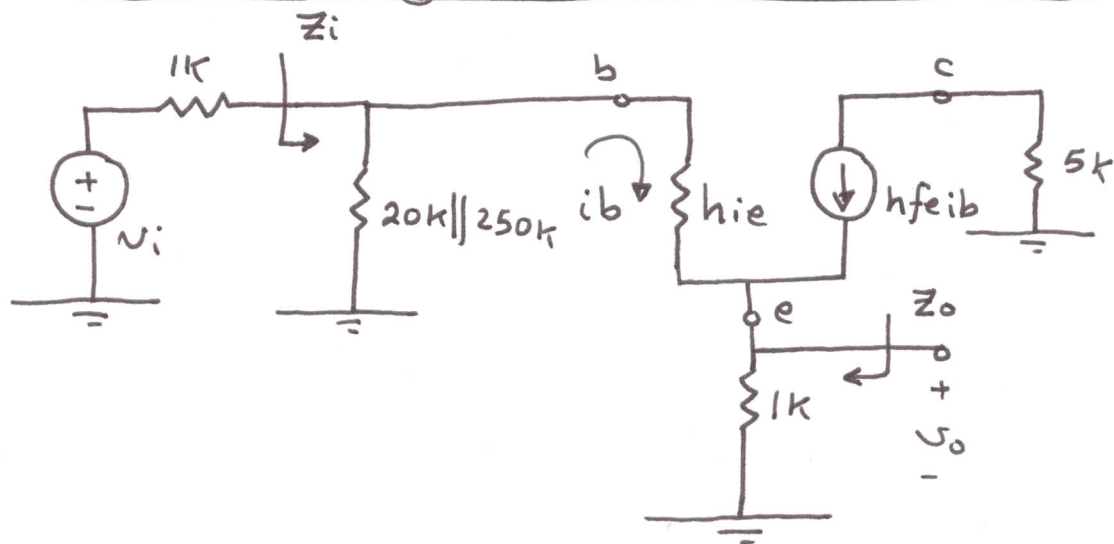


$$A_v = \frac{V_o}{V_i}$$

$$V_o = 1k i_e$$

$$i_e = (h_{fe} + 1) i_b$$

To find i_b \rightarrow base equivalent circuit

base equivalent circuit

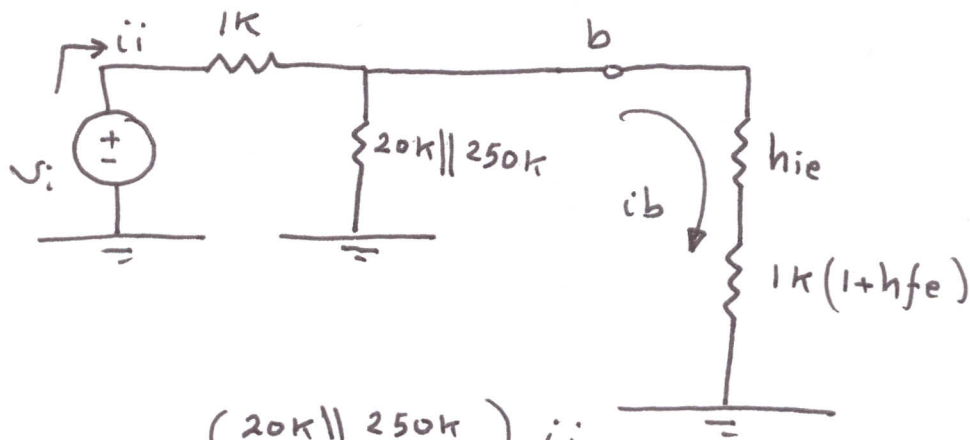

$$i_b = \frac{(20k \parallel 250k) i_i}{20k \parallel 250k + h_{ie} + 1k(1+h_{fe})}$$

$$i_i = \frac{v_i}{1k + Z_i}$$



$$i_i = \frac{v_i}{1k + [20k \parallel 250k] \parallel [h_{ie} + 1k(1+h_{fe})]}$$

$$Z_i = (20k \parallel 250k) \parallel (h_{ie} + 1k(1+h_{fe})) = 13.66k$$

$$A_v = \frac{v_o}{v_i} = 0.9149$$

$$A_i = \frac{i_o}{i_i} = 13.9$$

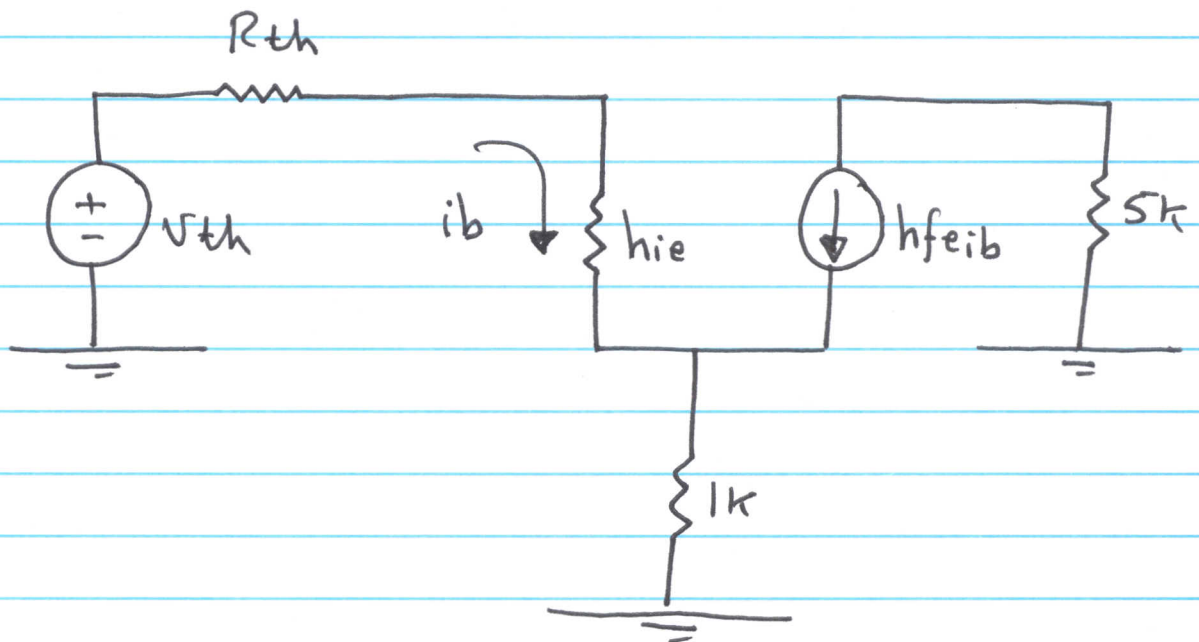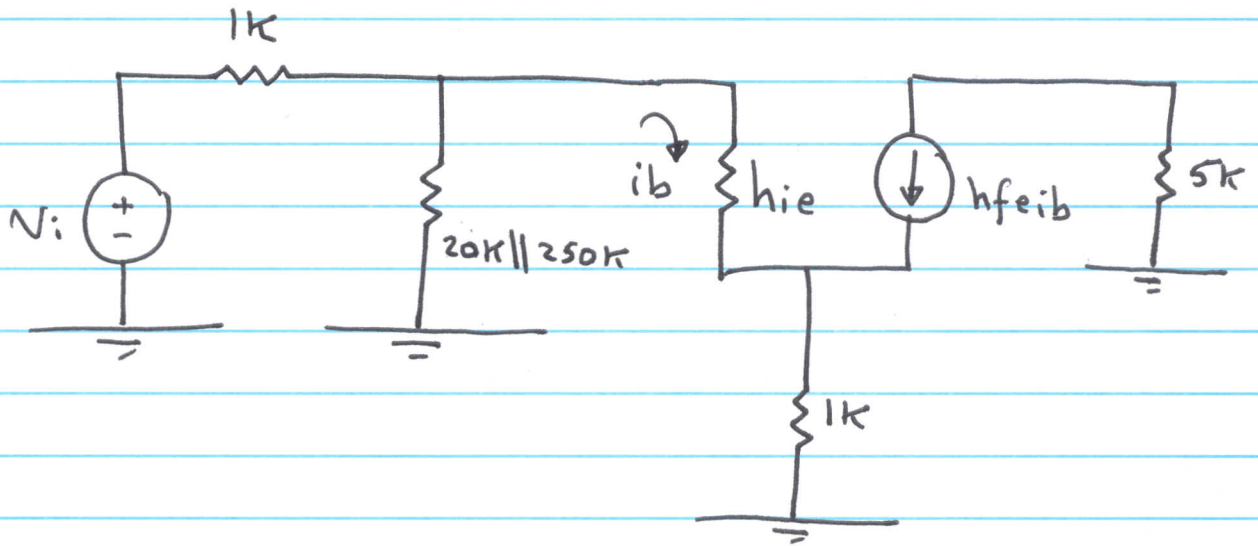
★ To find $Z_o \rightarrow$ emitter equivalent ckt




$$R_{th} = 1k \parallel 20k \parallel 250k$$

$$V_{th} = \frac{20k \parallel 250k}{20k \parallel 250k + 1k} V_i$$

emitter equivalent circuit

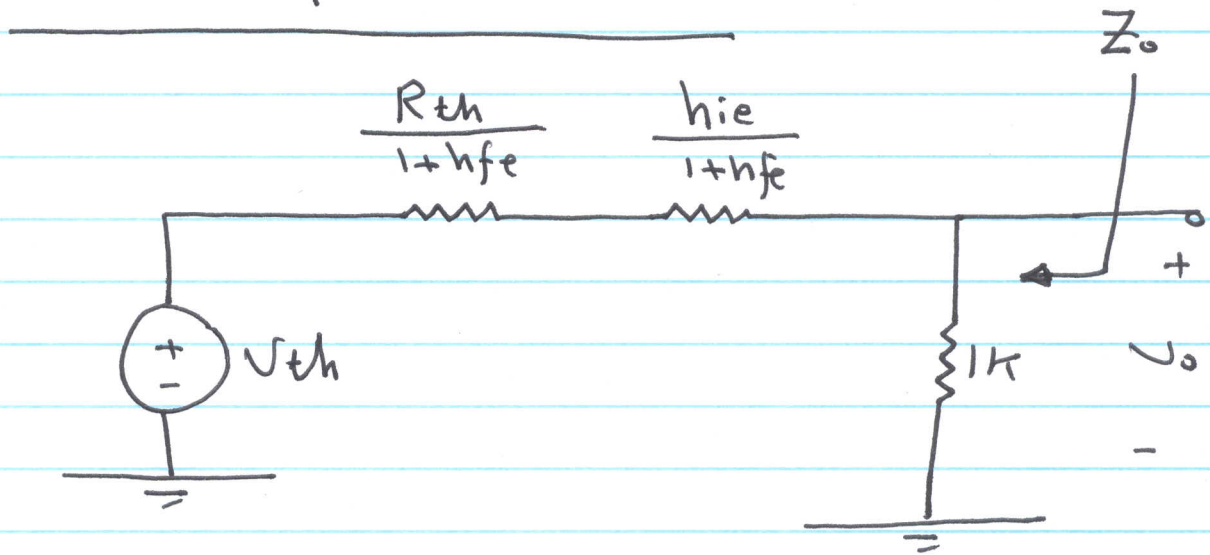

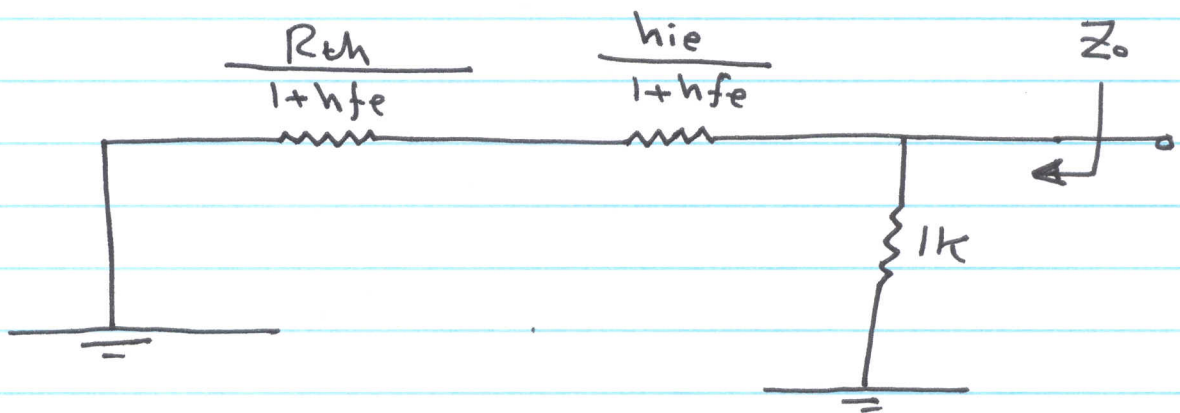To find Z_o , we set $N_i = 0$, $\therefore V_{th} = 0$



$$Z_o = 1k \parallel \left(\frac{R_{th} + h_{ie}}{1 + h_{fe}} \right)$$

$$Z_o = 1k \parallel \left(\frac{1k \parallel 20k \parallel 250k + h_{ie}}{1 + h_{fe}} \right) = 36.8 \Omega$$

\therefore For Common Collector amplifier


$$A_v < 1 ; A_i > 1$$

Z_i very Large ; Z_o very small


The Common Collector as a Buffer

Although the small signal voltage gain of the common collector (emitter follower) is less than 1, it can be used to improve the total voltage gain of a multistage amplifier.

Common emitter amplifier :

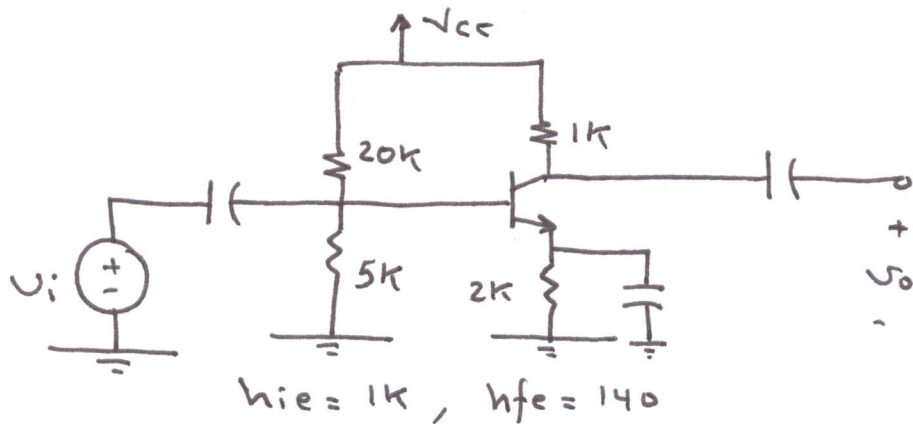


ac small signal equivalent circuit :

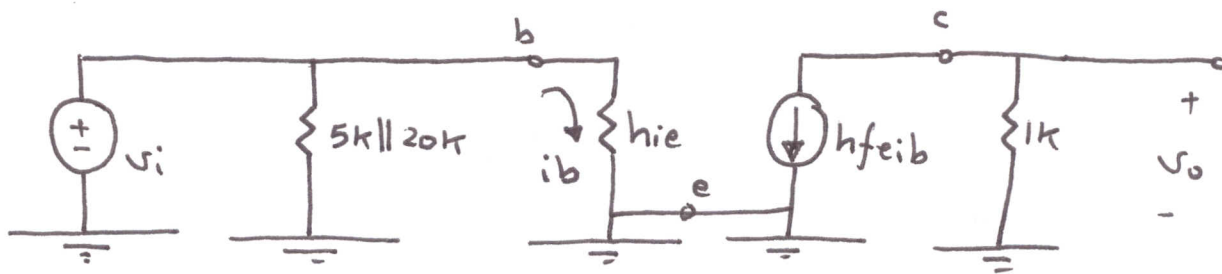


$$A_{V_o} = \frac{V_o}{V_i} = -140$$

Common emitter amplifier with R_L :

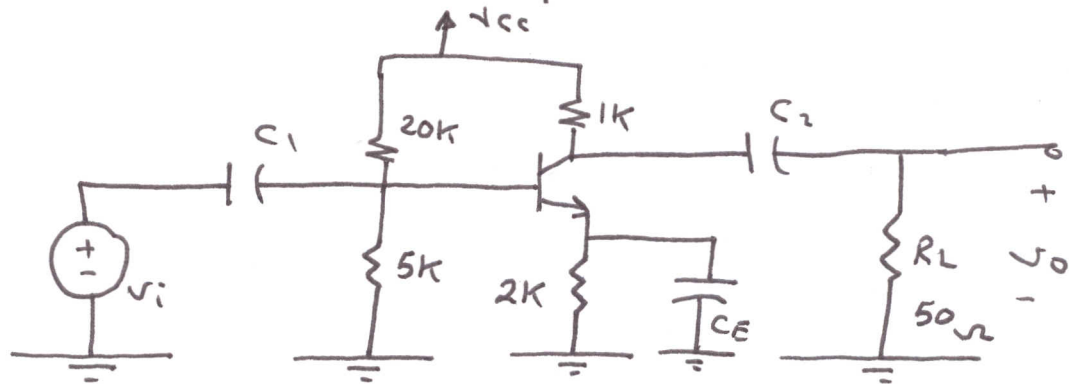


ac small signal equivalent circuit :

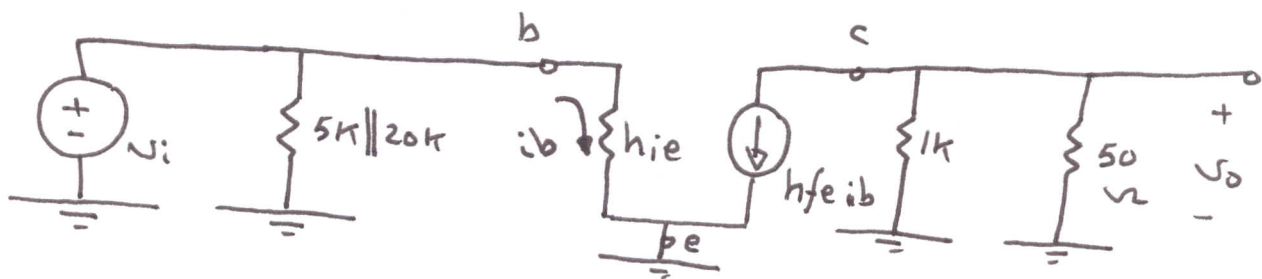


$$A_v = \frac{V_o}{V_i} = -6.67$$

Multistage Amplifier

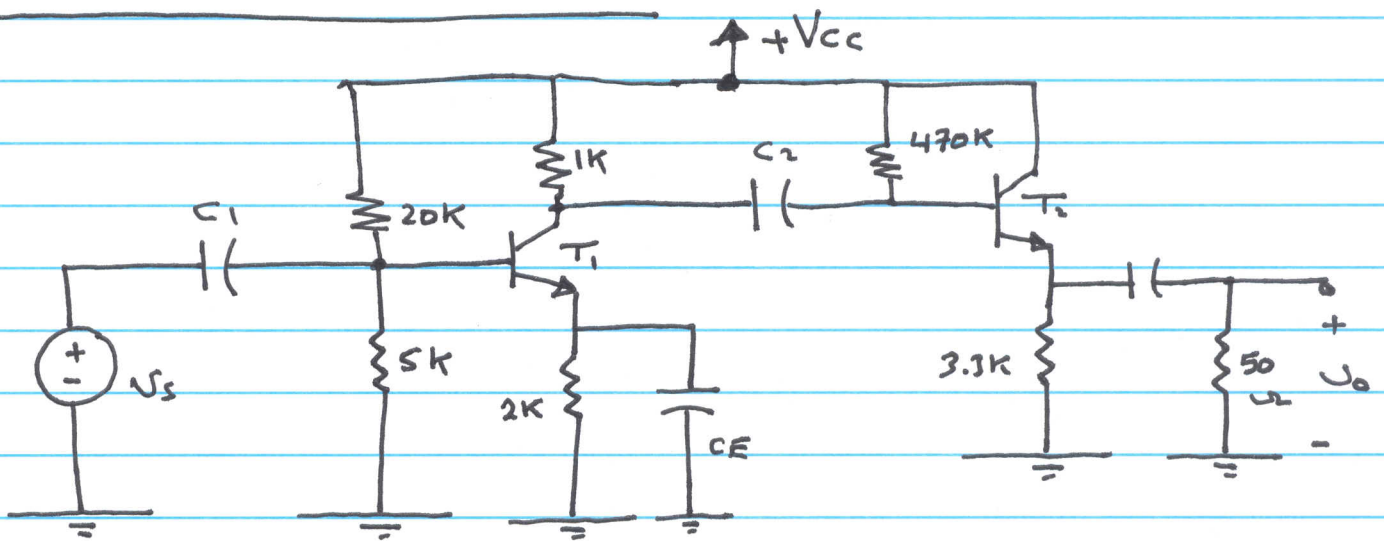



$$h_{fe1} = 140, h_{ie1} = 1k, h_{fe2} = 100, h_{ie2} = 2.24k$$

Ac small signal equivalent circuit :

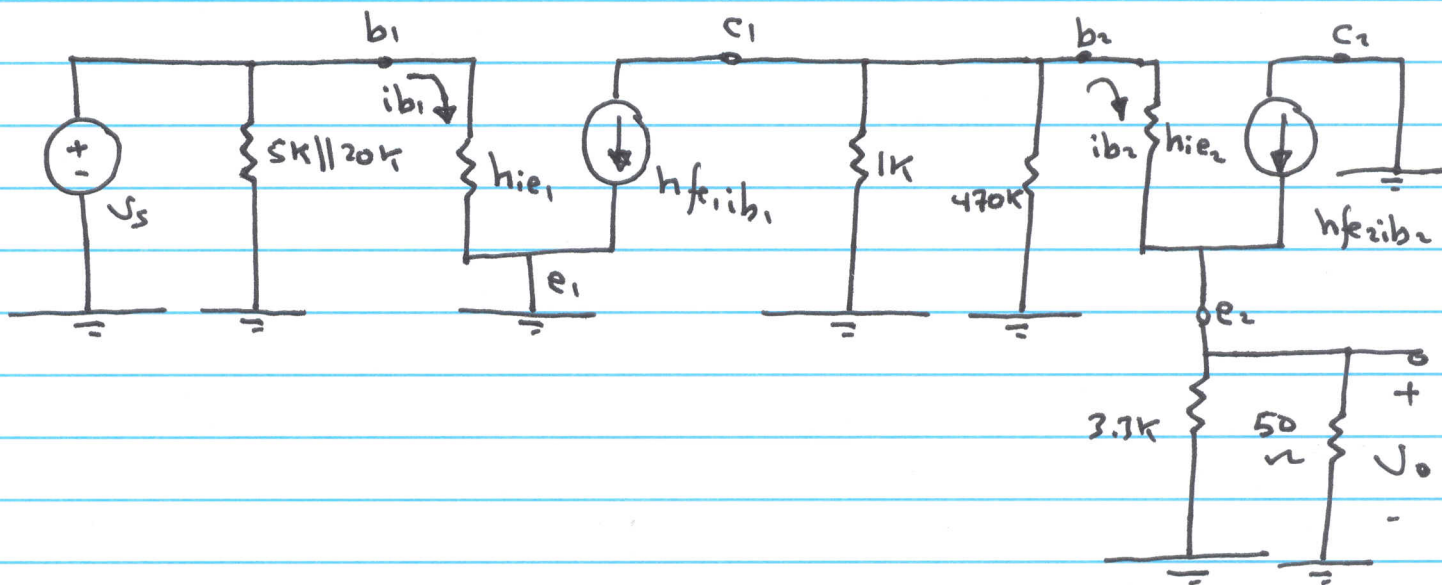

using Thevenin's theorem

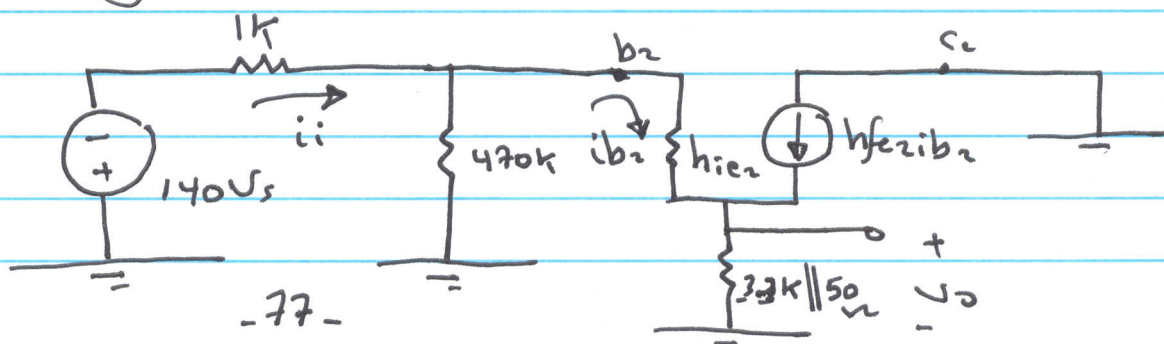

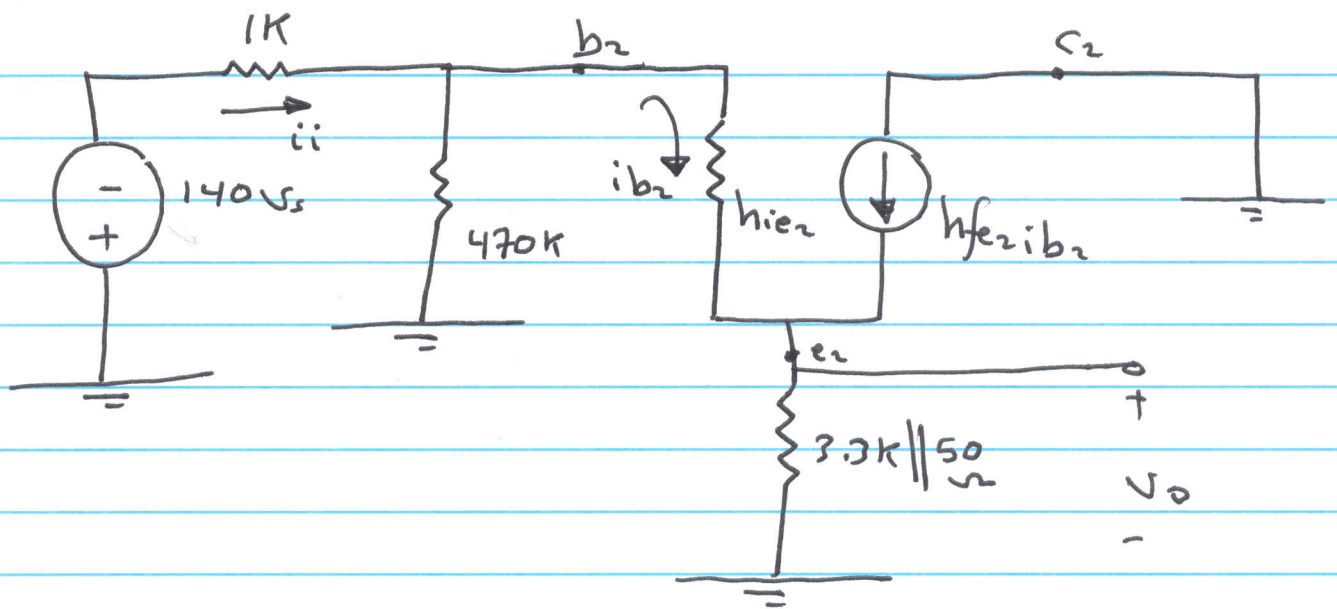

$$V_o = (3.3k \parallel 50 \Omega) (1 + h_{fe2}) i_{b2}$$

$$i_{b2} = i_i \frac{470k}{470k + h_{ie2} + (3.3k \parallel 50 \Omega) (1 + h_{fe2})}$$

$$i_i = \frac{-140 V_s}{1k + 470k \parallel [h_{ie2} + (3.3k \parallel 50 \Omega) (1 + h_{fe2})]}$$

$$\therefore A_V = -85$$