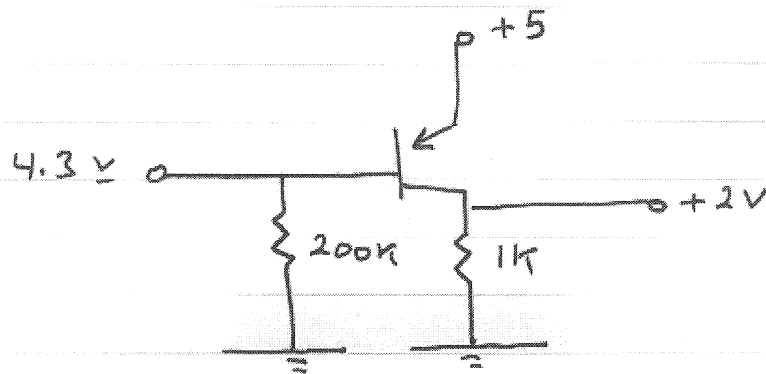


4.20

a)




$$I_B = \frac{V_B}{200k} = 0.0215 \text{ mA}$$

$$V_C = 1k I_C \quad \therefore I_C = \frac{2}{1k} = 2 \text{ mA}$$

$$\beta = \frac{I_C}{I_B} = 93$$

b)

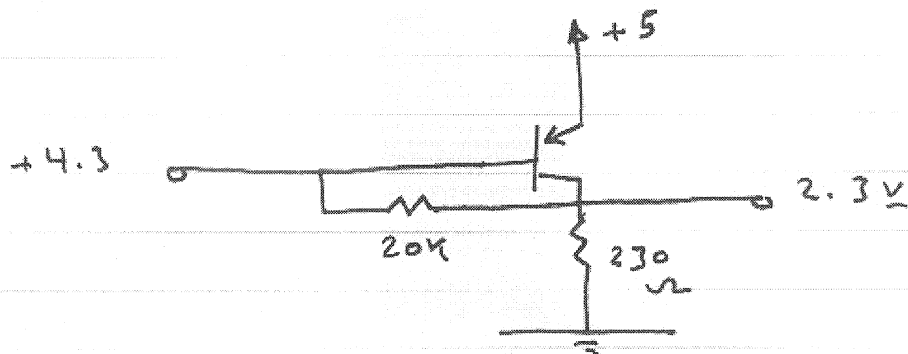

$$V_C = (230\Omega) (I_C + I_B)$$


$$\therefore I_C + I_B = I_E = \frac{2.3}{230} = 10 \text{ mA}$$

$$I_B = \frac{V_B - V_E}{20k} = \frac{4.3 - 2.3}{20k} = 0.1 \text{ mA}$$

$$I_C = I_E - I_B = 9.9 \text{ mA}$$

$$\beta = \frac{I_C}{I_B} = 99$$

c)

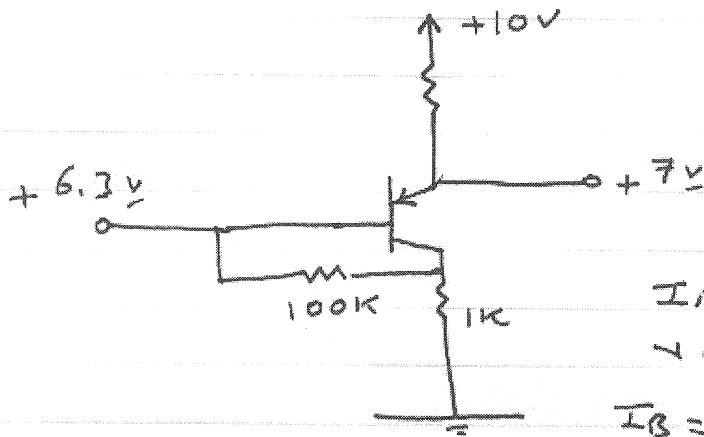

$$I_E = \frac{10 - 7}{1k} = 3mA$$


$$V_C = 1k I_E = 3V$$

$$I_B = \frac{6.3 - 3}{100k} = 33 \mu A$$

$$I_C = 2.967mA \quad \therefore \beta = \frac{I_C}{I_B} = 89.9$$

4.26

a)

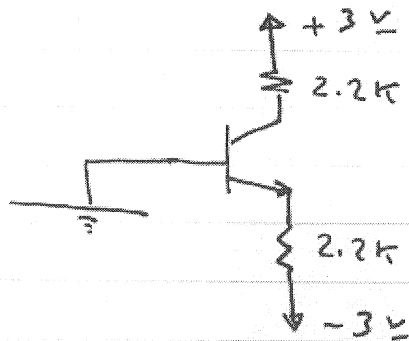

$$\beta = 30$$


$$V_B = 0, \quad V_E = -0.7V, \quad I_E = \frac{-0.7 + 3}{2.2k} = 1.05mA$$

$$I_C = \alpha I_E = 1.02mA$$

$$I_B = \frac{I_C}{\beta} = 0.034mA$$

$$V_C = 3 - (2.2k) I_C = 0.756V$$

b)

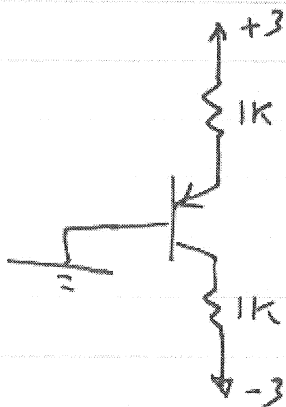

$$V_B = 0, \quad V_E = 0.7V$$


$$I_E = \frac{3 - 0.7}{1k} = 2.3mA$$

$$I_C = \alpha I_E = 2.23mA$$

$$I_B = \frac{I_C}{\beta} = 0.743mA$$

$$V_C = 1k I_C - 3 = -0.77V$$

c)

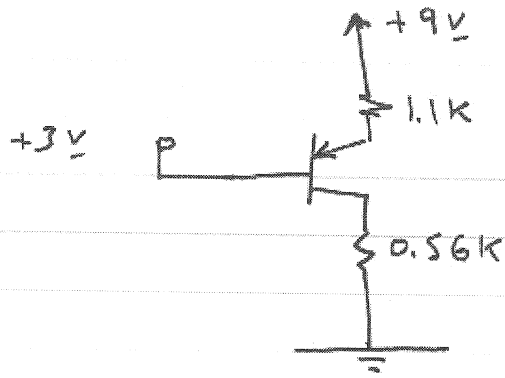


$$V_{EB} = V_E - V_B \quad \therefore V_E = 3.7 \text{ V}$$

$$I_E = \frac{9 - 3.7}{1.1 \text{ k}} = 4.82 \text{ mA}, \quad I_C = \alpha I_E = 4.66 \text{ mA}$$

$$V_C = (0.56 \text{ k}) I_C = 2.62 \text{ V}; \quad I_B = \frac{I_C}{\beta} = 0.155 \text{ mA}$$

d)

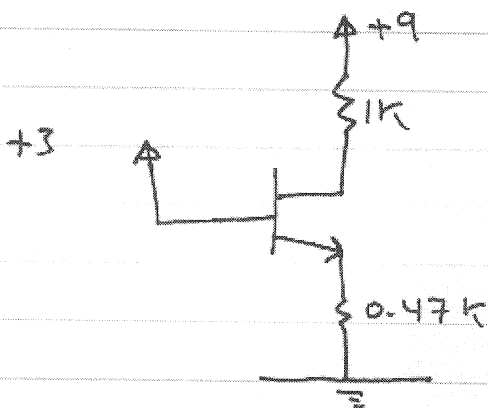

$$V_E = 3 - 0.7 = 2.3 \text{ V}$$

$$I_E = \frac{2.3}{0.47} = 4.89 \text{ mA}$$


$$I_C = \alpha I_E = 4.73 \text{ mA}$$

$$V_C = 9 - 1 \text{ k} I_C = 4.22 \text{ V}$$

$$I_B = \frac{I_C}{\beta} = 0.158 \text{ mA}$$

4.46

a)

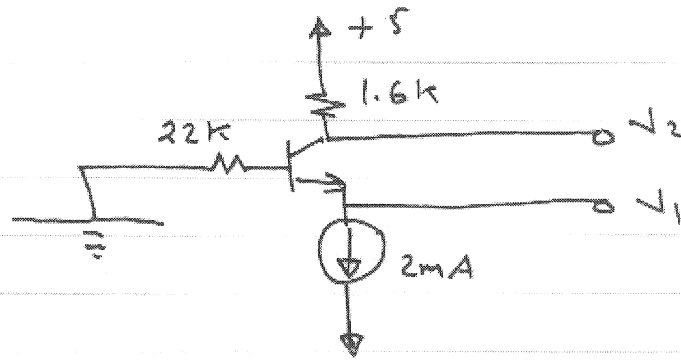

$\beta = \infty$


$\therefore I_B \rightarrow 0$

$I_E = 2\text{mA} \quad \therefore I_C = \alpha I_E \approx I_E = 2\text{mA}$

$V_2 = 5 - (1.6\text{k}) I_C = 1.8\text{V}$

$V_1 = V_{EB} = -0.7 \quad (\text{since } I_B \rightarrow 0) \quad V_B = 0$

b)

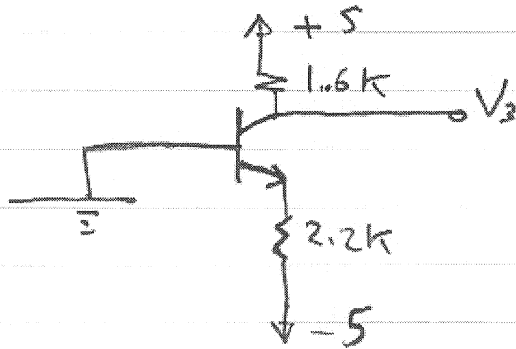


$I_E = \frac{5 - 0.7}{2.2\text{k}} = 1.954\text{mA}$

$V_3 = 5 - (1.6\text{k}) I_C$

$\therefore V_3 = 1.87\text{V}$

c) The same answers as part (b)

d)

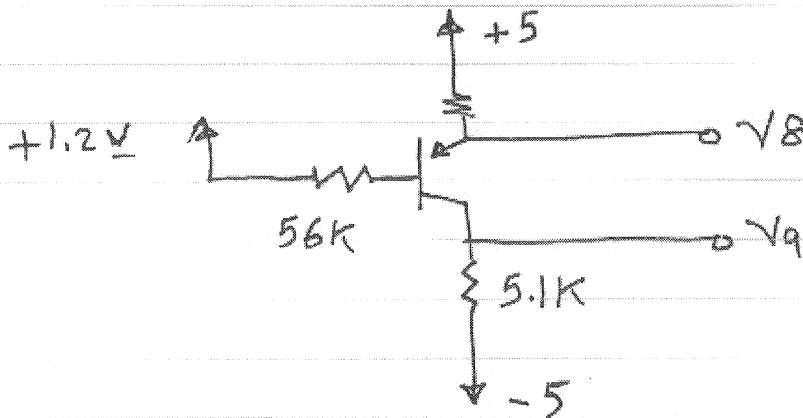


$$V_B = 56k I_B + 1.2V \approx 1.2V$$

$$I_E = \frac{5 - 0.7 - 1.2}{3.3k} = 0.939 \text{ mA}$$

$$V_8 = 5 - 3.3k I_E = 1.9V$$

$$V_9 = (5.1k) I_C - 5 = -0.209V$$

e)

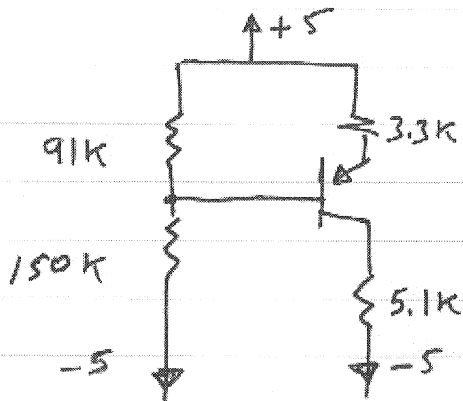

$$R_{TH} = 90k \parallel 150k$$

$$R_{TH} = 56.64k$$

$$V_{TH} = V_B = \frac{150k}{150k + 90k} \cdot 10 = 5$$


$$\therefore V_{TH} = 1.224V$$

$$I_E = \frac{5 - 0.7 - 1.224}{3.3k} = 0.9321 \text{ mA}$$

$$V_{11} = 5 - (3.3k) I_E = 1.924V$$

$$V_{12} = (5.1k) I_C - 5 = -0.2463V$$

4-50

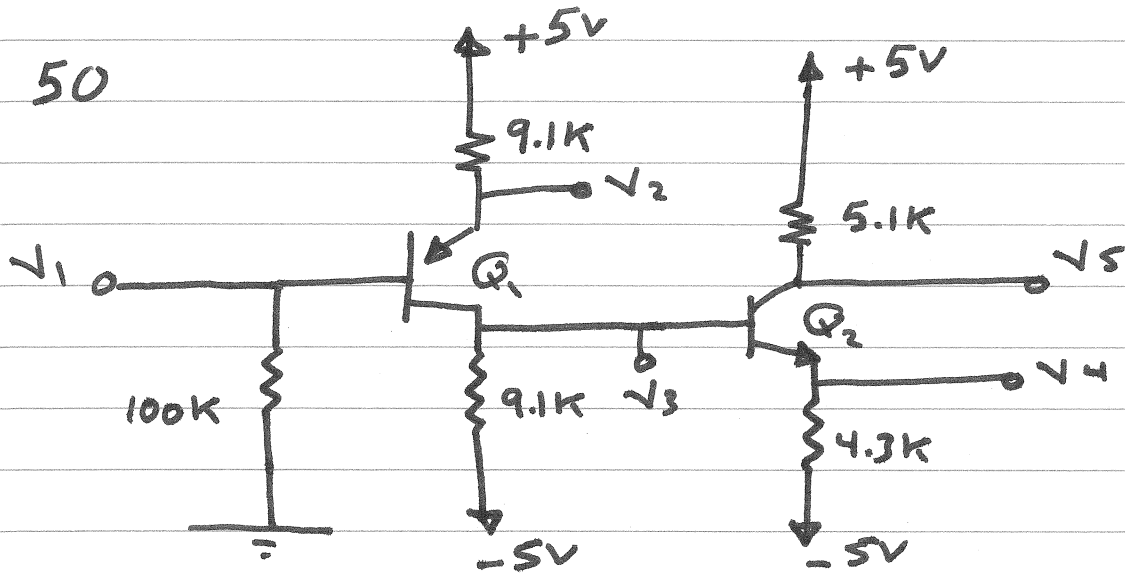

a) $\beta = \infty$; $I_B \approx 0$ and $I_C \approx I_E$

$$V_1 = 100k I_B = 0$$

$$5 = 9.1k I_{E1} + V_{BE1} + 100k I_{B1}$$

$$\therefore I_{E1} = \frac{5 - 0.7}{9.1k} = 0.4725 \text{ mA}$$

$$V_2 = 5 - 9.1k I_{E1} = 0.7 \text{ V}$$

$$V_3 = 9.1k (I_{C1} - I_{B2}) - 5 = -0.7 \text{ V}$$

$$-9.1k (I_{C1} - I_{B2}) + V_{BE2} + 4.3k I_{E2} = 0$$

$$\therefore I_{E2} = 0.837 \text{ mA}$$

$$V_4 = 4.3k I_{E2} - 5 = -1.4 \text{ V}$$

$$V_5 = 5 - 5.1k I_{C2} = 0.73 \text{ V}$$

$$b) \quad \beta = 100$$

$$5 = 9.1k I_{E1} + V_{EB1} + 100k I_B$$

$$\therefore I_{E1} = \frac{5 - 0.7}{9.1k + \frac{100k}{101}} = 0.426 \text{ mA}$$

$$I_{B1} = \frac{I_{E1}}{101} = 0.00422 \text{ mA}$$

$$I_{C1} = 0.422 \text{ mA}$$

$$V_1 = 100k I_{B1} = 0.422 \text{ V}$$

$$V_2 = 5 - 9.1k I_{E1} = 1.1234 \text{ V}$$


$$-9.1k (I_{C1} - I_{B2}) + 0.7 + 4.3k I_{E2} = 0$$

$$\therefore I_{E2} = 0.715 \text{ mA}$$

$$V_3 = 9.1k (I_{C1} - I_{B2}) - 5 = -1.22 \text{ V}$$

$$V_4 = 4.3k I_{E2} - 5 = -1.9255 \text{ V}$$

4.51

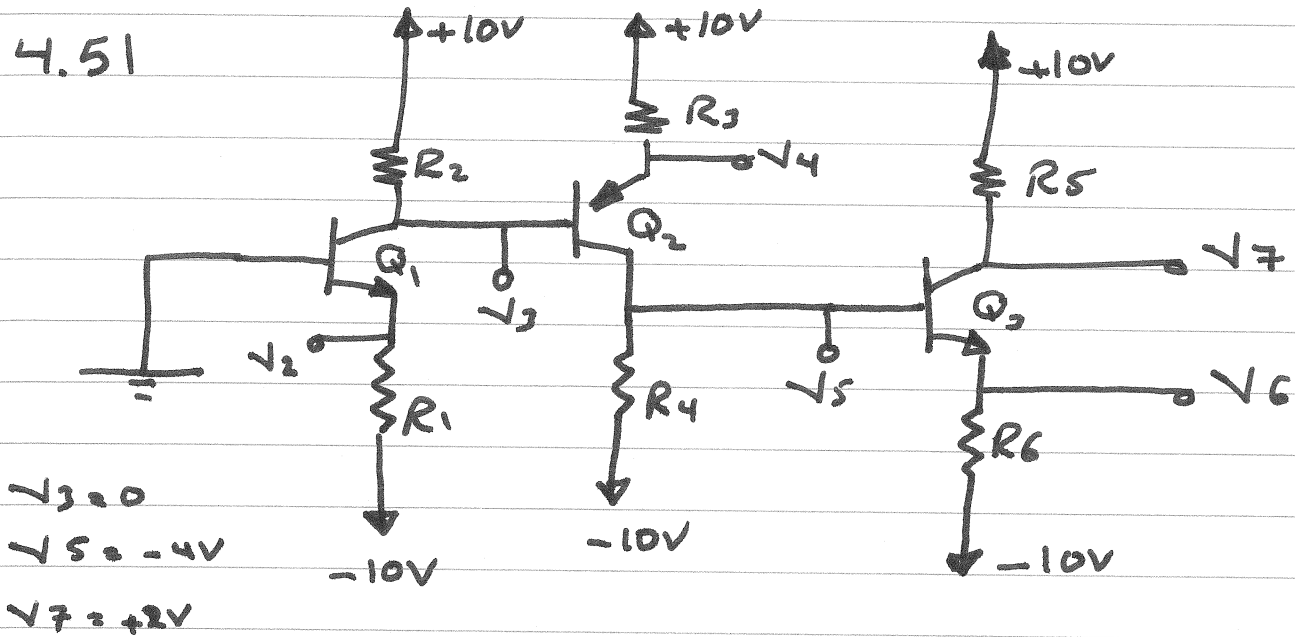

$$I_{E1} = I_{E2} = 2mA ; I_{E3} = 4mA$$

a) $\beta = \infty \rightarrow I_B \approx 0 ; I_C \approx I_E$

$$V_2 = -V_{BE1} = -0.7$$

$$R_1 = \frac{-0.7 + 10}{I_{E1}} = \frac{10 - 0.7}{2mA} = 4.65K \rightarrow 4.7K$$

$$R_2 = \frac{10 - V_3}{I_{C1}} = \frac{10}{2mA} = 5K \rightarrow 5.1K$$

$$V_4 = V_{EB2} + V_3 = 0.7 + 0 = 0.7V$$

$$R_3 = \frac{10 - V_4}{I_{E2}} = \frac{10 - 0.7}{2mA} = 4.65K \rightarrow 4.7K$$

$$R_4 = \frac{V_5 + 10}{I_{E2}} = \frac{-4 + 10}{2mA} = 3K$$

$$V_6 = V_{EB3} + V_5 = -0.7 - 4 = -4.7V$$

$$R_6 = \frac{V_6 + 10}{I_{E3}} = \frac{-4.7 + 10}{4mA} = 1.325K \rightarrow 1.3K$$

$$R_5 = \frac{10 - V_7}{I_{C3}} = \frac{10 - 2}{4mA} = 2K$$

$$b) \quad \beta = 100$$

$$10 = V_{BE1} + R_1 I_{E1}$$

$$\therefore I_{E1} = \frac{10 - 0.7}{R_1} = \frac{10 - 0.7}{4.7k} = 1.98 \text{ mA}$$

$$I_{C1} = \alpha I_{E1} = \frac{100}{101} I_{E1} = 1.96 \text{ mA}$$

$$R_3 I_{E2} + V_{BE2} - R_2 (I_{C1} - I_{B2}) = 0$$

$$\therefore I_{E2} = \frac{R_2 I_{C1} - V_{BE2}}{R_3 + \frac{R_2}{\beta + 1}} = 1.96 \text{ mA}$$

$$I_{C2} = \alpha I_{E2} = 1.94 \text{ mA}$$

$$-R_4 (I_{C2} - I_{B2}) + V_{BE3} + R_6 I_{E3} = 0$$

$$\therefore I_{E3} = 3.85 \text{ mA}$$

$$\therefore I_{C3} = 3.81 \text{ mA}$$

$$V_2 = R_1 I_{E1} - 10 = -0.694 \text{ V}$$

$$V_3 = 10 - R_3 I_{E2} - 0.7 = 0.058 \text{ V}$$

$$V_4 = 10 - R_3 I_{E3} = 0.788 \text{ V}$$

$$V_6 = R_6 I_{E3} - 10 = -5 \text{ V}$$

$$V_5 = V_{BE3} + V_6 = -4.3 \text{ V}$$

$$V_7 = 10 - R_5 I_{C3} = 2.38 \text{ V}$$