

## ENEE233 CH4 Homework Problems

4.20 Measurements on the circuits of Fig. P4.20 produce labeled voltages as indicated. Find the value of  $\beta$  for each transistor.



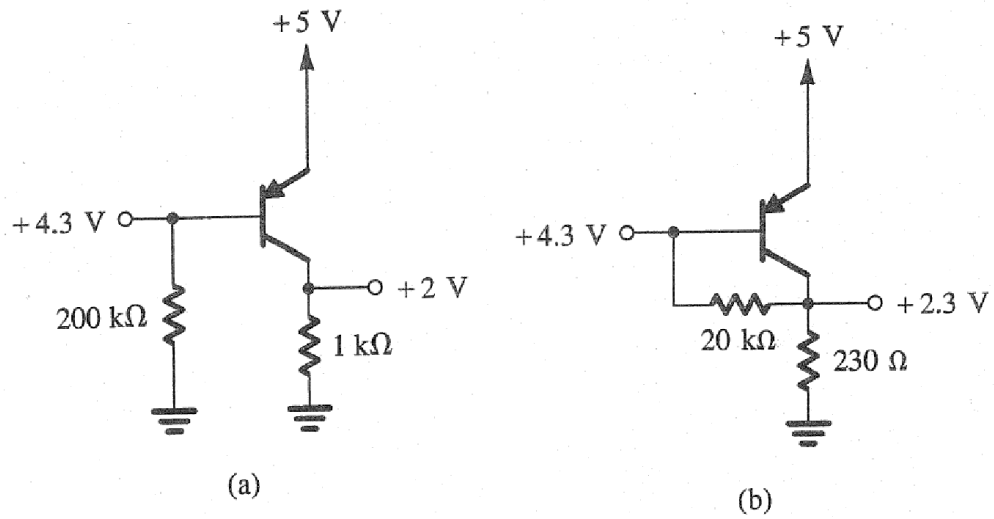
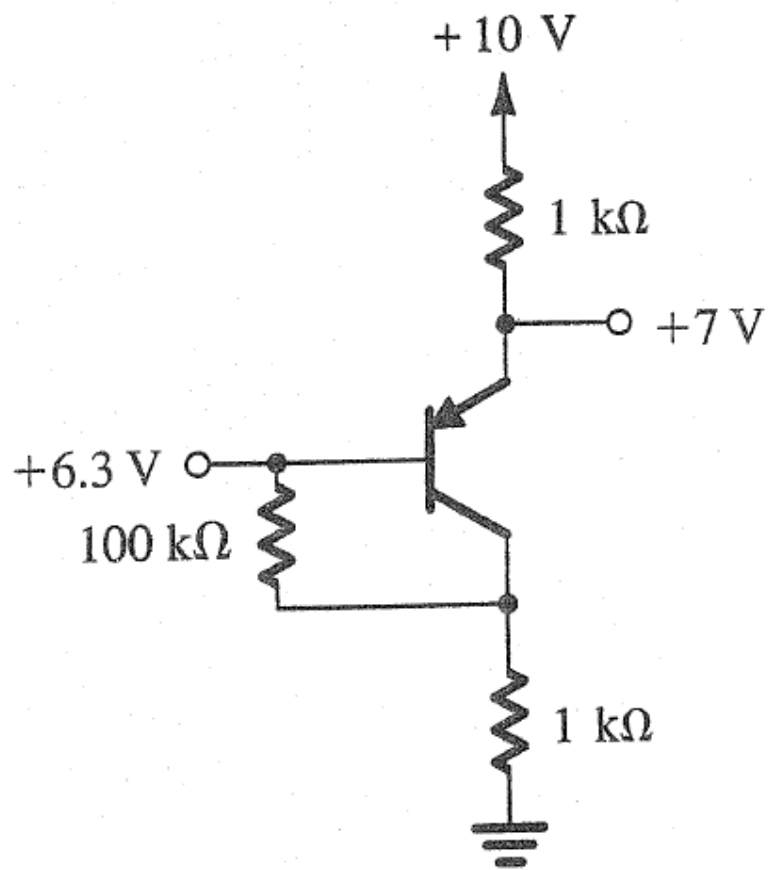



Figure P4.20

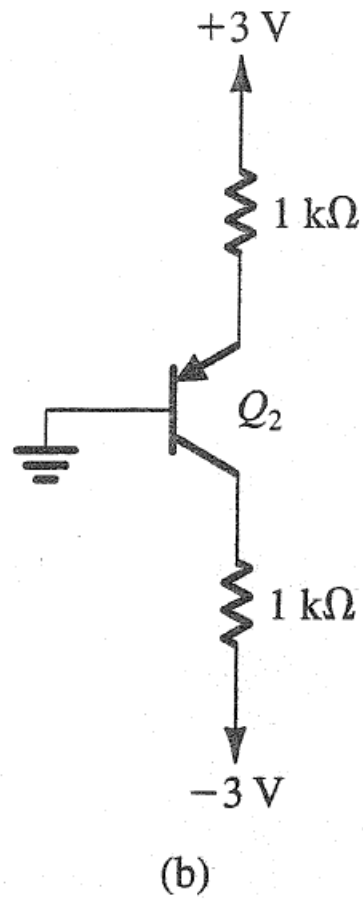


(c)

**4.26** For each of the circuits shown in Fig. P4.26, find the emitter, base, and collector voltages and currents. Use  $\beta = 30$ , but assume  $|V_{BE}| = 0.7 \text{ V}$  independent of current level.

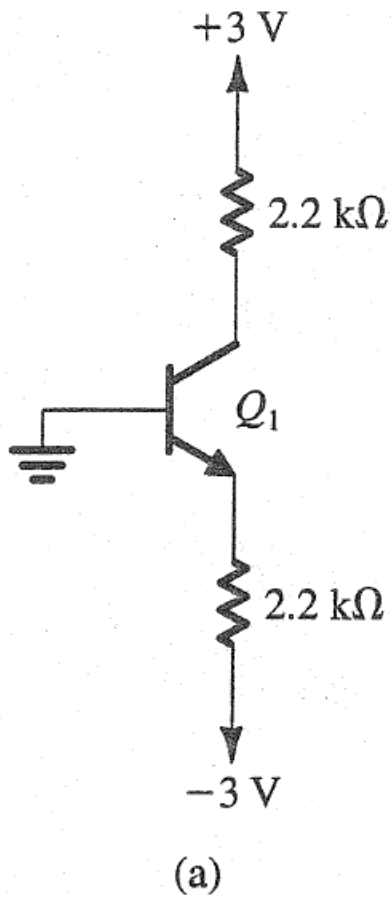

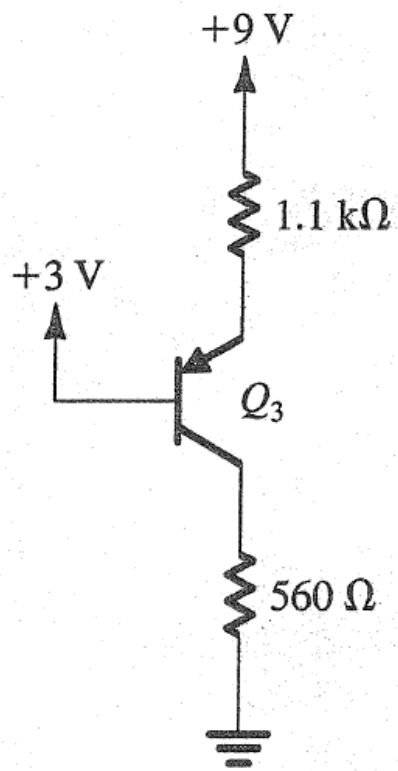


(c)

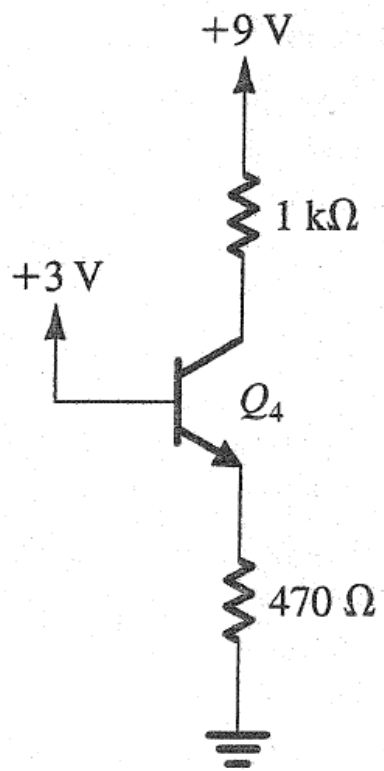


(d)

Figure P4.26

4.46 For the circuits in Fig. P4.46, find values for the labeled node voltages and branch currents. Assume  $\beta$  to be very high and  $|V_{BE}| = 0.7\text{V}$ .

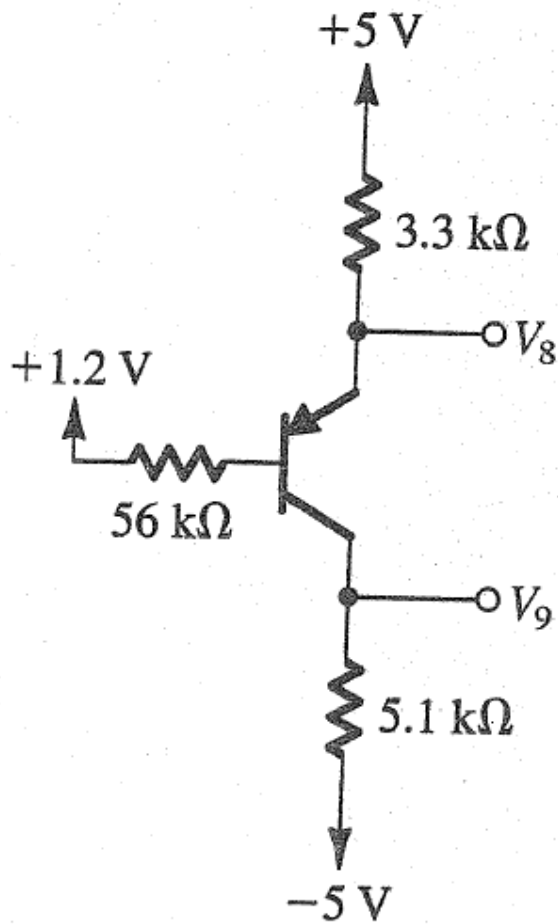

(d)

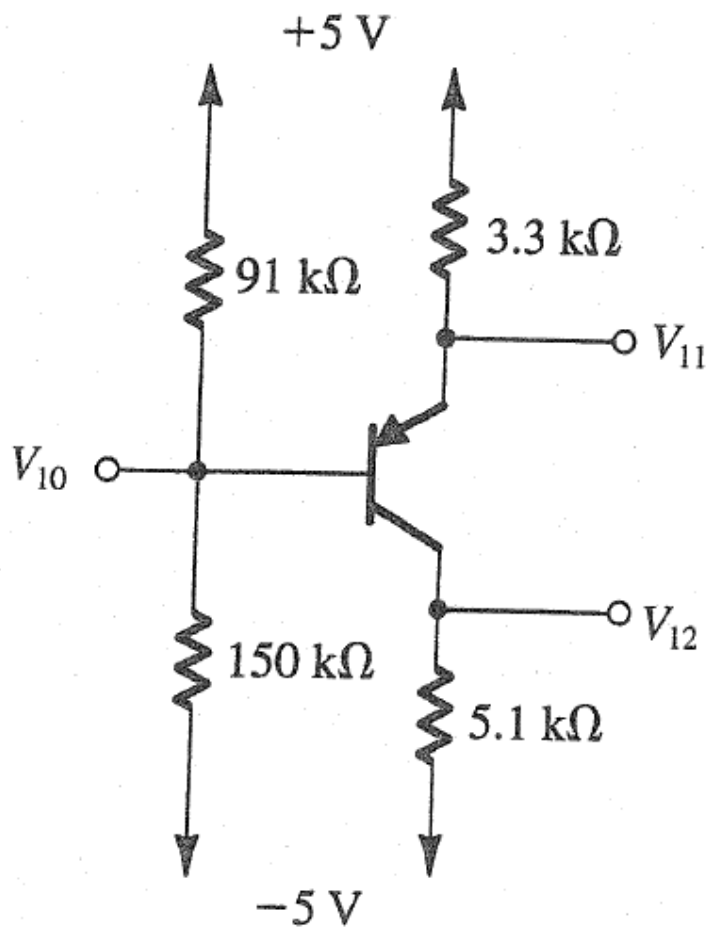

(e)

Figure P4.46

\*4.50 For the circuit shown in Fig. P4.50, find the labeled node voltages for:

- (a)  $\beta = \infty$
- (b)  $\beta = 100$


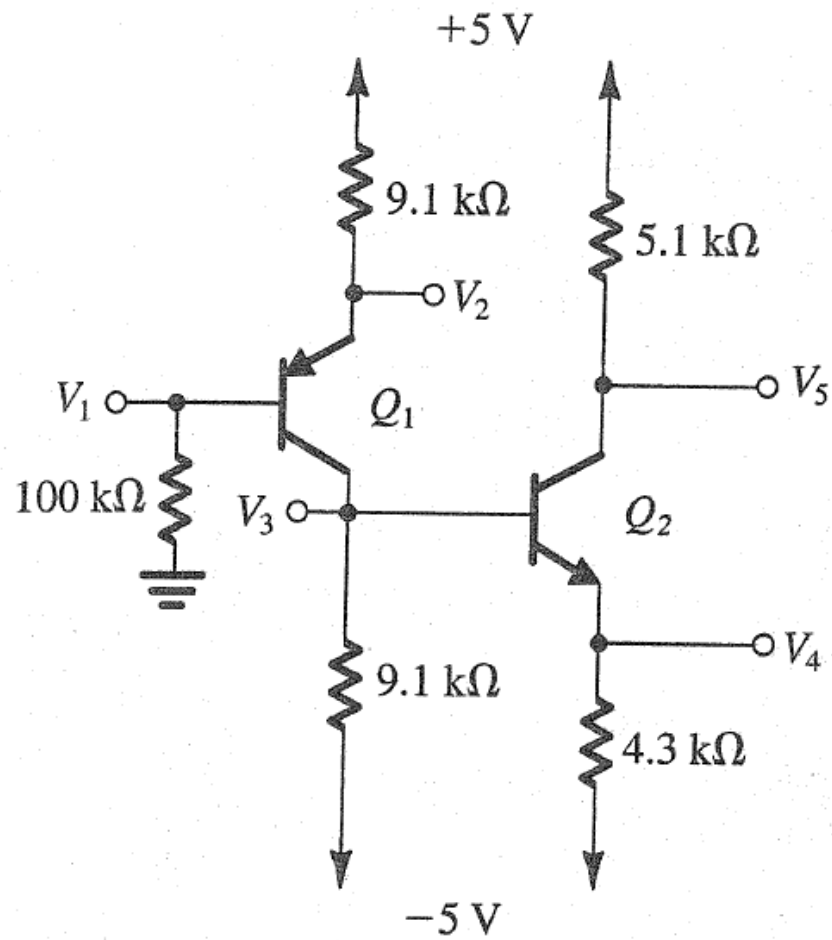


Figure P4.50

**D \*4.51** Using  $\beta = \infty$ , design the circuit shown in Fig. P4.51 so that the bias currents in  $Q_1$ ,  $Q_2$ , and  $Q_3$  are 2 mA, 2 mA, and 4 mA, respectively, and  $V_3 = 0$ ,  $V_5 = -4$  V, and  $V_7 = 2$  V. For each resistor, select the nearest standard value utilizing the table of standard values for 5% resistors in Appendix G. Now, for  $\beta = 100$ , find the values of  $V_3$ ,  $V_4$ ,  $V_5$ ,  $V_6$ , and  $V_7$ .

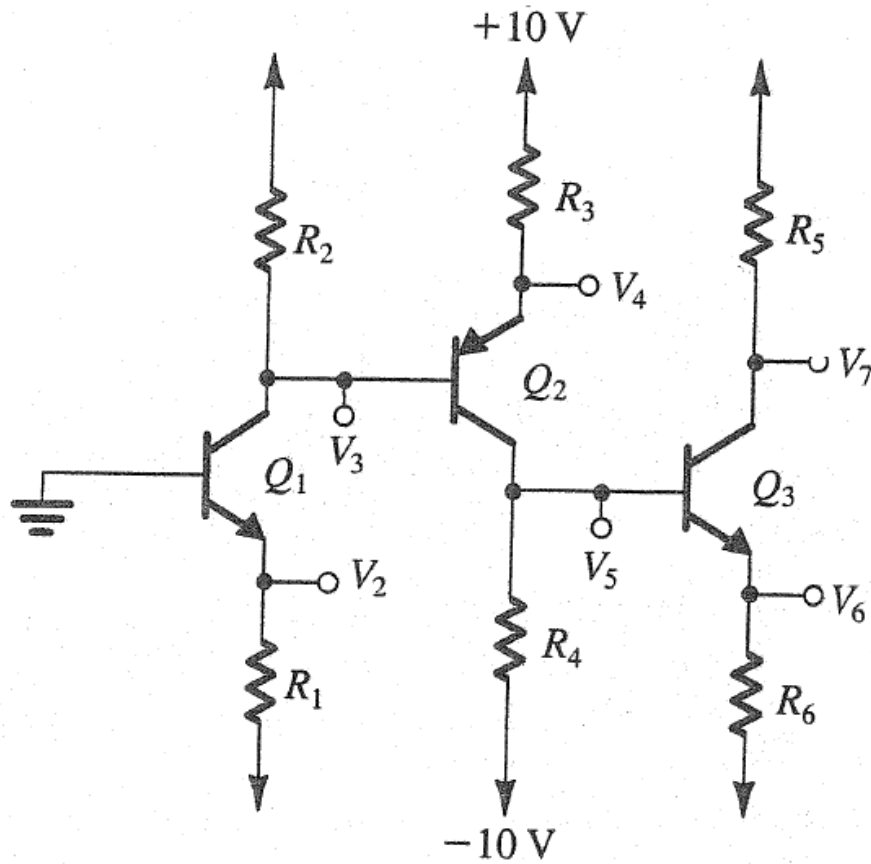

**Figure P4.51**