
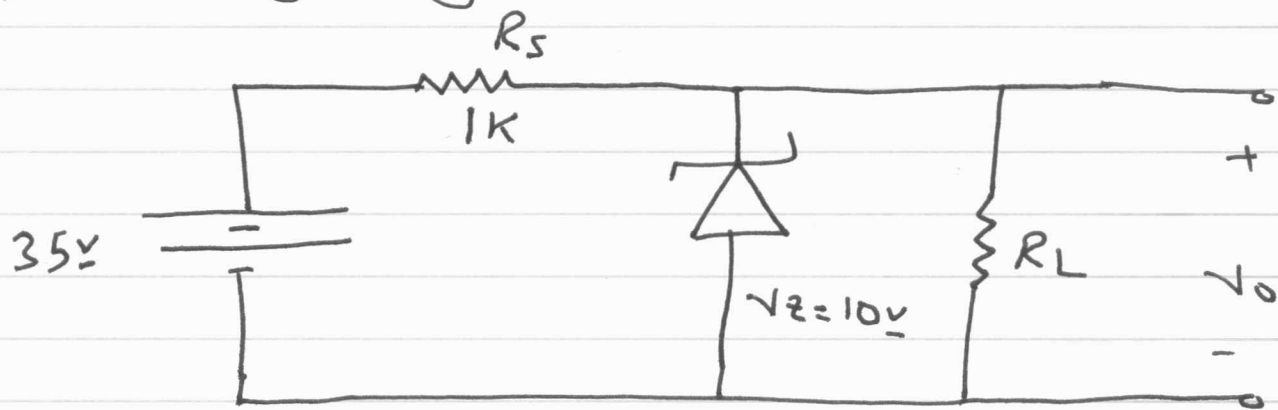


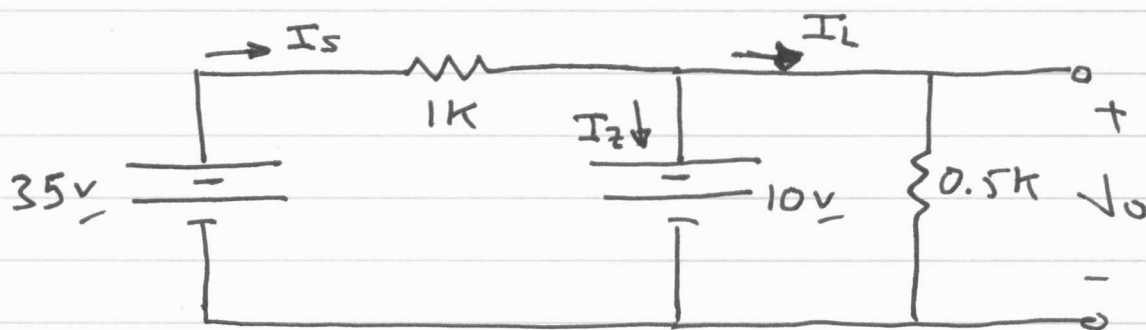2) Voltage regulation with load variation



a) Let $R_L = 0.5K$

The Zener diode is in the breakdown region. Prove !!



$$\therefore V_o = V_z = 10V$$


$$I_s = \frac{35 - 10}{1K} = 25mA$$

$$I_L = \frac{V_o}{R_L} = \frac{10V}{0.5K} = 20mA$$

$$\therefore I_z = I_s - I_L = 5mA$$

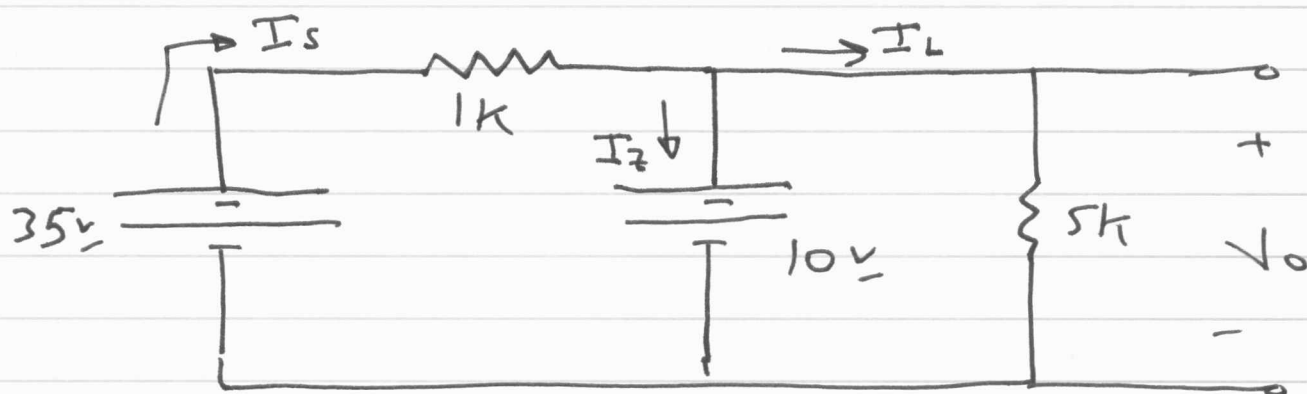b) let $R_L = 5k$

\therefore the Zener diode is in the break down region. Prove !!



$$V_o = V_z = 10V$$

$$I_s = \frac{35 - 10}{1k} = 25mA$$


$$I_L = \frac{V_o}{R_L} = \frac{10V}{5k} = 2mA$$

$$\therefore I_z = I_s - I_L = 23mA$$

In the four cases we must verify that

$$I_z(\max) > I_z > I_z(\min)$$

Design of R_s

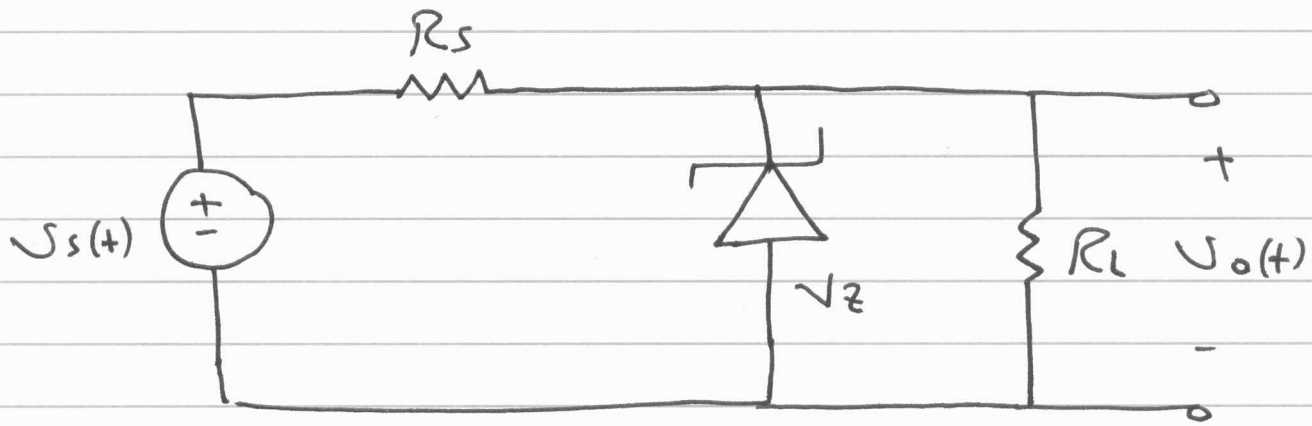

given : $V_s(\min)$ and $V_s(\max)$

$R_L(\min)$ and $R_L(\max)$

and $(V_z, I_z(\min), I_z(\max))$

$$I_z = I_s - I_L$$

$$* I_z = \frac{V_s(t) - V_z}{R_s} - I_L > I_z(\min)$$

The worst condition

$$\frac{V_s(\min) - V_z}{R_s} - I_L(\max) > I_z(\min)$$

$$\therefore R_s < \frac{V_s(\min) - V_z}{I_z(\min) + I_L(\max)}$$

$$* I_z = \frac{V_s(t) - V_z}{R_s} - I_L < I_z(\max)$$

The worst condition

$$\frac{V_s(\max) - V_z}{R_s} - I_L(\min) < I_z(\max)$$

$$\therefore R_s > \frac{V_s(\max) - \sqrt{Z}}{I_z(\max) + I_L(\min)}$$


Combining the two results

$$\frac{V_s(\min) - \sqrt{Z}}{I_z(\min) + I_L(\max)} > R_s > \frac{V_s(\max) - \sqrt{Z}}{I_z(\max) + I_L(\min)}$$

not that $I_L(\max) = \frac{\sqrt{Z}}{R_L(\min)}$

and $I_L(\min) = \frac{\sqrt{Z}}{R_L(\max)}$

Example

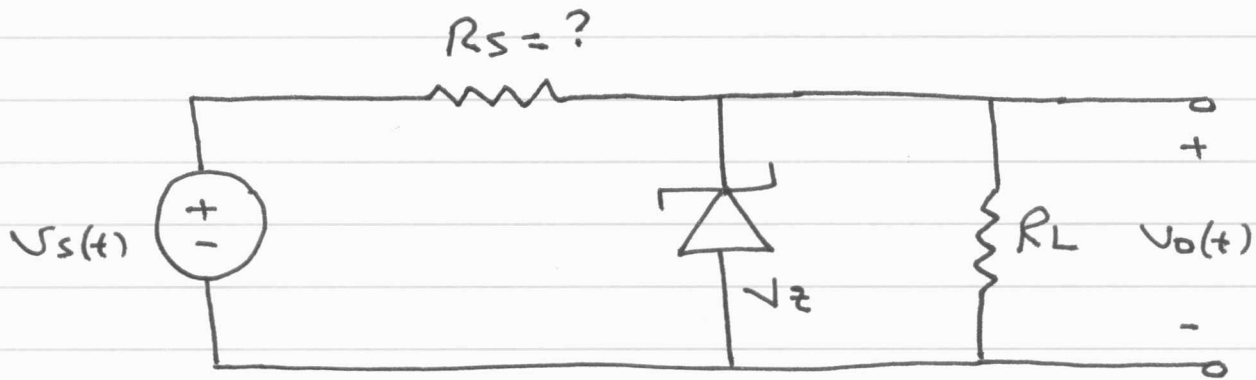

given :

Zener diode : $I_z(\min) = 5 \text{ mA}$
 $I_z(\max) = 200 \text{ mA}$

Load : $R_L(\min) = 500 \Omega$; $\therefore I_L(\max) = 20 \text{ mA}$
 $R_L(\max) = \infty$; $\therefore I_L(\min) = 0$

input signal : $V_s(\min) = 15 \text{ V}$
 $V_s(\max) = 20 \text{ V}$

$$\frac{V_s(\min) - V_z}{I_z(\min) + I_L(\max)} > R_s > \frac{V_s(\max) - V_z}{I_z(\max) + I_L(\min)}$$

$$200 > R_s > 50 \Omega$$

\therefore let $R_s = 100 \Omega$

To determine the effectiveness of the voltage regulator, we define two indicators

$$a) \text{ Load regulation} = \frac{\Delta V_o}{\Delta I_L}$$

assuming V_s constant

$$b) \text{ Line regulation} = \frac{\Delta V_o}{\Delta V_s}$$


assuming R_L fixed

For the simple voltage regulator, and using ideal model for the Zener diode

$$\frac{\Delta V_o}{\Delta I_L} = 0$$

$$\text{and } \frac{\Delta V_o}{\Delta V_s} = 0$$

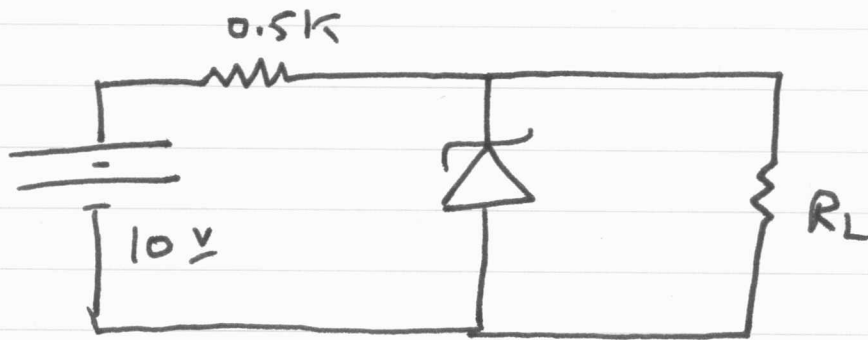a) Load regulation = $\frac{\Delta V_o}{\Delta I_L}$



$\infty \geq R_L \geq 2k$

The Zener have


$V_{zT} = 6.8V$ @ $I_{zT} = 5mA$ and $r_z = 20\Omega$

$V_z = V_{z0} + r_z I_z$

$\therefore V_{z0} = 6.7V$

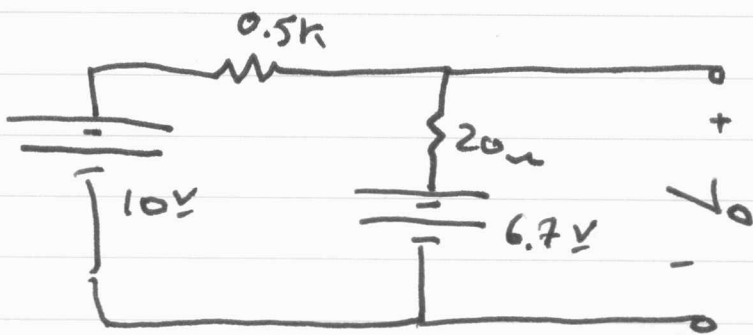1) let $R_L = \infty$

Since $V_S > V_{z0}$ \therefore The Zener is in breakdown





$V_o = 20 I_z + 6.7$

$I_z = \frac{10 - 6.7}{520} = 6.35mA$

$\therefore V_o = 6.83V$

2) let $R_L = 2k\Omega$

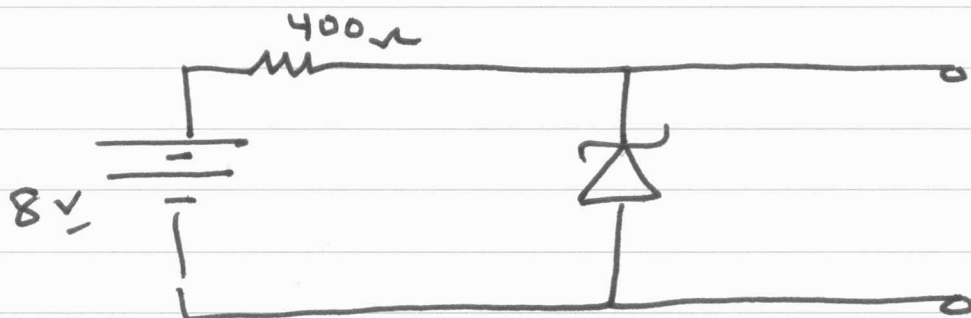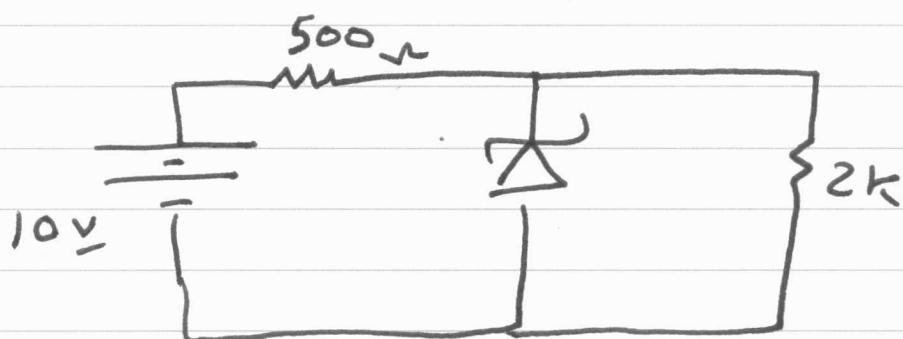

$$V_{TH} = \frac{2000}{2000 + 500} \cdot 10 = 8 \text{ V}$$

$$R_{TH} = 500 \parallel 2000 = 400 \Omega$$

Since $V_{TH} > V_{z0}$, Zener in breakdown

$$V_o = V_{z0} + V_z I_z$$

$$V_o = 6.7 + 20 \left(\frac{8 - 6.7}{420} \right) = 6.76 \text{ V}$$

$$I_L = \frac{V_o}{R_L} = \frac{6.76}{2k} = 3.38 \text{ mA}$$

$$\frac{\Delta V_o}{\Delta I_L} = \frac{6.76 - 6.83}{3.38 - 0} = \frac{-70 \text{ mV}}{3.38 \text{ mA}} = -20.7 \frac{\text{mV}}{\text{mA}}$$

$$b) \text{ Line regulation} = \frac{\Delta V_o}{\Delta V_s}$$

1. when $V_s = 10 \text{ V}$

$$11.7 \text{ V} \approx 10 \text{ V}$$

$$V_o = 6.76 \text{ V}$$

2. when $V_s = 11 \text{ V}$



$$V_{TH} = 8.8 \text{ V}$$

$$R_{TH} = 0.4 \text{ k}$$

$$V_o = V_{Z_0} + r_z I_z$$

$$V_o = 6.7 + 20 \left(\frac{8.8 - 6.7}{420} \right) = 6.8$$

$$\frac{\Delta V_o}{\Delta V_s} = \frac{6.8 - 6.76}{11 - 10} = +38 \frac{\text{mV}}{\text{V}}$$

For the following circuit; Calculate and sketch the output voltage for

$$V_s(t) = 10 \sin \omega t \text{ V}$$

given $V_z = 5 \text{ V}$

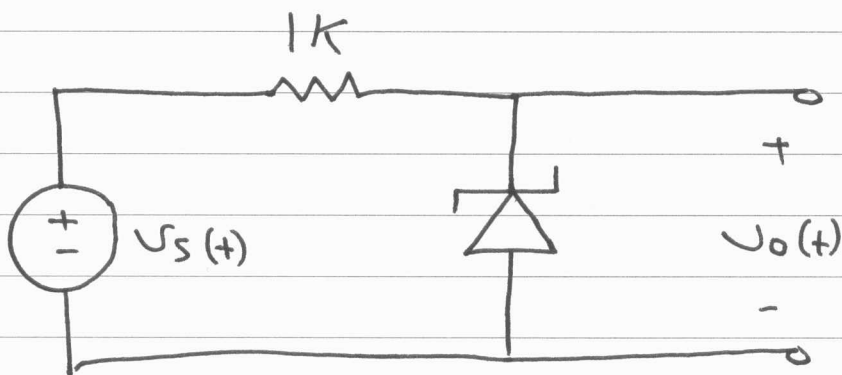


Fig. (1)

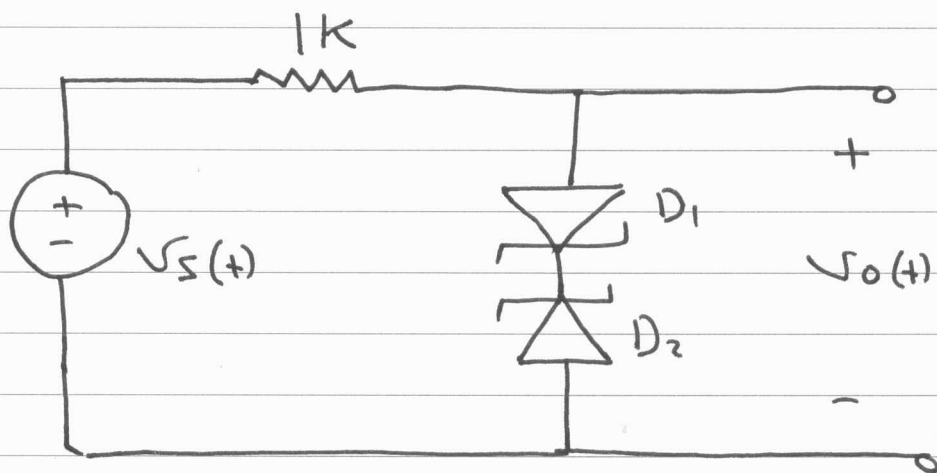


Fig. (2)