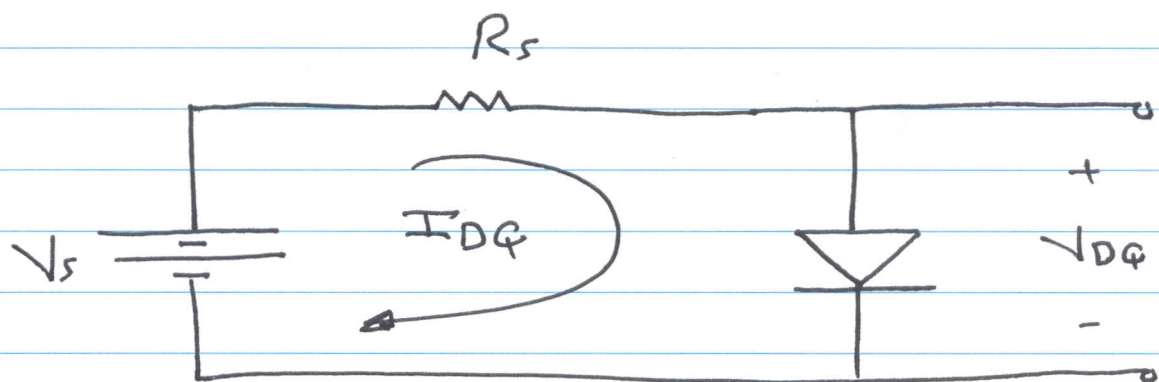



Ac Small Signal Analysis



$$I_{DQ} = I_s \left(e^{\frac{V_{DQ}}{nV_T}} - 1 \right)$$

$$I_{DQ} \approx I_s e^{\frac{V_{DQ}}{nV_T}}$$

now

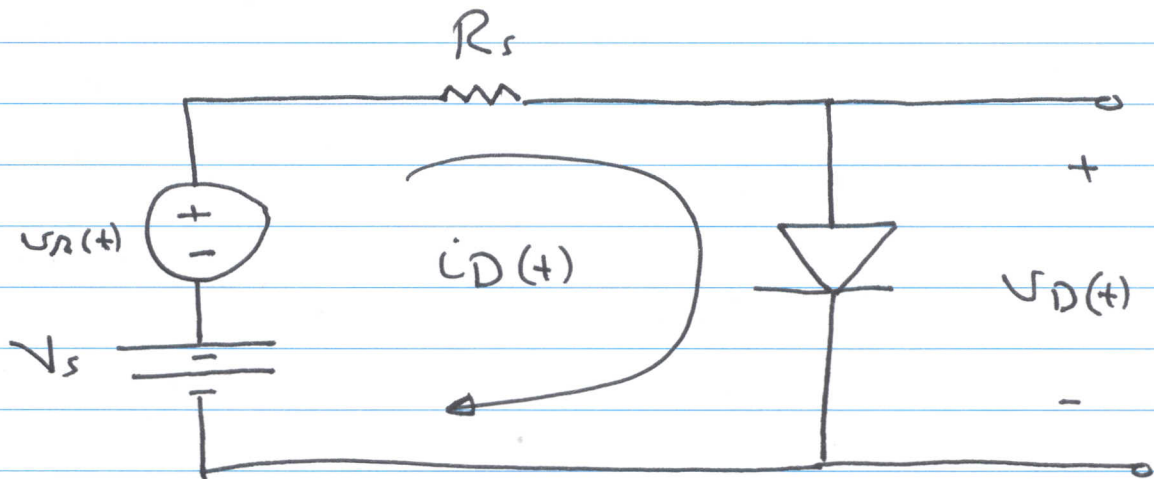

$$i_D(t) = I_{DQ} + i_d$$

$$v_D(t) = V_{DQ} + v_d$$

$$i_D(t) = I_s \left(e^{\frac{v_D(t)}{nV_T}} - 1 \right)$$

and since the diode is forward biased

$$i_D(t) \cong I_s e^{\frac{v_D(t)}{nV_T}}$$

$$i_D(t) = I_s e^{\frac{v_{DQ} + v_d}{nV_T}}$$

$$i_D(t) = I_s e^{\frac{v_{DQ}}{nV_T}} \cdot e^{\frac{v_d}{nV_T}}$$

$$i_D(t) = I_{DQ} \cdot e^{\frac{v_d}{nV_T}}$$

using $e^x \approx 1 + x$; x very small

$$\therefore i_D(t) = I_{DQ} \left(1 + \frac{v_d}{nV_T} \right)$$

$$i_D(t) = I_{DQ} + \frac{v_d}{\frac{nV_T}{I_{DQ}}}$$

But $i_D(t) = I_{DQ} + i_d$

$$\therefore i_d = \frac{v_d}{\frac{nV_T}{I_{DQ}}} = \frac{v_d}{r_d}$$

where $r_d = \frac{nV_T}{I_{DQ}} \approx \frac{V_T}{I_{DQ}}$

$$\therefore \text{ If } v_s(t) = v_s + v_r(t)$$

$v_s \equiv$ Dc Component


$v_r(t) \equiv$ ac Component

and the amplitude of $v_r(t)$ is small
and the diode is always on ;


We could use the superposition

theorem to find the response $(i(t), v(t))$

Example


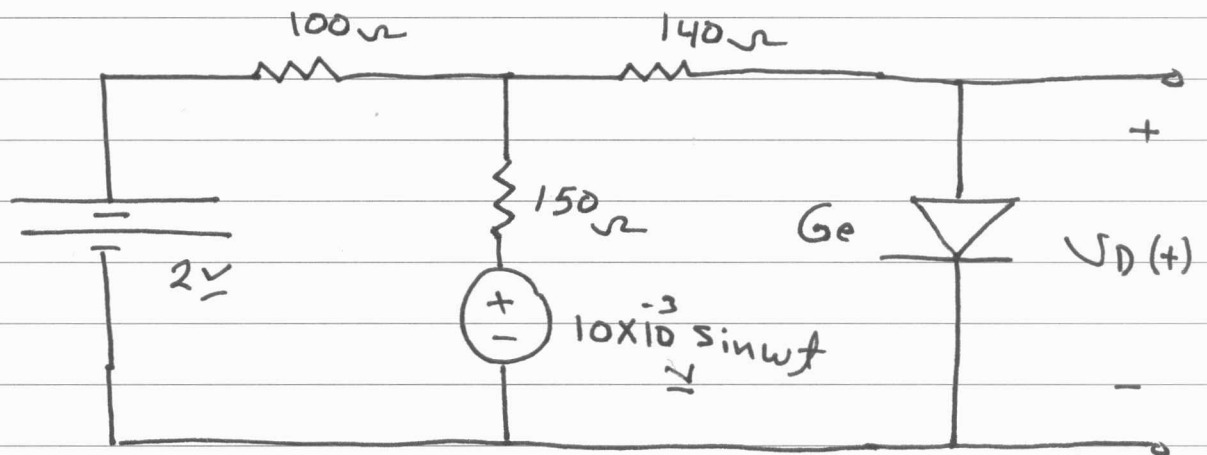


Find $V_D(t)$.

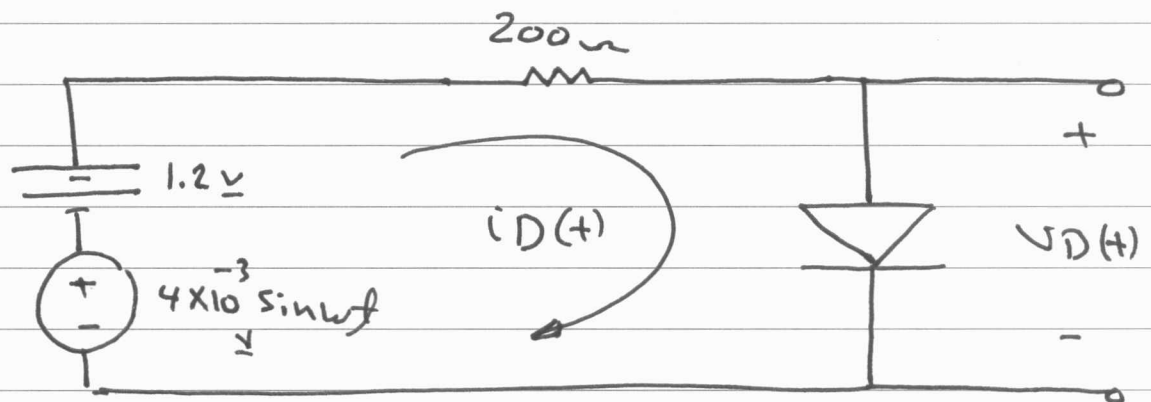

Since we have a dc source ($1.2V$) and an ac signal ($4 \times 10^{-3} \sin \omega t$) and the diode is always on; we use superposition theorem to find $V_D(t)$

1) To Find V_{DQ} (DC Analysis)

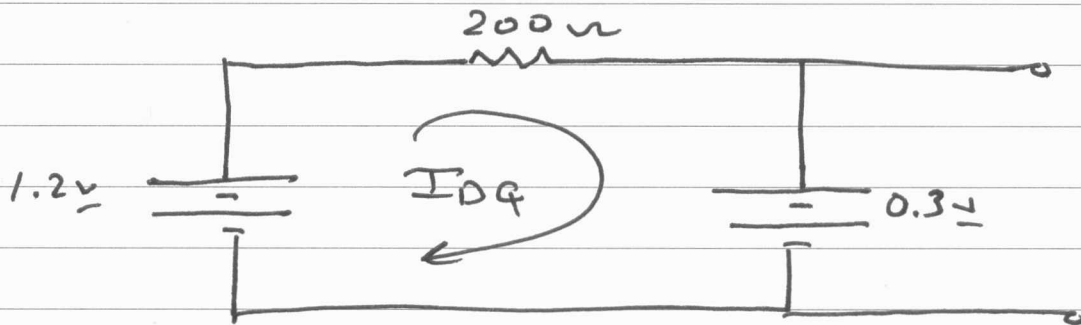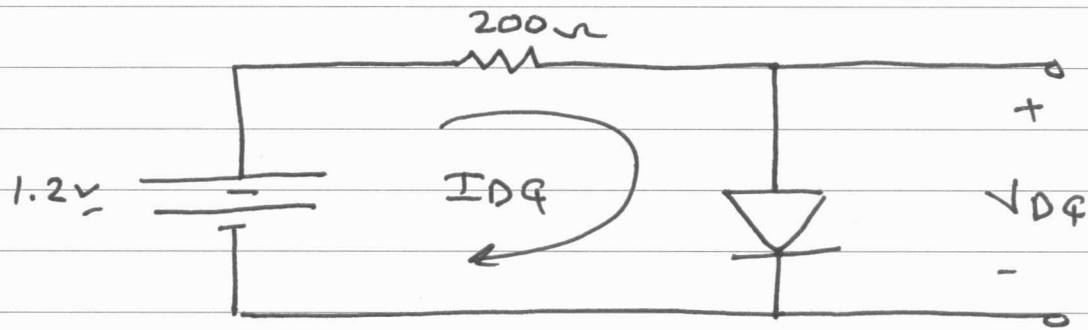



$$\therefore V_{DQ} = 0.3 \text{ V}$$

$$\text{and } I_{DQ} = \frac{1.2 \text{ V} - 0.3 \text{ V}}{200 \Omega} = 4.5 \text{ mA}$$

$$\therefore r_d = \frac{V_T}{I_{DQ}} = \frac{25.69 \text{ mV}}{4.5 \text{ mA}} = 5.69 \Omega$$

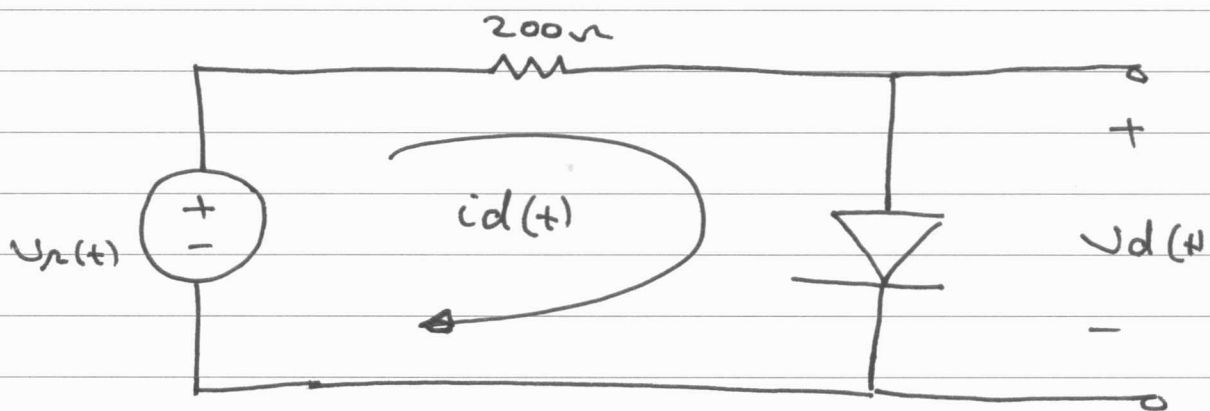2) To find $v_d(t)$ (ac small signal analysis)



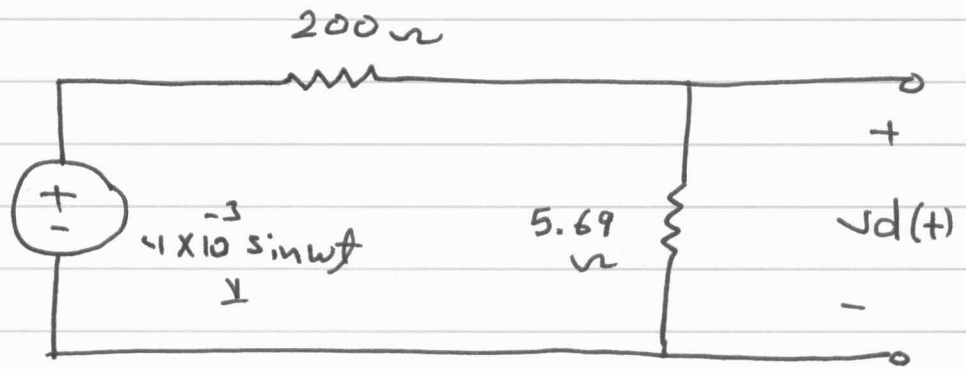

$$v_d(t) = \frac{5.69}{200 + 5.69} \cdot 4 \times 10^{-3} \sin \omega t \approx$$

$$v_d(t) = 0.1165 \times 10^{-3} \sin \omega t \approx$$

$$\therefore v_D(t) = v_{DC} + v_d(t)$$

$$v_D(t) = (0.3 + 0.1165 \times 10^{-3} \sin \omega t) \approx$$