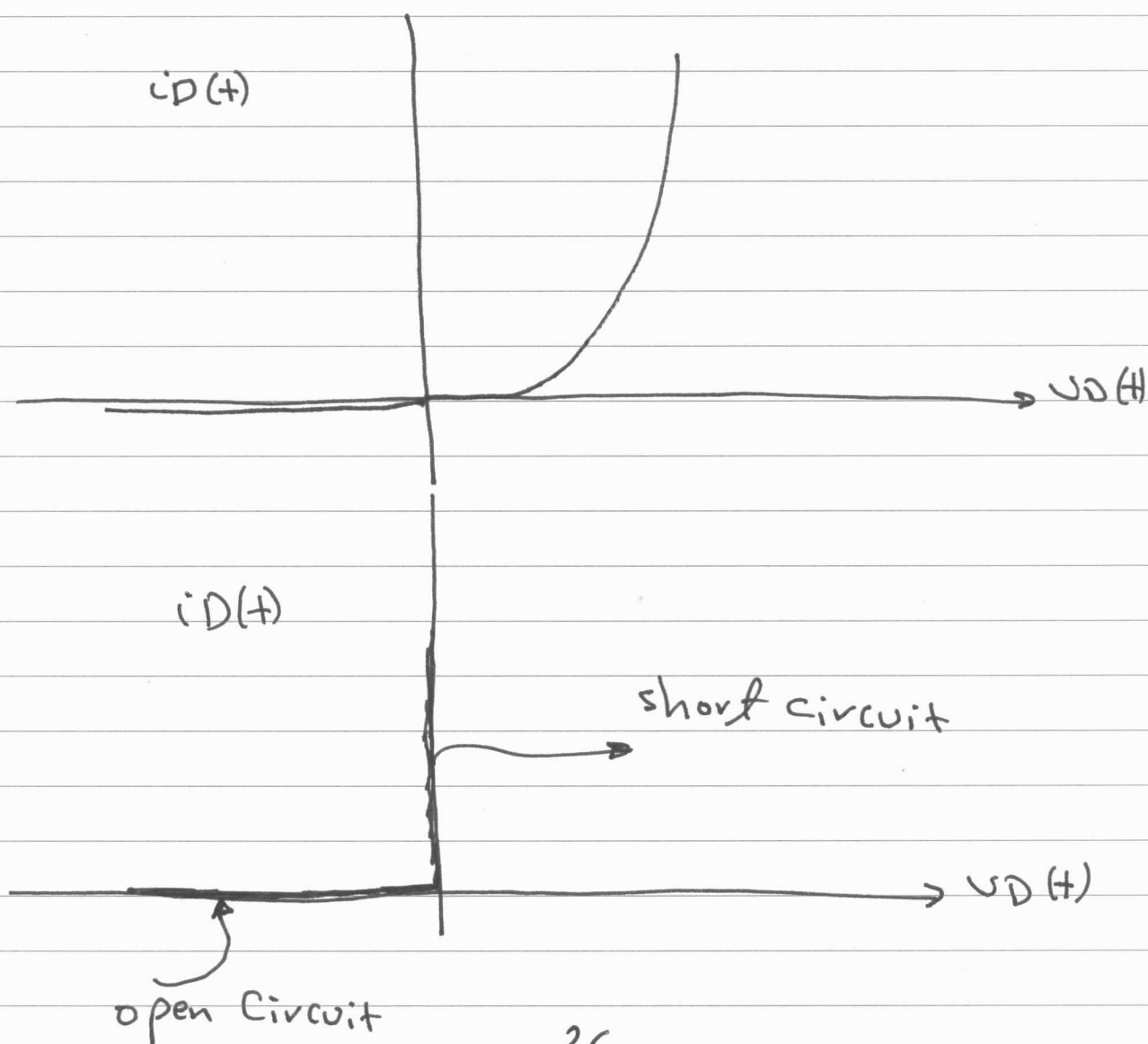


### 3) The use of models

A piece wise Linear models is an electrical equivalent circuit of a non linear electronic device. It is composed of Linear circuit elements arranged to approximate the characteristics of the electronic device.



#### a) ideal diode model



\* When  $V_s \geq 0$ ; the Diode is on, and replaced with short circuit


\* When  $V_s < 0$ ; the diode is off, and replaced with open circuit

b) Knee voltage model

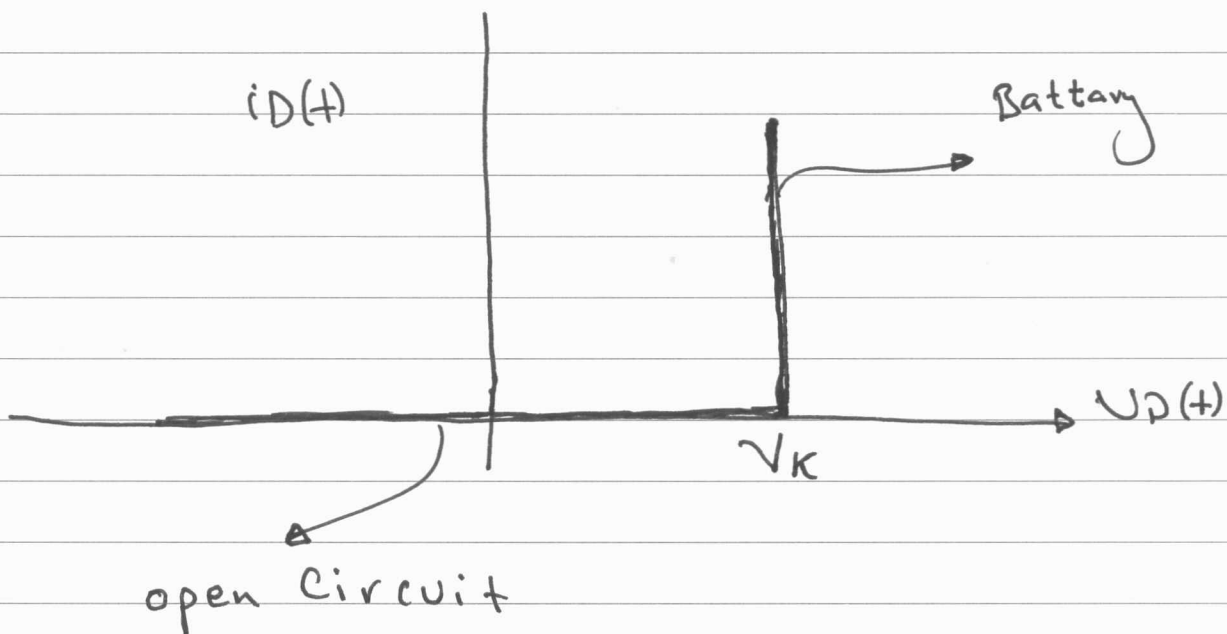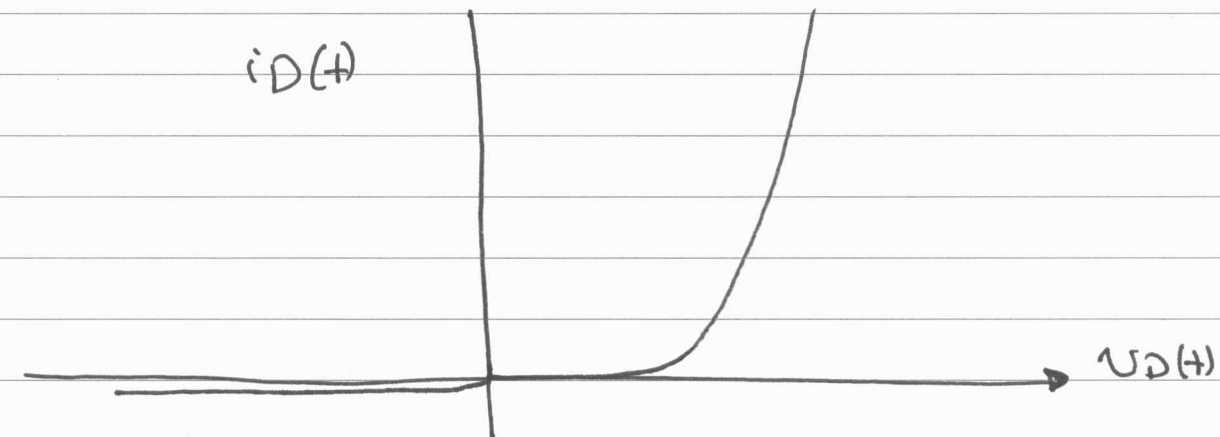


\* When  $V_s \geq V_K$ , the diode is on and replaced with a constant voltage


Source

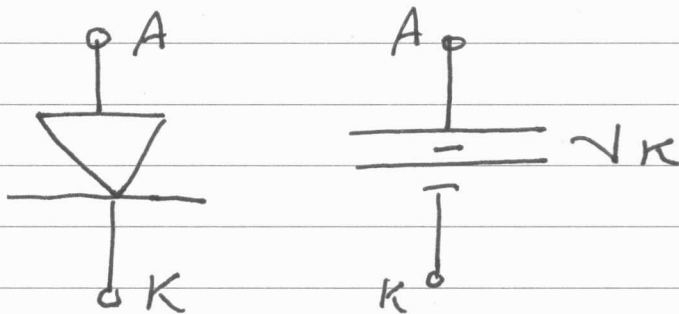

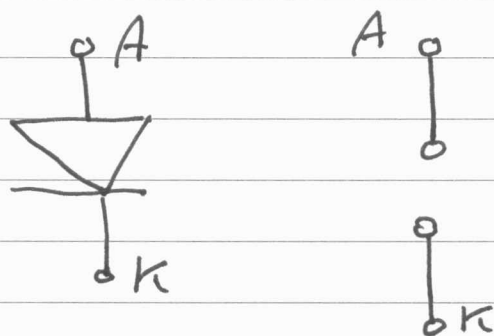
\* When  $V_s < V_K$ , the diode is off and replaced with open circuit



### c) Dynamic resistance model

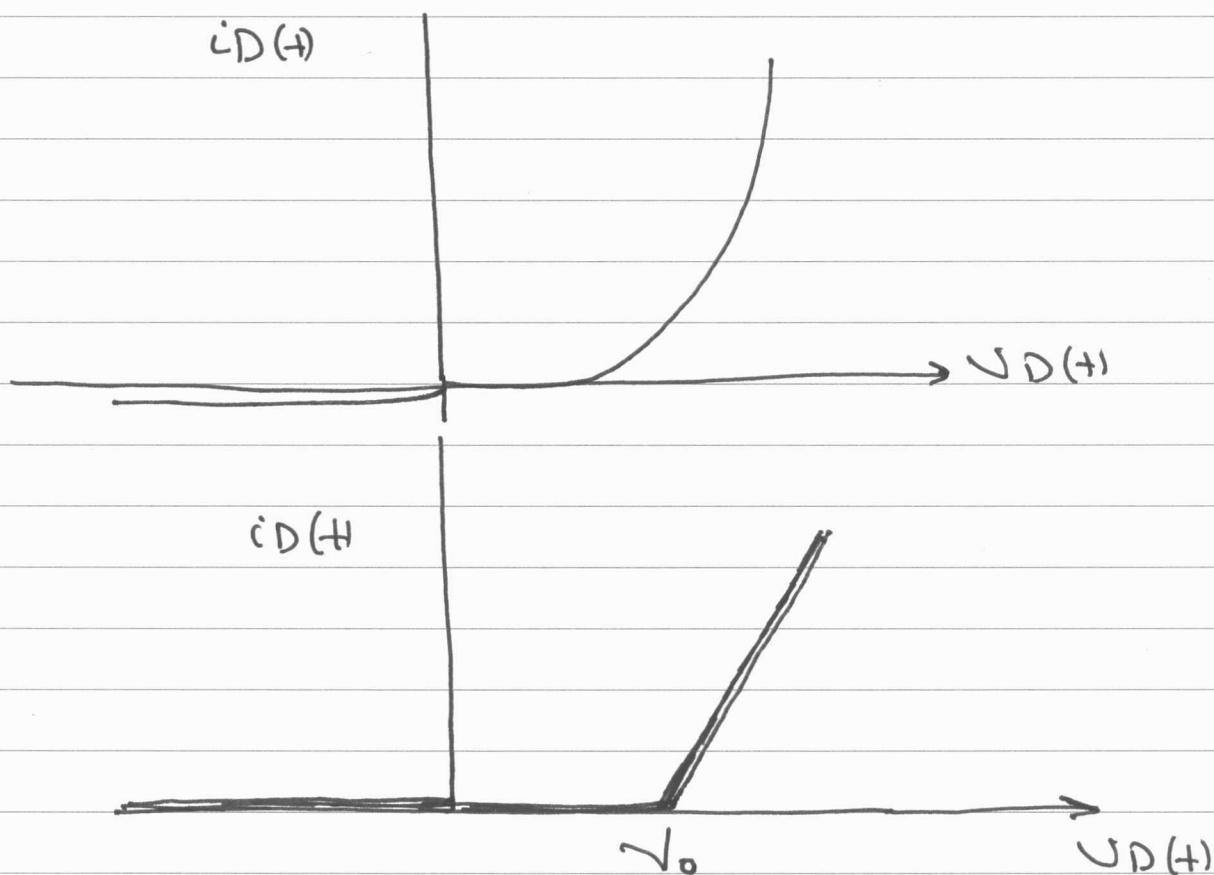


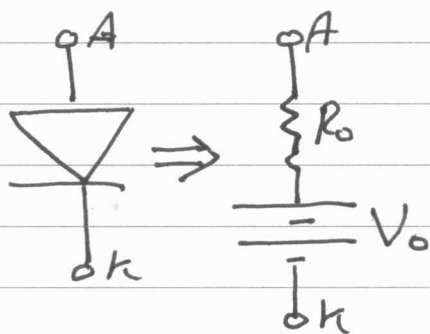\* When  $v_s \geq V_0$ , the diode is on, and replaced with



\* When  $v_s < V_0$ , the diode is off, and replaced with open circuit

## Example

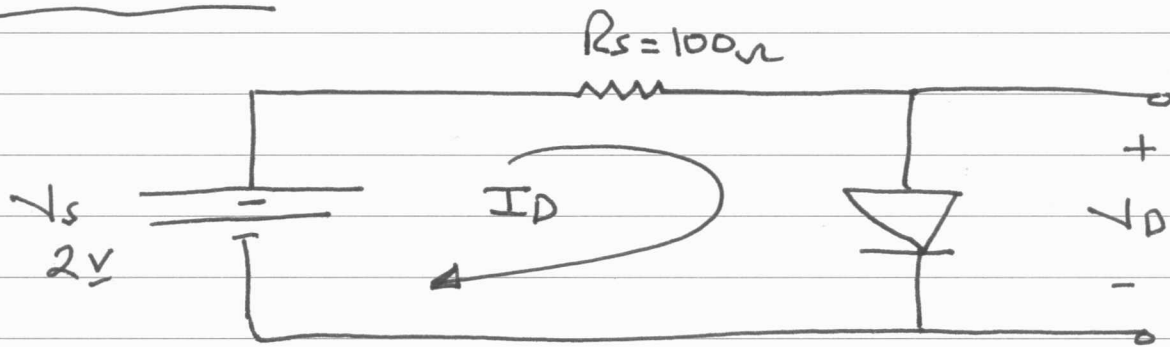


Find the Q point ( $I_{DQ}$ ,  $V_{DQ}$ ) using

- ideal diode model
- knee voltage model

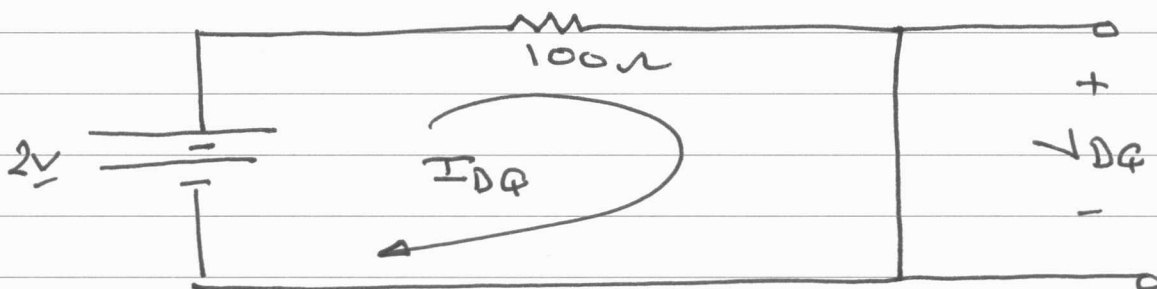a) using ideal diode model


Since  $V_s > 0$ , the diode is on and replaced with short circuit.




$$\therefore I_{DQ} = \frac{2}{100} = 20 \text{ mA}$$

$$\therefore V_{DQ} = 0 \text{ V}$$

b) using knee voltage model

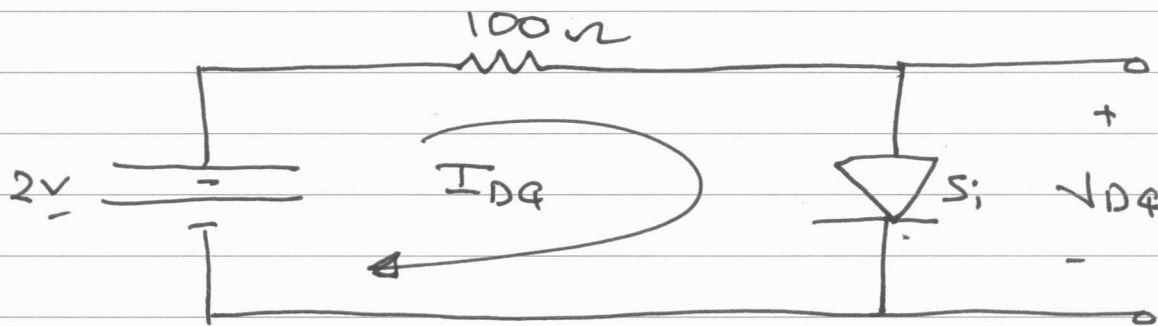

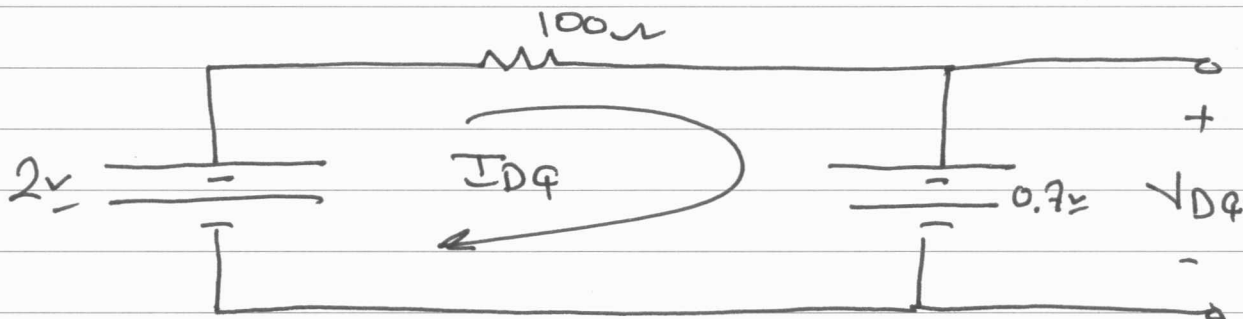Since  $V_s > 0.7$ , the diode is on,  
and replaced with  $V_K = 0.7V$



$$I_{DQ} = \frac{2 - 0.7}{100} = 13 \text{ mA}$$

$$V_{DQ} = 0.7 \text{ V}$$

c) using non linear mathematics

$$I_{DQ} = 12.137 \text{ mA}$$

$$V_{DQ} = 0.7863 \text{ V}$$

Taking the knee voltage into account

\* If  $V_s > 10V_K$ , we could use ideal diode model.

\* If  $V_s < 10V_K$ , we must use the knee voltage model.