
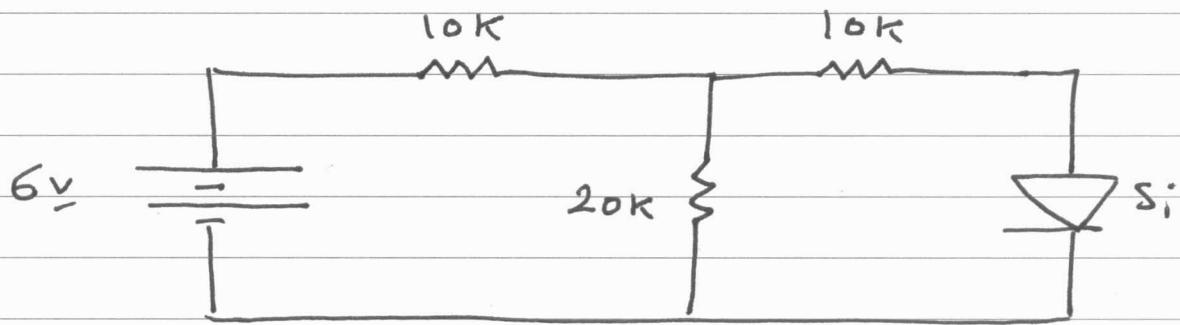


## Example

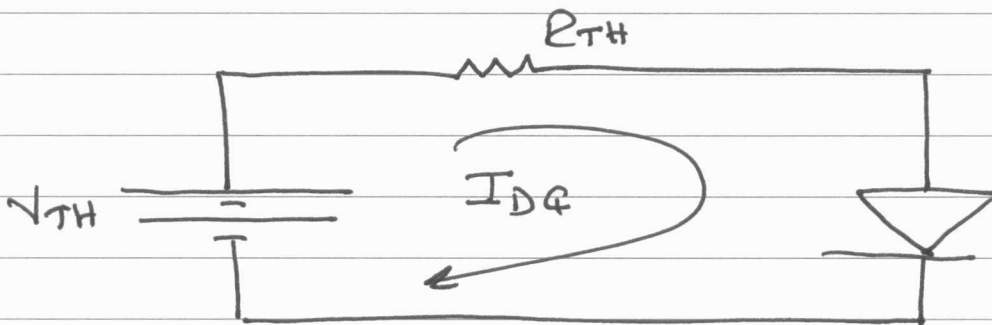

Find the Q point

Using thevenin's theorem, the circuit is simplified to




$$R_{TH} = 10k + 10k \parallel 20k = 16.7k$$

$$V_{TH} = \frac{20k}{20k + 10k} \cdot 6 = 4V$$

Since  $V_{TH} \gg V_K$ , the diode is on

Since  $V_{TH} < 10V_K$ , we must use the

Knee voltage model

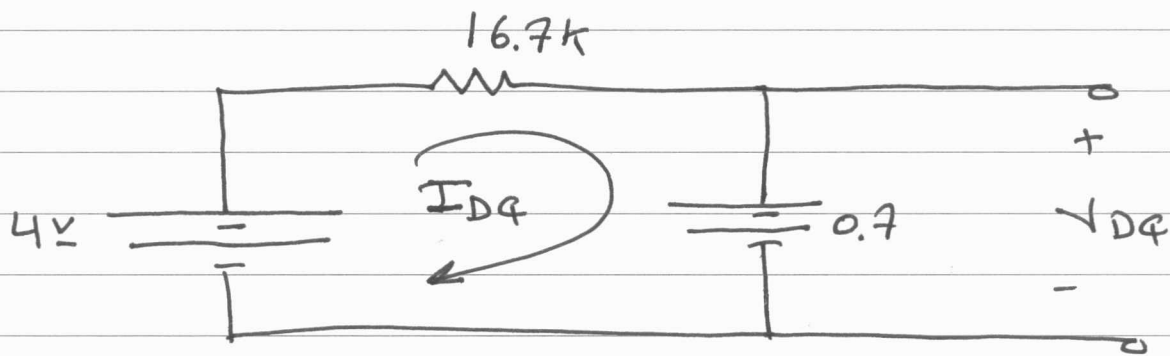


$$I_{DQ} = \frac{4 - 0.7}{16.7k} = 0.198 \text{ mA}$$

$$V_{DQ} = V_K = 0.7 \text{ V}$$

### Second method

assume the diode is on, replace it

with  $V_K = 0.7 \text{ V}$

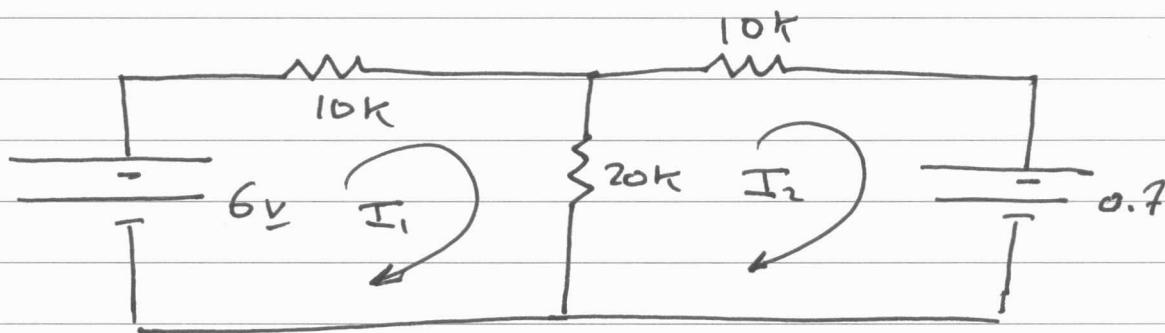

$$6 = 30 I_1 - 20 I_2$$

$$-0.7 = -20 I_1 + 30 I_2$$


Solve for  $I_2 = 0.198 \text{ mA}$

$$\therefore I_D = I_2 = 0.198 \text{ mA}$$

Since  $I_D > 0$ ,  $\therefore$  our assumption is OK


# Diode Large-Signal Applications

## 1) Diode Clipper Circuit

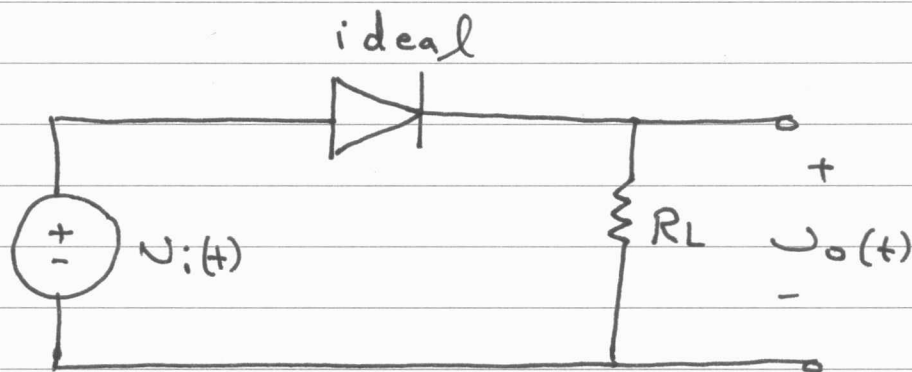

a) assume the diode is on

b) replace it with short circuit

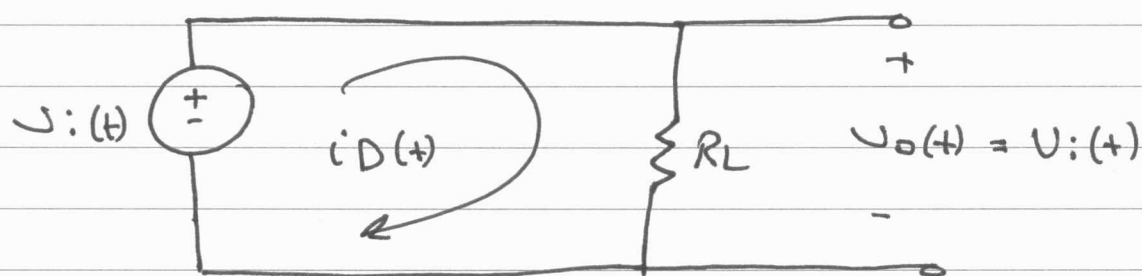

c)  $i_D(t) > 0$


$$i_D(t) = \frac{v_i(t)}{R_L} > 0$$

$$\therefore v_i(t) > 0$$


$\therefore$  When  $v_i(t) > 0$ , the diode is on

and  $v_o(t) = v_i(t)$

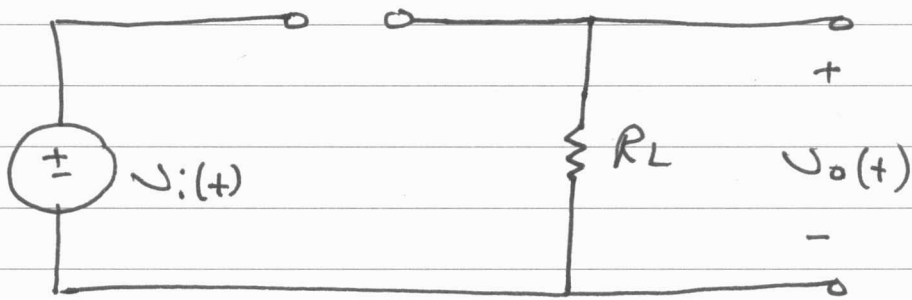$\therefore$  When  $V_i(t) < 0$  ; the diode is OFF





$$V_o(t) = 0$$

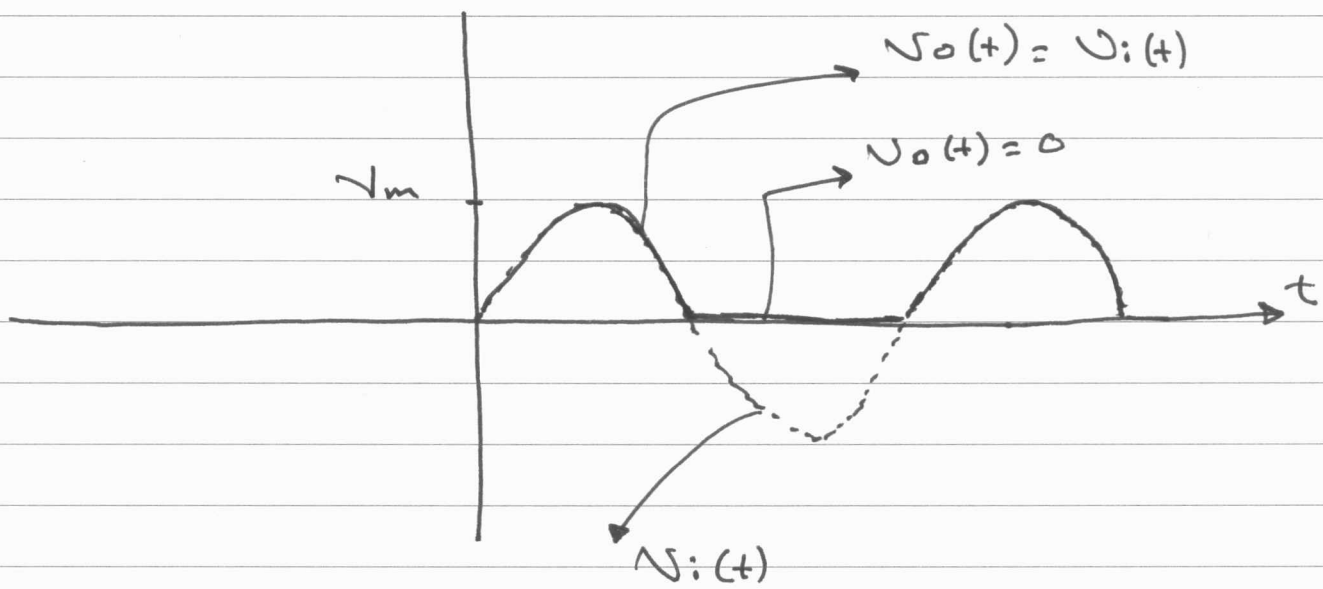


$\therefore$  The Clipper Circuit used to eliminate portion of the input signal.

# Example

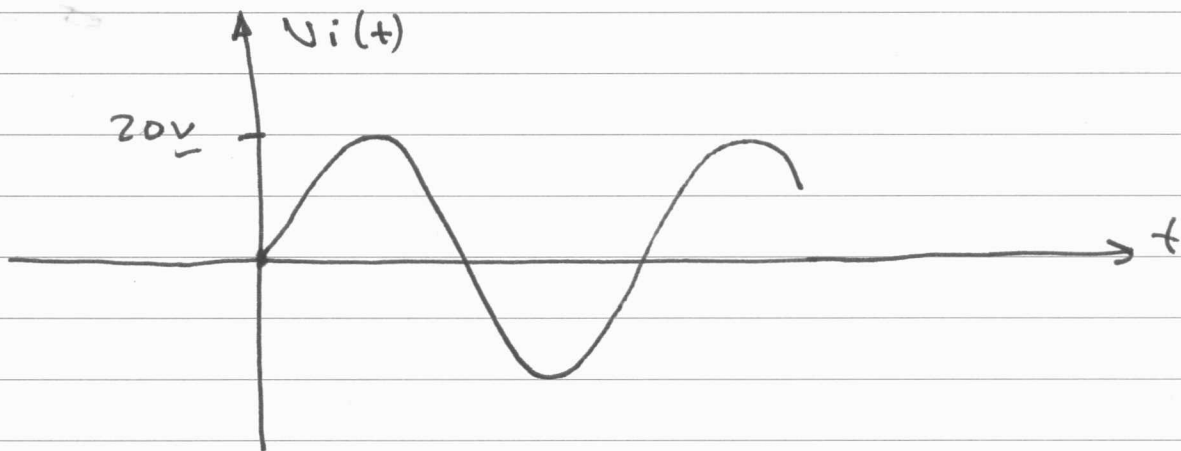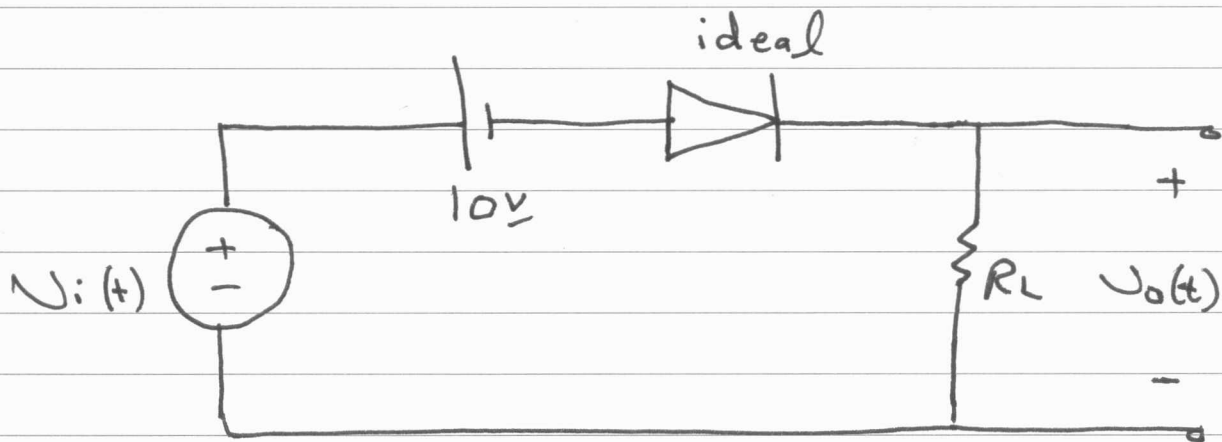

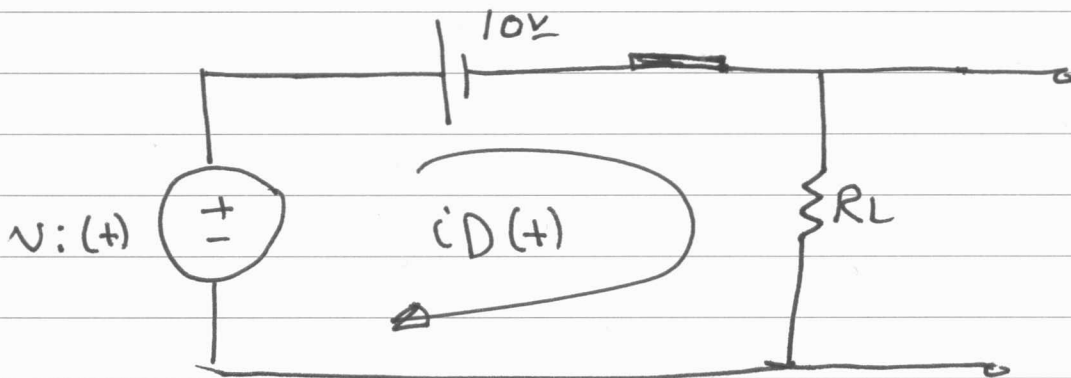- assume that the diode is on
- replace it with short circuit
- $i_D(t) > 0$



$$i_D(t) = \frac{v_i(t) - 10}{R_L} > 0$$

$$\therefore V_i(t) - 10 > 0$$


$$\therefore V_i(t) > 10 \Rightarrow$$

$\therefore$  when  $V_i(t) > 10 \underline{\neq}$ , the diode is on and  $V_o(t) = V_i(t) - 10$


and also we can prove that

when  $V_i(t) < 10 \underline{\neq}$ , the diode is

OFF

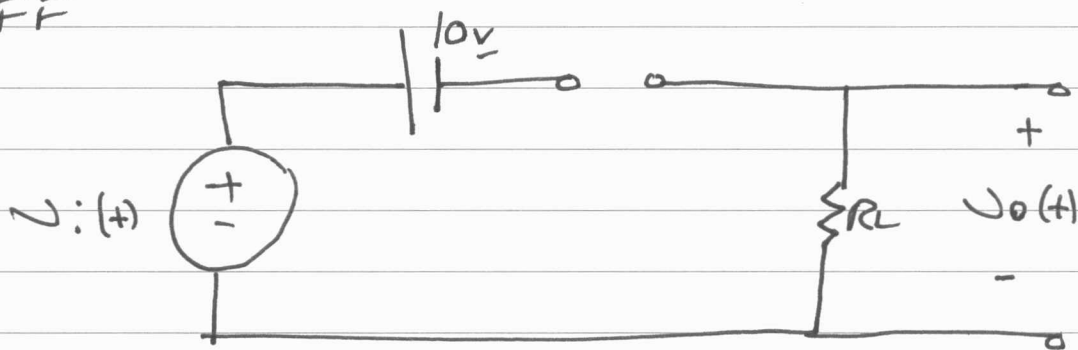


$$\therefore V_o(t) = 0$$

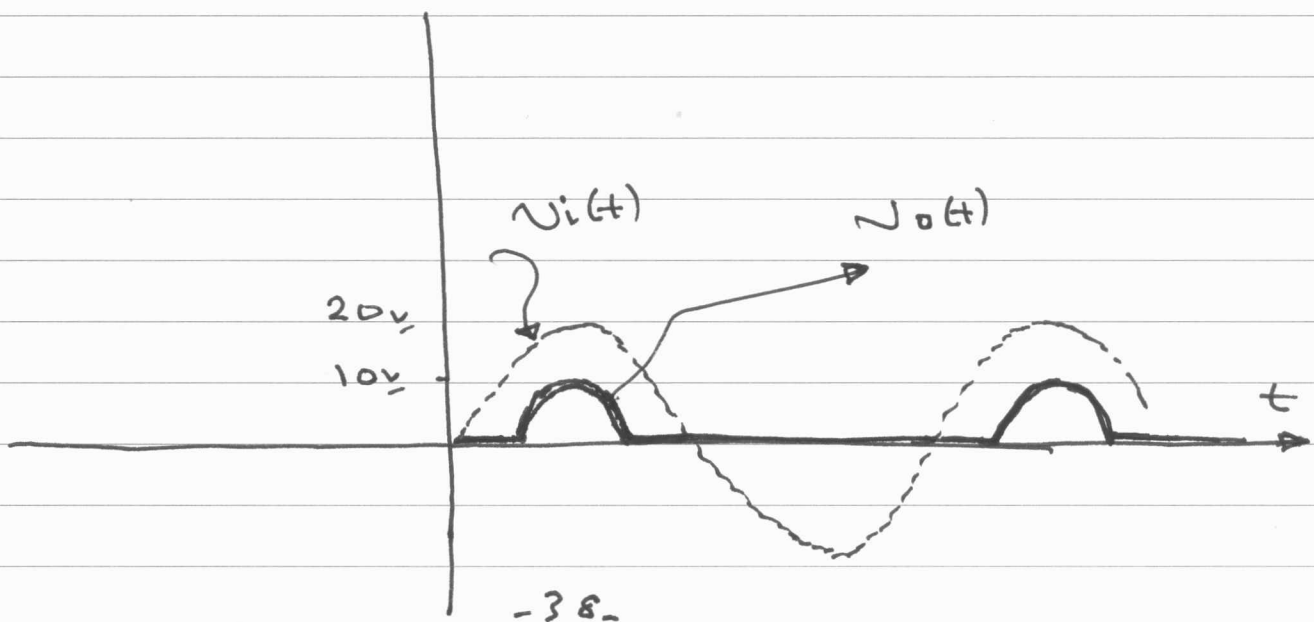
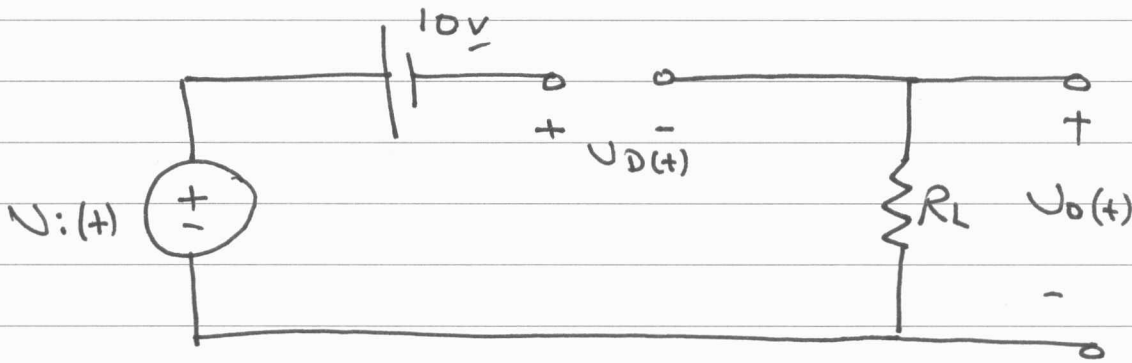
## Second method

- assume that the diode is OFF
- replace it with open circuit
- $V_D(t) < 0$



$$V_D(t) = -10 + V_i(t) < 0$$

$$\therefore V_i(t) < 10 \text{ V}$$

$\therefore$  When  $V_i(t) < 10 \text{ V}$ , the diode is OFF, and  $V_o(t) = 0$