
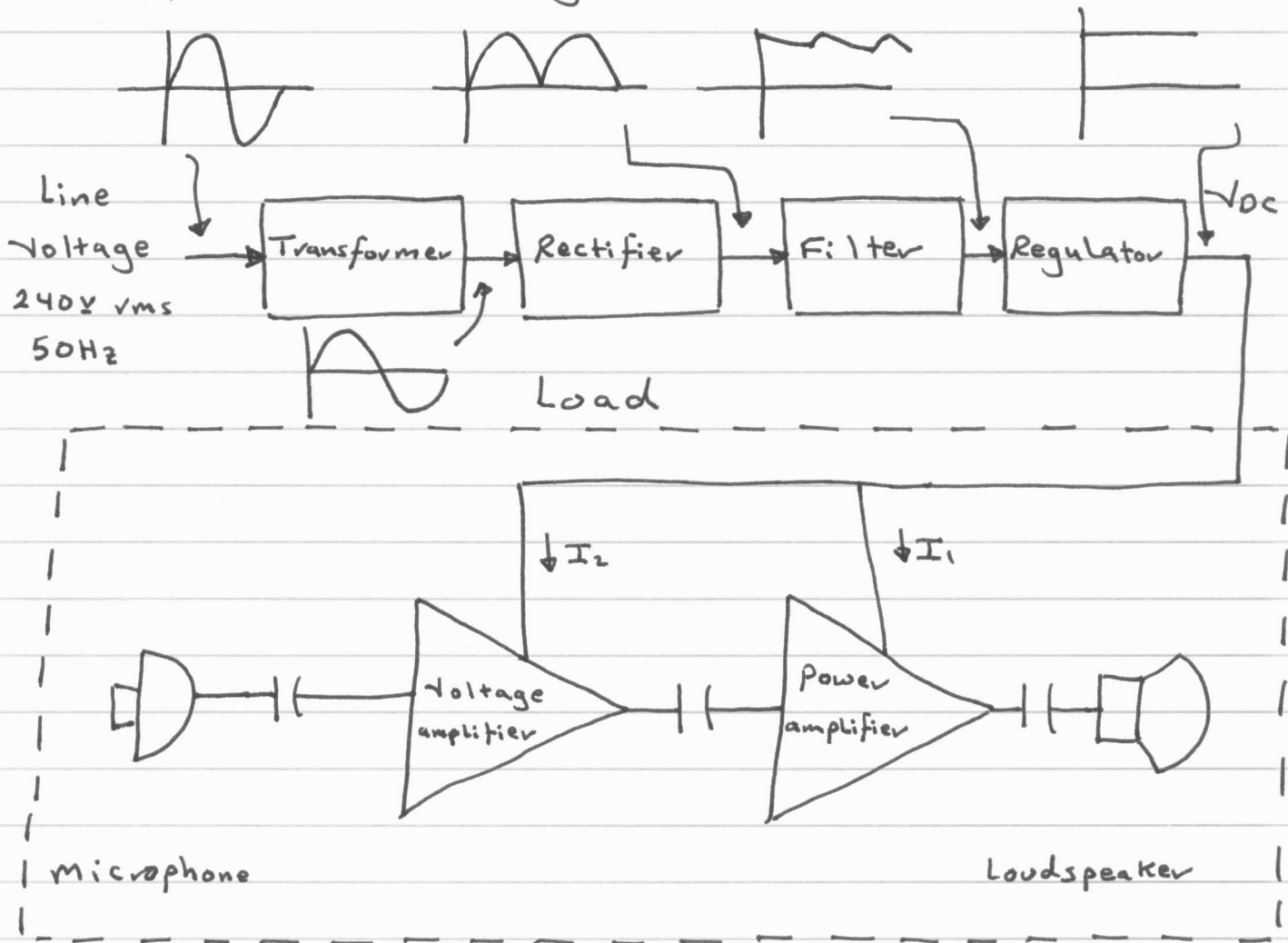

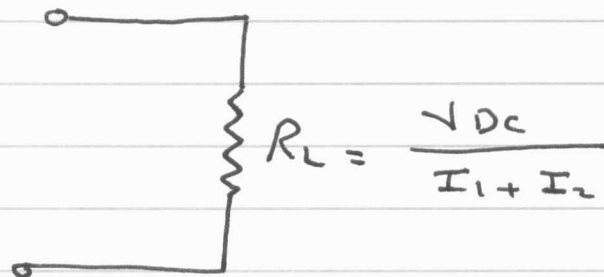
# Dc Power Supply


ALL electronic Circuits and systems require a stable source of dc voltage and current (or dc power) to operate correctly.



Load model




$$R_L = \frac{V_{DC}}{I_1 + I_2}$$

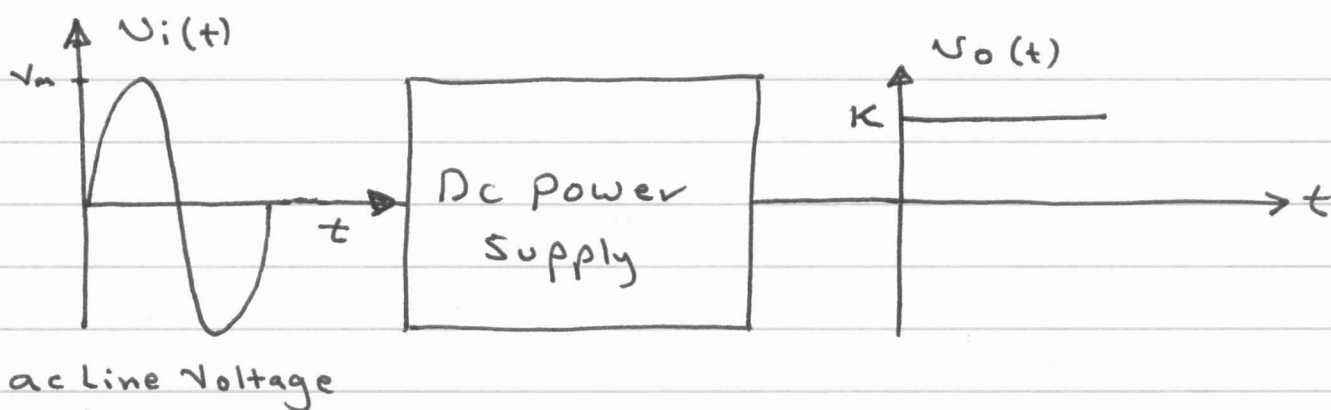

The basic power supply consists of a transformer, rectifier, filter, and a regulator

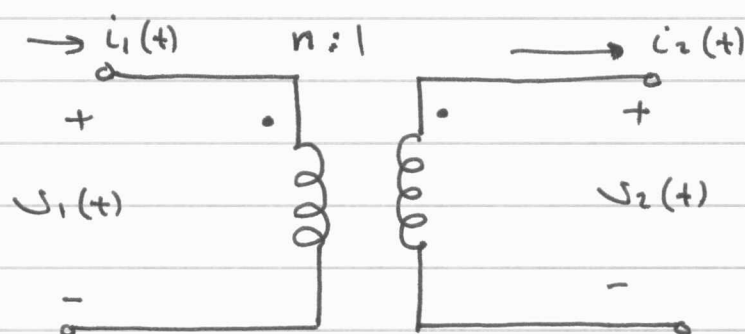Transformer : used to increase or decrease the amplitude of the ac line voltage





$$V_2(t) = \frac{1}{n} V_1(t)$$

$$i_2(t) = n i_1(t)$$

Rectifier : used to Convert the ac Voltage

(Zero-average value) into either positive or negative pulsating dc

### 1. Half-Wave Rectifier

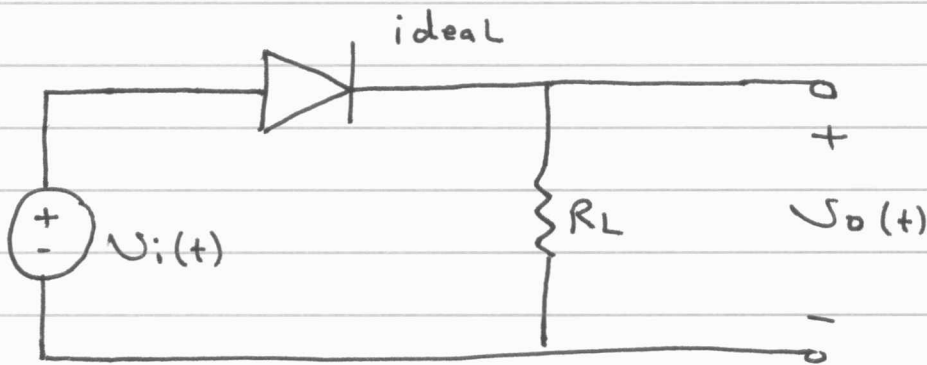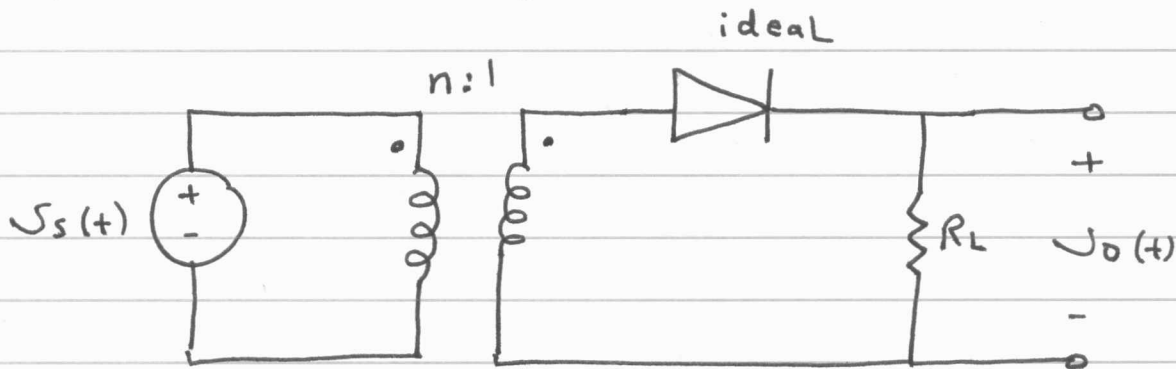

$$v_i(t) = \frac{v_s(t)}{n}$$

a) when  $v_i(t) > 0$ , Diode is on (short circuit)





$$\therefore v_o(t) = v_i(t)$$

$$\therefore v_D(t) = 0$$

b) when  $v_i(t) < 0$ , Diode is OFF (open circuit)

$$\therefore v_o(t) = 0$$

$$\therefore v_D(t) = v_i(t)$$

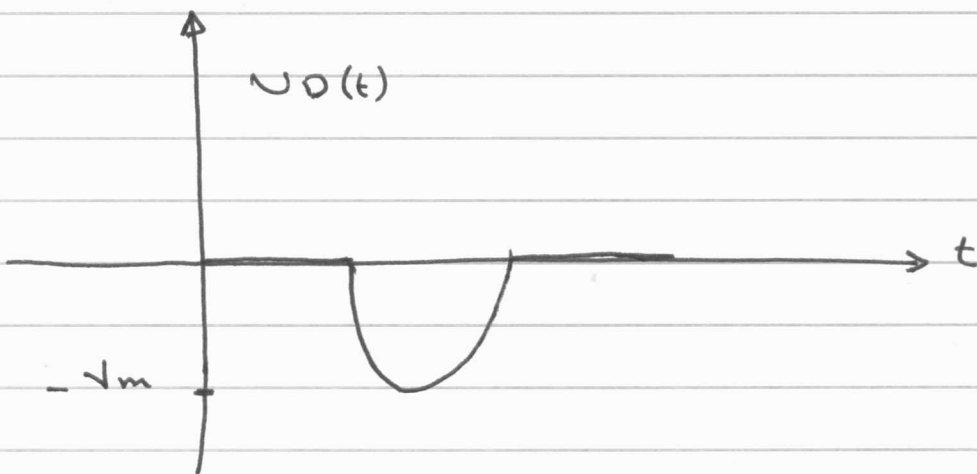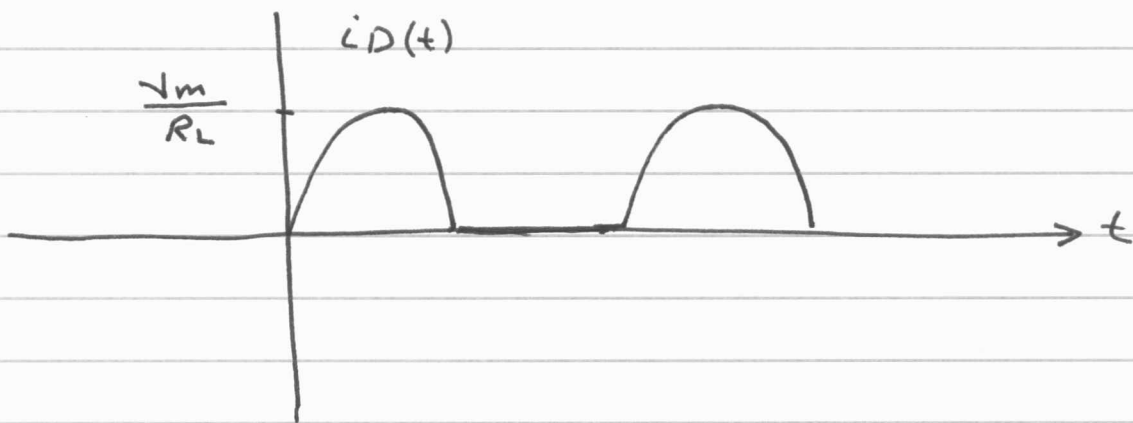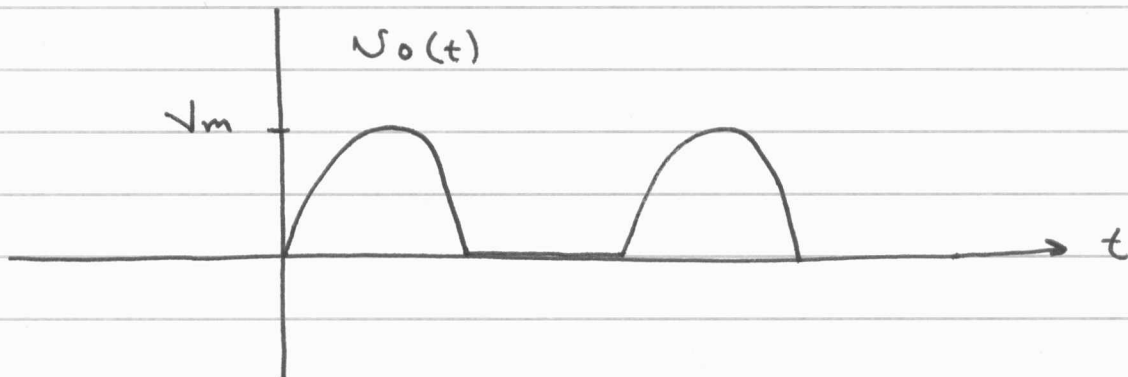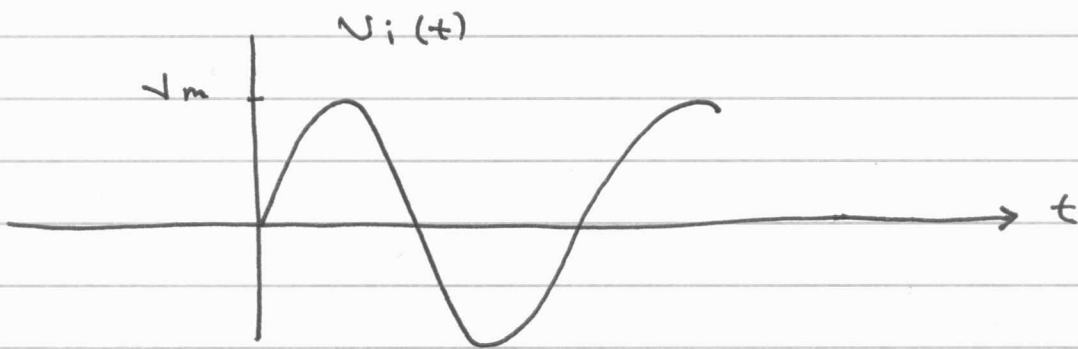


$$V_{0,av} = \frac{1}{T} \int_0^T V_0(t) dt$$

$$= \frac{1}{2\pi} \int_0^\pi \sin \theta d\theta$$

$$V_{0,av} = \frac{V_m}{\pi}$$

$$T = T_0$$

$$f = f_0$$

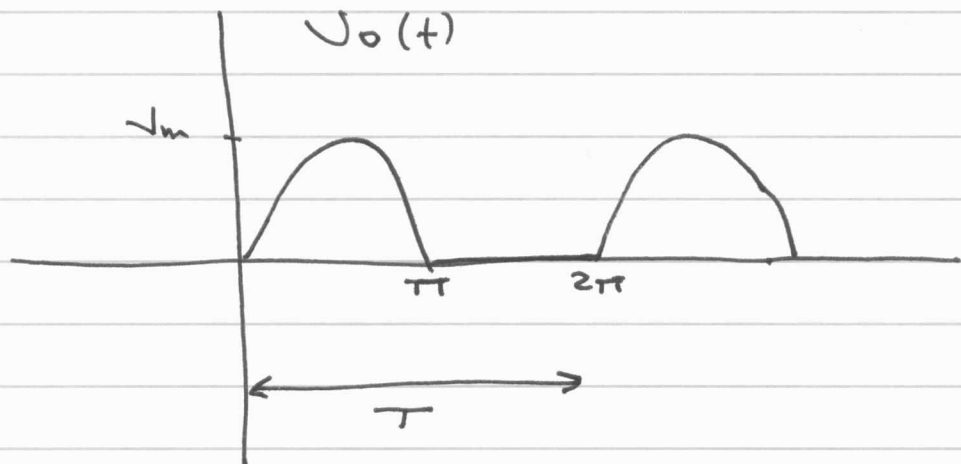

$$i_D(t)_{av} = \frac{V_m}{\pi R_L}$$

# Important Electrical Ratings

$I_{FM} \equiv$  maximum forward current


$I_{FM} =$  Maximum average current that can safely be sustained by the diode when it is forward biased

$V_{RM} \equiv$  maximum reverse voltage

$V_{RM} =$  maximum voltage that can be applied to the diode in the reverse bias polarity before voltage breakdown occurs

$PIV \equiv$  Peak inverse voltage

$$PIV = V_{RM}$$

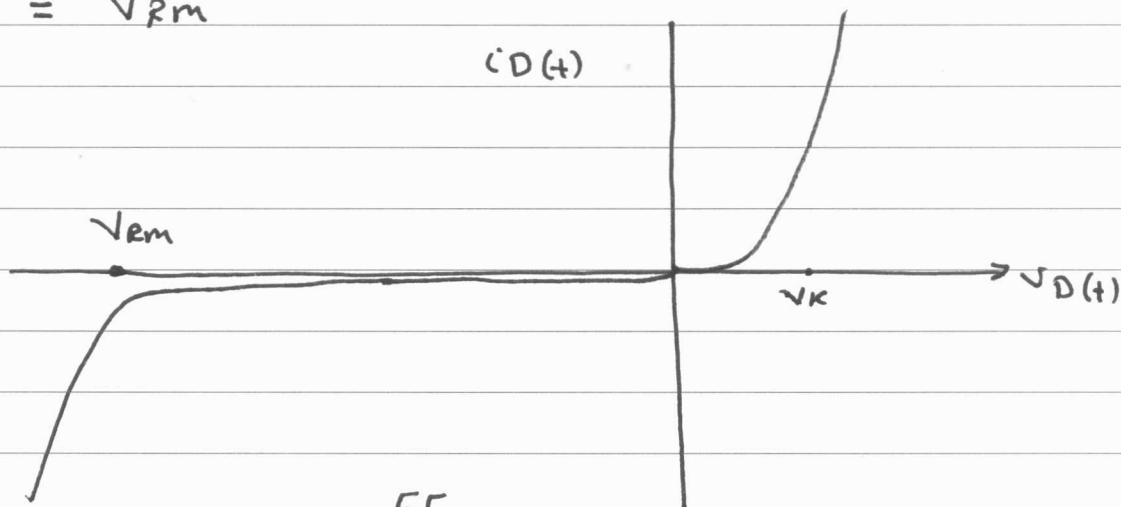


∴ For the half-wave rectifier

$$V_{o,av} = \frac{V_m}{\pi}$$

$$I_{FM} = \frac{V_m}{\pi R_L}$$

$$PIV = -V_m$$

When  $V_i(t) < 0$ , Diode is OFF

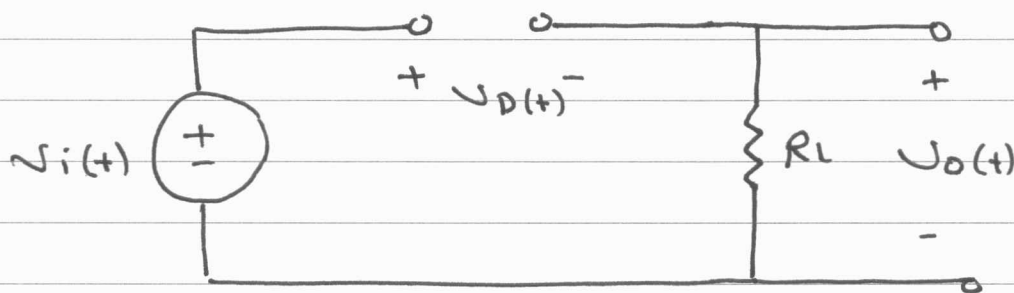


$$V_D(t) = V_i(t) < 0$$

$$\therefore V_{D(t),max} = -V_m$$



## 2) Full-wave Rectifier
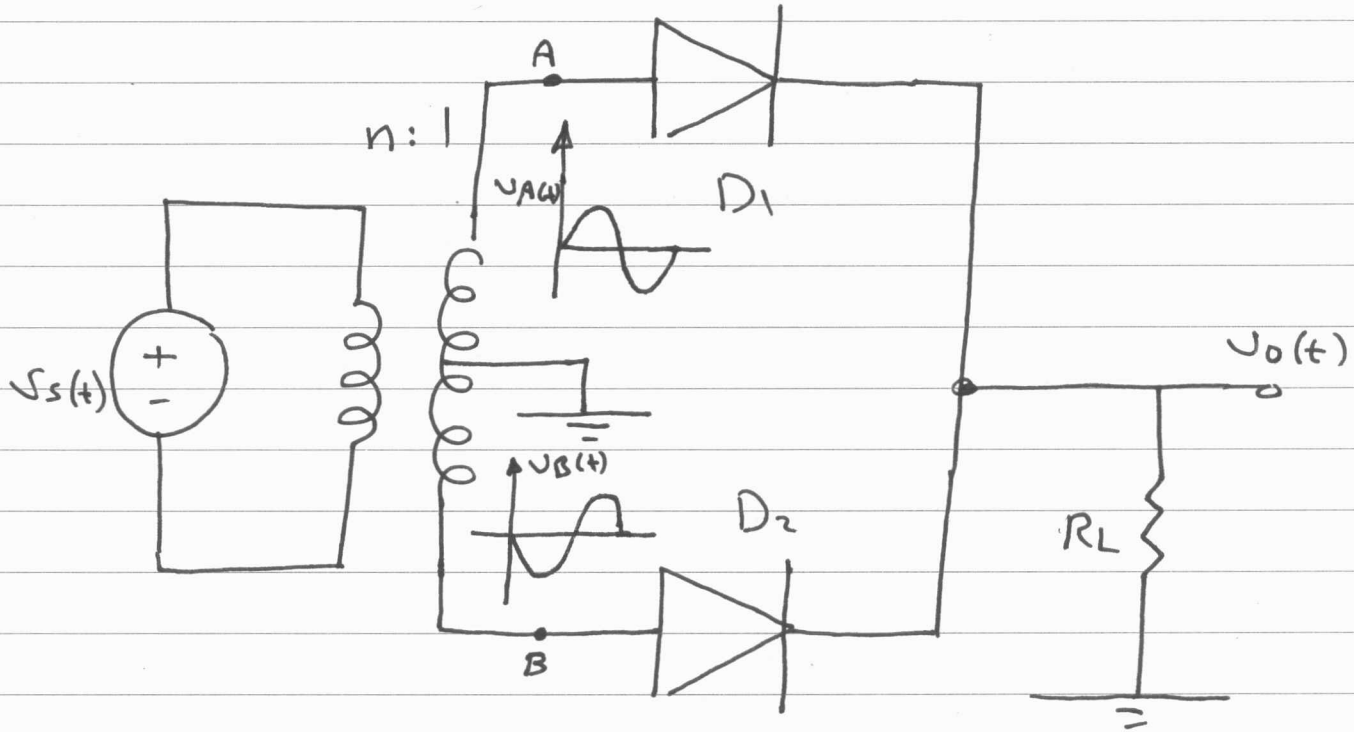
### a) Center-tapped transformer full-wave Rectifier




$V_A(t)$ ,  $V_B(t)$  have the same amplitude

But  $180^\circ$  out of phase

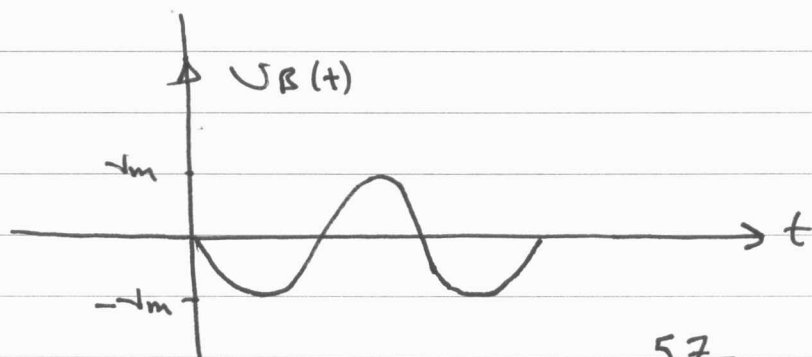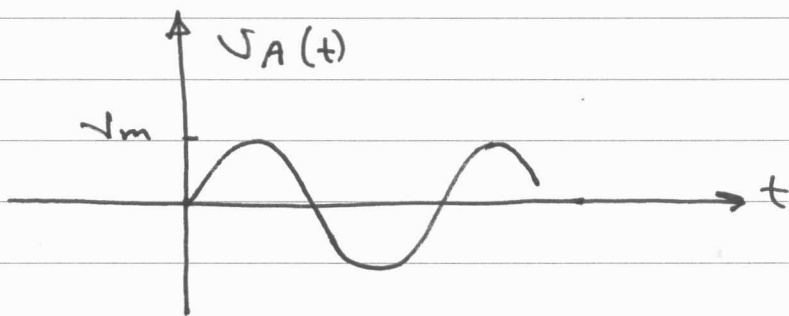




# Simplified Circuit

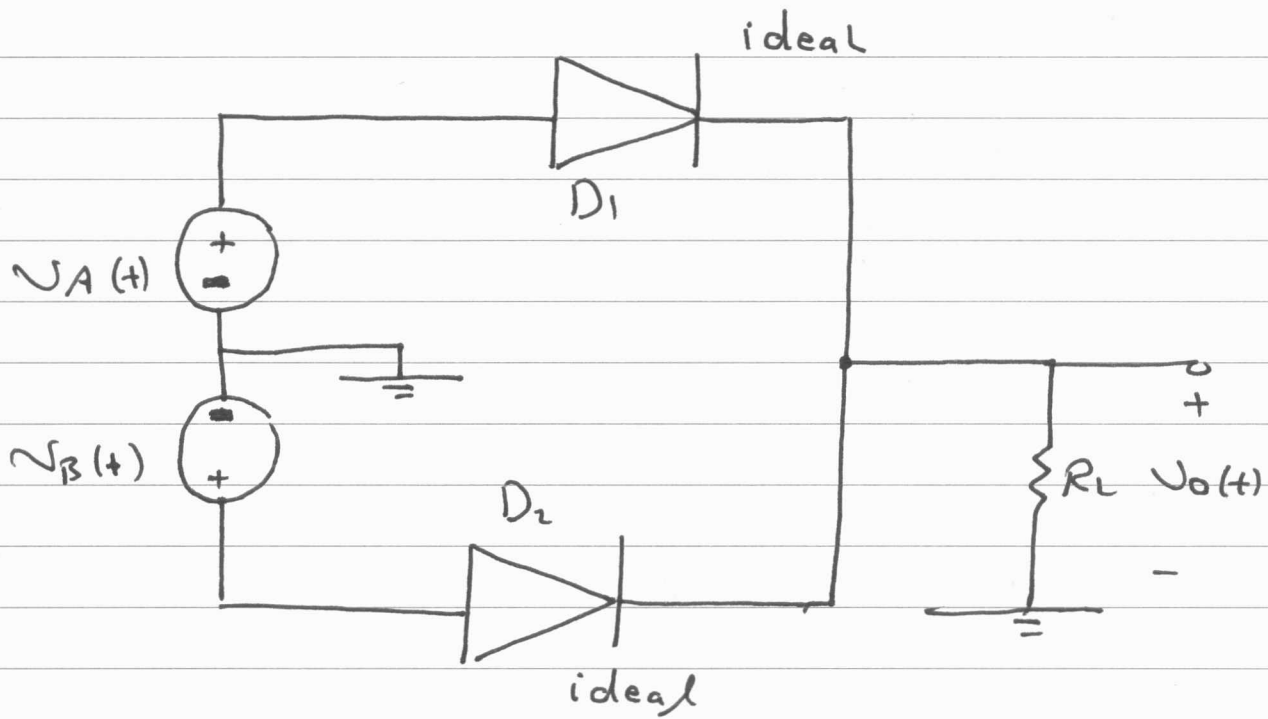


1) When  $v_s(t) > 0$

$v_A(t) > 0$  ,  $D_1$  is ON

$v_B(t) < 0$  ,  $D_2$  is OFF

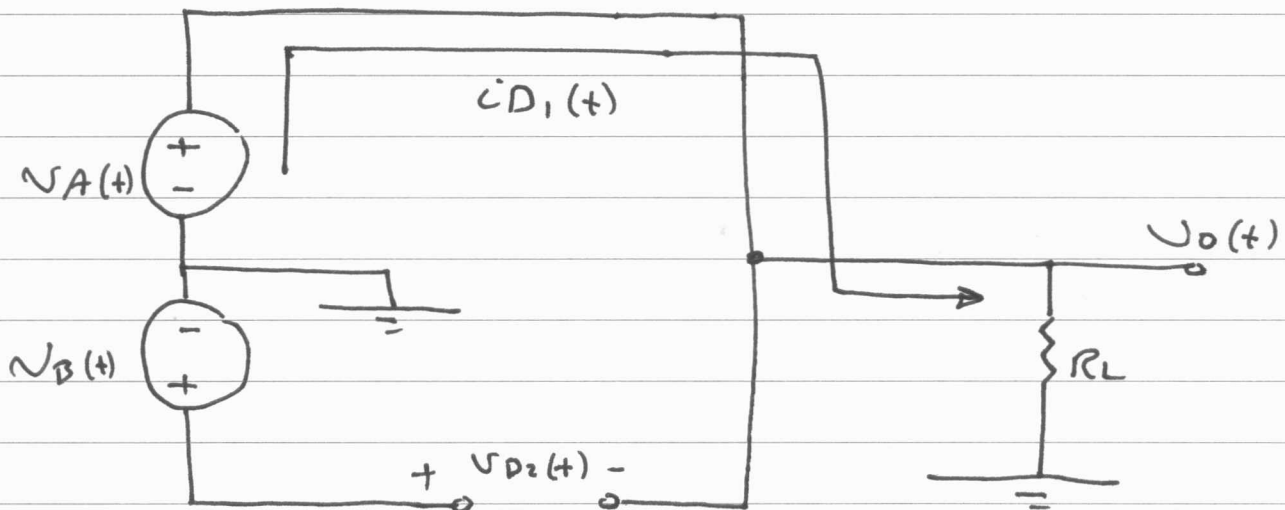

$$v_o(t) = v_A(t)$$

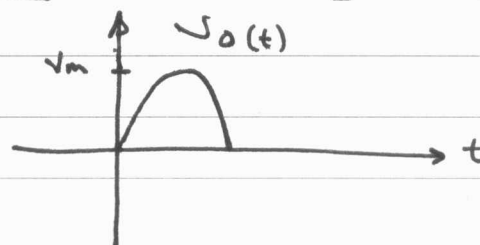

$$V_{D_2}(t) = V_B(t) - V_A(t)$$

$$V_{D_2}(t)_{\max} = -V_m - V_m$$


$$V_{D_2}(t)_{\max} = -2V_m$$

$$\therefore \text{PIV} = -2V_m$$


2) When  $V_S(t) < 0$

$V_A < 0$  ;  $D_1$  is OFF




$V_B > 0$  ;  $D_2$  is ON

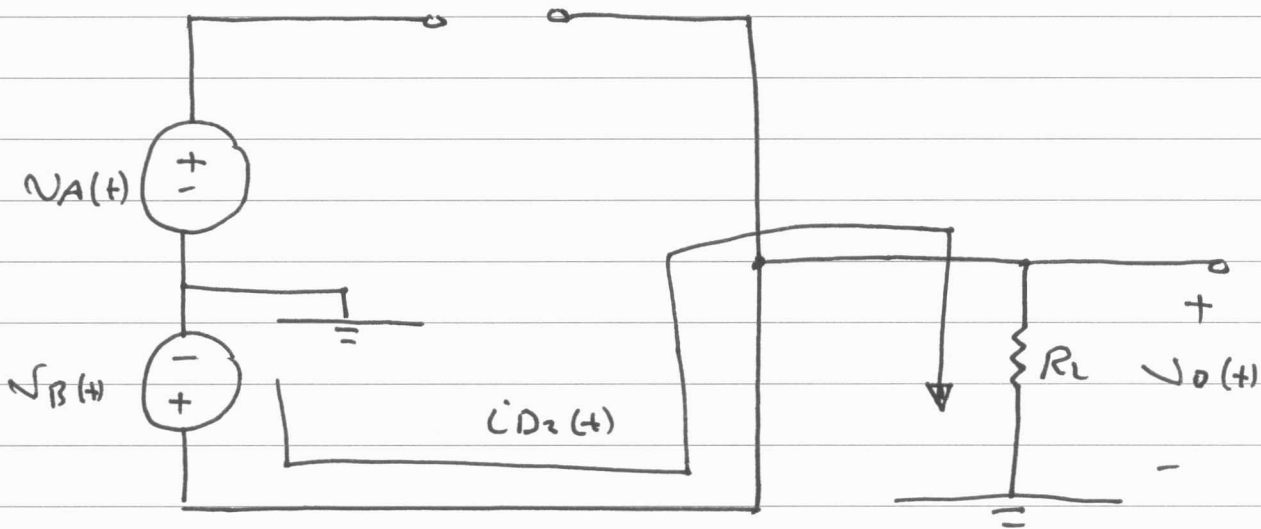

$$\therefore V_O(t) = V_B(t) > 0$$

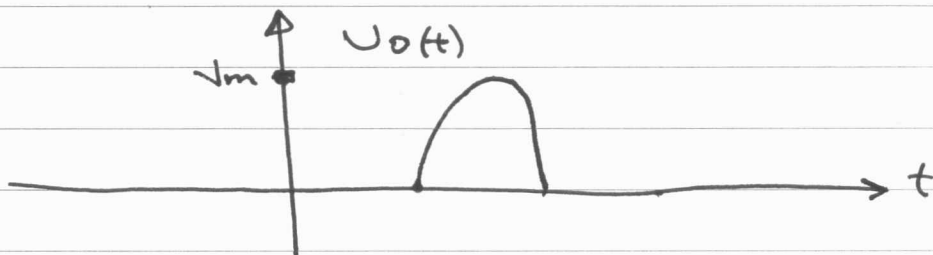

∴ For a Complete Cycle of  $V_s(t)$

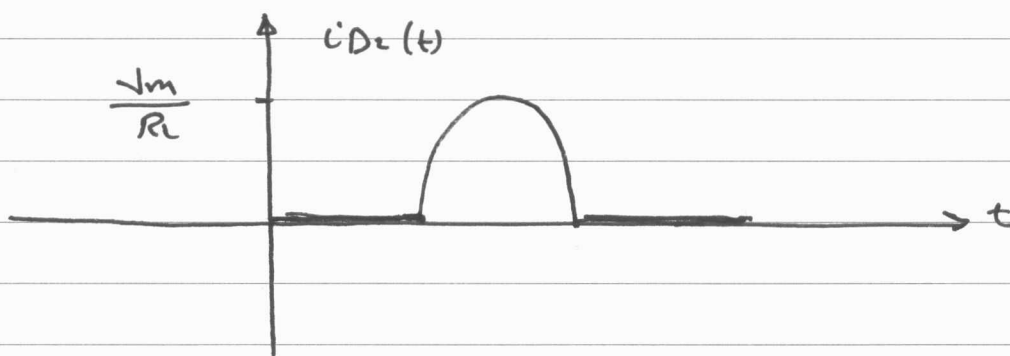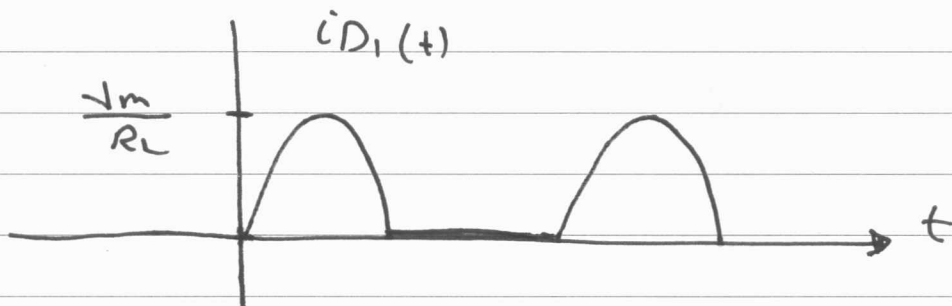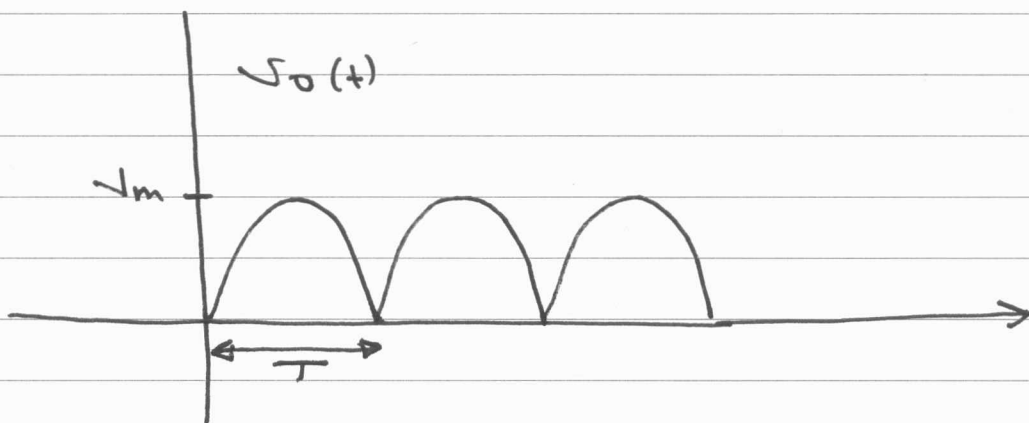

$$V_{o,av} = \frac{2V_m}{\pi}$$

$$PIV = -2V_m$$

$$T = \frac{1}{2}T_0$$

$$f = 2f_0$$