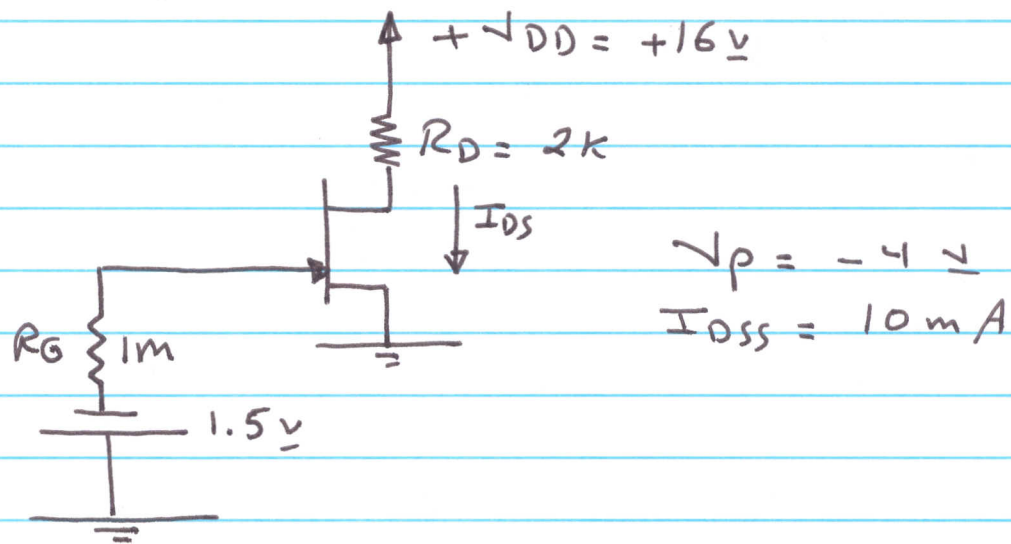


JFET Biasing Circuits

1) Fixed bias circuit



Find Q point

Since $V_{GS} = -1.5\text{V}$, the JFET could be either in the ohmic or pinch off region.

assume that the JFET is in the pinch off region

$$\therefore I_{DS} = I_{DSS} \left(1 - \frac{V_{GS}}{V_p} \right)^2$$

$$V_{GS} = V_G - V_S = -1.5 - 0 = -1.5\text{V}$$

$$\therefore I_{DS} = 3.9\text{mA}$$

$$V_{DD} = R_D I_{DS} + V_{DS}$$

$$\therefore V_{DS} = 8.2 \text{ V}$$

For the JFET to be in the pinch off region

$$|V_{DS}| > |V_P| - |V_{GS}|$$

$$> |-4| - |-1.5|$$


$$|V_{DS}| > 2.5$$

Since $V_{DS} > 2.5 \text{ V}$, \therefore our assumption is OK


graphical method

$$I_{DS} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$V_{GS} = -1.5\text{V}$$

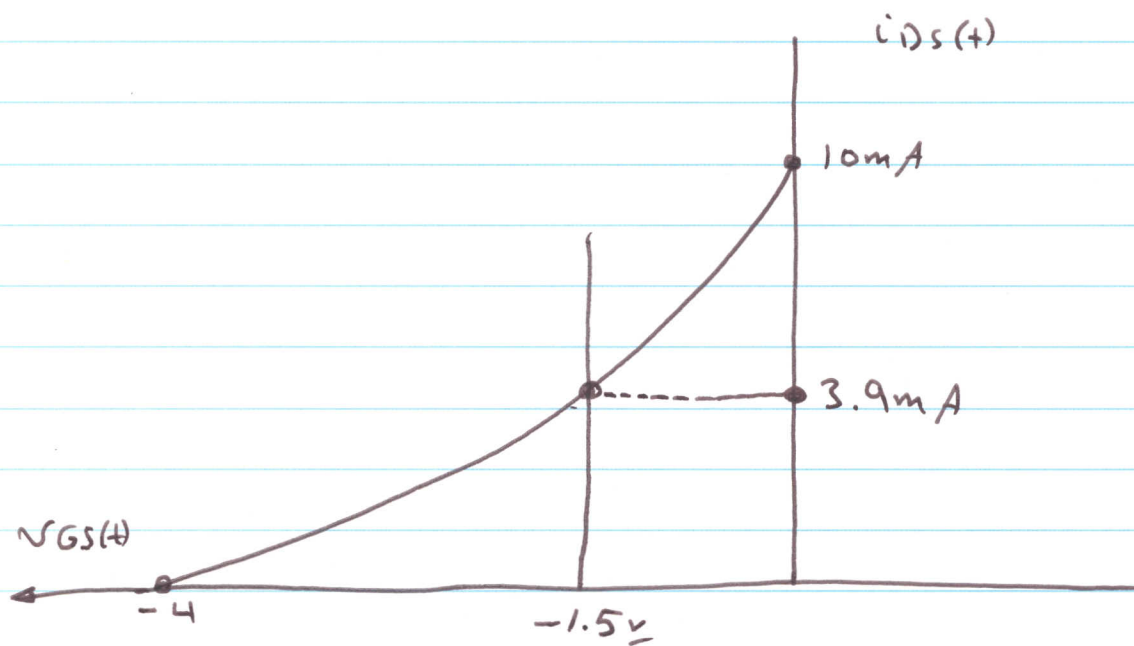

2) Self-bias Circuit

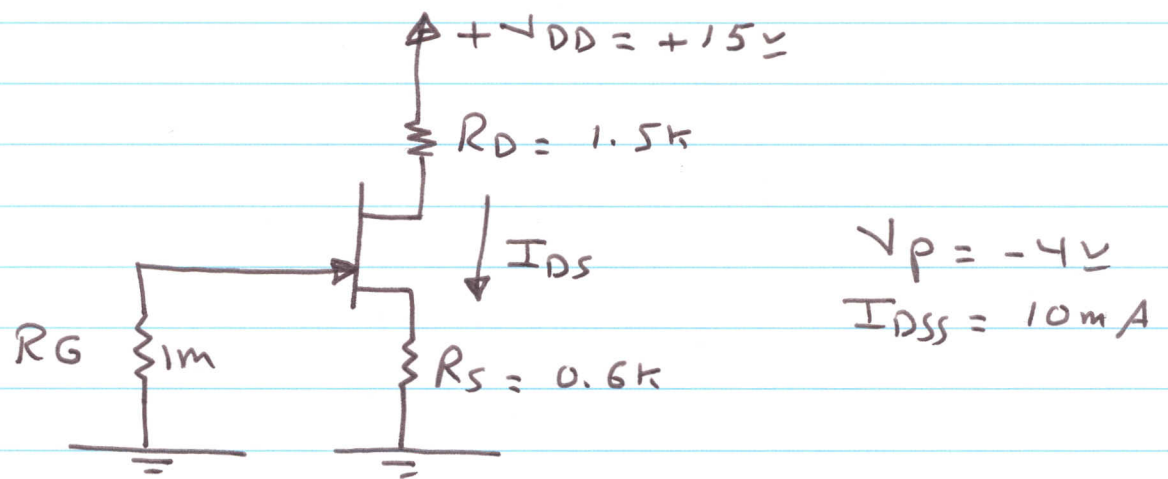

assume that the JFET is in the pinch off region.

$$I_{DS} = I_{DSS} \left(1 - \frac{V_{GS}}{V_p} \right)^2 \quad \text{--- (1)}$$

$$V_{GS} = V_G - V_S$$

$$V_{GS} = 0 - R_S I_{DS} = -R_S I_{DS} \quad \text{--- (2)}$$

Sub (2) into (1)

$$I_{DS} = 10 \times 10^{-3} \left(1 - \frac{-0.6k I_{DS}}{-4} \right)^2$$

$$\therefore I_{DS} = 14.77mA, 3mA$$

Since $I_{DS} = 14.77mA > I_{DSS}$

$$\therefore I_{DS} = 3mA$$

$$\therefore V_{GS} = -1.8V$$

$$V_{DD} = R_D I_{DS} + V_{DS} + R_S I_{DS}$$

$$\therefore V_{DS} = 8.7 \text{ V}$$

For the JFET to be in the pinch off region

$$|V_{DS}| > |V_P| - |V_{GS}|$$

$$> | -4 | - | -1.8 |$$

$$|V_{DS}| > 2.2 \text{ V}$$

\therefore Since $|V_{DS}| > 2.2 \text{ V}$, \therefore the JFET

is in the pinchoff region and our

assumption is OK and

$$I_{DS} = 3.9 \text{ mA}$$

$$V_{DS} = 8.7 \text{ V}$$

and $V_{GS} = -1.8 \text{ V}$


graphical method

$$I_{DS} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$


$$V_{GS} = - (0.6k) I_{DS}$$

When $V_{GS} = 0 \rightarrow I_{DS} = 0 \text{ mA}$

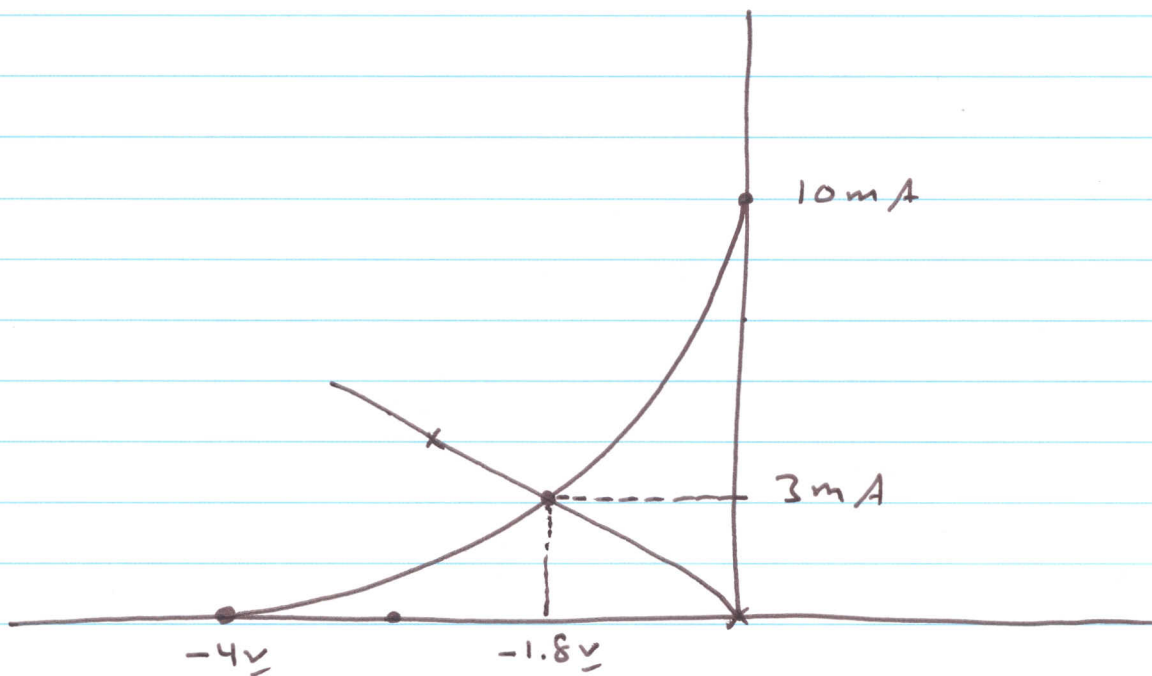When $V_{GS} = -3 \text{ V} \rightarrow I_{DS} = 5 \text{ mA}$



3) Voltage Divider bias Circuit

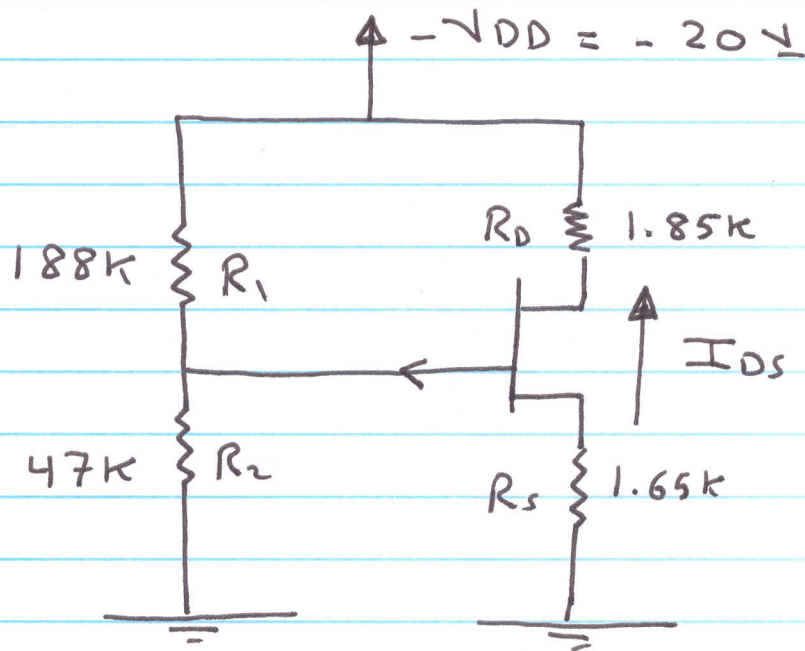

$$I_{DSS} = 18\text{mA}$$

$$V_p = +5\text{V}$$

$$I_{DS} = I_{DSS} \left(1 - \frac{V_{GS}}{V_p} \right)^2 \quad \text{--- (1)}$$

$$V_{GS} = V_G - V_S$$

$$V_G = \frac{47\text{k}}{47\text{k} + 188\text{k}} (-20) = -4\text{V}$$

$$V_S = -R_S I_{DS} = -(1.65\text{k}) I_{DS}$$

$$\therefore V_{GS} = -4 + (1.65\text{k})(I_{DS}) \quad \text{--- (2)}$$

Sub (2) into (1), we obtain

$$I_{DS} = \begin{cases} 4.02\text{mA} \quad \checkmark \\ 7.4\text{mA} \quad \times \end{cases}$$

$$V_{DS} = -5.93\text{V}$$

graphical method

$$I_{DS} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$V_{GS} = -4 + (1.65 \text{ k}) I_{DS}$$

When $V_{GS} = -4 \text{ V}$; $\longrightarrow I_{DS} = 0$

When $V_{GS} = 0 \text{ V}$; $\longrightarrow I_{DS} = 2.42 \text{ mA}$

