
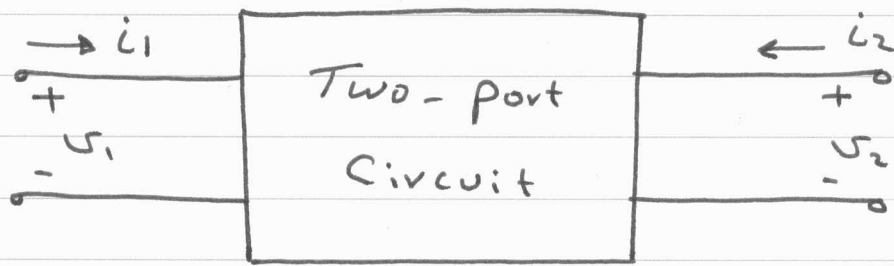


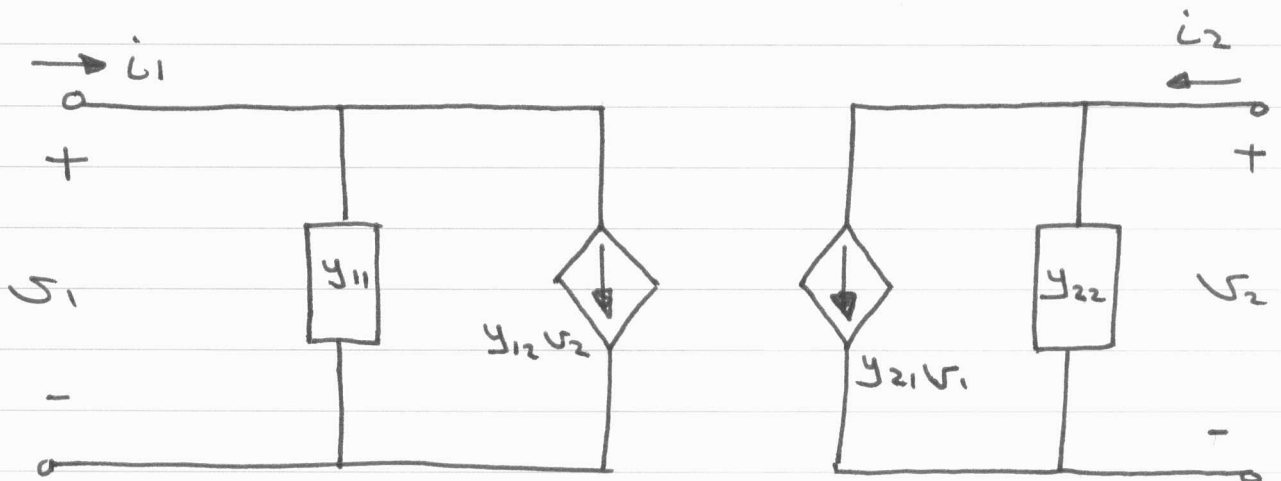
Ac Small Signal Equivalent Circuit For FET



$$i_1 = y_{11} v_1 + y_{12} v_2$$

$$i_2 = y_{21} v_1 + y_{22} v_2$$



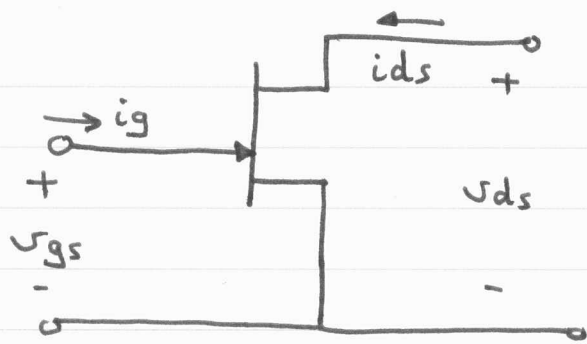

$$i_g = y_{11} v_{gs} + y_{12} v_{ds}$$

$$i_{ds} = y_{21} v_{gs} + y_{22} v_{ds}$$

$$y_{11} = \left. \frac{i_g}{v_{gs}} \right|_{v_{ds}=0} = \left. \frac{\Delta i_G(t)}{\Delta v_{GS}(t)} \right|_{v_{DS}(t) = V_{DSQ}}$$

$$i_G(t) = 0$$

$$\therefore y_{11} = 0 \quad (\text{open circuit})$$

$$y_{12} = \left. \frac{i_g}{v_{ds}} \right|_{v_{gs}=0} = \left. \frac{\Delta i_G(t)}{\Delta v_{DS}(t)} \right|_{v_{GS}(t) = V_{GSQ}}$$

$$\text{But } i_G(t) = 0$$

$$\therefore y_{12} = 0$$

$$\therefore y_{12} v_{gs} = 0 \quad (\text{open circuit})$$

$$y_{22} = \left. \frac{i_{ds}}{v_{ds}} \right|_{v_{gs}=0} = \left. \frac{\Delta i_{DS}(t)}{\Delta v_{DS}(t)} \right|_{v_{GS}(t) = V_{GSQ}}$$

$$\frac{1}{y_{22}} = r_{ds} = \frac{V_A}{I_{DSSQ}}$$

$$y_{21} = \left. \frac{i_{ds}}{v_{gs}} \right|_{v_{ds}=0} = \left. \frac{\Delta i_{DS}(t)}{\Delta v_{GS}(t)} \right|_{v_{DS}(t) = V_{DSQ}}$$

$$y_{21} = \left. \frac{d i_{DS}(t)}{d v_{GS}(t)} \right|_Q$$

$y_{21} = g_m$; Forward Transconductance

1) For JFET and DMOSFET

$$i_{DS}(t) = I_{DSS} \left(1 - \frac{v_{GS}(t)}{V_P} \right)^2$$

$$g_m = \left. \frac{-2 I_{DSS}}{V_P} \left(1 - \frac{v_{GS}(t)}{V_P} \right) \right|_Q$$




$$g_m = \frac{-2 I_{DSS}}{V_P} \left(1 - \frac{v_{GS}}{V_P} \right)$$

2) For EMOSFET

$$i_{DS}(t) = K_n (V_{GS}(t) - V_T)^2$$


$$g_m = 2 K_n (V_{GS} - V_T)$$
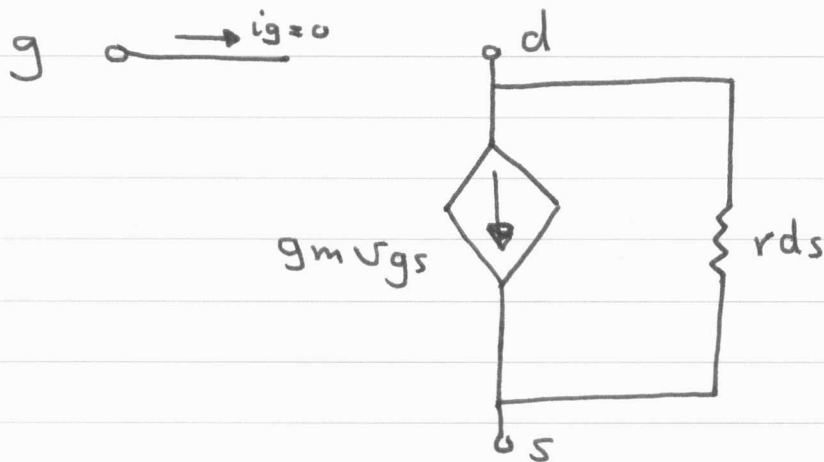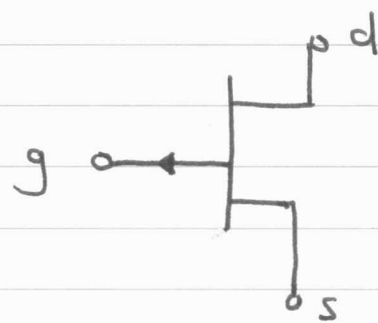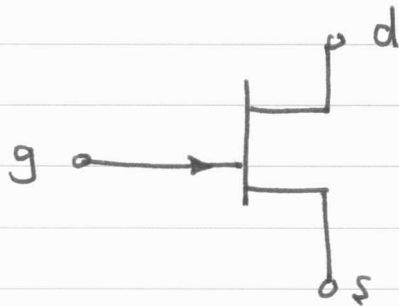
$$g_m = 2 \sqrt{K_n I_{OS}} \quad \text{proof !!}$$






ac small signal equivalent circuit of JFET

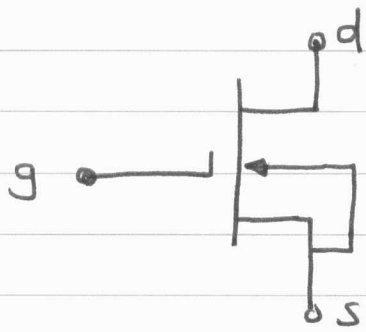Ac Small Signal Equivalent Circuit For MOSFET




or

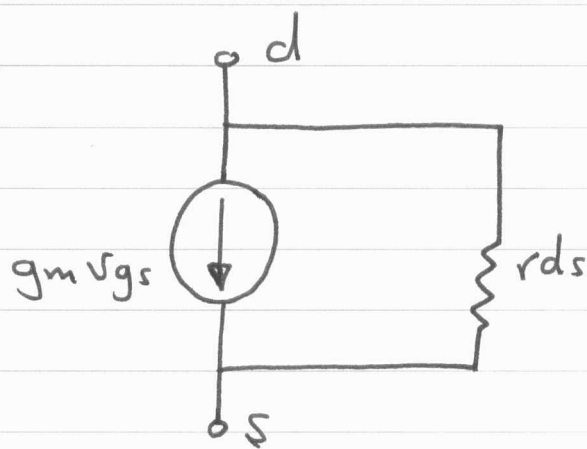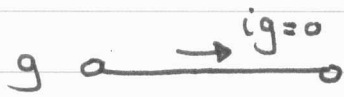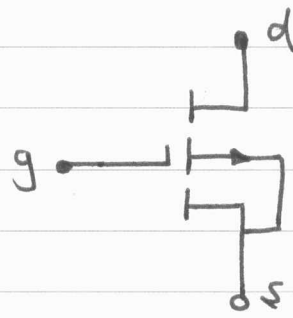

FET Ac Small Signal Amplifiers

1) Common Source Amplifier

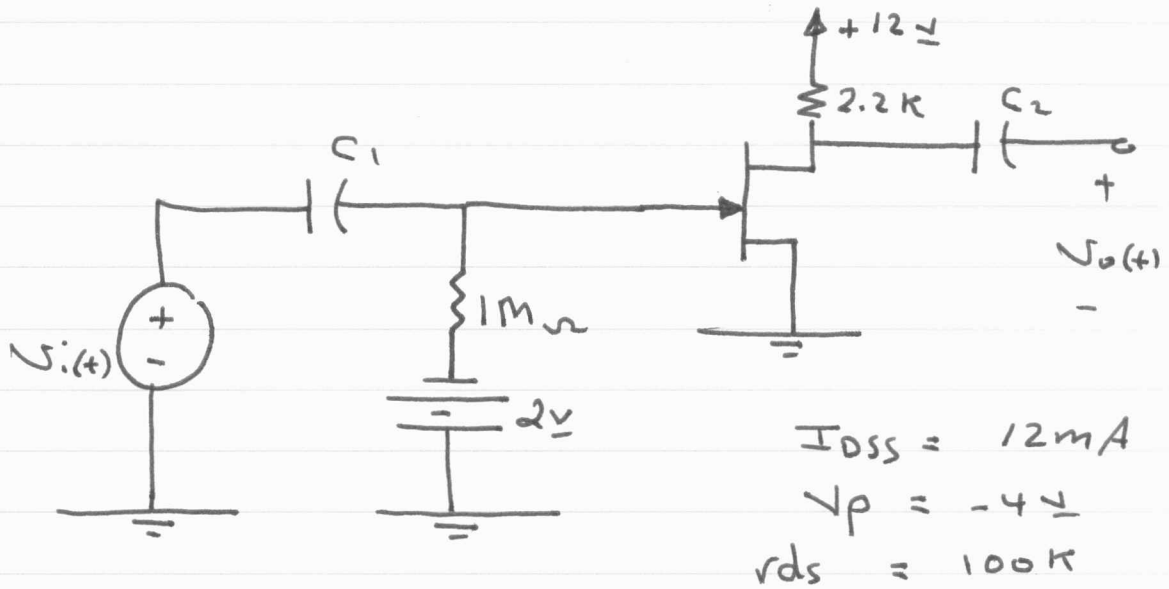


$$g_m = \frac{-2I_{DSS}}{V_p} \left(1 - \frac{V_{GS}}{V_p} \right)$$


$$V_{GS} = -2\text{V}$$

$$\therefore g_m = 3\text{mS}$$

ac small signal Equivalent Circuit

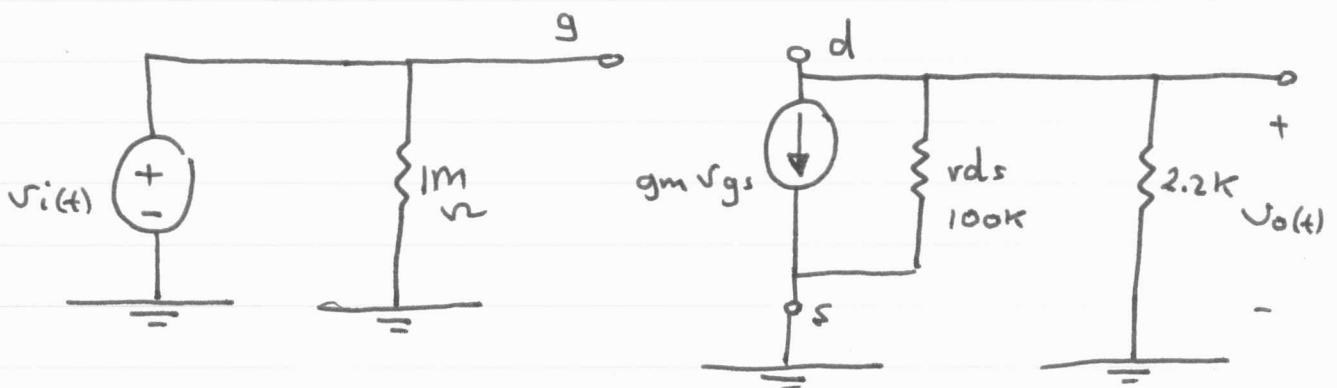

Ac Small Signal Equivalent Circuit

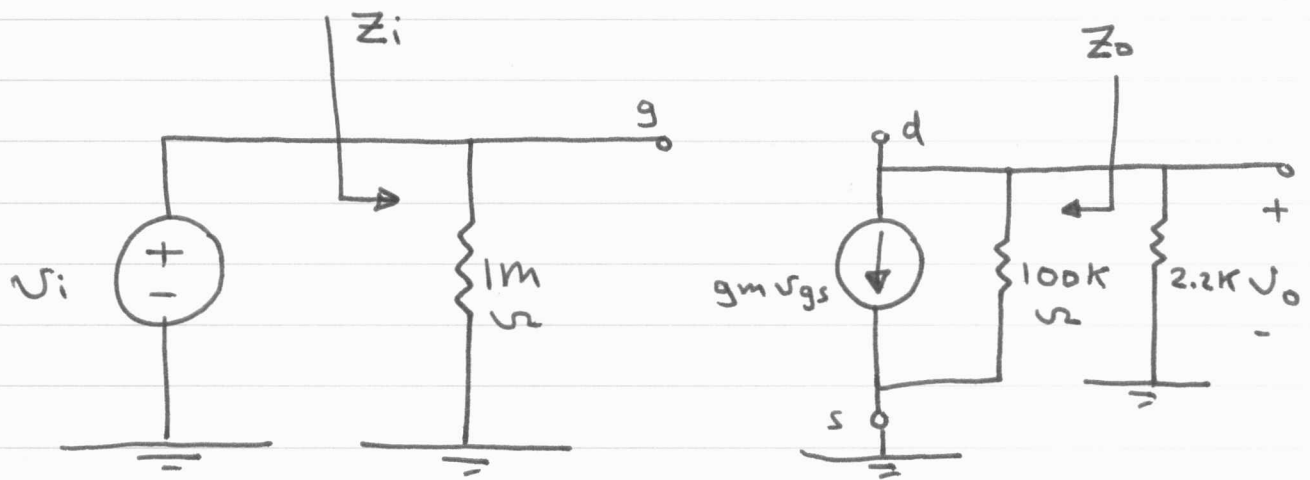

$$V_o = -g_m V_{gs} (100k \parallel 2.2k)$$

$$V_{gs} = V_g - V_s$$

$$V_g = V_i \quad ; \quad V_s = 0$$


$$\therefore A_v = \frac{V_o}{V_i} = -g_m (2.2k \parallel 100k)$$

$$A_v = -6.6$$

$$Z_i = 1M\Omega$$


$$Z_o = r_{ds} = 100k$$

Example

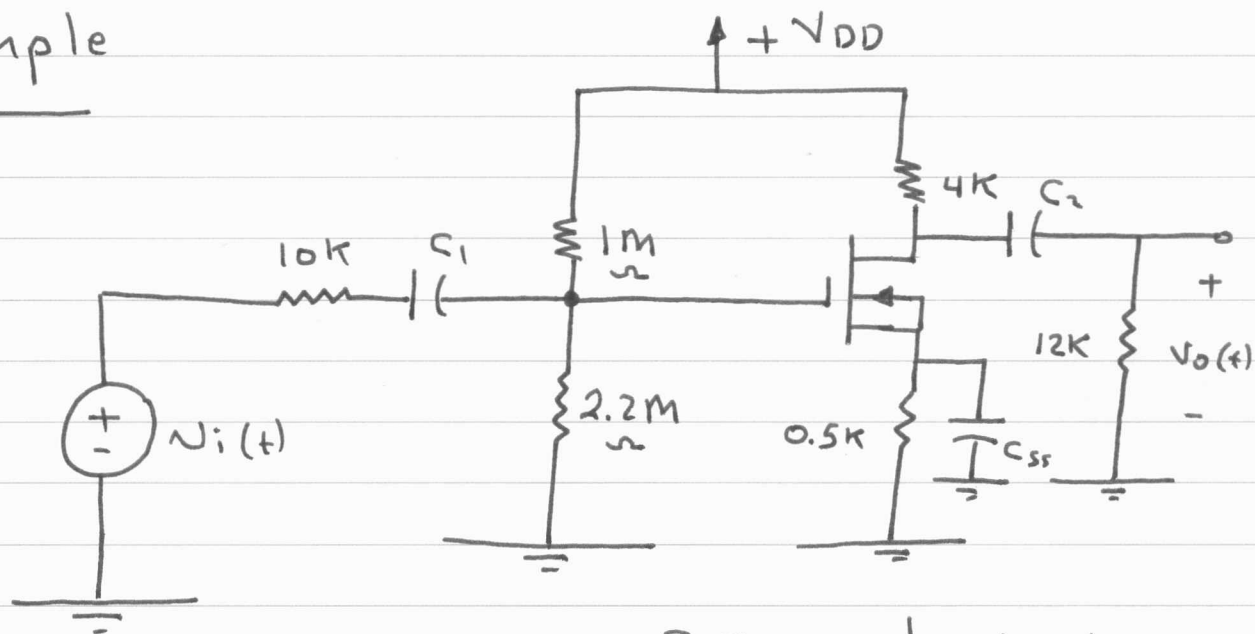

$$g_m = 4 \text{ mS} ; r_{ds} = 100 \text{ k}\Omega$$

ac small signal equivalent CKT :

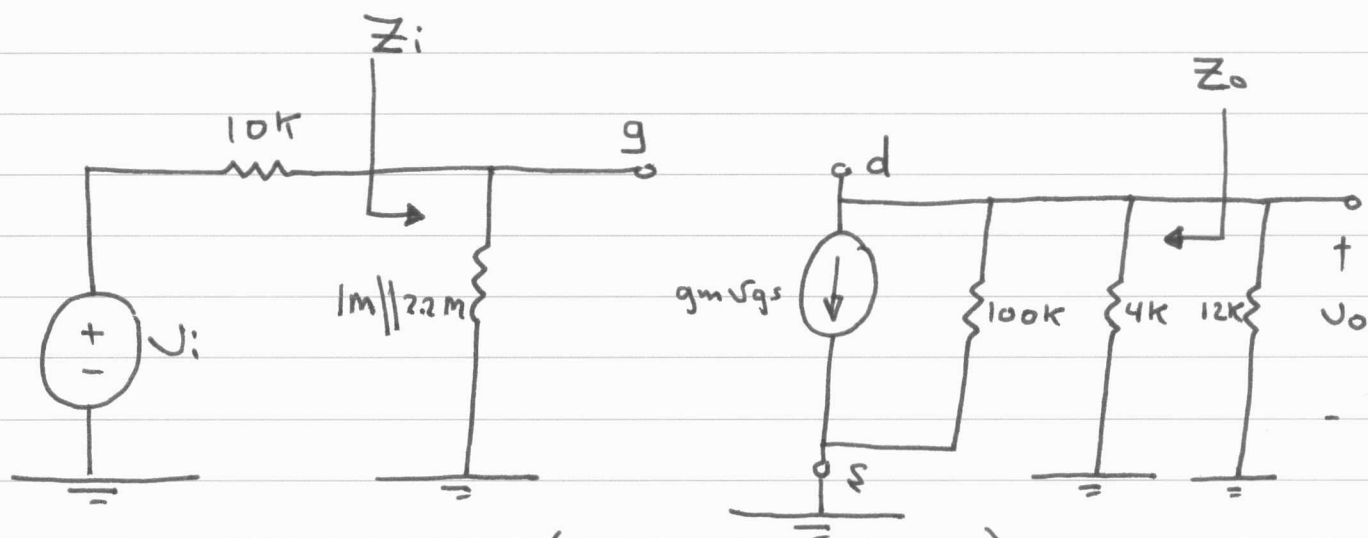

$$V_o = -g_m V_{gs} (100k \parallel 4k \parallel 12k)$$


$$V_{gs} = V_g - V_s$$

$$V_g = \frac{1M \parallel 2.2M}{1M \parallel 2.2M + 10k} V_i ; V_s = 0$$


$$\therefore A_v = \frac{V_o}{V_i} = -11.48$$

$$Z_i = 1M \parallel 2.2M ; Z_o = 100k \parallel 4k$$

Example

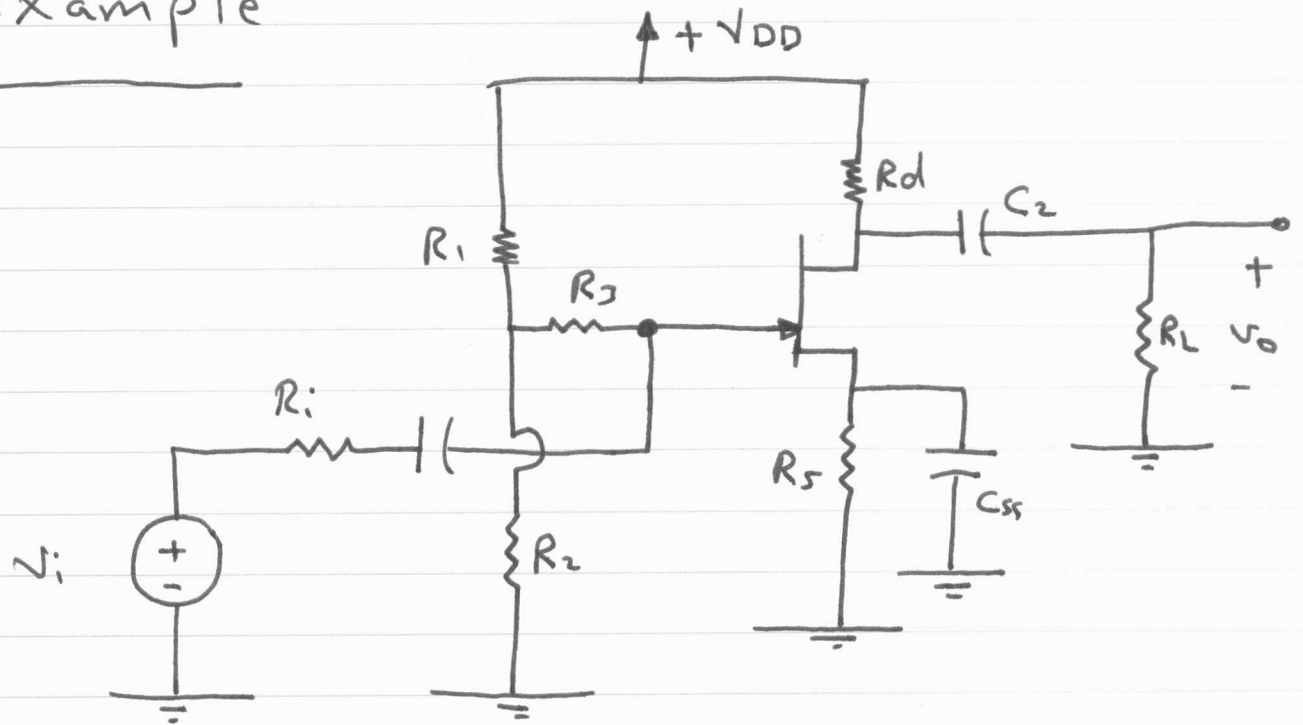

ac small signal equivalent ckt :

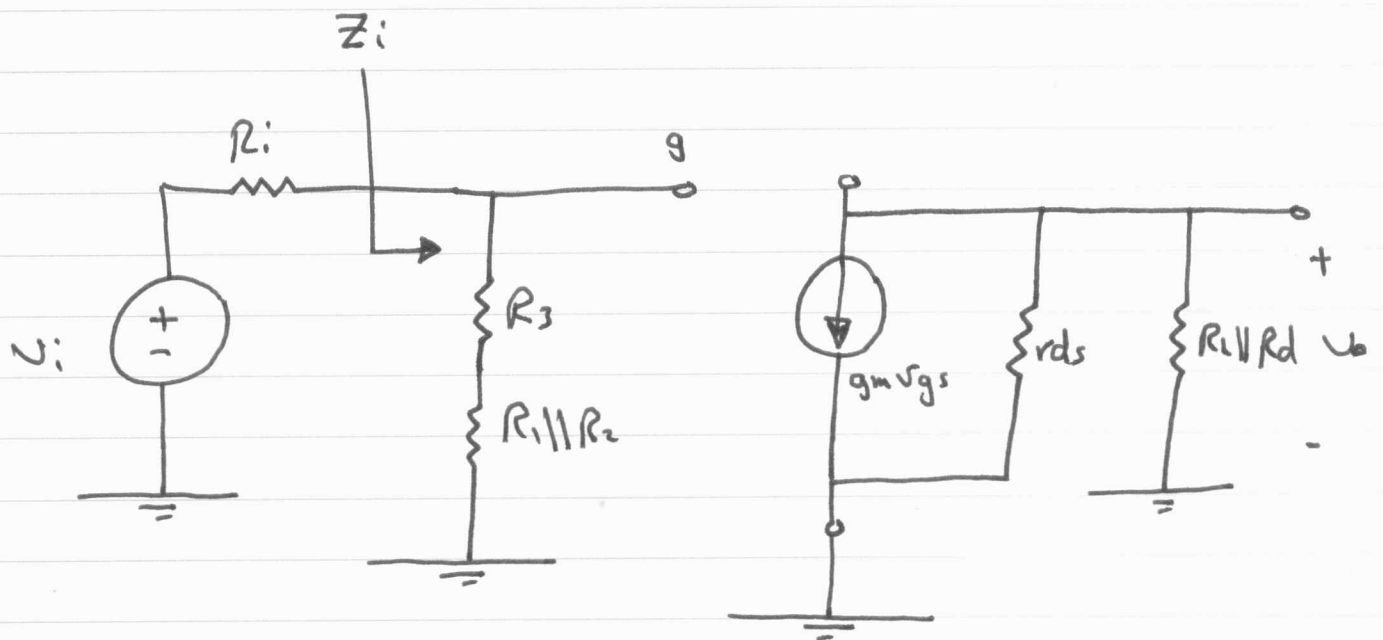

$$Z_i = R_3 + R_1 \parallel R_2$$