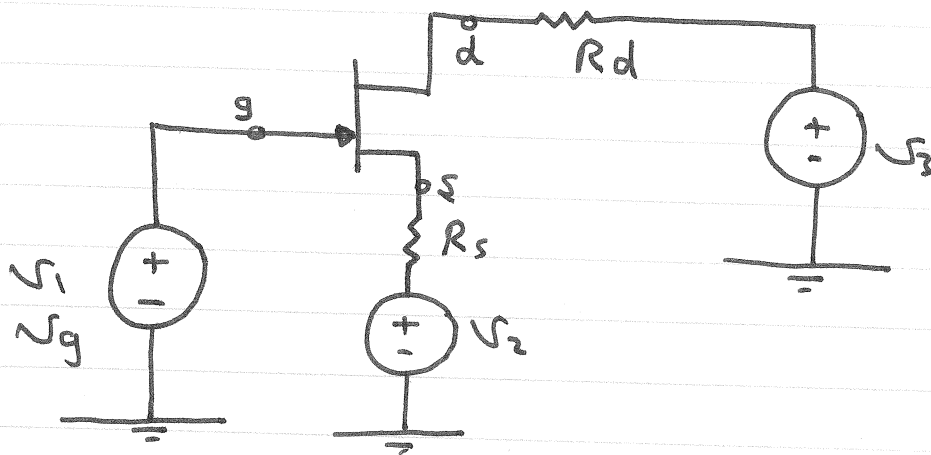



# Impedance Reflection


---



ac small signal equivalent CKT :

---

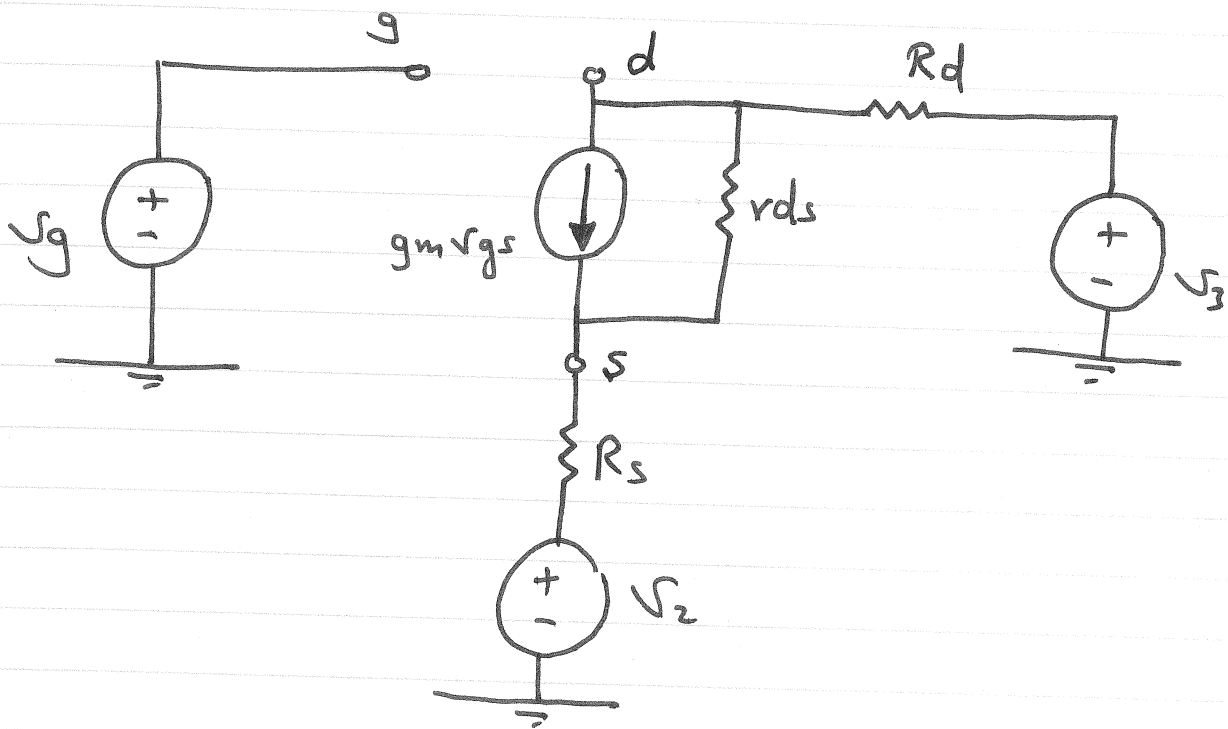

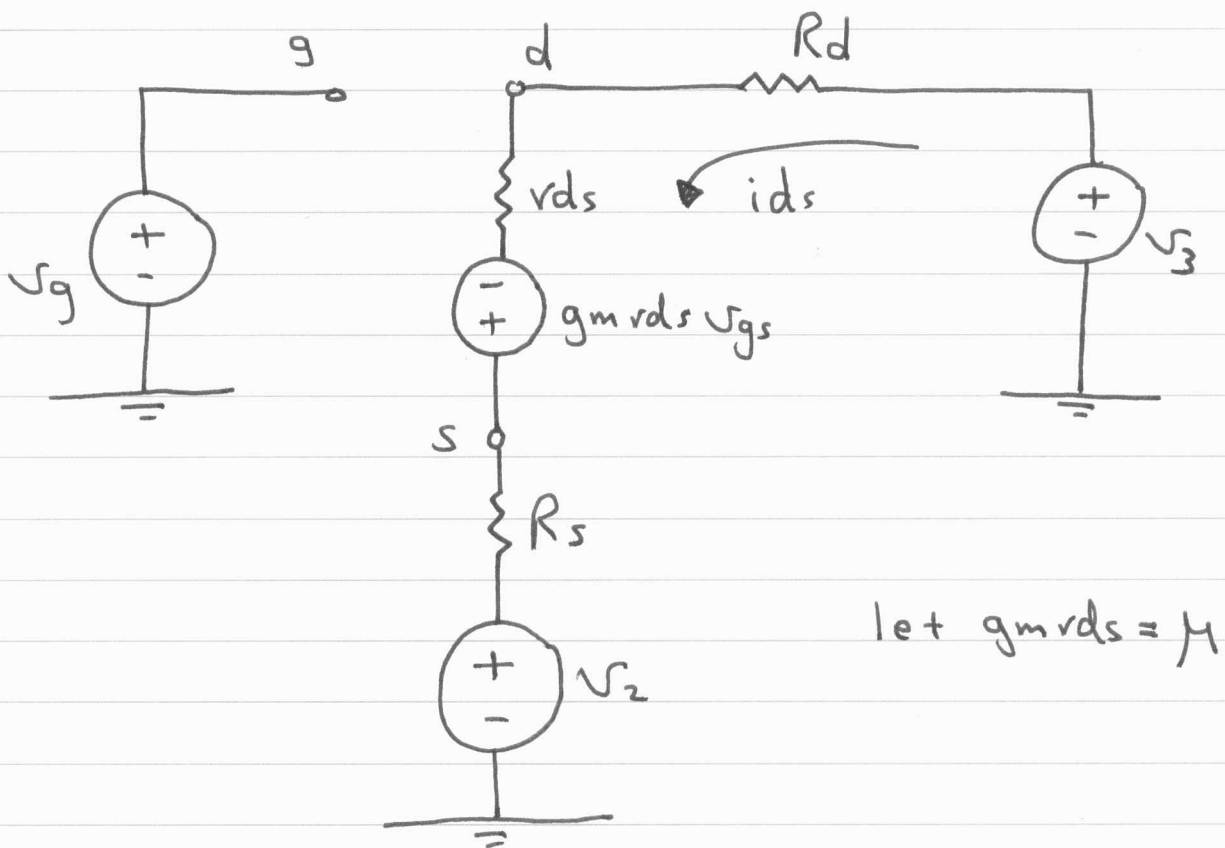

$$i_{ds} = \frac{V_3 + M V_{gs} - V_2}{R_d + R_s + r_{ds}}$$


$$V_{gs} = V_g - V_s$$

$$V_s = R_s i_{ds} + V_2$$

$$\therefore i_{ds} = \frac{M V_g + V_3 - (M+1) V_2}{r_{ds} + R_d + (M+1) R_s}$$


$$i_{ds} = \frac{Mv_g + v_3 - (M+1)v_2}{r_{ds} + R_d + (M+1)R_s}$$

Drain equivalent CKT

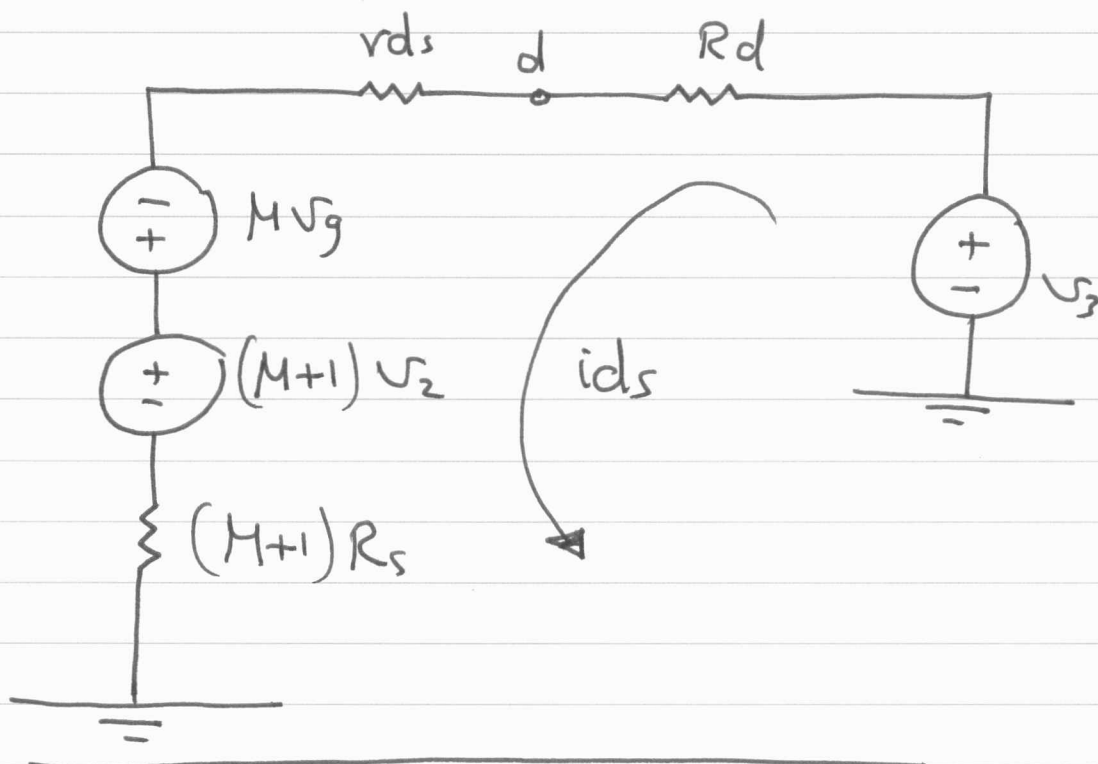


$$i_{ds} = \frac{\frac{M}{M+1} v_g + \frac{v_3}{M+1} - v_2}{R_s + \frac{R_d + r_{ds}}{M+1}}$$


Source equivalent CKT

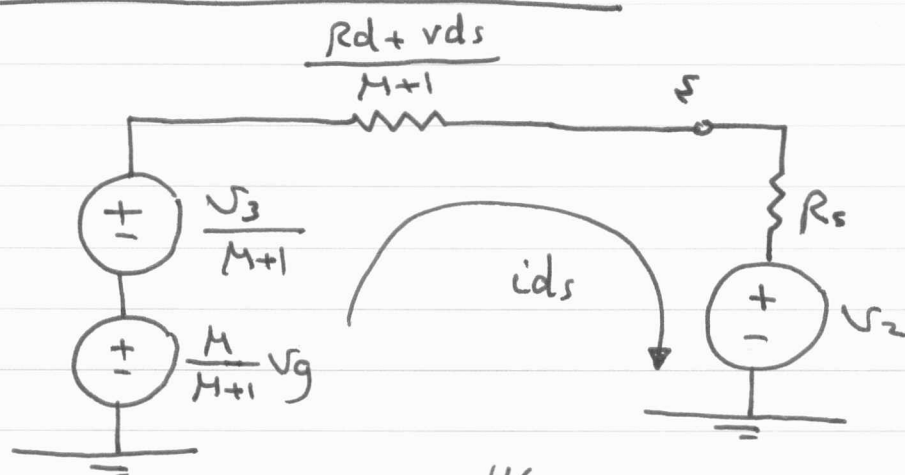


# Phase Splitting Circuit

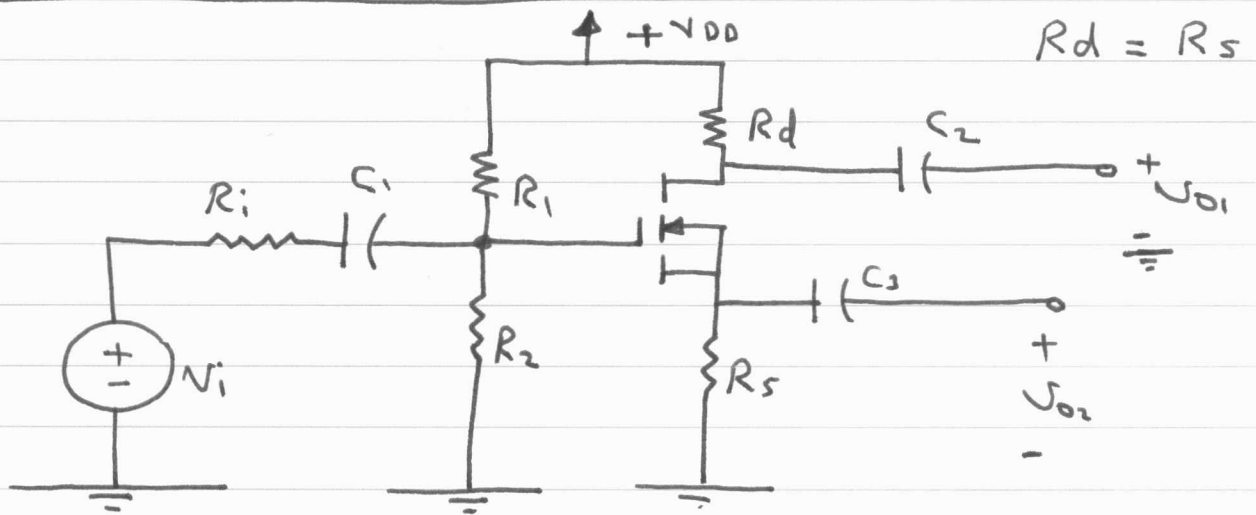

## Ac Small Signal equivalent ckt

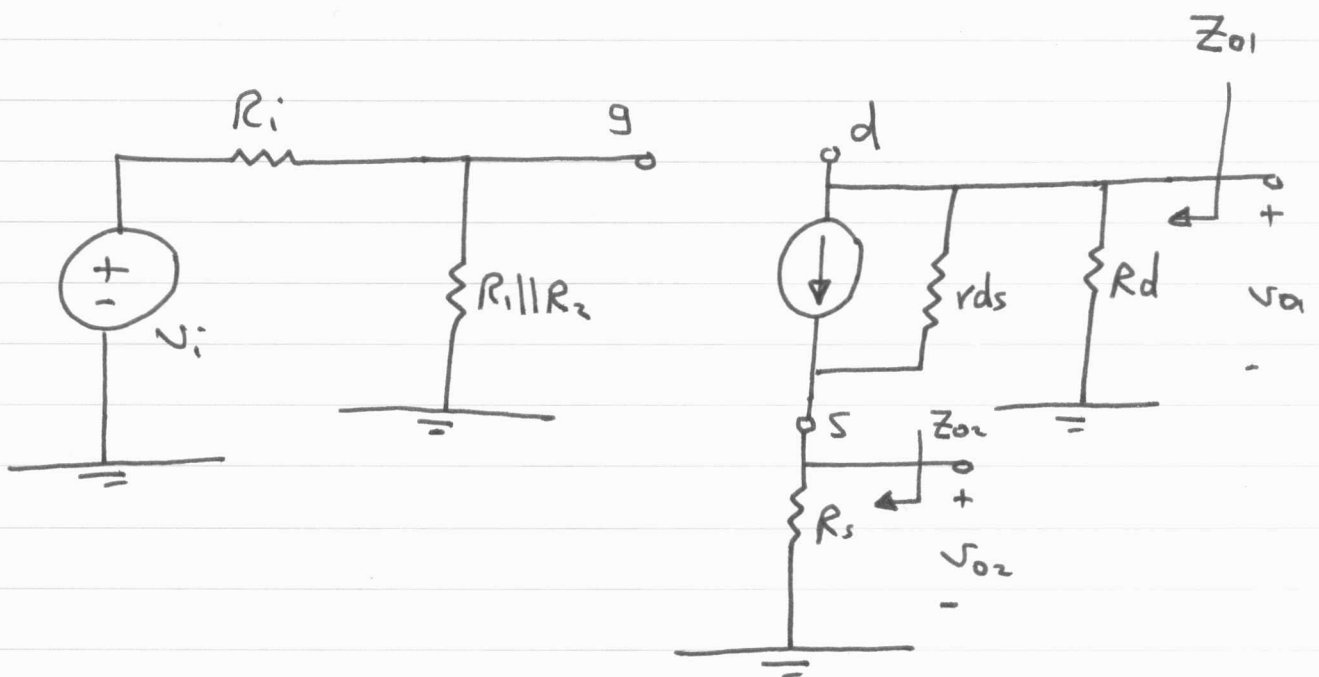

a) To find  $V_{o1}$ , and  $Z_{o1}$

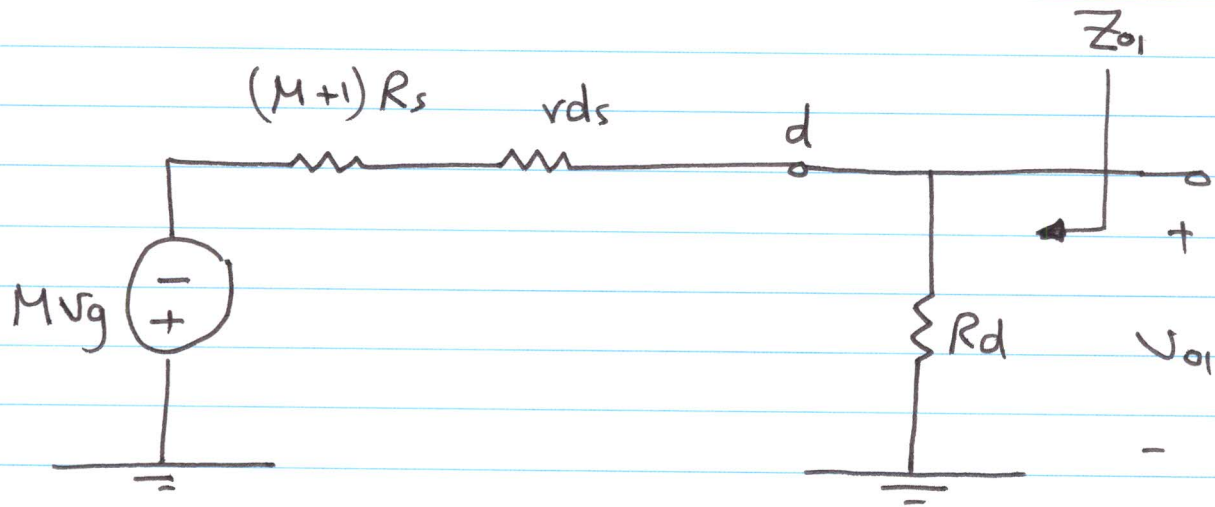

$$V_{o1} = - \frac{R_d M V_g}{R_d + r_{ds} + (M+1)R_s}$$

$$V_g = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_i} V_i$$

$$\therefore V_{o1} = - \frac{(R_1 \parallel R_2)}{R_1 \parallel R_2 + R_i} \cdot \frac{R_d M V_i}{R_d + r_{ds} + (M+1)R_s}$$

$$Z_{o1} = R_d \parallel (r_{ds} + (M+1)R_s)$$

if  $r_{ds} = \infty$

$$\therefore Z_{o1} = R_d$$

b) To find  $V_{o2}$ , and  $Z_{o2}$



$$V_{o2} = \frac{R_s \left( \frac{M}{M+1} \right) V_g}{R_s + \frac{R_d + v_{ds}}{M+1}}$$

$$V_g = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_i} V_i$$

$$V_{o2} = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_i} \frac{R_s \left( \frac{M}{M+1} \right) V_i}{R_s + \frac{R_d + v_{ds}}{M+1}}$$

$$V_{o2} = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_i} \frac{R_s M V_i}{(R_d + v_{ds}) + (M+1)R_s}$$

$$\therefore |V_{o2}| = |V_{o1}|$$

$$\text{if } R_s = R_d$$

$$Z_{o2} = R_s \parallel \frac{R_d + v_{ds}}{M+1}$$

$$Z_{o2} = R_s \parallel \frac{R_d + r_{ds}}{M+1}$$


if  $r_{ds} = \infty$

$$\frac{R_d + r_{ds}}{M+1} = \frac{R_d + r_{ds}}{g_m r_{ds} + 1}$$



$$\lim_{r_{ds} \rightarrow \infty} \frac{R_d + r_{ds}}{g_m r_{ds} + 1} = \frac{1}{g_m}$$

$$\therefore \text{if } r_{ds} = \infty ; Z_{o2} = R_s \parallel \frac{1}{g_m}$$

# Common Gate Amplifier

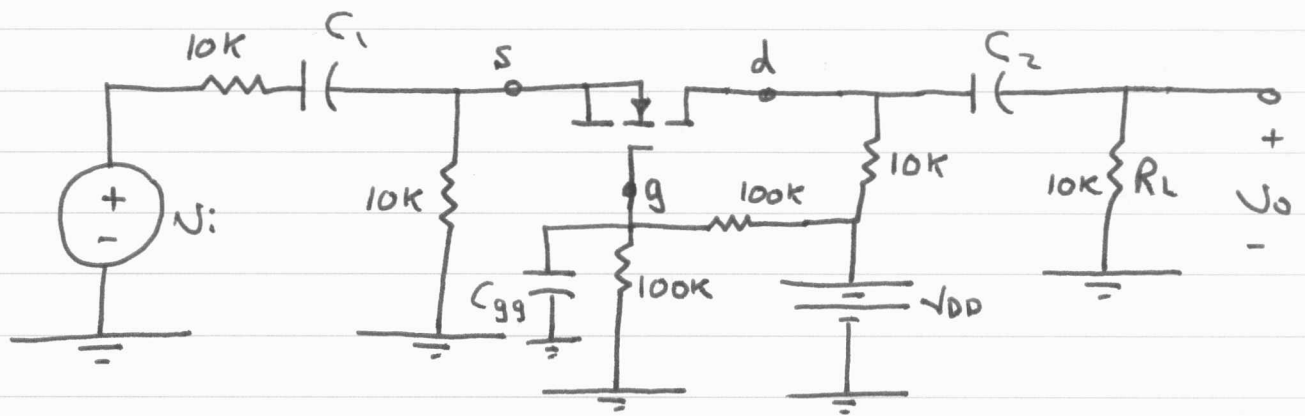


## Ac Small Signal Equivalent Circuit

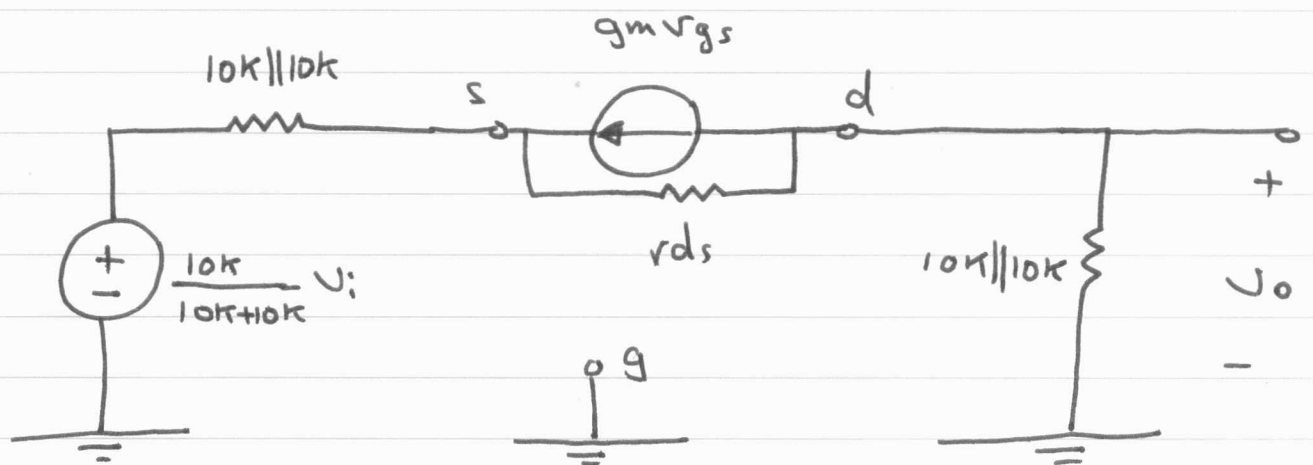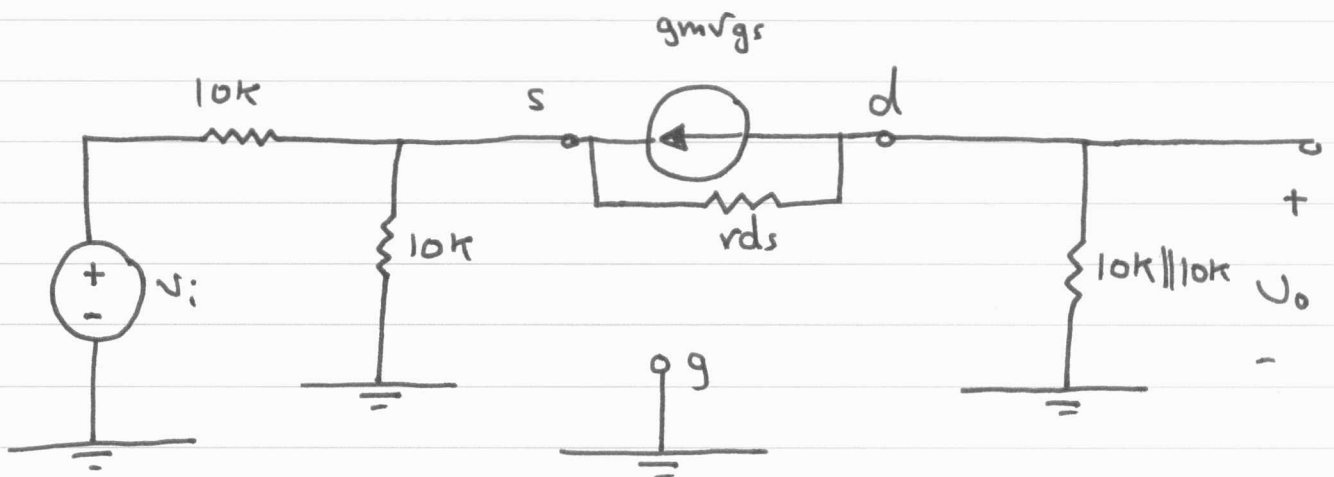




To Find  $V_o$  , and  $Z_o$

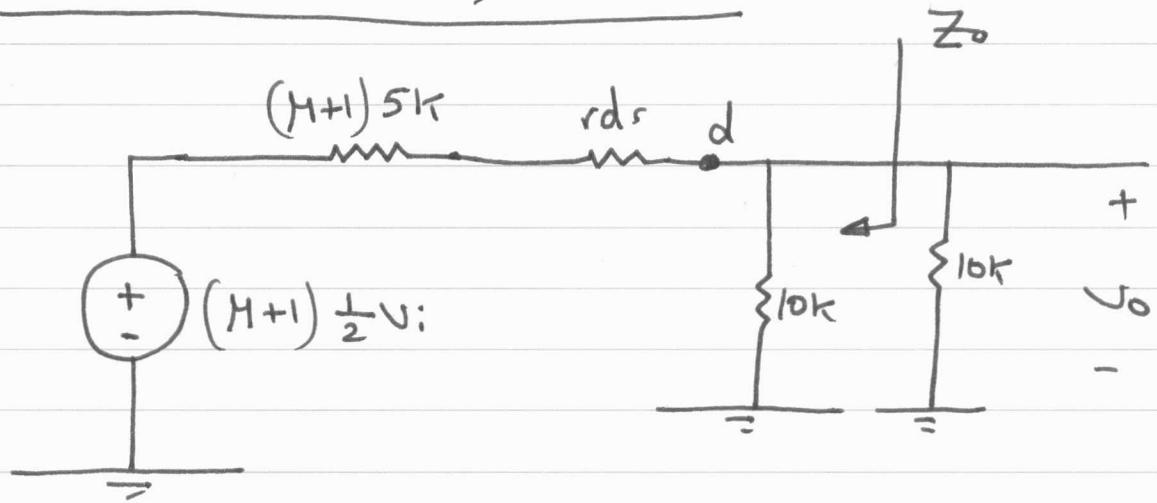

$$V_o = \frac{(10k \parallel 10k) (M+1) \frac{1}{2} V_i}{10k \parallel 10k + r_{ds} + (M+1) 5k}$$

$$Z_o = 10k \parallel [r_{ds} + (M+1) 5k]$$

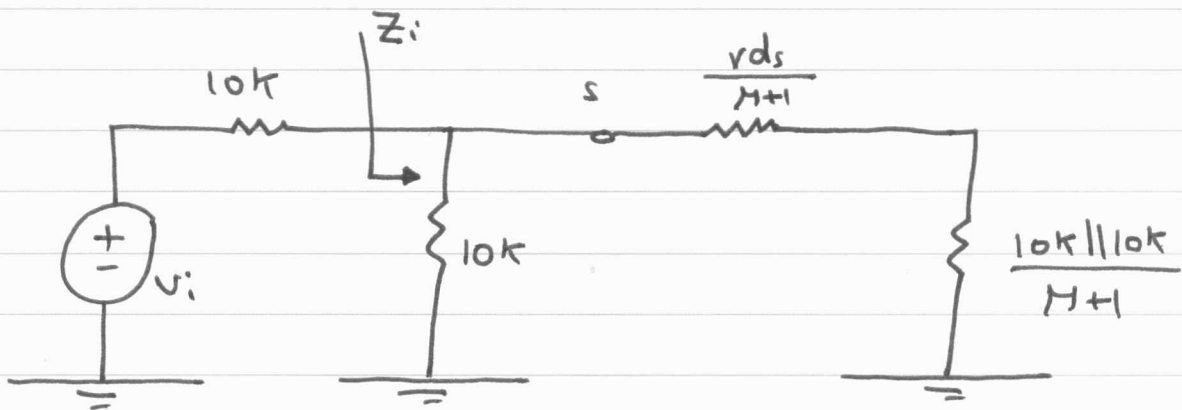To find  $Z_i \rightarrow$  Source equivalent ckt



$$Z_i = 10k \parallel \frac{r_{ds} + 10k \parallel 10k}{M+1}$$


# Common Source Amplifier : Design

Design the MOSFET Amplifier shown

to have a gain of 10 and  $Z_i = 1M\Omega$


Assume  $V_{GS} = 3V$ ,  $V_{DS} = 4V$ ,  $I_{DS} = 5mA$

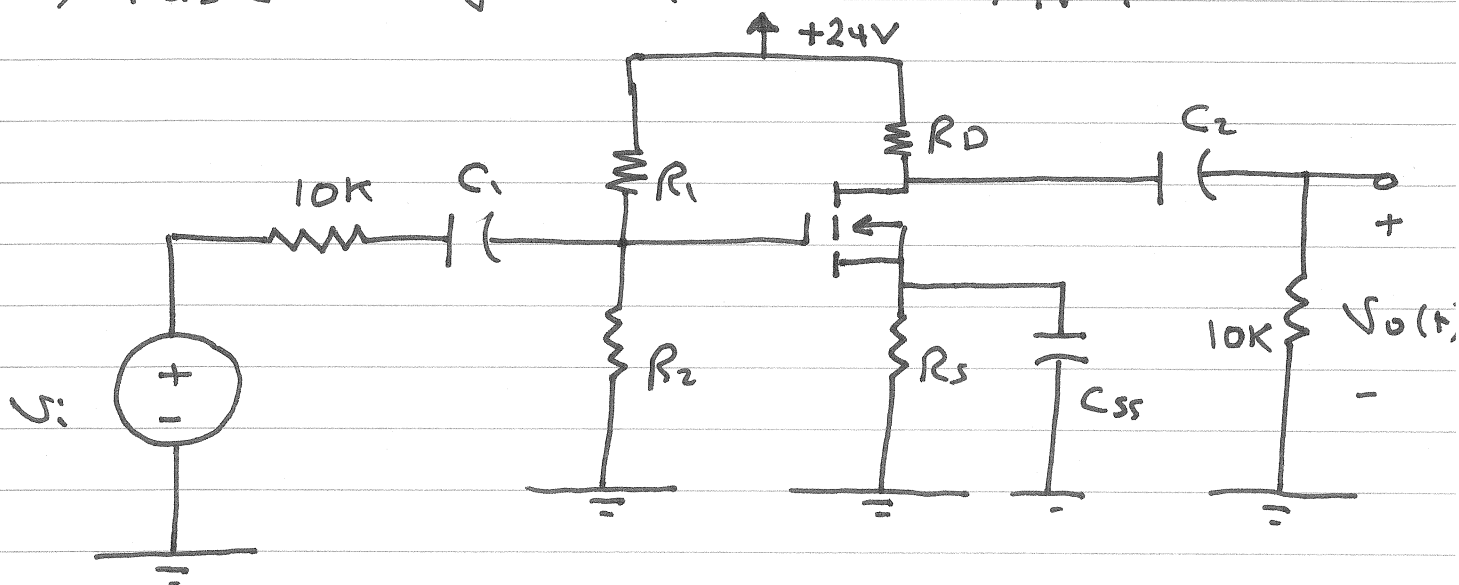,  $r_{ds} = 20K\Omega$  and  $K_n = 2mA/V^2$ .



# Solution

ac small signal equivalent circuit

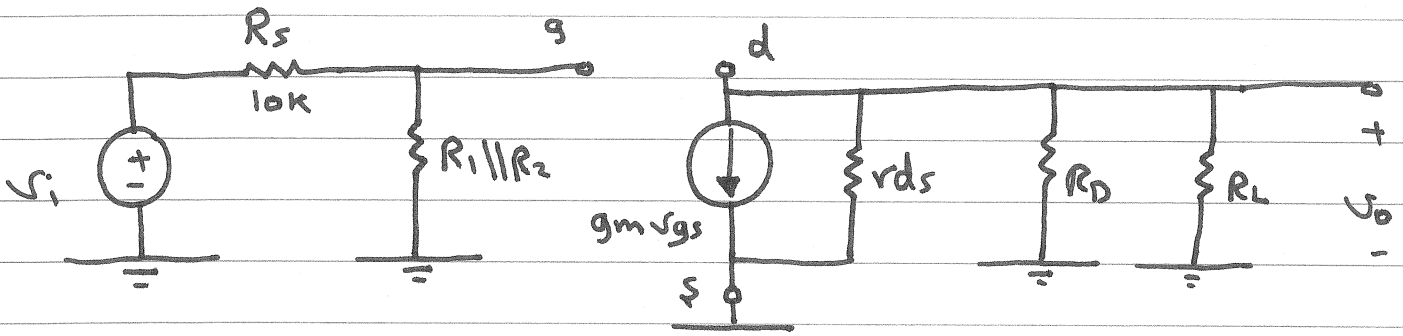

$$v_o = -g_m v_{gs} (r_{ds} \parallel R_D \parallel R_L)$$

$$v_{gs} = v_g - v_s = v_g = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_s} v_i$$

$$v_{gs} = \frac{Z_i}{Z_i + 10k} v_i = \frac{1m}{1m + 10k} v_i \approx v_i$$

$$\therefore |A_v| = g_m (r_{ds} \parallel 10k \parallel R_D)$$

$$|A_v| = g_m (6.67k \parallel R_D)$$

$$g_m = 2\sqrt{K_n I_{D_s}} = 6.23 \text{ mS}$$

$$\therefore \text{For } |A_v| = 10 \rightarrow R_D = 2.1k$$

From DC Analysis

$$V_{DD} = (R_D + R_S) I_{DS} + V_{DS}$$

$$\therefore R_D + R_S = 4 \text{ k}$$

$$\therefore R_S = 1.9 \text{ k}$$

$$\therefore V_S = 9.5 \text{ V}$$

$$V_G = V_{GS} + V_S$$

$$V_G = 3 + 9.5 = 12.5 \text{ V}$$

$$V_G = \frac{R_2}{R_1 + R_2} V_{DD} = 12.5 \text{ V}$$

$$Z_i = \frac{R_1 R_2}{R_1 + R_2} = 1 \text{ M}\Omega$$

Solving for  $R_1$  and  $R_2$

$$R_1 = 1.92 \text{ M}\Omega$$

$$R_2 = 2.1 \text{ M}\Omega$$