

ENEE 231 Ch 5 Homework Solutions

$$5.30 \quad I_{DS} = 1 \text{ mA}, \quad V_D = 0 \text{ V}$$

$$I_{DS} = \frac{V_{DD} - V_D}{R_D}$$

$$\therefore R_D = \frac{V_{DD} - V_D}{I_{DS}} = \frac{2.5 - 0}{1 \text{ mA}} = 2.5 \text{ k}\Omega$$

$$I_{DS} = \frac{1}{2} \mu_0 C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$

$$1 \text{ mA} = \frac{1}{2} (60) \left(\frac{100}{3} \right) (V_{GS} - 1)^2$$

$$\therefore V_{GS} = 2 \text{ V}$$

$$V_{GS} = V_G - V_S$$

$$\therefore V_S = -2 \text{ V}$$

$$I_{DS} = \frac{V_S - V_{SS}}{R_S} = \frac{-2 + 2.5}{1 \text{ mA}} = 0.5 \text{ k}\Omega$$

5.33

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \frac{W_1}{L_1} \left(\sqrt{V_{GS1}} - \sqrt{V_T} \right)^2$$

$$\sqrt{V_{GS1}} = \sqrt{V_{DS1}} = 1.5 \text{ V}$$

$$120 \mu\text{A} = \left(\frac{1}{2} \right) \left(250 \frac{\mu\text{A}}{\sqrt{2}} \right) \frac{W_1}{0.25 \mu\text{m}} \left(1.5 - 0.6 \right)^2$$

$$\therefore W_1 = 0.296 \mu\text{m}$$


$$\sqrt{V_{GS2}} = \sqrt{V_{G2}} - \sqrt{V_{S2}} = 3.5 - 1.5 = 2 \text{ V}$$

$$I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W_2}{L_1} \left(\sqrt{V_{GS2}} - \sqrt{V_T} \right)^2$$

$$\therefore W_2 = 0.122 \mu\text{m}$$

$$R = \frac{5 - 3.5}{120 \mu\text{A}} = 12.5 \text{ K}$$

5.54

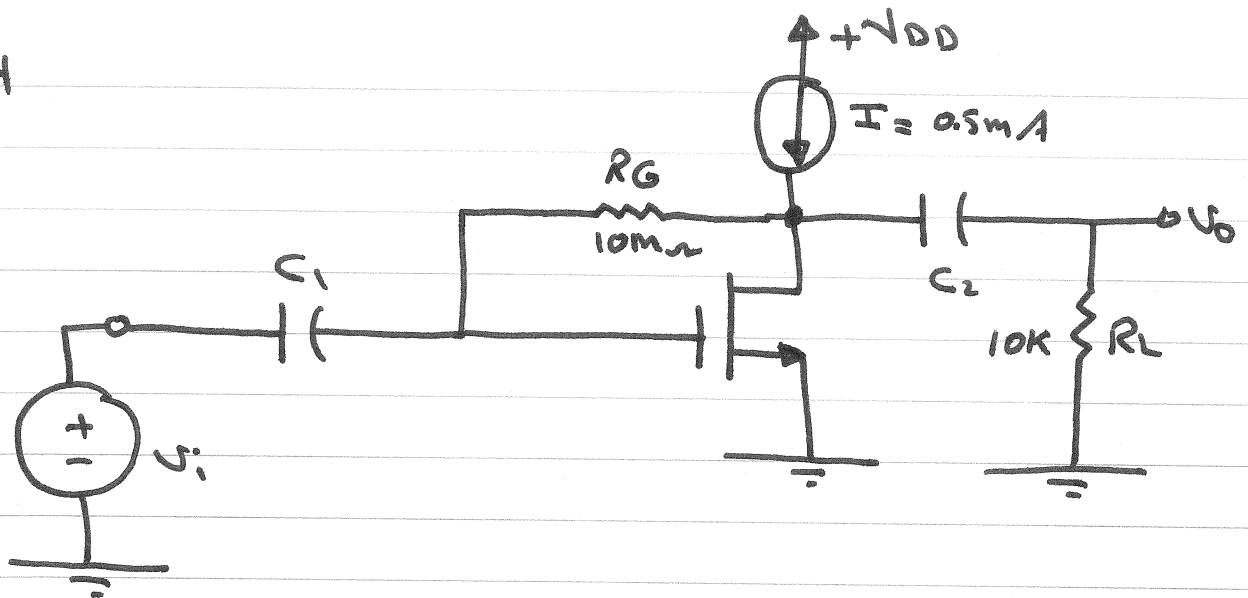

$$V_T = 0.9\text{V}, \quad V_A = 50\text{V}, \quad V_D = 2\text{V}$$


$$r_{ds} = \frac{V_A}{I_{D_S}} = \frac{50\text{V}}{0.5\text{mA}} = 100\text{K}\Omega$$

$$I_{D_S} = K_n (V_{G_S} - V_T)^2$$

$$g_m = 2K_n (V_{G_S} - V_T)$$

$$\therefore g_m = \frac{2 I_{D_S}}{V_{G_S} - V_T} = 0.9\text{mA/V}$$

ac Small Signal equivalent Ckt

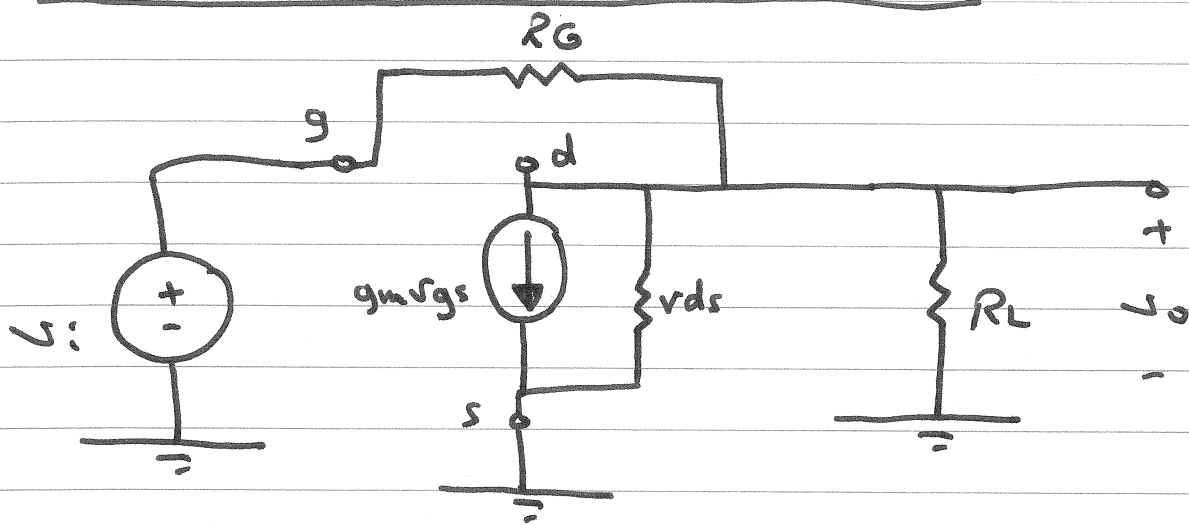

$$\text{KCL : } 0 = g_m v_{gs} + \frac{v_o}{r_{ds}} + \frac{v_o}{R_L} + \frac{v_o - v_i}{R_G}$$

$$v_{gs} = v_g - v_s$$

$$v_g = v_i, \quad v_s = 0$$

$$\therefore A_v = \frac{v_o}{v_i} = -8.265$$

For $I_{DS} = 0.5 \text{ mA}$

$$I_{DS} = K_n (v_{GS} - v_T)^2$$


$$\therefore K_n = \frac{I_{DS}}{(v_{GS} - v_T)^2} = \frac{0.5 \text{ mA}}{(2 - 0.9)^2} = 0.412 \text{ mA/V}^2$$

Now For $I_{DS} = 1 \text{ mA}$

$$I_{DS} = K_n (v_{GS} - v_T)^2 = 1 \text{ mA}$$

$$\therefore v_{GS} = 2.456 \text{ V}, \quad \therefore v_D = 2.456 \text{ V}$$

5.82

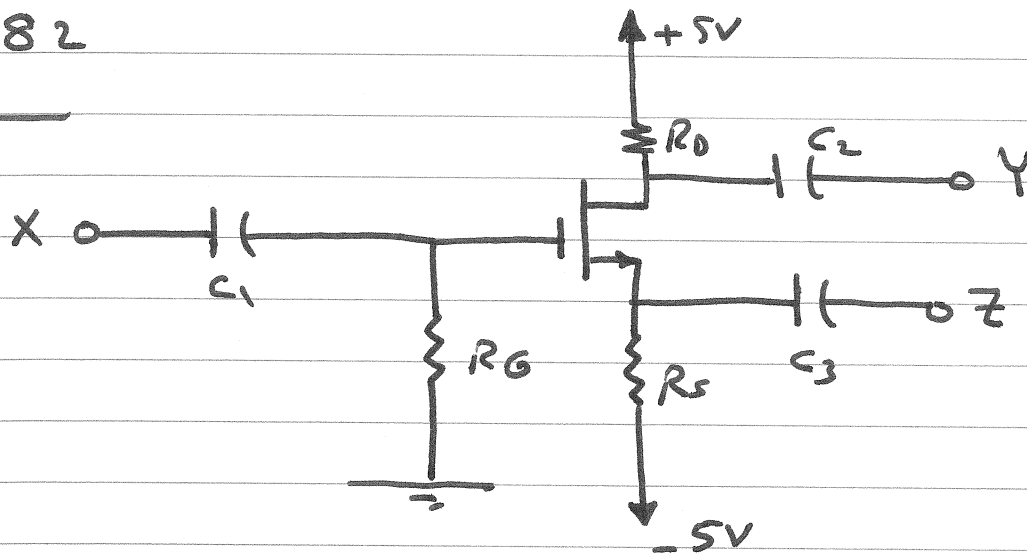

For the n-channel E-MOSFET to be in the pinch off region ; $V_{DS} > V_{GS} - V_T$

or $V_D > V_G - V_T$

$$\therefore V_D(\min) = V_G - V_T = 0 - 1 = -1V$$

$$\therefore \text{let } V_D = 0$$

$$5 = R_D I_{DS} + V_D$$

$$\therefore R_D = \frac{5 - V_D}{I_{DS}} = \frac{5}{0.1mA} = 50K \Omega$$

$$I_{DS} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$

$$0.1mA = \left(\frac{1}{2}\right) \left(0.8 \frac{mA}{V^2}\right) (V_{GS} - 1)^2$$

$$\therefore V_{GS} = 1.5V$$

$$KVL : V_{GS} + R_S I_{DS} - 5 = 0$$


$$\therefore R_S = 35K$$

$$Z_i = R_G = 10\text{M}\Omega$$

$$g_m = \frac{2I_{D_S}}{V_{G_S} - V_T} = 0.4\text{mA/V}$$

$$r_{d_s} = \frac{V_A}{I_{D_S}} = 400\text{k}$$

c)

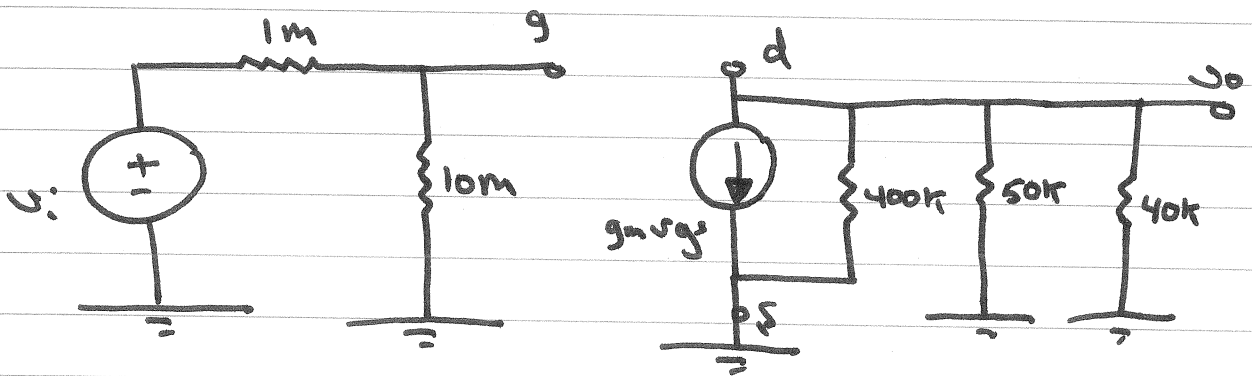


$$v_o = -g_m v_{gs} (400\text{k} \parallel 50\text{k} \parallel 40\text{k})$$

$$v_{gs} = v_g - v_s = v_g$$


$$v_g = \frac{10\text{M}}{1\text{M} + 10\text{M}} v_i$$

$$\therefore A_v = \frac{v_o}{v_i} = -7.66$$

d)

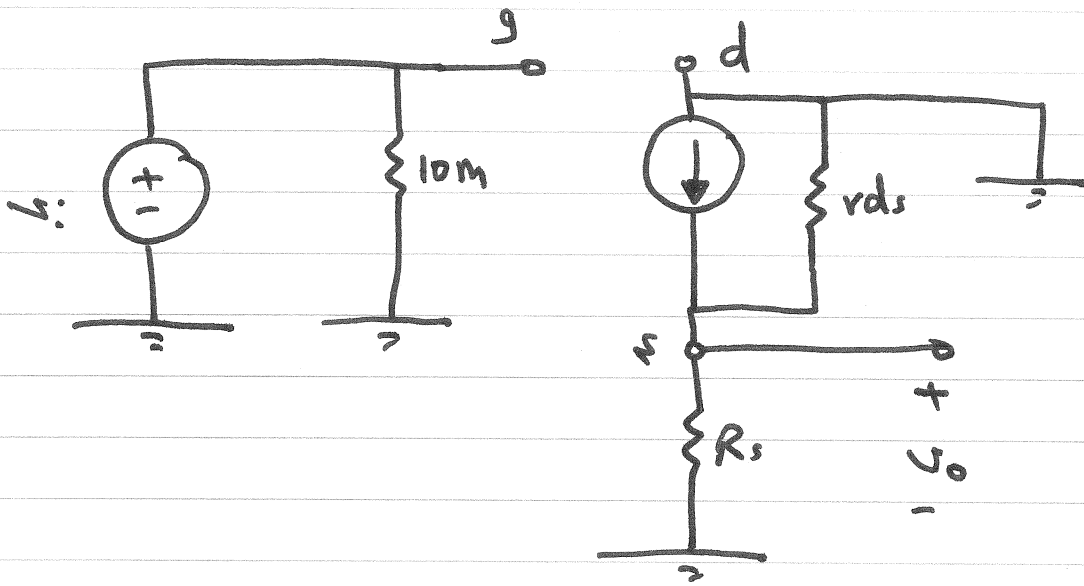

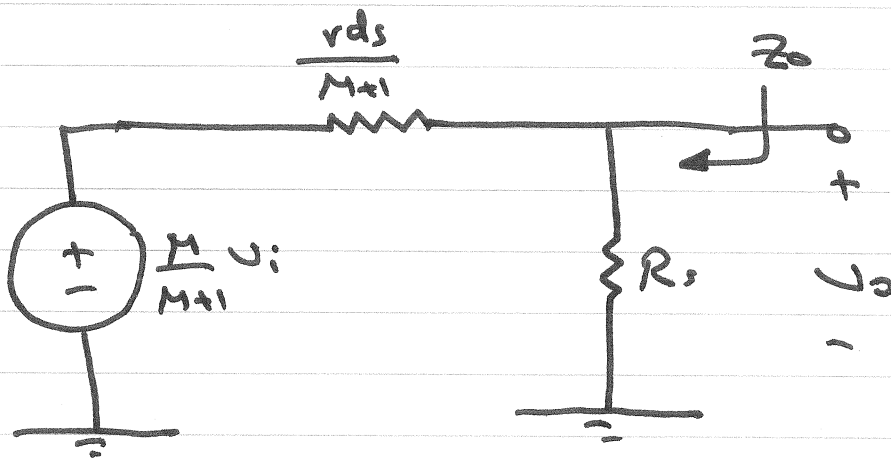To find v_o , we go to source equivalent CRT




$$\mu = g_m r_{ds} = 160$$


$$v_o = \frac{R_s}{R_s + \frac{r_{ds}}{\mu+1}} \cdot \frac{\mu}{\mu+1} v_i$$

$$\therefore A_v = \frac{v_o}{v_i} = 0.93$$

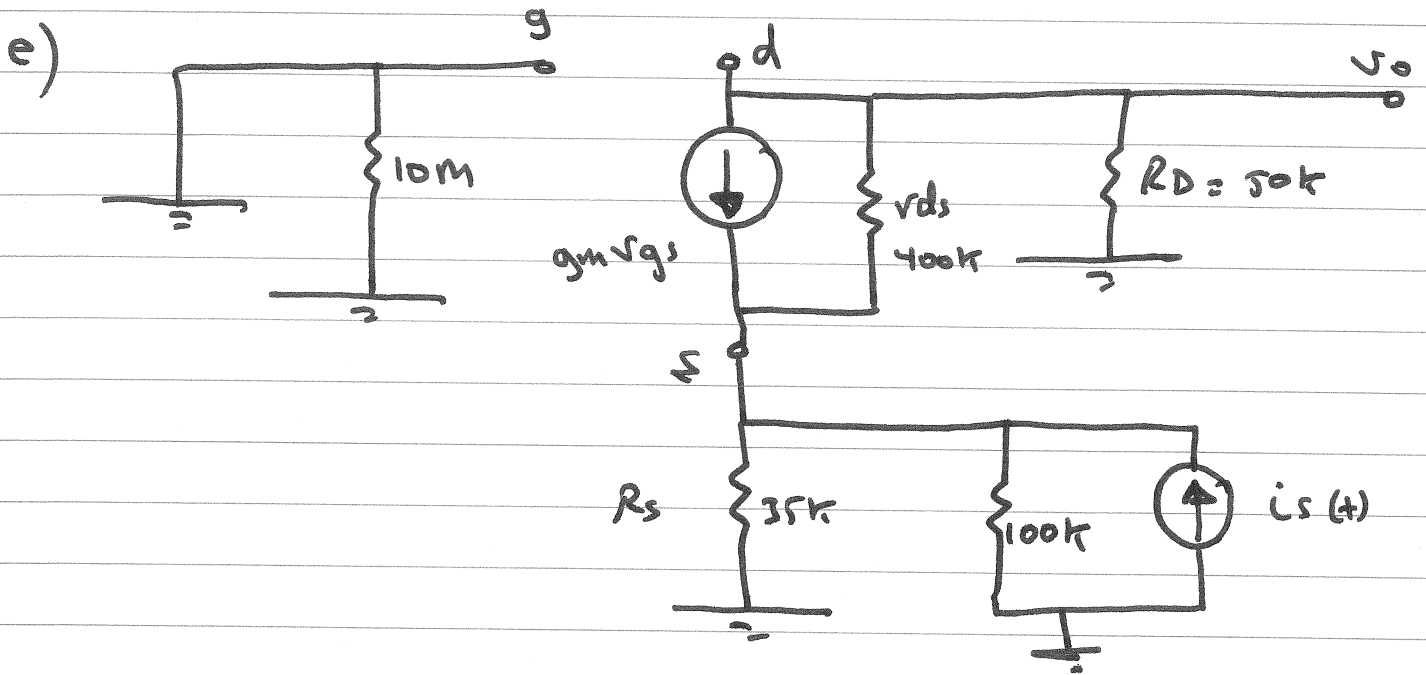
$$Z_o = R_s \parallel \frac{r_{ds}}{\mu+1}$$



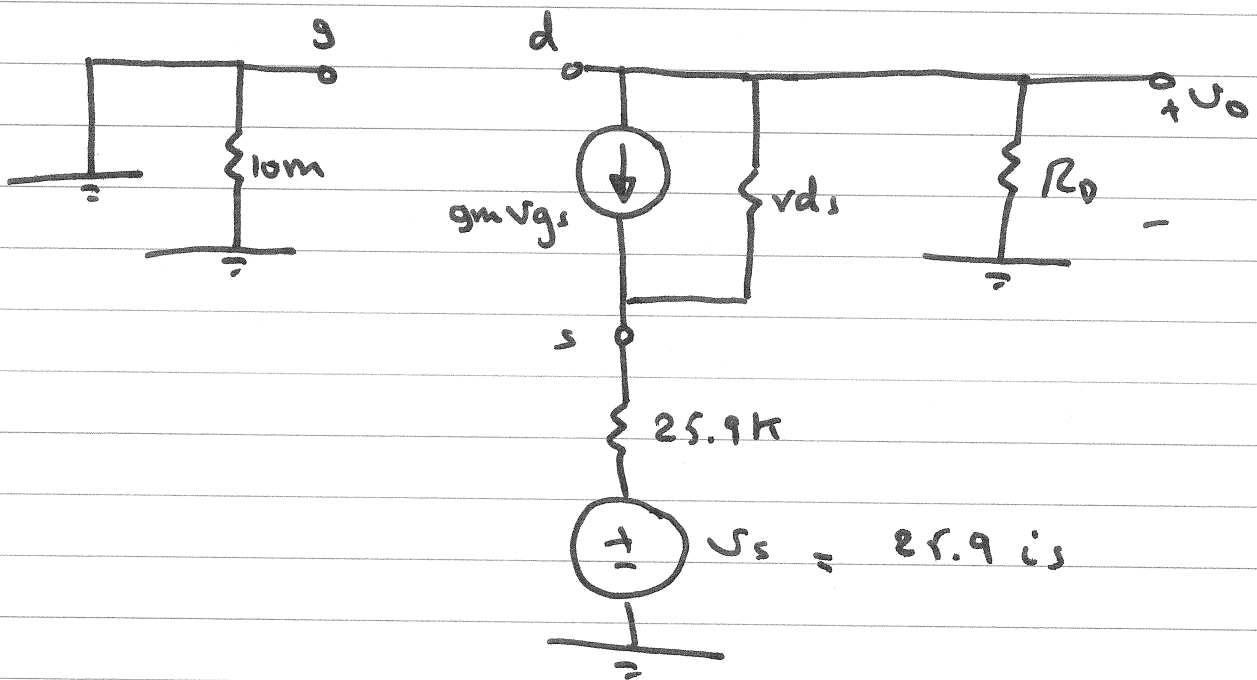The circuit can be simplified to the following



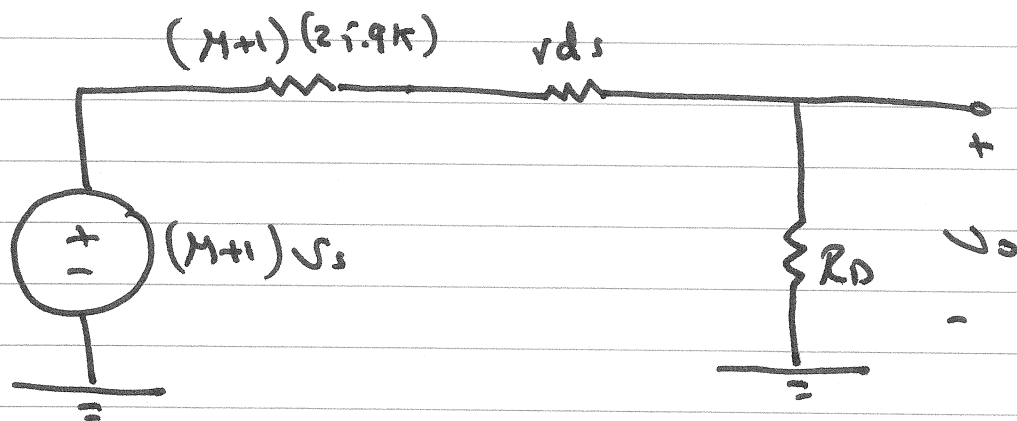To find V_o , we go to drain equivalent CRT



$$I_s = (25.9 \text{ k}) i_s \quad ; \quad M = g_m v_{ds} = 160$$

$$V_o = \frac{R_D (M+1) I_s}{R_D + (M+1)(25.9 \text{ k})}$$

$$\therefore A_v = \frac{V_o}{I_s} = 1.74$$

$$\therefore V_o = 1.74 I_s$$


$$V_o = 1.74 (25.9 \text{ k})(10 \text{ mA})$$

$$V_o = \underline{0.45 \text{ V}}$$

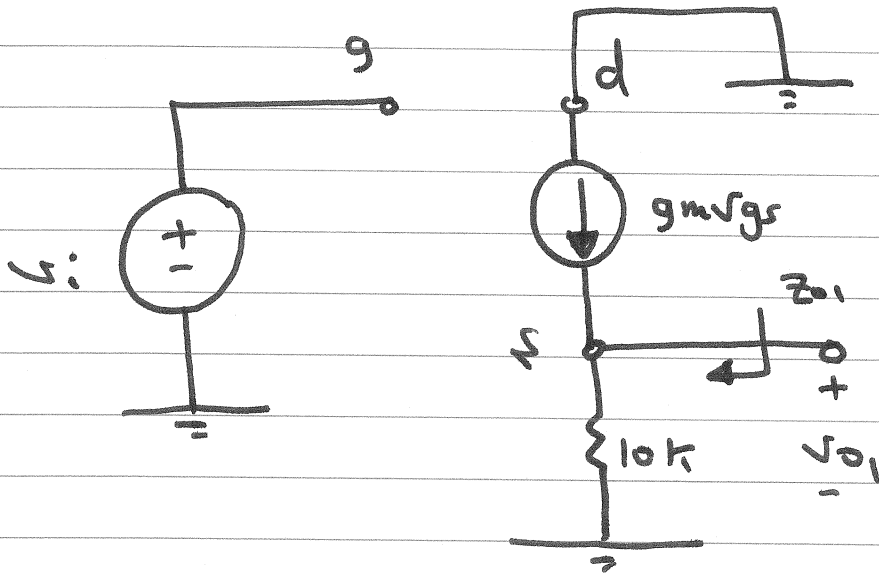5.83

$$g_m = 5 \text{ mA/V}, \quad r_{ds} = \infty$$

ac small signal equivalent ckt for 5.83 (a)



$$v_{o1} = g_m v_{gs} (10k)$$


$$v_{gs} = v_g - v_s$$

$$v_g = v_i \quad ; \quad v_s = (10k) g_m v_{gs} = v_{o1}$$

$$\therefore A_{v1} = \frac{v_{o1}}{v_i} = \frac{50}{51} \approx 1$$

$$Z_{o1} = 10k \parallel \frac{1}{g_m} = 10k \parallel 0.2k \approx 0.196k$$

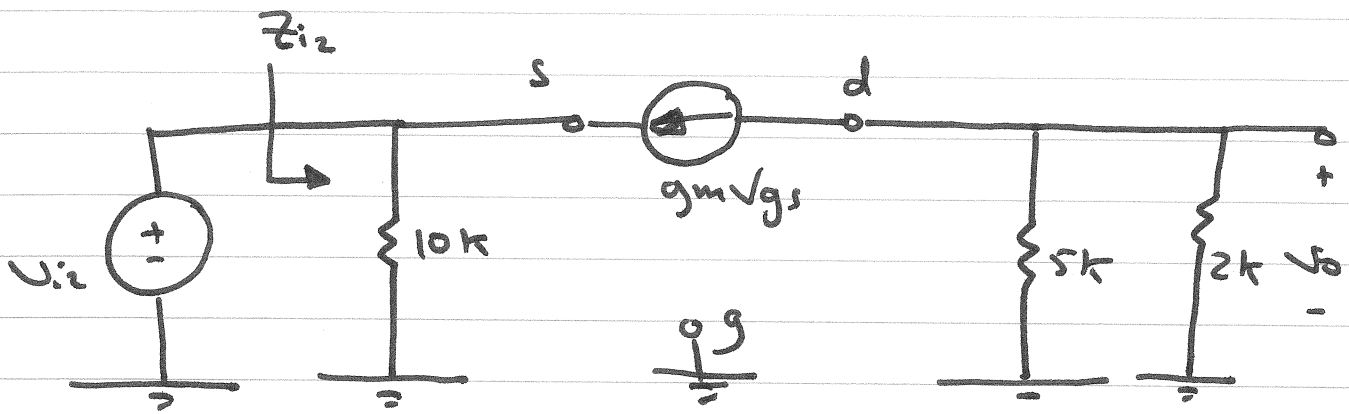ac small signal equivalent ckt for 5.83 (b)





$$Z_{i2} = 10k \parallel \frac{1}{g_m} = 0.196k$$

$$v_o = -g_m v_{gs} (5k \parallel 2k)$$

$$v_{gs} = v_g - v_s = 0 - v_s = v_{i2}$$

$$\therefore A_{v2} = \frac{v_o}{v_{i2}} = 7.143$$

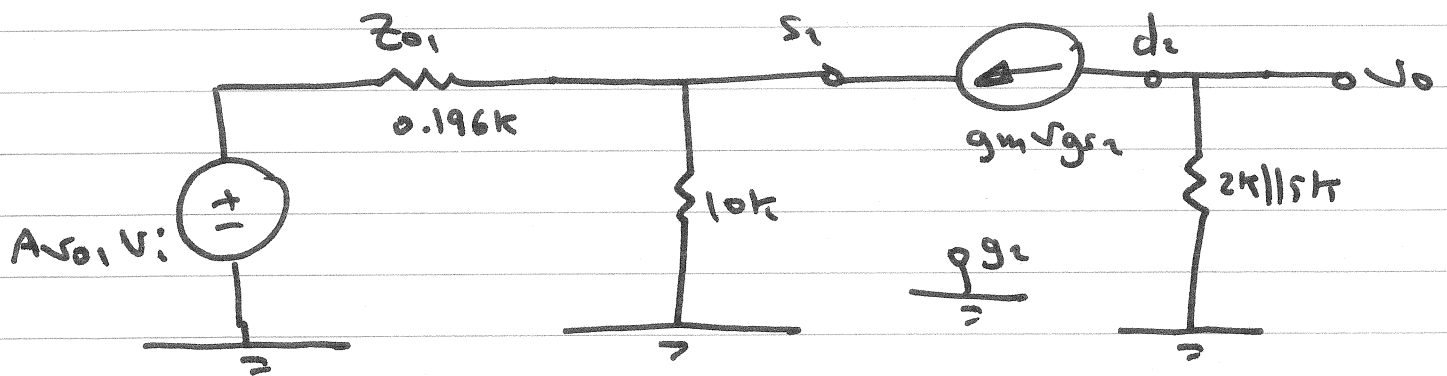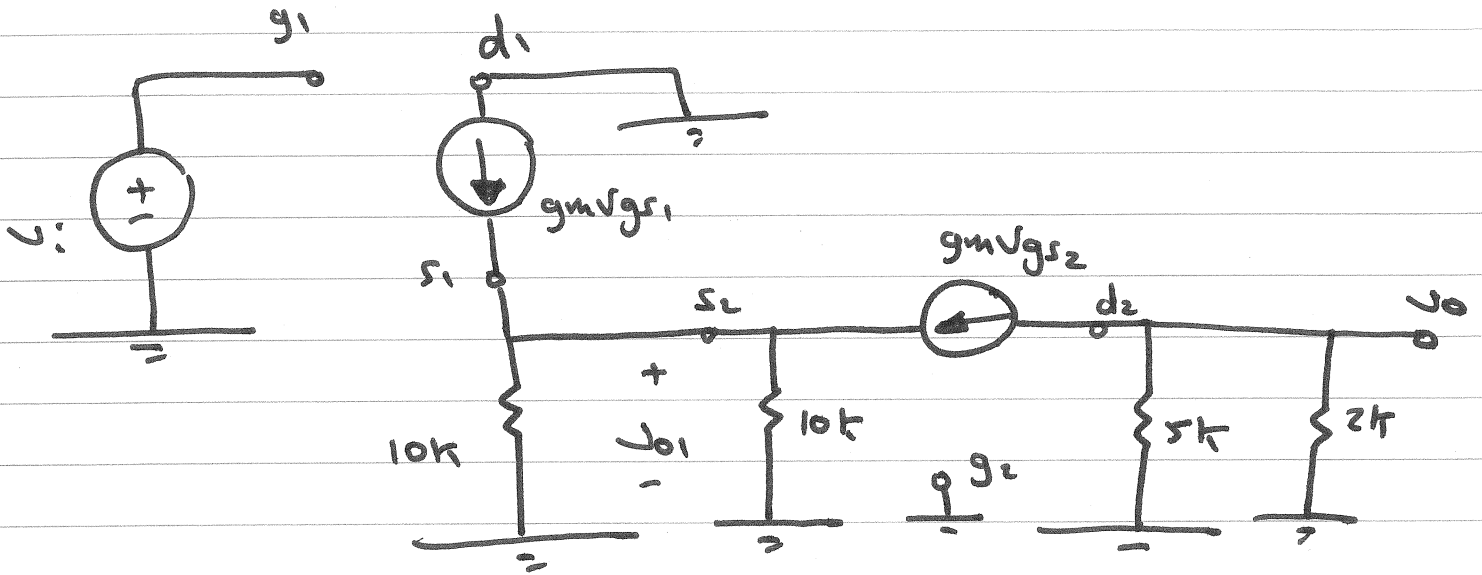ac small signal equivalent CRT for the complete amplifier:



$$V_o = -g_m v_{gs2} (2k \parallel 5k)$$

$$v_{gs2} = v_{g2} - v_{s2} = -v_{s2}$$

$$v_{s2} = \frac{Z_{i2}}{Z_{i2} + Z_{01}} A_{v01} V_i$$

$$A_v = \frac{V_o}{V_i} = (0.49)(7.143) = 3.5$$