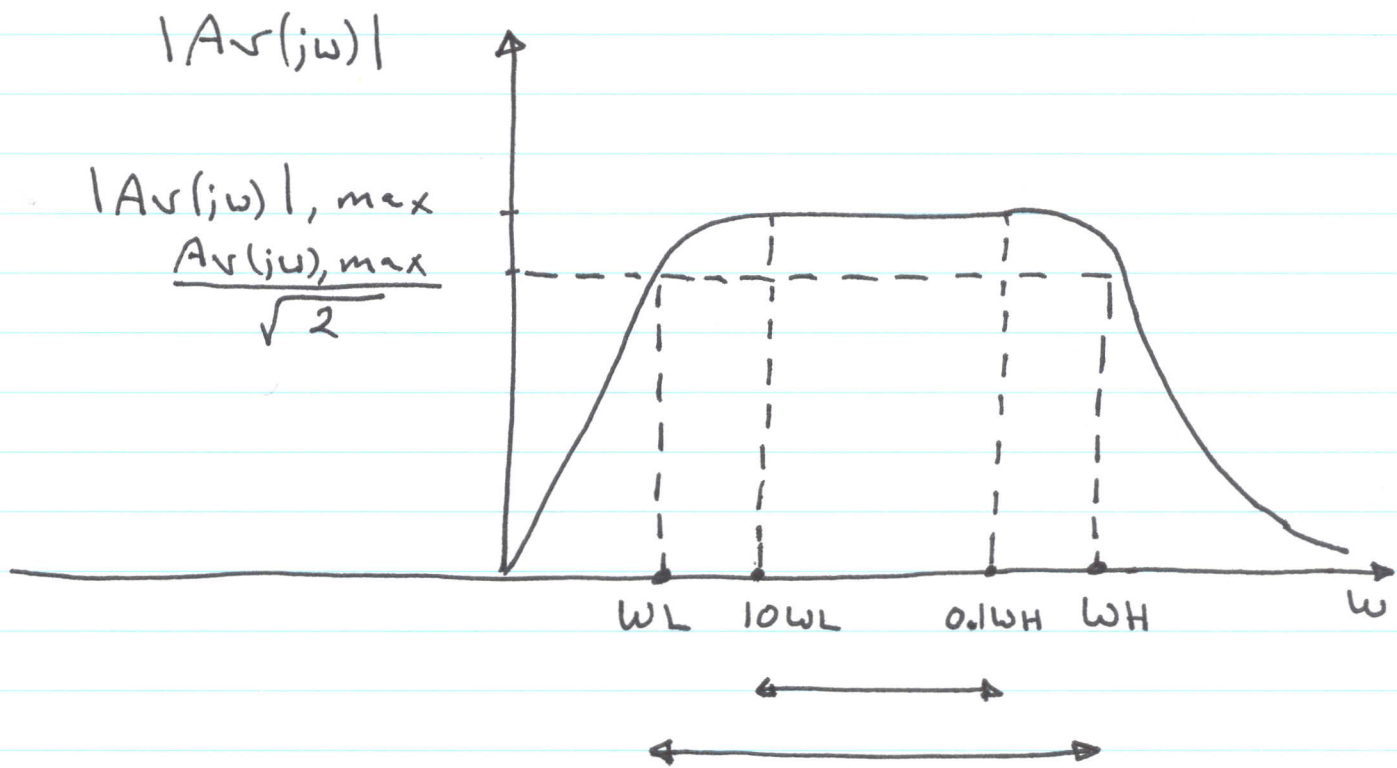


# Frequency Response



$\omega_L$  : Lower cutoff frequency

$\omega_H$  : Upper cutoff frequency

$$\left. |A_v(j\omega)| \right|_{\substack{\omega = \omega_L \\ \omega = \omega_H}} = \frac{|A_v(j\omega)|_{max}}{\sqrt{2}} = \frac{|A_v|_{mid}}{\sqrt{2}}$$

$$\text{Bandwidth} = \omega_H - \omega_L$$

$$\text{Midband range} = 0.1\omega_H - 10\omega_L$$

- The signal passed through an ac amplifier is usually a complex waveform containing many different frequency components, rather than a single frequency sine wave.


For example, audio-frequency signal such as speech and music are combination of many different sine waves occurring simultaneously with different amplitude and different frequencies in the range from 20 Hz to 20 kHz.

- In order for an output to be an amplified version of the input, an amplifier must amplify every frequency component in the signal by the same amount.


- Bandwidth must cover the entire range of frequency components if undistorted amplification is to be achieved.

# Series Capacitance and Low-frequency Response

---

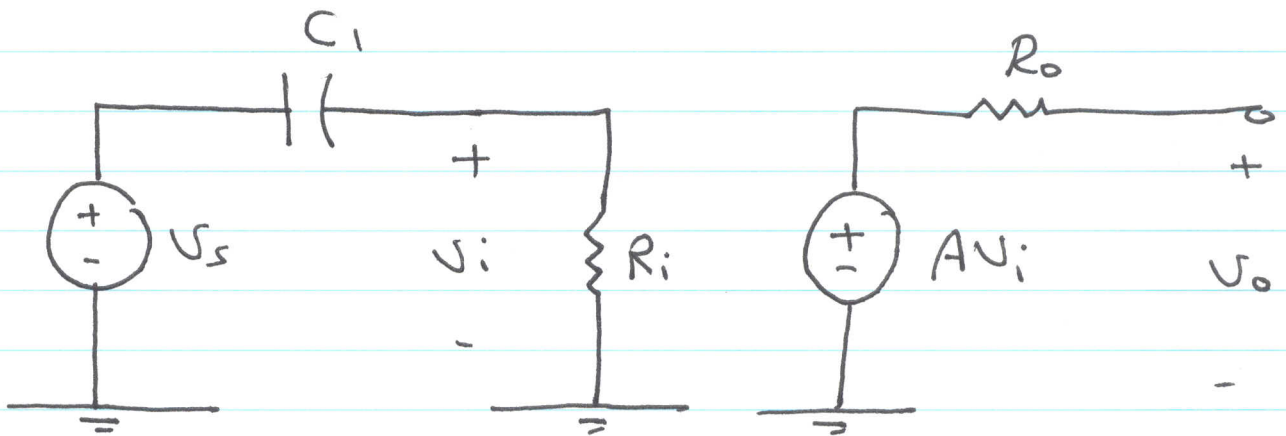

1) At midband range

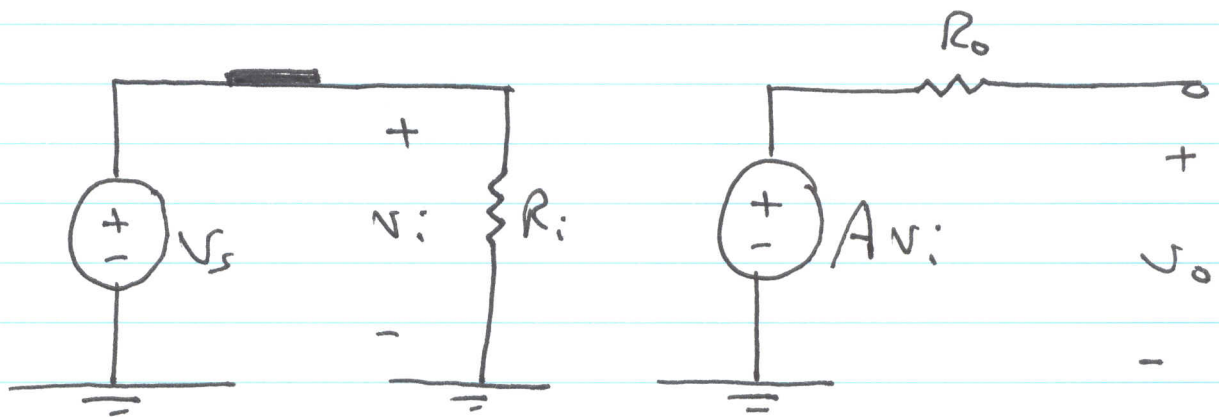


$$V_o = AV_i$$

$$V_i = V_s$$

$$\therefore \frac{V_o}{V_i} = A = A_v(\text{mid})$$

2) At Low-frequency

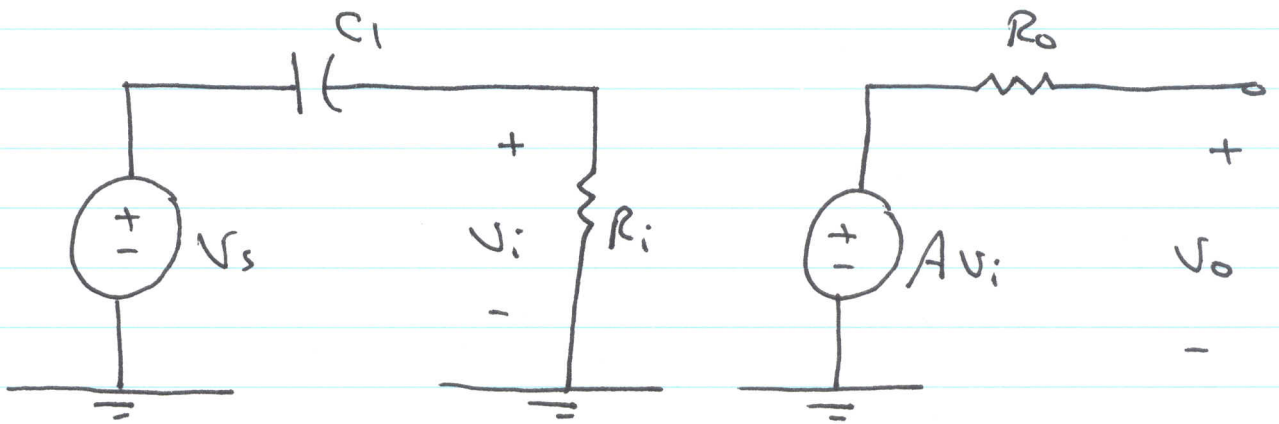

$$\vec{V}_o = A \vec{V}_i$$

$$\vec{V}_i = \frac{R_i}{R_i + \frac{1}{j\omega C_1}} \vec{V}_s$$

$$\frac{\vec{V}_o}{\vec{V}_s} = A_V(j\omega) = A \frac{R_i}{R_i + \frac{1}{j\omega C_1}}$$

$$A_V(j\omega) = A \frac{1}{1 + \frac{1}{jR_i\omega C_1}}$$

$$|A_V(j\omega)| = A \frac{1}{\sqrt{1 + \left(\frac{1}{R_i\omega C_1}\right)^2}}$$

a) If  $\omega \rightarrow 0$  ;  $|A_V(j\omega)| \rightarrow 0$

b) If  $\omega \rightarrow \infty$  ;  $|A_V(j\omega)| \rightarrow A$

c) If  $\omega = \frac{1}{R_i C}$  ;  $|A_V(j\omega)| = \frac{A}{\sqrt{2}}$


$$\therefore \omega_L = \frac{1}{R_i C}$$

$$\text{Let } \omega_{c_1} = \frac{1}{R_{TH} C_1}$$


$$\omega_{c_1} = \frac{1}{R_i C_1}$$

$$\therefore \omega_L = \omega_{c_1}$$

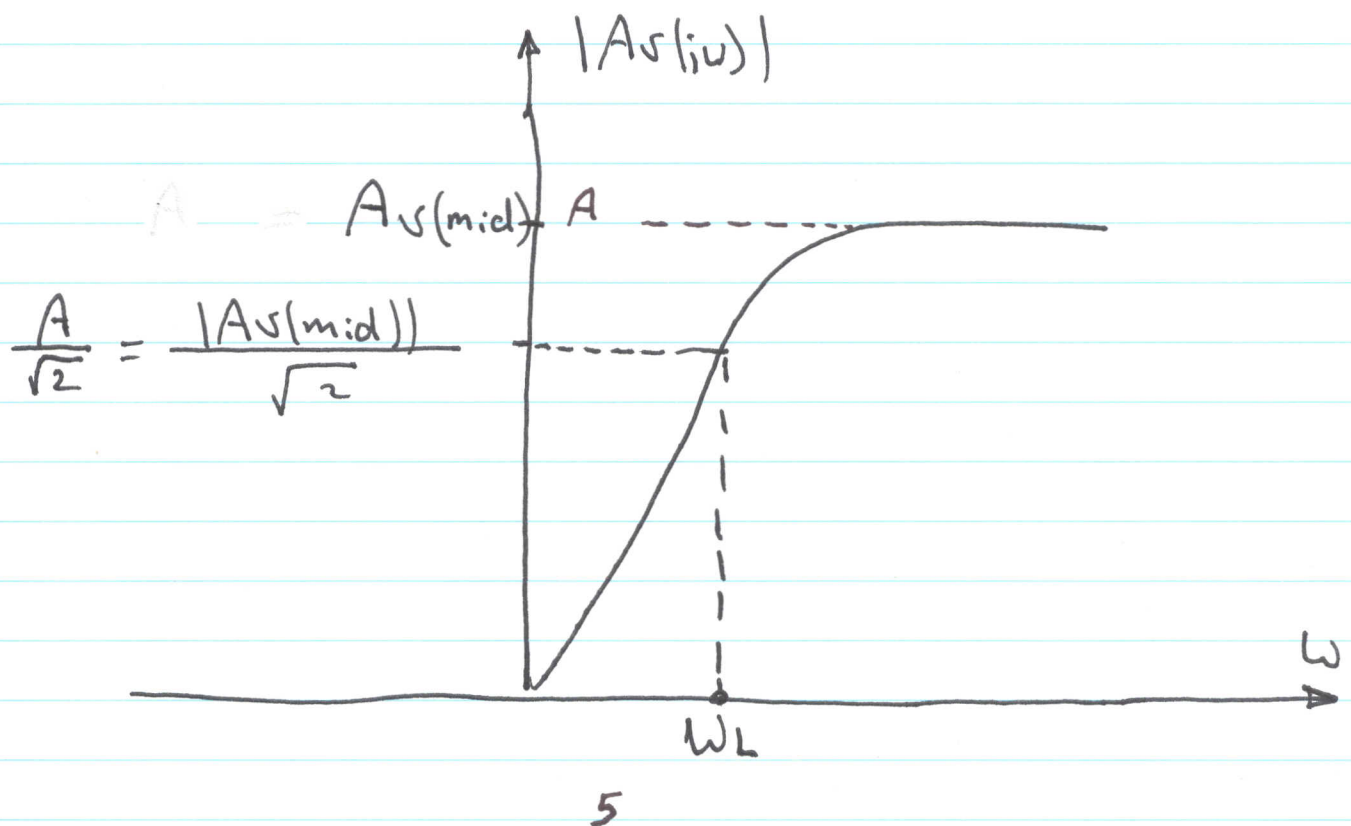
Where  $\omega_{c_1}$  is the corner frequency of  $C_1$ .



# Input and output Coupling Capacitors

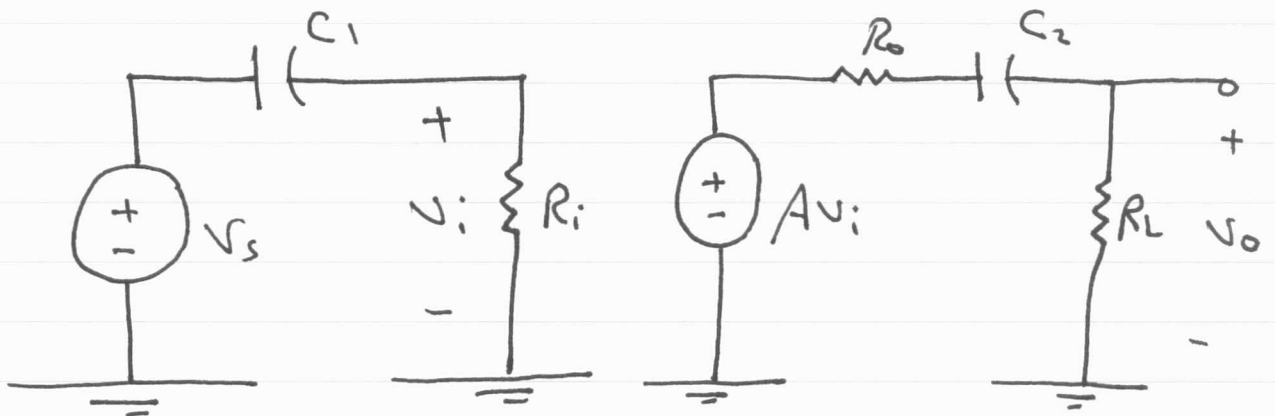

1) At midband range

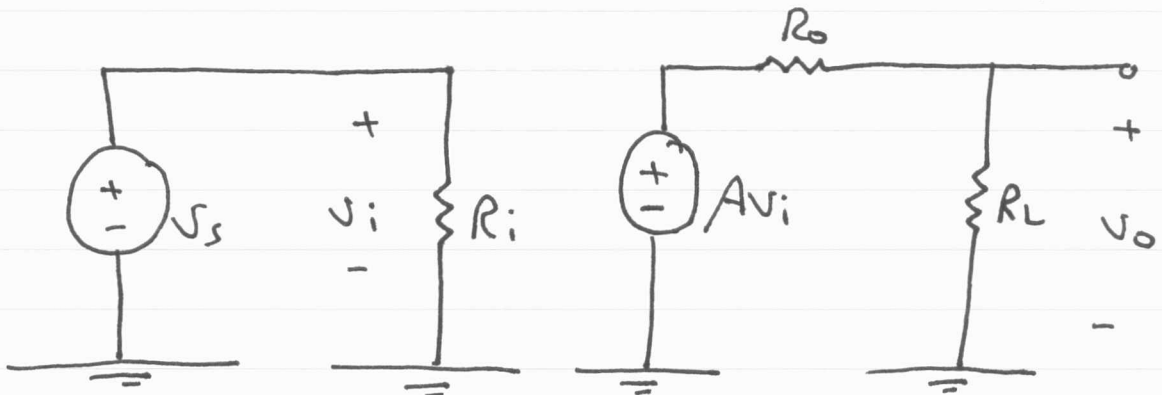


$$V_o = \frac{R_L}{R_L + R_o} A V_i$$

$$V_i = V_s$$

$$A_v(\text{mid}) = \frac{V_o}{V_s} = A \frac{R_L}{R_L + R_o}$$

2) At low-frequency

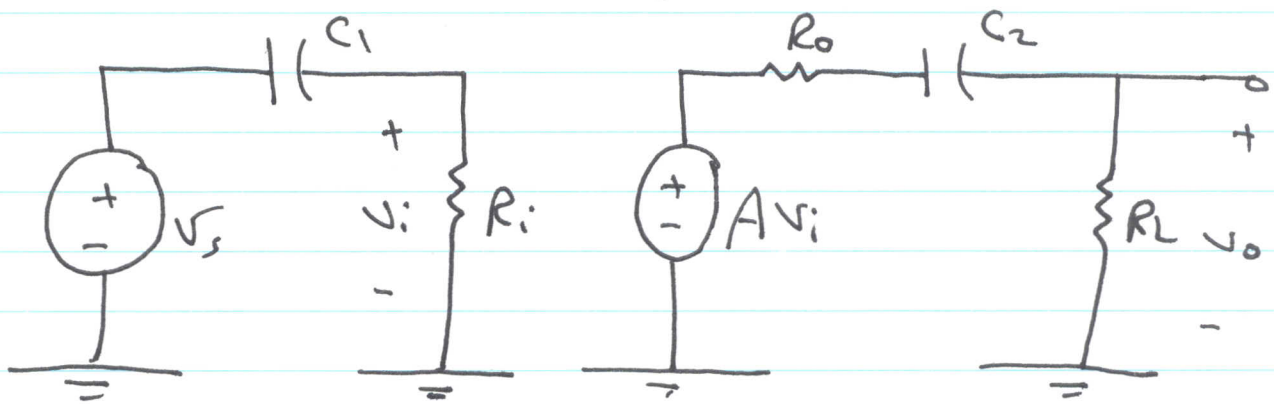

$$\vec{V}_o = \frac{R_L}{R_L + R_o + \frac{1}{j\omega C_2}} A \vec{V}_i$$

$$\vec{V}_i = \frac{R_i}{R_i + \frac{1}{j\omega C_1}} V_s$$

$$A_V(j\omega) = \frac{\vec{V}_o}{\vec{V}_s} = A \frac{R_L}{R_L + R_o} \left( \frac{1}{1 + \frac{\omega C_1}{j\omega}} \right) \left( \frac{1}{1 + \frac{\omega C_2}{j\omega}} \right)$$

Where  $\omega_{c1} = \frac{1}{R_i C_1}$

$$\omega_{c2} = \frac{1}{(R_o + R_L) C_2}$$

$$\therefore A_V(j\omega) = A_V(\text{mid}) \left( \frac{1}{1 + \frac{\omega_{c1}}{j\omega}} \right) \left( \frac{1}{1 + \frac{\omega_{c2}}{j\omega}} \right)$$

$$|A_V(j\omega)| = \frac{A_V(\text{mid})}{\sqrt{2}}$$

$$\therefore \left| \left( 1 + \frac{\omega_{c1}}{j\omega_L} \right) \left( 1 + \frac{\omega_{c2}}{j\omega_L} \right) \right| = \sqrt{2}$$

$$\therefore \omega_L^2 = \frac{\omega_{c1}^2 + \omega_{c2}^2}{2} + \frac{\sqrt{\omega_{c1}^4 + \omega_{c2}^4 + 6\omega_{c1}^2\omega_{c2}^2}}{2}$$

a) Let  $\omega_{c1} = 616 \text{ v/s}$

$$\omega_{c2} = 17.86 \text{ v/s}$$

$$\therefore \omega_L = 616.517 \text{ v/s}$$

b) Let  $\omega_{c1} = 200 \text{ v/s}$

$$\omega_{c2} = 750 \text{ v/s}$$

$$\therefore \omega_L = 798 \text{ v/s}$$

$$\therefore \text{if } \omega_{c1} > \omega_{c2} > \omega_{c3}$$

$$\therefore \omega_{c1} + \omega_{c2} + \omega_{c3} > \omega_L > \omega_{c1}$$



$$A_V(j\omega) = A_V(\text{mid}) \frac{1}{\left(1 + \frac{\omega_{c1}}{j\omega}\right) \left(1 + \frac{\omega_{c2}}{j\omega}\right)}$$

Let  $\omega_{c1} > \omega_{c2}$  ;  $\omega_L > \omega_{c1}$

$$\left| A_V(j\omega_L) \right| = \frac{A_V(\text{mid})}{\left| \left(1 + \frac{\omega_{c1}}{j\omega_L}\right) \left(1 + \frac{\omega_{c2}}{j\omega_L}\right) \right|}$$

$$\left| A_V(j\omega_L) \right| = \frac{A_V(\text{mid})}{\sqrt{2}}$$

$$\therefore \left| \left(1 + \frac{\omega_{c1}}{j\omega_L}\right) \left(1 + \frac{\omega_{c2}}{j\omega_L}\right) \right| = \sqrt{2}$$

Since  $\omega_{c1} > \omega_{c2}$  , and  $\omega_L > \omega_{c1}$

$$\left| \left(1 + \frac{\omega_{c1}}{j\omega_L}\right) \left(1 + \frac{\omega_{c2}}{j\omega_L}\right) \right| = \sqrt{2}$$

$$\left| \left(1 + \frac{\omega_{c1}}{j\omega_L}\right) \right| = \sqrt{2}$$

$$\sqrt{1 + \left(\frac{\omega c_1}{\omega_L}\right)^2} = \sqrt{2}$$

$$\therefore \omega c_1 = \omega_L \quad (\text{Lower Limit})$$

To find the upper Limit

$$\left| \left(1 + \frac{\omega c_1}{j\omega_L}\right) \left(1 + \frac{\omega c_2}{j\omega_L}\right) \right| = \sqrt{2}$$

$$\left| 1 + \frac{\omega c_1 + \omega c_2}{j\omega_L} - \frac{\omega c_1}{\omega_L} \cdot \frac{\omega c_2}{\omega_L} \right| = \sqrt{2}$$

$$\text{But } \frac{\omega c_1}{\omega_L} < 1 \quad \text{and} \quad \frac{\omega c_2}{\omega_L} \ll 1$$

$$\therefore \frac{\omega c_1}{\omega_L} \cdot \frac{\omega c_2}{\omega_L} \ll 1$$

$$\therefore \text{Let } \frac{\omega c_1}{\omega_L} \cdot \frac{\omega c_2}{\omega_L} \rightarrow 0$$

$$\left| \left(1 + \frac{\omega c_1 + \omega c_2}{j\omega_L}\right) \right| = \sqrt{2}$$

$$\sqrt{1 + \left(\frac{w_{c1} + w_{c2}}{w_L}\right)^2} = \sqrt{2}$$

$$\therefore \frac{w_{c1} + w_{c2}}{w_L} = 1$$

$$\therefore w_L = w_{c1} + w_{c2} \quad (\text{upper Limit})$$

$\therefore$  if  $w_{c1} > w_{c2}$

$$w_{c1} + w_{c2} > w_L > w_{c1}$$