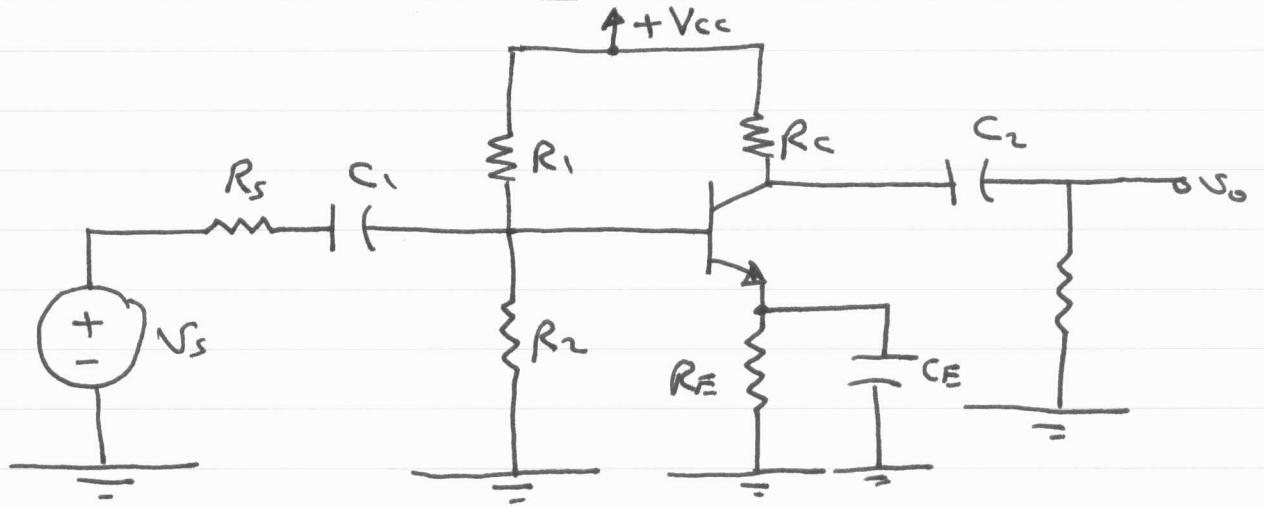


# CE Amplifier Low-frequency Analysis





$$h_{ie} = 10.45 \text{ k} \quad , \quad h_{fe} = 350 \quad , \quad R_1 \parallel R_2 = 16.67 \text{ k}$$

$$R_C = 5 \text{ k} \quad , \quad R_L = 2 \text{ k} \quad , \quad R_E = 5 \text{ k} \quad , \quad R_S = 1 \text{ k}$$


$$C_1 = 3 \text{ } \mu\text{F} \quad , \quad C_2 = 8 \text{ } \mu\text{F} \quad , \quad \text{and} \quad C_E = 50 \text{ } \mu\text{F}$$

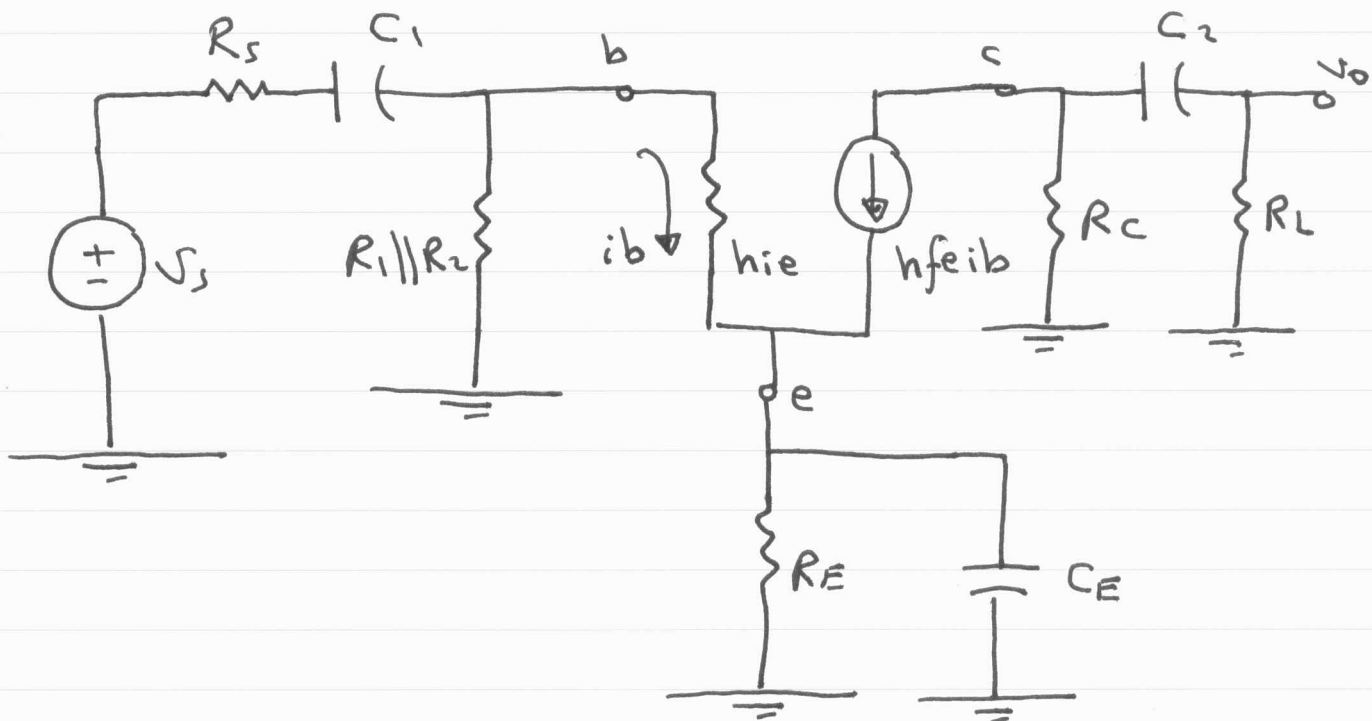ac small signal low-frequency equivalent CRT



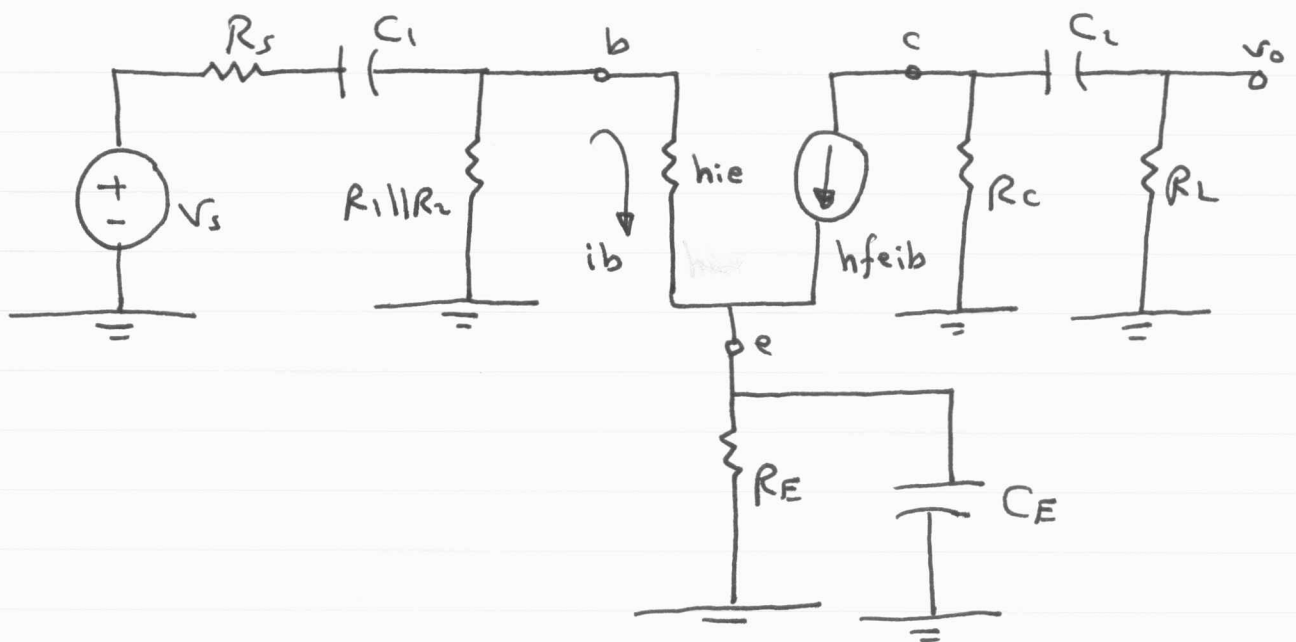

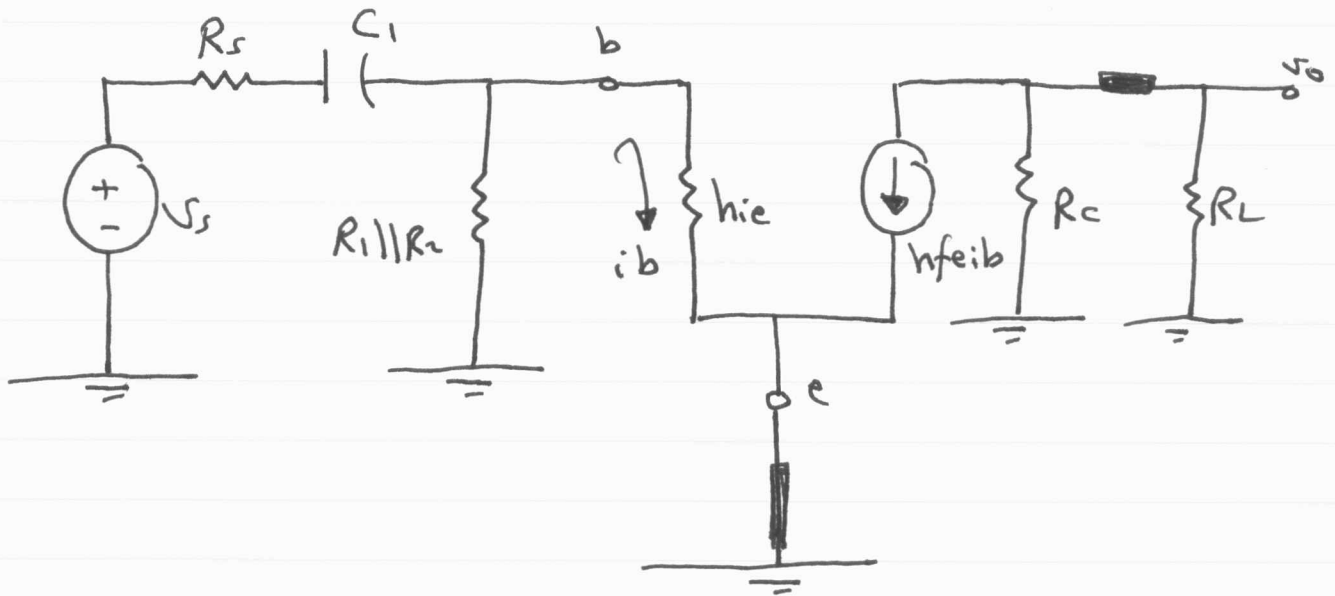1) To find  $\omega_{c_1}$ , set  $C_E$ , and  $C_2$  short




$$\omega_{c_1} = \frac{1}{R_{TH_1} C_1}$$

$$R_{TH_1} = R_s + (R_1 \parallel R_2) \parallel h_{ie}$$

$$\therefore \omega_{c_1} = 44.9 \text{ rad/s}$$

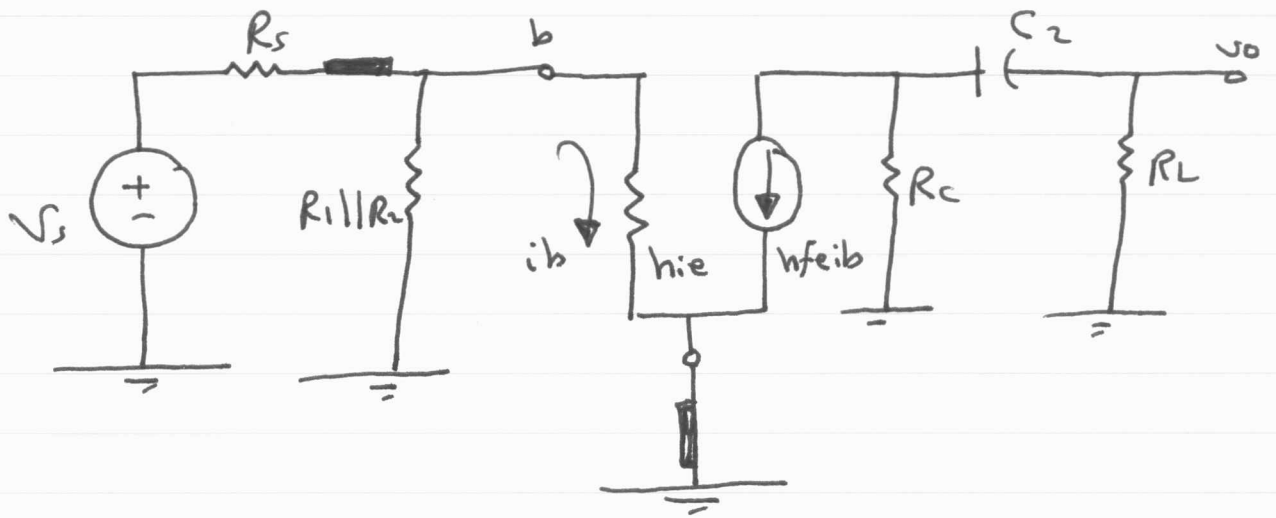2) To find  $\omega_{c2}$ ; set  $C_1$  and CE Shunt




$$\omega_{c2} = \frac{1}{R_{TH2} C_2}$$

$$R_{TH2} = R_L + R_c$$

$$\therefore \omega_{c2} = 17.86 \text{ v/s}$$

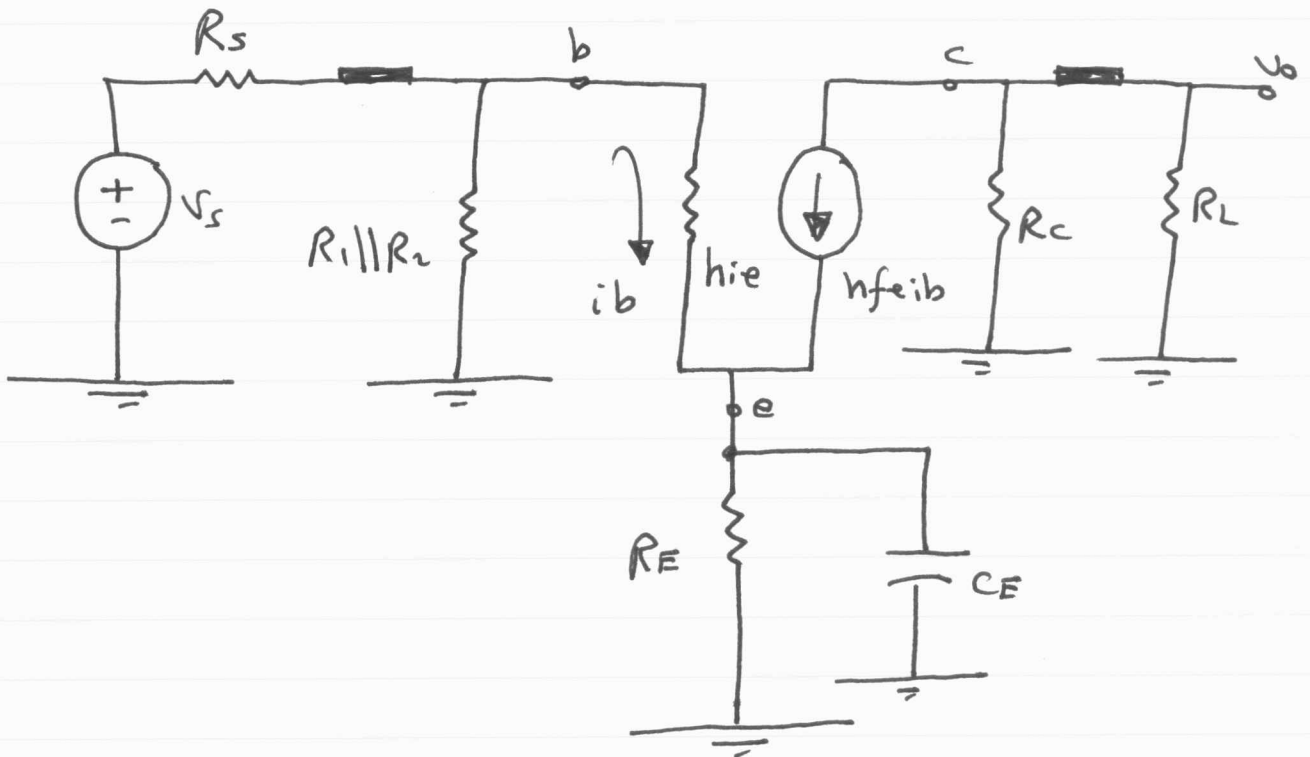3) To find  $\omega_{CE}$ ; Set  $C_1$ , and  $C_2$  short



$$\omega_{CE} = \frac{1}{R_{TH3} C_E}$$

$$R_{TH3} = R_E \parallel \left( \frac{R_s \parallel R_1 \parallel R_2 + h_{ie}}{h_{fe} + 1} \right)$$


$$\therefore \omega_{CE} = 616 \text{ v/s}$$

$$\omega_{C1} + \omega_{C2} + \omega_{CE} > \omega_L > \omega_{CE}$$

$$679 \text{ v/s} > \omega_L > 616 \text{ v/s}$$

$$\omega_L \equiv 645 \text{ v/s} \quad \text{Exact}$$

# CE Amplifier Low-frequency Design

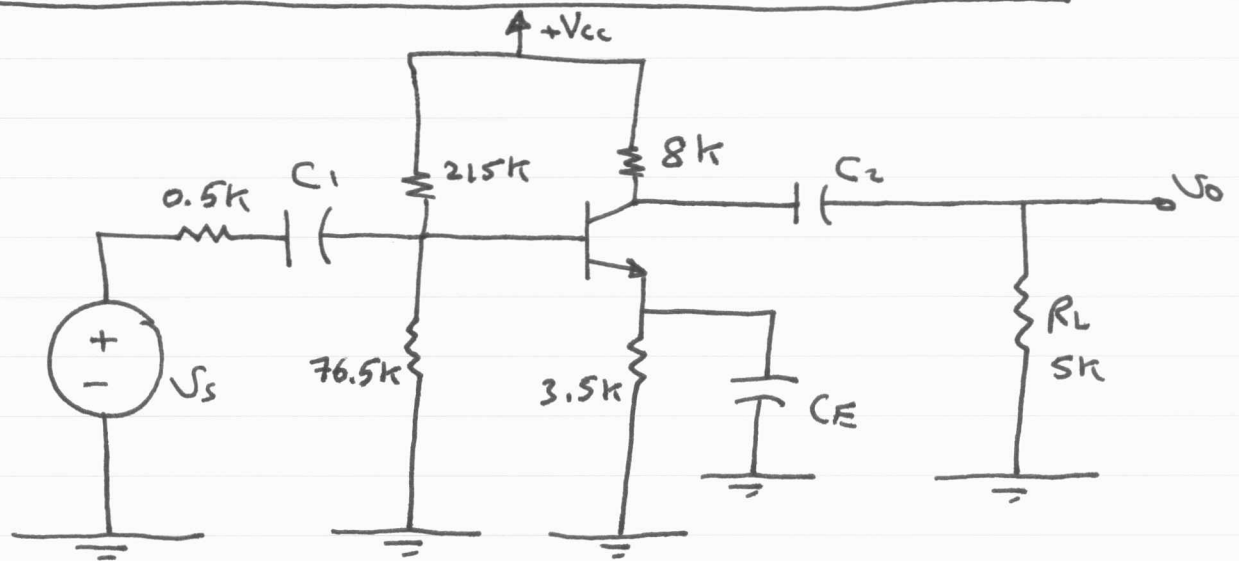

$$h_{fe} = 450, \text{ and } h_{ie} = 5.78k$$

Complete the design so that  $\omega_L = 1000 \text{ rad/s}$

$$* \quad \omega_{C_1} + \omega_{C_2} + \omega_{C_E} = \omega_L = 1000 \text{ rad/s}$$

$$* \quad \omega_{C_E} \geq 70\% \omega_L$$

$$\omega_{C_E} \geq 0.7 \omega_L$$

$$\omega_{C_E} = 890 \text{ rad/s}$$

$$\omega_{C_1} = 100 \text{ rad/s}$$

$$\omega_{C_2} = 10 \text{ rad/s}$$

$$\omega_{CE} = \frac{1}{\left[ R_E \parallel \left( \frac{R_s \parallel R_1 \parallel R_2 + h_{ie}}{h_{fe} + 1} \right) \right] C_E} = 890 \text{ v/s}$$

$$\therefore C_E = 72.2 \text{ } \mu\text{F}$$

$$\omega_{C_1} = \frac{1}{[R_s + R_1 \parallel R_2 \parallel h_{ie}] C_1} = 100 \text{ v/s}$$

$$\therefore C_1 = 1.74 \text{ } \mu\text{F}$$

$$\omega_{C_2} = \frac{1}{[R_c + R_L] C_2} = 10 \text{ v/s}$$


$$\therefore C_2 = 1.54 \text{ } \mu\text{F}$$

Choose  $C_E = 80 \text{ } \mu\text{F}$


$$C_1 = C_2 = 2 \text{ } \mu\text{F}$$

$$\therefore \omega_L = 982 \text{ v/s}$$
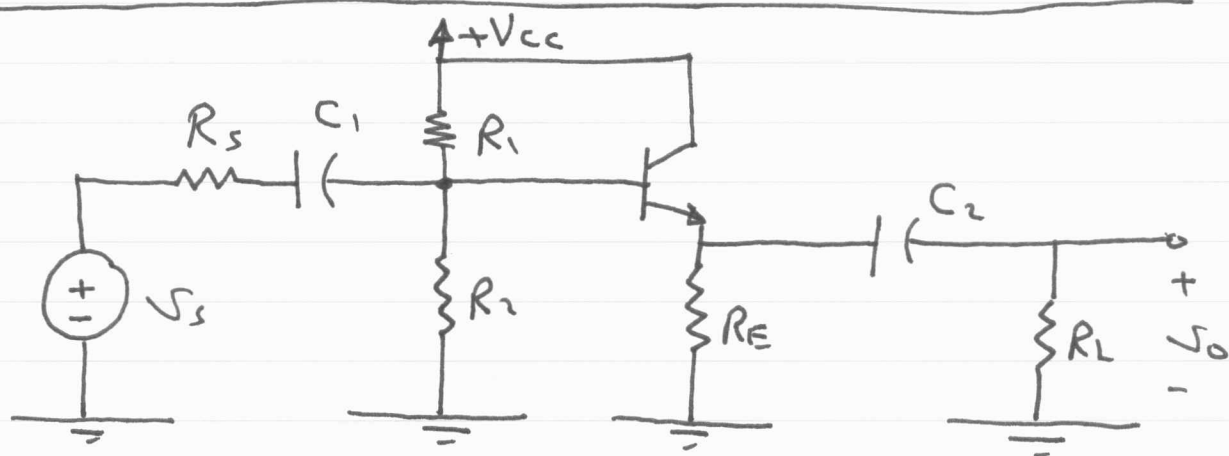
# Common Collector Low-Frequency Response



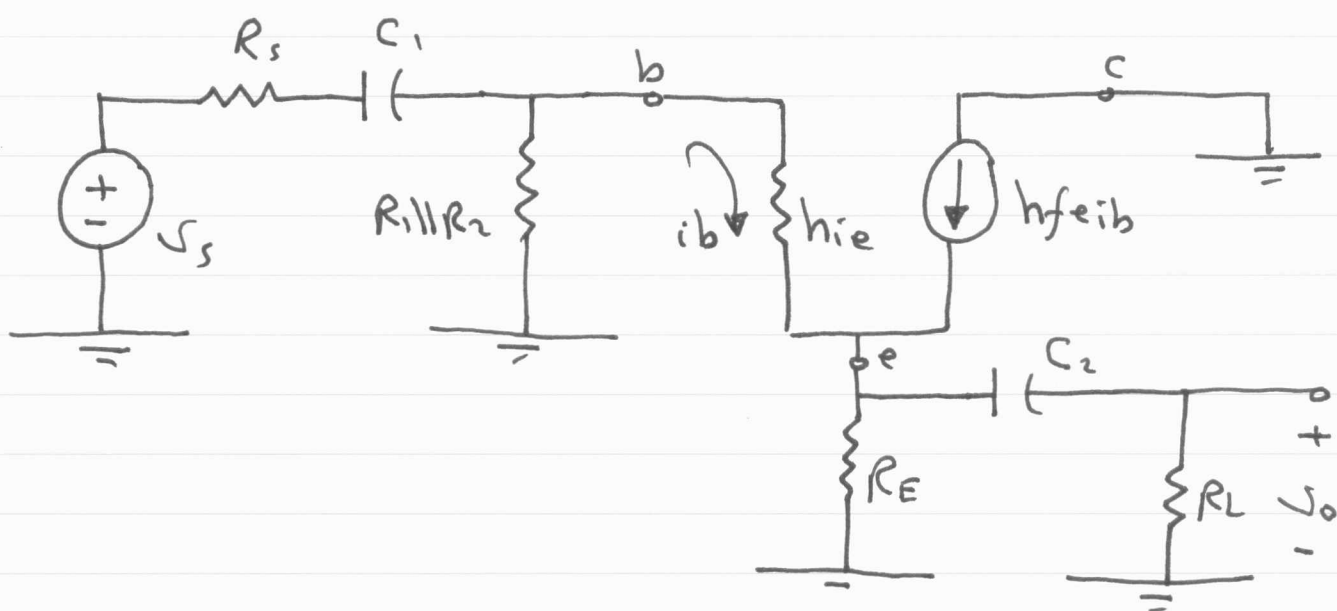
ac small signal low-frequency equivalent ckt:



$$\omega_{c_1} = \frac{1}{C_1 \left[ R_s + R_1 \parallel R_2 \parallel (h_{ie} + (R_E \parallel R_L)(1 + h_{fe})) \right]}$$

$$\omega_{c_2} = \frac{1}{C_2 \left[ R_L + R_E \parallel \left( \frac{R_s \parallel R_1 \parallel R_2 + h_{ie}}{h_{fe} + 1} \right) \right]}$$


# CS Low-Frequency Analysis

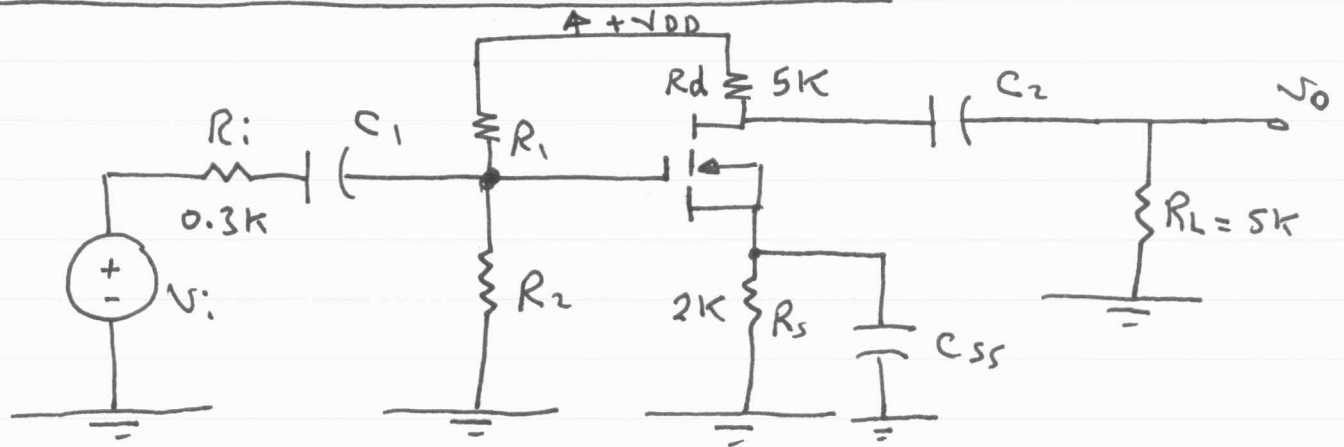

$$R_1 \parallel R_2 = 100k, \quad g_m = 10 \text{ mS}$$

$$C_1 = 0.2 \mu\text{F}, \quad C_2 = 1 \mu\text{F}, \quad \text{and } C_{ss} = 10 \mu\text{F}$$

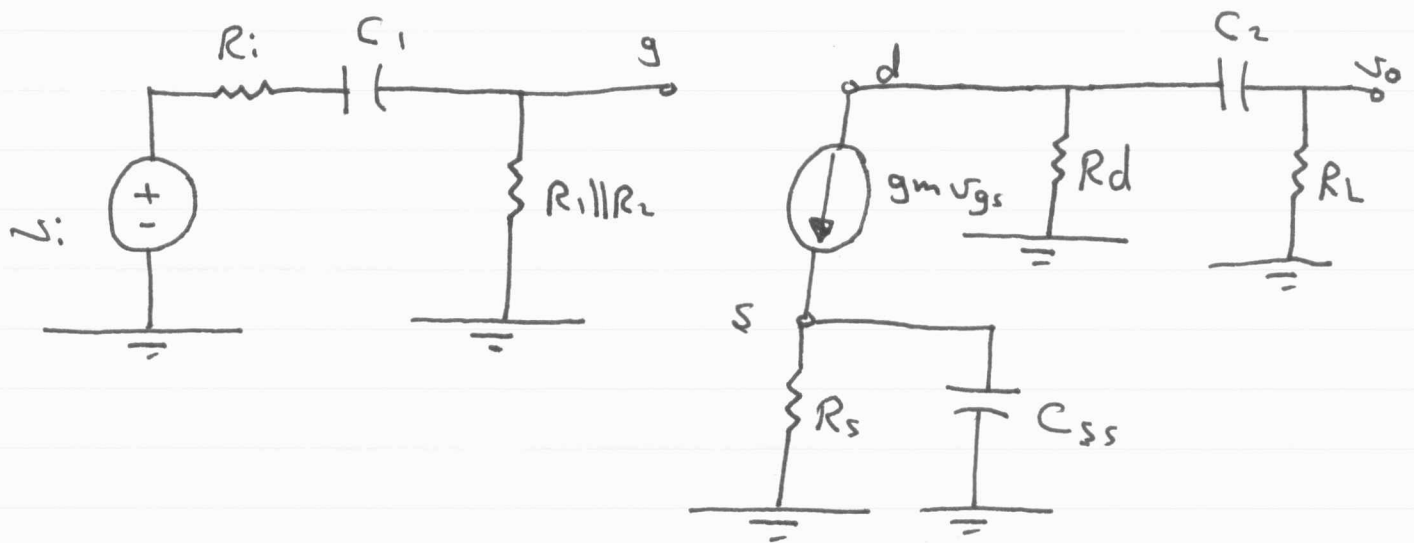Ac small signal low-frequency equivalent circuit :



$$\omega_{c1} = \frac{1}{C_1 [R_i + R_1 \parallel R_2]} = 49.9 \text{ v/s}$$

$$\omega_{c2} = \frac{1}{C_2 [R_L + R_d]} = 100 \text{ v/s}$$




$$\omega_{c_{ss}} = \frac{1}{C_{ss} \left[ R_s \parallel \frac{1}{g_m} \right]} = 1050 \text{ v/s}$$

$$\omega_{c_1} + \omega_{c_2} + \omega_{c_{ss}} > \omega_L > \omega_{c_{ss}}$$


$$1199.9 \text{ v/s} > \omega_L > 1050 \text{ v/s}$$

$$\omega_L \equiv 1059.4 \text{ v/s}$$

# Common Gate Low Frequency Analysis

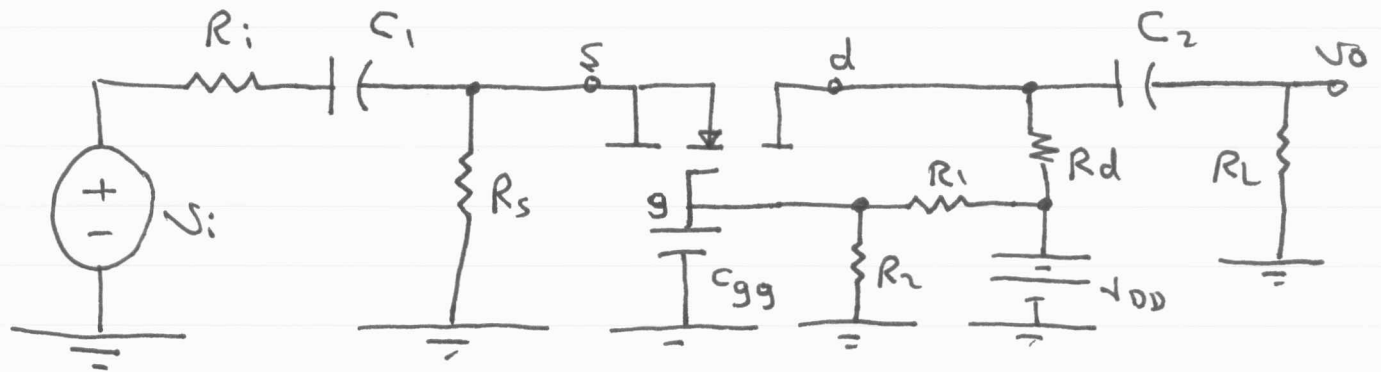

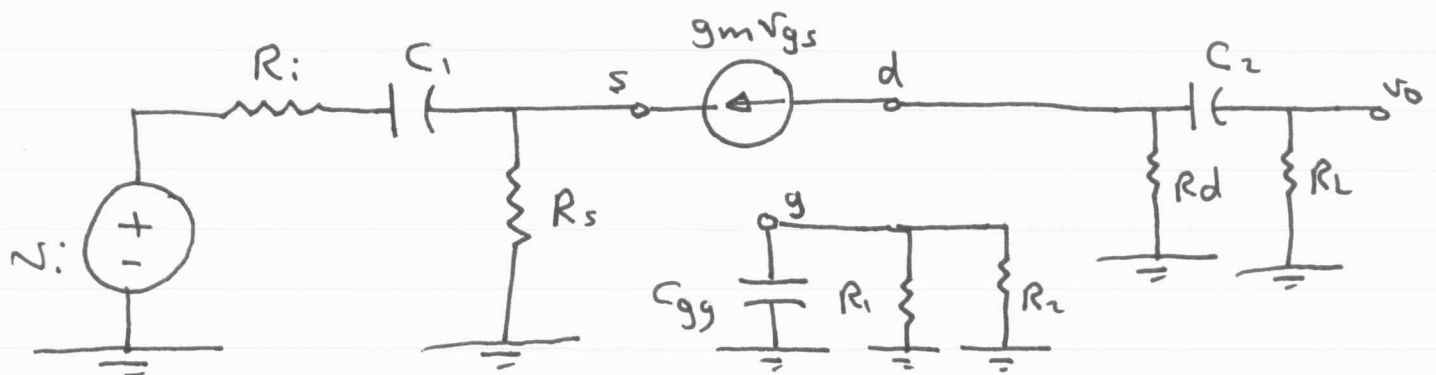Ac small signal low-frequency equivalent ckt :



$$\omega_{c1} = \frac{1}{C_1 \left[ R_i + R_s \parallel \frac{1}{g_m} \right]}$$

$$\omega_{c2} = \frac{1}{C_2 \left[ R_L + R_d \right]}$$

$$\omega_{cgg} = \frac{1}{C_{gg} \left[ R_1 \parallel R_2 \right]}$$