
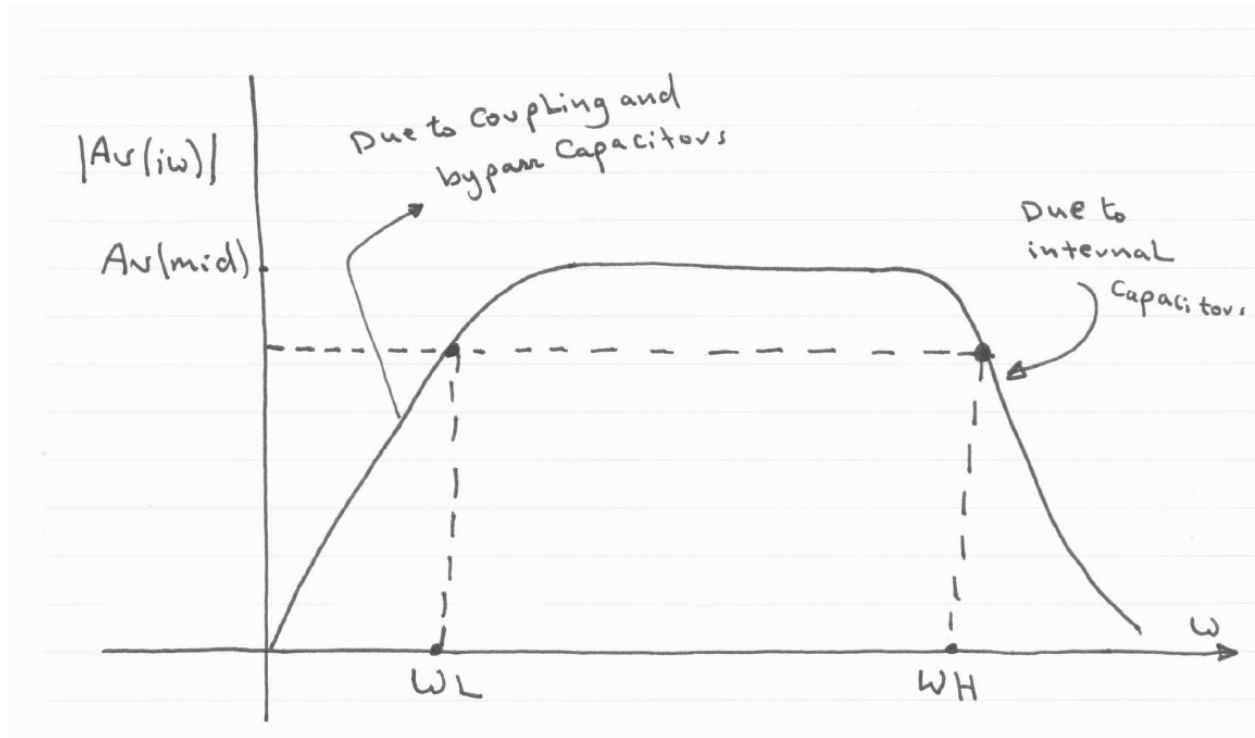



Amplifier frequency response

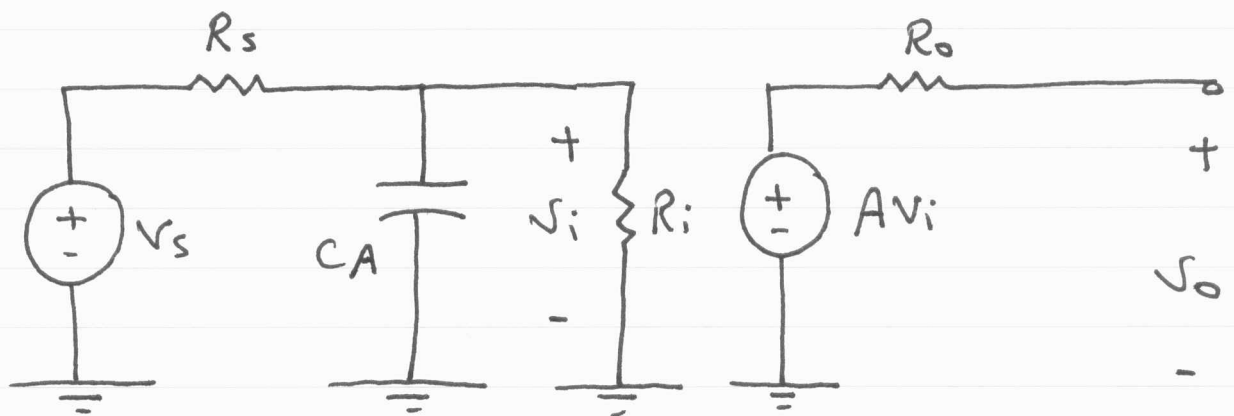

Shunt Capacitance and the high-frequency Response



1) At midband

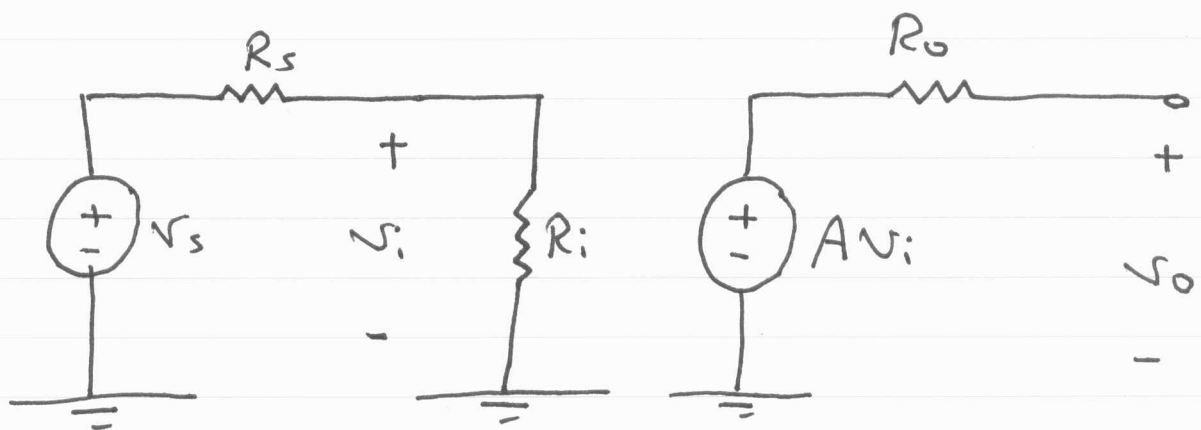


$$V_o = A V_i$$

$$V_i = \frac{R_i}{R_i + R_s} V_s$$

$$\therefore A_v(\text{mid}) = \frac{V_o}{V_s} = A \frac{R_i}{R_i + R_s}$$

2) At high frequency

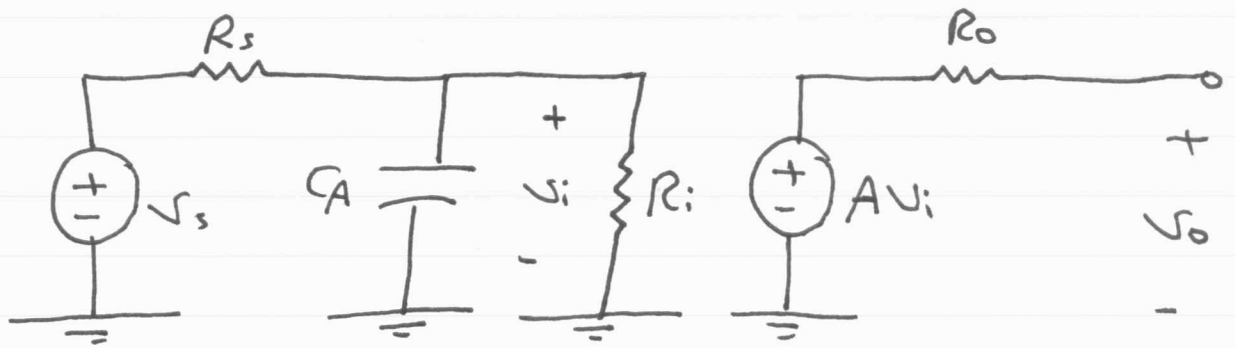

$$\vec{v}_o = A \vec{v}_i$$

$$\vec{v}_i = \frac{R_i \parallel \frac{1}{j\omega C_A}}{R_i \parallel \frac{1}{j\omega C_A} + R_s} \vec{v}_s$$

$$\therefore A_V(j\omega) = \frac{\vec{v}_o}{\vec{v}_s} = A \frac{R_i}{R_i + R_s} \frac{1}{1 + j\omega C_A (R_s \parallel R_i)}$$

$$\therefore A_V(j\omega) = A_V(\text{mid}) \frac{1}{1 + j\omega C_A (R_s \parallel R_i)}$$

$$|A_V(j\omega)| = A_V(\text{mid}) \frac{1}{\sqrt{1 + [\omega C_A (R_s \parallel R_i)]^2}}$$

a) For small ω ; $|A_V(j\omega)| = A_V(\text{mid})$

b) For large ω ; $|A_V(j\omega)| \approx 0$

c) For $\omega = \frac{1}{C_A (R_s \parallel R_i)}$; $|A_V(j\omega)| = \frac{A_V(\text{mid})}{\sqrt{2}}$

$$\therefore \omega_H = \frac{1}{C_A (R_s \parallel R_i)}$$


but $\omega_{CA} = \frac{1}{C_A R_{TH}}$

$$\omega_{CA} = \frac{1}{C_A (R_s \parallel R_i)}$$

$$\therefore \omega_H = \omega_{CA}$$

ω_H : The Upper Cut off frequency of the CRT

ω_{CA} : The Corner frequency of CA

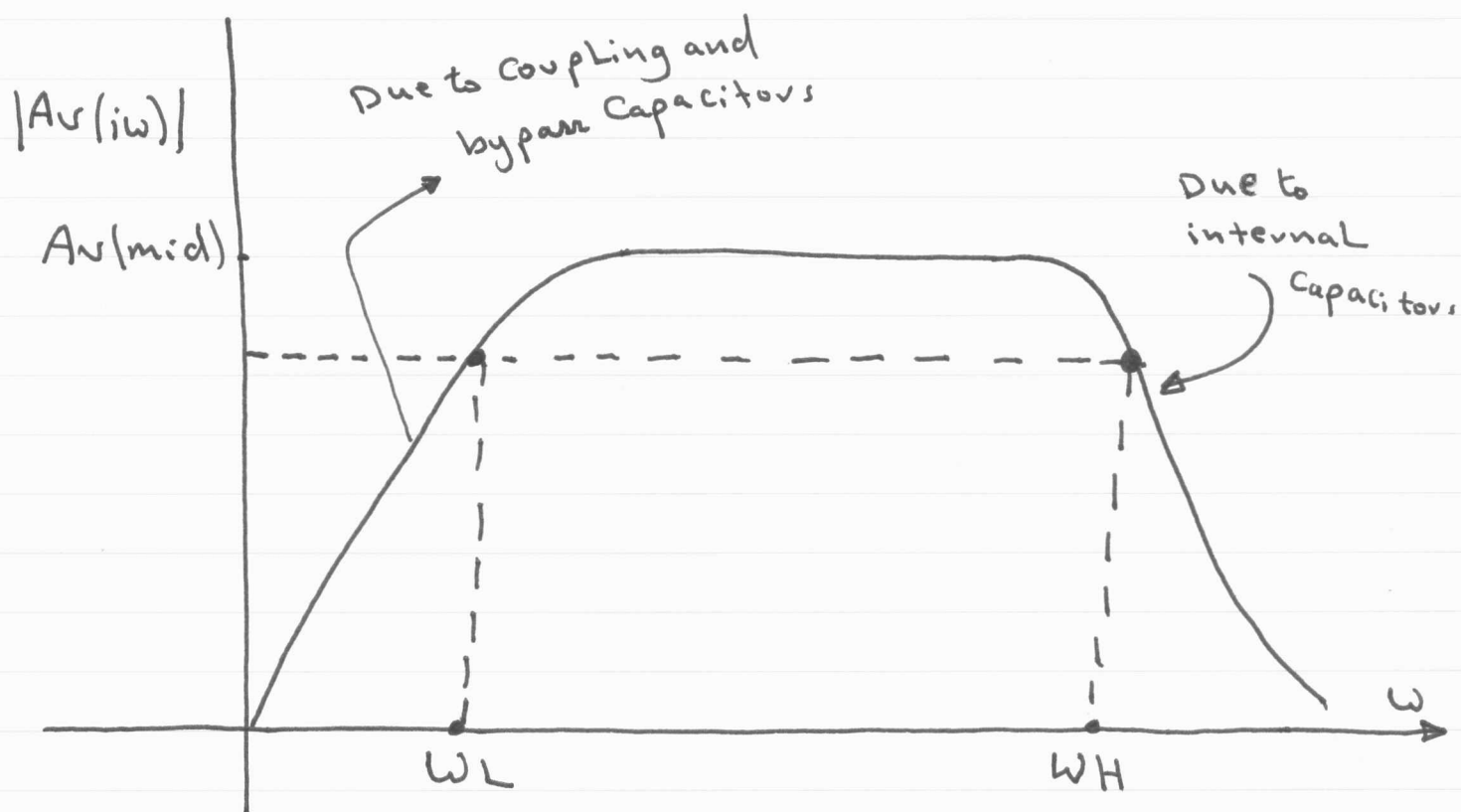

$$A_v(j\omega) = A_v(\text{mid}) \frac{1}{1 + j\omega C_A (R_s \parallel R_i)}$$

$$\omega_{CA} = \frac{1}{C_A (R_s \parallel R_i)}$$

$$\therefore A_v(j\omega) = A_v(\text{mid}) \frac{1}{1 + \frac{j\omega}{\omega_{CA}}}$$

If we have two internal capacitors :

$$A_v(j\omega) = A_v(\text{mid}) \frac{1}{\left(1 + \frac{j\omega}{\omega_A}\right) \left(1 + \frac{j\omega}{\omega_B}\right)}$$

if $\omega_A = 1 \text{ Mv/s}$, and $\omega_B = 5 \text{ Mv/s}$

$$\therefore \omega_H = 0.964 \text{ Mv/s}$$

\therefore if $\omega_A < \omega_B$; $\omega_H < \omega_A$

$$A_V(j\omega) = \frac{A_V(\text{mid})}{\left(1 + \frac{j\omega}{\omega_A}\right) \left(1 + \frac{j\omega}{\omega_B}\right)}$$

assuming $\omega_A < \omega_B$

$$\left| A_V(j\omega_H) \right| = \frac{A_V(\text{mid})}{\left| \left(1 + \frac{j\omega_H}{\omega_A}\right) \left(1 + \frac{j\omega_H}{\omega_B}\right) \right|} = \frac{A_V(\text{mid})}{\sqrt{2}}$$

$$\therefore \left| \left(1 + \frac{j\omega_H}{\omega_A}\right) \left(1 + \frac{j\omega_H}{\omega_B}\right) \right| = \sqrt{2}$$

Since $\omega_H < \omega_A$, and $\omega_H \ll \omega_B$

$$\therefore \frac{j\omega_H}{\omega_B} \rightarrow 0$$

$$\left| \left(1 + \frac{j\omega_H}{\omega_A}\right) \right| = \sqrt{2}$$

$$\sqrt{1 + \left(\frac{\omega_H}{\omega_A}\right)^2} = \sqrt{2}$$

$$\therefore \omega_H = \omega_A \quad (\text{Upper Limit})$$

$$\left| \left(1 + \frac{j\omega_H}{\omega_A} \right) \left(1 + \frac{j\omega_H}{\omega_B} \right) \right| = \sqrt{2}$$

$$\left| 1 + j\omega_H \left(\frac{1}{\omega_A} + \frac{1}{\omega_B} \right) - \frac{\omega_H \cdot \omega_H}{\omega_A \omega_B} \right| = \sqrt{2}$$

Since $\frac{\omega_H}{\omega_A} < 1$; and $\frac{\omega_H}{\omega_B} \ll 1$

$$\therefore \frac{\omega_H}{\omega_A} \cdot \frac{\omega_H}{\omega_B} \ll \ll 1$$

$$\left| 1 + j\omega_H \left(\frac{1}{\omega_A} + \frac{1}{\omega_B} \right) \right| = \sqrt{2}$$

$$\therefore \omega_H = \frac{1}{\frac{1}{\omega_A} + \frac{1}{\omega_B}}$$

(Lower Limit)

∴ if $\omega_A < \omega_B$

$$\frac{1}{\frac{1}{\omega_A} + \frac{1}{\omega_B}} < \omega_H < \omega_A$$

if $\omega_A = 1 \text{ Mv/s}$, $\omega_B = 5 \text{ Mv/s}$

$$\omega_H \cong 0.964 \text{ Mv/s}$$

$$\frac{1}{\frac{1}{\omega_A} + \frac{1}{\omega_B}} < \omega_H < \omega_A$$

$$0.83 \text{ Mv/s} < \omega_H < 1 \text{ Mv/s}$$

$$0.83 \text{ Mv/s} < 0.964 \text{ Mv/s} < 1 \text{ Mv/s}$$