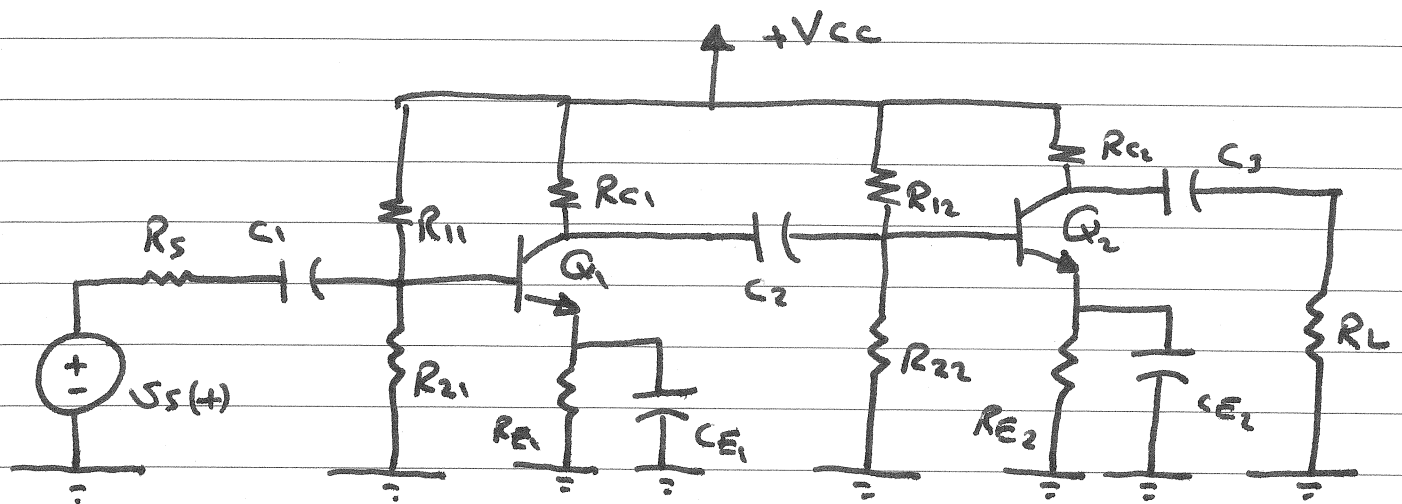


Multistage Amplifier Frequency Response



$$\begin{aligned}
 R_S &= 0.3\text{K} & R_{12} &= 123\text{K} \\
 R_{11} &= 123\text{K} & R_{22} &= 58\text{K} \\
 R_{21} &= 58\text{K} & R_{E2} &= 5\text{K} \\
 R_{E1} &= 5\text{K} & R_{C2} &= 8\text{K} \\
 R_{C1} &= 8\text{K} & R_L &= 2\text{K}
 \end{aligned}$$

$$\begin{aligned}
 C_{E1} &= 250\mu\text{F} & C_1 &= 10\mu\text{F} & C_3 &= 7.5\mu\text{F} \\
 C_{E2} &= 1150\mu\text{F} & C_2 &= 5\mu\text{F}
 \end{aligned}$$



$$h_{fe1} = h_{fe2} = 350 \quad r_{X1} = r_{X2} = 50\Omega$$

$$h_{ie1} = h_{ie2} = 9\text{K}$$



$$c_{be1} = c_{be2} = 18.7\text{pF}$$

$$c_{bc1} = c_{bc2} = 2\text{pF}$$

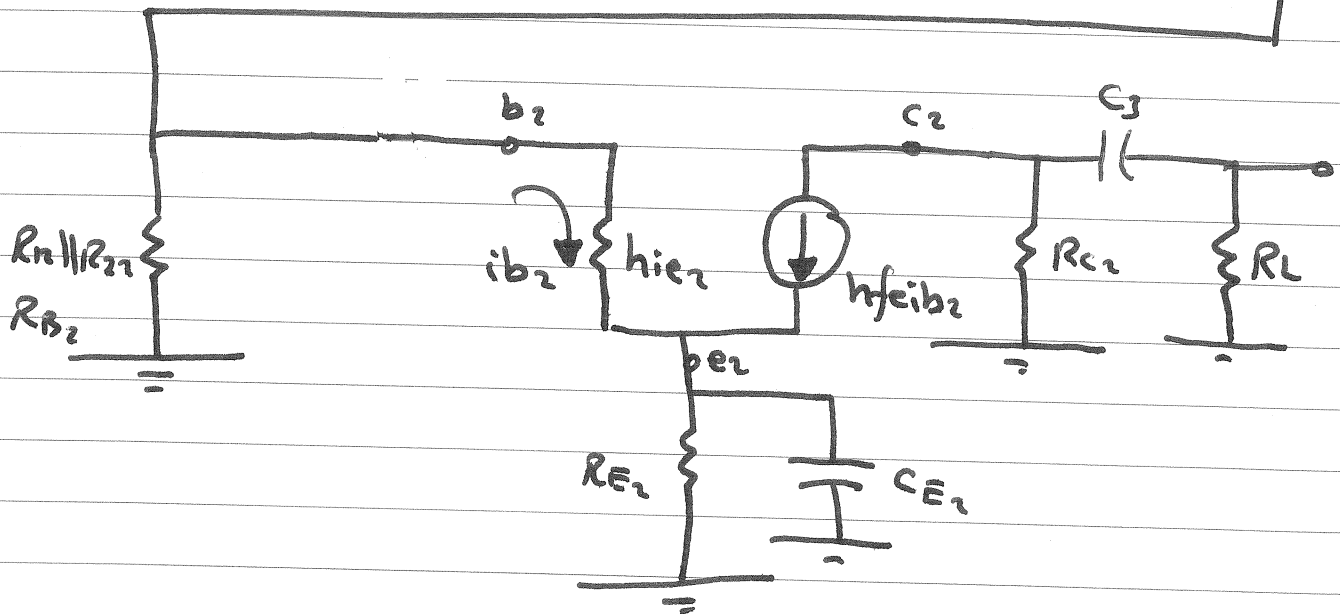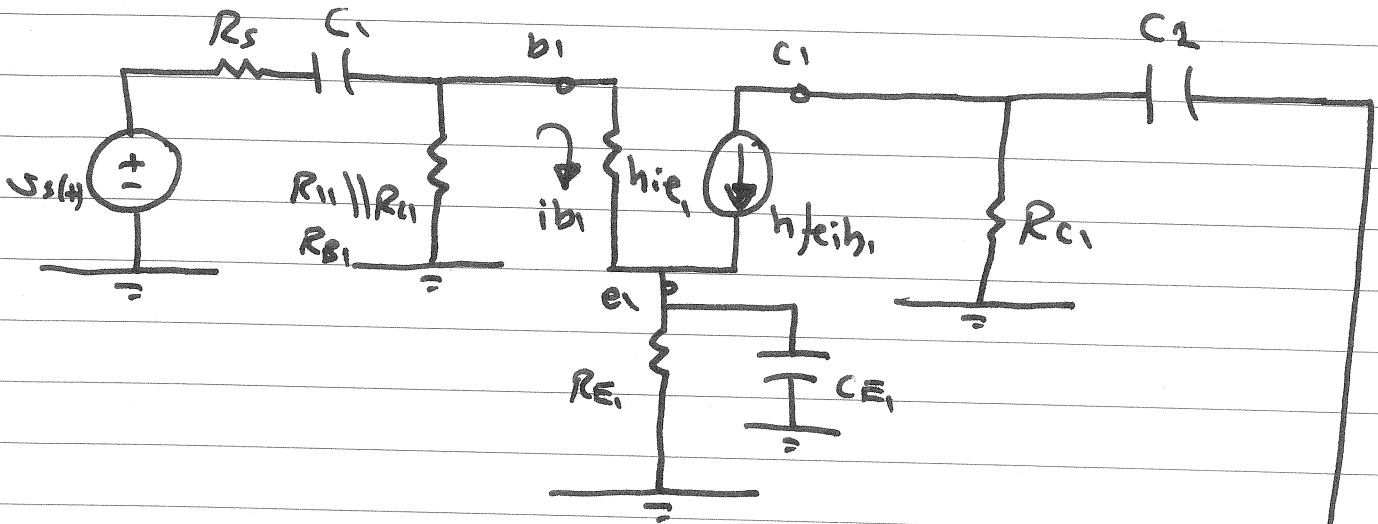ac small signal Low frequency equivalent ckr



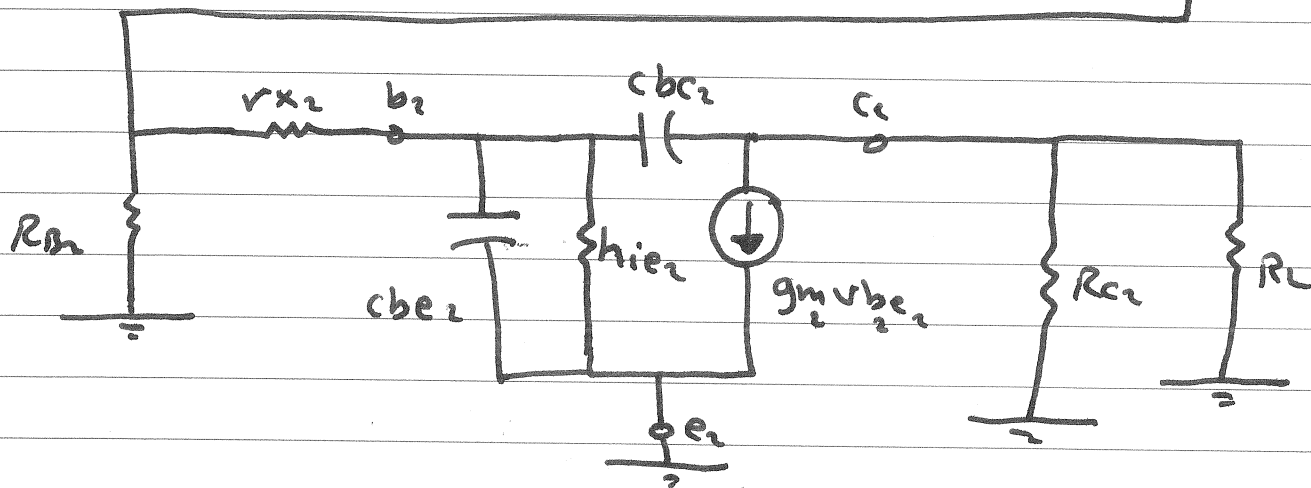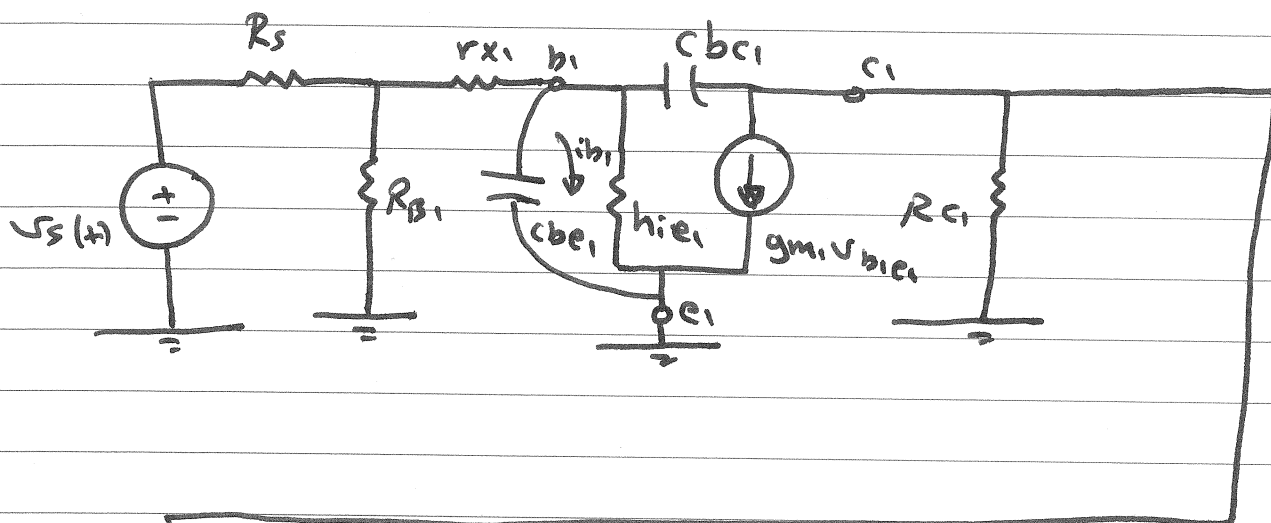ac small signal high-frequency equivalent ckt



An approximation for ω_L :

$$\omega_{C_1} = \frac{1}{C_1 (R_s + R_{B1} \parallel h_{ie1})} = 13.11 \text{ v/s} \quad ; R_{B1} = 58k \parallel 123k$$

$$\omega_{C_2} = \frac{1}{C_2 (R_{C1} + R_{B2} \parallel h_{ie2})} = 13.05 \text{ v/s} \quad R_{B2} \parallel R_{B1}$$

$$\omega_{C_3} = \frac{1}{C_3 (R_{C2} + R_L)} = 13.33 \text{ v/s}$$

$$\omega_{CE1} = \frac{1}{C_{E1} (R_{E1} \parallel \frac{h_{ie1} + R_{B1} \parallel R_s}{1 + h_{fe1}})} = 151. \text{ v/s}$$

$$\omega_{CE2} = \frac{1}{C_{E2} (R_{E2} \parallel \frac{h_{ie2} + R_{B2} \parallel R_{C1}}{1 + h_{fe2}})} = 19.68 \text{ v/s}$$

$$\therefore 211 \text{ v/s} > \omega_L > 151 \text{ v/s}$$

$$\omega_L = 169 \text{ v/s}$$

An approximation for ω_H :

$$1) \tau_{bc1} = C_{bc1} \cdot R_{bc1}$$

$$R_{bc1} = R_{L1} + (1 + g_{m1} R_{L1}) R_{S1}$$

$$R_{L1} = R_{C1} \parallel R_{B2} \parallel (r_{x2} + h_{ie2}) = 8k \parallel 39.4k \parallel (0.05k + 9k) = 3.83k$$

$$R_{S1} = h_{ie1} \parallel (r_{x1} + R_s \parallel R_{B1}) = 9k \parallel (0.05k + 0.3k \parallel 39.4k) = 0.335k$$

$$\tau_{bc1} = 108.2 \text{ ns}$$

$$\omega_{bc1} = 9.24 \text{ M v/s}$$

$$2) \tau_{bc2} = C_{bc2} R_{bc2}$$

$$R_{be1} = R_{s1} = 0.335k$$

$$\tau_{be1} = 6.3ns$$

$$\omega_{be1} = 158.7Mv/s$$

$$3) \tau_{bc2} = C_{bc2} R_{bc2}$$

$$R_{bc2} = R_{L2} + R_{s2} (1 + g_{m2} R_{L2})$$

$$R_{s2} = h_{ie2} \parallel (v_{x2} + R_{c1} \parallel R_{B2}) = 9k \parallel (0.05k + 8k \parallel 58.4k) = 3.84k$$

$$R_{L2} = R_{c2} \parallel R_L = 1.6k$$

$$\tau_{bc2} = 489ns$$

$$\omega_{bc2} = 2.044Mv/s$$

$$4) \tau_{be2} = C_{be2} R_{be2}$$

$$R_{be2} = R_{s2} = 3.84k$$

$$\tau_{be2} = 71.8ns$$

$$\omega_{be2} = 13.929Mv/s$$

$$\frac{1}{\tau_{be1} + \tau_{be2} + \tau_{bc1} + \tau_{bc2}} < \omega_H < 2.044Mv/s$$

$$1.481 < \omega_H < 2.044Mv/s$$

$$\omega_H = 1.504Mv/s$$