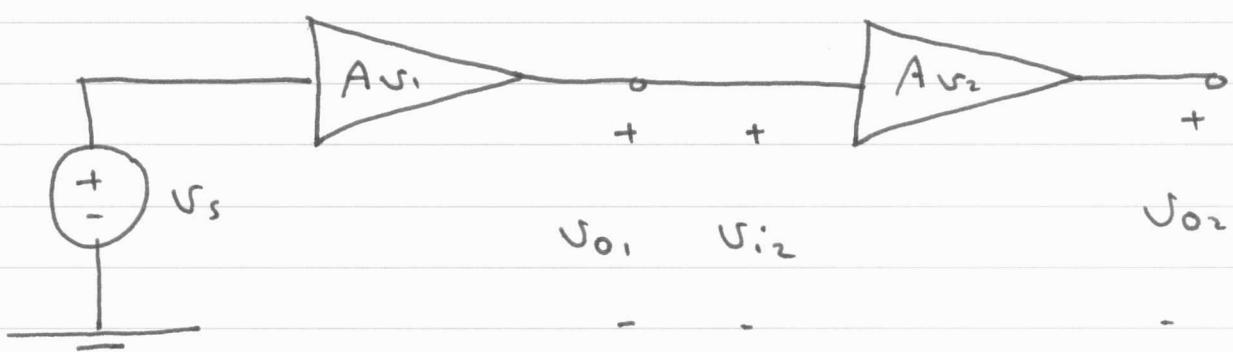


Multistage Amplifiers

1. Additional Amplification can be required.
2. Improving the performance of the amplifier (high input impedance, high gain, small output impedance).
3. Increasing the Bandwidth.



$$N_{o2} = A_{v2} N_s$$

$$N_{i2} = N_{i1} \quad (\text{in cascade})$$

$$N_{o1} = A_{v1} N_s$$

$$\therefore \frac{N_{o2}}{N_s} = A_{v1} \cdot A_{v2}$$

* When the output of one amplifier stage is connected to the input of another, the amplifier stages are said to be in Cascade.


$$* A_{\text{ST}} = A_{\text{S1}} \cdot A_{\text{S2}} \cdot A_{\text{S3}} \cdot \dots \cdot A_{\text{Sn}}$$

$A_{\text{S1}}, A_{\text{S2}},$ and A_{Sn} are the in-circuit gains.

Methods of Coupling

- 1) Capacitor Coupling
- 2) Direct Coupling
- 3) Transformer Coupling

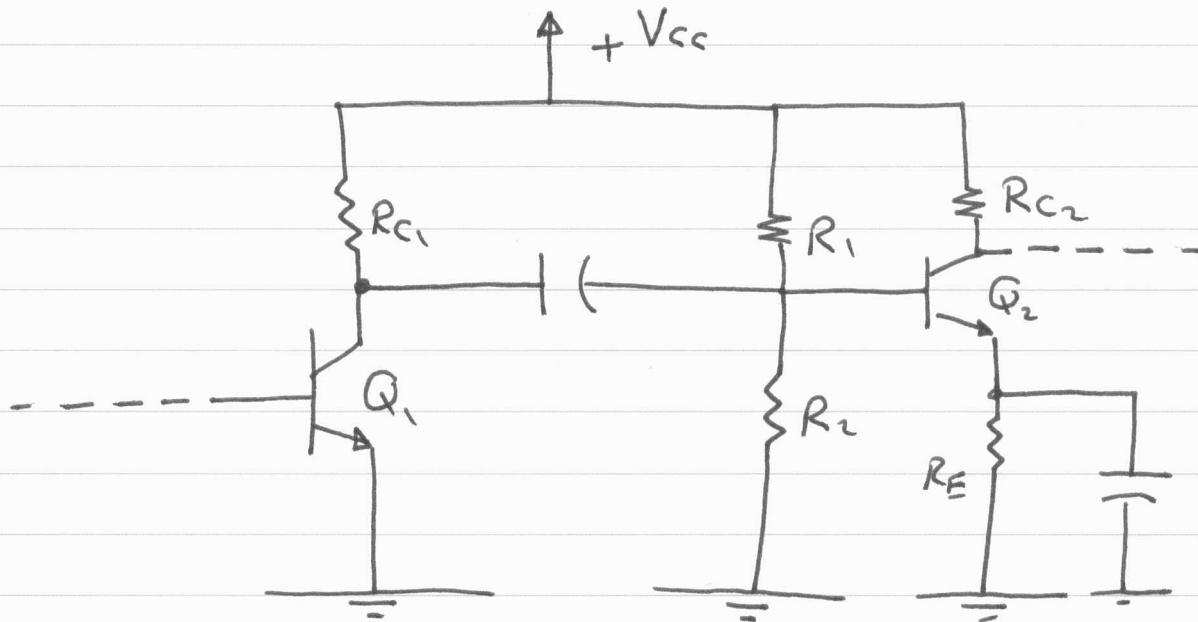I) Capacitor Coupled Multistage Amplifier




- The coupling capacitor blocks the flow of DC current while it permits the flow of ac signal between stages.
- It makes it possible to have a dc bias voltage at the output of one stage that is different from the dc bias voltage at the input to the next stage (stage isolation).

Disadvantages


- It effects the low-frequency response of the amplifier
- Is not used in integrated circuits, because it is difficult and uneconomical to fabricate Capacitors on a chip.

Example

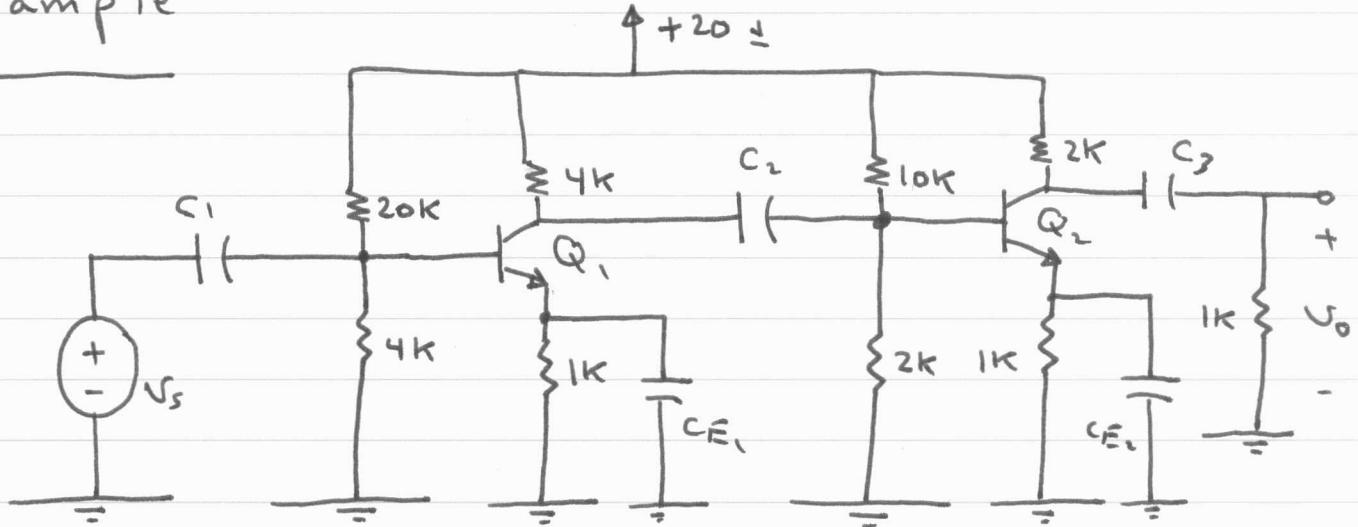

$$\beta_1 = \beta_2 = 50$$

Dc Analysis

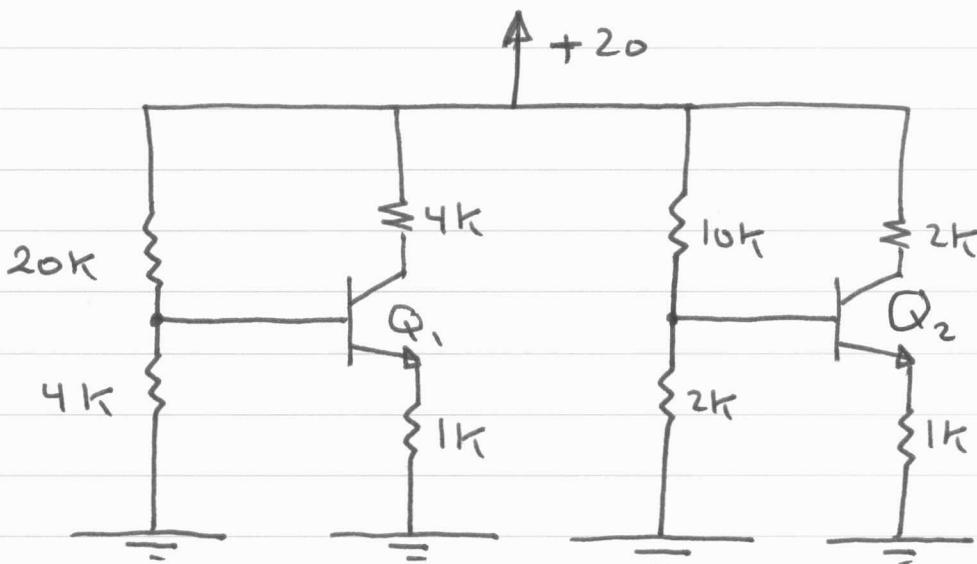

$$R_{TH1} = 4k \parallel 20k = 3.33k$$

$$V_{TH1} = \frac{4k}{4k+20k} (20) = 3.33V$$


$$I_{E1} = 2.47mA \rightarrow h_{ie1} \approx 0.51k$$

$$R_{TH2} = 2k \parallel 10k = 1.67k$$

$$V_{TH2} = \frac{2k}{2k+10k} (20) = 3.33V$$

$$I_{E2} = 2.55mA \rightarrow h_{ie2} \approx 0.51k$$

Ac small signal equivalent circuit

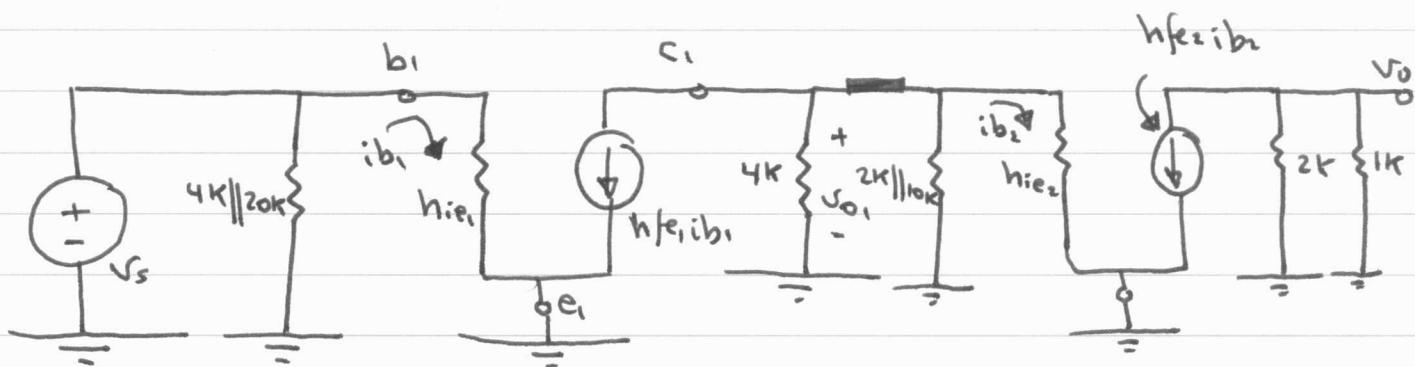

$$Av_T = Av_1 \cdot Av_2$$

$$- Av_1 = \frac{V_{o1}}{V_s}$$

$$V_{o1} = -h_{fe1}ib_1 (4k \parallel 2k \parallel 10k \parallel h_{ie1})$$

$$ib_1 = \frac{V_s}{h_{ie1}}$$

$$\therefore Av_1 = -35.14$$

$$- Av_2 = \frac{V_{o2}}{V_{i2}} = \frac{V_{o2}}{V_{o1}} = \frac{V_o}{V_{o1}}$$

$$V_{o2} = -h_{fe2}ib_2 (2k \parallel 1k)$$

$$ib_2 = \frac{V_{o1}}{h_{ie2}}$$

$$\therefore Av_2 = -66.66$$

$$\therefore Av_T = Av_1 \cdot Av_2$$

$$Av_T = 2342$$