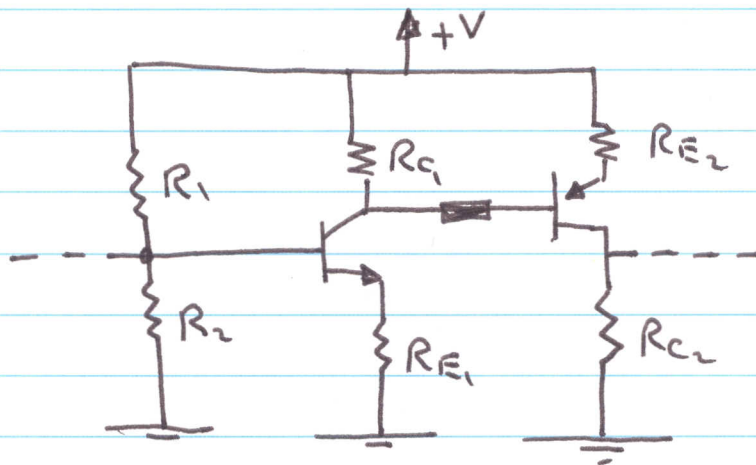


## 2) Direct-coupled multistage Amplifier



- Used in differential and operational amplifiers
- Used in Low and high frequency applications


### Disadvantages

Any change in the dc voltage at the output of one stage produce an identical change in dc voltage at the input to the next stage

\* We must use  $R_E$

\* We must use alternating transistor types (npn, pnp)

# Darlington Compound Configuration

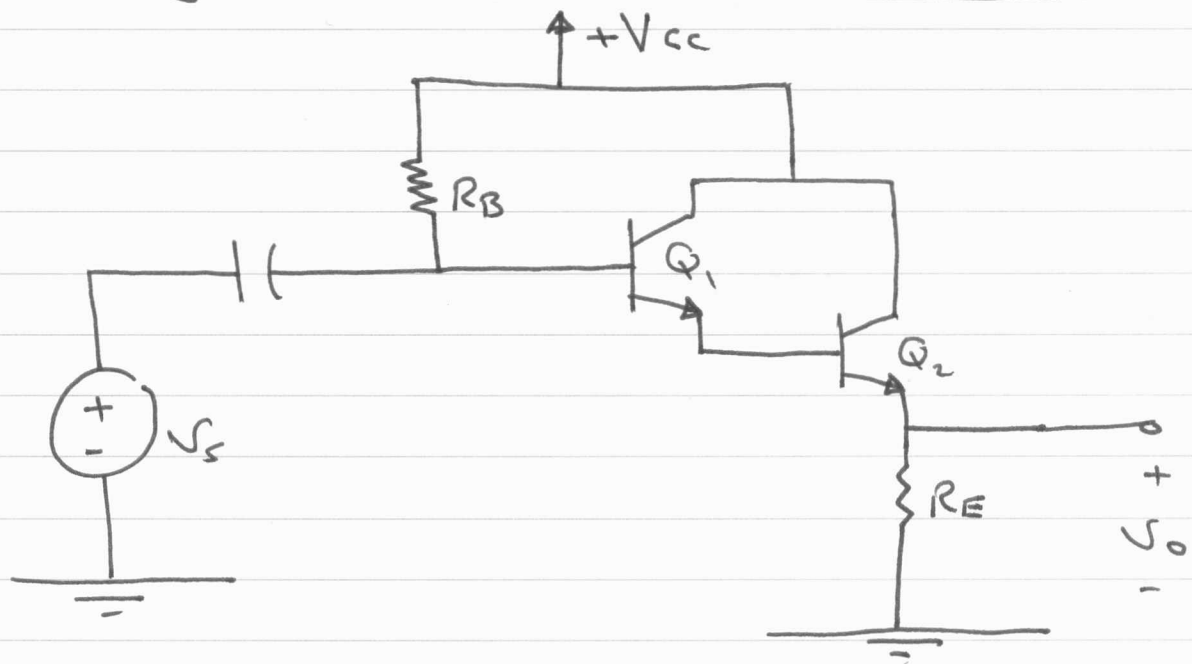

## Dc Analysis


$$V_{CC} = R_B I_{B1} + V_{BE1} + V_{BE2} + R_E I_{E2}$$

$$I_{E2} = (\beta_2 + 1) I_{B2}$$


$$I_{B2} = I_{E1}$$

$$I_{E1} = (\beta_1 + 1) I_{B1}$$
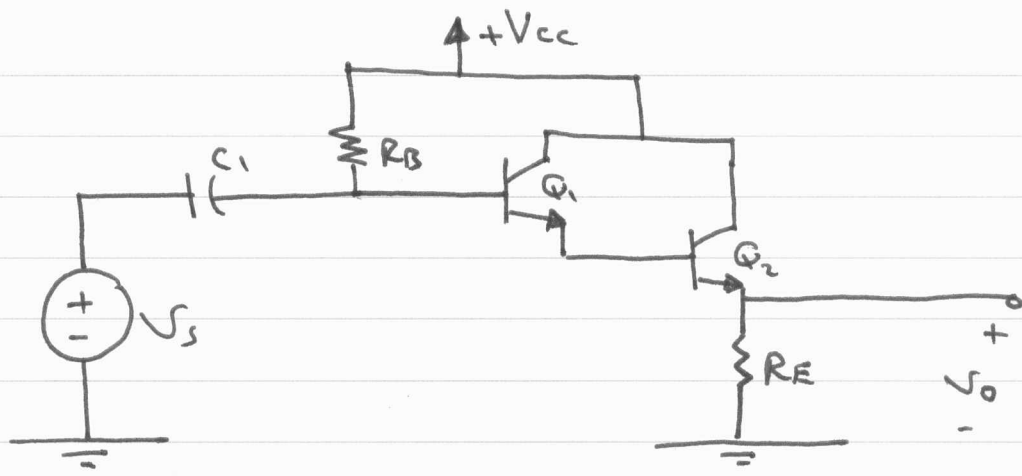
$$\therefore I_{E2} = (\beta_2 + 1)(\beta_1 + 1) I_{B1}$$



Ac small signal equivalent circuit

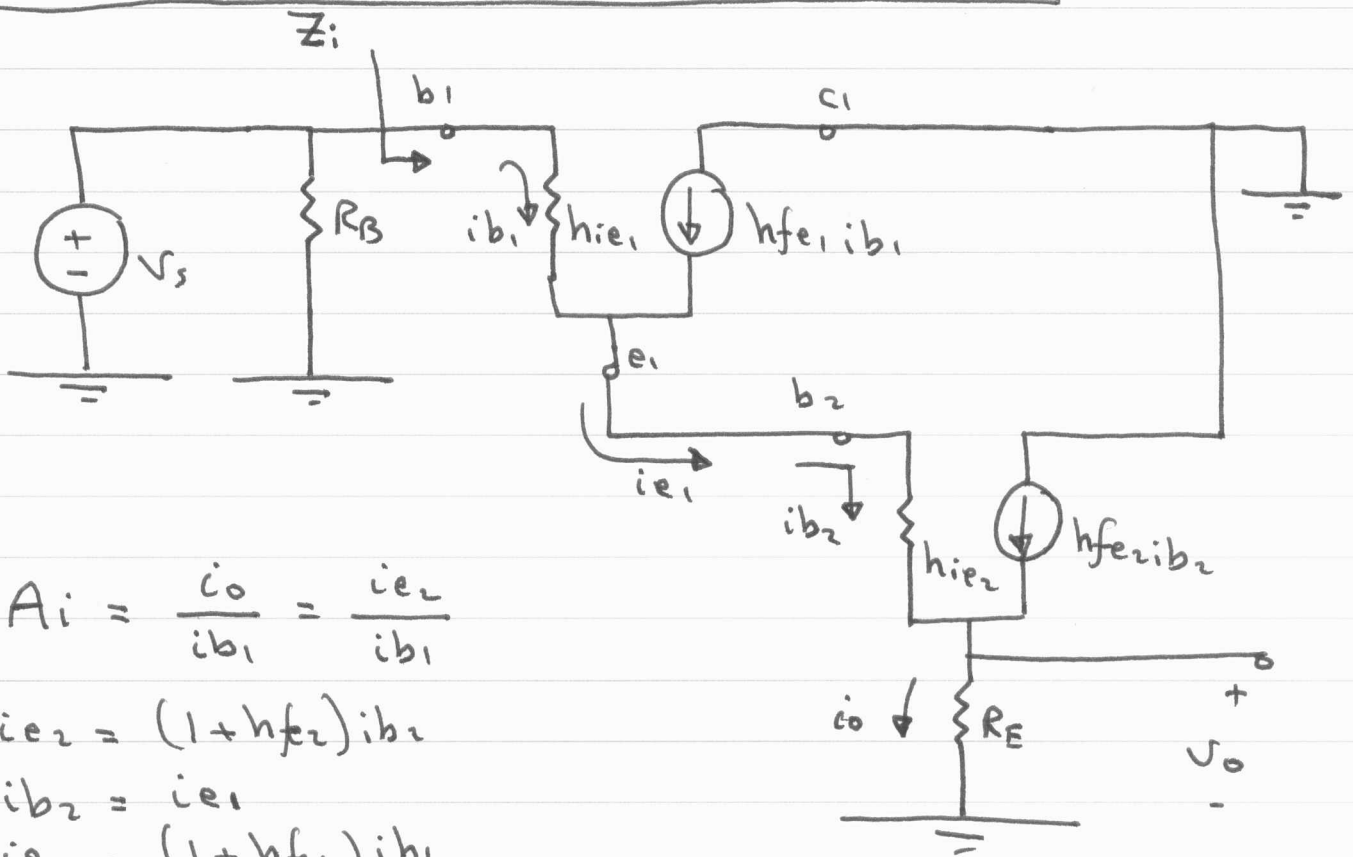

$$- A_i = \frac{i_o}{i_{b1}} = \frac{i_{e2}}{i_{b1}}$$

$$i_{e2} = (1 + h_{fe2}) i_{b2}$$

$$i_{b2} = i_{e1}$$

$$i_{e1} = (1 + h_{fe1}) i_{b1}$$




$$\therefore A_i = \frac{i_o}{i_{b1}} = (1 + h_{fe2})(1 + h_{fe1})$$

$$- A_v = \frac{V_o}{V_s}$$

$$V_o = R_E i_o$$

$$i_o = (1 + h_{fe2})(1 + h_{fe1}) i_{b1}$$

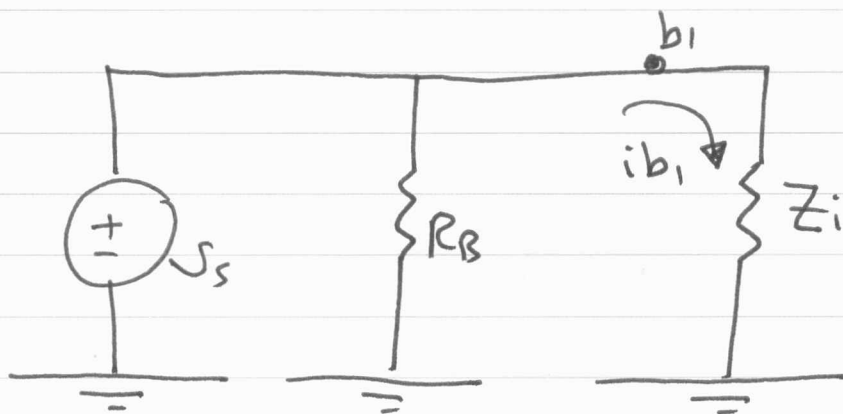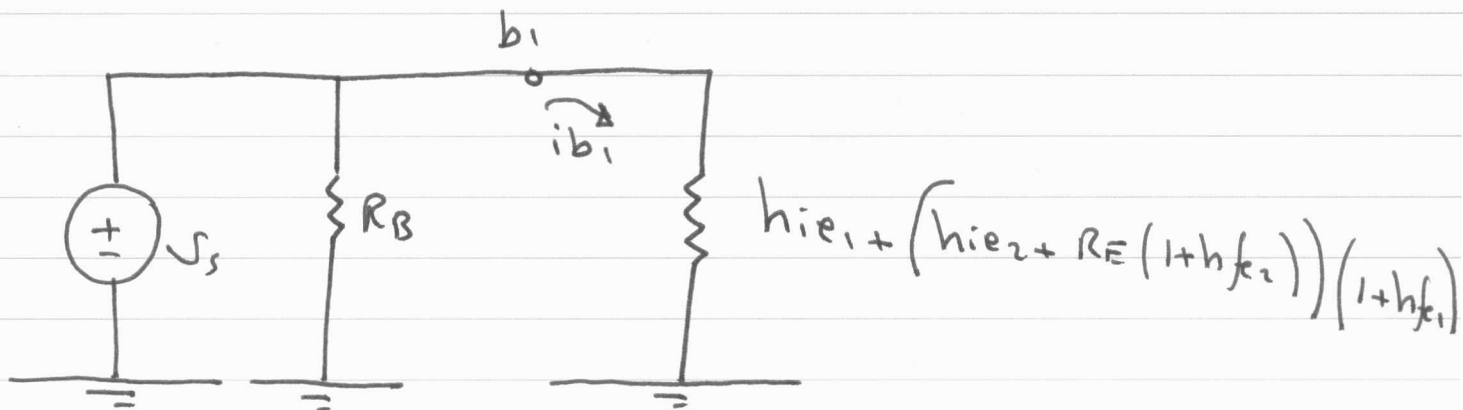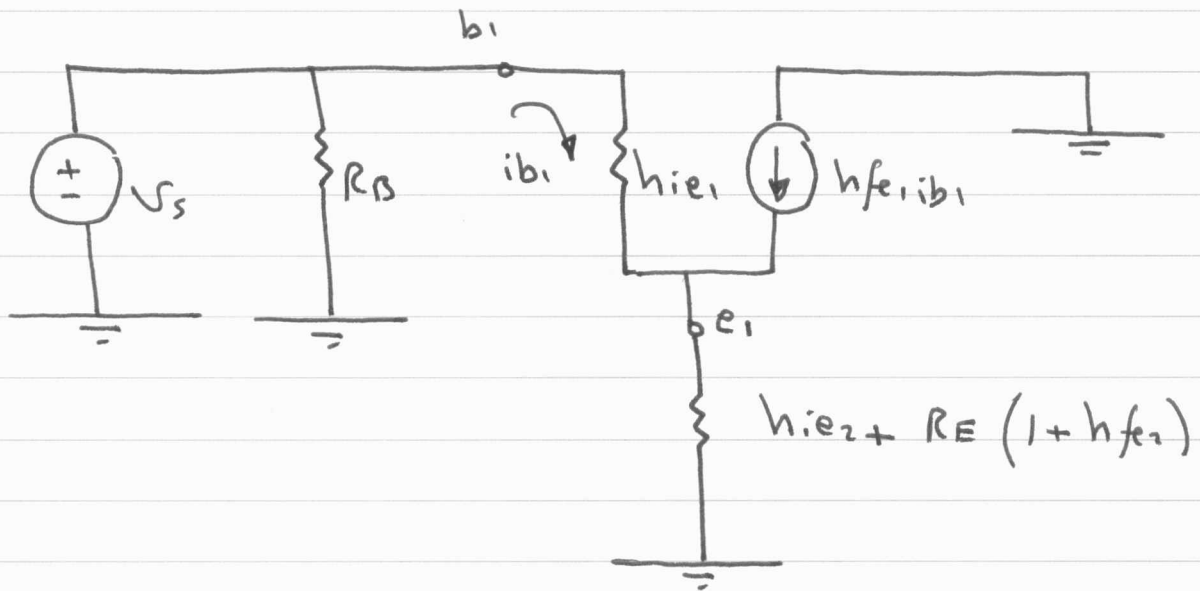To find  $i_{b1}$   $\longrightarrow$  base, equivalent circuit



$$i_{b1} = \frac{V_s}{Z_i}$$

$$Z_i = h_{ie1} + \left[ h_{ie2} + R_E(1+h_{fe2}) \right] \left[ 1+h_{fe1} \right]$$

$$\therefore A_v = \frac{R_E (1 + h_{fe2}) (1 + h_{fe1})}{h_{ie1} + (R_E (1 + h_{fe2}) + h_{ie2}) (1 + h_{fe1})} < 1$$

- To find  $Z_o$ , set  $v_s = 0$

$$Z_o = \frac{\frac{h_{ie1}}{h_{fe1+1}} + h_{ie2}}{h_{fe2+1}} \parallel R_E$$

$$\therefore A_i > 1$$


$$A_v < 1$$

$Z_i$  very very Large


$Z_o$  very very small

modified Buffer
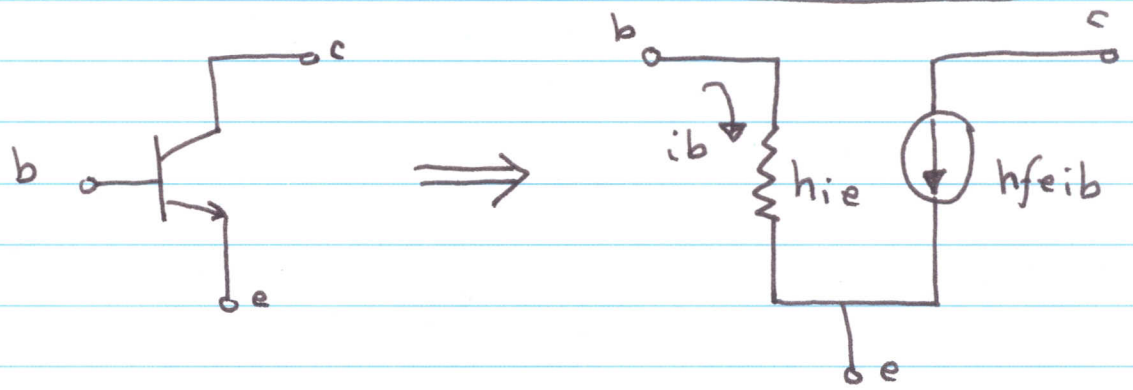
## Ac Small signal equivalent circuit of the BJT


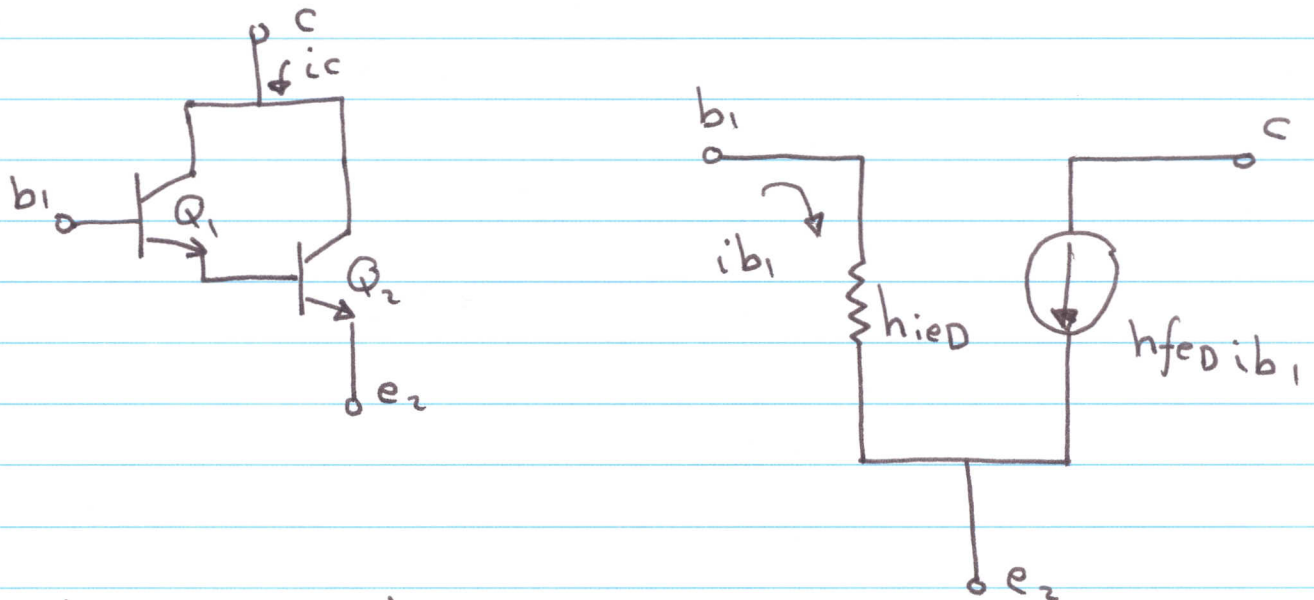
## Ac small signal equivalent circuit of the Darlington :



$$h_{ieD} = 2h_{ie1}$$

$$h_{feD} = h_{fe1} \cdot h_{fe2}$$

$$h_{feD} = \frac{i_c}{i_{b1}}$$

$$h_{ieD} = Z_i \text{ with } R_E = 0$$

$$h_{feD} = \frac{i_c}{i_{b1}}$$

$$i_c = i_{c1} + i_{c2}$$

$$i_c = h_{fe1} i_{b1} + h_{fe2} i_{b2}$$

$$i_c = h_{fe1} i_{b1} + h_{fe2} i_{e1}$$

$$i_c = h_{fe1} i_{b1} + h_{fe2} (1 + h_{fe1}) i_{b1}$$

$$i_c = [h_{fe1} + h_{fe2} + h_{fe2} h_{fe1}] i_{b1}$$

$$\therefore h_{feD} = h_{fe1} + h_{fe2} + h_{fe1} h_{fe2}$$

$$\therefore h_{feD} \approx h_{fe1} h_{fe2}$$

---

$$h_{ieD} = Z_i \Big|_{R_E = 0}$$

$$Z_i = h_{ie1} + \left( h_{ie2} + R_E (1 + h_{fe2}) \right) (1 + h_{fe1})$$

$$\therefore h_{ieD} = h_{ie1} + (1 + h_{fe1}) h_{ie2}$$

$$= h_{ie1} + (1 + h_{fe1}) \frac{(1 + h_{fe2}) \cancel{I_{E2}} \cancel{V_T}}{I_{E2}}$$

$$= h_{ie1} + (1 + h_{fe1}) \frac{(1 + h_{fe2}) \cancel{V_T}}{(1 + h_{fe2}) I_{E1}}$$

$$\therefore h_{ieD} = h_{ie1} + \frac{(1 + h_{fe1}) r_T}{\beta_1}$$


$$h_{ieD} = h_{ie1} + h_{ie1}$$

$$h_{ieD} = 2h_{ie1}$$



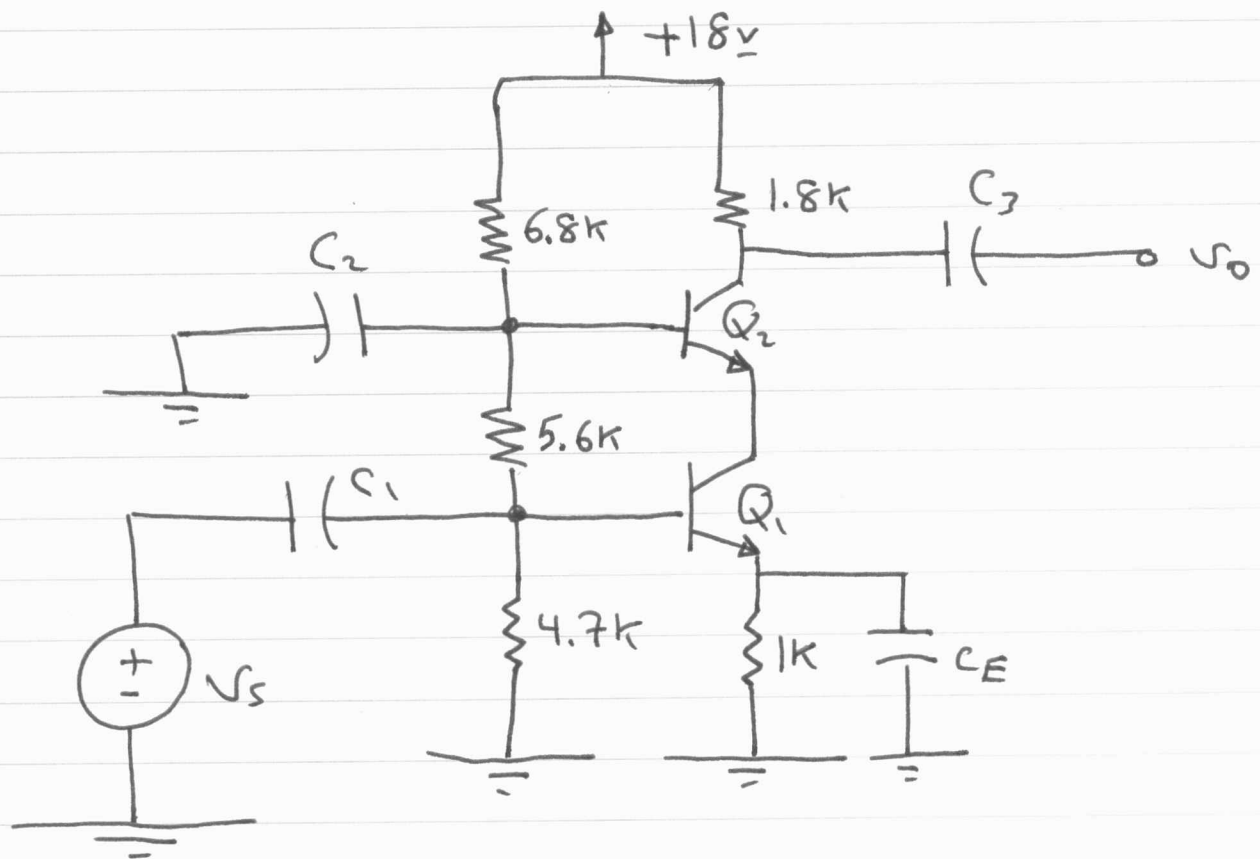
# Cascode Amplifier

- Used to amplify video signal
- It has a wide Bandwidth
- It Consists of a CE and CB stager  
or CS and CG stager



$$\beta_1 = \beta_2 = 100$$

# Dc Analysis

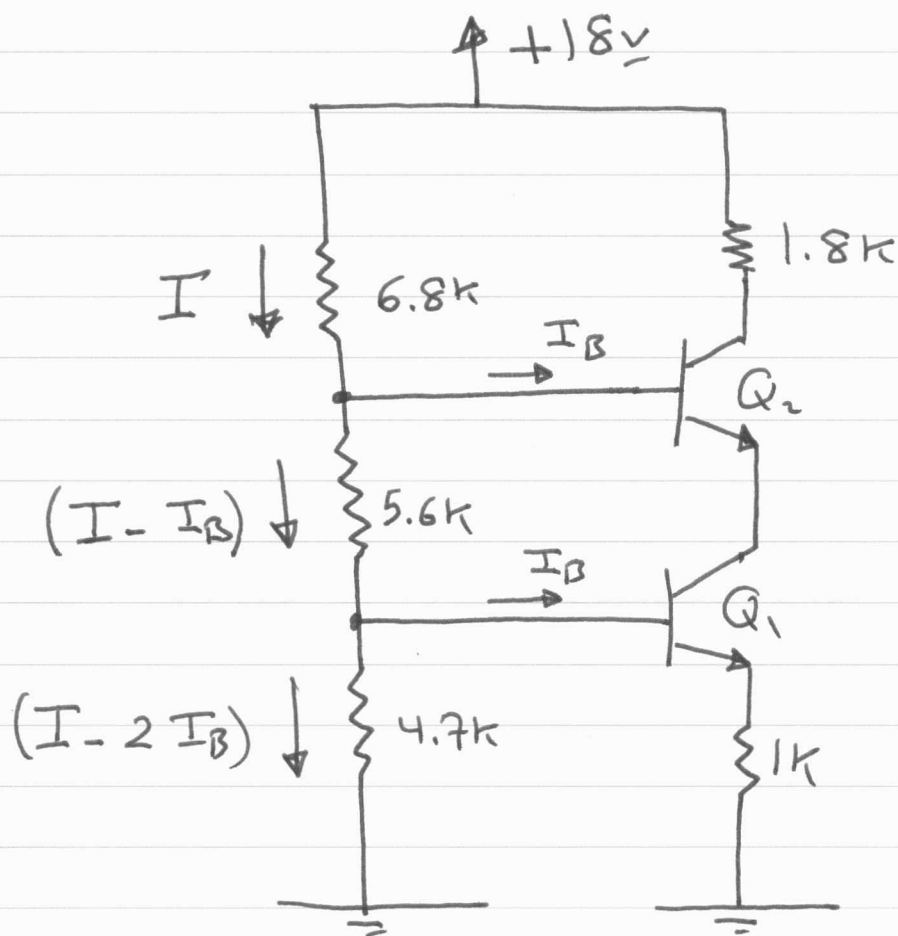

$$I_{C1} = I_{E2} \approx I_{C2}$$

and since  $\beta_1 = \beta_2$


$$I_{B1} = I_{B2} = I_B$$

$$18 = 6.8k I + 5.6k (I - I_B) + 4.7k (I - 2I_{B2})$$


$$18 = 6.8k I + 5.6k (I - I_B) + V_{BE1} + 1k I_{E1}$$

Solving for  $I_E = 4mA$

# Ac Small Signal Analysis

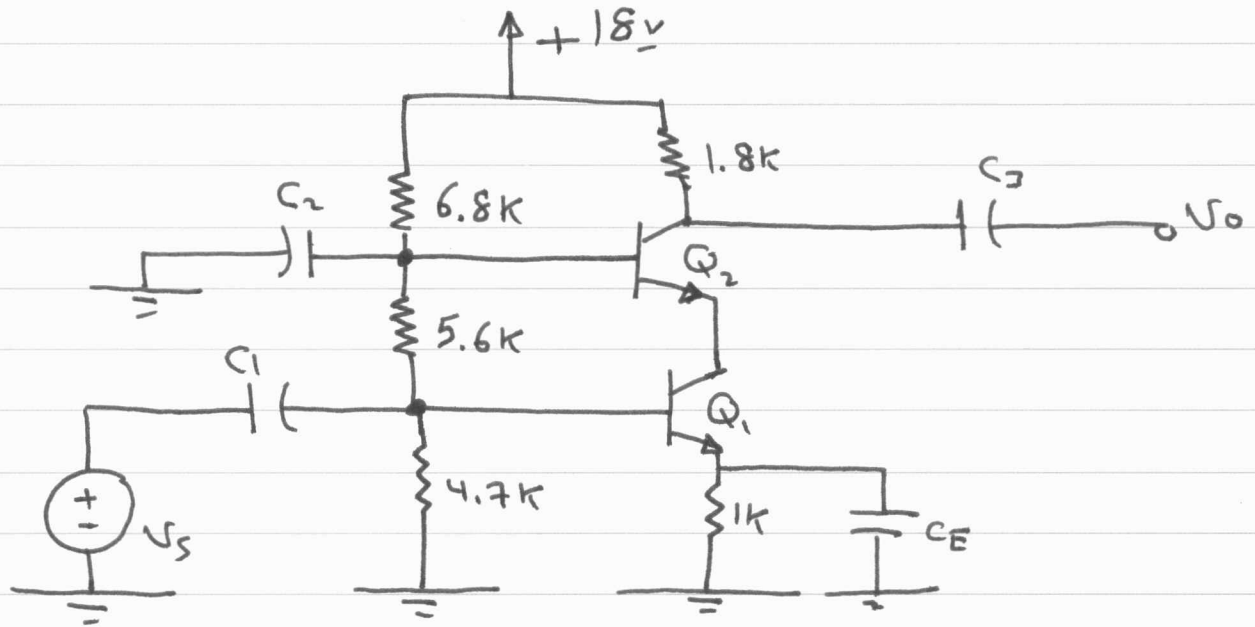

## Ac small signal equivalent circuit

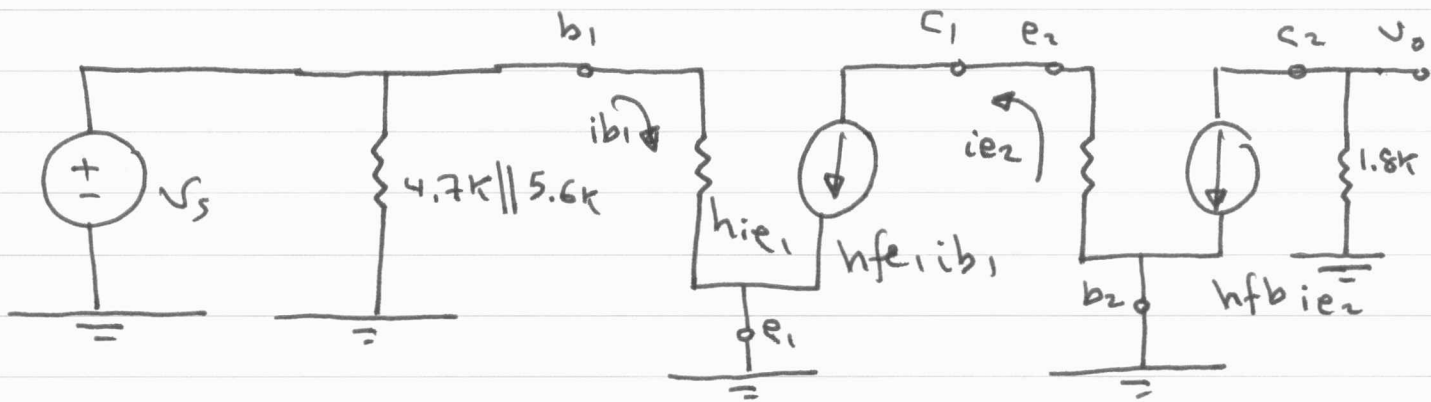

$$V_o = -h_{fb} i_{e2} (1.8k)$$

$$i_{e2} = h_{fe1} i_{b1}$$

$$i_{b1} = \frac{V_s}{h_{ie1}}$$

$$\therefore A_v = -294$$