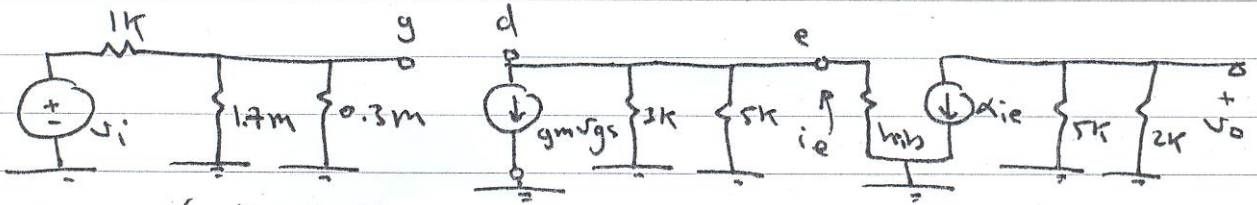


Q1: $h_{ib} = \frac{h_{ie}}{h_{fe} + 1} \approx 30 \Omega$



$v_o = - (5k \parallel 2k) \alpha_{ie}$

$i_e = g_m v_{gs} \cdot \frac{2k \parallel 5k}{2k \parallel 5k + h_{ib}} ; v_{gs} = v_g - v_s = \frac{0.3M \parallel 1.7M}{0.3M \parallel 1.7M + 1k} v_i$

$\therefore A_v \approx -5.62$

Q2: DC Analysis :

$V_{TH} = \frac{10k}{10k + 47k} \cdot 15 = 2.6V ; R_{TH} = 10k \parallel 47k = 8.25k$


$\therefore I_{E1} = 1.825mA ; h_{ie1} \approx 2.85k$

$V_{CC} = 3.3k(I_{E1} + I_{B2}) + 0.7 + 0.7 + (\beta_2 + 1)(\beta_1 + 1)I_{B2}(1k)$

$\therefore I_{E2} = 0.075mA ; I_{E3} = 7.575mA$

$h_{ie2} = 34.67k ; \therefore h_{ieD} \approx 70k ; h_{feD} \approx 10000$

ac small signal analysis :

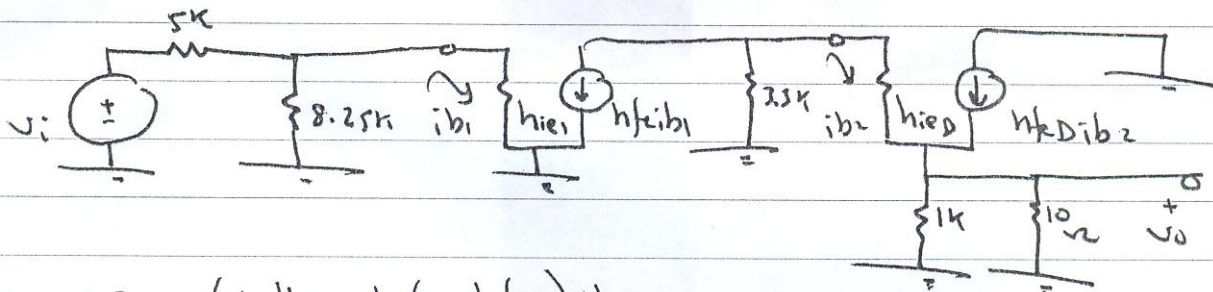

$v_o = (1k \parallel 10\Omega) (1 + h_{feD}) i_{b2}$

$i_{b2} = -h_{fe} i_{b1} \frac{3.3k}{3.3k + (1k \parallel 10\Omega) (1 + h_{feD})} ; i_{b1} = \frac{8.25k}{8.25k + h_{ie1}} i_i$

$i_i = \frac{v_i}{5k + Z_i} ; Z_i = 8.25k \parallel 2.85k \approx 2.1k$

$\therefore v_o \approx -40 v_i \rightarrow A_v \approx -40$

(b) $v_o = -h_{fe} i_{b1} (3.3k \parallel 10\Omega) ; i_{b1} = 0.74 i_i$

$i_i = 0.14 v_i$

$\therefore A_v = -0.207$

Q3: $V_{G1} = \frac{1m}{1m+1.5m} \cdot 20 = 8V$, $V_{S1} = 4.7k I_{DS1}$

$I_{DS1} = I_{DSS} \left(1 - \frac{V_{GS1}}{V_P} \right)^2 \rightarrow I_{DS} = \begin{cases} 1.92mA \quad \checkmark \\ 2.36mA \quad \times \end{cases}$

KVL: $4.1k I_{DS2} + V_{GS2} - 4.7k I_{DS2} = 0$

$V_{GS2} = -7.9 + (4.7k)(I_{DS2})$


$\therefore I_{DS2} = \begin{cases} 2.33mA \quad \times \\ 1.89mA \quad \checkmark \end{cases}$

KVL: $-(4.1k) I_{DS2} + V_{GS3} + (4.7k) I_{DS3} = 0$

$\therefore V_{GS3} = 7.8 - (4.7k)(I_{DS3})$

$\therefore I_{DS3} = \begin{cases} 1.88mA \quad \checkmark \\ 2.3mA \quad \times \end{cases}$

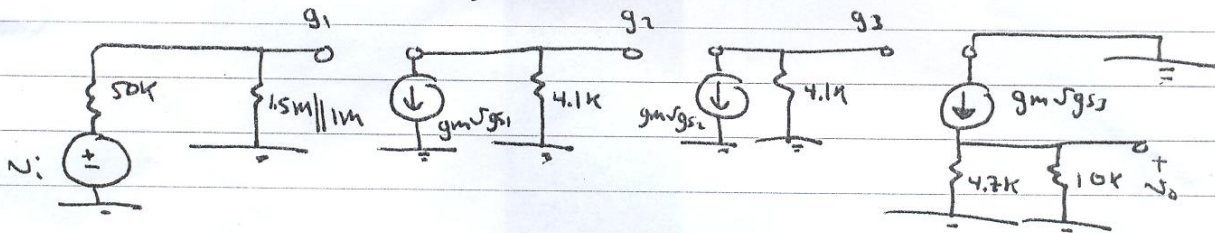$g_{m1} \approx g_{m2} \approx g_{m3} = 3.9 mS$



$V_o = (4.7k \parallel 10k) g_m V_{gs3}$; $V_{gs3} = V_{g3} - V_{s3}$, $V_{s3} = V_o$


$V_{g3} = -g_m V_{gs2} (4.1k)$, $V_{s2} = 0$

$V_{g2} = -g_m V_{gs1} (4.1k)$; $V_{s1} = 0$, $V_{g1} = \frac{1.5k \parallel 1m}{1.5m \parallel 1m + 50} V_i$

$A_v \approx -218$

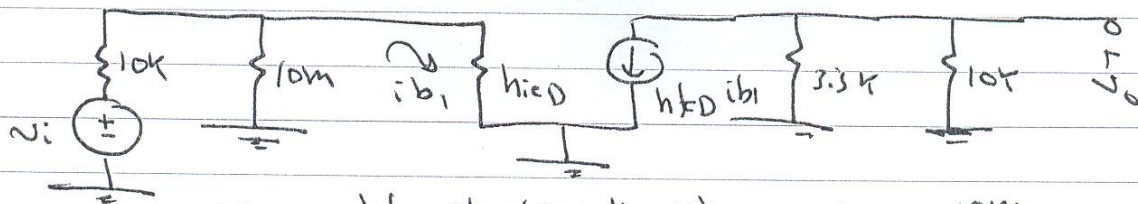Q4 DC Analysis $5 = 10M I_{B1} + 1.4 \rightarrow I_{B1} = 0.36 \mu A$

$h_{ie1} \approx 72k \rightarrow h_{ieD} \approx 144k$



$V_o = -h_{feD} i_{b1} (3.3k \parallel 10k)$; $i_{b1} = \frac{10m}{10m + h_{ieD}} i_i$

$i_i = \frac{V_i}{10k + Z_i}$; $Z_i = 10m \parallel h_{ieD}$

$\therefore A_v \approx -40$