
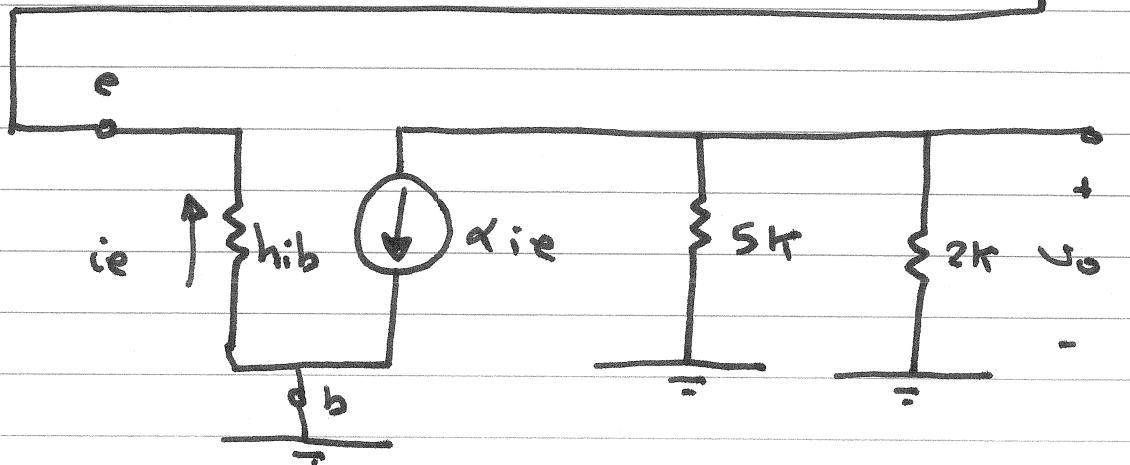


Solutions of Multistage Amplifiers

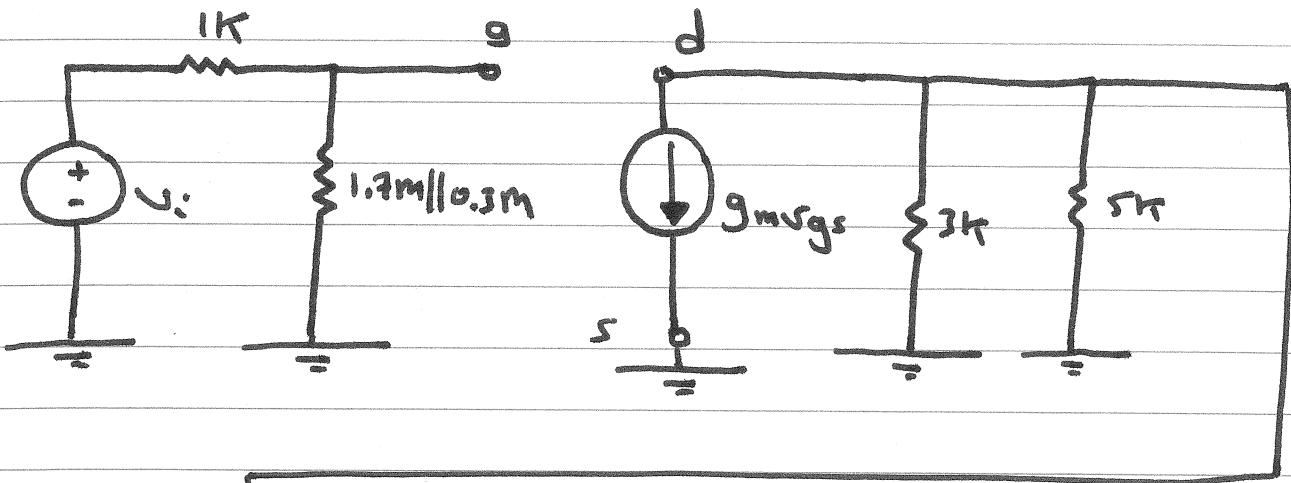Q 1 : $h_{ib} = \frac{h_{ie}}{1+h_{fe}} \approx 30 \Omega$



$$V_o = - (5k\Omega // 2k\Omega) \propto i_e$$

$$i_e = + g_m v_{gs} \frac{3k\Omega // 5k\Omega}{3k\Omega // 5k\Omega + h_{ib}}$$

$$v_{gs} = V_g - V_s = V_g = \frac{0.3M\Omega // 1.7M\Omega}{0.3M\Omega // 1.7M\Omega + 1k\Omega} V_i$$

$$\therefore A_v = -5.62$$

Q₂

$$V_{TH} = \frac{10k}{10k+47k} \cdot 15V = 2.6V$$

$$R_{TH} = 10k \parallel 47k = 8.25k$$

$$I_{E_1} = \frac{\sqrt{V_{TH} - 0.7}}{R_{TH} + R_{E_1}} = 1.825mA$$

$$h_{ie_1} = \frac{(\beta_1 + 1) V_T}{I_{E_1}} = 2.85k$$



$$V_{CC} = 3.3k (I_{C_1} + I_{B_1}) + 0.7 + 0.7 + 1k I_{E_2}$$

$$I_{E_2} = (\beta_2 + 1) (\beta_1 + 1) I_{B_1}$$

$$\therefore I_{E_2} = 0.075mA ; I_{E_3} = 7.575mA$$

$$h_{ie_2} = 34.67k \approx 35k \therefore h_{ie_D} \approx 70k$$
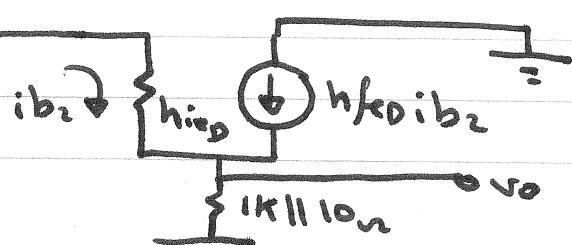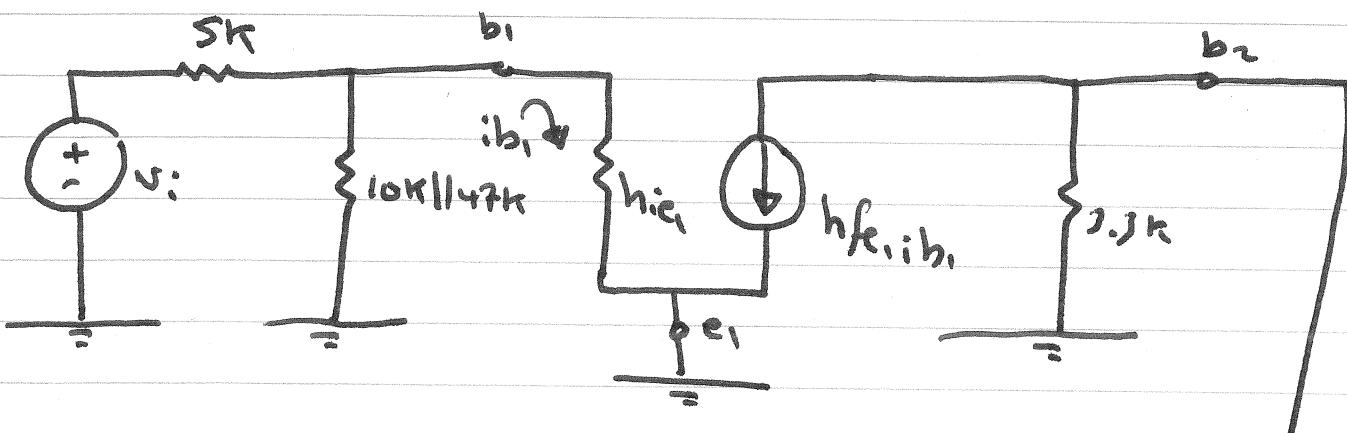
$$h_{fED} = h_{fe_2} \cdot h_{fe_3} = 10000$$



$$V_o = (1K \parallel 10\mu) (1 + h_{FE}) i_{B2}$$

$$i_{B2} = -h_{FE} i_{B1} \frac{3.3K}{3.3K + h_{IE}D + (1K \parallel 10\mu)(1 + h_{FE})}$$

$$i_{B1} = \frac{8.25K}{8.25K + h_{IE}} ii$$

$$ii = \frac{Vi}{5K + Z_i}$$

$$Z_i = 8.25K \parallel 2.85K \approx 2.1K$$

$$\therefore V_o = -40 Vi$$

b) $V_o = -h_{FE} i_{B1} (3.3K \parallel 10\mu)$

$$i_{B1} = 0.74 ii$$

$$ii = 0.14 Vi$$

$$\therefore V_o = -0.207 Vi$$

Q3

$$\sqrt{G_1} = \frac{1m}{1m+1.5m} \cdot 20 = 8V$$

$$\sqrt{G_1} = 4.7k \cdot I_{DS1}$$

$$I_{DS1} = I_{DSs} \left(1 - \frac{\sqrt{G_1}}{\sqrt{P}} \right)^2$$

$$\therefore I_{DS1} = \begin{cases} 1.92mA & \checkmark \\ 2.36mA & \times \end{cases}$$

$$KVL : 4.1k \cdot I_{DS2} + \sqrt{G_2} - 4.7k \cdot I_{DS2} = 0$$

$$\therefore \sqrt{G_2} = -7.9 + 4.7k \cdot I_{DS2}$$

$$I_{DS2} = I_{DSs} \left(1 - \frac{\sqrt{G_2}}{\sqrt{P}} \right)^2$$

$$\therefore I_{DS2} = \begin{cases} 2.33mA & \times \\ 1.89mA & \checkmark \end{cases}$$



$$KVL : \sqrt{G_3} + 4.7k \cdot I_{DS3} - 4.1k \cdot I_{DS3} = 0$$

$$\therefore \sqrt{G_3} = 7.8 - 4.7k (I_{DS3})$$

$$I_{DS3} = I_{DSs} \left(1 - \frac{\sqrt{G_3}}{\sqrt{P}} \right)^2$$

$$\therefore I_{DS2} = \begin{cases} 1.88 \text{ mA} & \checkmark \\ 2.3 \text{ mA} & \times \end{cases}$$
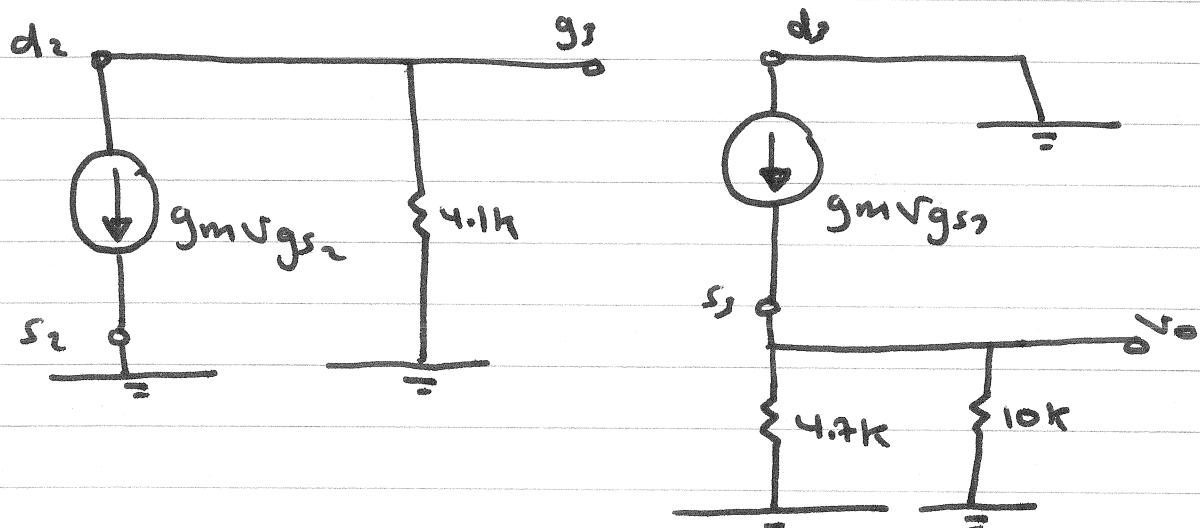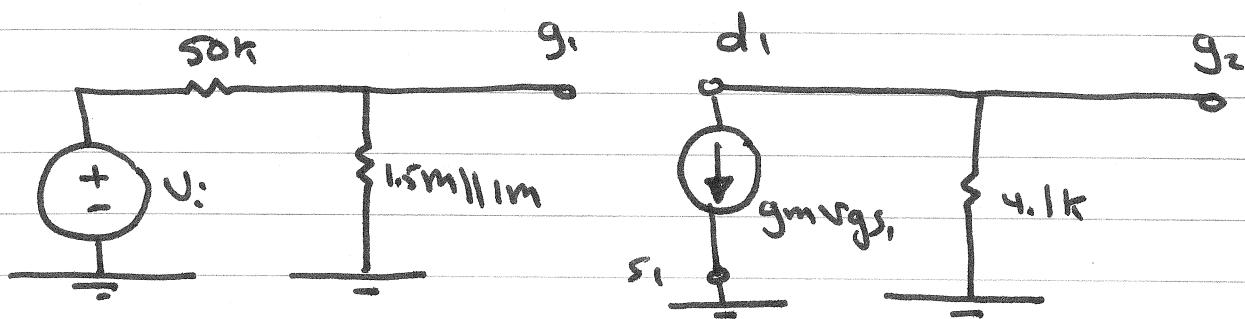
$$g_{m1} \approx g_{m2} \approx g_{m3} = 3.9 \text{ mA}$$



$$V_o = (4.7k \parallel 10k) g_m v_{gs2}$$

$$\sqrt{g_{s2}} = \sqrt{g_2} - \sqrt{s_2}$$

$$\sqrt{s_2} = V_o$$

$$\sqrt{g_2} = -g_m \sqrt{g_{s2}} (4.1k)$$

$$\sqrt{g_{s2}} = \sqrt{g_2} - \sqrt{s_2} = \sqrt{g_2} = -g_m \sqrt{g_{s1}} (4.1k)$$

$$\sqrt{g_{s1}} = \sqrt{g_1} - \sqrt{s_1} = \sqrt{g_1} = \frac{1.5mH/m}{1.5mH/m + 50k} V_i$$


$\therefore Av \approx 218$

Q4

$$5 = 10m I_{B1} + 0.7 + 0.7$$

$$\therefore I_{B1} = 0.36 \text{ mA}$$
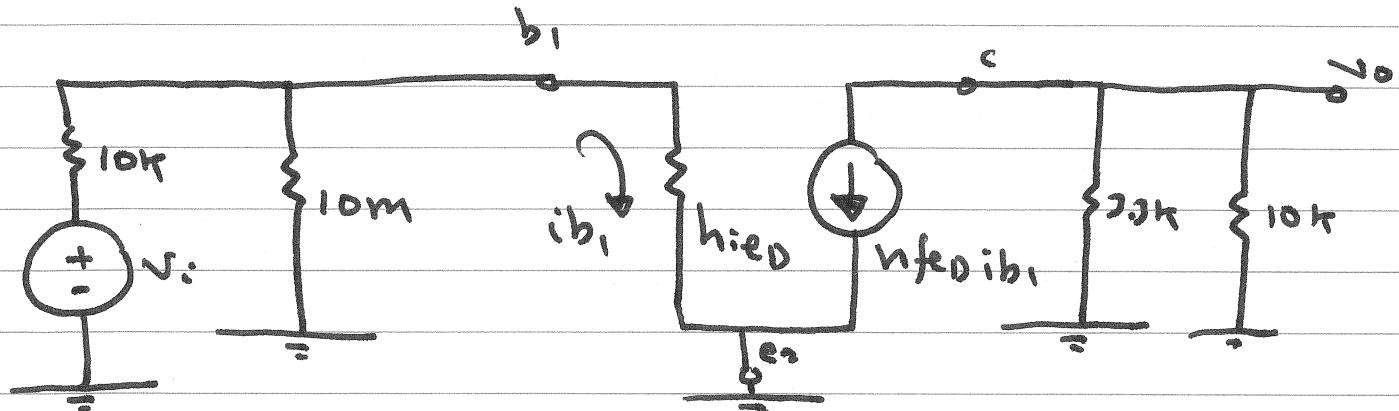
$$\therefore h_{ie1} = 72k \rightarrow h_{icd} = 144k$$



$$N_o = -h_{fed} i_{b1} (3.3k \parallel 10k)$$

$$i_{b1} = \frac{10m}{10m + h_{ie1}} ii$$

$$ii = \frac{V_i}{10k + 10m \parallel h_{icd}}$$

$$\therefore A_v \approx -40$$