

ENEE236 &amp; 241

# Analog Electronics

## L2 Semiconductor Diodes

Instructor: Nasser Ismail

ENEE236 – Analog Electronics


## Diode Operating Conditions

### No Bias

No external voltage is applied:  $V_D = 0\text{ V}$

There is no diode current:  $I_D = 0\text{ A}$


Only a modest depletion region exists

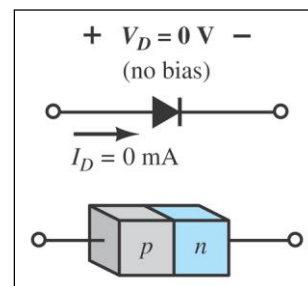

## Diode Operating Conditions
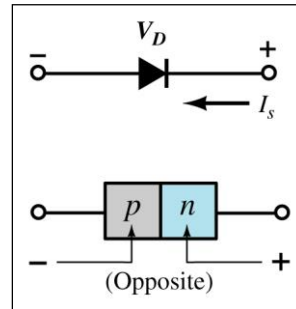
### Reverse Bias

External voltage is applied across the  $p$ - $n$  junction in the opposite polarity of the  $p$ - and  $n$ -type materials.




## Diode Operating Conditions
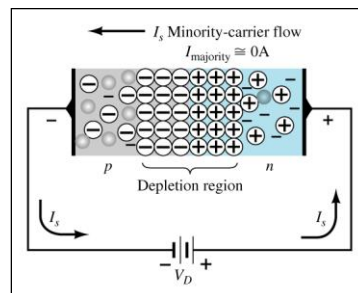
### Reverse Bias

The reverse voltage causes the depletion region to widen.

The electrons in the  $n$ -type material are attracted toward the positive terminal of the voltage source.




The holes in the  $p$ -type material are attracted toward the negative terminal of the voltage source.

## Diode Operating Conditions
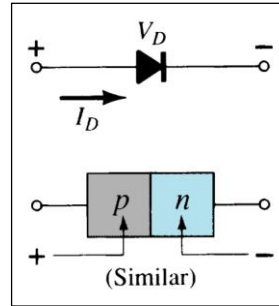
### Forward Bias

External voltage is applied across the  $p$ - $n$  junction in the same polarity as the  $p$ - and  $n$ -type materials.




## Diode Operating Conditions
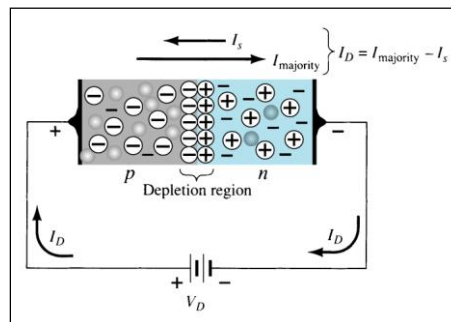
### Forward Bias

The forward voltage causes the depletion region to narrow.

The electrons and holes are pushed toward the  $p$ - $n$  junction.



The electrons and holes have sufficient energy to cross the  $p$ - $n$  junction.


## Zener Region

**The Zener region is in the diode's reverse-bias region.**

At some point the reverse bias voltage is so large the diode breaks down and the reverse current increases dramatically.

The maximum reverse voltage that won't take a diode into the zener region is called the **peak inverse voltage** or **peak reverse voltage**.

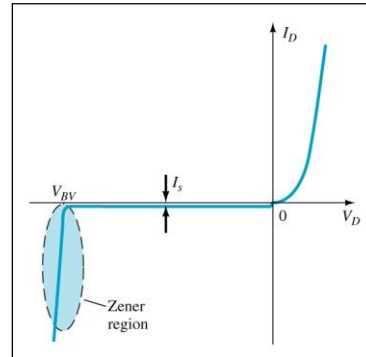The voltage that causes a diode to enter the zener region of operation is called the **zener voltage ( $V_Z$ )**.



## Forward Bias Voltage

The point at which the diode changes from no-bias condition to forward-bias condition occurs when the electrons and holes are given sufficient energy to cross the p-n junction. This energy comes from the external voltage applied across the diode.

The forward bias voltage required for a:

**gallium arsenide diode  $\cong 1.2$  V**

**silicon diode  $\cong 0.7$  V**

**germanium diode  $\cong 0.3$  V**

## Temperature Effects

**As temperature increases it adds energy to the diode.**

It reduces the required forward bias voltage for forward-bias conduction.

It increases the amount of reverse current in the reverse-bias condition.

It increases maximum reverse bias avalanche voltage.

***Germanium diodes are more sensitive to temperature variations than silicon or gallium arsenide diodes.***

## Resistance Levels

**Semiconductors react differently to DC and AC currents.**

*There are three types of resistance:*

**DC (static) resistance**


**AC (dynamic) resistance**

**Average AC resistance**

## DC (Static) Resistance

For a specific applied DC voltage ( $V_D$ ) the diode has a specific current ( $I_D$ ) and a specific resistance ( $R_D$ ).

$$R_D = \frac{V_D}{I_D}$$

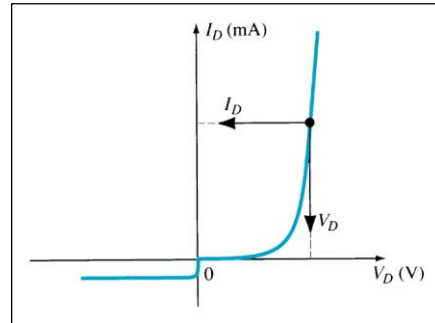

## AC (Dynamic) Resistance

In the forward bias region:

$$r'_d = \frac{26 \text{ mV}}{I_D}$$

The resistance depends on the amount of current ( $I_D$ ) in the diode.

The voltage across the diode is fairly constant (26 mV for 25°C).

In the reverse bias region:


$$r'_d = \infty$$

*The resistance is effectively infinite. The diode acts like an open.*

## Average AC Resistance

$$r_{av} = \frac{\Delta V_d}{\Delta I_d} \quad | \quad pt. \text{ to } pt.$$

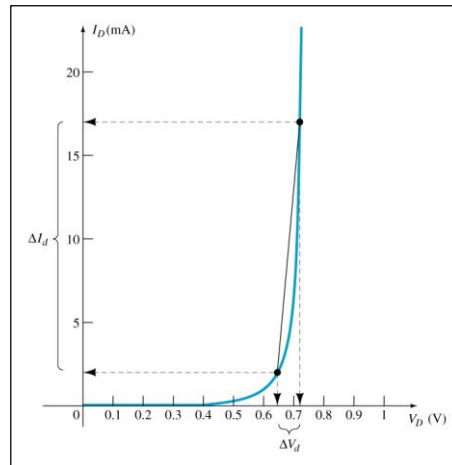
AC resistance can be calculated using the current and voltage values for two points on the diode characteristic curve.



### Diode Analysis Methods:


1. Using non-linear Math (not covered)
2. Using Diode Models (covered)
3. Using load line (covered)

## The Load Line Analysis

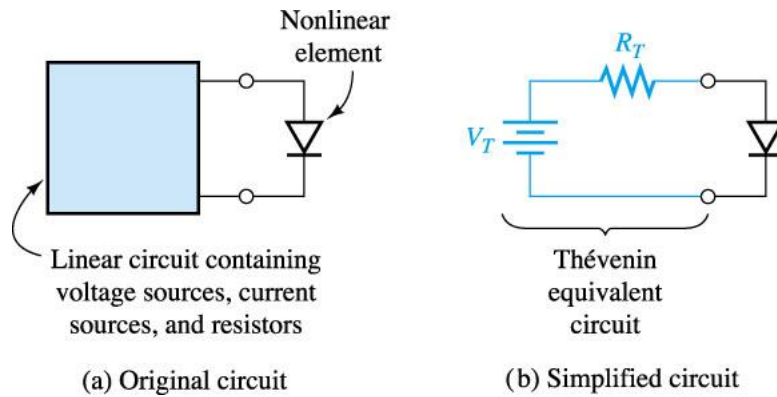

Analysis of a circuit containing a singular nonlinear element can be accomplished by "load-line analysis" of a simplified circuit.

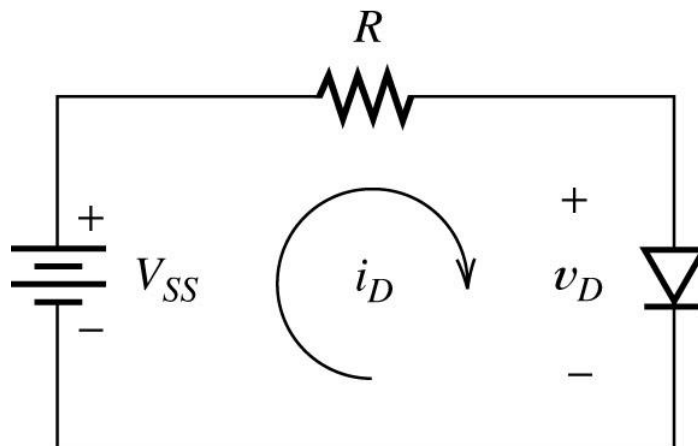
## The device operating point (= bias point = Q-point)




Circuit for load-line analysis.




## The load-line concept

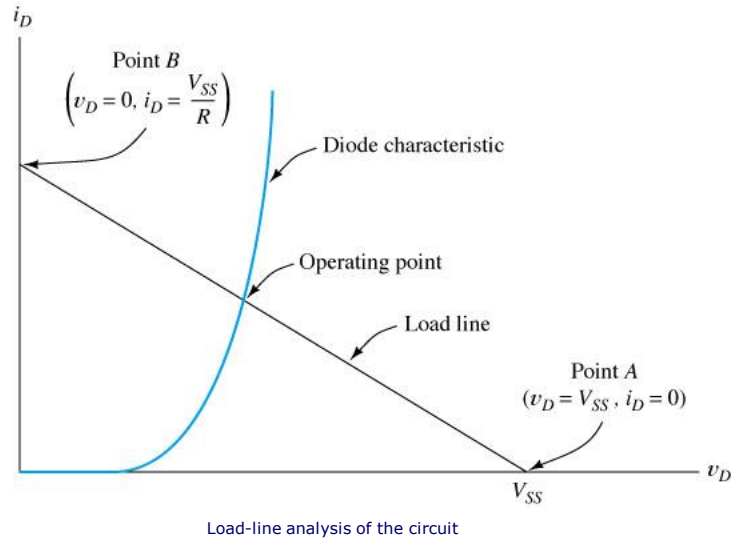

## The load-line concept

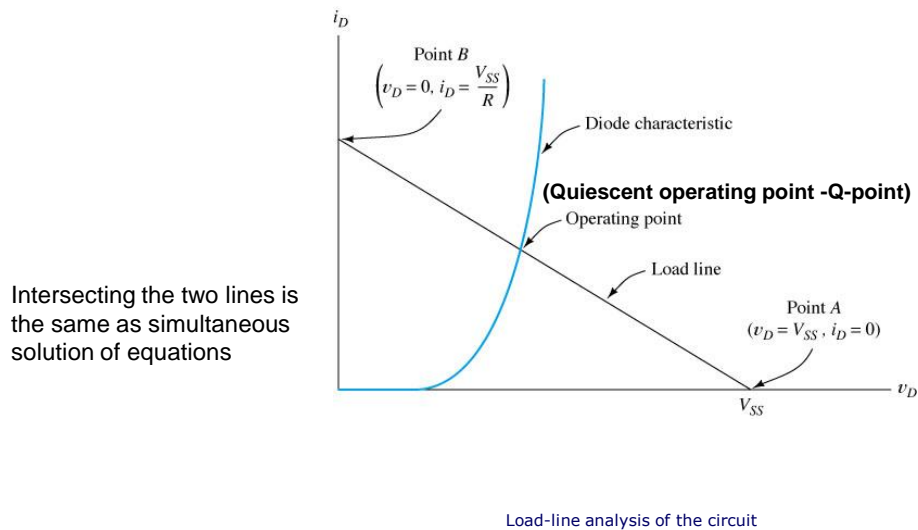



## The device Q-point (quiescent)

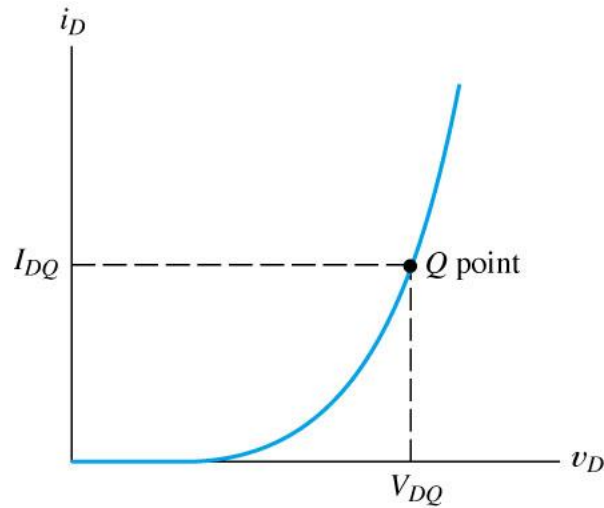

Diode characteristic, illustrating the Q-point.


## Diode (Models)

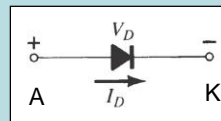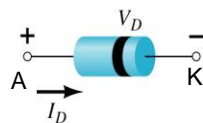- 1) Ideal Diode Model
- 2) Simplified/piecewise/ knee model
- 3) Complete diode model




## Ideal Diode Model

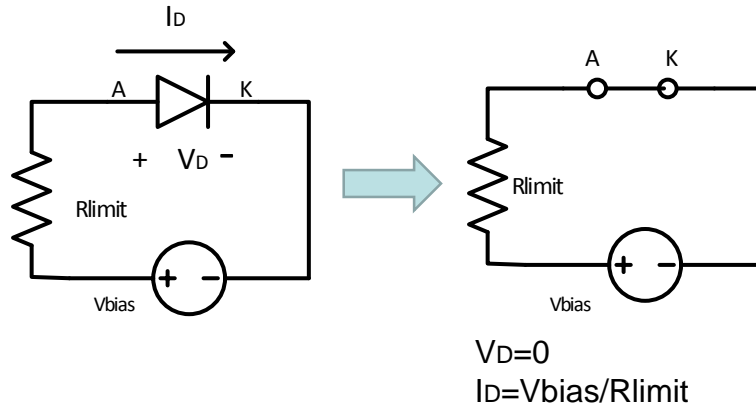- 1) if the diode is forward biased ==> diode is replaced by short circuit




## Ideal Diode Model

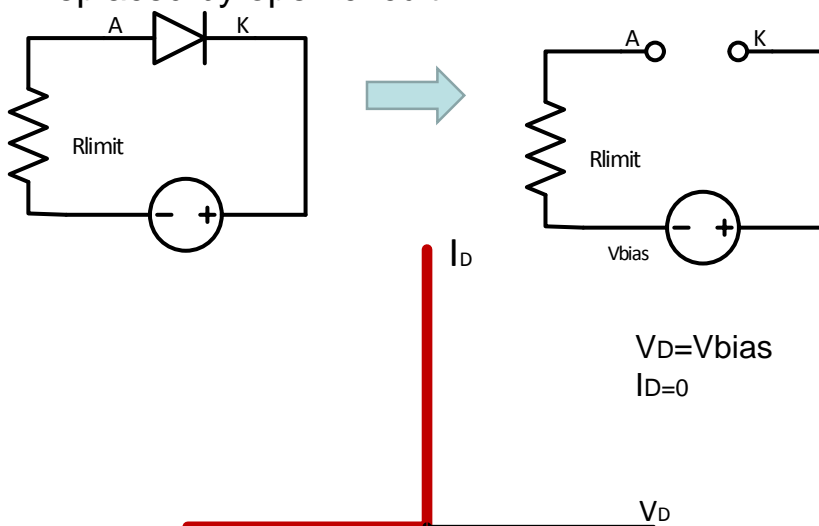- 2) if the diode is Reverse biased ==> diode is replaced by open circuit




## Simplified/piecewise/ knee model

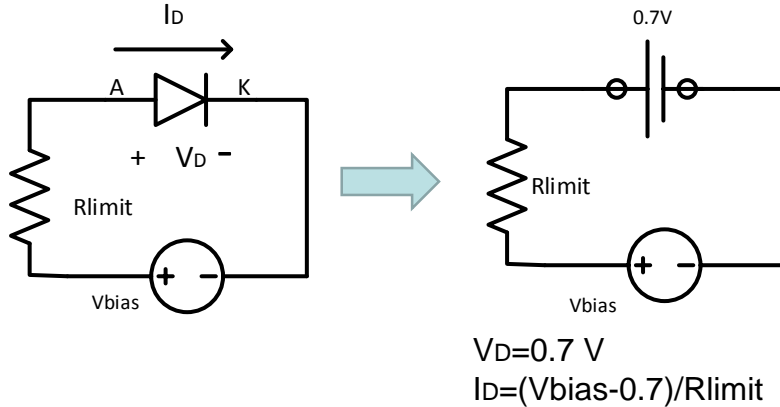- 1) if the diode is forward biased ==> diode is replaced by a 0.7V battery (for Si)




## Simplified/piecewise/ knee model

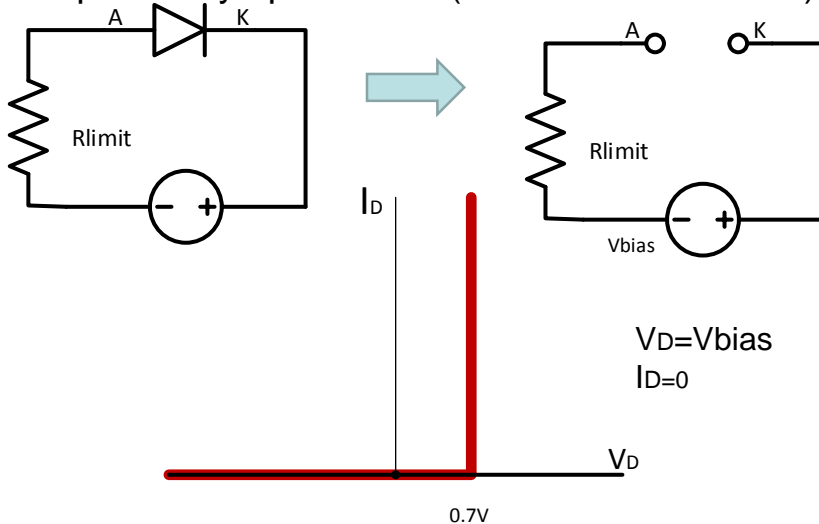- 2) if the diode is Reverse biased ==> diode is replaced by open circuit (same as ideal model)



## Complete Diode model

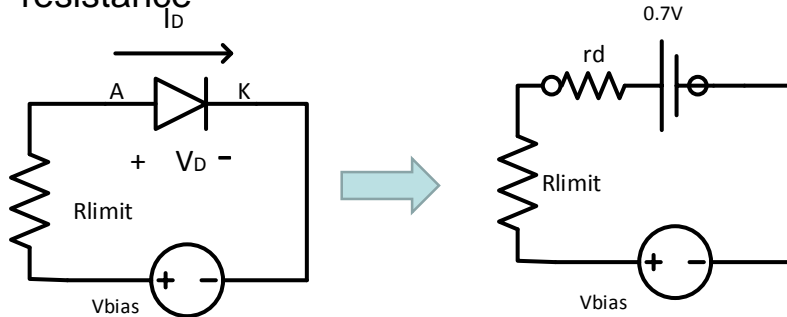- 1) if the diode is forward biased ==> diode is replaced by a 0.7V battery and forward dynamic resistance




$$V_D = 0.7 + I_D \cdot r_d$$

$$I_D = (V_{bias} - 0.7) / (R_{limit} + r_d)$$

## Complete Diode model

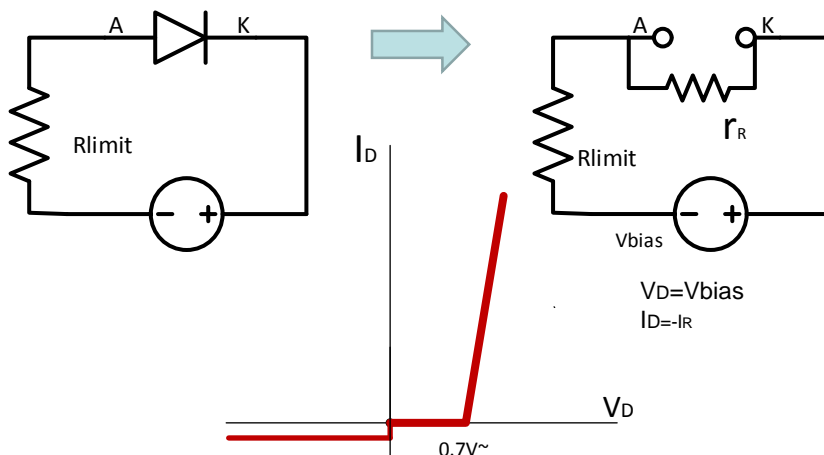- 2) if the diode is Reverse biased ==> diode is replaced by open circuit // to reverse resistance  $r_R$



$$V_D = V_{bias}$$


$$I_D = -I_R$$

## Diode Specification Sheets

*Diode data sheets contain standard information, making cross-matching of diodes for replacement or design easier.*

1. Forward Voltage ( $V_F$ ) at a specified current and temperature
2. Maximum forward current ( $I_F$ ) at a specified temperature
3. Reverse saturation current ( $I_R$ ) at a specified voltage and temperature
4. Reverse voltage rating, PIV or PRV or  $V_{(BR)}$ , at a specified temperature
5. Maximum power dissipation at a specified temperature
6. Capacitance levels
7. Reverse recovery time,  $t_{rr}$
8. Operating temperature range

## Diode Symbol and Packaging

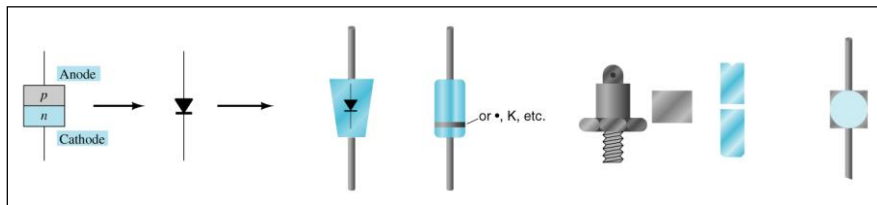

**The anode is abbreviated A**

**The cathode is abbreviated K**

## Diode Testing

Diodes are commonly tested using one of these types of equipment:

**Diode checker**

**Ohmmeter**

**Curve tracer**

## Diode Checker

Many digital multimeters have a diode checking function. The diode should be tested out of circuit.

*A normal diode exhibits its forward voltage:*


**Gallium arsenide  $\cong 1.2$  V**

**Silicon diode  $\cong 0.7$  V**

**Germanium diode  $\cong 0.3$  V**

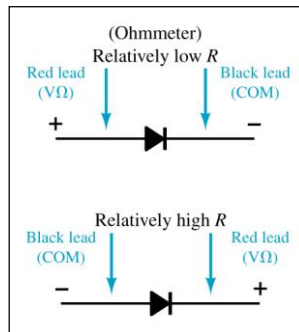
## Ohmmeter

An ohmmeter set on a low Ohms scale can be used to test a diode. The diode should be tested out of circuit.


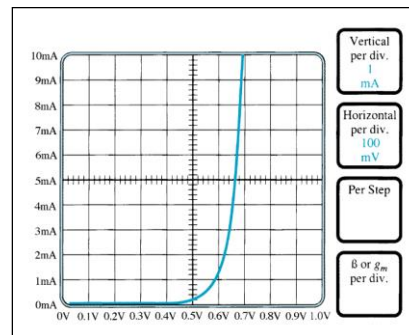
## Curve Tracer

A curve tracer displays the characteristic curve of a diode in the test circuit. This curve can be compared to the specifications of the diode from a data sheet.





## Other Types of Diodes

There are several types of diodes besides the standard  $p$ - $n$  junction diode. Three of the more common are:

**Zener diodes**

**Light-emitting diodes**


**Diode arrays**

## Zener Diode

A **Zener diode** is one that is designed to safely operate in its zener region; i.e., biased at the Zener voltage ( $V_Z$ ).


Common zener diode voltage ratings are between 1.8 V and 200 V

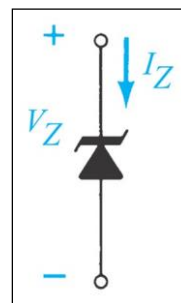The **Zener diode** is used for voltage regulation, details will be discussed later


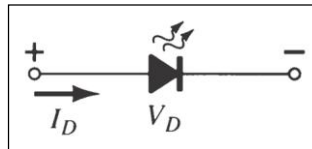
## Light-Emitting Diode (LED)

An **LED** emits light when it is forward biased, which can be in the infrared or visible spectrum.



The forward bias voltage is usually in the range of 2 V to 3 V.


## Diode Arrays

Multiple diodes can be packaged together in an integrated circuit (IC).




**A variety of diode configurations are available.**

Common Anode

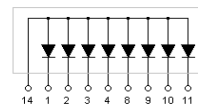

Common Cathode

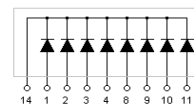


Example:

Find the Q-point ( $I_{DQ}$  and  $V_{DQ}$ )

a) Use ideal diode model

b) Use practical diode model

c) Use exact model

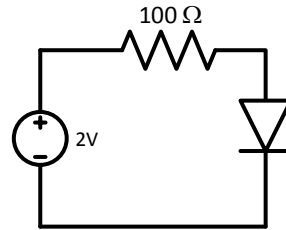


**Solution**

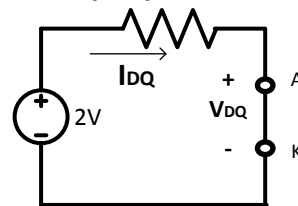a) Since  $V_A > V_K$ , diode is forward biased (ON)  $\implies$  it can be replaced by a short circuit

$$V_{DQ} = V_{AK} = 0 \text{ V}$$


$$I_{DQ} = 2\text{V} / 100 \text{ } \Omega = 20 \text{ mA}$$



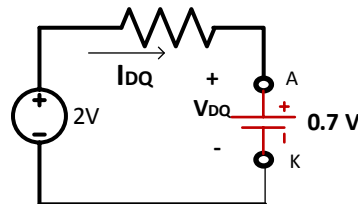b) When using practical model, diode is replaced by a 0.7 V battery

$$V_{DQ} = V_{AK} = 0.7 \text{ V}$$

$$I_{DQ} = (2 - 0.7) / 100 = 13 \text{ mA}$$



c) Exact solution yields

$$V_{DQ} = V_{AK} = 0.786 \text{ V}$$

$$I_{DQ} = 12.14 \text{ mA}$$

**Note:** If applied voltage is much higher than  $V_{AK}$  (at least 10 times), then ideal diode model is recommended


## ENEE236 – Analog Electronics

Example:

**Find the Q-point**

**( $I_{DQ}$  and  $V_{DQ}$ )**

**Solution**

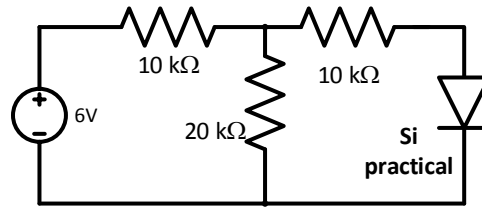


It is better to convert the two loop circuit to a single loop circuit by finding Thevenin's equivalent circuit

$$V_{TH} = 6V \cdot \frac{20k}{20k+10k} = 4V$$

$$R_{TH} = \frac{10k+20k}{10k} = 16.67 k\Omega$$


$$V_{DQ} = V_{AK} = 0.7V$$
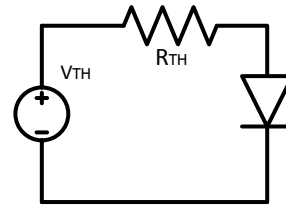
$$I_{DQ} = \frac{4-0.7}{16.67 k\Omega} = 0.198 mA$$




## ENEE236 – Analog Electronics

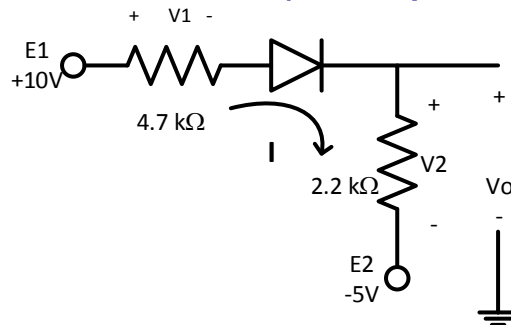
Example: **Find  $I$ ,  $V_1$ ,  $V$  and  $V_o$  (use simplified model)**



Solution:

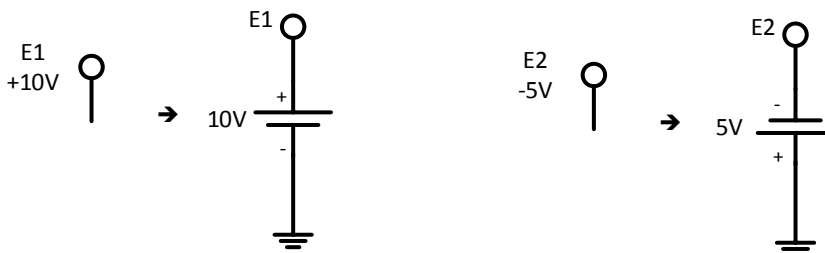

## EENE236 – Analog Electronics

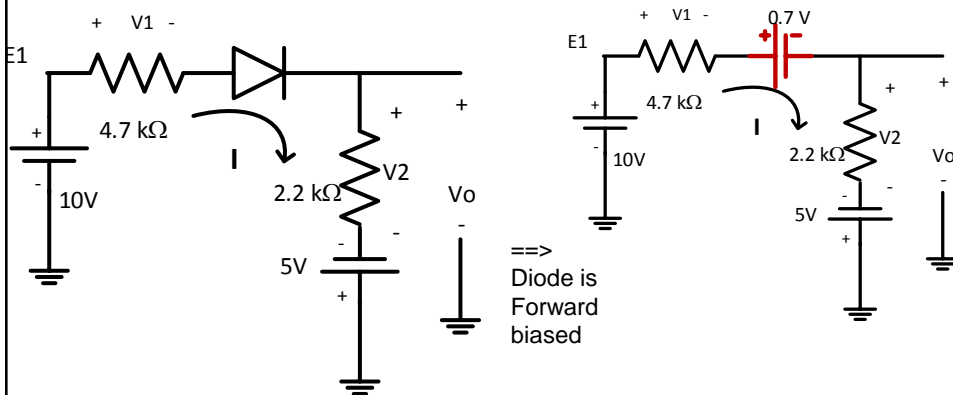

==>  
Diode is  
Forward  
biased

$$I = (10 + 5 - 0.7) \text{V} / (4.7 + 2.2) \text{ k}\Omega$$

$$= 2.07 \text{ mA}$$

$$V_1 = I \cdot R_1 = 9.73 \text{ V}$$

$$V_o = V_2 - 5 = -0.45 \text{ V}$$

$$V_2 = I \cdot R_2 = 4.55 \text{ V}$$

## EENE236 – Analog Electronics

**Find  $I_1$ ,  $I_2$ ,  $I_{D2}$  (use practical diode model)**

**Solution:**

Applied voltage is suitable for forward biasing both diodes

$$I_1 = 0.7 \text{ V} / 3.3 \text{ k}\Omega$$

$$= 0.212 \text{ mA}$$

$$I_2 = (20 - 0.7 - 0.7) / 5.6 \text{ k}\Omega$$

$$= 3.32 \text{ mA}$$

$$I_2 = I_1 + I_{D2}$$

$$I_{D2} = I_2 - I_1 = 3.32 - 0.212$$

$$= 3.11 \text{ mA}$$

