

ENEE236 & 241



Analog Electronics

L4 Diode Applications 2
Instructor: Nasser Ismail

Clampers

Function: A Clamper shifts the input waveform up or down (adds a dc offset) while keeping its shape and peak to peak value unchanged.

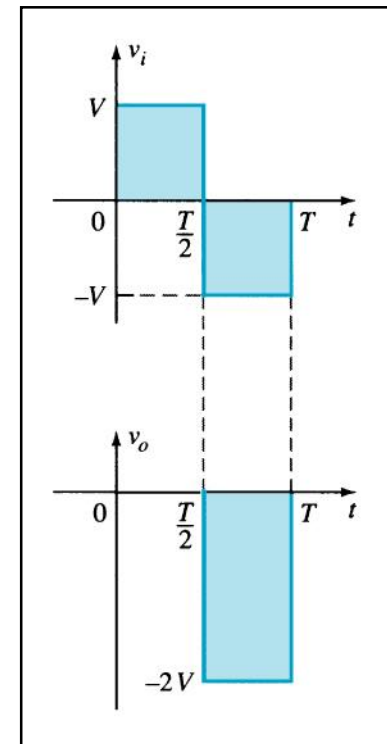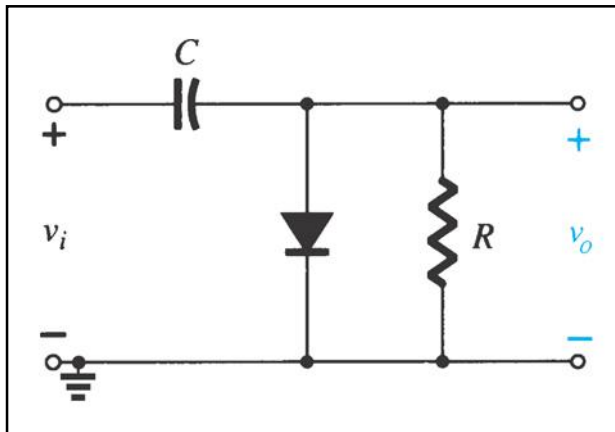It consists of a diode and capacitor (and maybe a series dc source) that can be combined to “clamp” an AC signal to a specific DC level and supply it to the load R





Steps for Clamper Circuit Analysis

- 1) Start analysis by examining Steps for the response of the portion of input that will forward bias the diode**
- 2) During diode On period, assume that the cap is charged instantaneously to a voltage level defined by surrounding network**
- 3) During OFF period, assume the cap holds the established voltage level (i.e. it behaves as constant dc voltage source)**
- 4) Consider value and polarity of V_o**
- 5) Check that total swing (peak to peak) of output equal swing of input.**

Example

Find and sketch $V_o(t)$

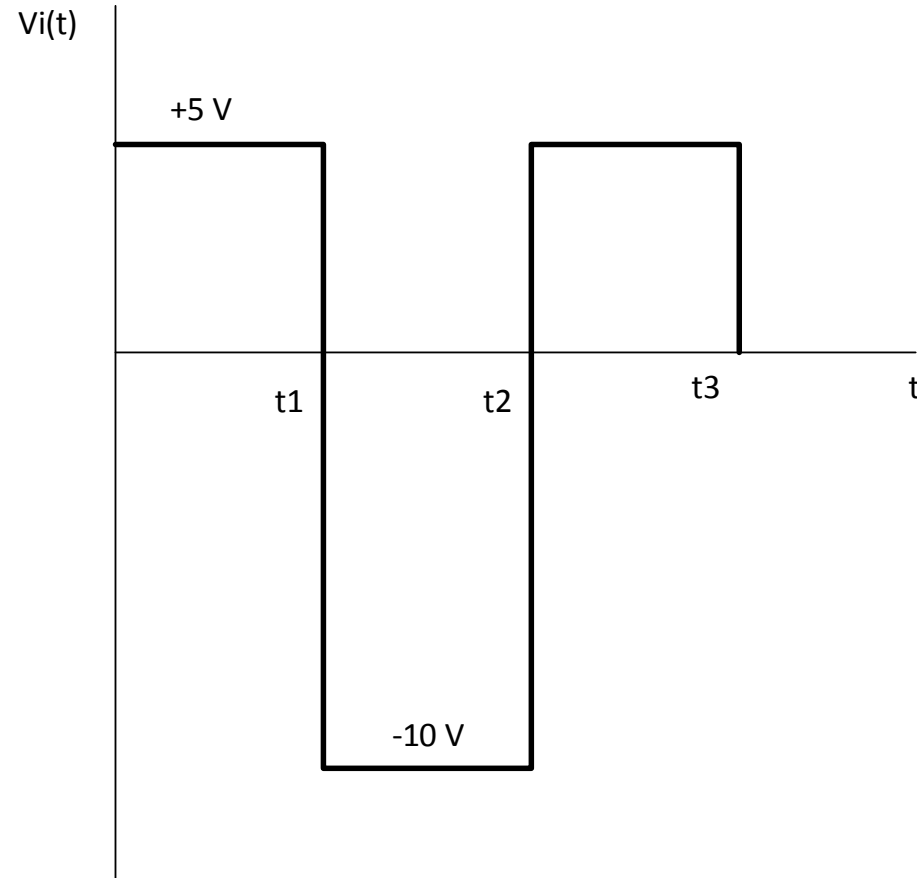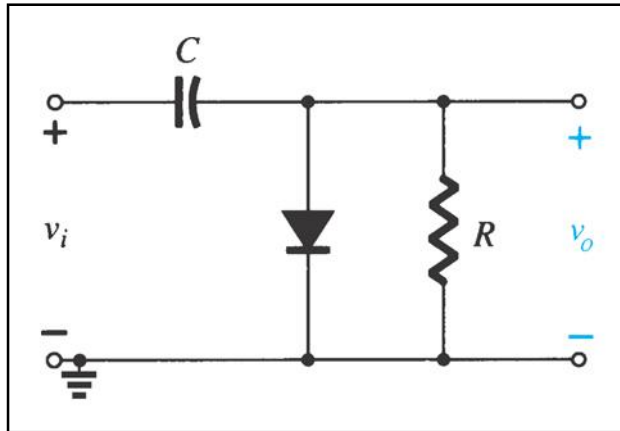



1) For $t < 0$ ($t = 0^-$) $V_C(0^-) = 0$

2) For $t > 0$ ($t = 0^+$) $V_C(0^+) = 0$

$V_i(0^+) = 5V$


$\Rightarrow D1$ is ON and it is replaced by short circuit

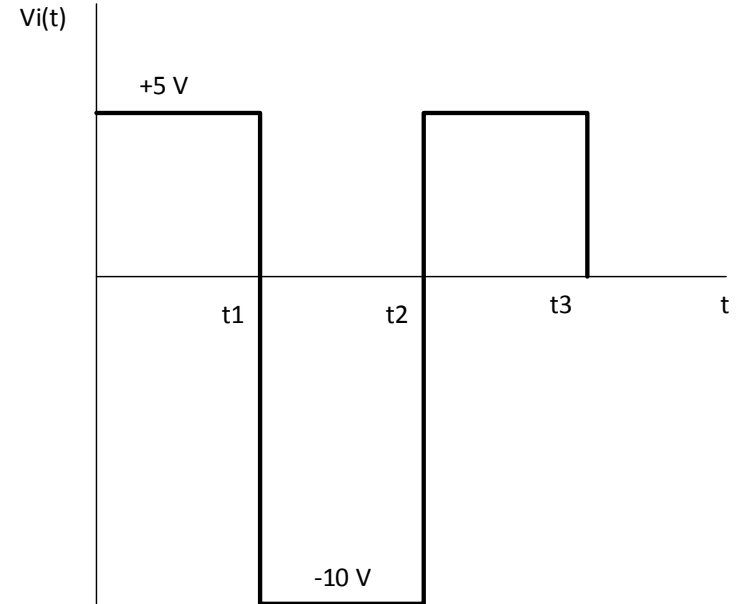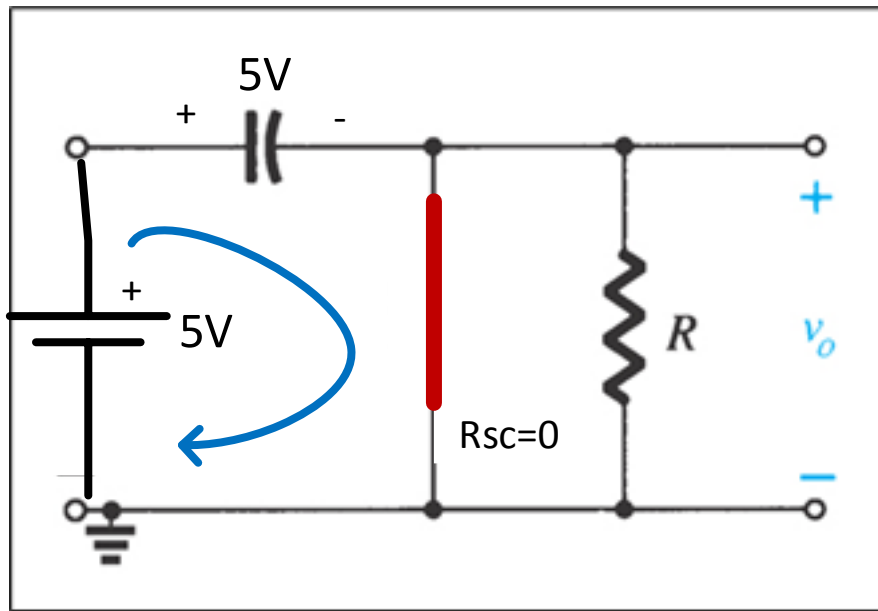3) for $0^+ < t < t_1$ equivalent circuit is \Rightarrow see next page




$\Rightarrow D1$ is ON, Cap charges instantaneously to +5V with shown polarity since $\tau_{\text{charge}} = R_{sc} \cdot C \cong 0$ and $V_o(t) = 0 \text{ V}$

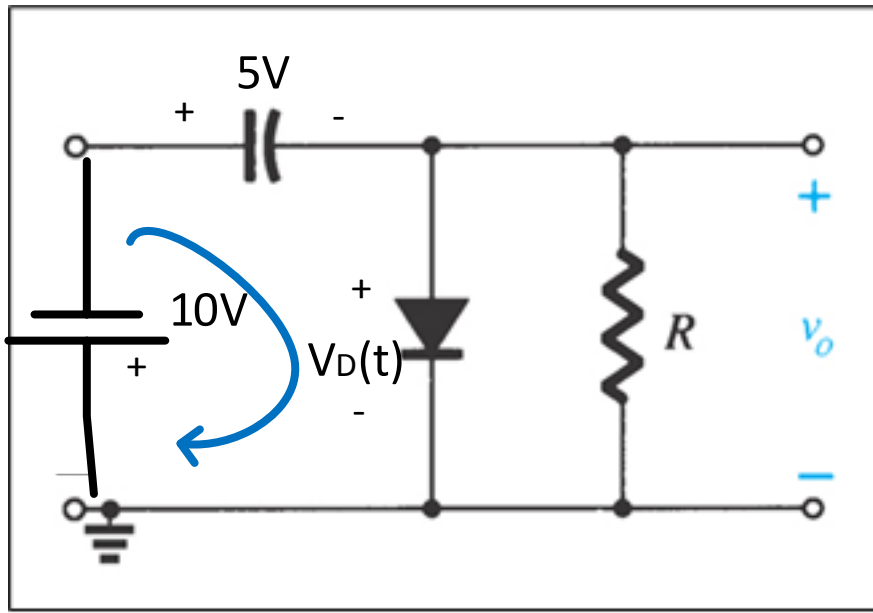4) for $t_1 < t < t_2$ voltage source reverses polarity, $V_i(t) = -10\text{V}$ while Cap keeps its charge $V_c = 5\text{V}$ since $\tau_{\text{discharge}} = R \cdot C$ is large




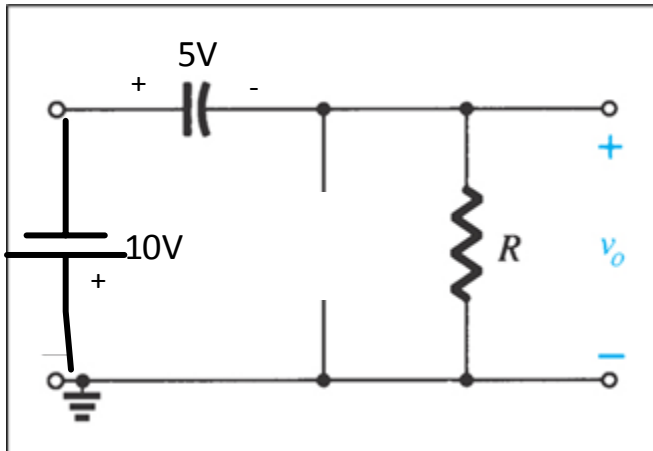KVL around the loop: $-10 - 5 - V_D(t) = 0$
 $\Rightarrow V_D(t) = -15 \text{ V} < 0, \therefore$ diode is OFF




$V_o(t) = V_D(t) = -15 \text{ V}$

$V_i(t)$

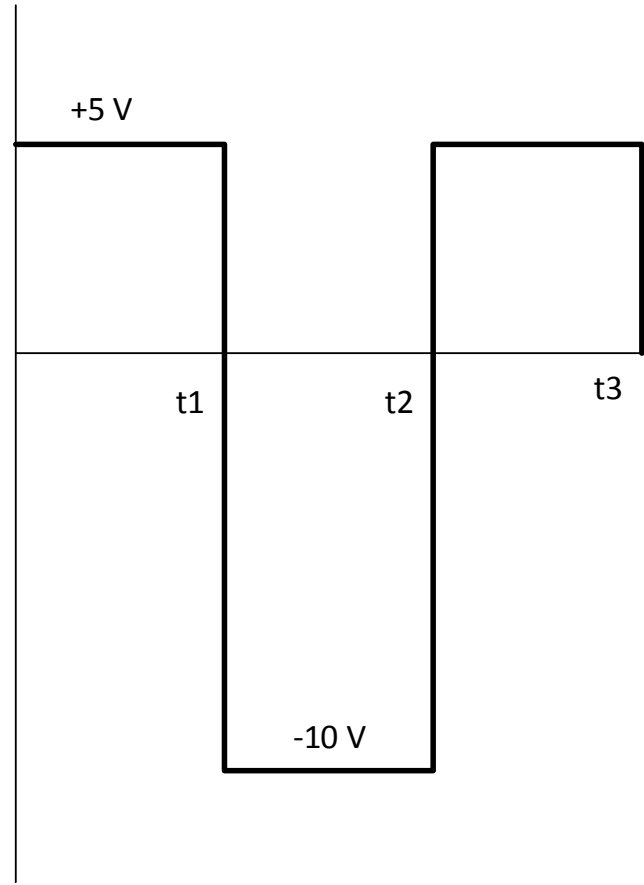

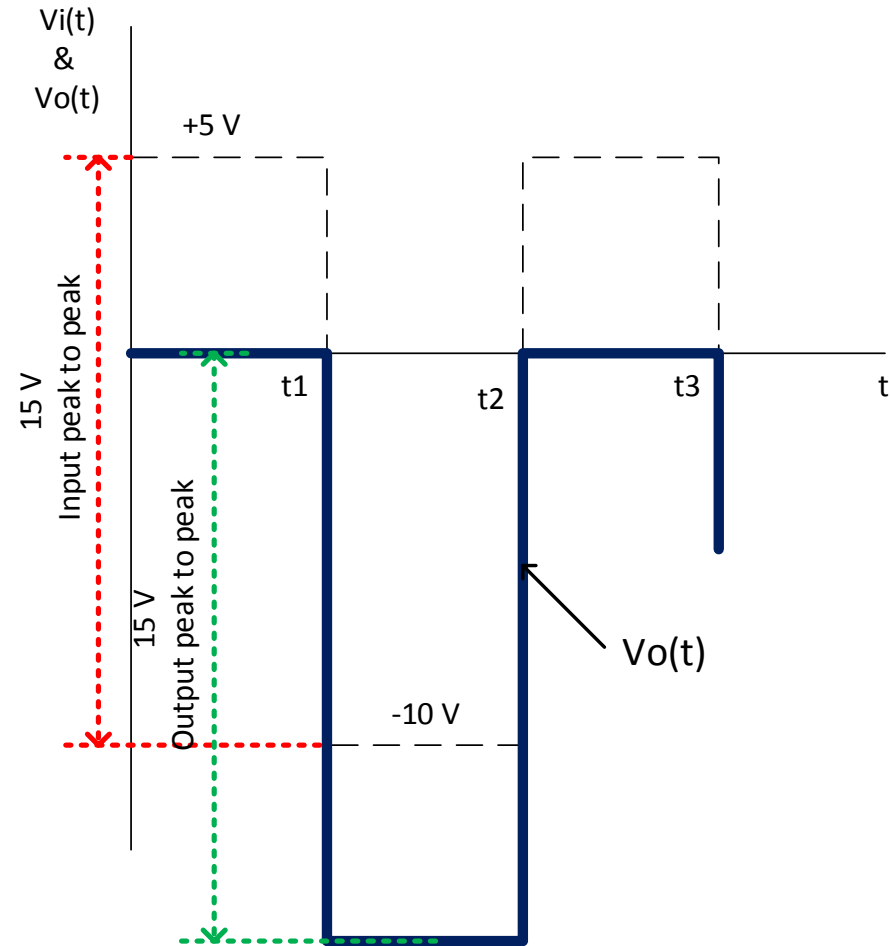
5) for $t_2 < t < t_3$, $V_i(t) = 5V$
 while $V_C = 5V$
 $V_D(t) = 5 - 5 = 0$

Diode is OFF and it will
 remain always off
 no matter what happens to $V_i(t)$
 $V_o(t) = V_D(t) = V_i(t) - 5$




Example

What happens if the diode was inverted

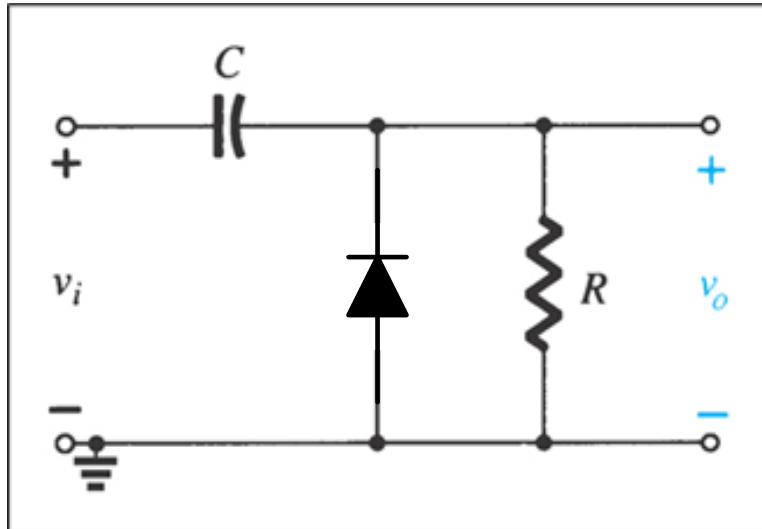

$V_i(t)$


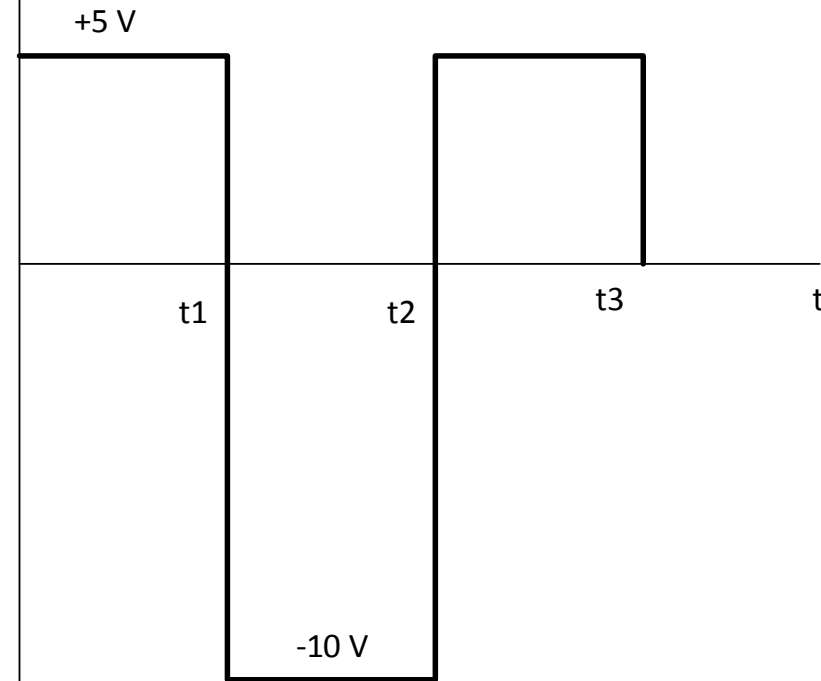


1) Consider $t_1 < t < t_2$ which makes the diode ON


$\Rightarrow D$ is ON and it is replaced by short circuit

$$V_o(t) = 0\text{ V}$$

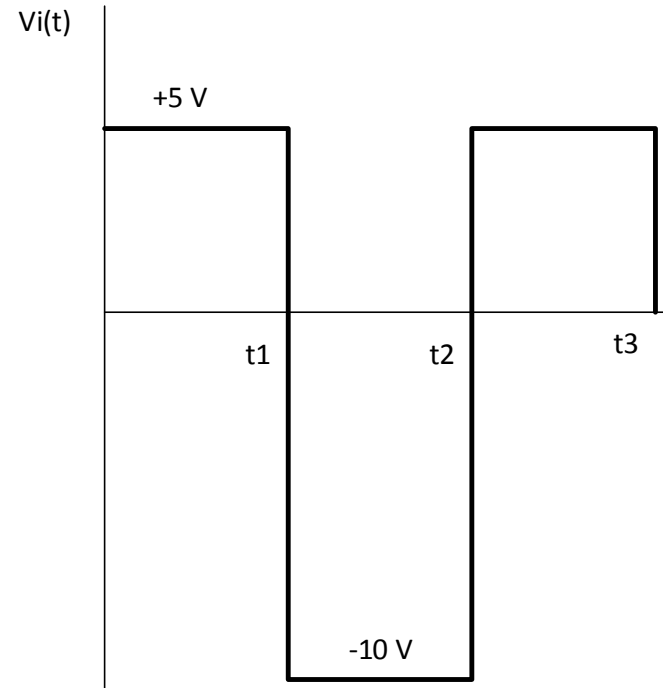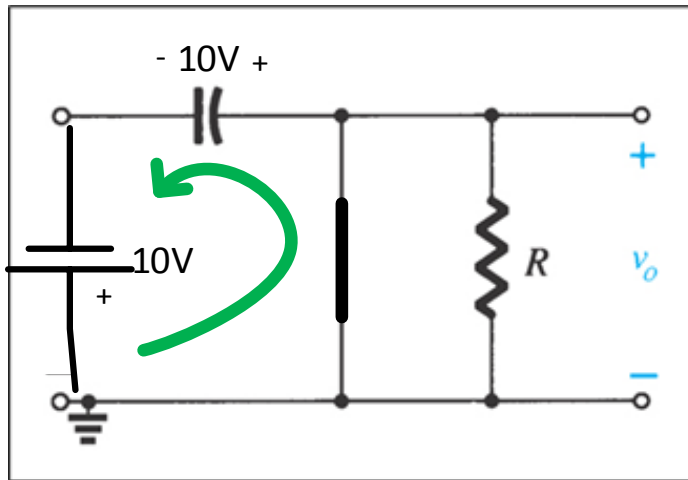
Cap is charged to 10V with shown polarity due to diode forward current $V_o(t) = 0\text{ V}$



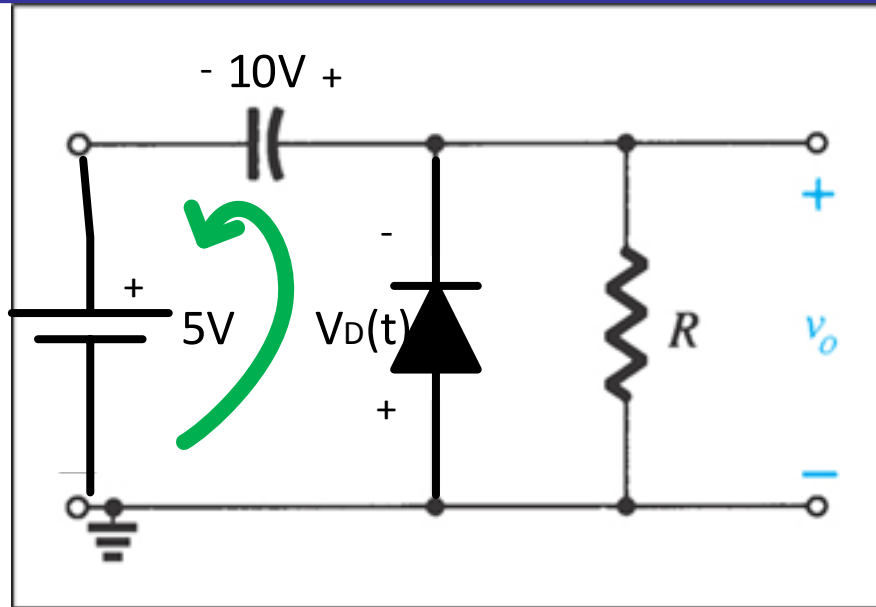
2) for $t_2 < t < t_3$ voltage source reverses polarity, $V_i(t) = +5\text{ V}$ while Cap keeps its charge $V_c = 10\text{ V}$



$V_i(t)$

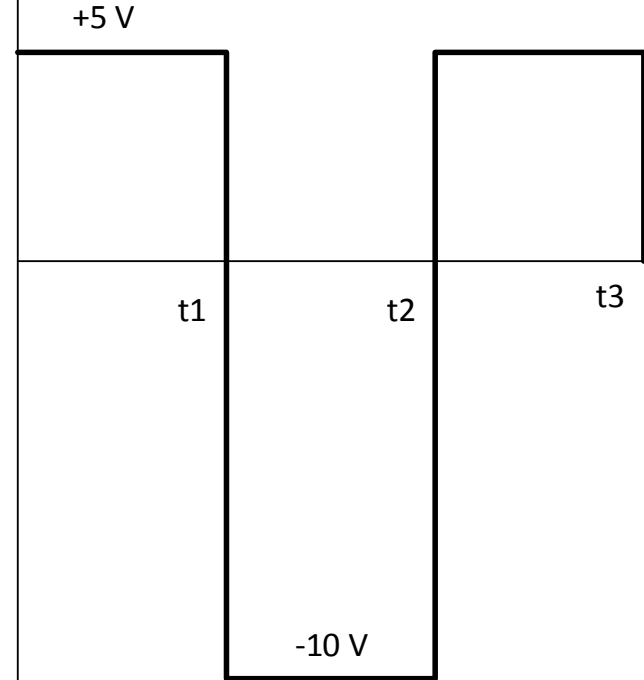

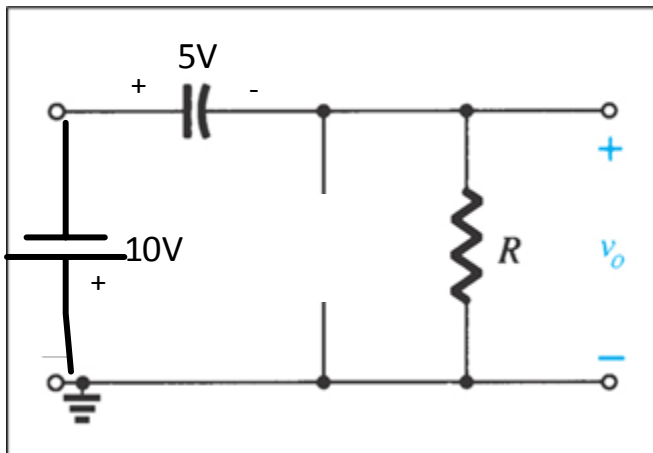KVL around the loop: $10 + 5 + V_D(t) = 0$
 $\Rightarrow V_D(t) = -15 \text{ V} < 0, \therefore$ diode is OFF



$V_o(t) = -V_D(t) = 15 \text{ V}$


Afterwards for any value of the given $V_i(t)$ diode remains OFF and $V_o(t) = V_i(t) + 10$

\therefore the clamper charges a cap and uses this charge to add up to the input to shift it up or down (i.e. add dc offset)



Important Note

For Proper Clamping action , $\tau_{discharge}$ must be large enough (at least 10 times the period of the input waveform)
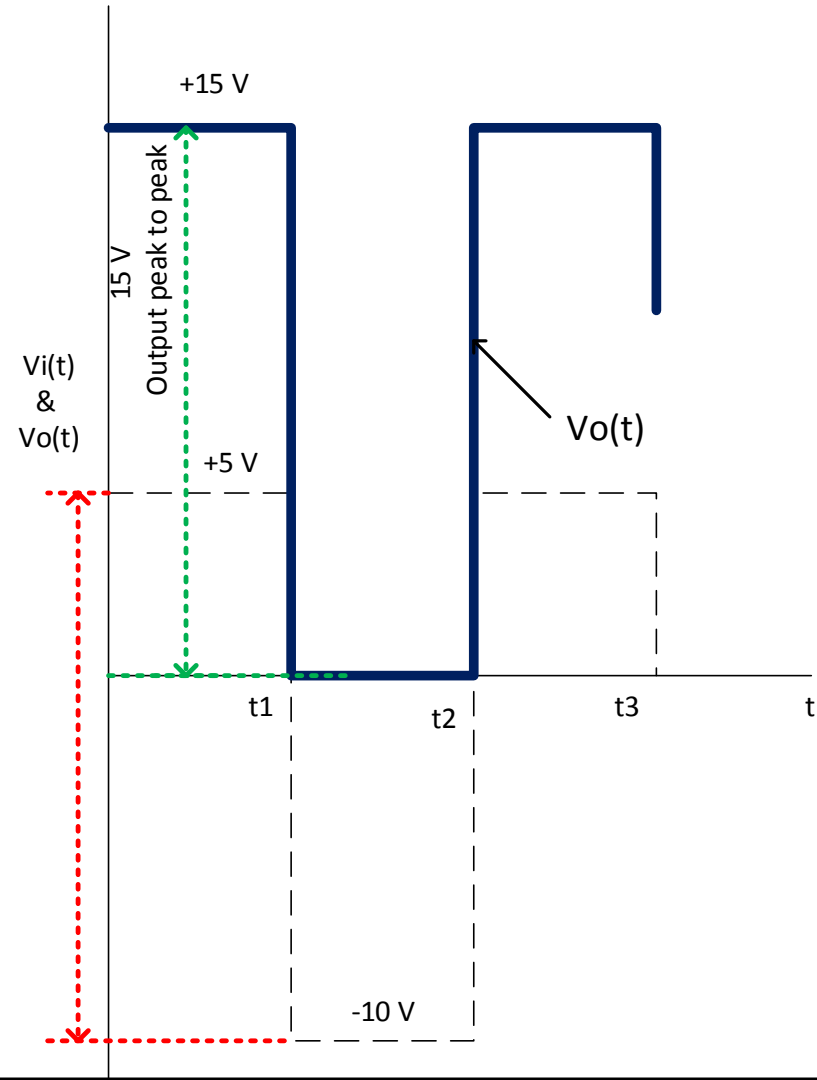
$$\tau_{discharge} = R.C > 10 (t_1 + t_2)$$



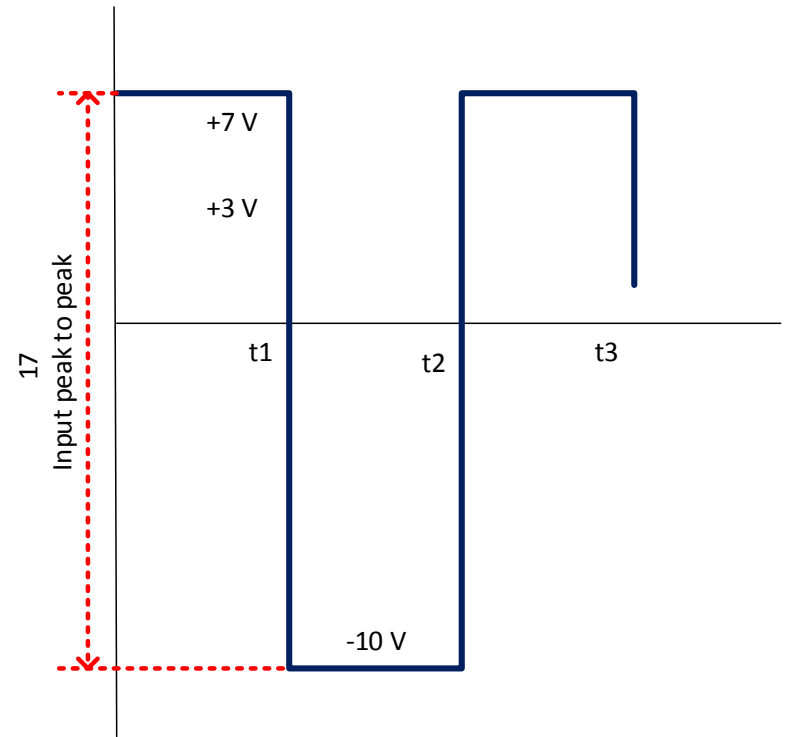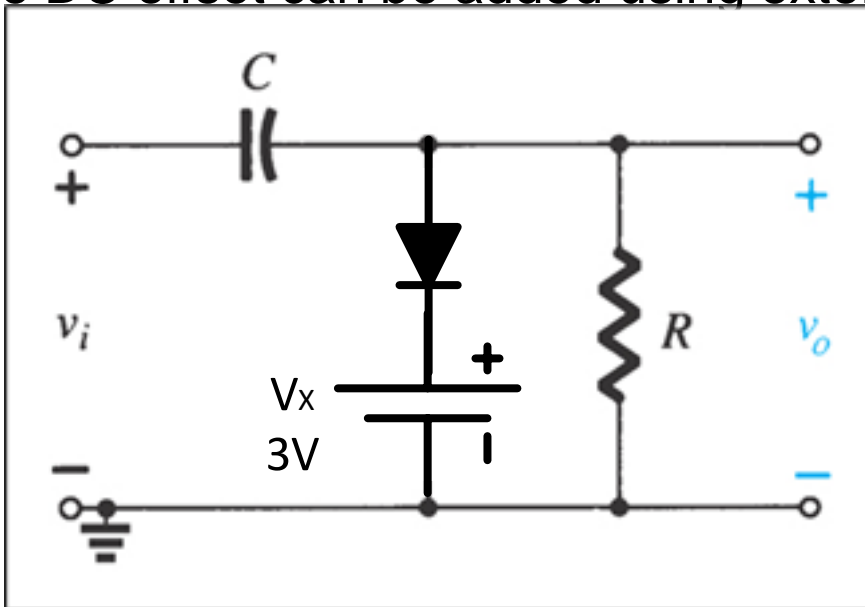
More DC offset can be added using external voltage source



1) When $V_i = +7\text{ V}$
 $7 - V_C(t) - V_X = 0$
 $\therefore V_C(t) = 7 - 3 = 4\text{ V}$
 $\Rightarrow V_O(t) = V_X = 3\text{ V}$

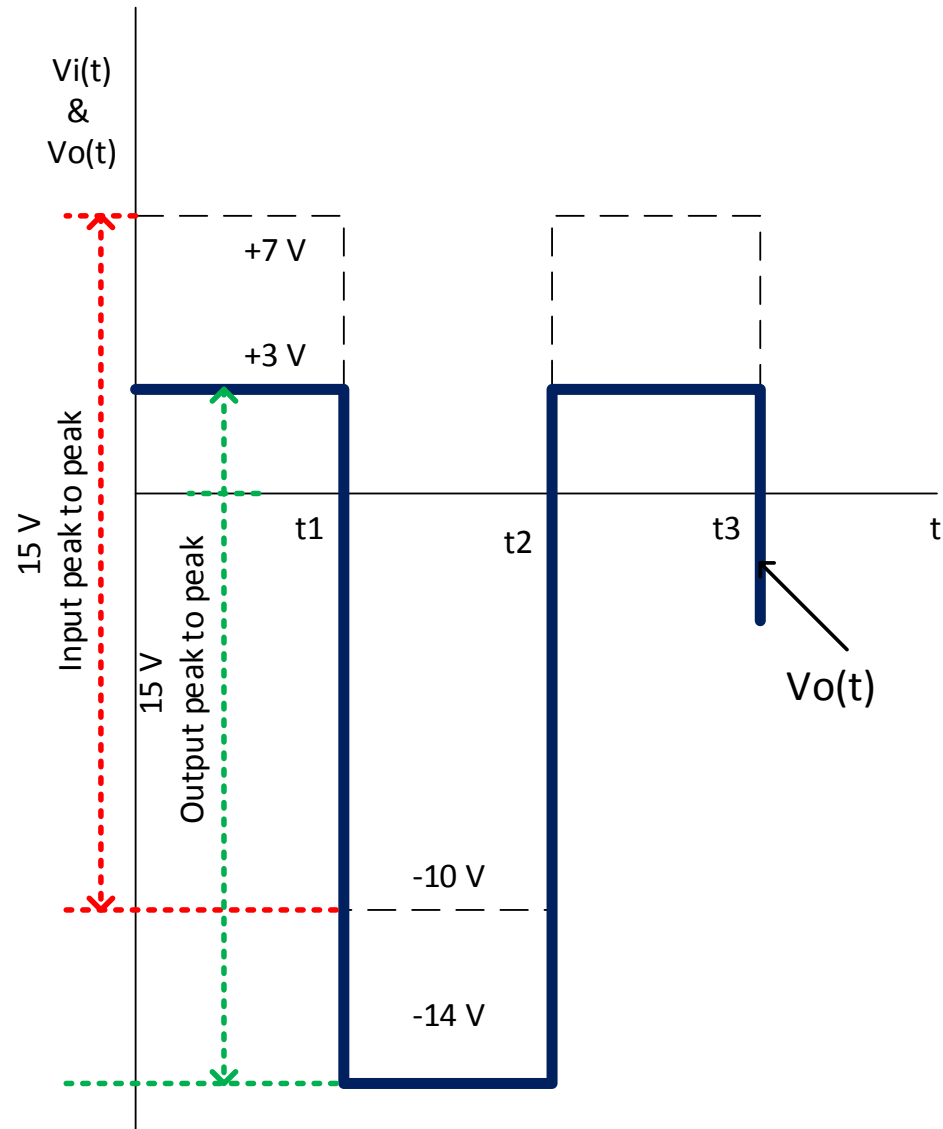
2) for $V_i = -10\text{ V}$
 $-10 - 4 - V_D(t) - 3 = 0$
 $\Rightarrow V_D(t) = -17\text{ V} < 0$ and diode is OFF

$\Rightarrow V_O(t) = V_i(t) - V_C(t)$
 $= V_i(t) - 4$
 $= -10 - 4 = -14\text{ V}$




Biased Clamper Circuits

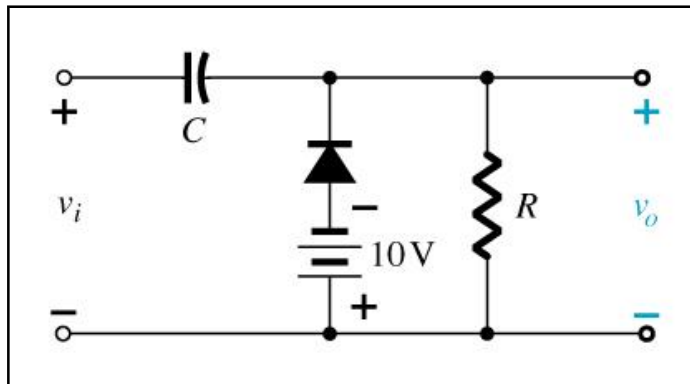The input signal can be any type of waveform such as a sine, square, or triangle wave.



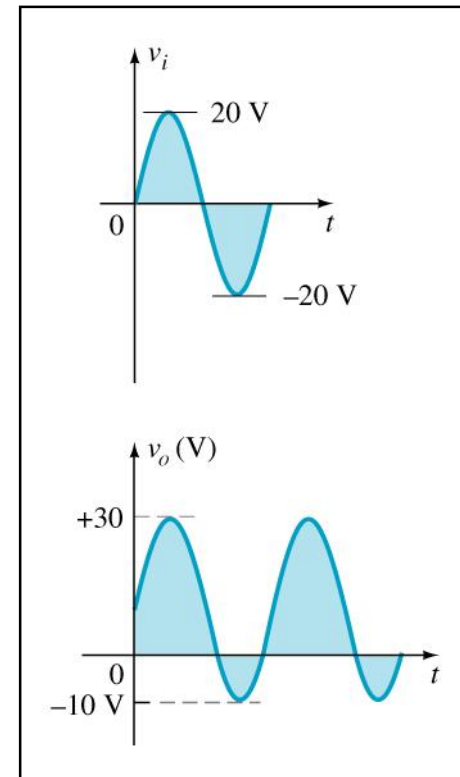The DC source lets you adjust the DC clamping level.



Summary of Clamper Circuits

Clamping Networks

