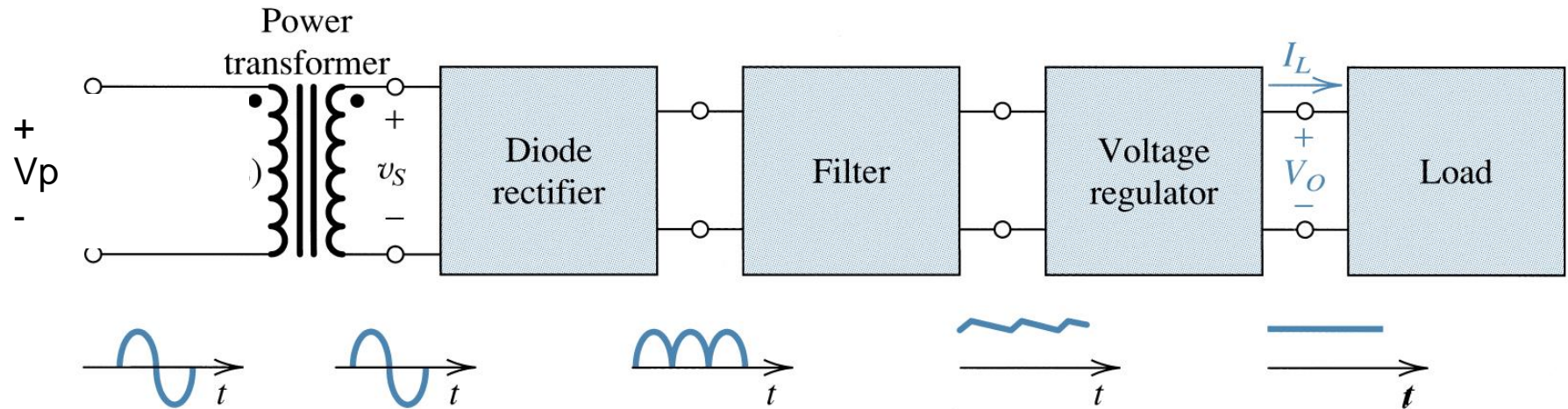


**ENEE236 & 241**

# **Analog Electronics**

**L5 Diode Applications 3**  
**Instructor: Nasser Ismail**


# Designing a power supply



Block diagram of a dc power supply.

# Designing a power supply

## 1) Transformer

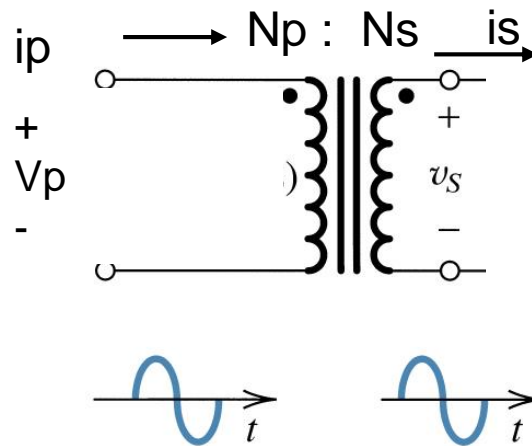

Usually steps down type to decrease the amplitude of the ac line voltage

$$\frac{V_p}{V_s} = \frac{N_p}{N_s}$$


$$\frac{i_s}{i_p} = \frac{N_p}{N_s}$$

$$n = \frac{N_s}{N_p} \quad \text{transformer turns ratio}$$

$$\Rightarrow V_s = nV_p$$

# Designing a power supply


## 2) Rectifier

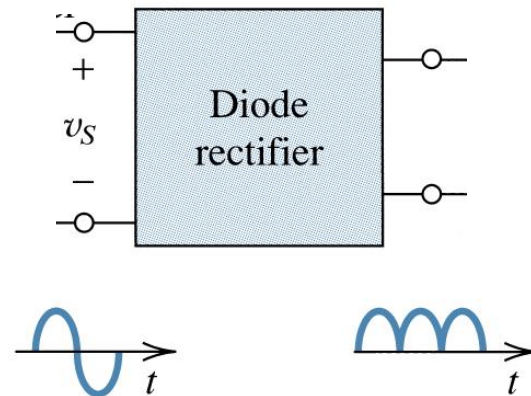


- Used to convert ac voltage (with zero average value) to pulsating dc voltage (non zero average)
- Rectifiers are two types:
  - a) Half Wave Rectifier
  - b) Full Wave Rectifier
    - Bridge Full Wave Rectifier
    - Center Tapped Transformer Full Wave Rectifier

# Half Wave Rectifier

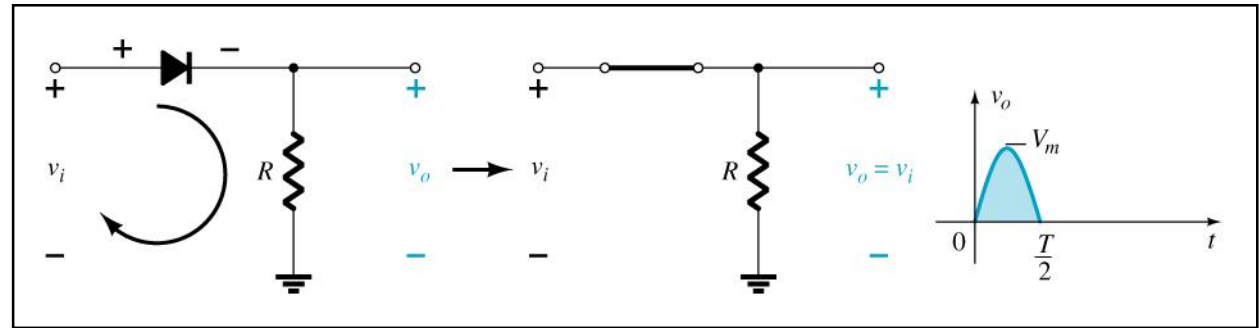1) When  $V_i(t) > 0$ ,  
 Diode is ON  
 $V_o = V_i$



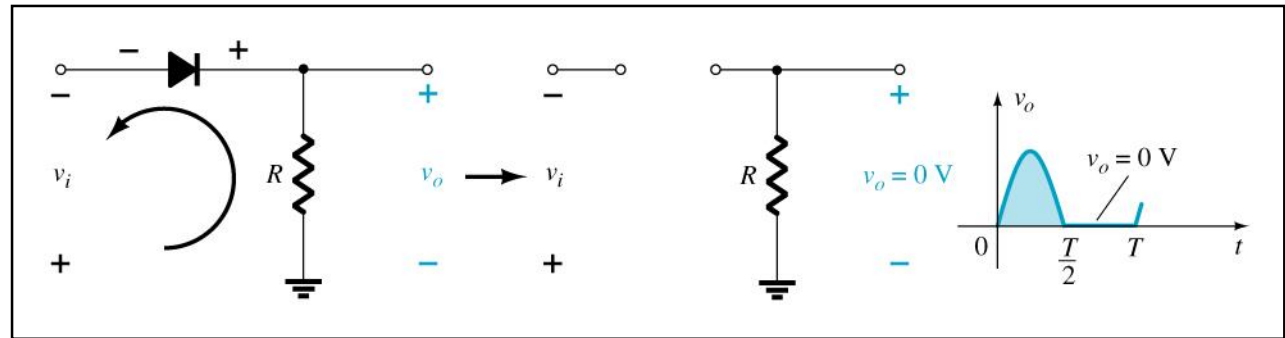2) When  $V_i(t) < 0$ ,  
 Diode is OFF  
 $V_o = 0$



The diode conducts only when it is forward biased, therefore only half of the AC cycle passes through the diode to the output.

$$V_{AVG} = \frac{1}{T} \int_0^T V_m \sin(\omega t) dt$$

# Half Wave Rectifier

$$\begin{aligned}
 V_{\text{AVG}} &= \frac{1}{T} \int_0^T V_m \sin(\omega t) dt \\
 &= \frac{1}{2\pi} \int_0^\pi V_m \sin(\theta) d\theta \\
 &= \frac{1}{2\pi} [-V_m \cos(\theta)]_0^\pi = \frac{V_m}{2\pi} [-\cos(\pi) - (-\cos(0))]
 \end{aligned}$$

$$\begin{aligned}
 V_{\text{AVG}} &= \frac{V_m}{2\pi} [ -(-1) - (-1) ] \\
 &= \frac{2V_m}{2\pi} = \frac{V_m}{\pi} \cong 0.318V_m
 \end{aligned}$$

$$T = T_o \quad \text{and} \quad f = f_o$$

(period and frequency of the rectified waveform is the same as ac input)

# Important Electrical Ratings

$I_{FM}$  - maximum Forward Current

$I_{FM}$  - maximum average current that can be safely sustained by the diode in the forward region

$$I_{FM} = \frac{V_{AVG}}{R_L}$$

$V_{RM}$  - Maximum Reverse voltage

$V_{RM}$  - Maximum voltage that can be applied to the diode in the reverse bias polarity before voltage breakdown occurs

PIV - Peak Inverse Voltage

$$PIV = V_{RM}$$

# PIV (For Half Wave Rectifier)


Because the diode is only forward biased for one-half of the AC cycle, it is also reverse biased for one-half cycle.

It is important that the reverse breakdown voltage rating of the diode be high enough to withstand the peak, reverse-biasing AC voltage.

$$V_D(t) = V_i(t)$$

$$V_D(t)_{\max} = -V_m$$

$$\text{PIV} = -V_m$$

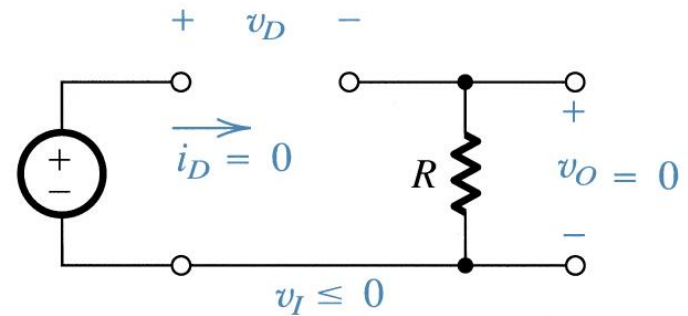




# Full-Wave Rectification

The rectification process can be improved by using a full-wave rectifier circuit.

Full-wave rectification produces a greater DC output:

$$\text{Half-wave: } V_{dc} = 0.318 V_m$$
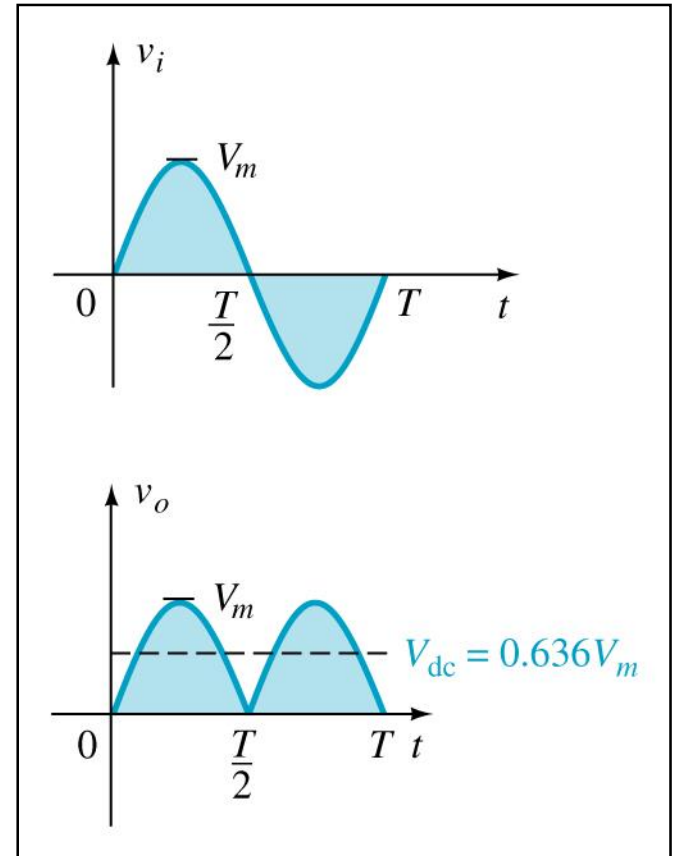
$$\text{Full-wave: } V_{dc} = 0.636 V_m$$



# Bridge Full-Wave Rectifier



A full-wave rectifier with four diodes that are connected in a bridge configuration

1) When  $V_i(t) > 0$ ,  
 D2, D3 are ON  
 D1, D4 are OFF

$$\Rightarrow V_o(t) = V_i(t)$$

2) When  $V_i(t) < 0$ ,  
 D2, D3 are OFF  
 D1, D4 are ON


$$\Rightarrow V_o(t) = -V_i(t)$$

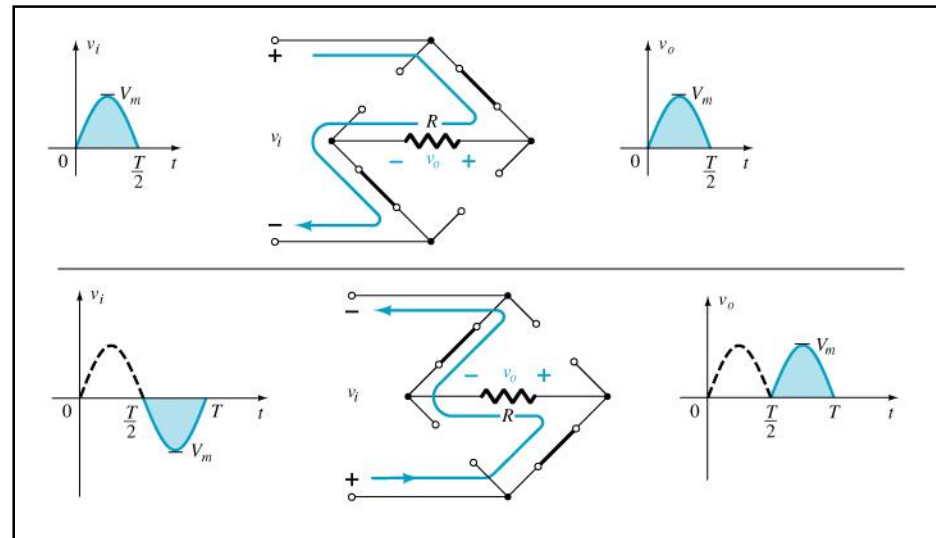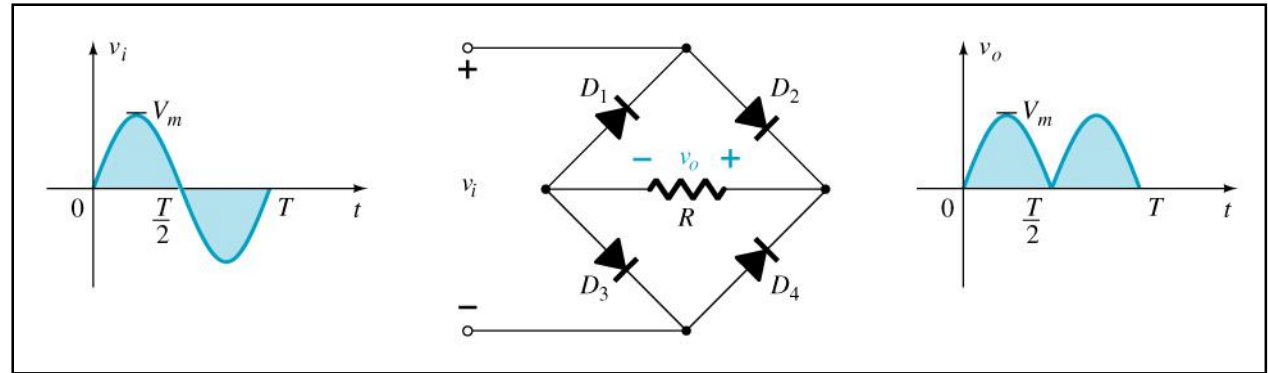
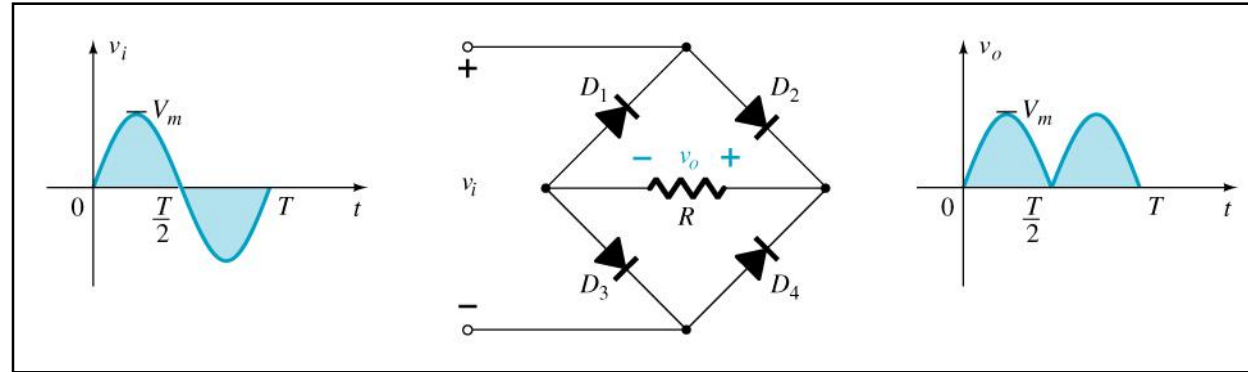
# Bridge Full-Wave Rectifier

$$V_{\text{AVG}} = \frac{1}{T} \int_0^T V_m \sin(\omega t) dt$$

$$= \frac{1}{\pi} \int_0^{\pi} V_m \sin(\theta) d\theta$$



$$V_{\text{AVG}} = \frac{2V_m}{\pi} \cong 0.636V_m$$

$$T = \frac{T_o}{2} \text{ and } f = 2f_o$$

(period and frequency of the rectified waveform is not the same as ac input)


# PIV for each of the 4 diodes

For ideal diode


$$V_{D1}(t) = -V_i(t)$$

$$V_{D1}(t)_{\max} = -V_m$$


$$\text{PIV} = -V_m$$

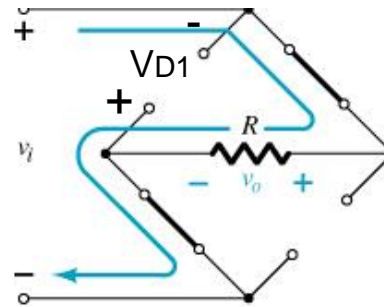
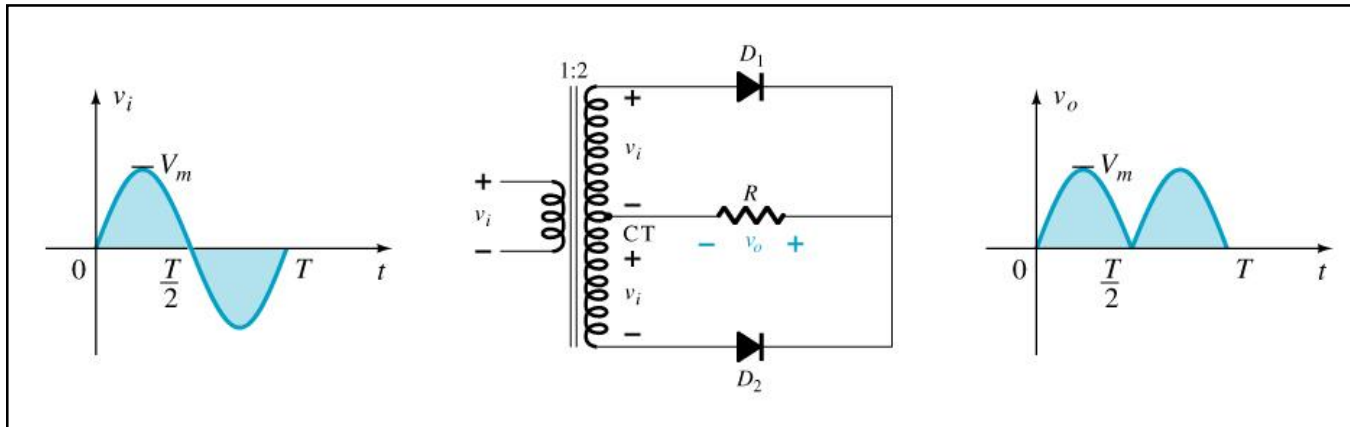
# Center Tapped Transformer Full-Wave Rectifier



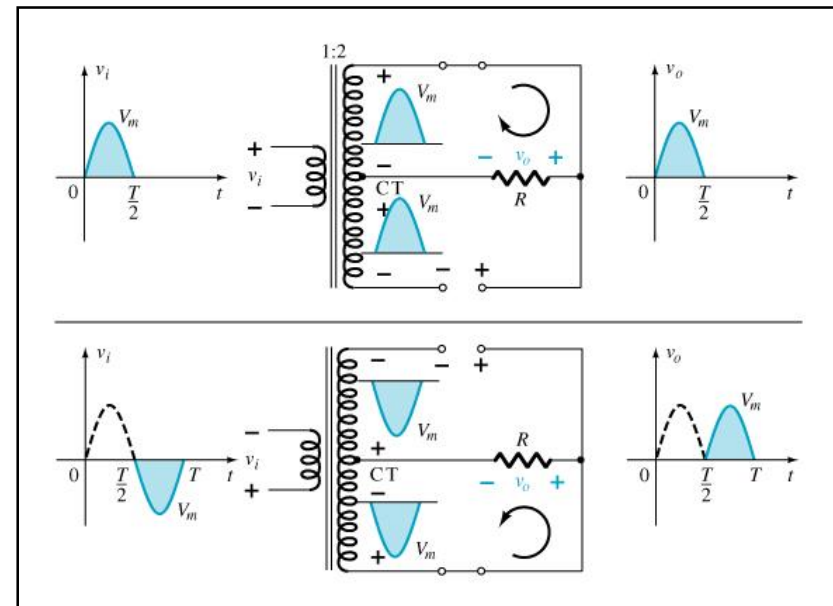Requires two diodes and a center-tapped transformer



# CT Transformer Full-Wave Rectifier

1) When  $V_i(t) > 0$ ,

D1 is ON

D2 is OFF


$$\Rightarrow V_o(t) = V_i(t)$$

2) When  $V_i(t) < 0$ ,

D1 is OFF

D2 is ON


$$\Rightarrow V_o(t) = -V_i(t)$$

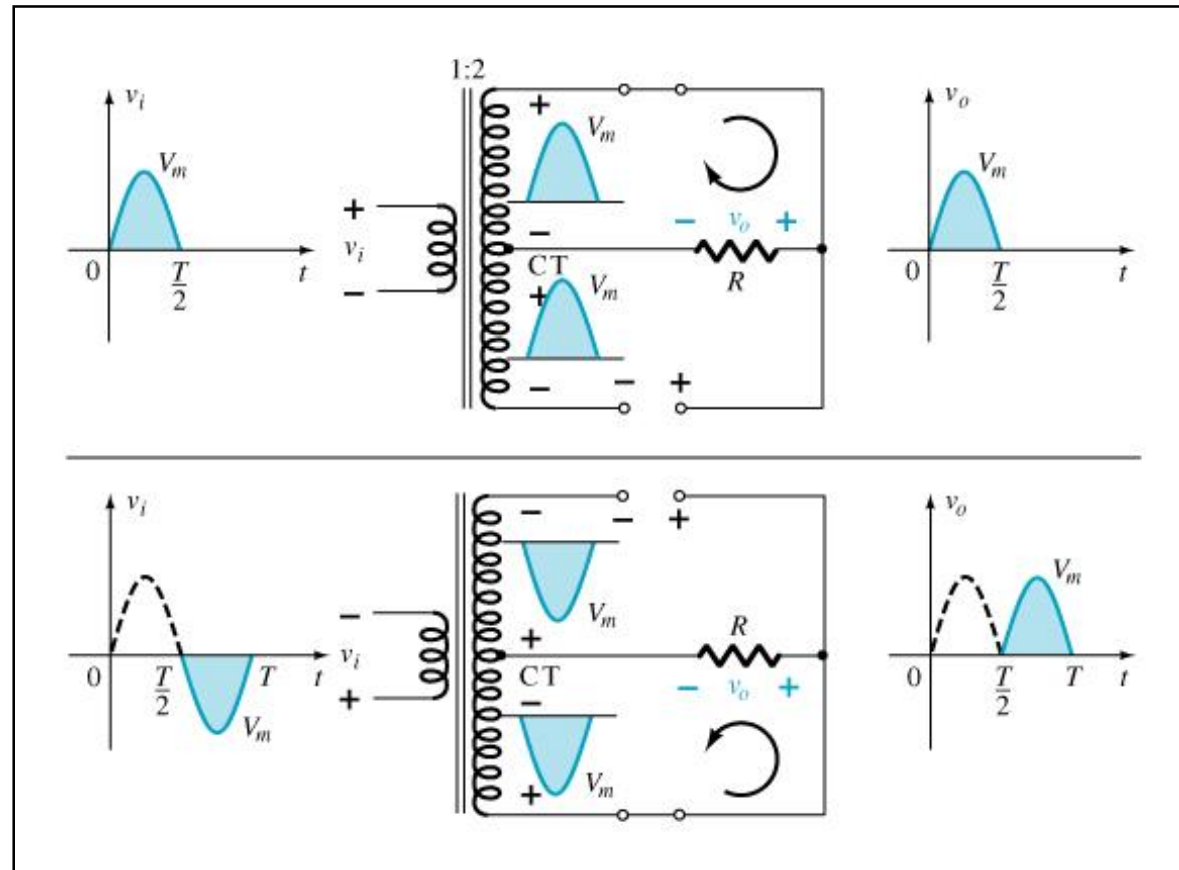


$$V_{AVG} = \frac{2V_m}{\pi} \cong 0.636V_m$$

$$T = \frac{T_o}{2} \text{ and } f = 2f_o$$

# CT Full-wave rectifier

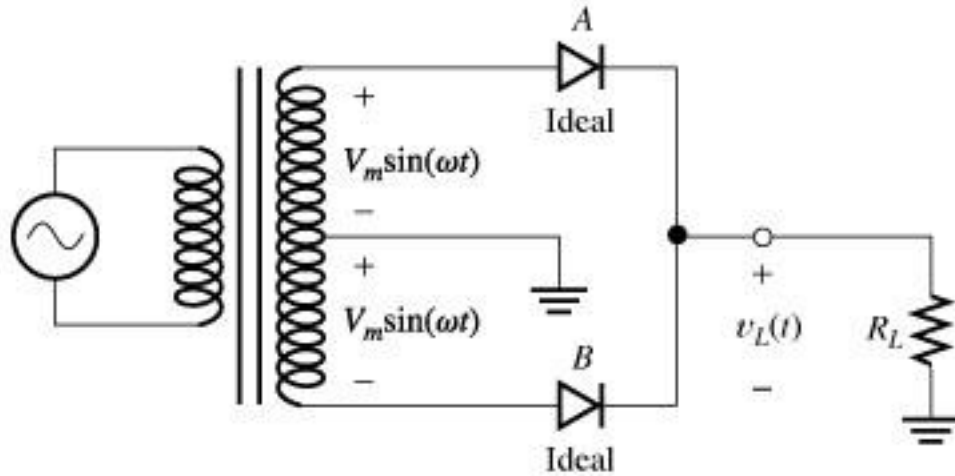

(a) Circuit diagram

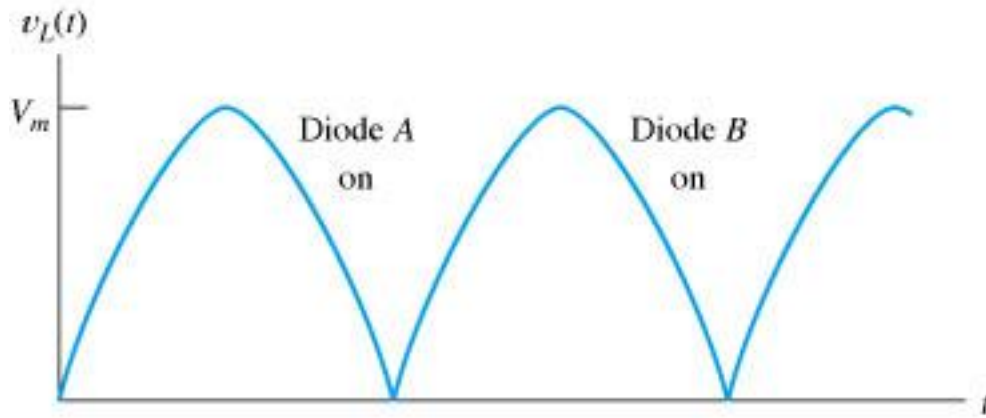

(b) Output voltage

# Summary of Rectifier Circuits


In the center tapped transformer rectifier circuit, the peak AC voltage is the transformer secondary voltage to the tap.

Rectifier	Ideal $V_{DC}$	Realistic $V_{DC}$
Half Wave Rectifier	$V_{DC} = 0.318 V_m$	$V_{DC} = 0.318 V_m - 0.7$
Bridge Rectifier	$V_{DC} = 0.636 V_m$	$V_{DC} = 0.636 V_m - 2(0.7 \text{ V})$
Center-Tapped Transformer Rectifier	$V_{DC} = 0.636 V_m$	$V_{DC} = 0.636 V_m - 0.7 \text{ V}$

$V_m$  = the peak AC voltage




### 3) Filter

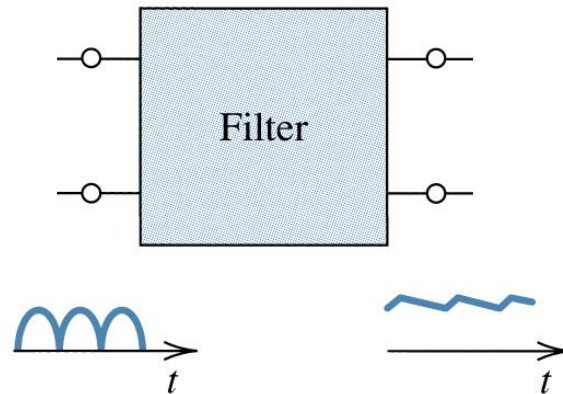


- One of dc power supply components
- Used to smooth out (remove) the pulsating DC produced by the rectifiers and to pass only the DC component
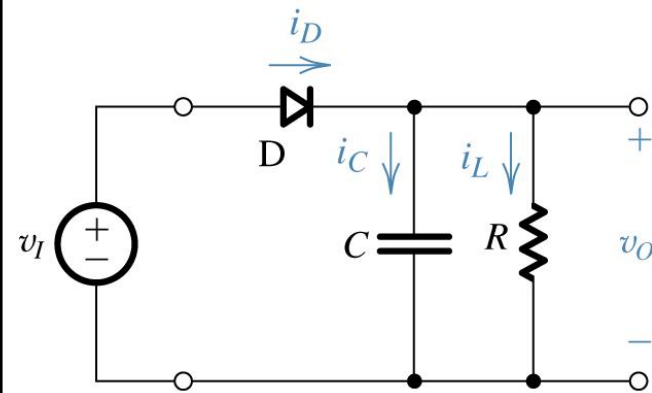
# Half-wave rectifier with smoothing (Filter) capacitor




(a)

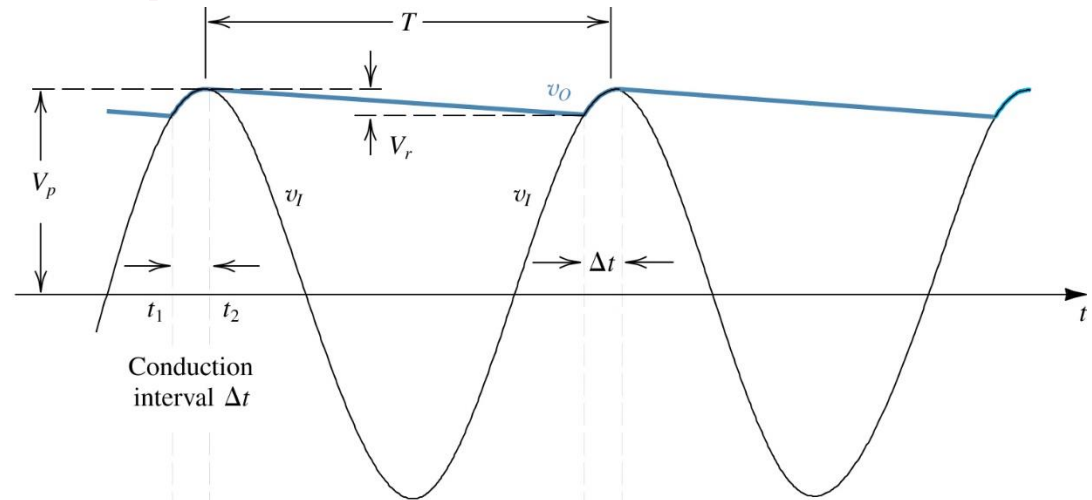- 1) When  $V_i(t) > V_c(t)$ , diode is ON and capacitor is charged
- 2) When  $V_i(t) < V_c(t)$ , diode is OFF and capacitor is discharged through R



(b)

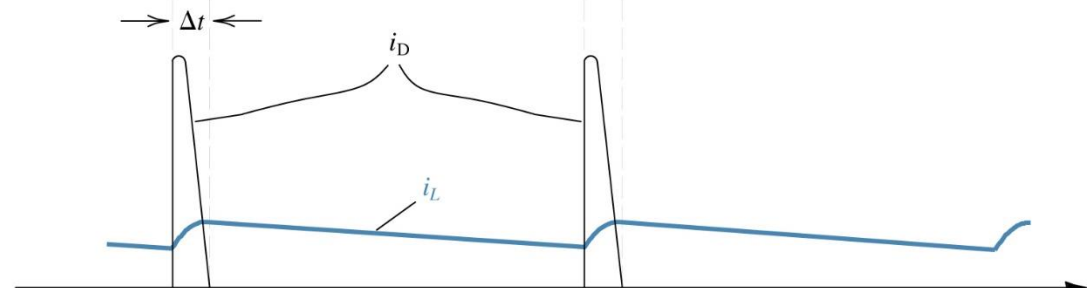


(c)

Voltage and current waveforms in half wave rectifier (peak detector) with  $CR \gg T$ . ( The diode is assumed ideal)

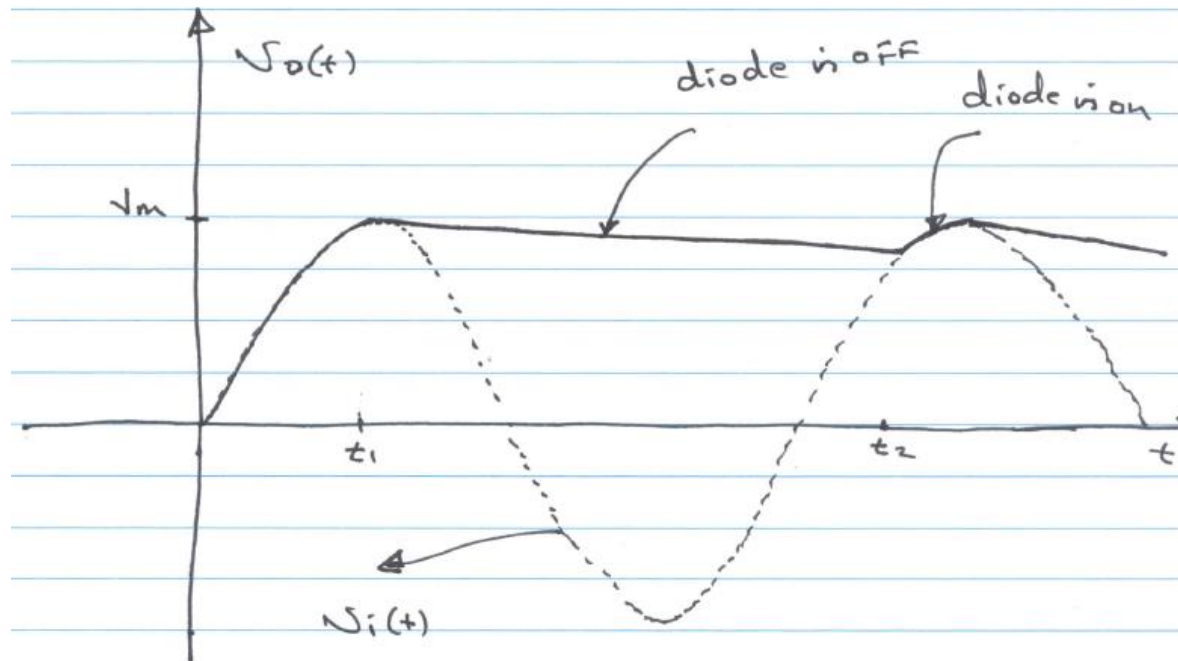
## Ripple Factor

Is an indication of the effectiveness of the filter




$$r\% = \frac{\text{RMS value of ripple voltage}}{\text{Average Value of output signal}} \cdot 100\%$$

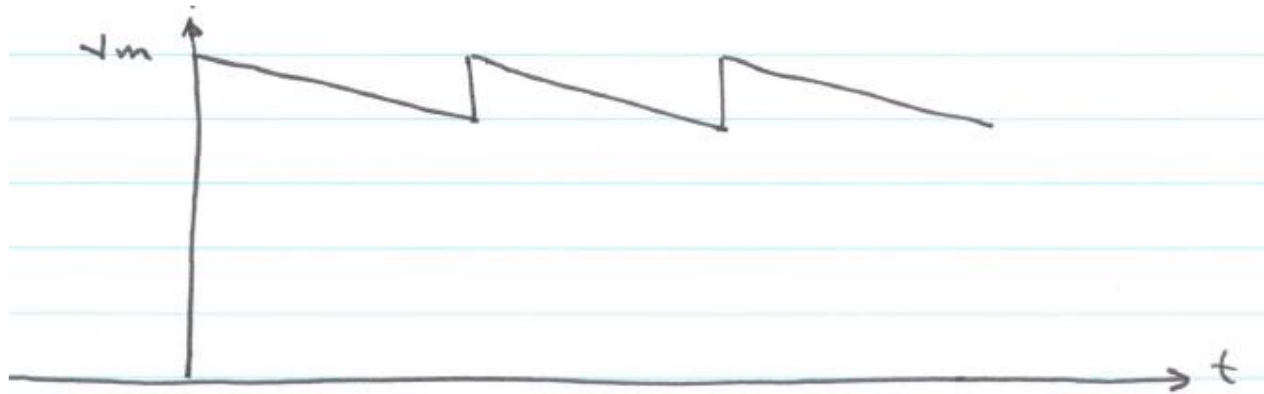The Output Voltage can be approximated as




$\Leftarrow$  DC voltage

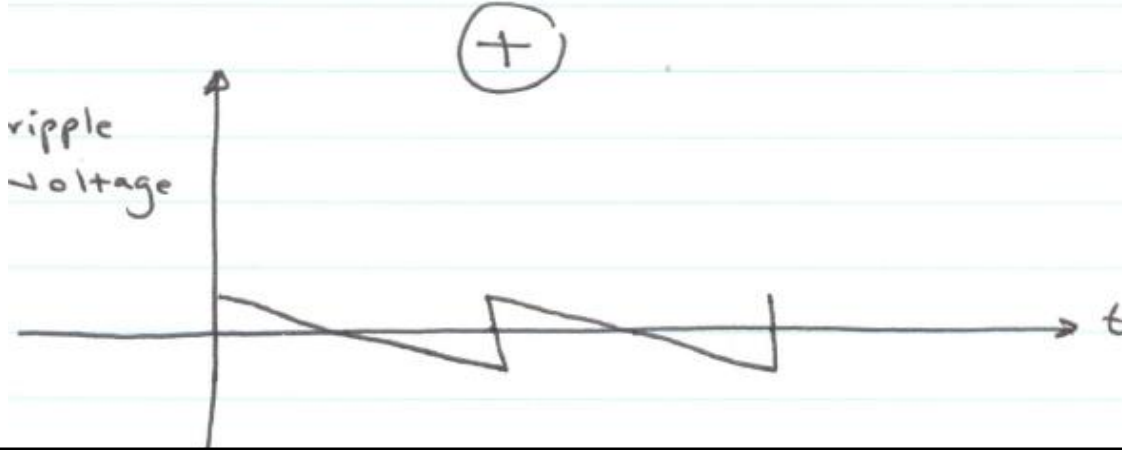

$\Leftarrow$  Ripple Voltage

The smaller the ripple voltage, the closer we get to DC

## Example

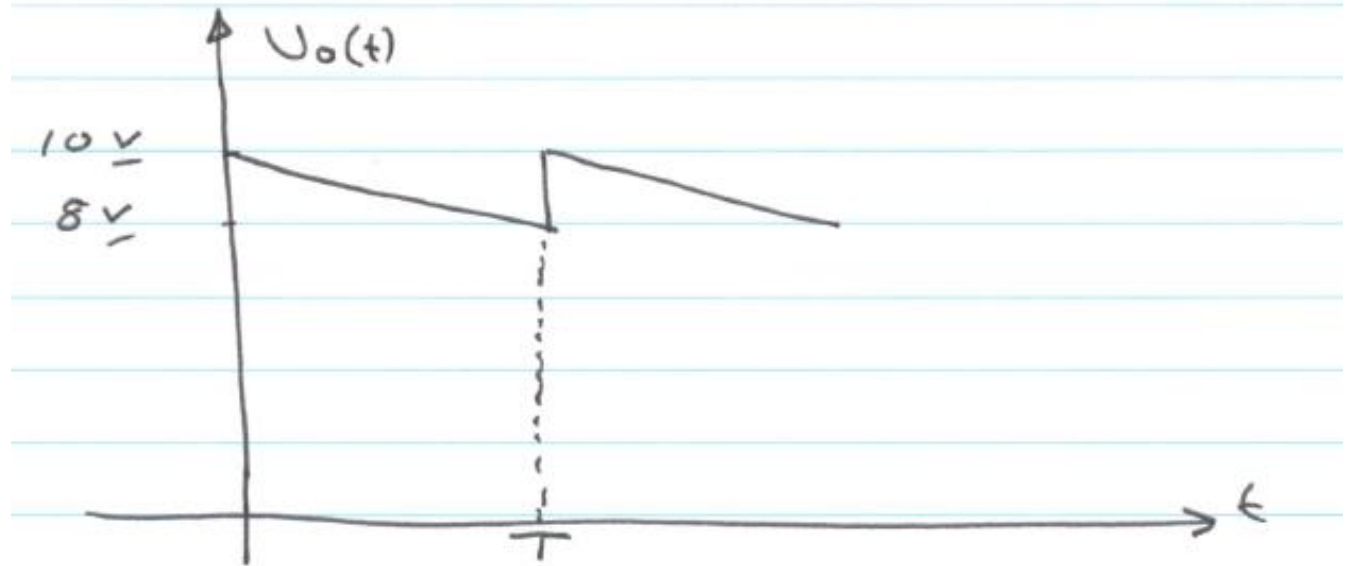

$$V_{O,DC} = V_{O,AVG} = \frac{1}{T} \int_0^T V_O(t) dt$$

$$= \frac{1}{T} (\text{Area})$$

$$= \frac{1}{T} \left( 8T + \frac{2T}{2} \right) = 9 \text{ V}$$

OR

$$V_{O,DC} = V_m - \frac{1}{2} V_{Lr,p-p}$$

where  $V_m = 10$

$$V_{Lr,p-p} = 2$$

$$V_{O,DC} = 10 - \frac{1}{2} \cdot 2 = 9 \text{ V}$$

**Also , for a triangular signal, the RMS value**


$$\text{RMS Value} = \frac{\text{Peak Value}}{\sqrt{3}}$$

OR

$$\text{RMS Value} = \frac{\text{Peak to peak Value}}{2\sqrt{3}} = \frac{V_{Lr,p-p}}{2\sqrt{3}}$$

$$\therefore r \% = \frac{\frac{V_{Lr,p-p}}{2\sqrt{3}}}{V_m - \frac{1}{2} V_{Lr,p-p}} \cdot 100\%$$

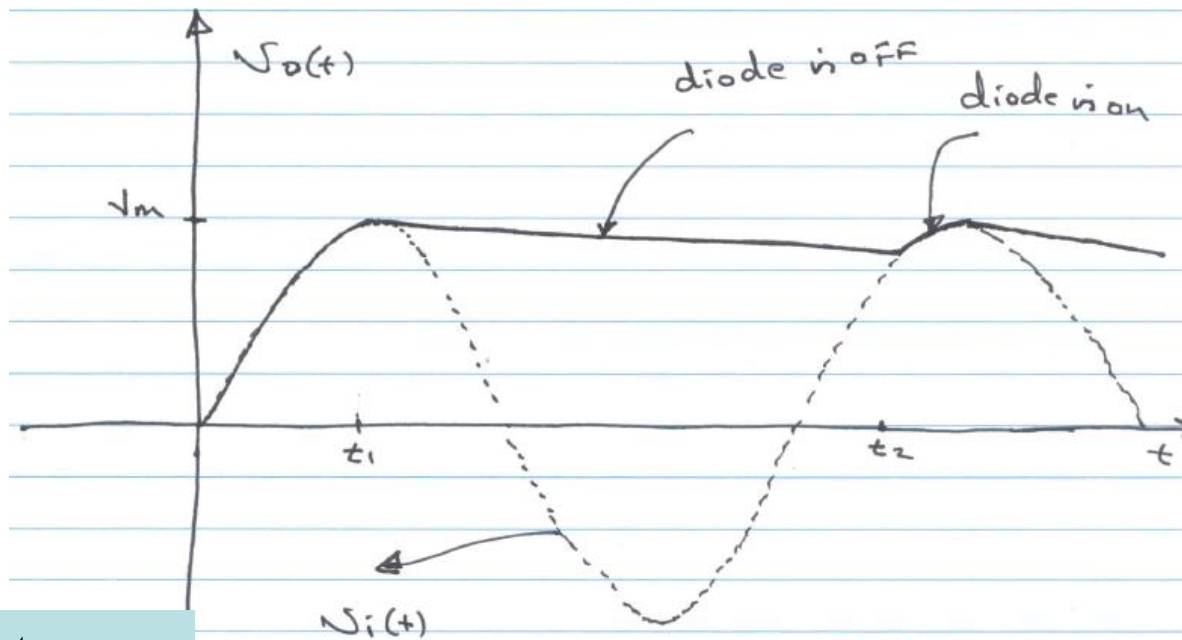⇒ To Determine the ripple factor we need to find the peak to peak ripple  $V_{Lr,p-p}$



For  $t_2 > t > t_1$

$$V_L(t) = V_m e^{\frac{-(t-t_1)}{RC}}$$

$$V_{Lr,p-p} = V_m \left[ 1 - e^{\frac{-(t_2-t_1)}{RC}} \right]$$

For  $t_2 > t > t_1$

$$V_{Lr,p-p} = V_L(t_1) - V_L(t_2)$$

$$V_{Lr,p-p} = V_m - V_m e^{\frac{-(t_2-t_1)}{RC}}$$

using  $e^{-x} \cong 1 - x$

using  $e^{-x} \cong 1 - x$

$$V_{Lr,p-p} = V_m \left[ 1 - e^{-\frac{(t_2 - t_1)}{RC}} \right] \Rightarrow V_{Lr,p-p} = V_m \left( \frac{(t_2 - t_1)}{RC} \right)$$

$$V_{L,dc} = V_m - \frac{1}{2} V_{Lr,p-p}$$



a) For Half Wave Rectifier

$$t_2 - t_1 \cong T_o = \frac{1}{f_o}$$

$$V_{Lr,p-p} = V_m \left( \frac{T_o}{RC} \right) = V_m \left( \frac{1}{f_o RC} \right)$$

$$V_{L,dc} = V_m \left( 1 - \frac{1}{2f_o RC} \right)$$

$$(V_{L,r})_{RMS} = \frac{V_{Lr,p-p}}{2\sqrt{3}}$$

$$(V_{L,r})_{RMS} = \frac{V_m}{2\sqrt{3}f_o RC}$$

$$\therefore r \% = \frac{(V_{L,r})_{RMS}}{V_{L,dc}} 100\%$$

$$\therefore r \% = \frac{1}{\sqrt{3}[2f_o RC - 1]} 100\%$$

## b) For Full Wave Rectifier

$$t_2 - t_1 \cong \frac{1}{2} T_o = \frac{1}{2f_o}$$


$$V_{Lr,p-p} = V_m \left( \frac{T_o}{2RC} \right) = V_m \left( \frac{1}{2f_o RC} \right)$$

$$V_{L,dc} = V_m \left( 1 - \frac{1}{4f_o RC} \right)$$

$$(V_{L,r})_{RMS} = \frac{V_{Lr,p-p}}{2\sqrt{3}}$$

$$(V_{L,r})_{RMS} = \frac{V_m}{4\sqrt{3}f_o RC}$$
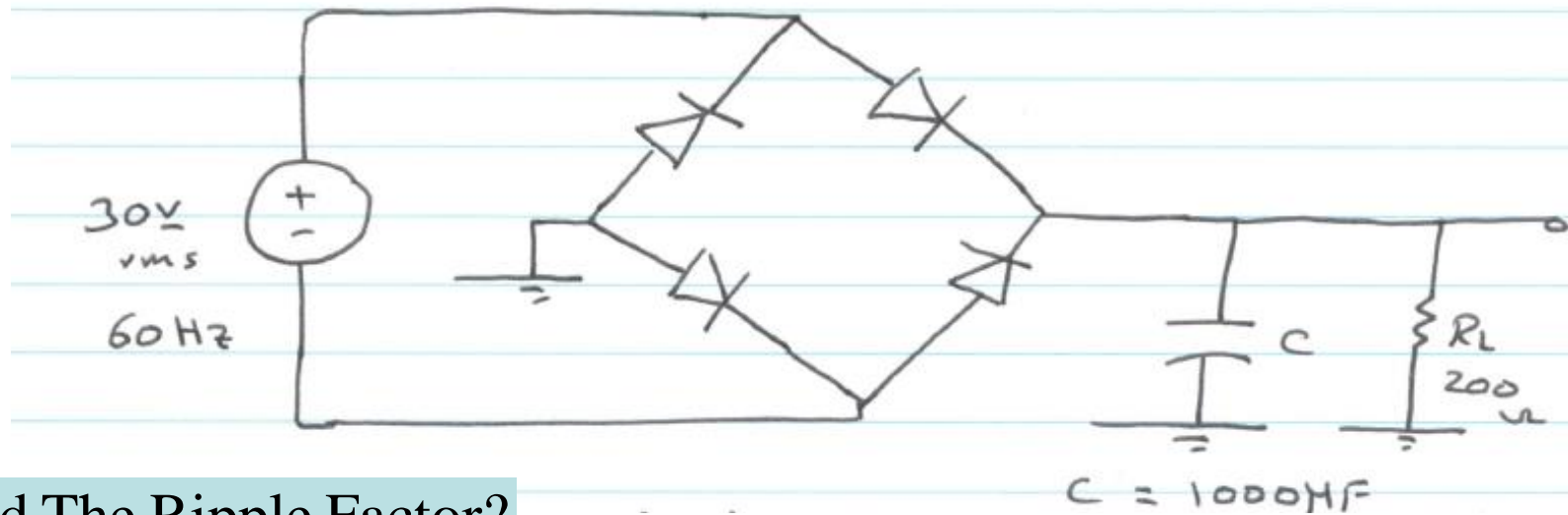
$$\therefore r \% = \frac{1}{\sqrt{3}[4f_o RC - 1]} 100\%$$



Find The Ripple Factor?

$$V_{L,dc} = V_m \left( 1 - \frac{1}{4f_o RC} \right) = 30\sqrt{2} \left( 1 - \frac{1}{4 * 60 * 200 * 1000\mu 0} \right) = 41.54 \text{ V}$$

$$V_{Lr,p-p} = V_m \left( \frac{T_o}{2RC} \right) = V_m \left( \frac{1}{2f_o RC} \right) = 1.7677 \text{ V}$$

$$\left( V_{L,r} \right)_{RMS} = \frac{V_{Lr,p-p}}{2\sqrt{3}} = 0.51 \text{ V}_{RMS} \quad \therefore r \% = \frac{0.51 \text{ V}}{41.54 \text{ V}} \cdot 100\% = 1.2272 \%$$