

ENEE236 & 241

Analog Electronics


L6 Diode Applications 4
Instructor: Nasser Ismail

Zener Diode

Simple Voltage Regulator

- *The Zener is used as a voltage regulator to maintain a constant dc output under variations in load current and ac line voltage*
- *It can also be used as protection device against overvoltage*
- *Analysis starts by defining state of diode followed by using appropriate model, then find unknown quantities*


Voltage Regulator

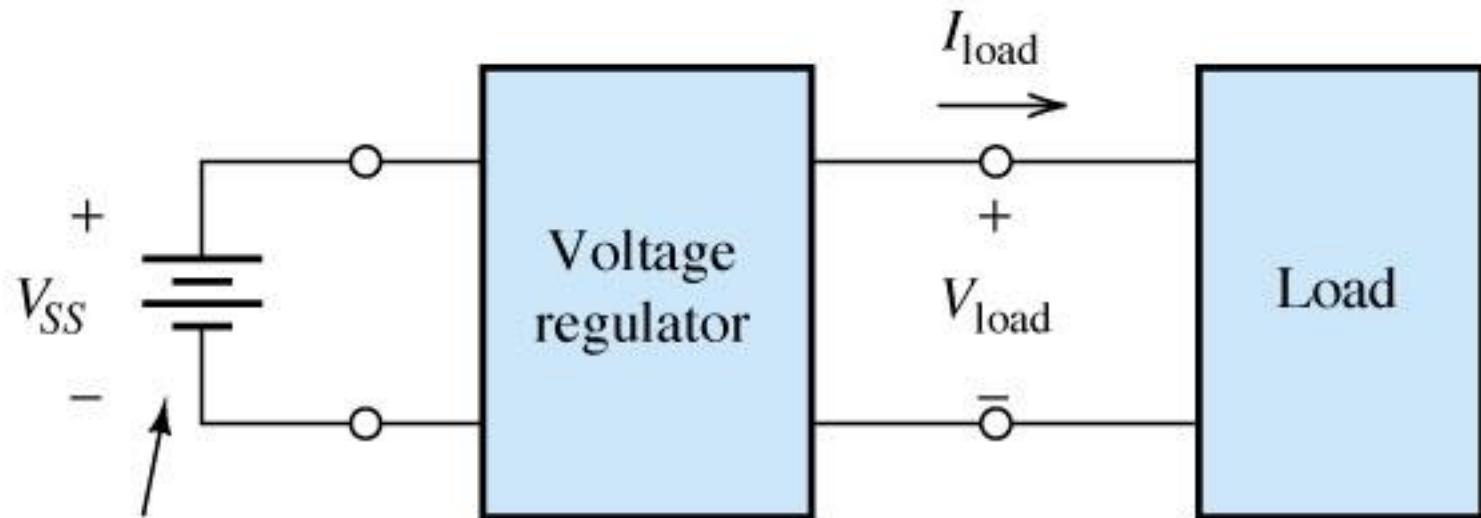

Variable source

A voltage regulator supplies constant voltage to a load.


Zener Diode V-I Curve

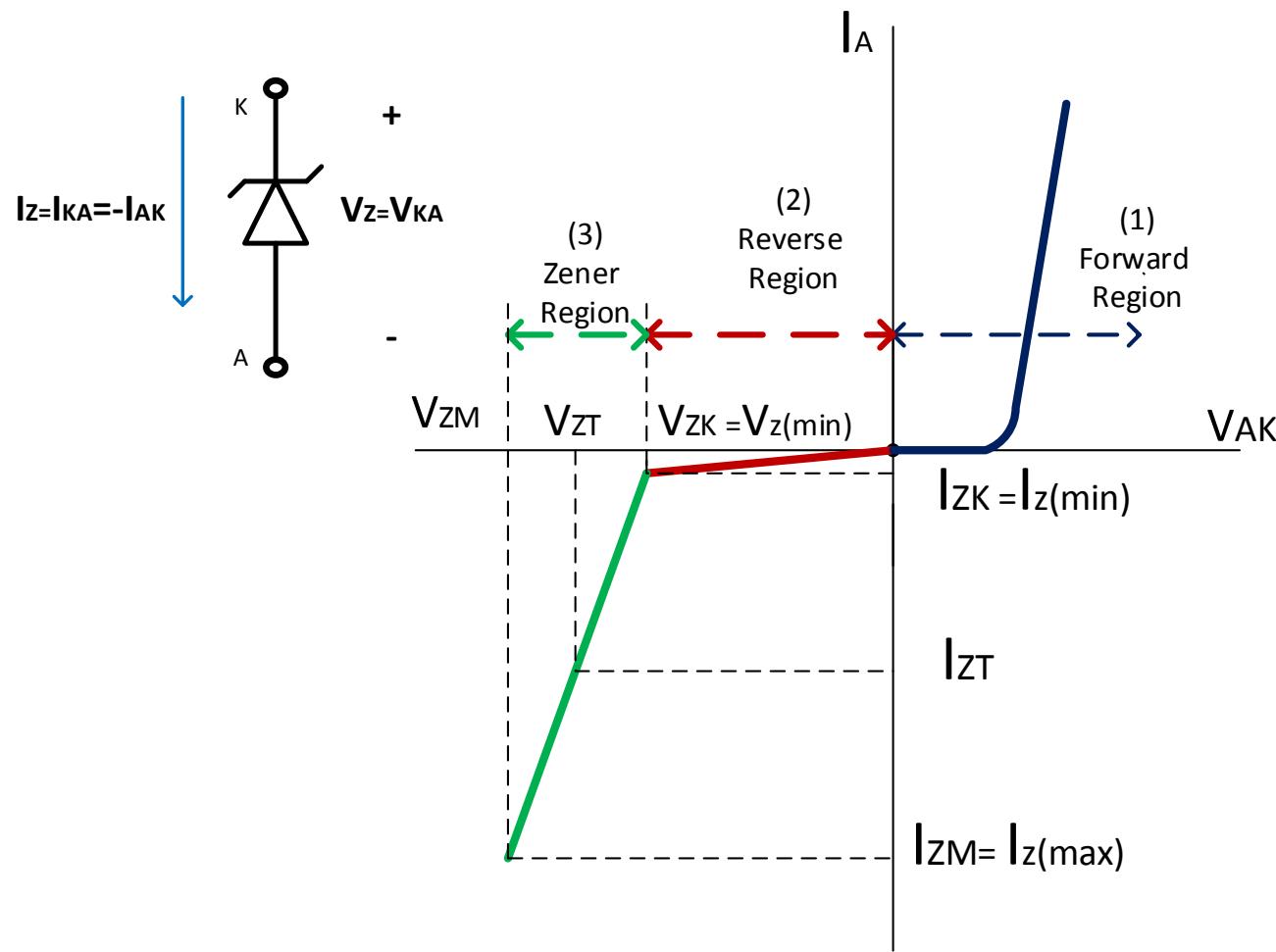

- If $I_{zK} < I_z < I_{zmax}$ zener will be in voltage regulation (zener) region

- In data sheet , we have I_{zT} , V_{zT}
- Zener currents will be assumed positive if passing from cathode to Anode
- If $I_z < I_{zK}$ zener will act as an open circuit
- If $I_z > I_{zmax}$ zener will damaged

Zener Diode Operation Regions

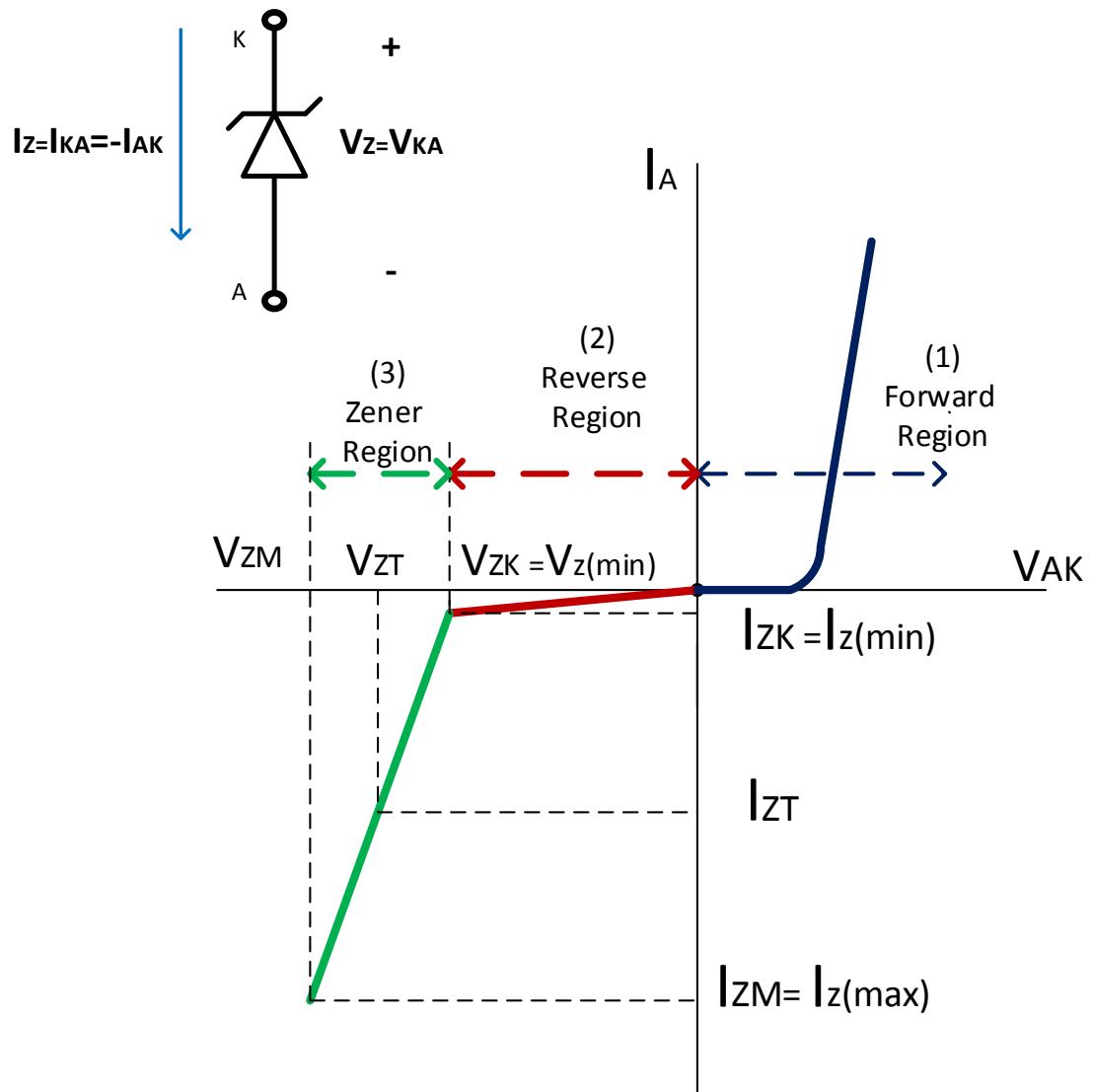

Region (1)

- When $V_{AK} > 0$, zener acts as regular diode ON
- Region (2)
- When $V_{zK} < V_{AK} < 0$, zener acts as regular diode OFF

➤ Region (3)
When $V_{ZK} > V_{AK}$,
This is the intended
operating region ,and the
zener acts as a voltage
regulator

➤ And $V_z = V_{KA}$,it can be replaced by either a battery or a battery in series with resistor r_Z

Zener Diode Operation & Models


The Zener is a diode that is operated in reverse bias at the Zener Voltage (V_z).

Conditions for zener diode to operate in the breakdown (Zener/ON) region When

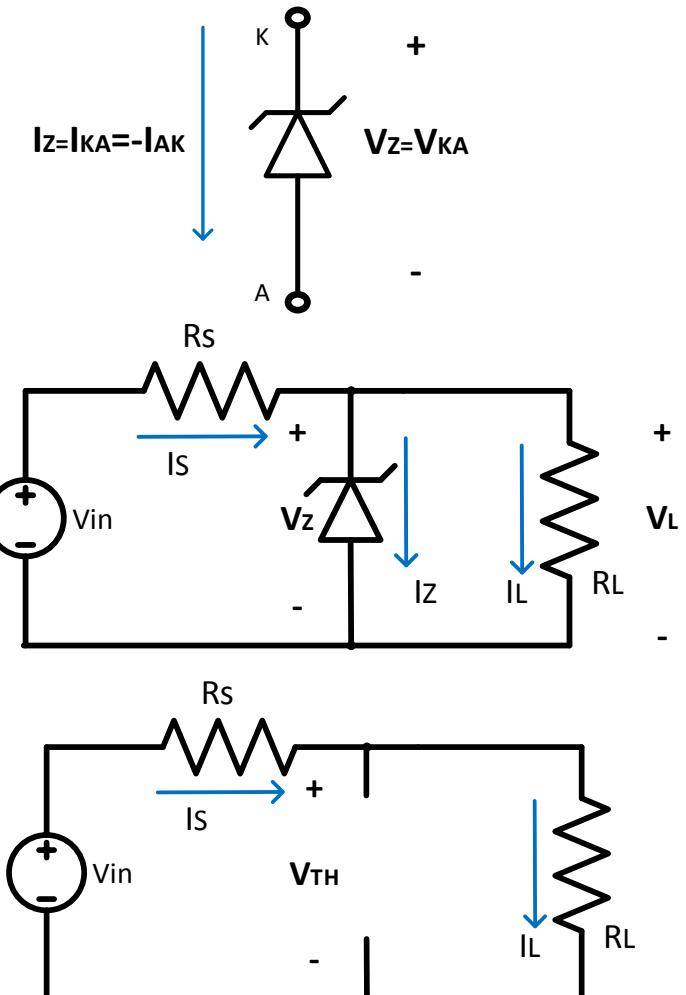1. Cathode is more positive than anode
2. $V_{th} \geq V_z$
3. $I_z > I_z(\min)$
4. $I_z < I_z(\max)$


\Rightarrow Voltage across the Zener is V_z

- Zener current: $I_z = I_s - I_L$
- The Zener Power: $P_z = V_z I_z$




Zener Diode Models

1. Ideal Model

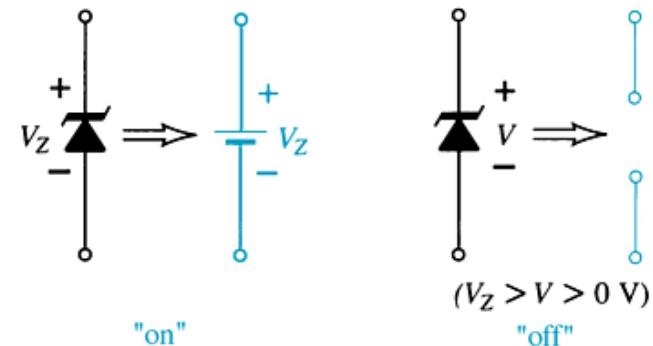

2. Simplified Model

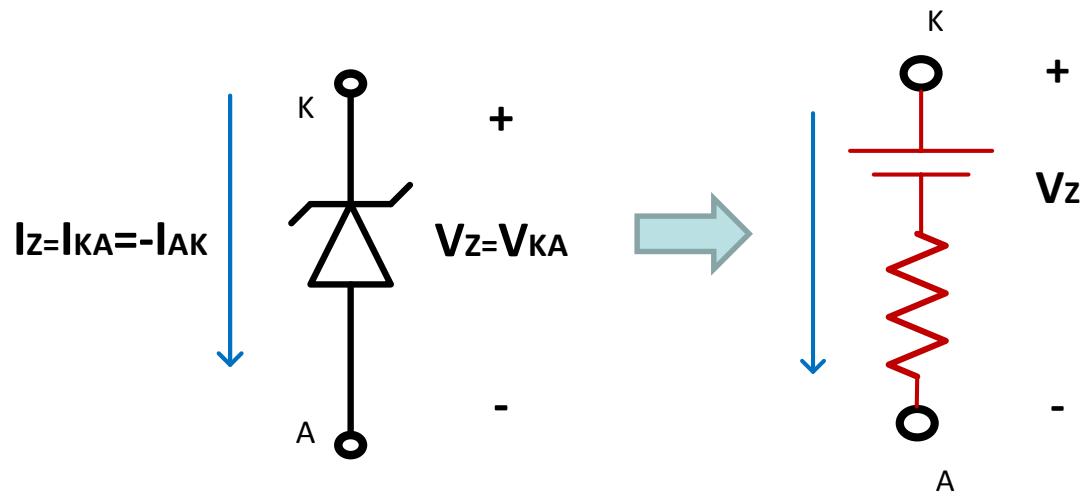

Fixed V_i , Variable R_L


- Due to the value of V_z , there is specific values of R_L (I_L) that ensure the zener is in the ON (regulation) state
- Too small values of R_L can result in zener being OFF

$$V_L = V_z = \frac{R_L}{R_L + R_s} V_{in}$$

$$R_{L(\min)} = \frac{R_s \cdot V_z}{V_{in} - V_z}$$

$$R_L \geq R_{L(\min)} \Rightarrow I_{L(\max)} = \frac{V_L}{R_L} = \frac{V_L}{R_{L(\min)}}$$

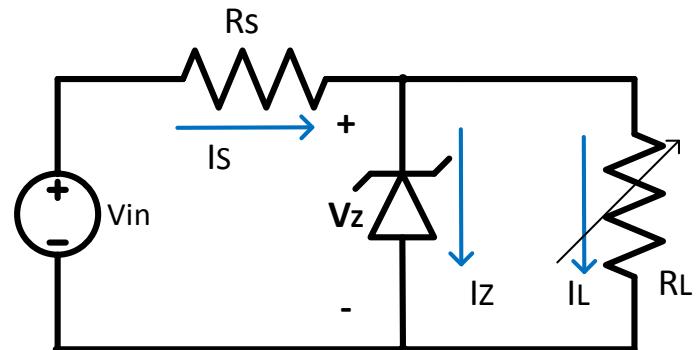Also, values of $R_L \geq R_{L(\max)}$ can result in $\Rightarrow I_Z > I_{Z(\max)}$



$$I_{L(\min)} = I_S - I_{Z(\max)}$$

⇓

$$R_{L(\max)} = \frac{V_z}{I_{L(\min)}}$$

Example

Given the following values of R_L , find the mode of operation of the zener and the voltage V_L

- a) $R_L = 0.1 \text{ k}\Omega$
- b) $R_L = 0.5 \text{ k}\Omega$
- c) $R_L = 5 \text{ k}\Omega$
- d) $R_L = \infty$

SOLUTION


a) $R_L = 0.1 \text{ k}\Omega$

using ideal model


$$V_{th} = \frac{R_L}{R_L + R_s} V_{in} = \frac{0.1}{0.1+1} 35 \text{ V} = 3.18 \text{ V}$$

Zener works in region 2 , it acts as open circuit
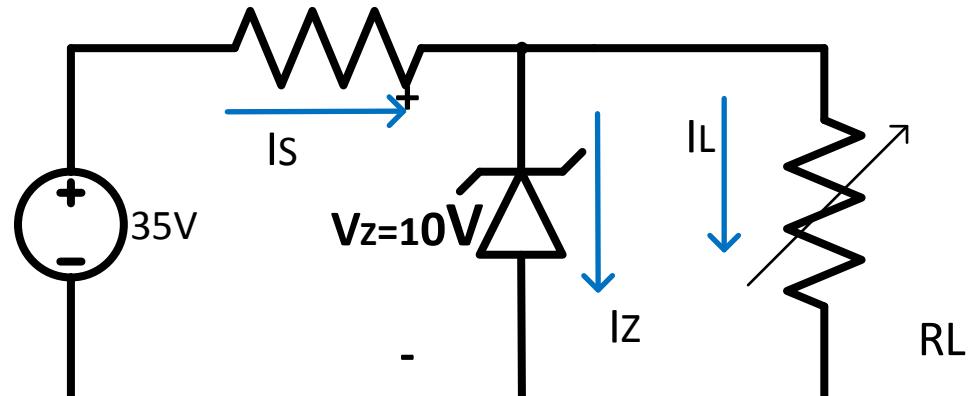
$$V_L = 3.18 \text{ V} \text{ (it is not regulated)}$$



Example

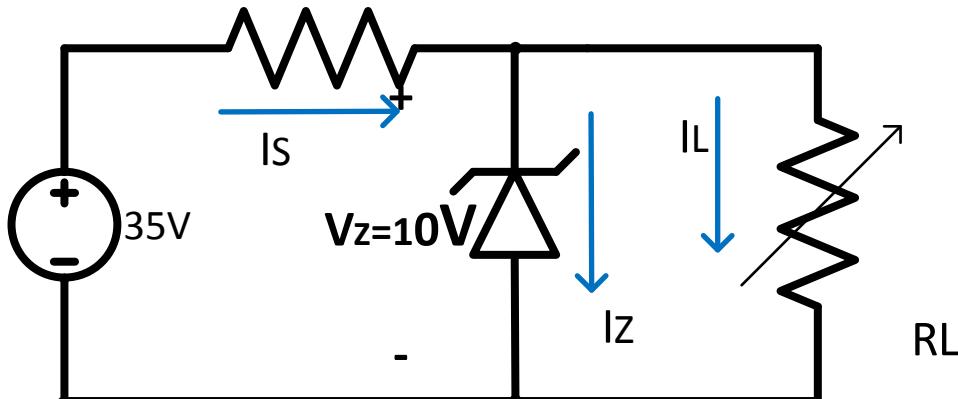

b) $R_L = 0.5 \text{ k}\Omega$

using ideal model

$$V_{th} = \frac{R_L}{R_L + R_s} V_{in} = \frac{0.5}{0.5+1} 35 \text{ V} = 11.67 \text{ V}$$

$$V_{th} > V_z$$

Zener works in region 3, it works as voltage regulator


$$V_L = V_z = 10 \text{ V}$$

$$I_s = \frac{35 \text{ V} - 10 \text{ V}}{1 \text{ k}\Omega} = 25 \text{ mA}$$

$$I_L = \frac{V_L}{R_L} = \frac{10}{0.5 \text{ k}\Omega} = 20 \text{ mA}$$

$$I_z = I_s - I_L = 5 \text{ mA}$$

Example

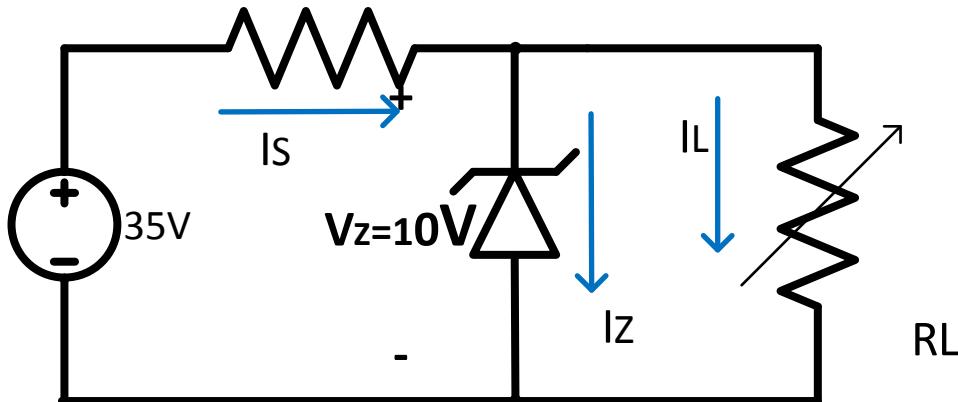

c) $R_L = 5 \text{ k}\Omega$

using ideal model

$$V_{th} = \frac{R_L}{R_L + R_s} V_{in} = \frac{5}{5+1} 35 \text{ V} = 29.17 \text{ V}$$

$$V_{th} > V_z$$

Zener works in region 3 , it works as voltage regulator


$$V_L = V_z = 10 \text{ V}$$

$$I_s = \frac{35 \text{ V} - 10 \text{ V}}{1 \text{ k}\Omega} = 25 \text{ mA}$$

$$I_L = \frac{V_L}{R_L} = \frac{10}{5\text{k}\Omega} = 2 \text{ mA}$$

$$I_z = I_s - I_L = 23 \text{ mA}$$

Example

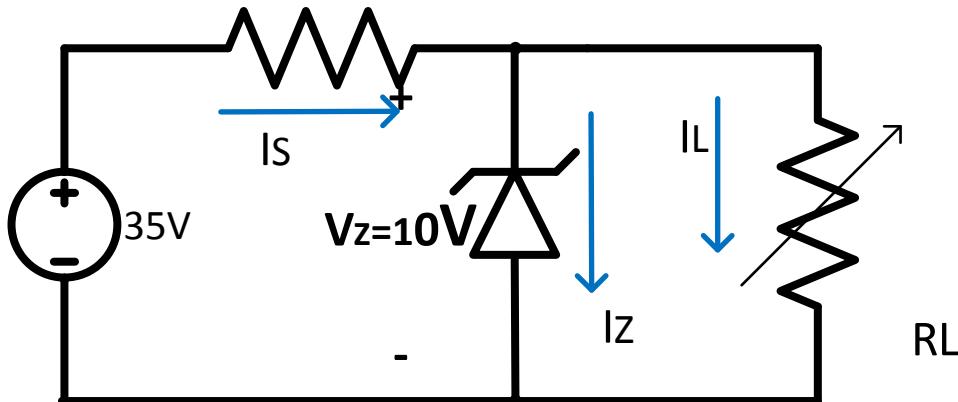

d) $R_L = 5 \text{ k}\Omega$

using ideal model

$$V_{th} = \frac{\infty}{\infty + R_s} V_{in} = 35 \text{ V}$$

$$V_{th} > V_Z$$

Zener works in region 3 , it works as voltage regulator

$$V_L = V_Z = 10 \text{ V}$$


$$I_S = \frac{35 \text{ V} - 10 \text{ V}}{1 \text{ k}\Omega} = 25 \text{ mA}$$

$$I_L = \frac{V_L}{R_L} = \frac{10}{\infty} = 0$$

$$I_Z = I_S - I_L = 25 \text{ mA}$$

Example

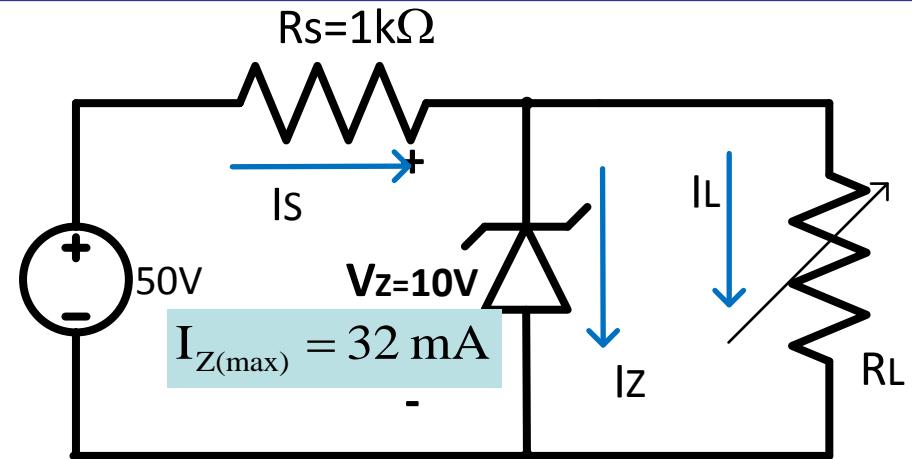- 1) Determine Range of R_L & I_L that will result in V_L be maintained at 10V
- 2) Determine the power rating of the zener diode



SOLUTION

- 1) To find $R_{L(\min)}$ that will turn the zener diode ON :

$$V_L = V_Z = \frac{R_L}{R_L + R_s} V_i \Rightarrow$$

$$R_L = \frac{R_s}{V_i - V_Z} V_Z$$

$$R_{L(\min)} = \frac{1 \text{ k}\Omega}{50 - 10} 10 = 250 \Omega$$

$$250 \Omega \leq R_L \leq 1.25 \text{ k}\Omega$$

- 2) To find $R_{L(\max)}$ \Rightarrow we need $I_{L(\min)}$

$$I_{L(\min)} = I_S - I_{Z(\max)}$$

$$I_S = \frac{V_i - V_Z}{R_s} = \frac{50 - 10}{1 \text{ k}\Omega} = 40 \text{ mA}$$

$$I_{L(\min)} = 40 - 32 = 8 \text{ mA}$$

\Downarrow

$$R_{L(\max)} = \frac{V_L}{I_{L(\min)}} = \frac{10 \text{ V}}{8 \text{ mA}} = 1.25 \text{ k}\Omega$$

$$3) P_{Z(\max)} = V_Z \cdot I_{Z(\max)} = 10 \text{ V} \cdot 32 \text{ mA} = 320 \text{ mW}$$

The zener diode is chosen with power rating $\geq P_{Z(\max)}$

Fixed RL, Variable Vin

For Fixed R_L , the voltage V_{in} must be large enough to turn the zener diode on (regulation region (3))


$$V_{in} = V_{in(\min)} = \frac{R_L + R_s}{R_L} V_Z$$

$V_{in(\max)}$ is limited by maximum zener current $I_{Z(\max)}$

$$I_s = I_z + I_L$$

$$I_{s(\max)} = I_{z(\max)} + I_L$$
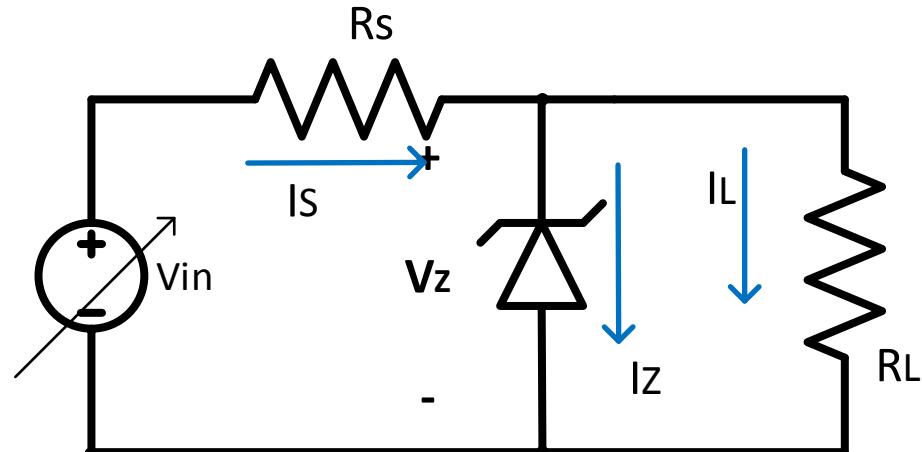
$$V_{i(\max)} = I_{s(\max)} \cdot R_s + V_Z$$



$$V_{in(\min)} \leq V_{in} \leq V_{in(\max)}$$

Example

Find the range of values of V_i that will maintain the zener in the ON (regulation) State

$$\begin{aligned} V_{in(min)} &= \frac{R_L + R_S}{R_L} V_Z \\ &= \frac{1200 + 220}{1200} 20 = 23.07 \text{ V} \end{aligned}$$


$$I_S = I_Z + I_L$$

$$I_{S(max)} = I_{z(max)} + I_L$$

$$I_L = \frac{V_L}{R_L} = \frac{20 \text{ V}}{1200 \Omega} = 16.67 \text{ mA}$$

$$I_{S(max)} = 60 \text{ mA} + 16.67 \text{ mA} = 76.67 \text{ mA}$$
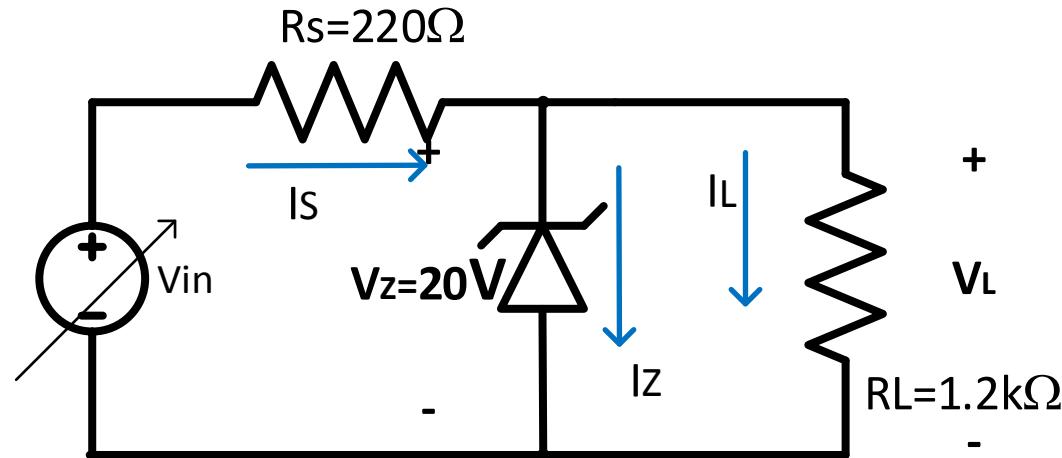
$$V_{i(max)} = (76.67 \text{ mA}) \cdot (220 \Omega) + 20 \text{ V} = 36.87 \text{ V}$$



$$I_{Z(max)} = 60 \text{ mA}$$

$$\therefore 23.07 \text{ V} \leq V_{in} \leq 36.87 \text{ V}$$

Design of R_s (Current limiting Resistor)

Given : $V_Z, I_{Z(\min)}, I_{Z(\max)}, V_{in(\min)}, V_{in(\max)}, R_{L(\min)}, R_{L(\max)}$

Find range of acceptable R_s in the voltage regulator

$$1) I_Z = I_S - I_L \geq I_{Z(\min)}$$

Worst Case : the smallest value of $(I_S - I_L)$


must be always higher than $> I_{Z(\min)}$

$$I_{S(\min)} - I_{L(\max)} \geq I_{Z(\min)}$$

$$\frac{V_{S(\min)} - V_Z}{R_s} - I_{L(\max)} \geq I_{Z(\min)}$$

$$I_{Z(\min)} + I_{L(\max)} \leq \frac{V_{S(\min)} - V_Z}{R_s}$$
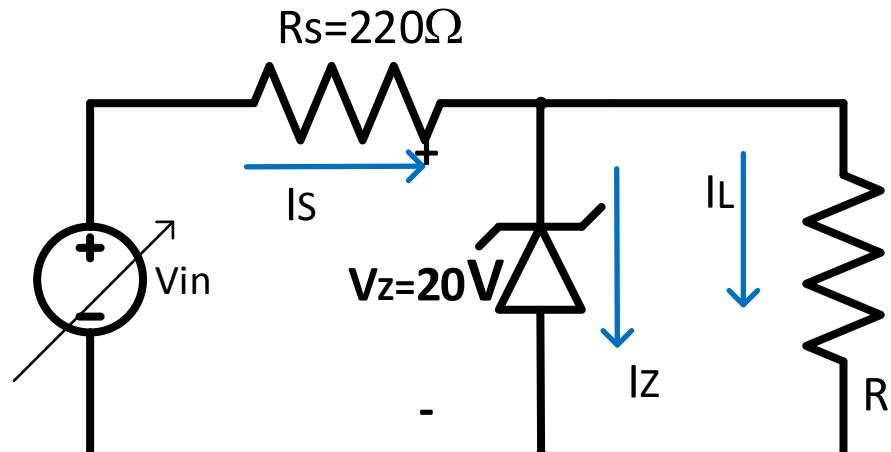
$$R_s \leq \frac{V_{S(\min)} - V_Z}{I_{Z(\min)} + I_{L(\max)}}$$



Design of R_s (Current limiting Resistor)

Given : $V_Z, I_{Z(\min)}, I_{Z(\max)}, V_{in(\min)}, V_{in(\max)}, R_{L(\min)}, R_{L(\max)}$

Find range of acceptable R_s in the voltage regulator

$$2) I_Z \leq I_{Z(\max)}$$

Worst Case : the largest value of $(I_S - I_L)$ must be always smaller than $I_{Z(\max)}$

$$I_{S(\max)} - I_{L(\min)} \leq I_{Z(\max)}$$

$$\frac{V_{S(\max)} - V_Z}{R_s} - I_{L(\min)} \leq I_{Z(\max)}$$

$$I_{Z(\max)} + I_{L(\min)} \geq \frac{V_{S(\max)} - V_Z}{R_s}$$

$$R_s \geq \frac{V_{S(\max)} - V_Z}{I_{Z(\max)} + I_{L(\min)}}$$

Note That

$$I_{L(\min)} = \frac{V_Z}{R_{L(\max)}}$$

$$I_{L(\max)} = \frac{V_Z}{R_{L(\min)}}$$

$$\frac{V_{S(\min)} - V_Z}{I_{Z(\min)} + I_{L(\max)}} \geq R_s \geq \frac{V_{S(\max)} - V_Z}{I_{Z(\max)} + I_{L(\min)}}$$

Design of R_s (Current limiting Resistor)

Given :

$$V_Z = 10 \text{ V},$$

$$I_{Z(\min)} = 5 \text{ mA}, I_{Z(\max)} = 200 \text{ mA},$$

$$V_{in(\min)} = 15 \text{ V}, V_{in(\max)} = 20 \text{ V},$$

$$R_{L(\min)} = 500, R_{L(\max)} = \infty$$

Find R_s ?

$$\frac{V_{S(\min)} - V_Z}{I_{Z(\min)} + I_{L(\max)}} \geq R_s \geq \frac{V_{S(\max)} - V_Z}{I_{Z(\max)} + I_{L(\min)}}$$

Solution

$$I_{L(\min)} = \frac{V_Z}{R_{L(\max)}} = \frac{10 \text{ V}}{500 \Omega} = 20 \text{ mA}$$

$$I_{L(\max)} = \frac{V_Z}{R_{L(\min)}} = \frac{10 \text{ V}}{\infty} = 0$$

$$200 \Omega \geq R_s \geq 50 \Omega$$

$$\text{let } R_s = 100 \Omega$$


Variation of Vz (using simplified model)

$$r_z = \frac{\Delta V_z}{\Delta I_z}$$

If V_{ZT} , I_{ZT} & r_z are known

$$\begin{aligned} V_{Z(\max)} &= V_{ZM} = V_{ZT} + \Delta I_z \cdot r_z \\ &= V_{ZT} + (I_{Z(\max)} - I_{ZT}) \cdot r_z \end{aligned}$$
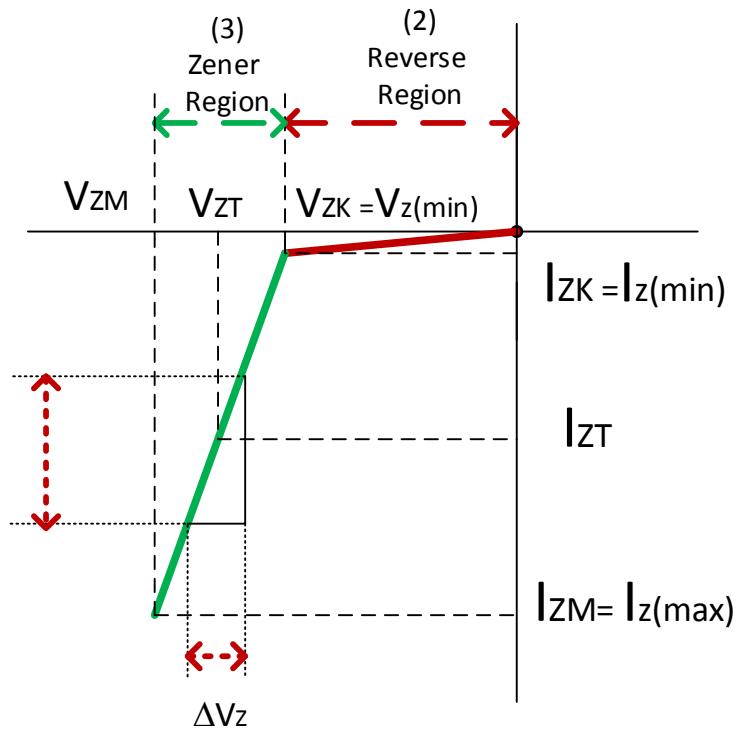
$$\begin{aligned} V_{Z(\min)} &= V_{ZK} = V_{ZT} - \Delta I_z \cdot r_z \\ &= V_{ZT} - (I_{ZT} - I_{Z(\min)}) \cdot r_z \end{aligned}$$



Example

If $V_{ZT} = 15V$ at $I_{ZT} = 17mA$

& $r_Z = 14 \Omega$

$I_{ZK} = 0.25 mA$



$P_{Zmax} = 1 \text{ Watt}$

Find :

1) Minimum and Maximum Values of V_Z

2) Value of R_s

3) Value of $R_{L(min)}$

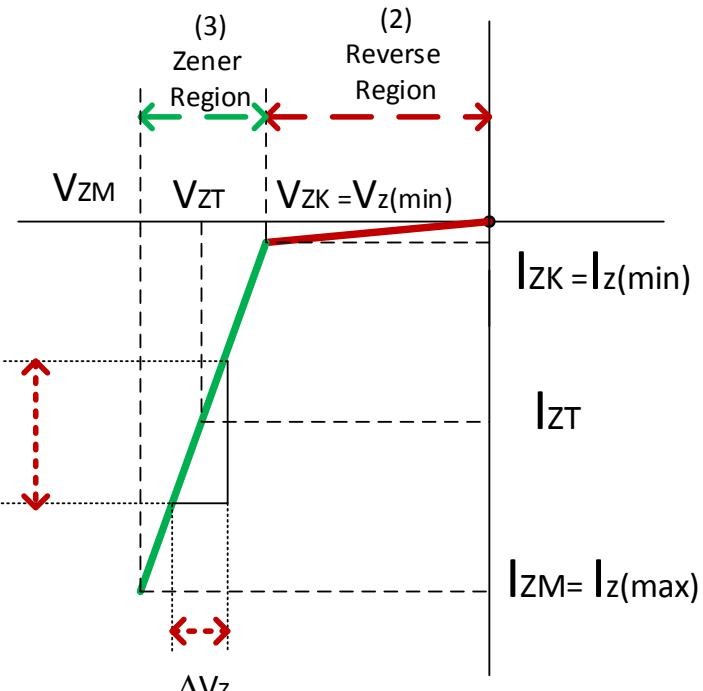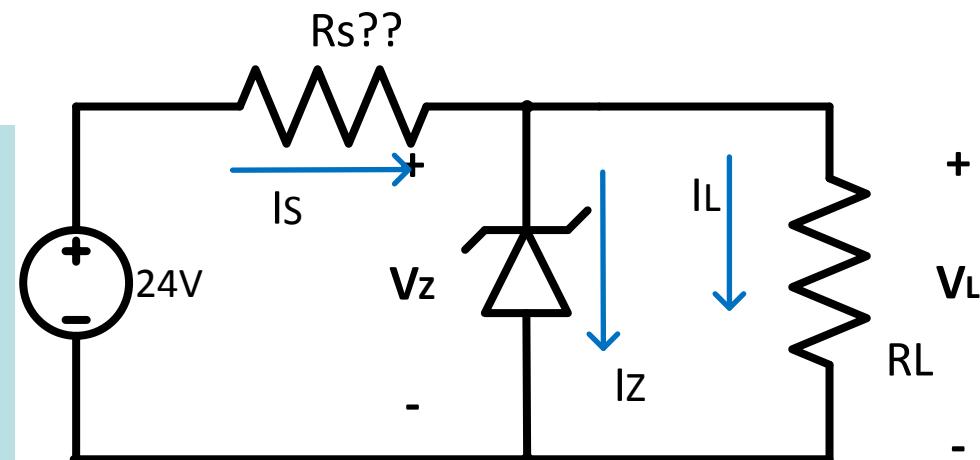


$$1) I_{Z(max)} \cong \frac{P_{Z(max)}}{V_Z} = \frac{1 \text{ Watt}}{15} = 66.7 \text{ mA}$$

$$\begin{aligned} V_{Z(max)} &= V_{ZM} = V_{ZT} + \Delta I_Z \cdot r_Z \\ &= V_{ZT} + (I_{Z(max)} - I_{ZT}) \cdot r_Z \\ &= 15 + (66.7 - 17) \text{ mA} (14 \Omega) = 15.7 \text{ V} \end{aligned}$$

$$\begin{aligned} V_{Z(min)} &= V_{ZK} = V_{ZT} - \Delta I_Z \cdot r_Z \\ &\equiv V_{ZT} - (I_{ZT} - I_{ZK}) \cdot r_Z \end{aligned}$$

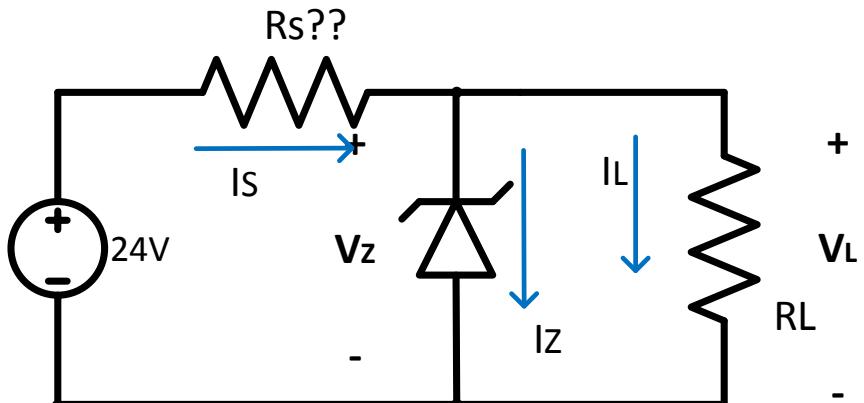Example

$$\begin{aligned}
 V_{Z(\min)} &= V_{ZK} = V_{ZT} - \Delta I_Z \cdot r_Z \\
 &= V_{ZT} - (I_{ZT} - I_{Z(\min)}) \cdot r_Z \\
 &= 15 - (17 - 0.25) \text{ mA} (14 \Omega) = 14.76 \text{ V}
 \end{aligned}$$



2) R_s


$$\frac{V_{S(\min)} - V_z}{I_{Z(\min)} + I_{L(\max)}} \geq R_s \geq \frac{V_{S(\max)} - V_z}{I_{Z(\max)} + I_{L(\min)}}$$

Here $V_{IN} = V_s$ is fixed \Rightarrow

$$R_s \geq \frac{V_s - V_{Z(\max)}}{I_{Z(\max)} + I_{L(\min)}} = \frac{24 - 15.7}{66.7 \text{ mA} + 0} = 124 \Omega$$

$$R_s \leq \frac{V_s - V_{Z(\min)}}{I_{Z(\min)} + I_{L(\max)}} = \frac{24 - 14.76}{0.25 \text{ mA} + ???}$$

we choose $R_s = 124 \Omega$


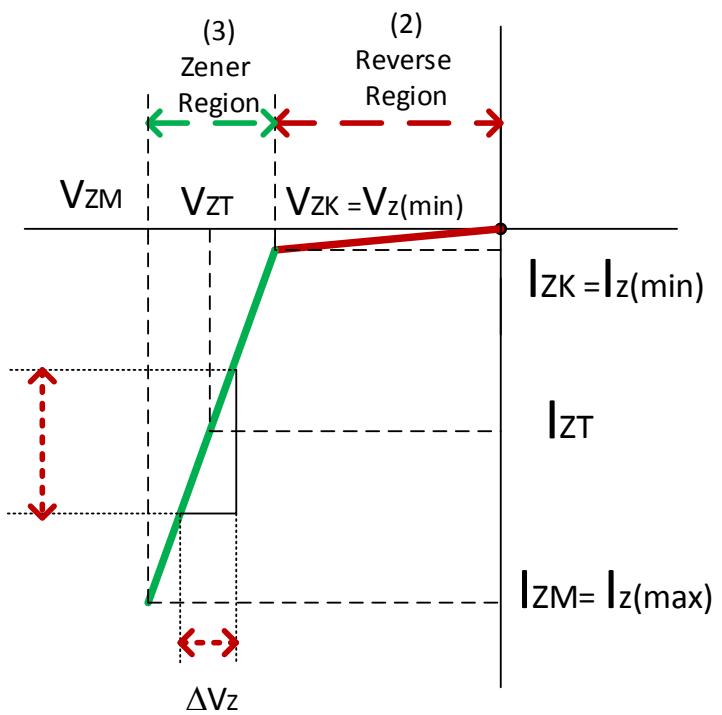


Example

$$3) R_{L(\min)} \Rightarrow I_{L(\max)}$$

$$I_{L(\max)} = I_S - I_{L(\min)} \\ = 66.7 \text{ mA} - 0.25 \text{ mA} = 66.45 \text{ mA}$$
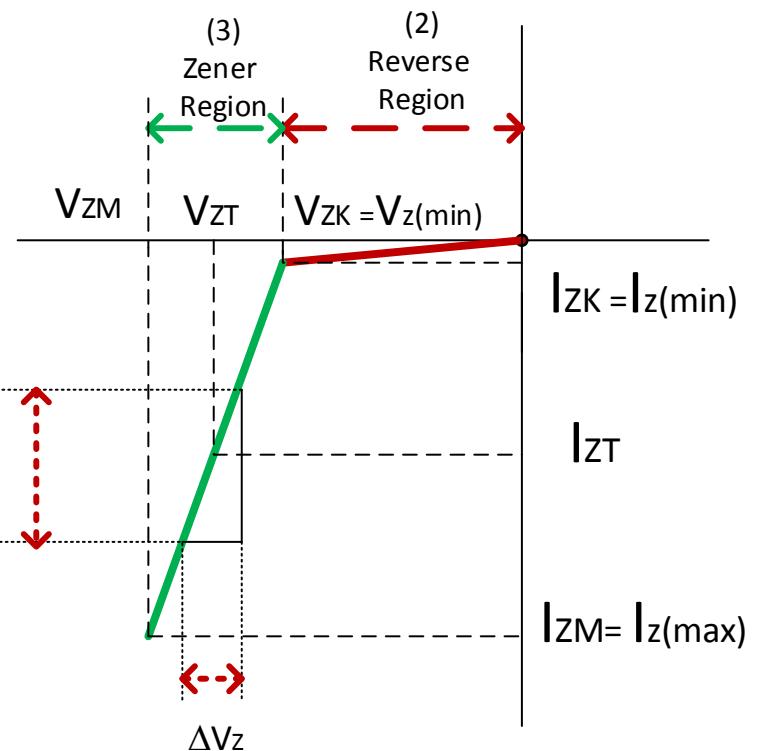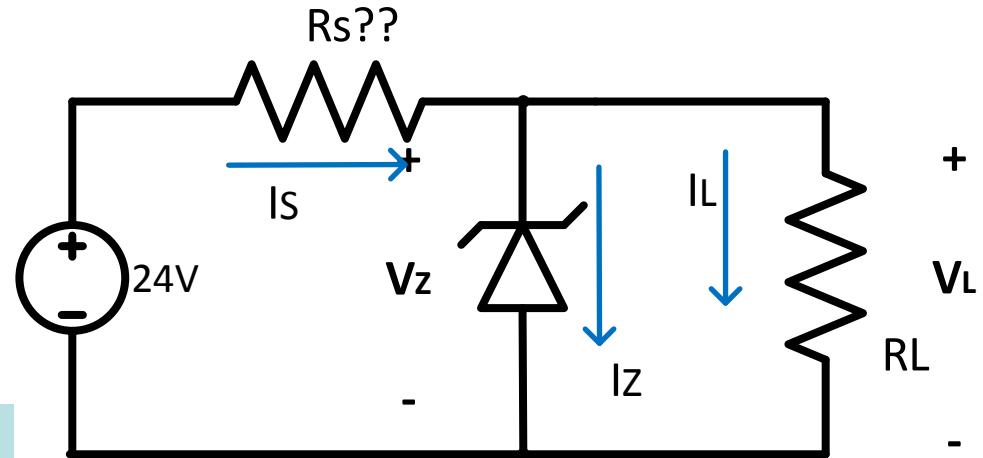
$$\therefore R_{L(\min)} = \frac{V_{Z(\min)}}{I_{L(\max)}} = \frac{14.76 \text{ V}}{66.45 \text{ mA}} \cong 222 \Omega$$



Clipper circuits using Zeners

- a) When $V_i(t) < -0.7$ V, Zener works in region (1) as regular diode ON

$$0.7 + i_D(t) \cdot R + V_i(t) = 0$$

$$i_D(t) = \frac{-V_i(t) - 0.7}{R} > 0$$

$$V_i(t) < -0.7$$




$$\therefore V_o(t) = -0.7$$

- b) When $V_z > V_i(t) > -0.7$ V, Zener works in region (2) as regular diode OFF

$$\therefore V_o(t) = V_i(t)$$

- c) When $V_i(t) > V_z$, Zener works in region (3) as voltage regulator



$$\therefore V_o(t) = V_z$$

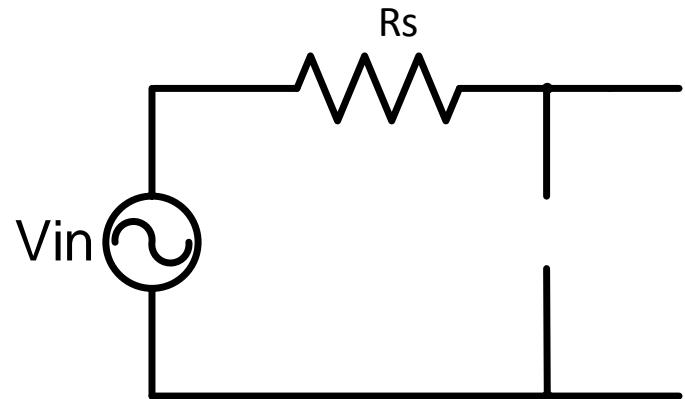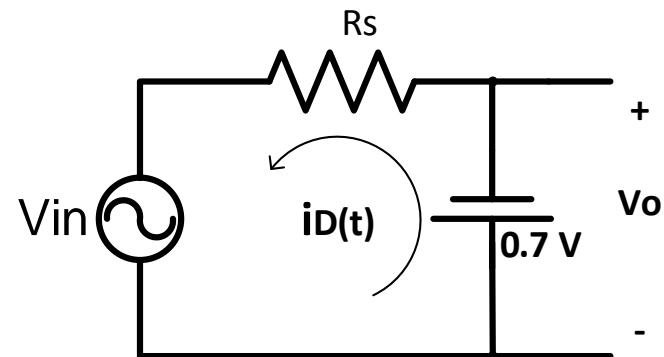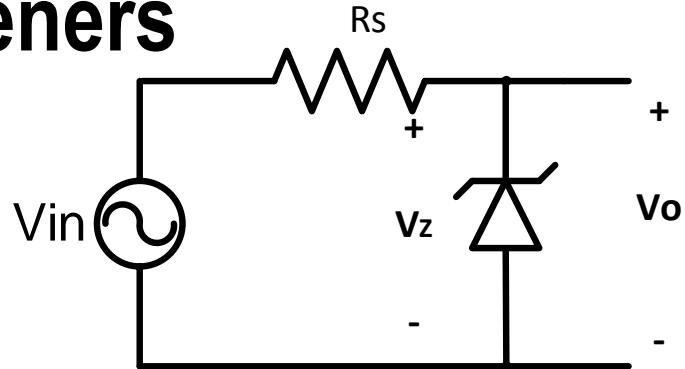

Clipper circuits using Zeners

c) When $V_i(t) > V_z$, Zener works in region (3) as voltage regulator

$$\therefore V_o(t) = V_z$$

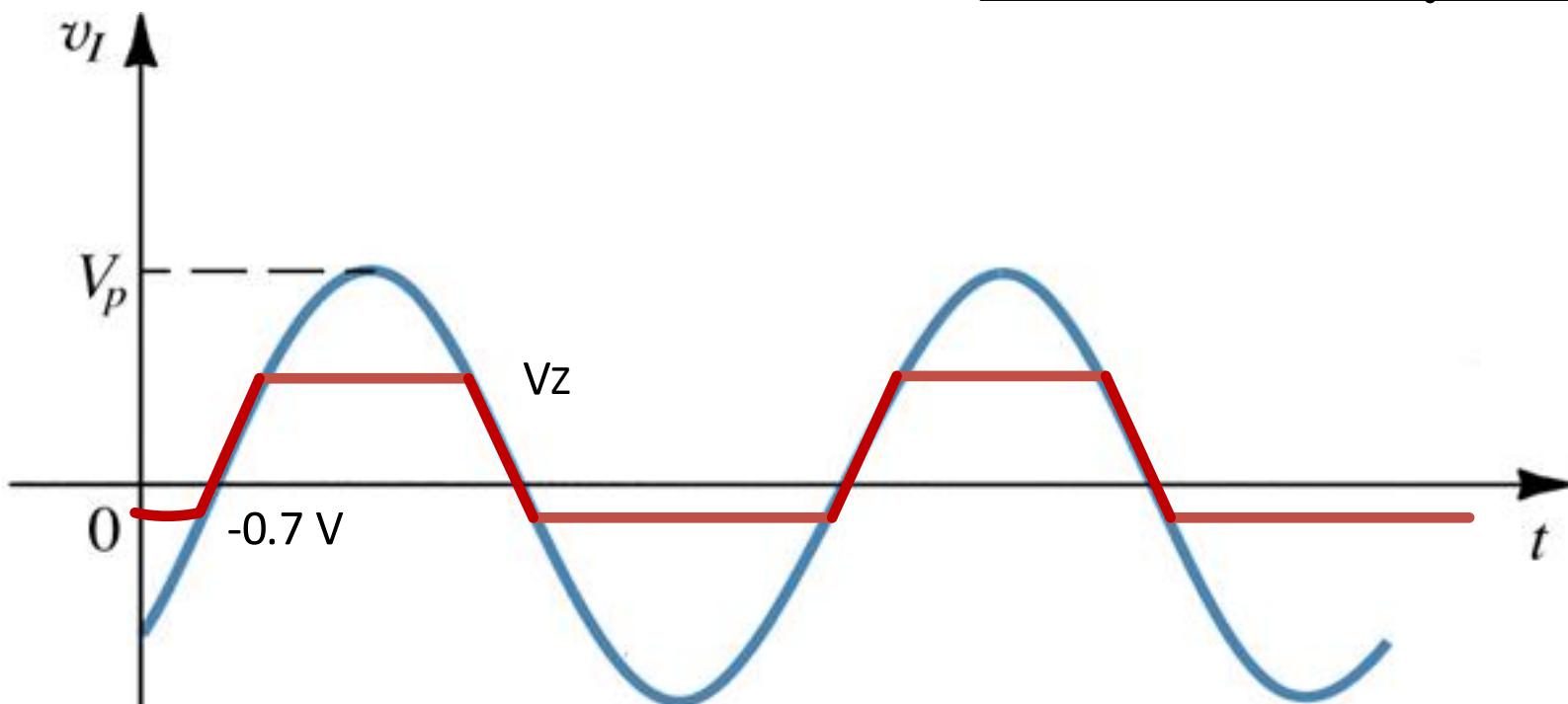
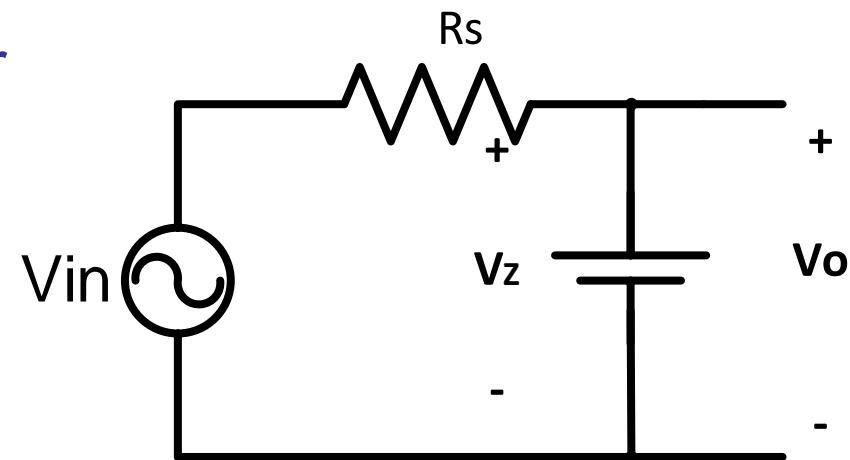


Clipper circuits using Zeners

Find and sketch $V_o(t)$


- a) When $0.7V < V_i(t) < V_{z2}$,
 D1- regular diode ON
 D2- regular diode OFF

$$\therefore V_o(t) = V_i(t)$$

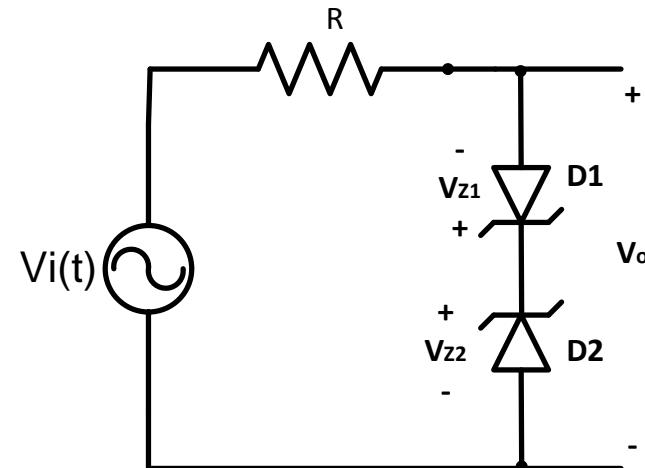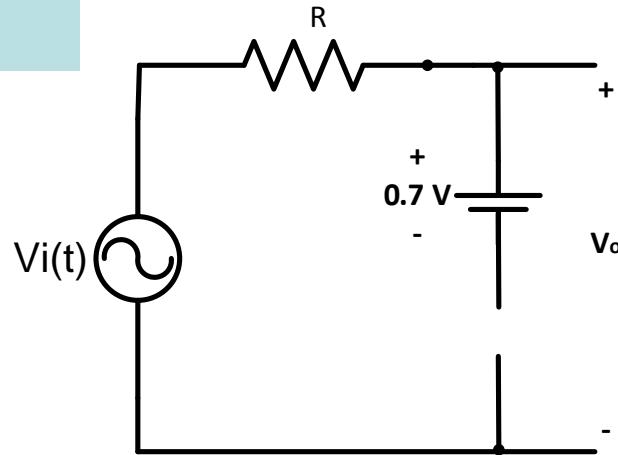

- b) When $V_i(t) > V_{z2}$
 D1 – ON (region 1)
 D2- Zener ON (region 3)

$$\therefore V_o(t) = V_{z2} + 0.7$$

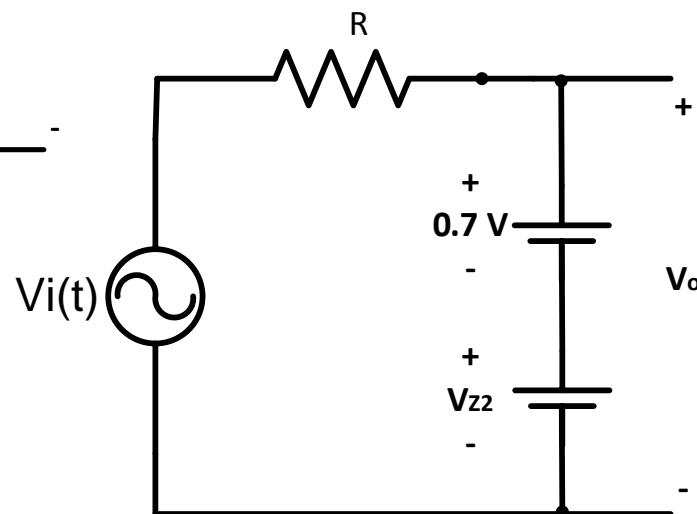


Clipper circuits using Zeners

c) When $-0.7V > V_i(t) > -V_{z1}$,

D1- regular diode OFF

D2- regular diode ON

$$\therefore V_o(t) = V_i(t)$$


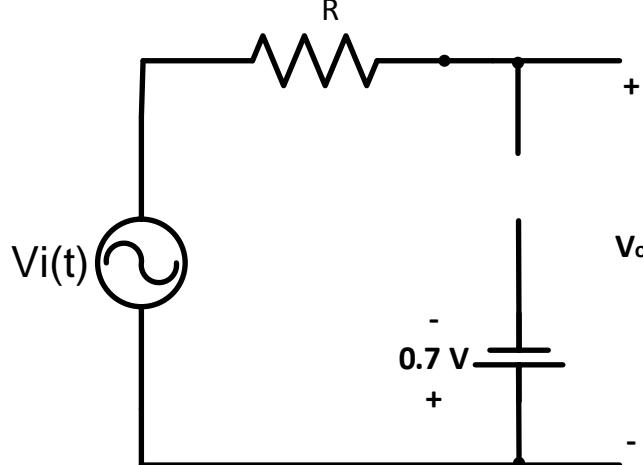


d) When $V_i(t) < -V_{z1}$


D2 – ON (region 1)

D1- Zener ON (reaion 3)

$$\therefore V_o(t) = -V_{z1} - 0.7$$

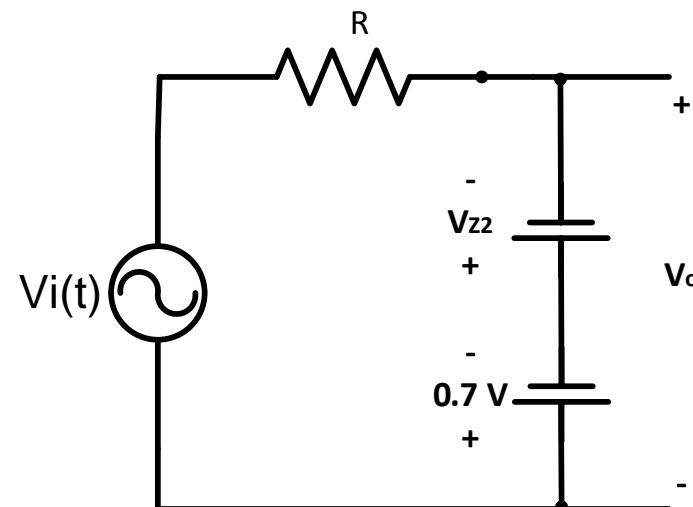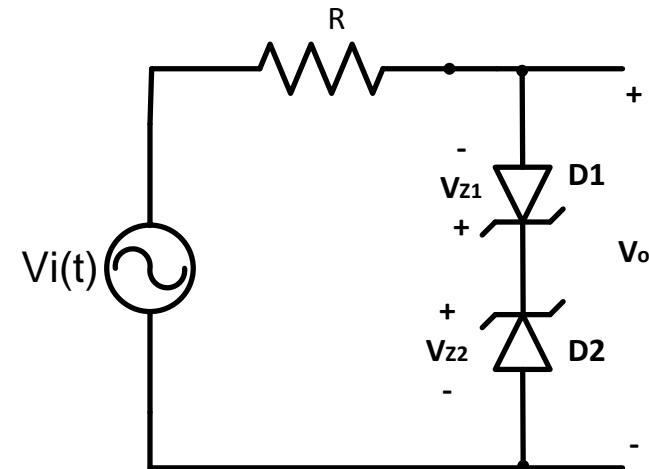

Clipper circuits using zeners

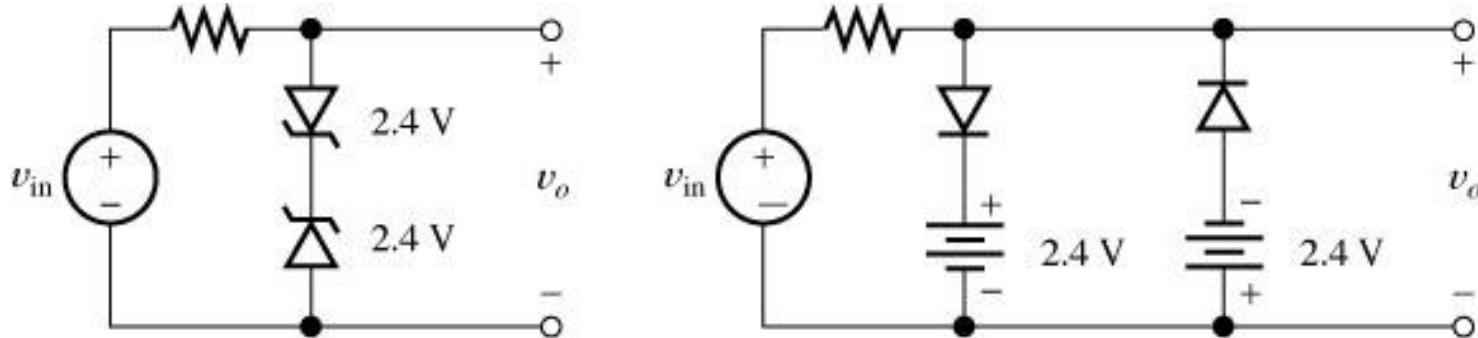

(c) Circuits for the characteristic of part (a)

Voltage-Multiplier Circuits


Voltage multiplier circuits use a combination of diodes and capacitors to step up the output voltage of rectifier circuits. Three common voltage multipliers are the:

Voltage Doubler

Voltage Tripler

Voltage Quadrupler

Voltage Doubler

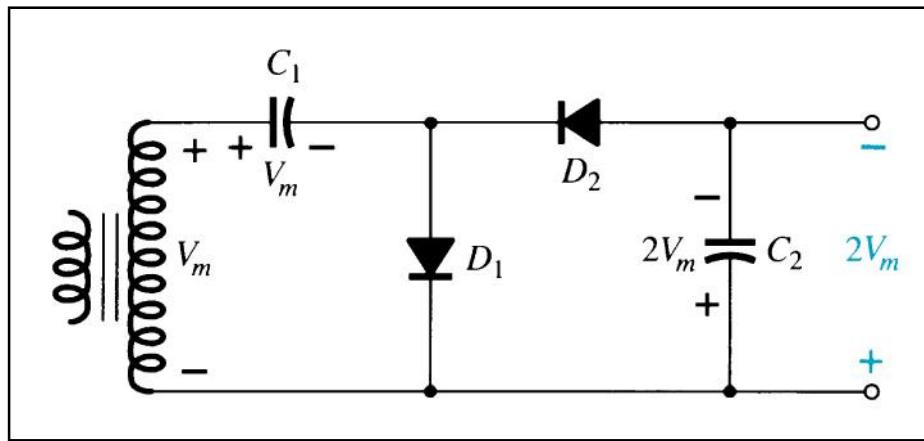

This half-wave voltage doubler's output can be calculated using:

$$V_{out} = V_{C2} = 2V_m$$

where V_m = peak secondary voltage of the transformer

Voltage Doubler


Positive Half-Cycle

D_1 conducts
 D_2 is switched off
 Capacitor C_1 charges to V_m


Negative Half-Cycle

D_1 is switched off
 D_2 conducts
 Capacitor C_2 charges to V_m

$$V_{\text{out}} = V_{C2} = 2V_m$$

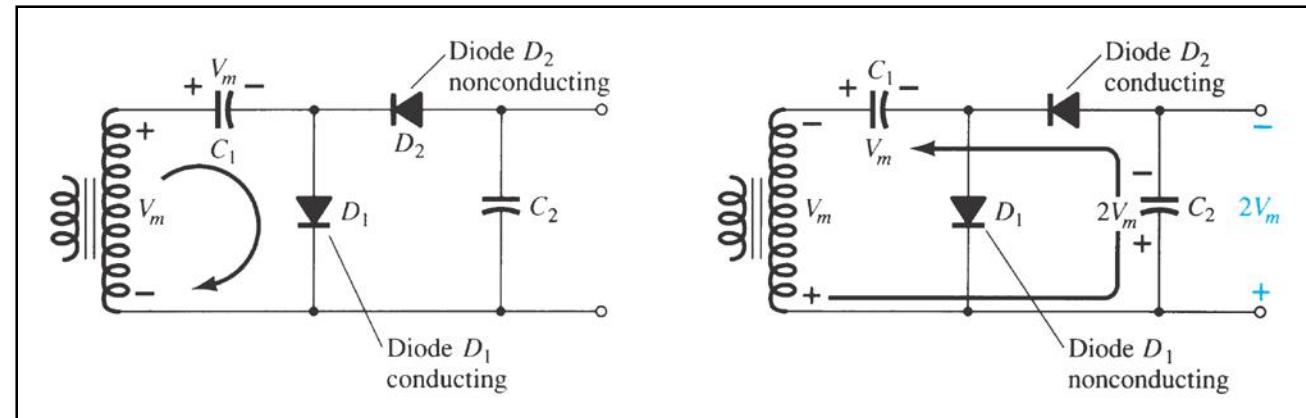

Voltage Tripler and Quadrupler

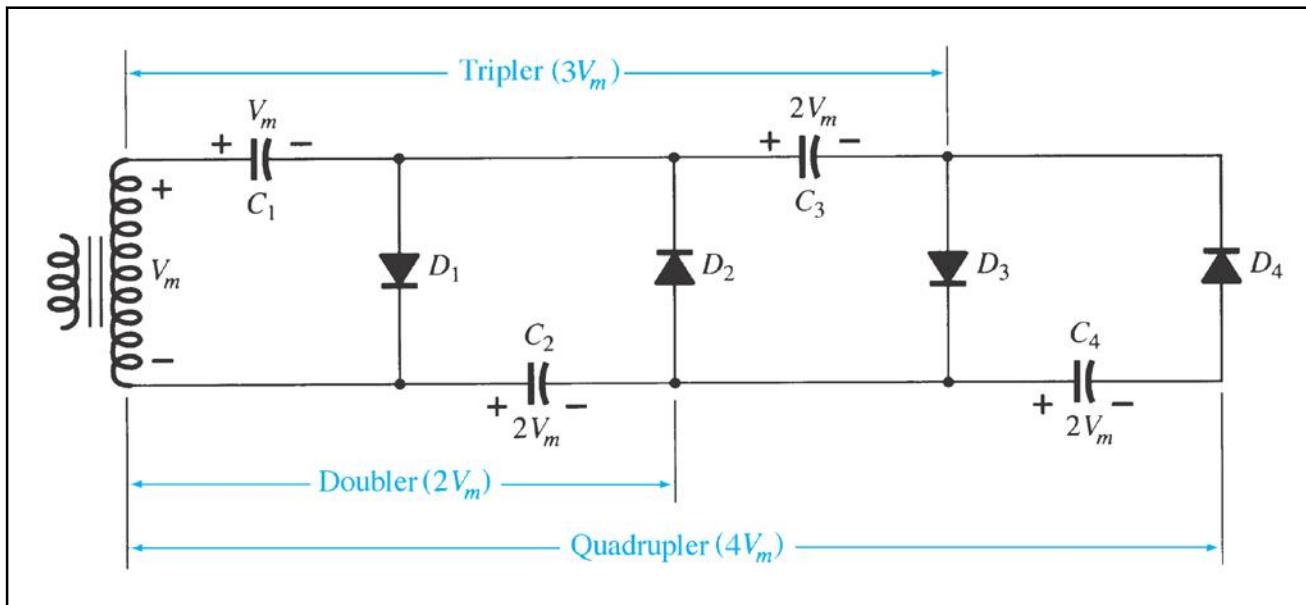

Practical Applications

Rectifier Circuits

Conversions of AC to DC for DC operated circuits
Battery Charging Circuits

Simple Diode Circuits

Protective Circuits against
Overcurrent
Polarity Reversal
Currents caused by an inductive kick in a relay circuit

Zener Circuits

Overvoltage Protection
Setting Reference Voltages