

ENEE236 & 241

Analog Electronics

L3 Diode Applications 1
Instructor: Nasser Ismail

Diode large – signal application

1) Diode clipper circuit



a) assume the diode is on
replace it with short circuit

$$i_D(t) > 0$$

$$i_D(t) = \frac{V_i(t)}{R_L} > 0$$



$$\therefore V_i(t) > 0$$

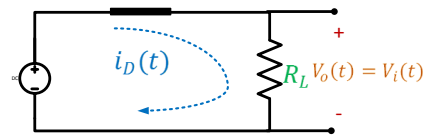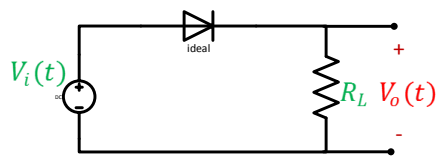\therefore when $V_i(t) > 0$, the diode is on and $V_o(t) = V_i(t)$



\therefore when $V_i(t) < 0$, the diode is off and $V_o(t) = 0$.

$V_o(t) = 0$.

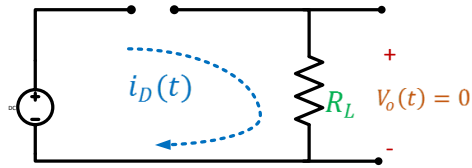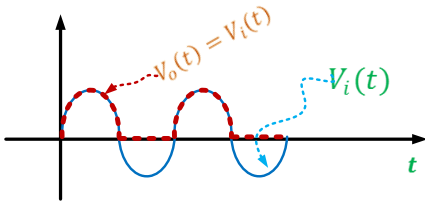




\therefore the clipper circuit used to eliminate portion of the input signal .

Example

a) assume that the diode is on

\rightarrow replace it with short circuit $V_i(t)$

$i_D > 0$

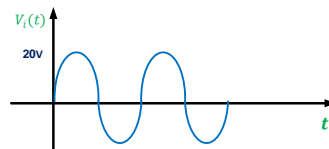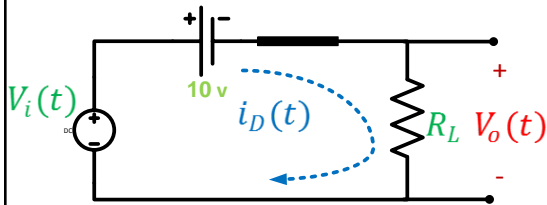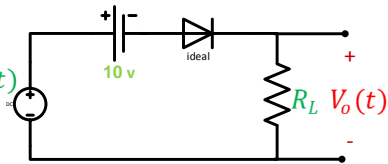

$$i_D(t) = \frac{V_i(t) - 10}{R_L} > 0$$

$$i_D(t) = \frac{V_i(t) - 10}{R_L} > 0$$

$$\therefore V_i(t) - 10 > 0$$

$$\therefore V_i(t) > 10$$

$$\therefore \text{when } V_i(t) > 10 \text{ V, the diode is on and } V_o(t) = V_i - 10$$

and also we can prove that when $V_i(t) < 10 \text{ V}$, the diode is off

$$\therefore V_o(t) = 0$$

The output

Second Method


assume that the diode is off ,replace it with open circuit

$$V_D(t) < 0$$

$$V_D(t) = -10 + V_i$$

$$V_i(t) < 10 \text{ V}$$



∴ when $V_i(t) < 10 \text{ V}$, the diode is off and $V_o(t) = 0$

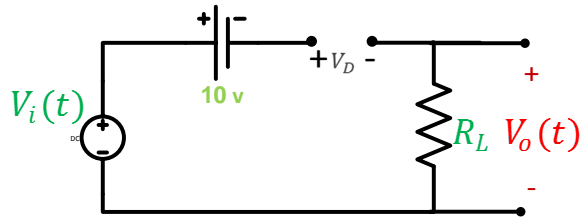


ENEE236 – Analog Electronics

Limiters (=Clipping circuits) (1)

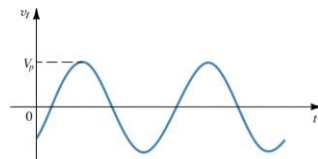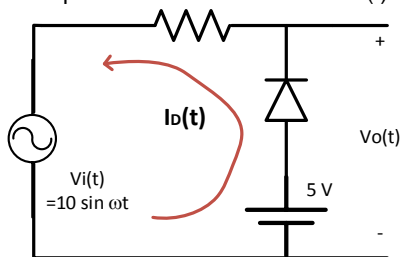Example: Calculate and sketch $V_o(t)$ using simplified diode model



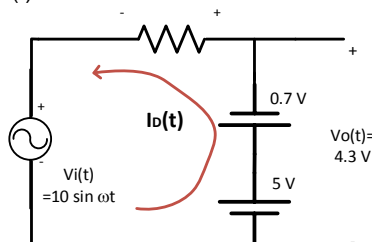1) Assume diode is ON, so we replace it by 0.7 V and $i_D(t)$ must be > 0




$$5\text{V} - 0.7\text{V} - i_D(t) \cdot R - V_i(t) = 0$$

$$i_D(t) \cdot R = 4.3\text{V} - V_i(t)$$

$$i_D(t) = \frac{4.3\text{V} - V_i(t)}{R} > 0$$


Limiters (=Clipping circuits) (2)

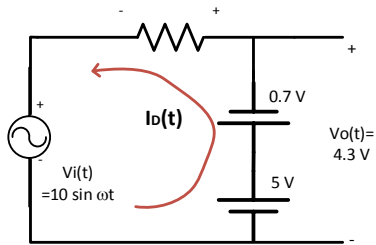

$$\begin{aligned} \therefore 4.3\text{V} - V_i(t) &> 0 \\ \Rightarrow V_i(t) &< 4.3\text{V} \end{aligned}$$

when $V_i(t) < 4.3\text{ V}$ diode is ON and
 $V_o(t) = 4.3\text{V}$

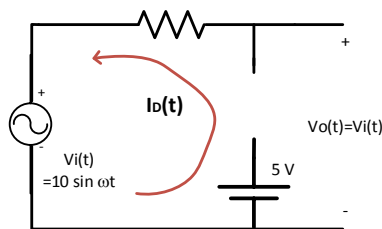
2) Otherwise, When $V_i(t)$ is $> 4.3\text{ V}$, Diode will be off and it is replaced by open circuit



$$\begin{aligned} \Rightarrow V_i(t) &> 4.3\text{V} \\ V_o(t) &= V_i(t) \end{aligned}$$

Limiters (=Clipping circuits) (3)


when $V_i(t) < 4.3\text{V}$, diode is ON & $V_o(t) = 4.3\text{V}$
when $V_i(t) > 4.3\text{V}$, diode is off & $V_o(t) = V_i(t)$

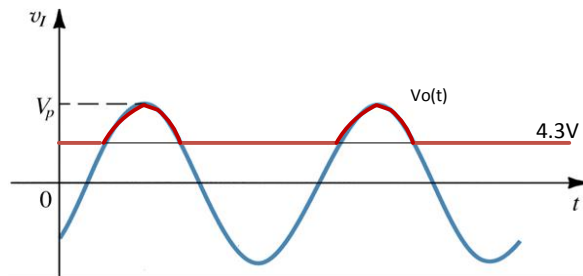

ENEE236 – Analog Electronics

Circuit Containing Two diodes

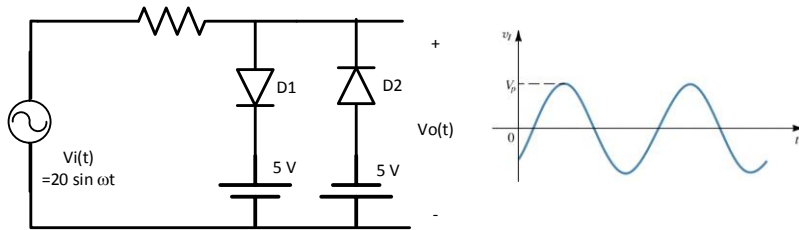Example: Calculate and sketch $V_o(t)$ using simplified diode model




Since the circuit contains two diodes, each of them can be either On or Off,
 → then there is 4 possible combinations for the states of D1 and D2

ENEE236 – Analog Electronics

- 1) Assume D1 is ON and D2 is OFF
 $i_{D1}(t) > 0$

$$i_{D1}(t) = \frac{V_i(t) - 5}{R} > 0$$

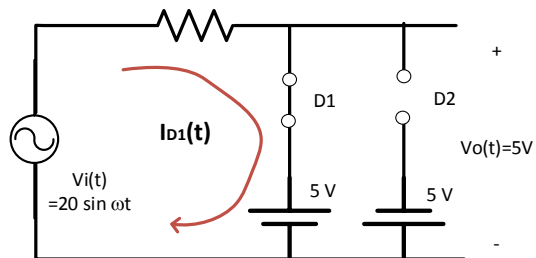


when $V_i(t) > 5\text{ V}$, $V_o(t) = 5\text{ V}$

ENEE236 – Analog Electronics

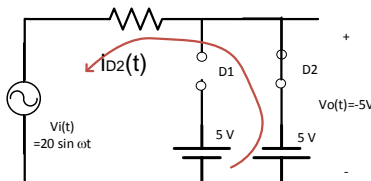2) Assume D2 is ON and D1 is OFF

$$i_{D2}(t) > 0$$

$$i_{D2}(t) = \frac{-V_i(t) - 5}{R} > 0$$



when $V_i(t) < -5V$, $V_o(t) = -5V$

ENEE236 – Analog Electronics


3) Assume D1 & D2 are ON

$V_o = +5V$??

$V_o = -5V$??




This is invalid configuration and impossible to occur

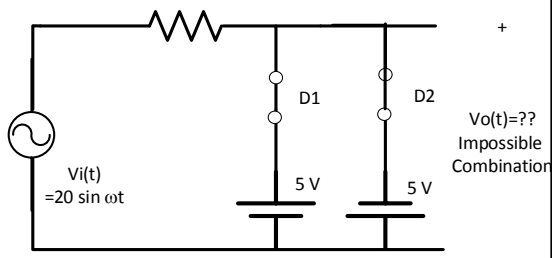


ENEE236 – Analog Electronics

4) Assume D1 & D2 are both OFF


$V_o(t) = V_i(t)$

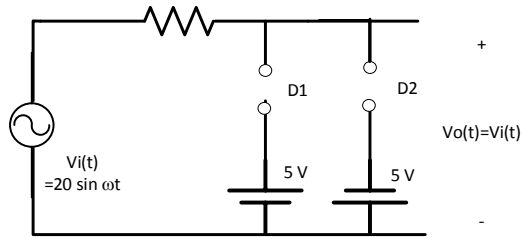

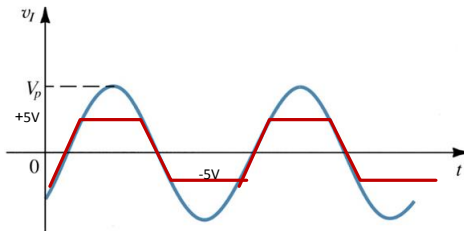
This occurs for the remaining part of the input voltage waveform:
 $-5V < V_i(t) < 5V$




Summary of Clipper Circuits

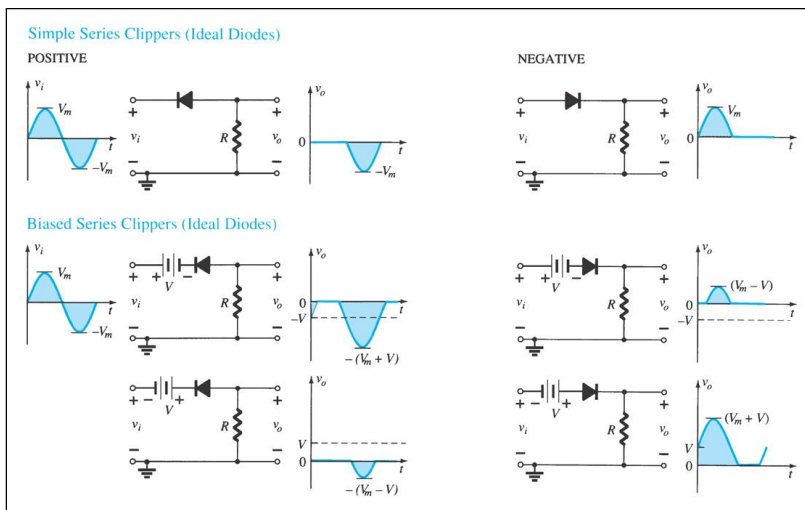

Summary of Clipper Circuits

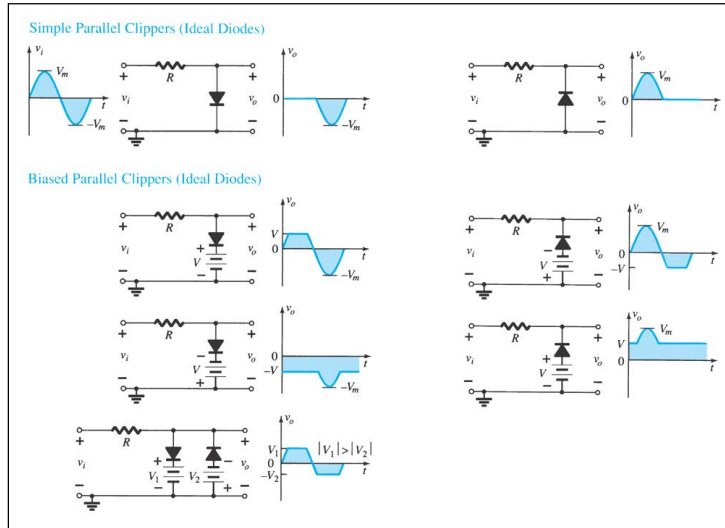

Summary of Clipper Circuits

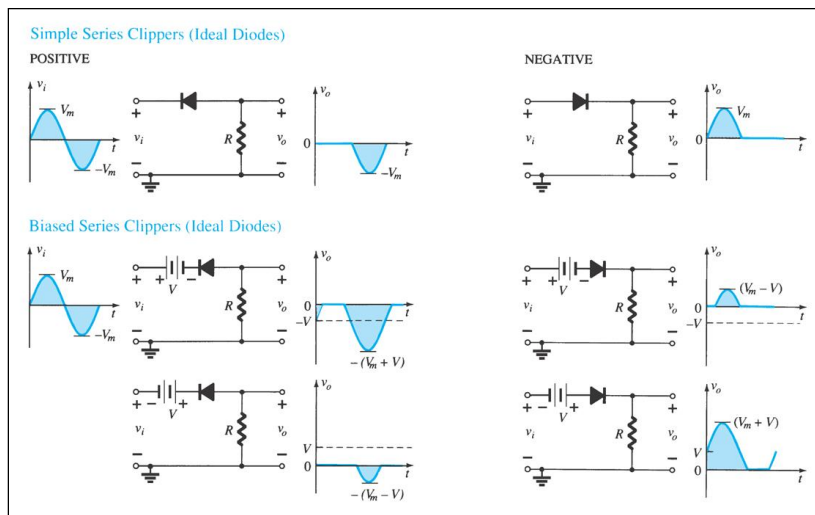

ENEE236 – Analog Electronics

ENEE236 & 241



Analog Electronics

L4 Diode Applications 2
Instructor: Nasser Ismail

Clampers

Function: A Clamper shifts the input waveform up or down (adds a dc offset) while keeping its shape and peak to peak value unchanged.

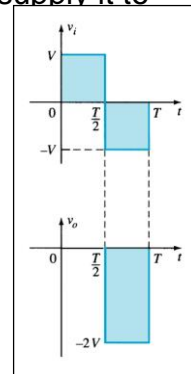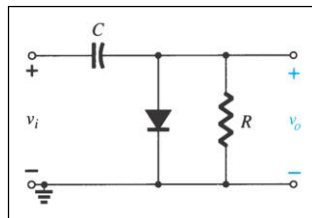It consists of a diode and capacitor (and maybe a series dc source) that can be combined to “clamp” an AC signal to a specific DC level and supply it to the load R





Steps for Clamper Circuit Analysis

- 1) Start analysis by examining the portion of input that will forward bias the diode
- 2) During diode On period, assume that the cap is charged instantaneously to a voltage level defined by surrounding network
- 3) During OFF period, assume the cap holds the established voltage level (i.e. it behaves as constant dc voltage source)
- 4) Consider value and polarity of V_o
- 5) Check that total swing (peak to peak) of output equal swing of input.

ENEE236 – Analog Electronics

Example

Find and sketch $V_o(t)$?

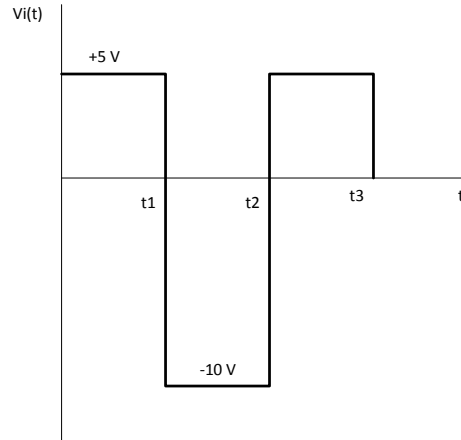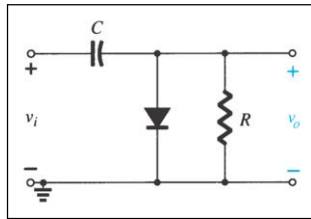

1) For $t < 0$ ($t = 0^-$) $V_C(0^-) = 0$



2) For $t > 0$ ($t = 0^+$) $V_C(0^+) = 0$

$V_i(0^+) = 5V$

$\Rightarrow D1$ is ON and it is replaced by short circuit

3) for $0^+ < t < t_1$ equivalent circuit is \Rightarrow see next page

ENEE236 – Analog Electronics

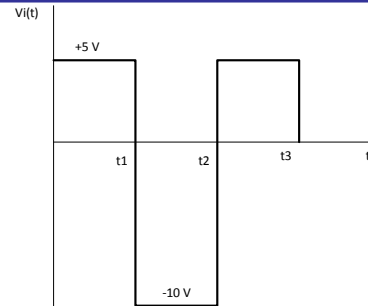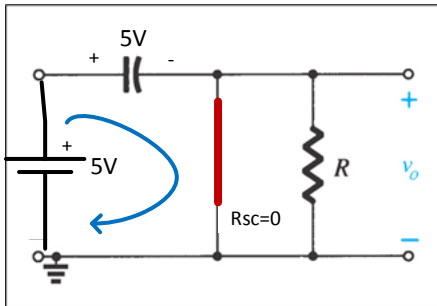

$\Rightarrow D1$ is ON, Cap charges instantously to $+5V$ with shown polarity since $\tau_{\text{charge}} = R_{sc} \cdot C \cong 0$ and $V_o(t) = 0V$

4) for $t_1 < t < t_2$ voltage source reverses polarity, $V_i(t) = -10V$ while Cap keeps its charge $V_c = 5V$ since $\tau_{\text{discharge}} = R \cdot C$ is large

ENEE236 – Analog Electronics

$V_i(t)$

KVL around the loop: $-10 - 5 - V_D(t) = 0$
 $\Rightarrow V_D(t) = -15 \text{ V} < 0, \therefore$ diode is OFF

$V_o(t) = V_D(t) = -15 \text{ V}$

ENEE236 – Analog Electronics



5) for $t_2 < t < t_3$, $V_i(t) = 5\text{V}$
 while $V_c = 5\text{V}$
 $V_D(t) = 5 - 5 = 0$

Diode is OFF and it will remain always off no matter what happens to $V_i(t)$
 $V_o(t) = V_D(t) = V_i(t) - 5$

ENEE236 – Analog Electronics

Example

What happens if the diode was inverted

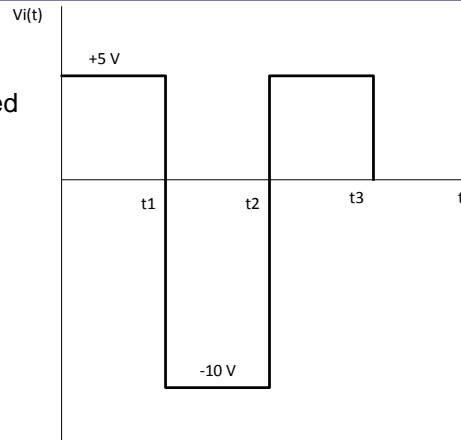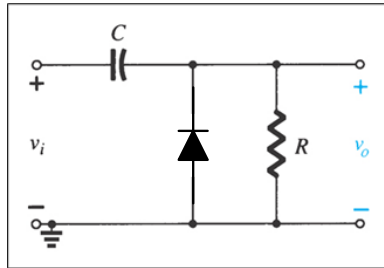



1) Consider $t_1 < t < t_2$ which makes the diode ON

⇒ D is ON and it is replaced by short circuit

$V_o(t) = 0V$

ENEE236 – Analog Electronics

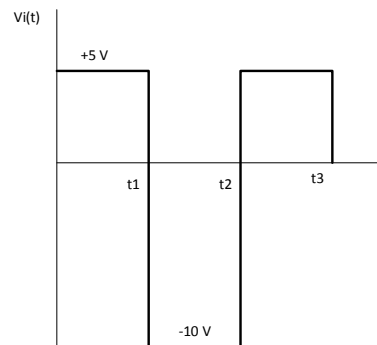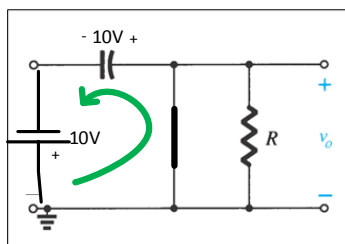Cap is charged to 10V with shown polarity due to diode forward current $V_o(t) = 0V$



2) for $t_2 < t < t_3$ voltage source reverses polarity, $V_i(t) = +5V$ while Cap keeps its charge $V_c = 10V$

ENEE236 – Analog Electronics

$V_i(t)$

KVL around the loop : $10 + 5 + V_D(t) = 0$
 $\Rightarrow V_D(t) = -15 \text{ V} < 0, \therefore$ diode is OFF

$V_o(t) = -V_D(t) = 15 \text{ V}$

ENEE236 – Analog Electronics

Afterwords for any value of the given $V_i(t)$ diode remains OFF and $V_o(t) = V_i(t) + 10$

\therefore the clamper charges a cap and uses this charge to add to the input to shift it up or down (i.e. add dc offset)



Important Note

For Proper Clamping action , $\tau_{discharge}$ must be large enough (at least 10 times the period of the input waveform)

$\tau_{discharge} = R.C > 10(t_1 + t_2)$

ENEE236 – Analog Electronics

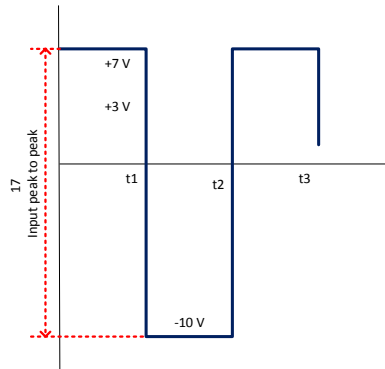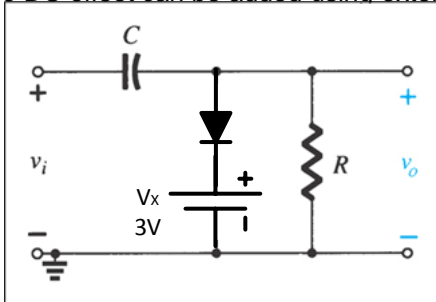More DC offset can be added using external voltage source




1) When $V_i = +7\text{ V}$
 $7 - V_C(t) - V_X = 0$
 $\therefore V_C(t) = 7 - 3 = 4\text{ V}$
 $\Rightarrow V_o(t) = V_X = 3\text{ V}$


2) for $V_i = -10\text{ V}$
 $-10 - 4 - V_D(t) - 3 = 0$
 $\Rightarrow V_D(t) = -17\text{ V} < 0$ and diode is OFF

$\Rightarrow V_o(t) = V_i(t) - V_C(t)$
 $= V_i(t) - 4$
 $= -10 - 4 = -14\text{ V}$

ENEE236 – Analog Electronics

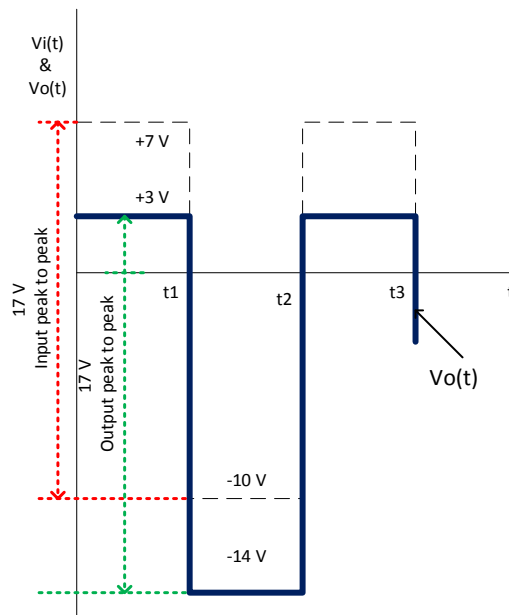



Summary of Clamper Circuits

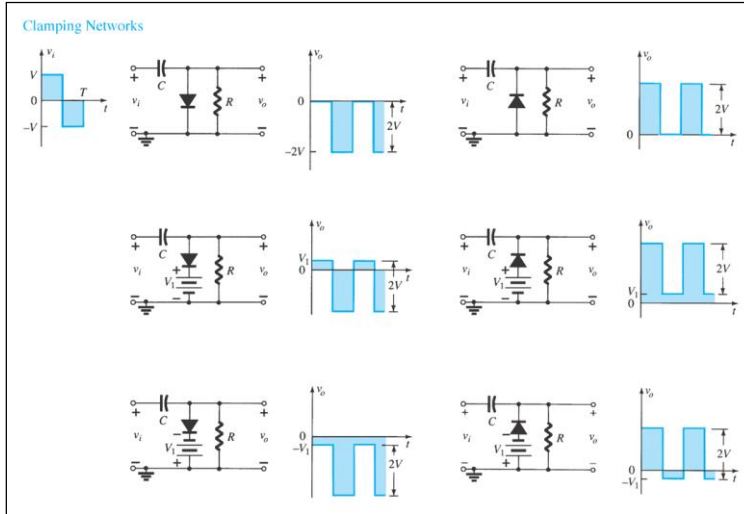

Voltage Multiplier

D_1 , and D_2 are ideal
 $V_{C1}(0^+) = V_{C2}(0^-) = 0$

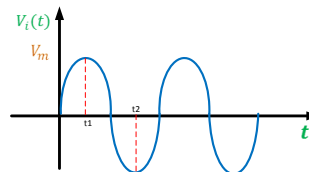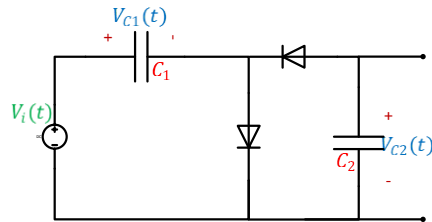- A) at $t=0^+$
 $V_i(0^+) = \text{positive}$
 $V_{C1}(0^+) = V_{C2}(0^+) = 0$
 $\therefore D_1$ on, and D_2 off
- B) in the interval
charge towards V_m
at t_1 ; $V_c(t_1) = V_m$



- C) at $t = t_1^+$
 - $V_{c1}(t_1^+) = V_m$
 - $V_i(t_1^+) < V_m$
 - $\therefore D_1$ is off, and D_2 is on
- D) in the interval $t_2 > t > t_1$
 - C_2 charges toward V_m
 - at $t = t_2$
 - $V_{c2}(t_2) = 2V_m$
 - $V_{c2}(t_2) = -V_i(t_2) + V_m$
 - $V_{c2}(t_2) = V_m + V_m$
 - $V_{c2}(t_2) = 2V_m$
- E) at $t = t_2^+$
 - D_2 is off, D_1 is off
 - $V_{c1}(t_2^+) = V_m$
 - $V_{c2}(t_2^+) = 2V_m$

Practical Applications

Rectifier Circuits

Conversions of AC to DC for DC operated circuits
Battery Charging Circuits

Simple Diode Circuits

Protective Circuits against
Overcurrent
Polarity Reversal
Currents caused by an inductive kick in a relay circuit

Zener Circuits

Overvoltage Protection
Setting Reference Voltages